

ECEN474: (Analog) VLSI Circuit Design

Fall 2011

Lecture 14: Simple OTA





Sebastian Hoyos
Analog & Mixed-Signal Center
Texas A&M University

Agenda

- Simple OTA Parameters

Differential Pair

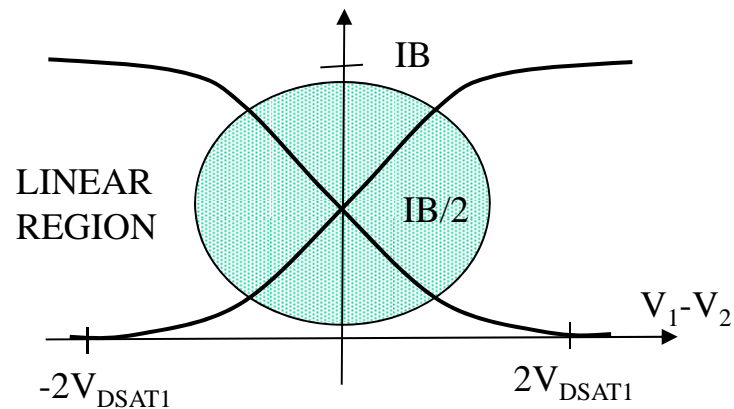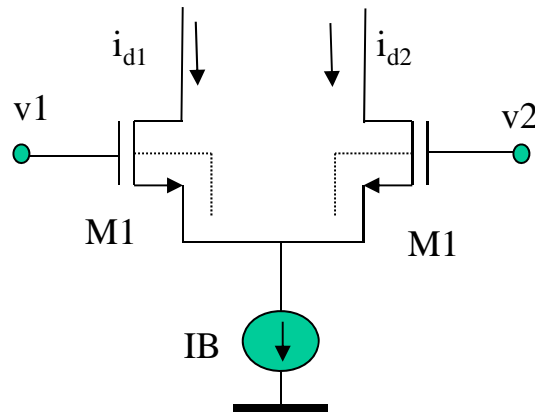

If both transistors are saturated

$$i_{d1} + i_{d2} = IB$$

$$i_{d1} = \frac{\mu_n C_{OX}}{2} \frac{W}{L} (V_{gs1} - V_T)^2$$

$$i_{d2} = \frac{\mu_n C_{OX}}{2} \frac{W}{L} (V_{gs2} - V_T)^2$$


Solving these equations ==>

For Derivation, see Sedra/Smith Ch8

$$i_{d1} = \frac{IB}{2} + \frac{g_{m1}(v_1 - v_2)}{2} \sqrt{1 - \left(\frac{v_1 - v_2}{2V_{DSAT1}} \right)^2}$$

$$i_{d2} = \frac{IB}{2} - \frac{g_{m1}(v_1 - v_2)}{2} \sqrt{1 - \left(\frac{v_1 - v_2}{2V_{DSAT1}} \right)^2}$$

Differential Pair

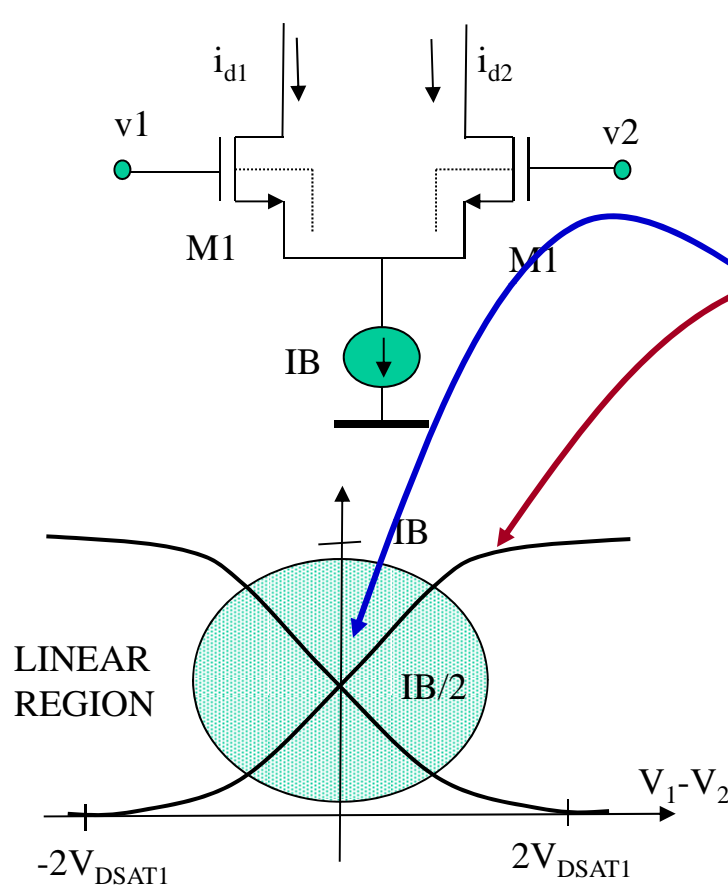

Is a non-linear circuit

$$i_{d1} - i_{d2} = g_{m1} (v_1 - v_2) \sqrt{1 - \left(\frac{v_1 - v_2}{2V_{DSAT1}} \right)^2}$$

Non-linear term


For $v_d = v_1 - v_2 < V_{DSAT1} \implies$

$$i_{d1} - i_{d2} = \sqrt{\mu_n C_{OX} \frac{W}{L} I_B} (v_1 - v_2)$$

Note:


Linear range increases for large V_{DSAT1}
 V_{GS} is also increased (limited by VSS)

Operational Transconductance Amplifier

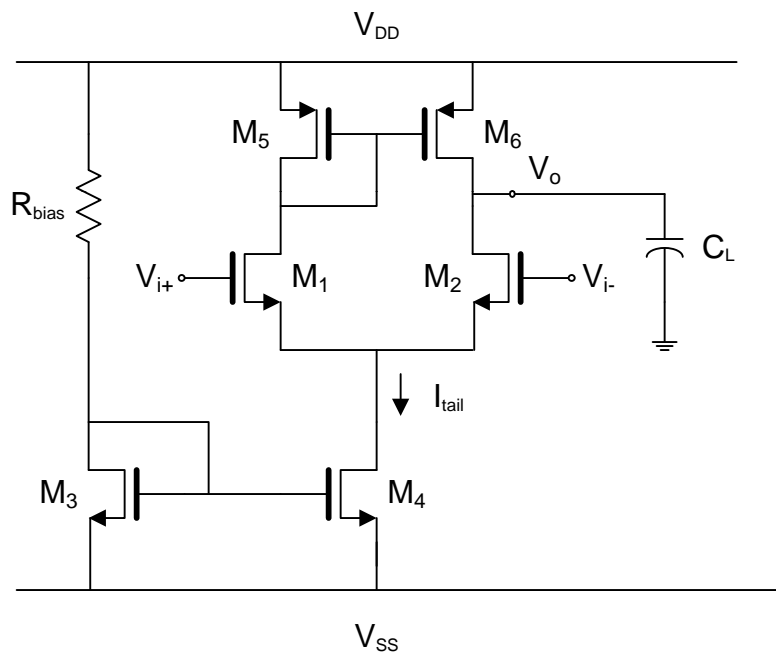

- Important Parameters
 - Differential Gain
 - Gain-Bandwidth Product
 - Common-Mode Input Range
 - Common-Mode Gain
 - Common-Mode Rejection Ratio (CMRR)
 - Power-Supply Rejection Ratio (PSRR)
 - Slew Rate

OTA Differential Gain

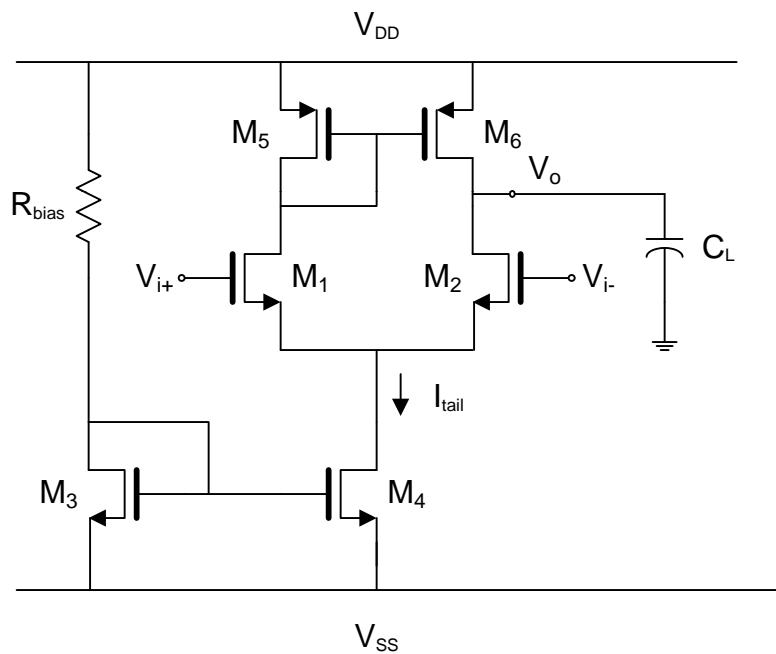

Let $V_{i+} = \frac{v_{id}}{2}$ and $V_{i-} = -\frac{v_{id}}{2}$


$$v_o = -g_{m2}r_{out} \left(-\frac{v_{id}}{2} \right) - \frac{g_{m1}}{g_{m5}} \left(-g_{m5}r_{out} \right) \left(\frac{v_{id}}{2} \right)$$

By design $g_{m1} = g_{m2}$ and $g_{m5} = g_{m6}$

$$v_o = g_{m1}r_{out}v_{id}$$

$$A_{DM} = \frac{v_o}{v_{id}} = g_{m1}r_{out} = \frac{g_{m1}}{g_{o6} + g_{o2}}$$

OTA Gain-Bandwidth Product (GBW)

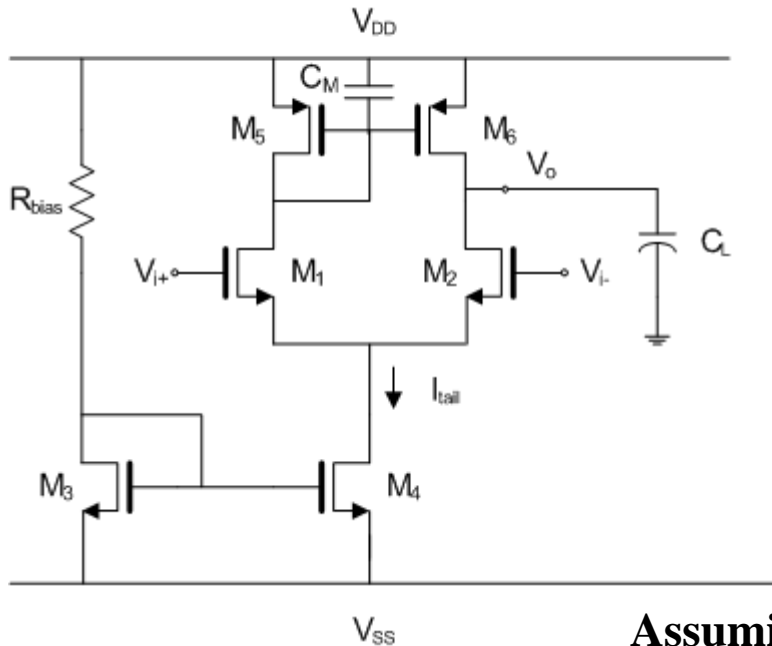


$$A_{DM} = \frac{g_{m1}}{g_{o6} + g_{o2}}$$

The circuit will have 2 poles


ω_{po} at the output node and ω_{pm} at the "mirror" node

$$\omega_{po} \approx \frac{g_{o6} + g_{o2}}{C_L}, \quad \omega_{pm} \approx \frac{g_{m5}}{C_M}$$

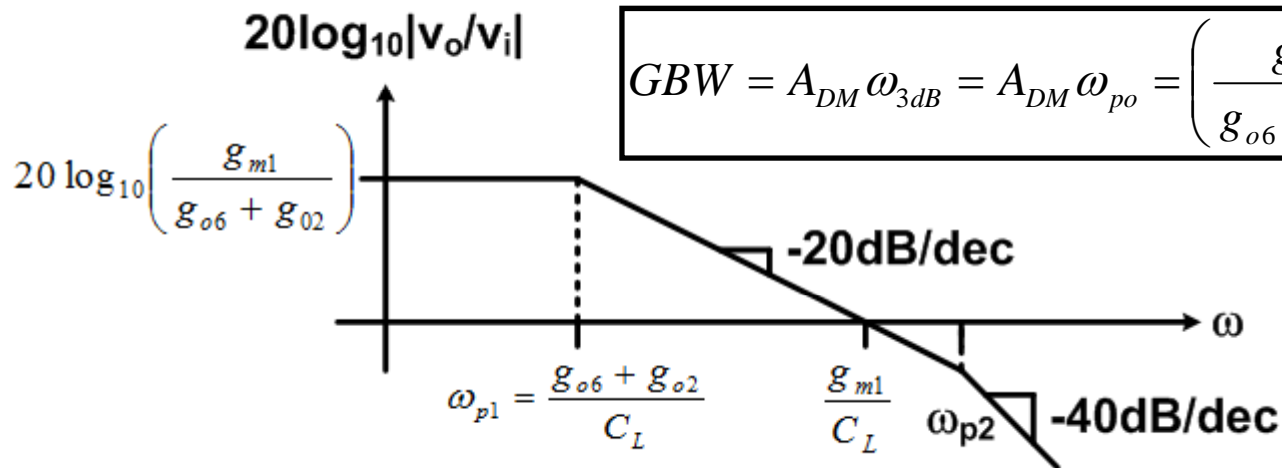Assuming the poles are widely spaced and ω_{po} dominates



OTA Common-Mode Input Range

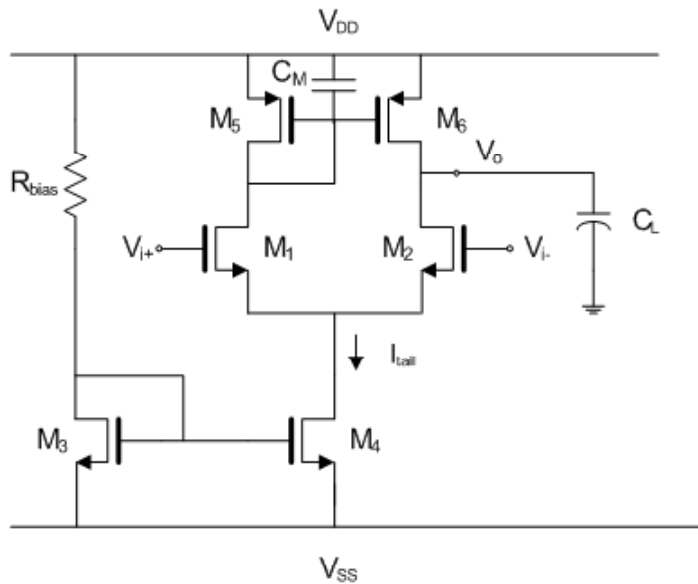

- Common-mode input range set by transistor saturation conditions

- Low-end set by tail current source saturation

$$V_{icm} \geq V_{SS} + V_{DSAT4} + V_{GS1} = V_{SS} + \sqrt{\frac{2I_{tail}}{\mu_n C_{ox} \frac{W}{L_4}}} + \sqrt{\frac{I_{tail}}{\mu_n C_{ox} \frac{W}{L_1}}} + V_{Tn1}$$


- High-end set by differential pair saturation

$$V_{icm} \leq V_{ocm} + V_{T1} = V_{DD} - V_{GS5} + V_{T1} = V_{DD} - \left(\sqrt{\frac{I_{tail}}{\mu_p C_{ox} \frac{W}{L_5}}} + |V_{Tp5}| \right) + V_{Tn1}$$

$$V_{SS} + \sqrt{\frac{2I_{tail}}{\mu_n C_{ox} \frac{W}{L_4}}} + \sqrt{\frac{I_{tail}}{\mu_n C_{ox} \frac{W}{L_1}}} + V_{Tn1} \leq V_{icm} \leq V_{DD} - \left(\sqrt{\frac{I_{tail}}{\mu_p C_{ox} \frac{W}{L_5}}} + |V_{Tp5}| \right) + V_{Tn1}$$

OTA Common-Mode Gain


[Sedra]

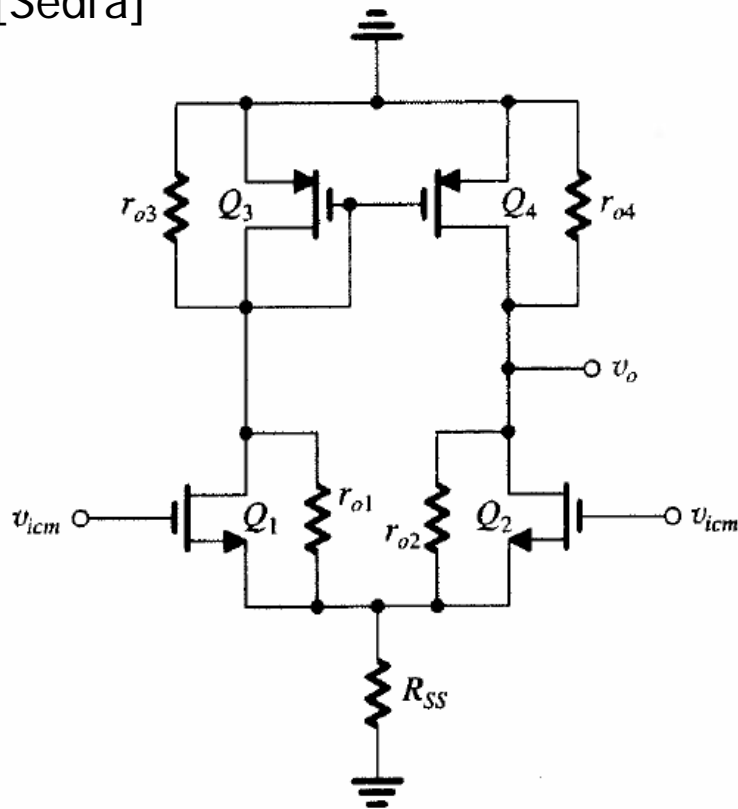

- Ideally, common-mode perturbations are suppressed by the differential amplifier, i.e. $A_{cm} = 0$
- Finite common-mode gain exists due to amplifier asymmetries and finite tail current source impedance
- Note transistor numbers are different from previous slides, as I borrow figures from Sedra/Smith text

OTA Common-Mode Gain

[Sedra]

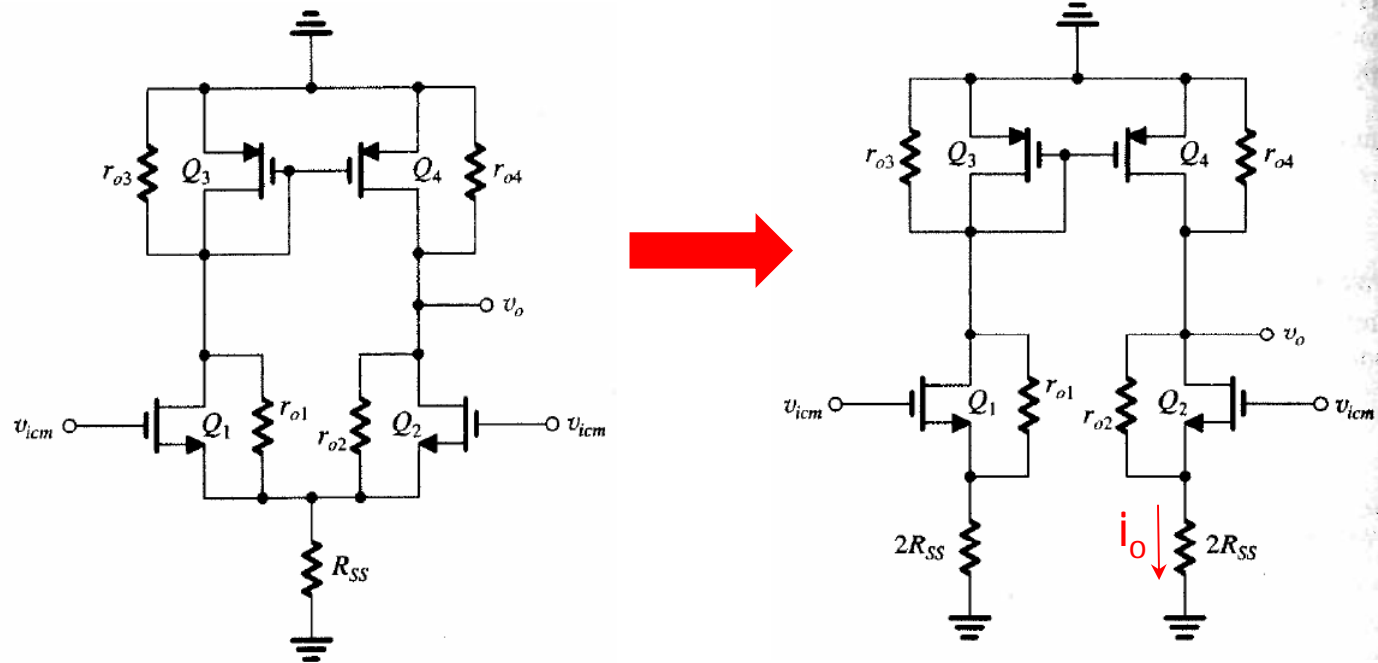

$$v_s = v_{icm} \frac{(2R_{SS} \parallel r_{o1})}{(2R_{SS} \parallel r_{o1}) + (1/g_{m1})}$$


$$\approx v_{icm}$$

$$i_o = \frac{v_{icm}}{2R_{SS}}$$

$$G_{mcm} \equiv \frac{i_o}{v_{icm}} = \frac{1}{2R_{SS}}$$

OTA Common-Mode Gain


[Sedra]

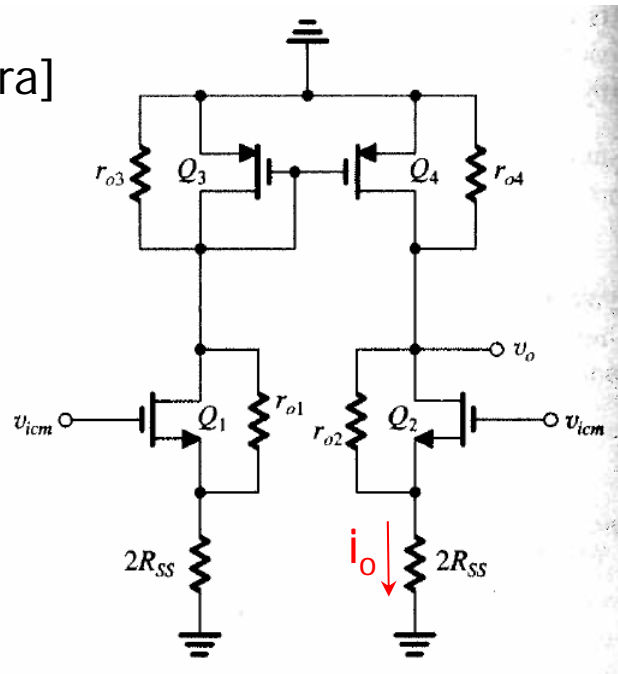

$$G_{mcm} \equiv \frac{i_o}{v_{icm}} = \frac{1}{2R_{SS}}$$

$$R_{o1} = 2R_{SS} + r_{o1} + (g_{m1}r_{o1})(2R_{SS})$$

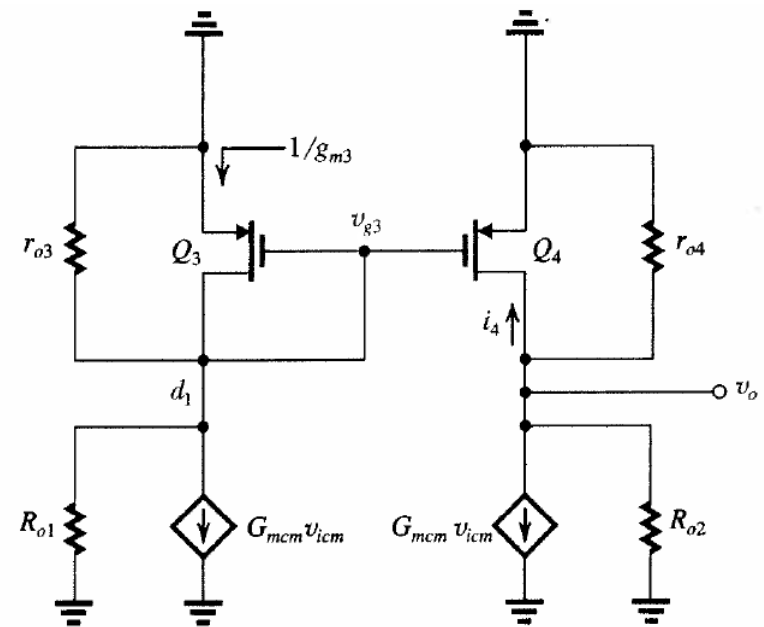
$$R_{o2} = 2R_{SS} + r_{o2} + (g_{m2}r_{o2})(2R_{SS})$$



$$v_{g3} = -G_{mcm}v_{icm} \left(R_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \right)$$

$$i_4 = -g_{m4}G_{mcm}v_{icm} \left(R_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \right)$$

OTA Common-Mode Gain

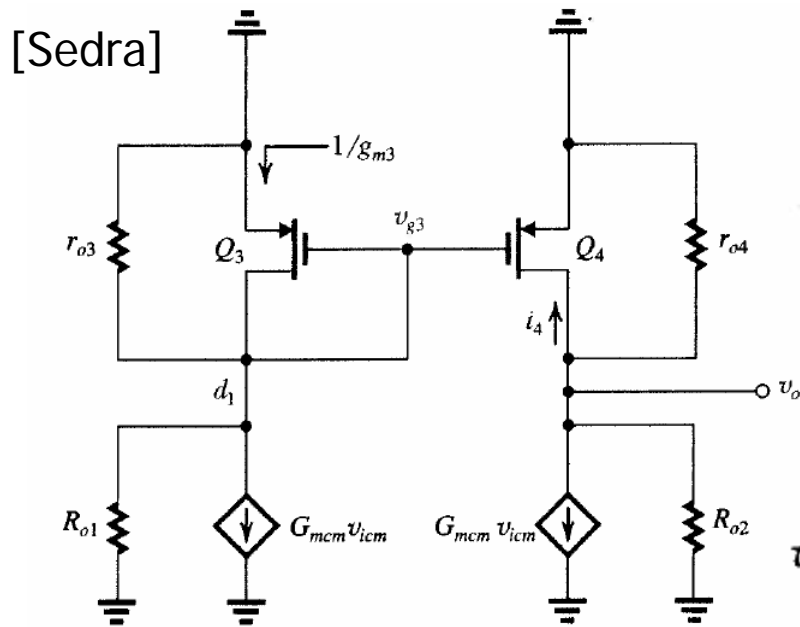

$$i_4 = -g_{m4} G_{mcm} v_{icm} \left(R_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \right)$$

KCL at v_o

$$G_{mcm} v_{icm} + i_4 + \frac{v_o}{R_{o2}} + \frac{v_o}{r_{o4}} = 0$$


$$v_o = -v_{icm} \frac{r_{o4} \parallel R_{o2}}{2R_{SS}} \left[1 - g_{m4} \left(R_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \right) \right]$$

Since $R_{o2} \gg r_{o4}$ and $R_{o1} \gg r_{o3}$ and $g_{m3} = g_{m4}$

$$A_{cm} \equiv \frac{v_o}{v_{icm}} \approx -\frac{r_{o4}}{2R_{SS}} \frac{1}{1 + g_{m3} r_{o3}}$$

$$A_{cm} \approx -\frac{1}{2g_{m3} R_{SS}}$$

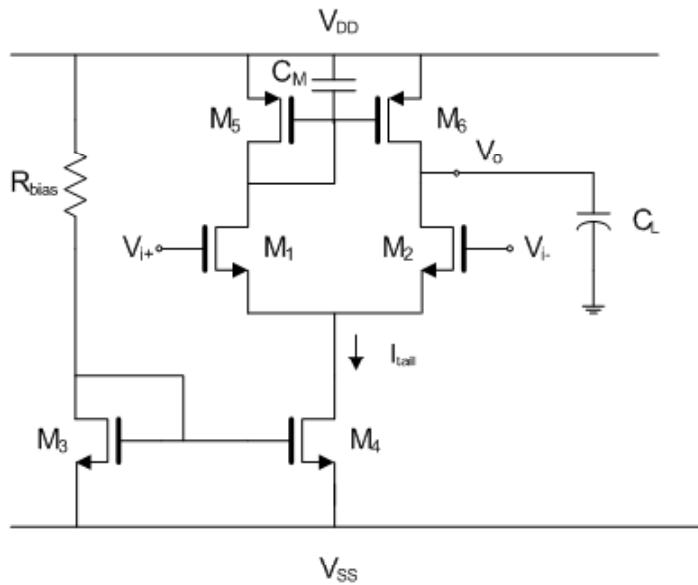OTA Common-Mode Gain & Rejection Ratio (CMRR)



$$A_{cm} = \frac{v_o}{v_{CM}} \approx -\frac{1}{2g_{m6}r_{o4}}$$

- To improve (lower) common-mode gain, we need a high tail current impedance


- An amplifier figure-of-merit is the common-mode rejection ratio (CMRR)

$$CMRR = 20 \log_{10} \left| \frac{A_{dm}}{A_{cm}} \right|$$

$$CMRR = 20 \log_{10} \left| \frac{A_{dm}}{A_{cm}} \right| = 20 \log_{10} \left| \left(\frac{g_{m1}}{g_{o6} + g_{o2}} \right) (-2g_{m6}r_{o4}) \right|$$

OTA Power-Supply Rejection Ratio (PSRR)

[Razavi]

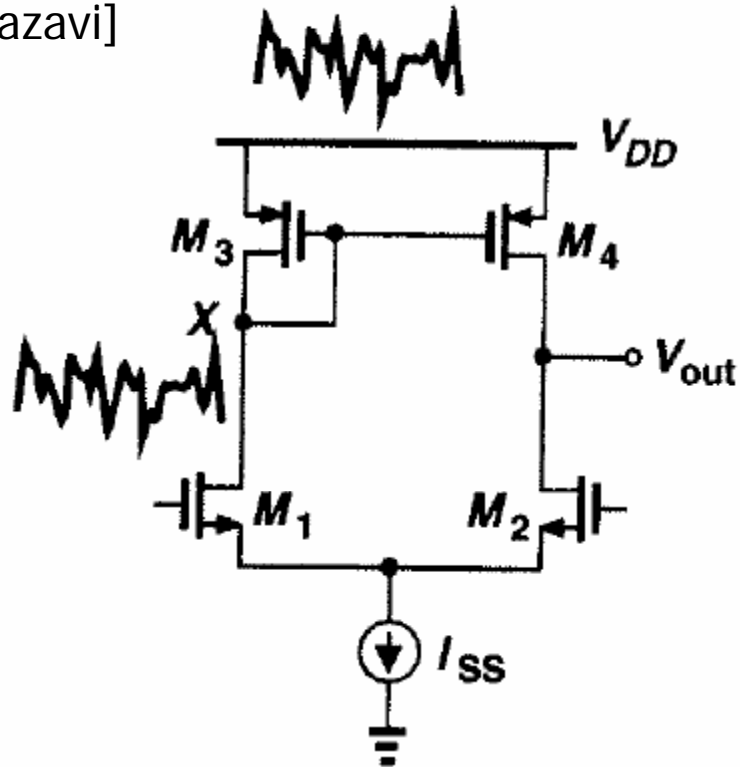

$$PSRR^+ = 20 \cdot \log_{10} \left(\left| \frac{A_{dm}}{v_o/v_{DD}} \right| \right)$$

$$PSRR^- = 20 \cdot \log_{10} \left(\left| \frac{A_{dm}}{v_o/v_{SS}} \right| \right)$$



$$A_{dm} = \frac{g_{m1}}{g_{o2} + g_{o4}}$$

$$A_{vdd} \approx 1$$

$$PSRR^+ \approx \frac{g_{m1}}{g_{o2} + g_{o4}}$$


OTA Slew Rate

[Razavi]

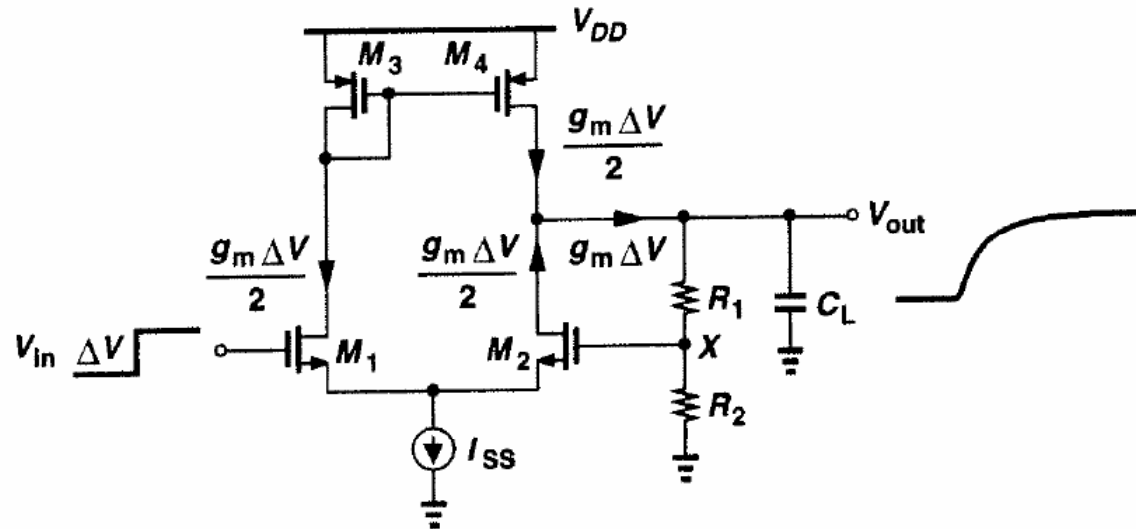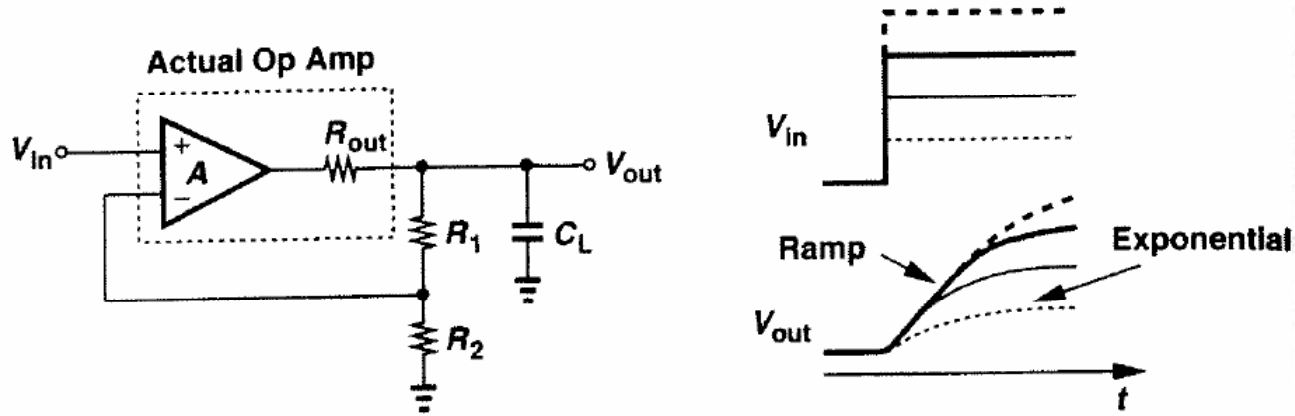


OTA Slew Rate

[Razavi]

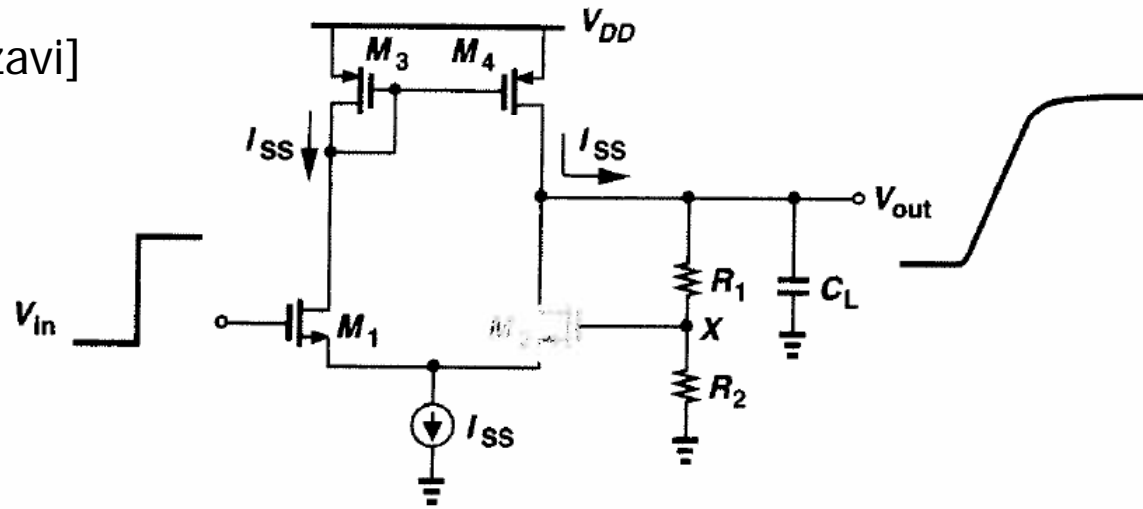
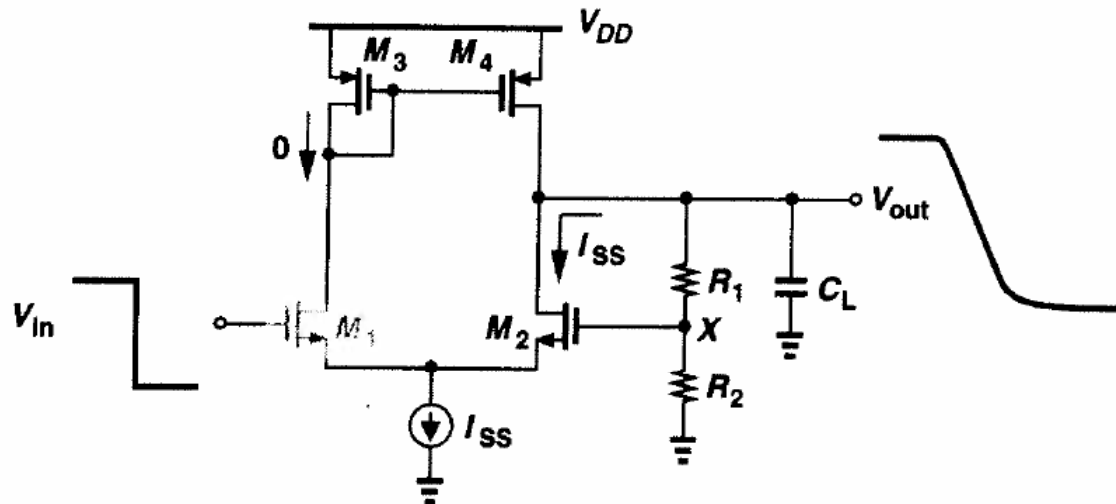
$$\text{Slew Rate} = \frac{I_{SS}}{C_L}$$



Next Time

- Other OTA Circuits