

ECEN474: (Analog) VLSI Circuit Design

Fall 2011

Lecture 18: Feedback & Stability



Sebastian Hoyos

Analog & Mixed-Signal Center
Texas A&M University

Agenda



- Feedback in opamp circuits
- Stability Considerations
 - Nyquist Criteria
 - Phase & Gain Margin

If the OPAMP is not precise, how we can design accurate systems?

Answer is FEEDBACK!!!

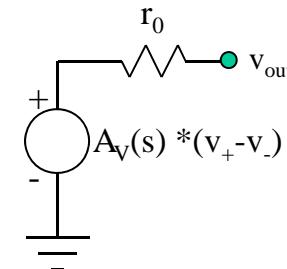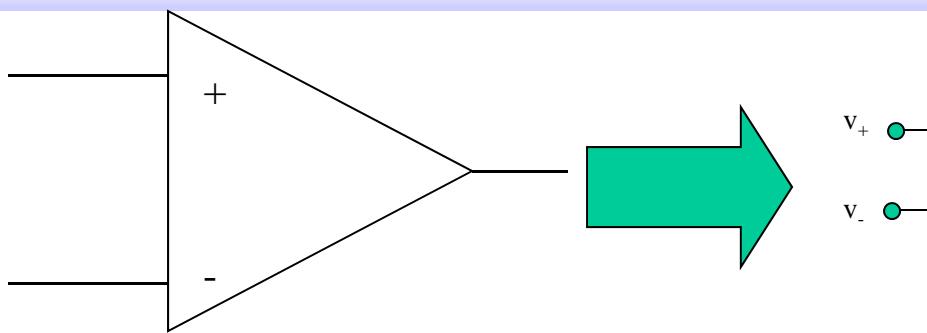Examples of our daily life


- Can you shave yourself closing your eyes?
 - Can you drive your car closing your eyes?
 - Can you adjust the supply voltages without a voltage indicator?
 - Can you measure (without any equipment) the magnetic field generated by your cellular phone?
 - Can you control properly your daily activities without feedback?
-
- If you measure the output at the time you apply the stimuli you can better control the system!!**



$$A_V \equiv \frac{A_{VDC}}{1 + \frac{s}{\omega_p}}$$

$$GBW = A_{VDC} * \omega_p \equiv \frac{g_m}{C_M}$$


$$R_{out} = r_0$$

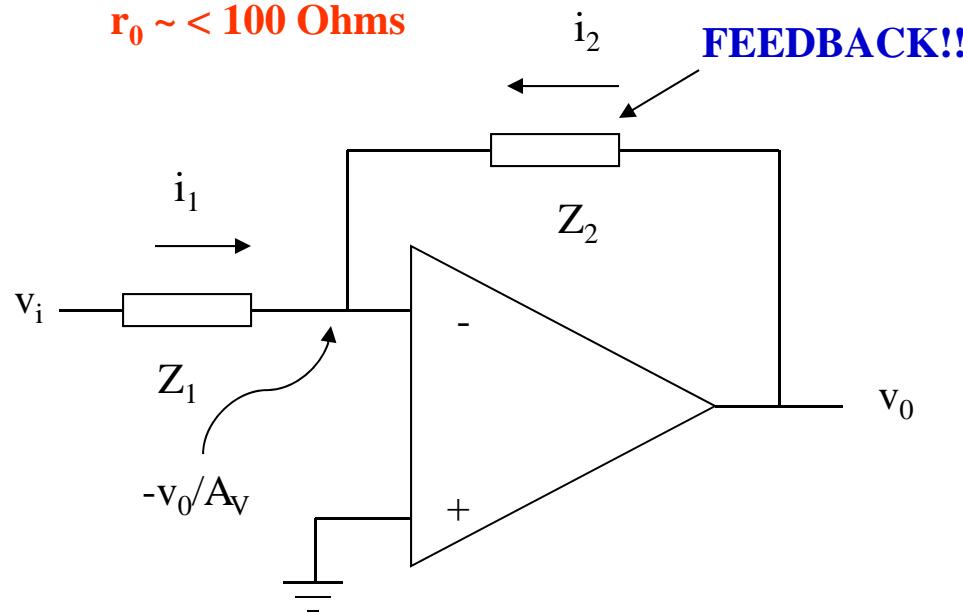

If $A_V \sim \infty$ then
 $v_- = 0$ VIRTUAL GROUND

$$i_1 = -i_2$$

$$\frac{v_i}{Z_1} = -\frac{v_o}{Z_2} \quad \frac{v_o}{v_i} = -\frac{Z_2}{Z_1}$$

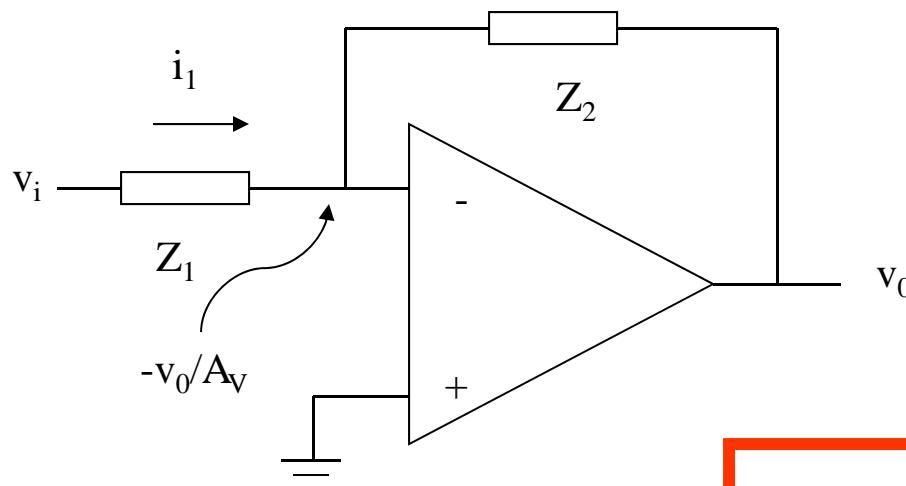i_2 

If A_V is finite then $v_- \neq 0$

$$i_1 = -i_2 \quad \text{if } Z_{in} = \infty$$


or

$$(v_i - (-v_0/A_V))Y_1 = (v_0 - (-v_0/A_V))Y_2$$

$$A_V = \frac{A_{VDC}}{1 + \frac{s}{\omega_P}}$$


$$R_{out} = 0 \quad \text{and} \quad Z_{in} = \infty$$
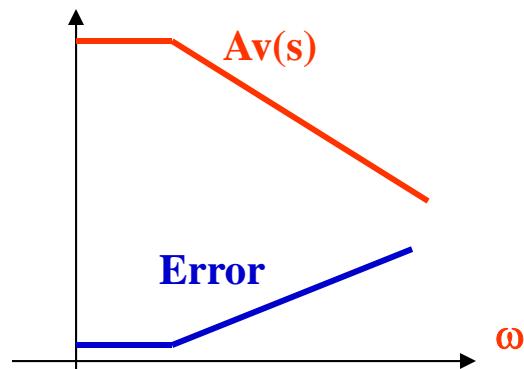
$$\frac{v_0}{v_i} = -\frac{Y_1}{Y_2} \left[\frac{1}{1 + \frac{1}{A_V} \left(1 + \frac{Y_1}{Y_2} \right)} \right] = -\frac{Z_2}{Z_1} \left[\frac{1}{1 + \frac{1}{A_V} \left(1 + \frac{Z_2}{Z_1} \right)} \right]$$



Using the approximation $\frac{1}{1+x} \approx 1-x$ for small x
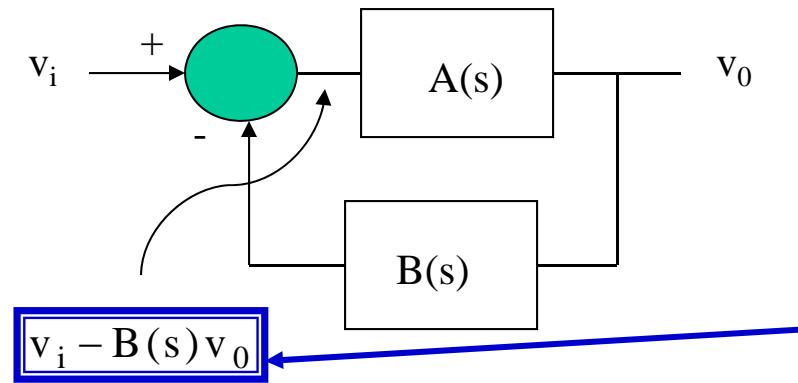
$$\text{Error} = -\frac{1}{A_V} \left(1 + \frac{Z_2}{Z_1} \right) = -\frac{1 + \frac{s}{\omega_P}}{A_{DC}} \left(1 + \frac{Z_2}{Z_1} \right)$$



FEEDBACK:

- If you measure the output at the time you apply the stimuli you can better control the system!!

Definitions:

A(s): Amplifier gain (very large but not very well controlled)


B(s): Feedback Factor (Very well controlled)

T(s)=A(s)B(s): Loop Gain (Extremely important parameter!!)

Applying **Mason Rule:**

$$\frac{v_o}{v_i} = \frac{\text{Direct trajectory}}{1 - \text{loop gain}} = \frac{A(s)}{1 - (-T(s))} = \frac{A(s)}{1 + A(s)B(s)}$$

Feedback Configuration

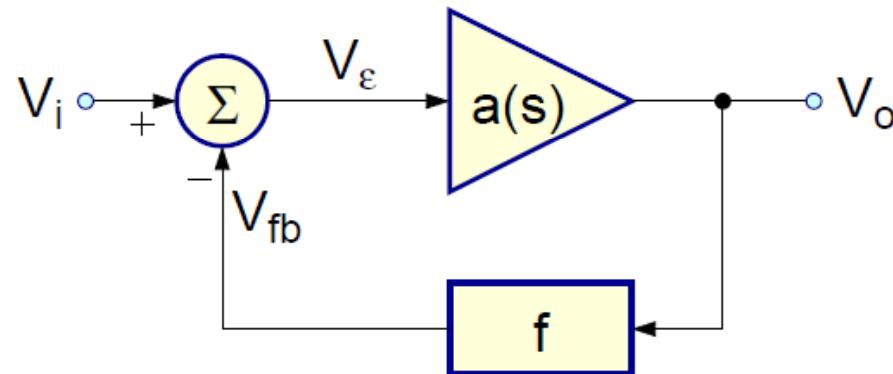

[Karsilayan]


Here $f = \text{feedback factor}$ ($B(s)$ in previous slides)

$$a(s) = \frac{V_o}{V_\varepsilon}(s) = \frac{a_o}{1 - \frac{s}{p_1}}$$

$$A_{CL}(s) = \frac{V_o}{V_i}(s) = \frac{a(s)}{1 + a(s)f} = \frac{\frac{a_o}{1 + a_o f}}{1 - \frac{s}{(1 + a_o f)p_1}}$$

Gain-Bandwidth

[Karsilayan]

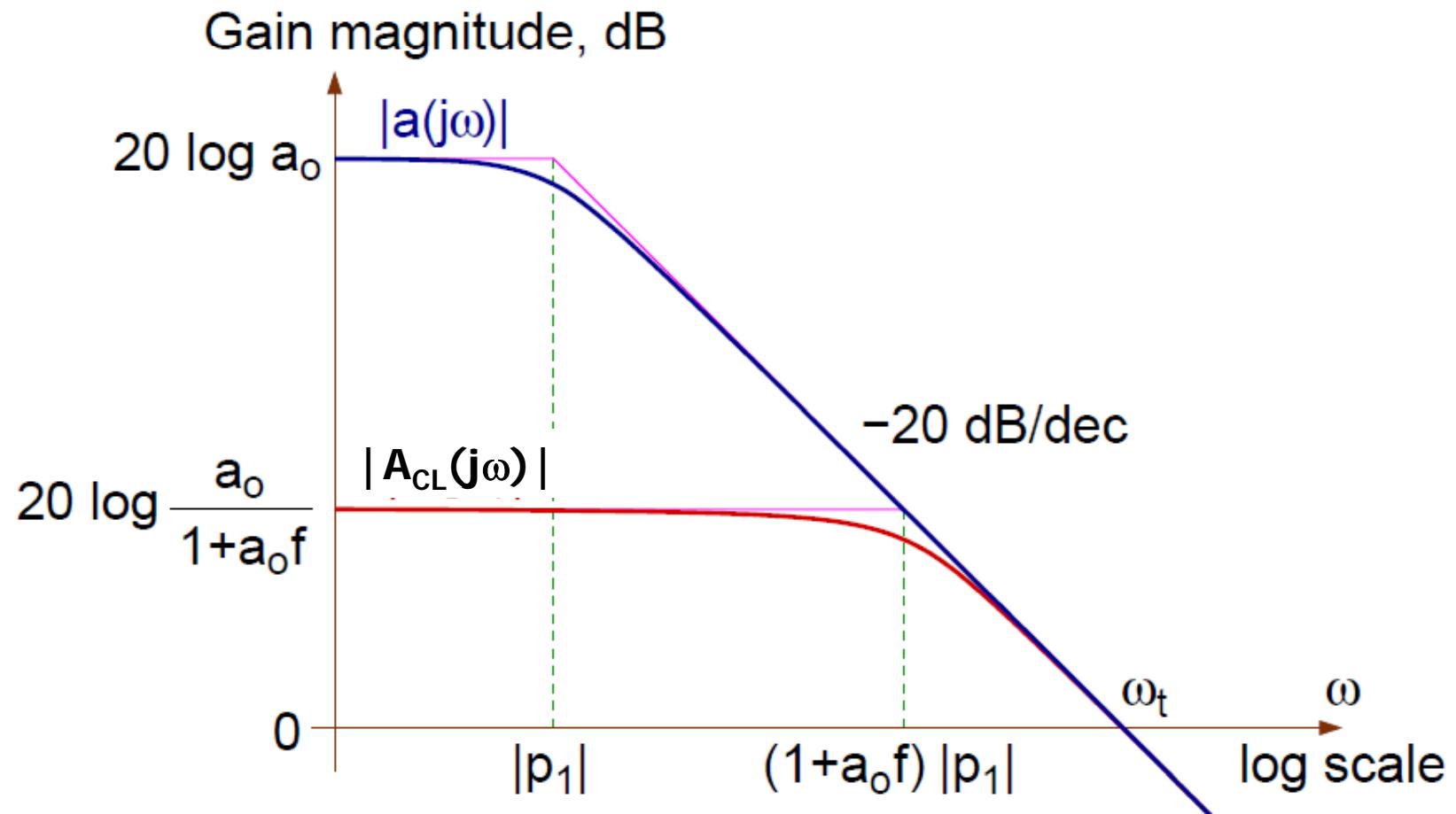

Instability and the Nyquist Criterion

[Karsilayan]

Transfer function of a 3-pole amplifier:

$$a(s) = \frac{a_o}{\left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right)\left(1 - \frac{s}{p_3}\right)}$$

Nyquist criterion for stability of the amplifier:


Consider a feedback amplifier with a stable $T(s)$. If the Nyquist plot of $T(j\omega)$ encircles the point (-1,0), the feedback amplifier is unstable.

Recall $T(s)$ is the loop gain

$$T(s) = A(s)B(s) = a(s)f$$


Magnitude & Phase

3-pole amplifier

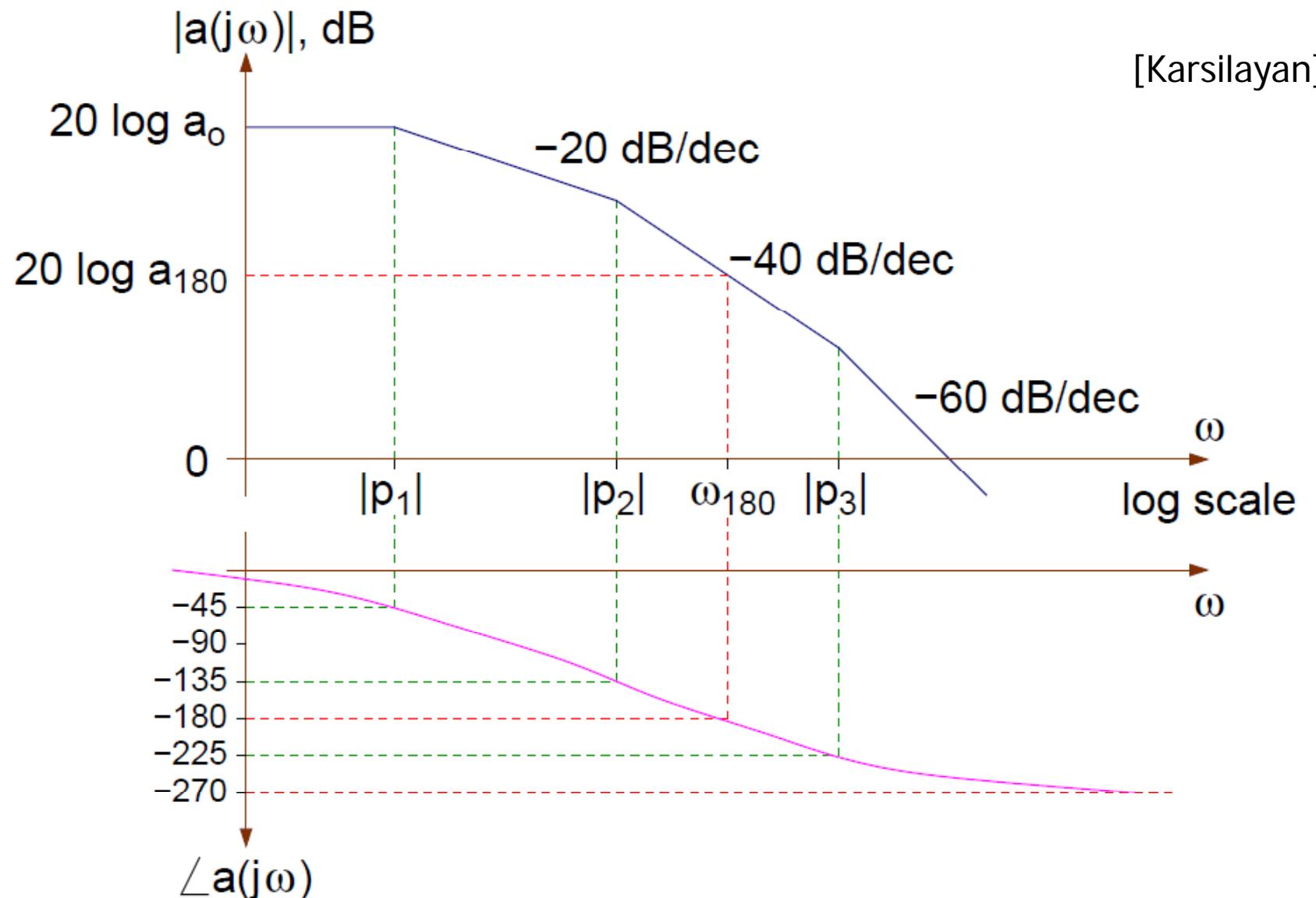


Magnitude & Phase

$$T(s) = a(s)f_1$$

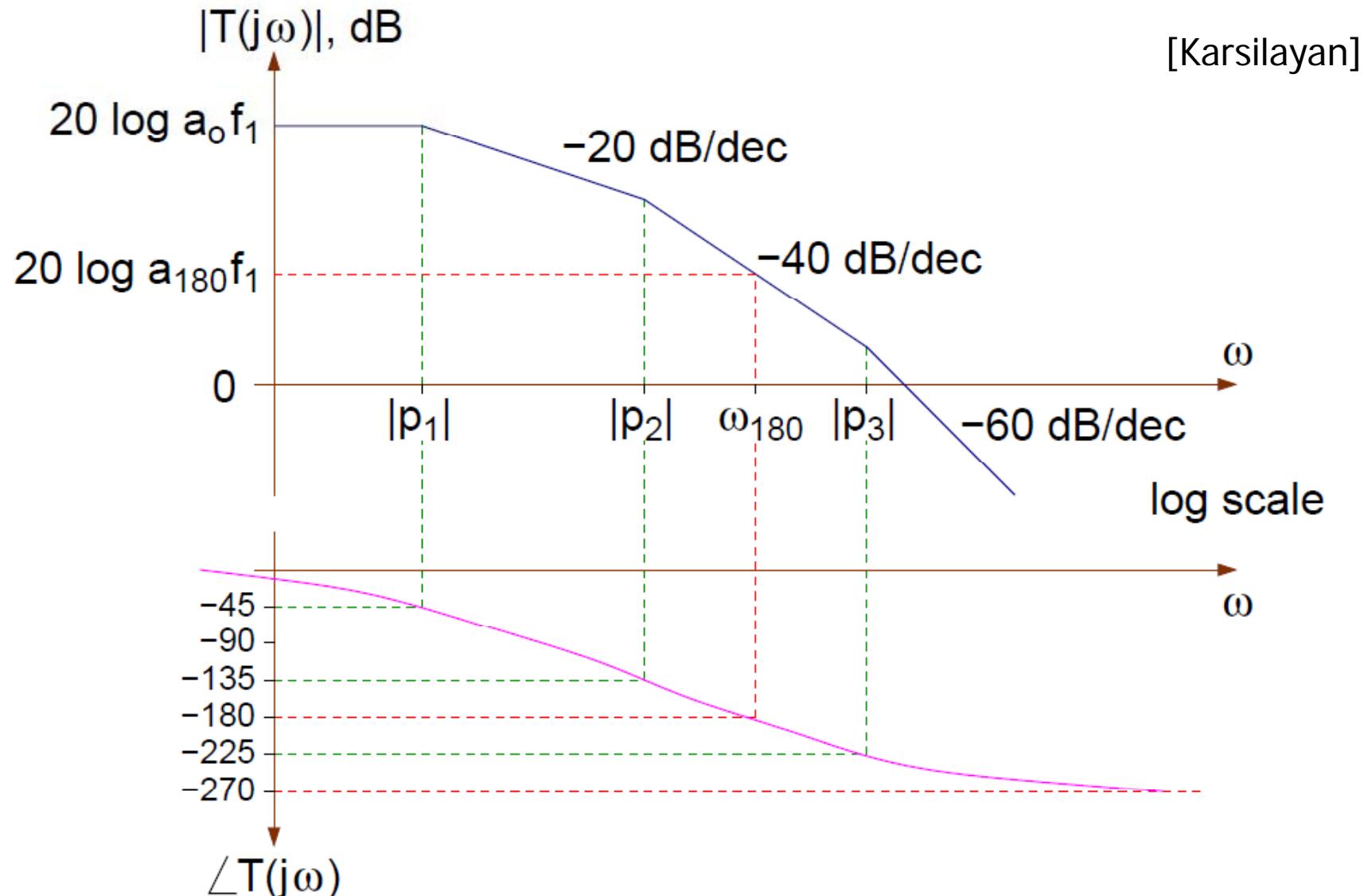


Nyquist Plot

$$T(s) = a(s)f_1$$

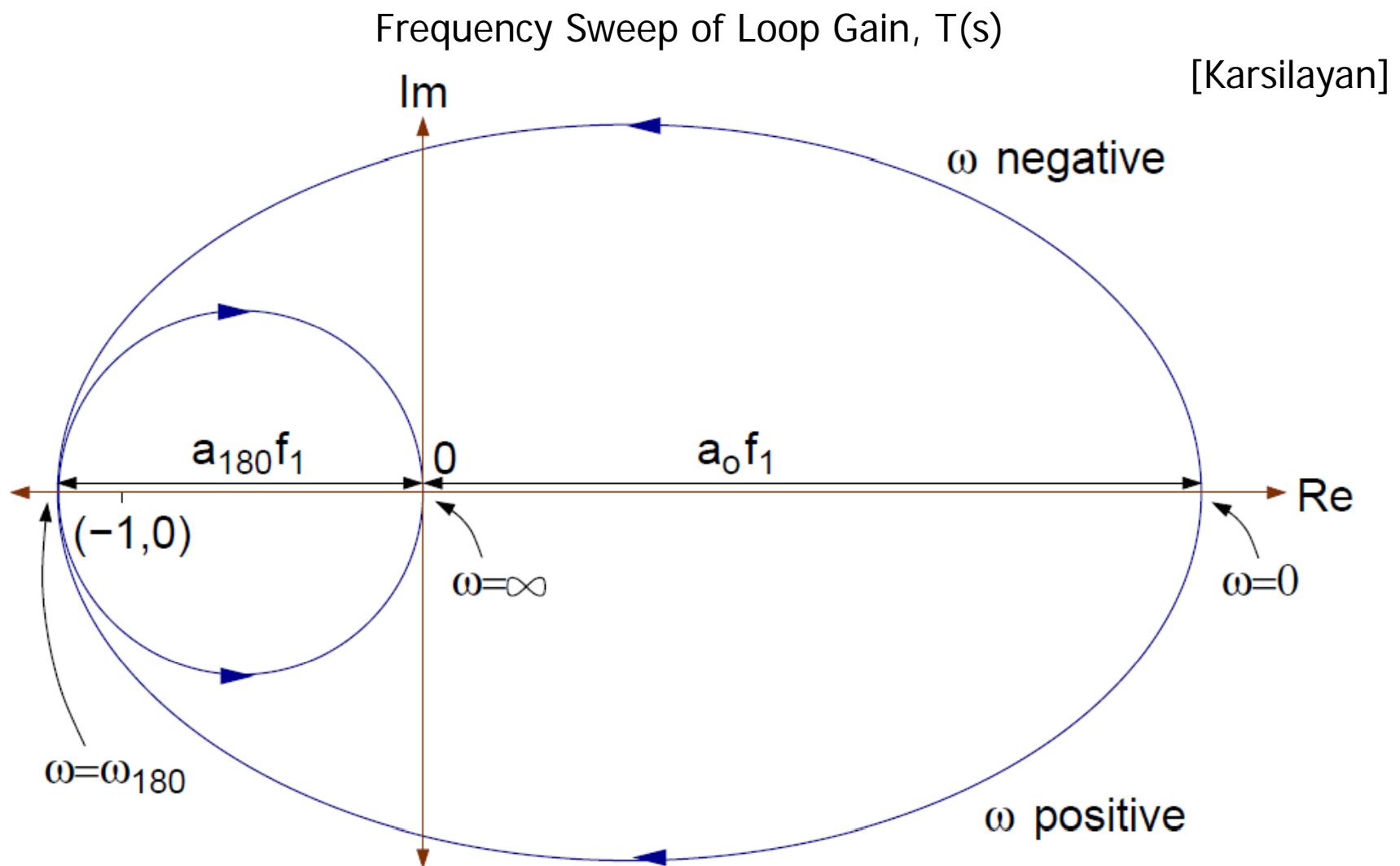

Magnitude & Phase


$$T(s) = a(s)f_2$$

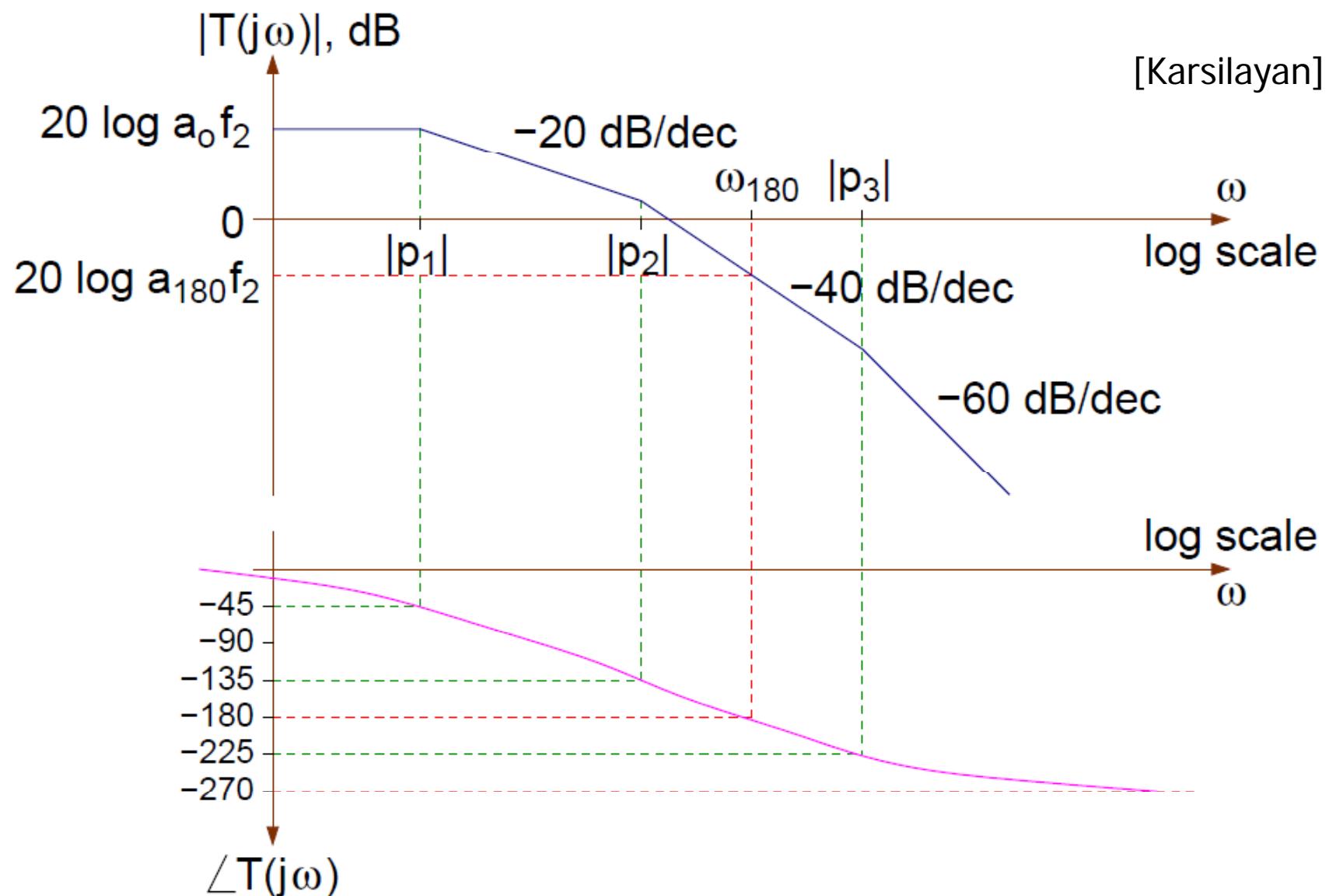


Nyquist Plot

$$T(s) = a(s)f_2$$

[Karsilayan]

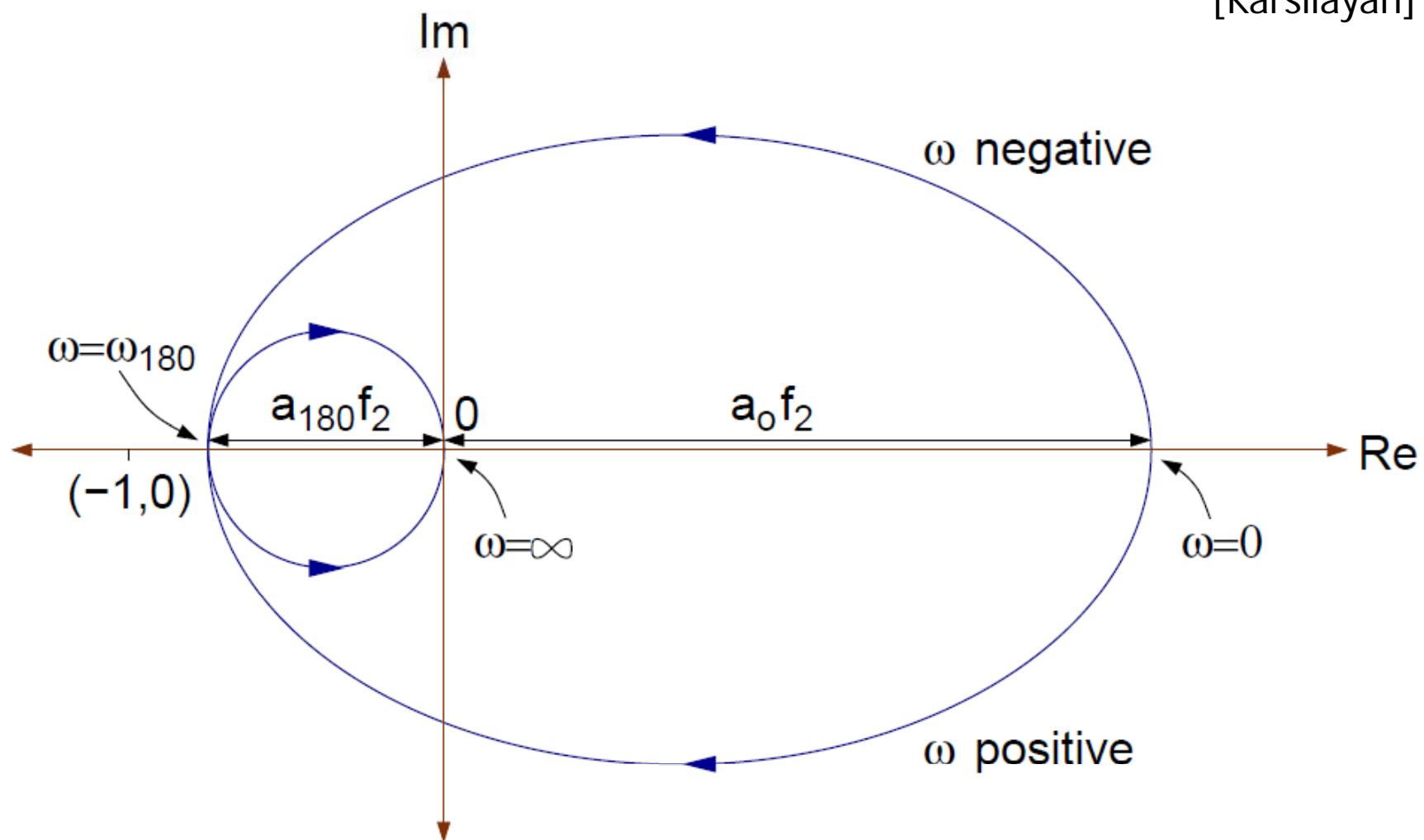

Gain & Phase Margin

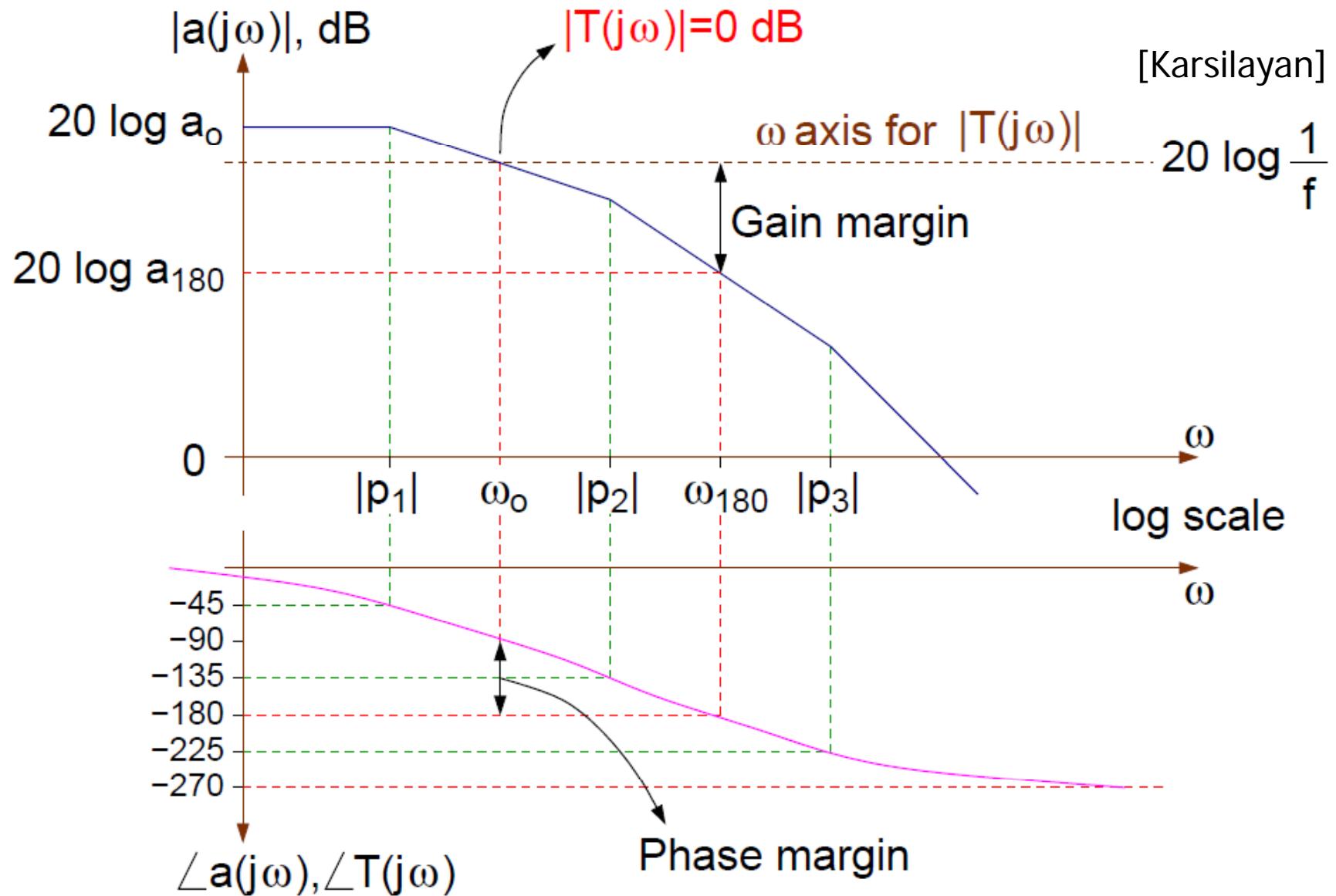

Stability Criteria

Nyquist:

$$|\mathbf{T}(j\omega_{180})| = a_{180}f < 1 \Rightarrow \text{Stable}$$

[Karsilayan]

Gain Margin (**GM**):

$$GM = 20 \log \frac{1}{|\mathbf{T}(j\omega_{180})|} = -20 \log |\mathbf{T}(j\omega_{180})|$$

$$GM > 0 \Rightarrow \text{Stable}$$

Phase Margin (**PM**):

$$PM = 180^\circ + \angle \mathbf{T}(j\omega_0)$$

$$PM > 0 \Rightarrow \text{Stable}$$

Phase Margin

[Karsilayan]

$$|\mathbf{T}(j\omega_0)| = 1 \Rightarrow |a(j\omega_0)|f = 1 \Rightarrow |a(j\omega_0)| = \frac{1}{f}$$

$$PM = 45^\circ \Rightarrow \angle T(j\omega_0) = -135^\circ, A_{CL}(j\omega_0) = \frac{a(j\omega_0)}{1 + T(j\omega_0)}$$

$$A_{CL}(j\omega_0) = \frac{a(j\omega_0)}{1 + e^{-j135^\circ}} = \frac{a(j\omega_0)}{1 - 0.7 - 0.7j}$$

$$|A_{CL}(j\omega_0)| = \frac{|a(j\omega_0)|}{|0.3 - 0.7j|} = \frac{1}{0.76f} = \frac{1.3}{f}$$


$$PM = 30^\circ \Rightarrow \angle T(j\omega_0) = -150^\circ, |A_{CL}(j\omega_0)| = 1.92/f$$

$$PM = 60^\circ \Rightarrow \angle T(j\omega_0) = -120^\circ, |A_{CL}(j\omega_0)| = 1/f$$

$$PM = 90^\circ \Rightarrow \angle T(j\omega_0) = -90^\circ, |A_{CL}(j\omega_0)| = 0.7/f$$

Closed-Loop Frequency Response


[Karsilayan]

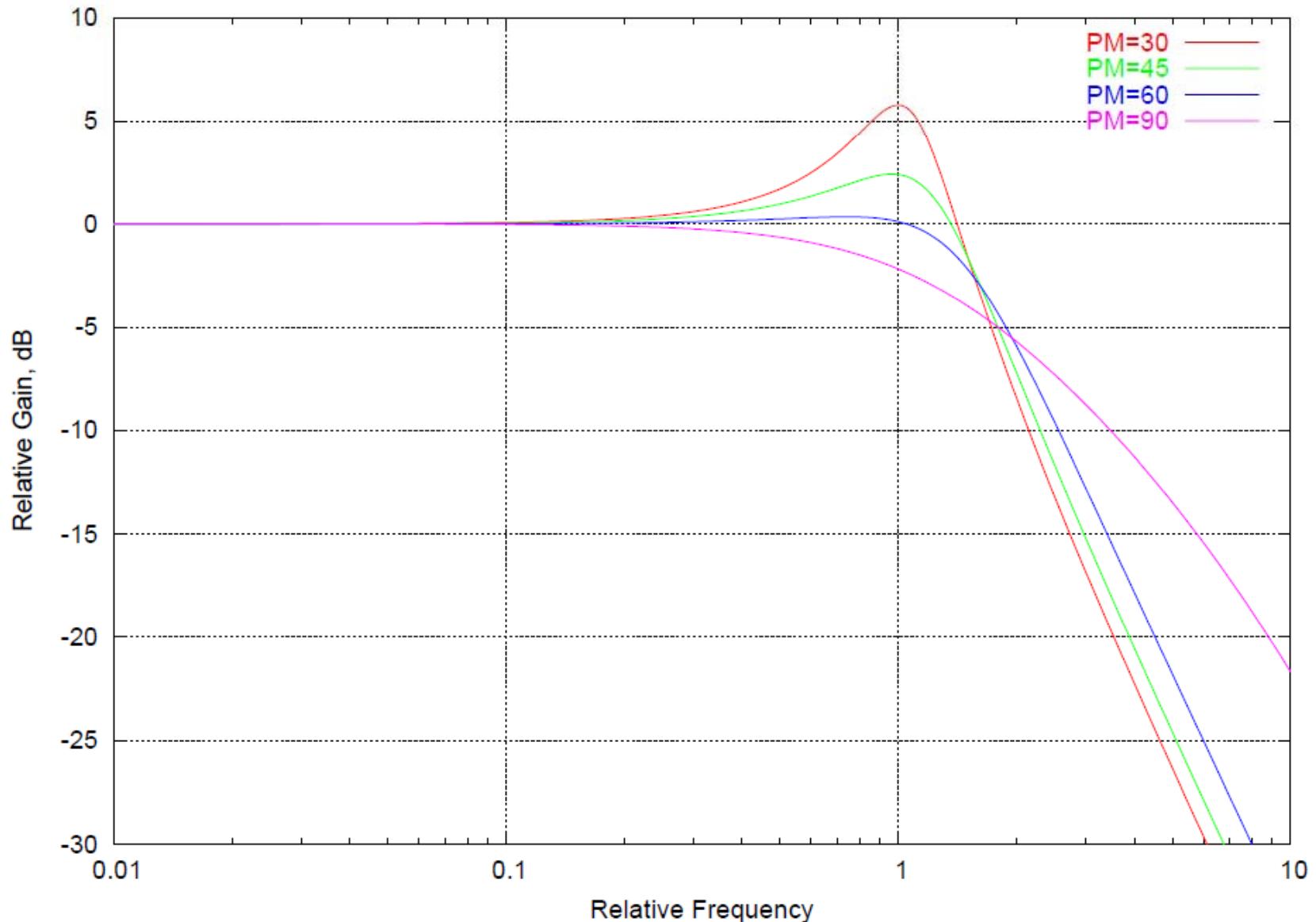


Closed-Loop Step Response

[Karsilayan]


PM = 30°

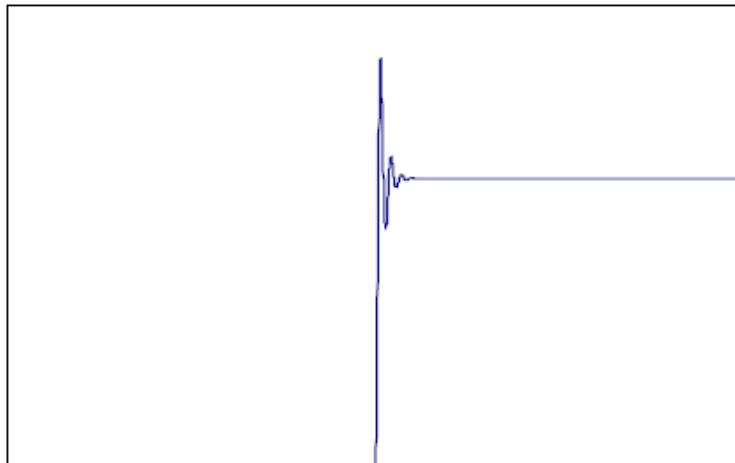


PM = 45°

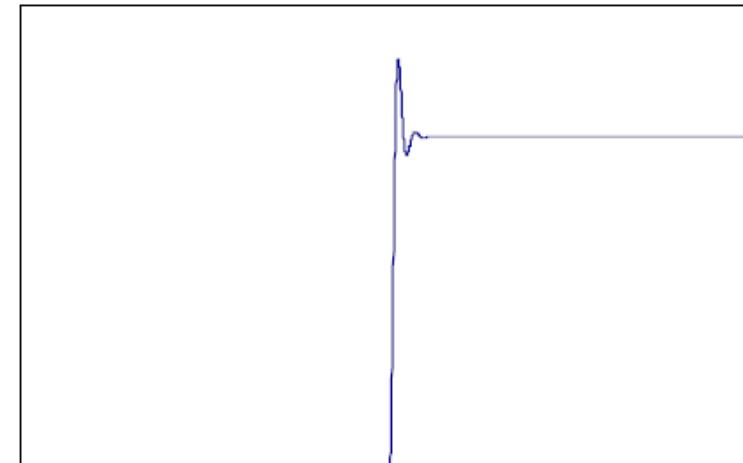

PM = 60°

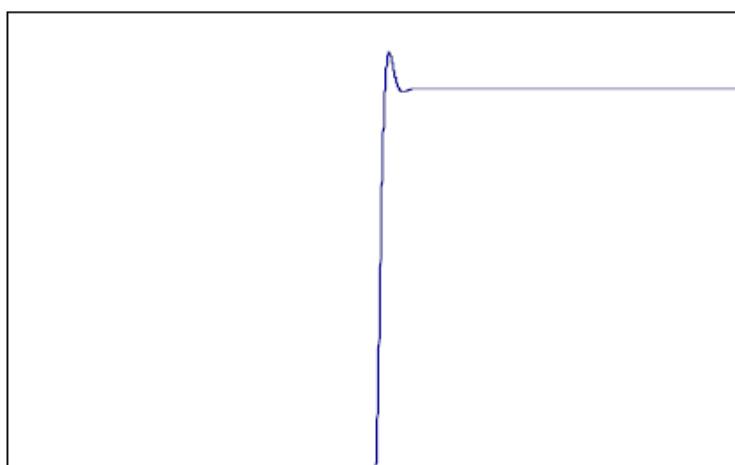


PM = 90°

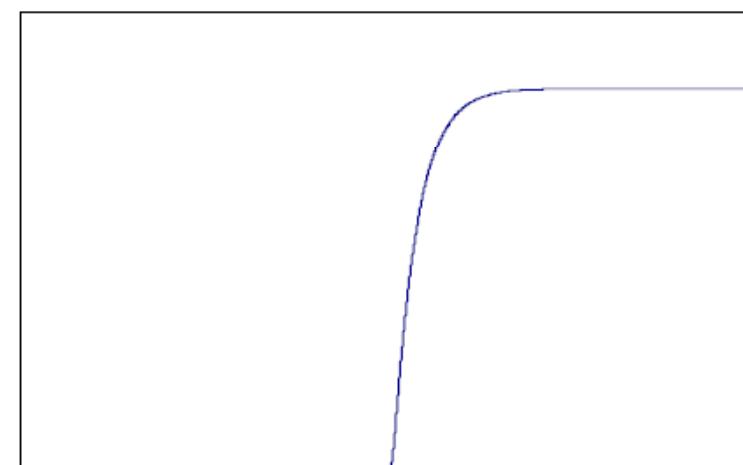

Non-Inverting Amplifier Example

ELEN-474

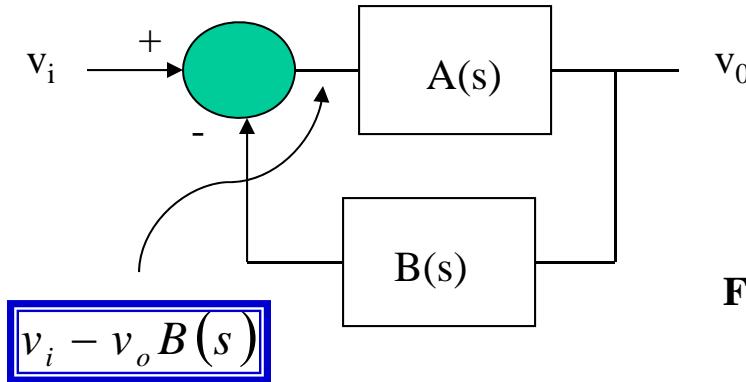

$$\frac{v_o}{v_i} = \frac{A(s)}{1 - (-T(s))}$$

If $T(s) \gg 1$, then $\frac{v_o}{v_i} \approx \frac{A(s)}{T(s)} = \frac{1}{B(s)}$

For Error, can write : $\frac{v_o}{v_i} = \frac{1}{B(s)} \left[\frac{T(s)}{1+T(s)} \right] = \frac{1}{B(s)} \left[\frac{1}{1 + \frac{1}{T(s)}} \right]$

$$\text{Error} \propto -\frac{1}{T(s)}$$


Key points:

If you want to amplify your signal: $B(s)$ must be an attenuator (voltage divider!!)


The error is determined by the overall loop gain: $T(s)=A(s)B(s)$

$$B(s) = \frac{Z_1}{Z_1 + Z_2} = \frac{1}{1 + \frac{Z_2}{Z_1}}$$
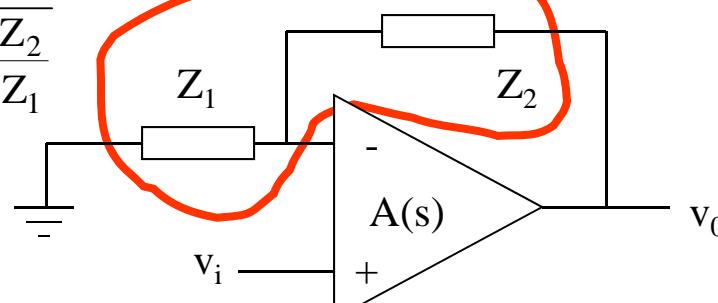
$$\frac{v_o(s)}{v_i(s)} \approx 1 + \frac{Z_2}{Z_1}$$






$A(s)$ is amplifier response only

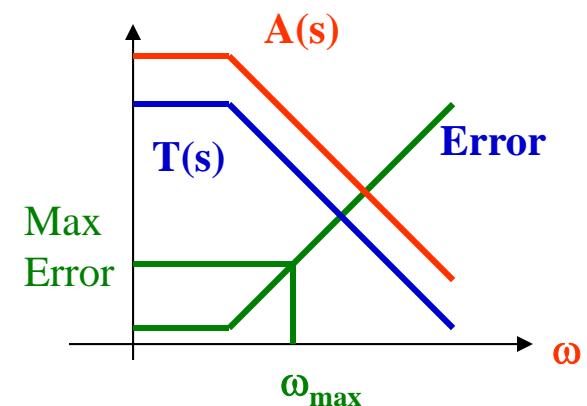

Inverting Amplifier: Apply superposition

A(s) and B(s) are sharing some elements!!

A(s)= ? B(s) = ? T(s) = ?

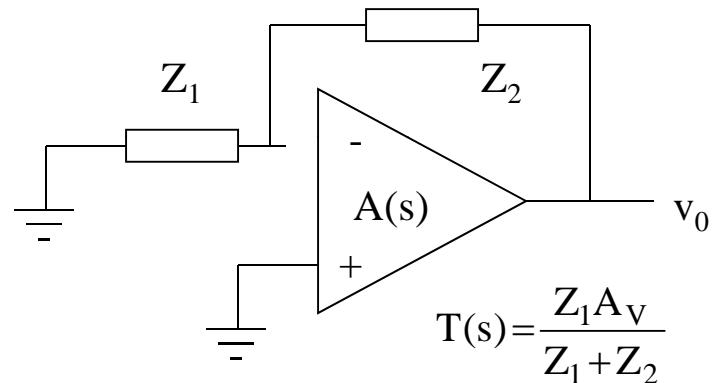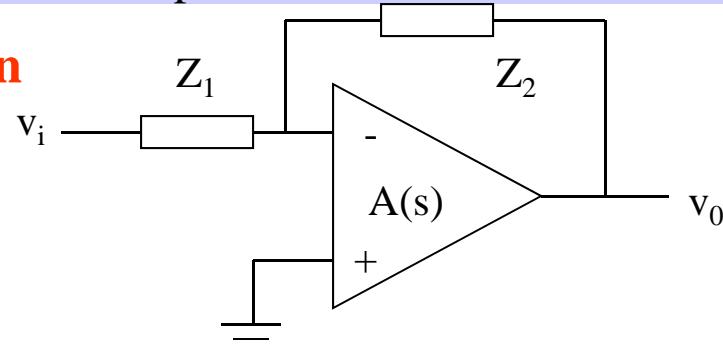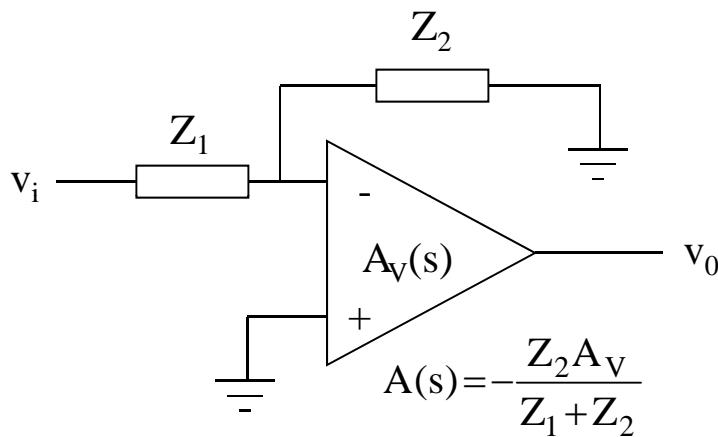

From $T(s) = A(s)B(s)$

$$B(s) = \frac{T(s)}{A(s)} = -\frac{Z_1}{Z_2}$$

$$\boxed{\frac{v_o(s)}{v_i(s)} \cong \frac{1}{B(s)} = -\frac{Z_2}{Z_1}}$$

$$\frac{v_o}{v_i} = \frac{A(s)}{1+T(s)} = -\frac{\frac{Z_2 A_V}{Z_1 + Z_2}}{1 + \frac{Z_1 A_V}{Z_1 + Z_2}} = -\frac{Z_2}{Z_1} \begin{pmatrix} \frac{1}{1 + \frac{Z_2}{Z_1}} \\ 1 + \frac{Z_2}{Z_1} \end{pmatrix}$$

Next Time

- Common-Mode Feedback Techniques