

# ECEN474: (Analog) VLSI Circuit Design

## Fall 2011

---

### Lecture 21: OTA CMFB Examples



Sebastian Hoyos  
Analog & Mixed-Signal Center  
Texas A&M University



# Agenda

---


- Multi-OTA stages CMFB
- OTA-C filter w/ CMFB example
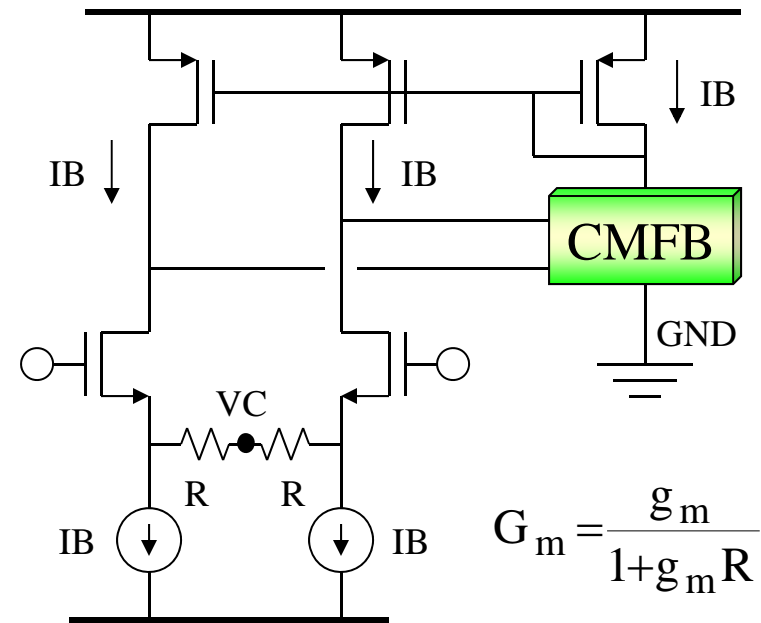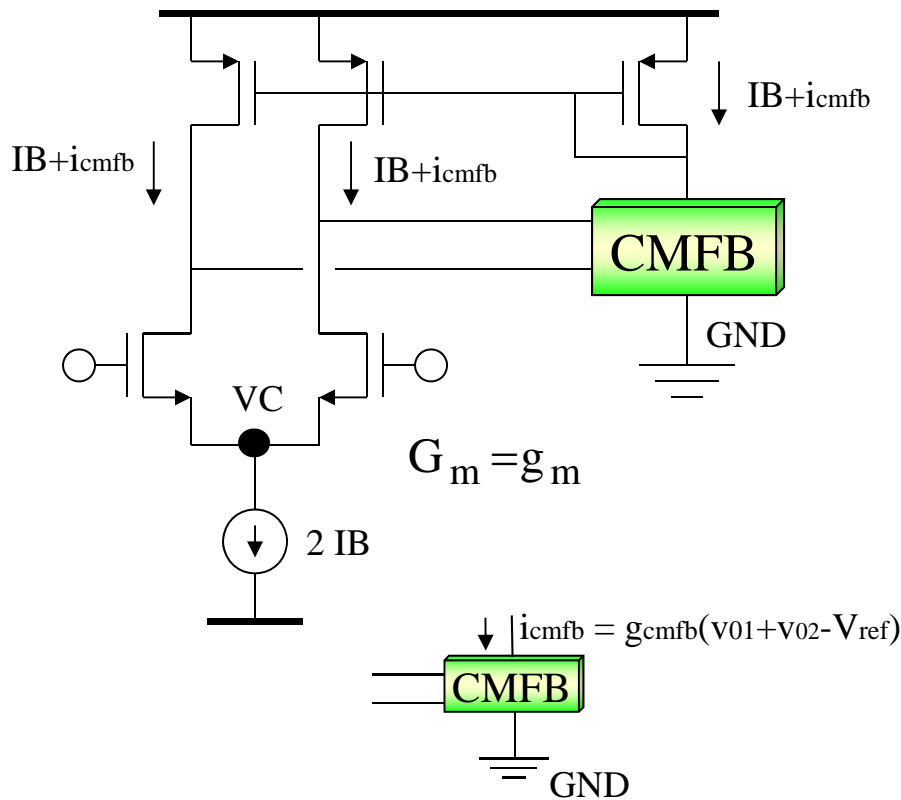
## CMFB is required for Differential Structures

CMFB Requirements: Fixes the OTA output (low offset) ==> High dc loop gain  
Reduction of common-mode noise==> Large Bandwidth



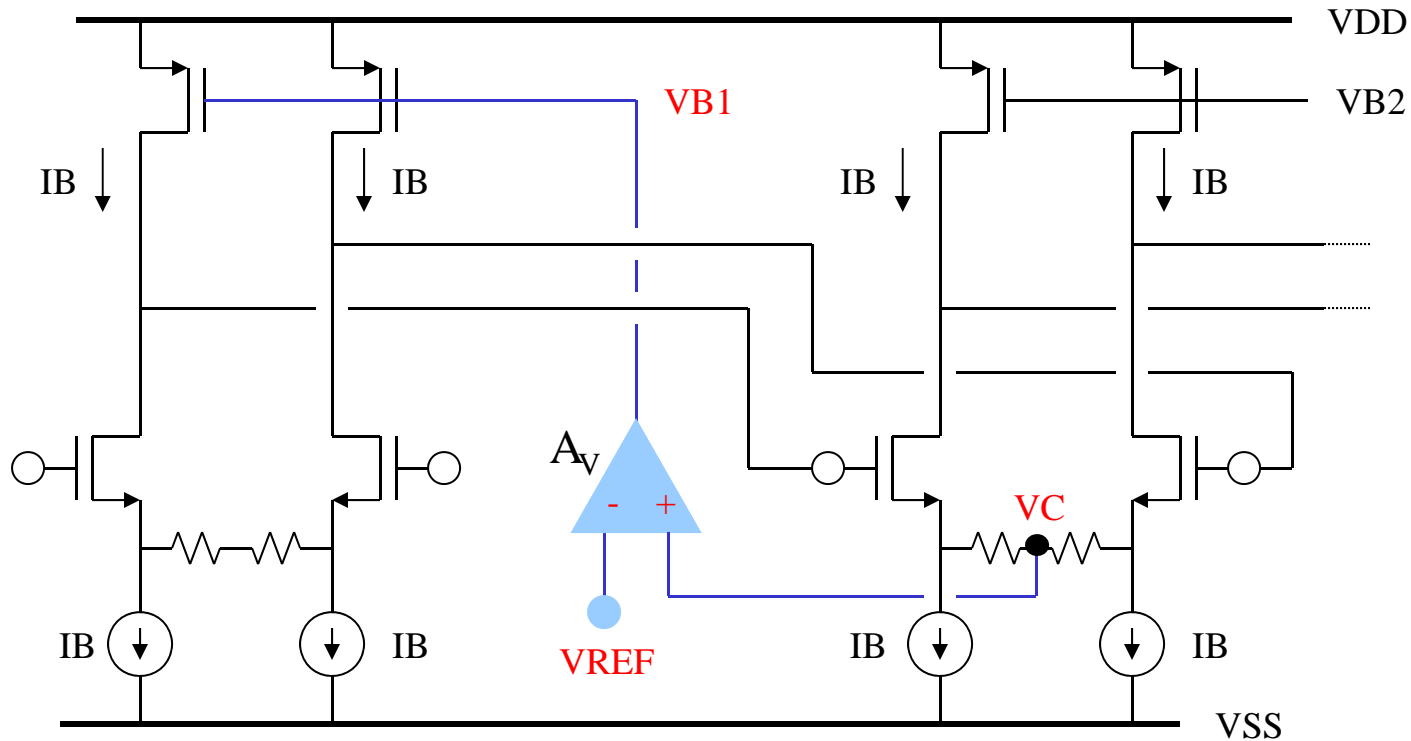
## Efficient CMFB for Differential Pair Based OTAs




**Common-mode loop gain =  $A_v G_m R_L$**

**3 poles in the CMFB loop. Loop stability requires  $A_v G_m / C_L < \omega_{p2} @ V_C, \omega_{p3} @ V_{B1}$**
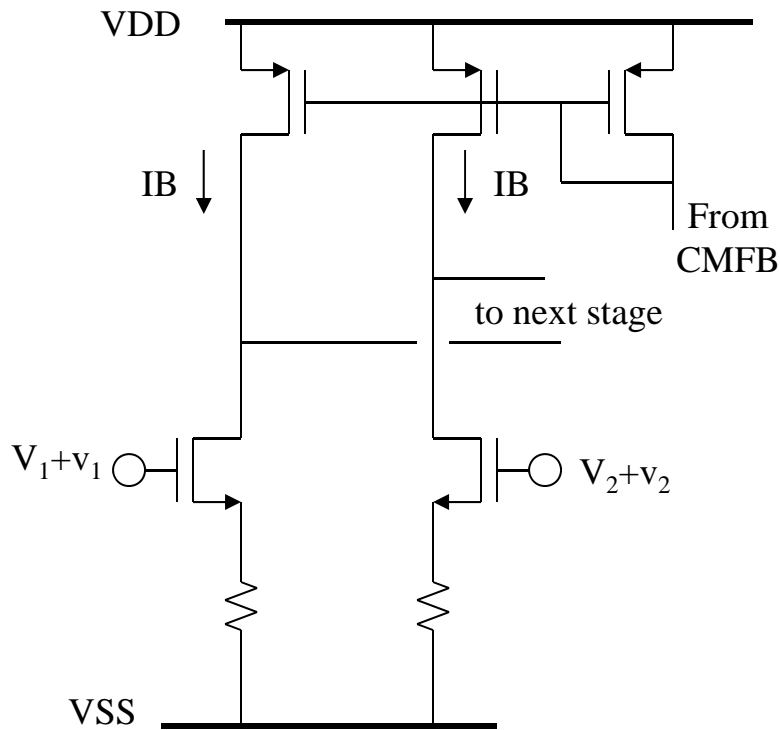
## Pseudo-Differential OTAs with Source Degeneration




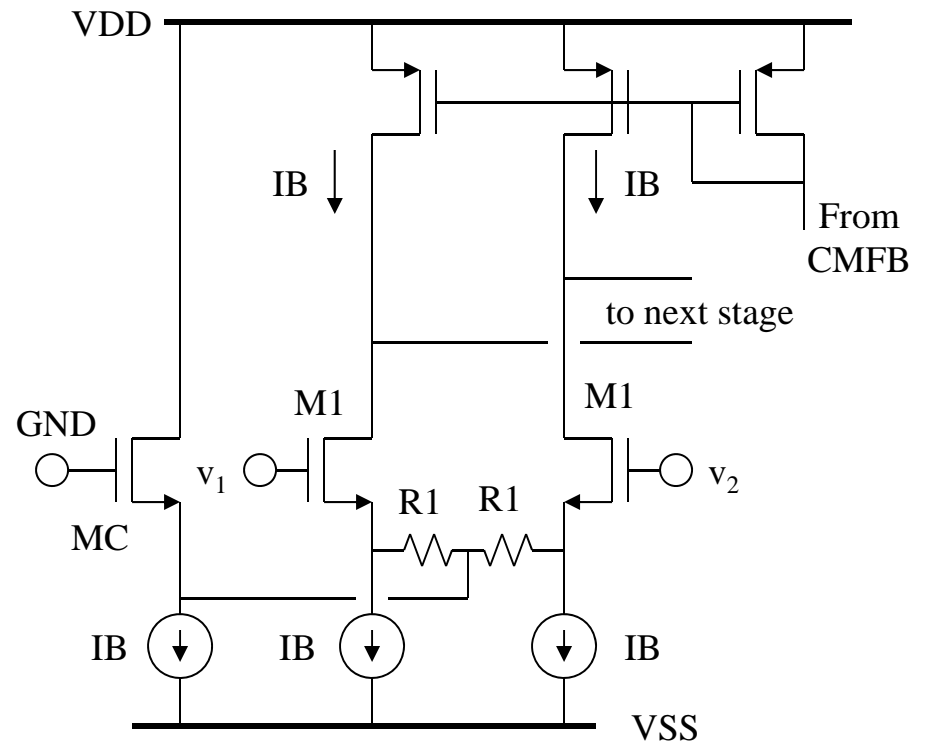**Sensitive to supply noise and common-mode input signals**




**Little sensitive to supply noise and Common-mode noise**
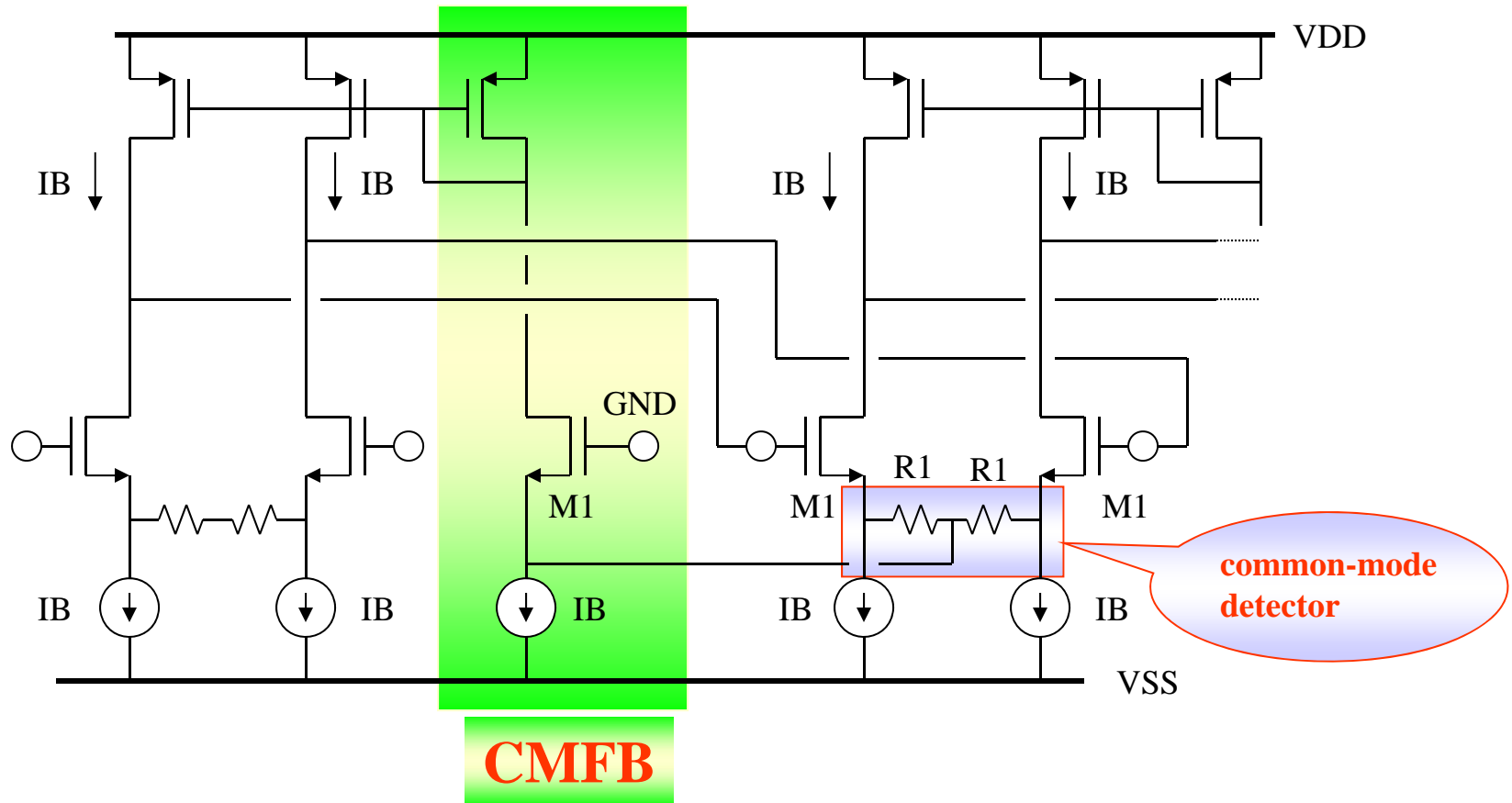
# Efficient CMFB for Pseudo-Differential OTAs


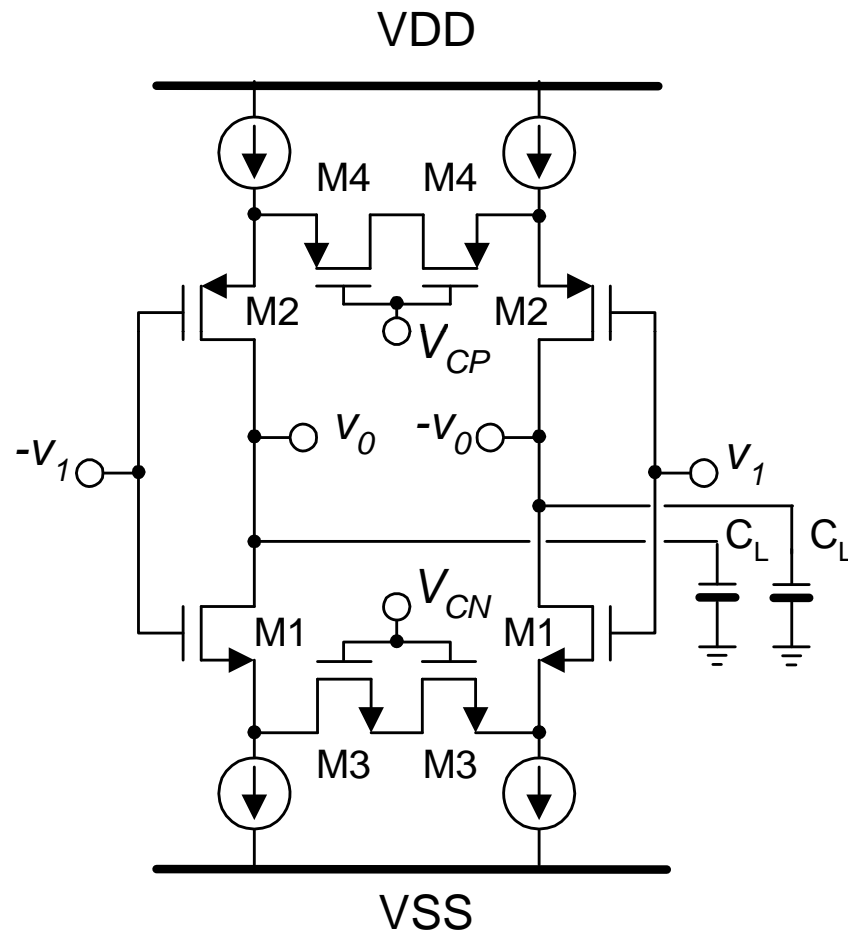
## OTA based on complementary differential pairs




- Efficient OTA based on linear complementary differential pairs

$$G_m = \frac{g_{m1}}{g_{m1}R_{M3} + 1} + \frac{g_{m2}}{g_{m2}R_{M2} + 1}$$

- Linear circuit due to source degeneration M3 and M4
- Suitable for fast applications
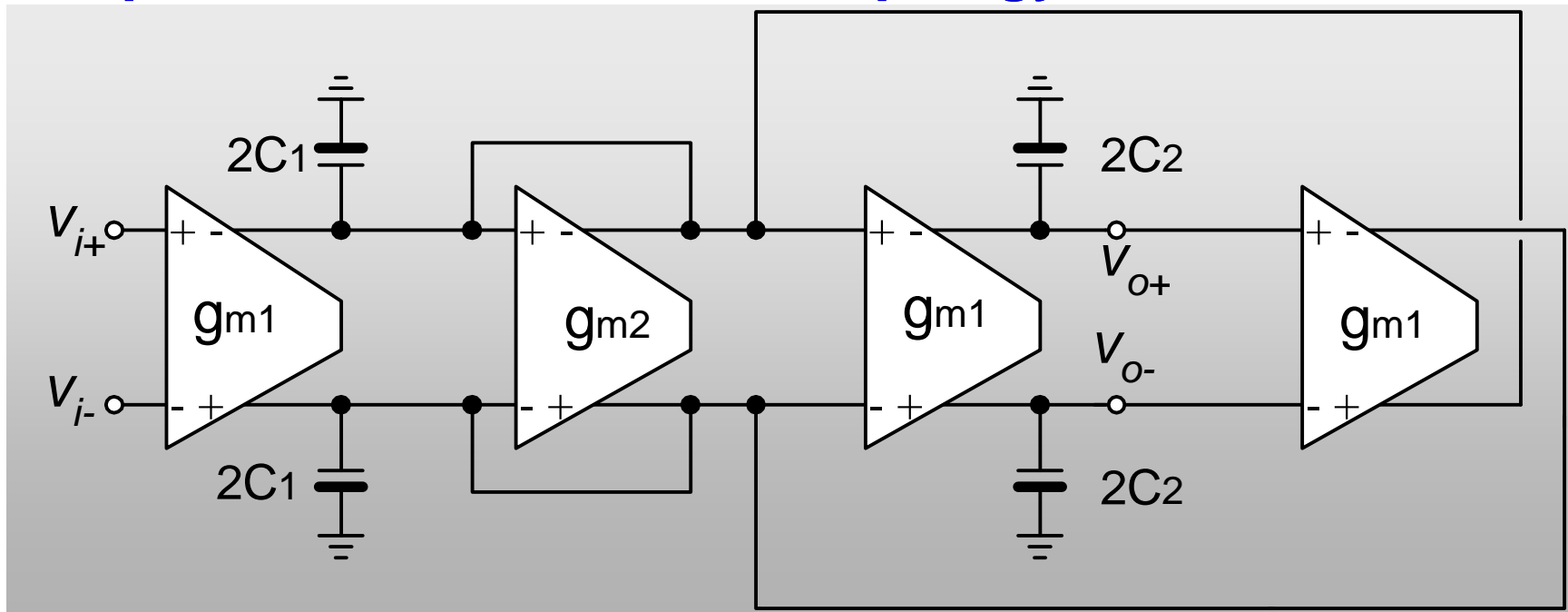
# Filter is based on Biquadratic Cells: Biquad Realization in Gm-C topology




	$f_0$ (MHz)	$G_{m1}$ (mA/V)	$G_{m2}$ (mA/V)
Biquad 1	537.6	5.4	9.6
Biquad 2	793.2	5.4	5.07

**!!! Fast CMFB is required**



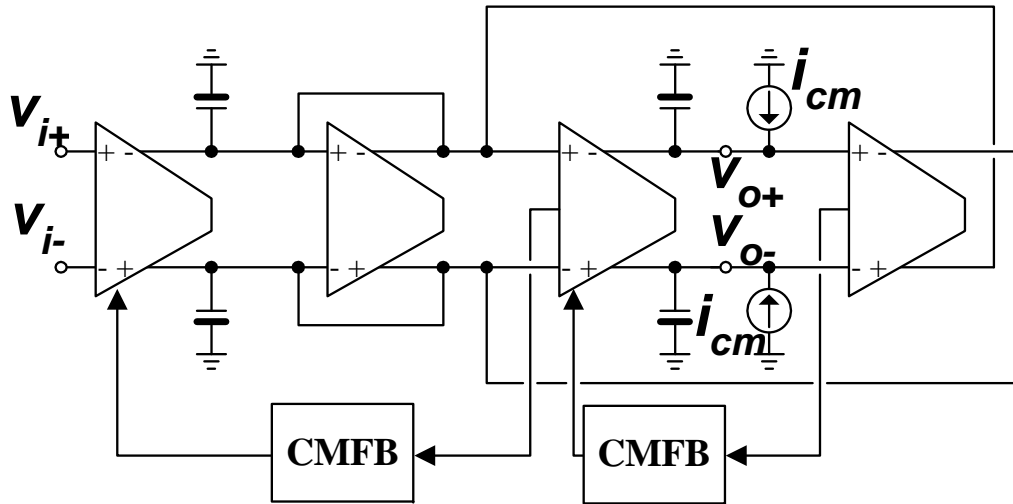
# Time Domain characterization of the CMFB




- Common-mode characterization using common-mode current pulses
- One CMFB circuit per pole

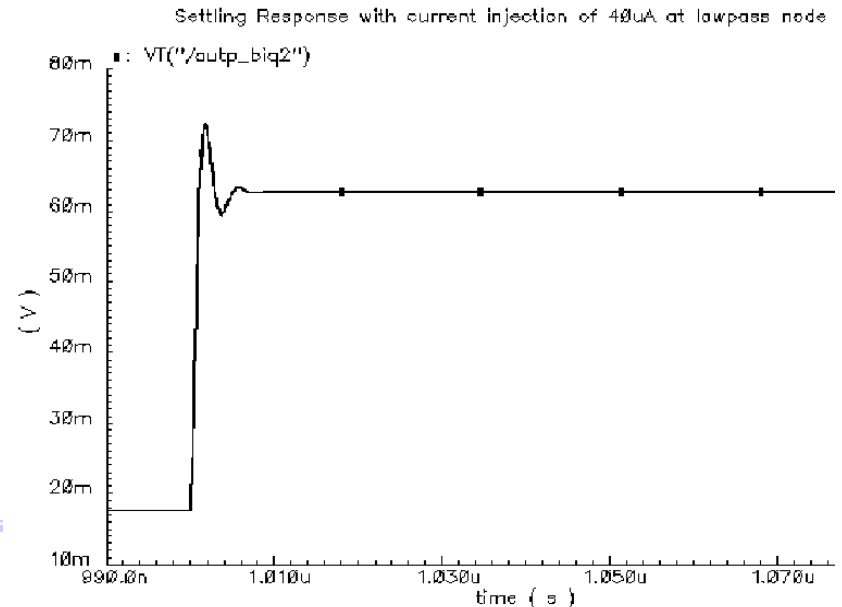- Pulse response of the CMFB
- Phase margin is better than 45 degrees



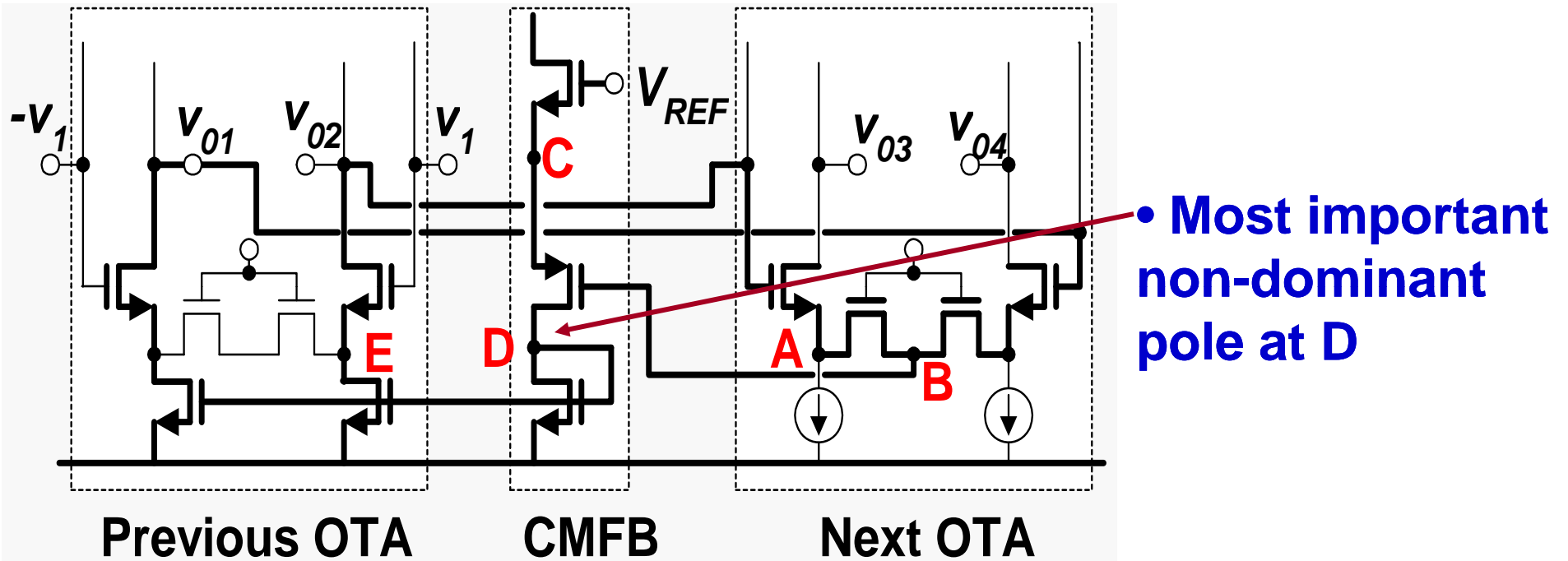
## OTA with Class AB Common-mode Feedback



- Common-mode signal is detected at next stage
- Class AB error amplifier is used
- 5 non-dominant poles at A~E
- 2 LHP zeros at A and C (Helpful in BW extension)

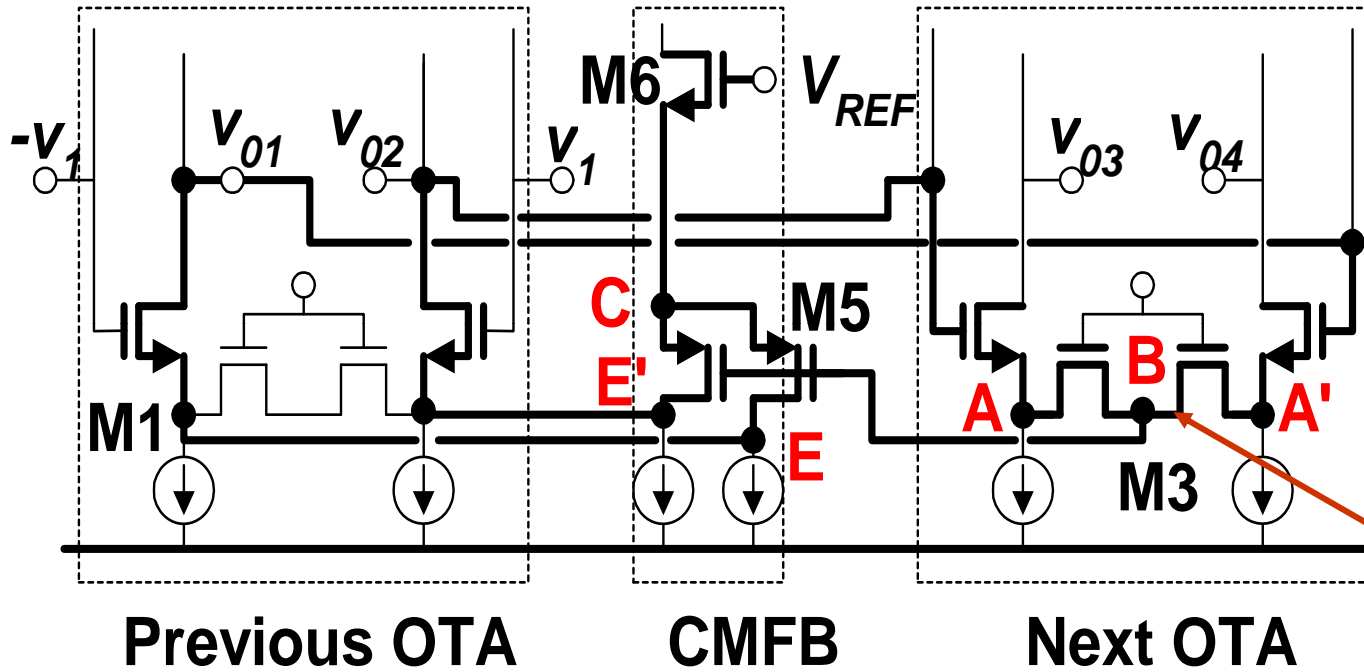
# Optimized Class AB Common-mode Feedback




• **Most important non-dominant pole at B**

- **Class AB error amplifier is used**
- **4 non-dominant poles at A~E**
- **2 LHP zeros at A and C (Helpful in BW extension)**
- **Node D was eliminated**

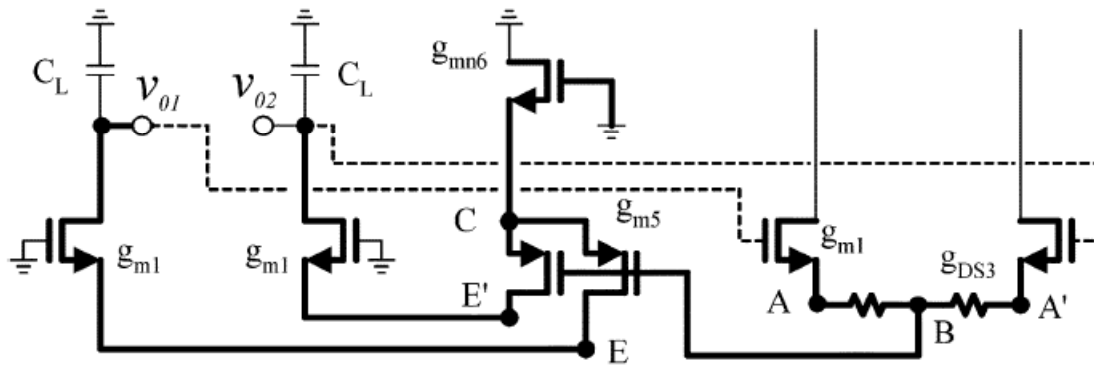
# Analysis of Class AB Common-mode Feedback


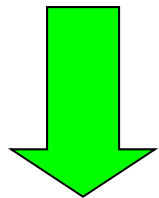
$$A_{VCMFB} \approx \frac{\frac{g_{m5}}{\left(1 + \frac{2g_{m5}}{g_{m6}}\right) g_L}}{\left(1 + \frac{sC_L}{g_L}\right) \left(1 + \frac{sC_B}{g_{03}}\right) \left(1 + \frac{sC_D}{g_{m1}}\right)}$$



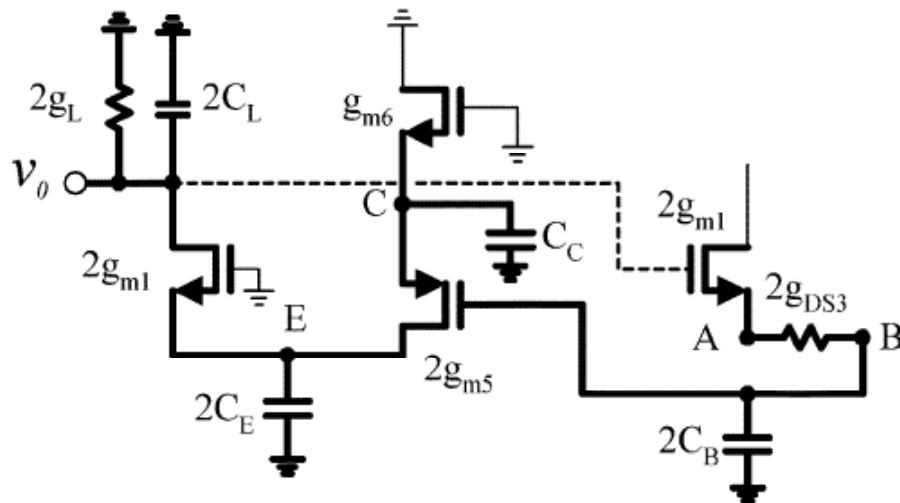CMFB can be simplified taking advantage of circuit's symmetry



- 2 pole-zero pairs (A and C) are very close to each other

- More stable CMFB

---

## Remarks

- **DC operating points for high impedances are difficult to fix**
- **Fully differential amplifiers with high output impedance nodes must use common-mode feedback circuits .**
- **Common mode circuits can fix the DC operating points as well as minimize the common mode output components.**
- **Low voltage constraints impose optimal bias conditions at both the input and output ports of an amplifier.**
- **Common mode circuits for LV should be used both at the input and output**

# Next Time

---

- Analog Applications
  - OTA-C Filters
  - Variable-Gain Amplifiers
  - Switch-Cap Filters, Broadband Amplifiers
- Output Stages
- Bandgap Reference Circuits
- Distortion