

# ECEN474: (Analog) VLSI Circuit Design

## Fall 2011

---

### Lecture 26: Transimpedance Amplifiers (TIAs)



Sebastian Hoyos  
Analog & Mixed-Signal Center  
Texas A&M University



# Agenda

---

- Transimpedance Amplifiers
  - Common-Gate TIAs
  - Feedback TIAs
- Material is related primarily to Project #6

# Transimpedance Amplifier (TIA)



---

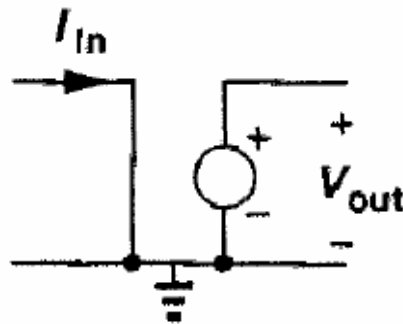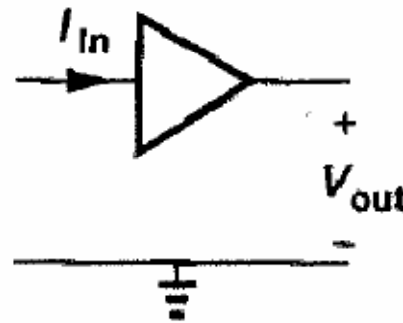

$$\text{Transimpedance } Z_T = \frac{v_{out}}{i_{in}} \quad (\Omega)$$



Also expressed in units of  $\text{dB}\Omega$  for  $20\log(|Z_T|)$

# Optical Receiver Front-End

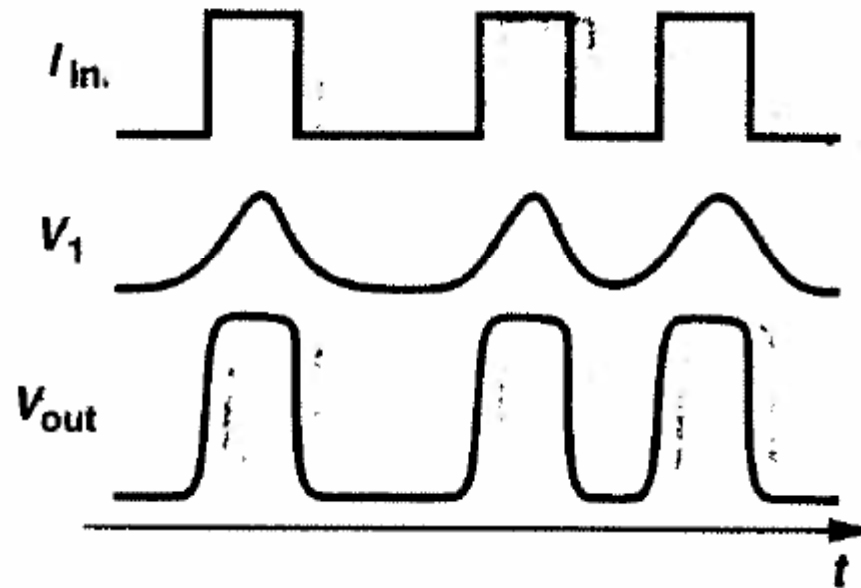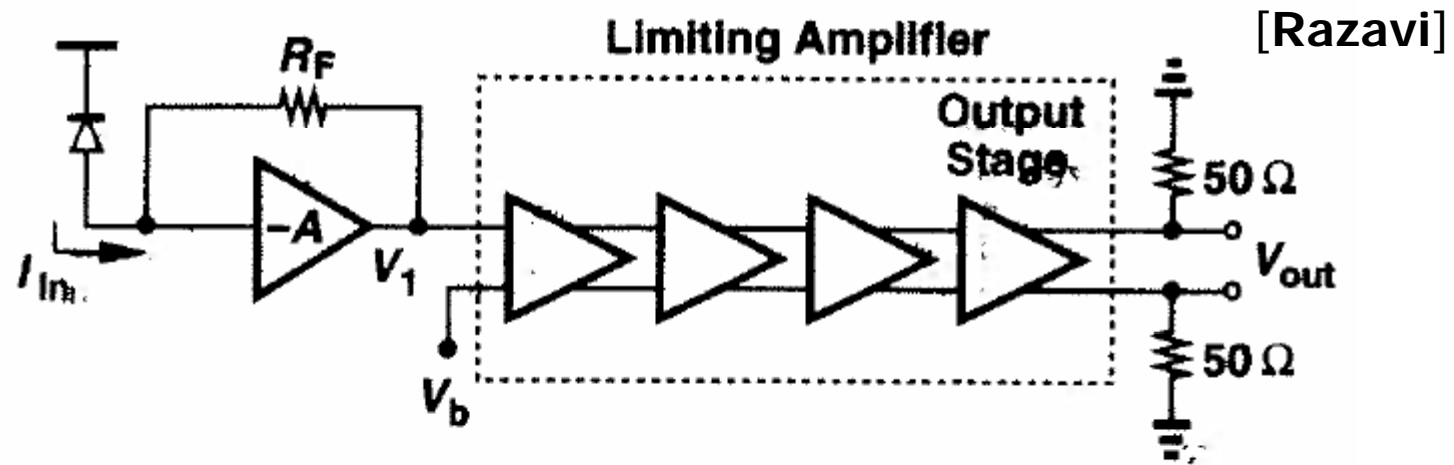

# Resistive Front-End

[Razavi]

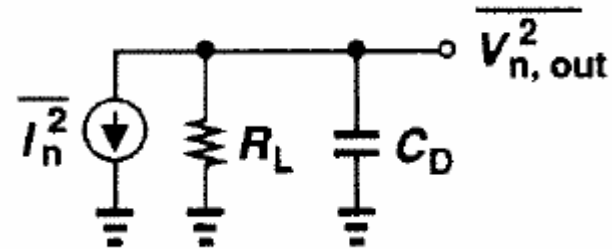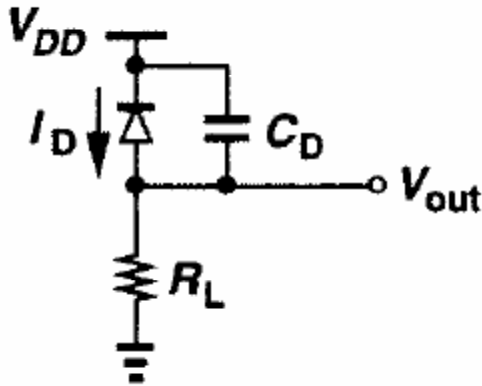

$$\overline{V_{n,out}^2} = \int_0^{\infty} \overline{I_n^2} Z_T^2 df = \int_0^{\infty} \frac{4kT}{R_L} \left( \frac{R}{1 + j2\pi fRC} \right)^2 df = \frac{kT}{C_D}$$

$$R_T = R_{in} = R_L$$

$$BW_{3dB} = \omega_p = \frac{1}{R_{in} C_D} = \frac{1}{R_L C_D}$$



$$\overline{I_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{R_L^2} = \frac{kT}{R_L^2 C_D}$$

$$I_{n,in,rms} = \frac{\sqrt{KT/C_D}}{R_L}$$

- Direct trade-offs between transimpedance, bandwidth, and noise performance

# Common-Gate TIA

[Razavi]

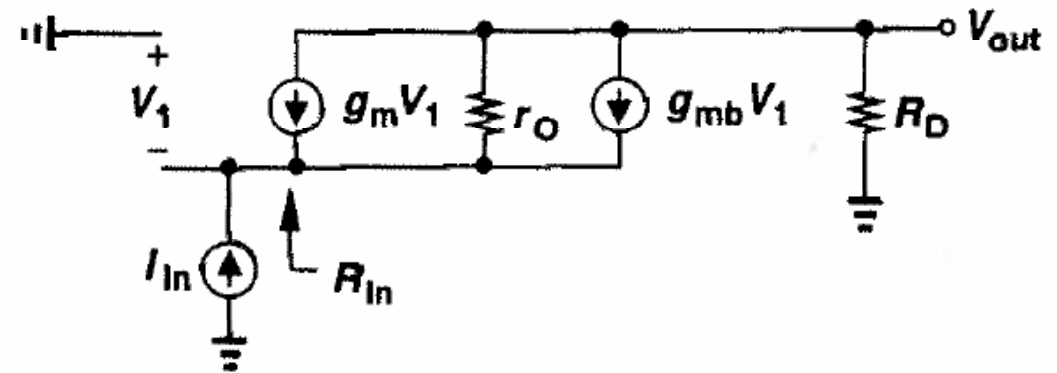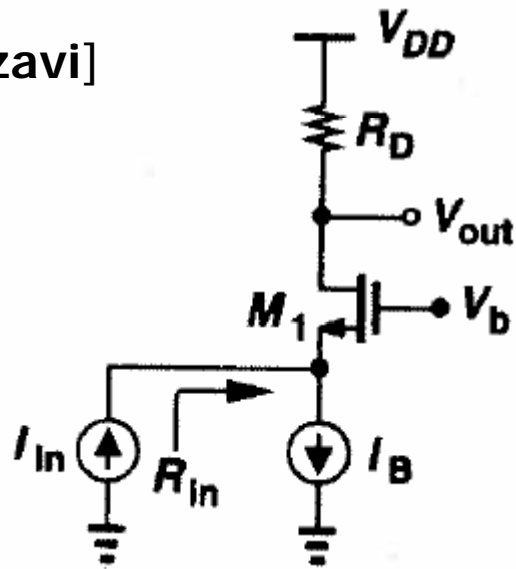


$$R_T = R_D$$

$$R_{in} = \frac{r_o + R_D}{1 + (g_m + g_{mb})r_o} \approx \frac{1}{g_m}$$

- Input resistance (input bandwidth) and transimpedance are decoupled

# Common-Gate TIA Frequency Response

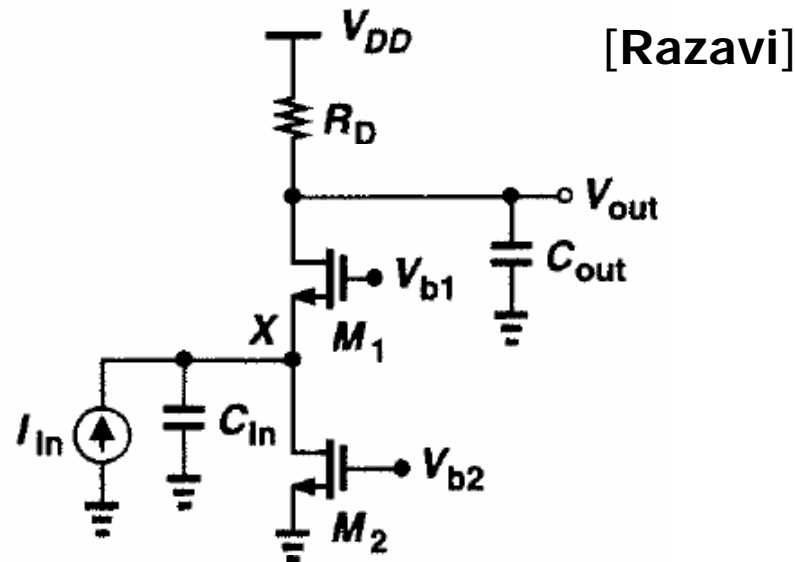


Neglecting transistor  $r_o$  :

$$\frac{V_{out}}{i_{in}} = \frac{R_D}{\left(1 + s \frac{C_{in}}{g_{m1} + g_{mb1}}\right) (1 + s R_D C_{out})}$$

- Often the input pole may dominate due to large photodiode capacitance (100 – 500fF)

# Common-Gate TIA Noise

[Razavi]

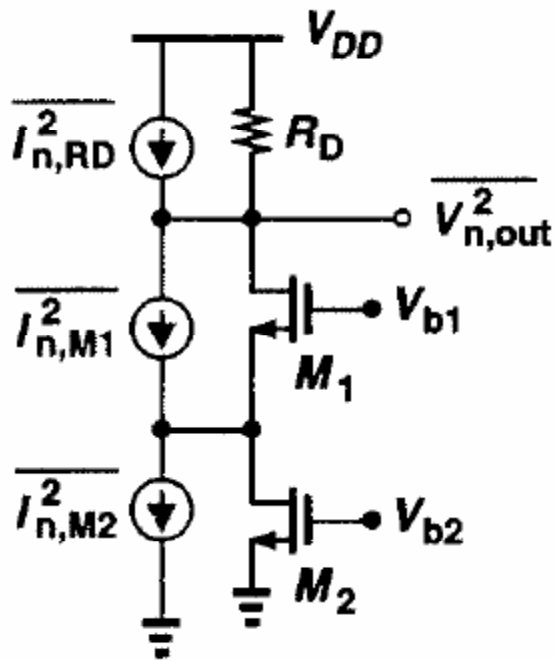

Neglecting transistor  $r_o$  :

$$\overline{V_{n,out}^2} = \left( \overline{I_{n,M2}^2} + \overline{I_{n,RD}^2} \right) R_D^2 = 4kT \left( \frac{2}{3} g_{m2} + \frac{1}{R_D} \right) R_D^2 \quad \left( \frac{\text{V}^2}{\text{Hz}} \right)$$

$$\overline{I_{n,in}^2} = 4kT \left( \frac{2}{3} g_{m2} + \frac{1}{R_D} \right) \quad \left( \frac{\text{A}^2}{\text{Hz}} \right)$$

- Both the bias current source and  $R_D$  contribute to the input noise current
- $R_D$  can be increased to reduce noise, but voltage headroom can limit this
- Common-gate TIAs are generally not for low-noise applications
- However, they are relatively simple to design with high stability



# Regulated Cascode (RGC) TIA

A packaged low-noise high-speed regulated cascode transimpedance amplifier  
using a 0.6 $\mu\text{m}$  N-well CMOS technology

Sung Min Park and C. Toumazou

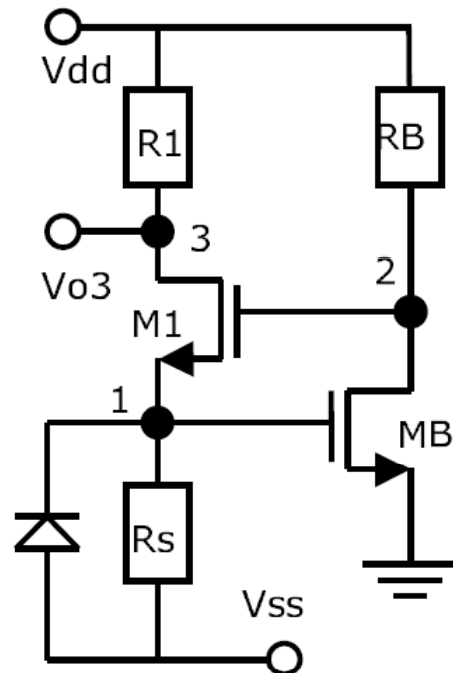



Figure 1. Schematic diagram of the regulated cascode (RGC) input stage

$$Z_{in}(0) \cong \frac{1}{g_{m1}(1 + g_{mB}R_B)}$$

# CMOS 20GHz TIA
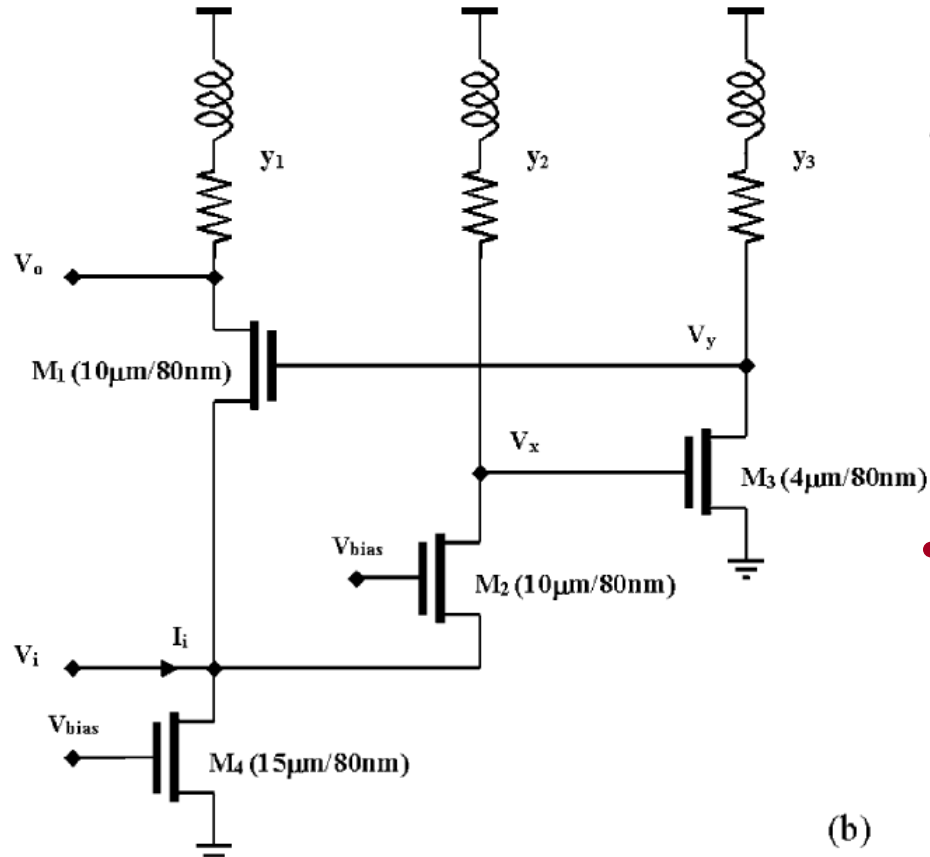
## A Low-Power 20-GHz 52-dBΩ Transimpedance Amplifier in 80-nm CMOS

Christian Kromer, *Member, IEEE*, Gion Sialm, Thomas Morf, *Member, IEEE*, Martin L. Schmatz, *Member, IEEE*, Frank Ellinger, *Member, IEEE*, Daniel Erni, *Member, IEEE*, and Heinz Jäckel, *Member, IEEE*



$$Z_i \approx \frac{1}{g_{m1} (1 + |A_2 A_3|) + j\omega C_{i,tot}}$$


$$A_2 = g_{m2} R_2 \quad A_3 = -g_{m3} R_3$$

- Inductors provide bandwidth extension at zero power cost, but very large area cost

(b)

# Feedback TIA w/ Ideal Amplifier

[Sackinger]

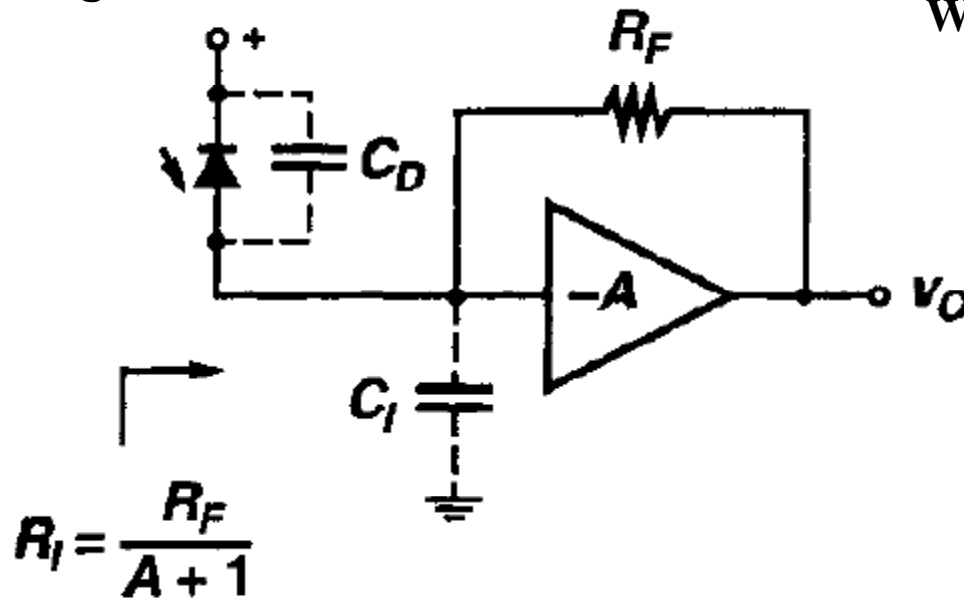

With Infinite Bandwidth Amplifier :

$$Z_T(s) = -R_T \left( \frac{1}{1 + s/\omega_p} \right)$$

$$R_T = \frac{A}{A+1} R_F$$


$$R_{in} = \frac{R_F}{A+1}$$

$$\omega_p = \frac{1}{R_{in} C_T} = \frac{A+1}{R_F (C_D + C_I)}$$

- Input bandwidth is extended by the factor  $A+1$
- Transimpedance is approximately  $R_F$
- Can make  $R_F$  large without worrying about voltage headroom considerations

# Feedback TIA w/ Finite Amplifier Bandwidth

[Sackinger]

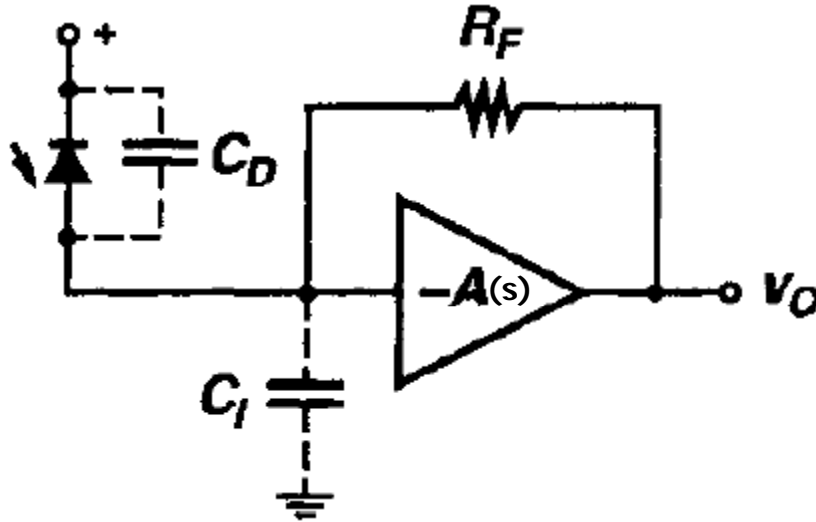

With Finite Bandwidth Amplifier :

$$A(s) = \frac{A}{1 + \frac{s}{\omega_A}} = \frac{A}{1 + sT_A}$$

$$Z_T(s) = -R_T \left( \frac{1}{1 + s/(\omega_o Q) + s^2/\omega_o^2} \right)$$

$$R_T = \frac{A}{A+1} R_F$$

$$\omega_o = \sqrt{\frac{A+1}{R_F C_T T_A}}$$

$$Q = \frac{\sqrt{(A+1)R_F C_T T_A}}{R_F C_T + T_A}$$

$$R_{in} = \frac{R_F}{A+1}$$

# Next Time

---

- Feedback TIA Examples
- Multi-Stage (Limiting) Amplifiers
- Bandgap References
- Distortion