

ECEN474: (Analog) VLSI Circuit Design

Fall 2011

Lecture 9: Frequency Response



Sebastian Hoyos
Analog & Mixed-Signal Center
Texas A&M University



Announcements

- Reading
 - Razavi's CMOS book chapters 3 & 6

Agenda


- Common-Source Amp Frequency Response
- Open-Circuit Time Constants ($OC\tau$)
Bandwidth Estimation Technique

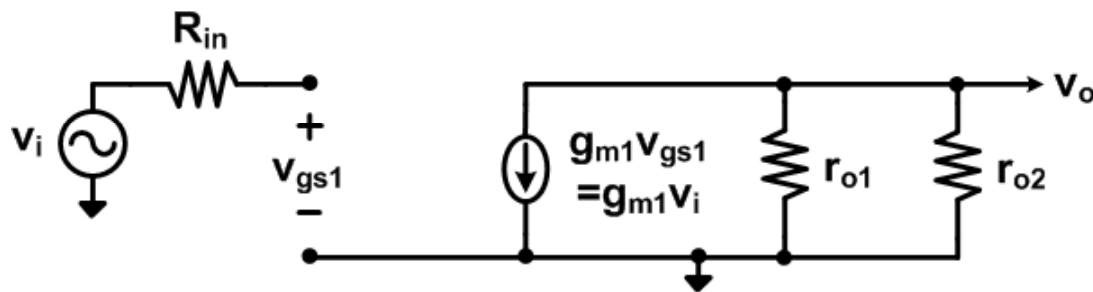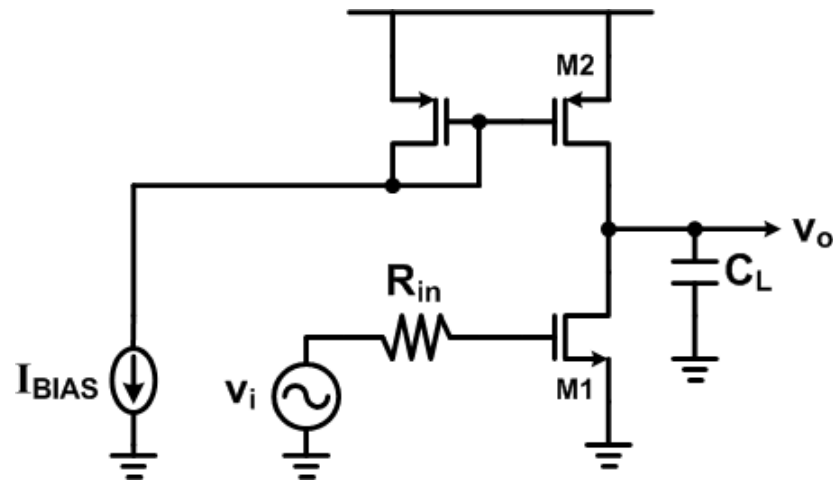Common-Source Amplifier: Low Frequency Response



$$\frac{v_o}{v_i} = -\frac{g_{m1}}{g_{o1} + g_{o2}}$$

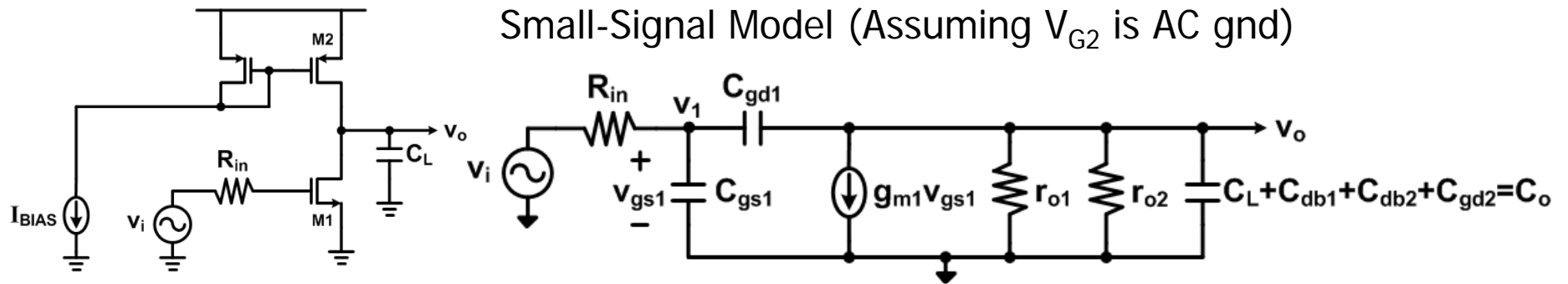Common-Source Amplifier: High Frequency Response



Small-Signal Model (Assuming V_{G2} is AC gnd)

$$\text{KCL @ Node } v_1 : (v_1 - v_i)G_{in} + v_1sC_{gs1} + (v_1 - v_o)sC_{gd1} = 0$$

$$\text{KCL @ Node } v_o : (v_o - v_1)sC_{gd1} + g_{m1}v_1 + v_o(g_o + sC_o) = 0$$

$$\text{where } g_o = g_{o1} + g_{o2}$$

After some algebra, we get
the exact transfer function:

$$\frac{v_o}{v_i} = \frac{-g_m r_o \left(1 - s \frac{C_{gd1}}{g_{m1}}\right)}{1 + sa + s^2 b}$$


where

$$a = R_{in} [C_{gs1} + C_{gd1}(1 + g_m r_o)] + r_o (C_{gd1} + C_o)$$

and

$$b = R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)$$

Common-Source Amp Frequency Response

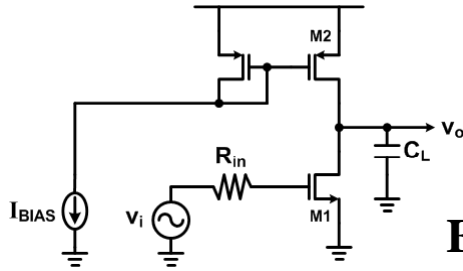

Exact Transfer Function :
$$\frac{v_o}{v_i} = \frac{-g_m r_o \left(1 - s \frac{C_{gd1}}{g_{m1}}\right)}{1 + sa + s^2 b}$$

For the common case when the two poles are real and far apart

Denominator
$$D(s) = \left(1 - \frac{s}{\omega_{p1}}\right) \left(1 - \frac{s}{\omega_{p2}}\right) = 1 - s \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right) + \frac{s^2}{\omega_{p1} \omega_{p2}} \cong 1 - \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1} \omega_{p2}}$$

Thus,
$$\omega_{p1} = -\frac{1}{a} = -\frac{1}{R_{in} [C_{gs1} + C_{gd1} (1 + g_{m1} r_o)] + r_o (C_{gd1} + C_o)}$$

and the transfer function can be approximated as a single pole system

$$A(s) = \frac{v_o}{v_i} \cong \frac{-g_{m1} r_o}{1 + s(R_{in} [C_{gs1} + C_{gd1} (1 + g_{m1} r_o)] + r_o (C_{gd1} + C_o))}$$

Open-Circuit Time Constants (OC τ)

- Open-circuit time constants technique can be used to estimate bandwidth
 - Much easier than deriving transfer function
 - Accurate for systems with one dominant pole

$$\text{All - Pole Transfer Function : } \frac{v_o(s)}{v_i(s)} = \frac{a_0}{(\tau_1 s + 1)(\tau_2 s + 1) \dots (\tau_n s + 1)}$$

$$\text{Denominator : } b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + 1$$



$$\text{Here } b_n = \prod_{i=1}^n \tau_i \quad \text{and} \quad b_1 = \sum_{i=1}^n \tau_i$$

A Dominant - Pole System can be approximated as

$$\frac{v_o(s)}{v_i(s)} \cong \frac{a_0}{b_1 s + 1} = \frac{a_0}{\left(\sum_{i=1}^n \tau_i \right) s + 1}$$

$$\text{Bandwidth } \omega_h \cong \frac{1}{b_1} = \frac{1}{\sum_{i=1}^n \tau_i} = \omega_{h,est}$$

Open-Circuit Time Constants ($OC\tau$)

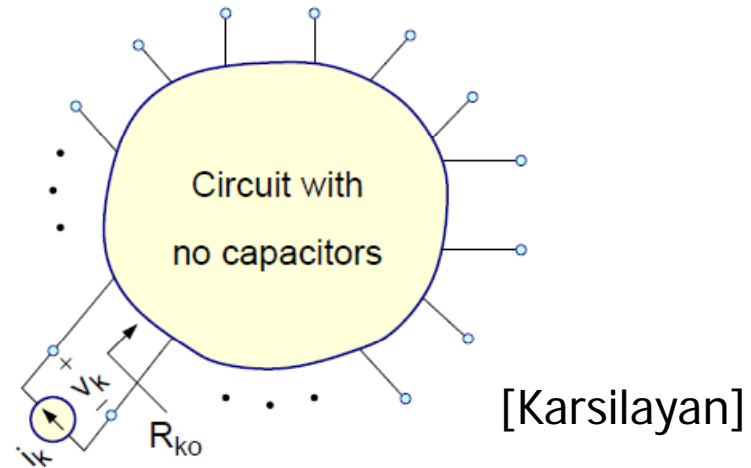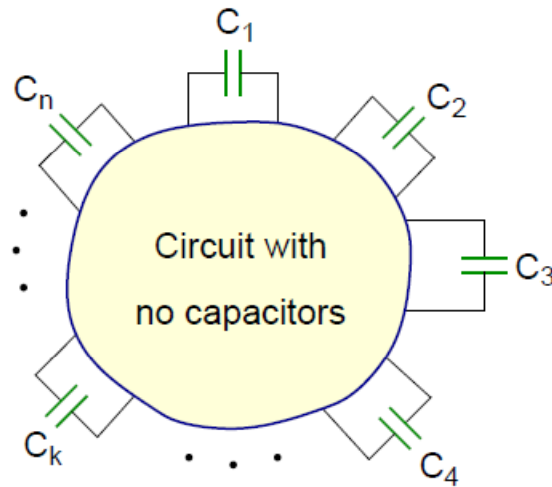


[Karsilayan]


- To compute time-constants
 1. Compute effective resistance R_{ko} facing each k th capacitor with all other caps open-circuited
 2. Form the product $\tau_{ko} = R_{ko} C_k$
 3. Sum all n "open-circuit" time constants

$$\omega_{h,est} = \frac{1}{\sum_{k=1}^n R_{ko} C_k}$$

Common-Source Amp w/ $OC\tau$

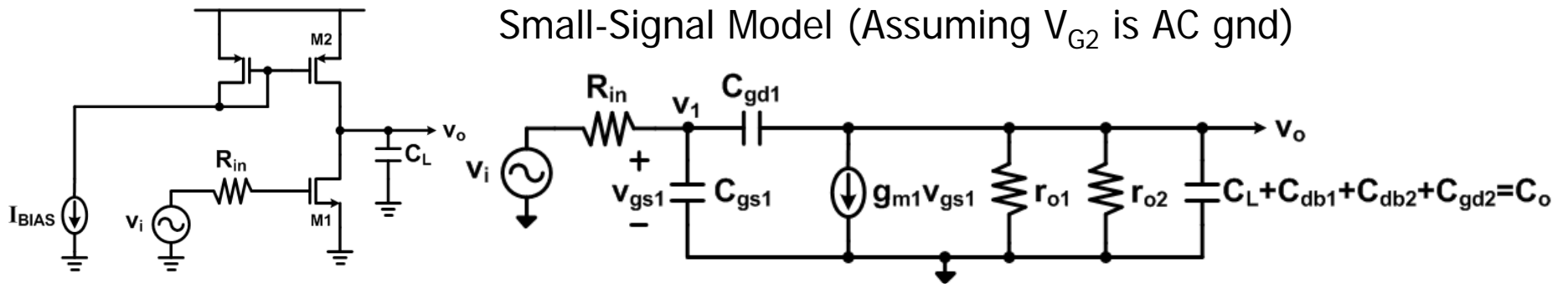


- For C_{gs1}

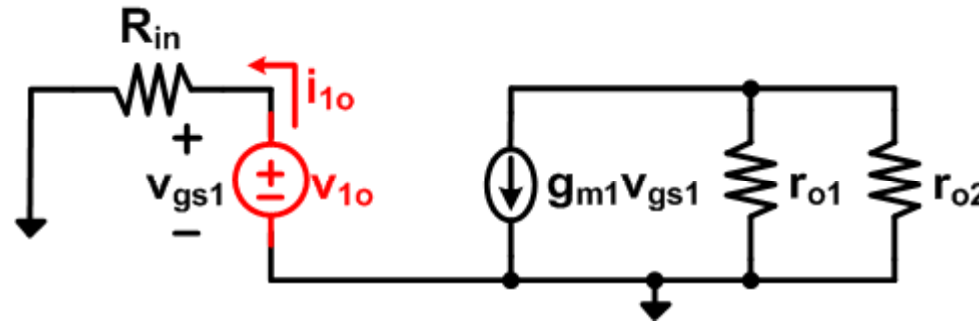


$$R_{1o} = \frac{v_{1o}}{i_{1o}} = \frac{v_{1o}}{\left(\frac{v_{1o}}{R_{in}}\right)} = R_{in}$$

$$\tau_{1o} = R_{in} C_{gs1}$$

Common-Source Amp w/ $OC\tau$

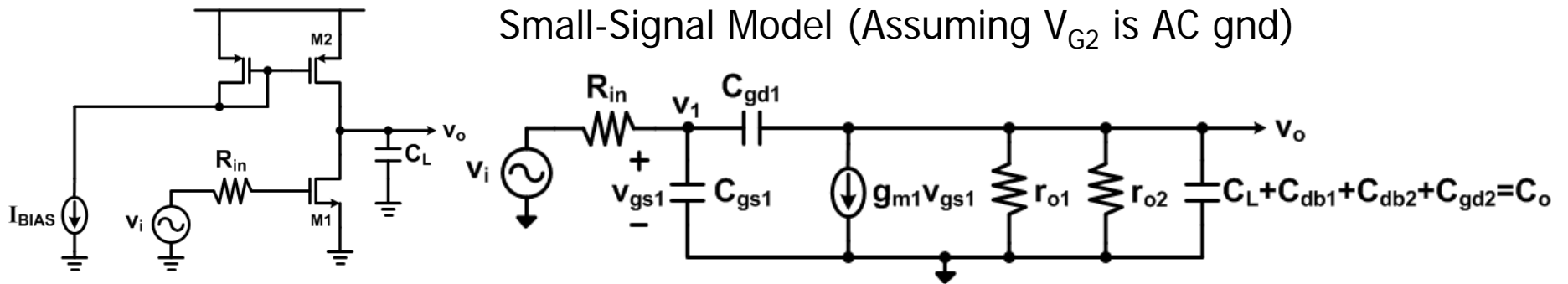

- For C_{gd1}

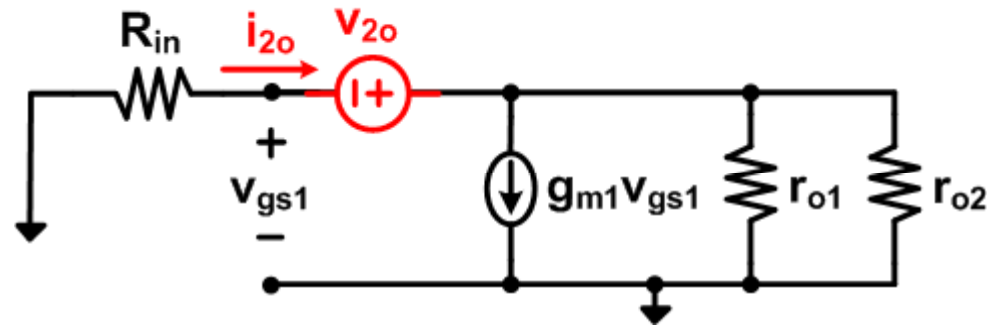

$$(1) \quad i_{2o} = g_m v_{gs1} + \frac{(v_{2o} + v_{gs1})}{r_o}$$


$$(2) \quad v_{gs1} = -i_{2o} R_{in}$$

Plugging (2) into (1) and solving for $\frac{v_{2o}}{i_{2o}}$


$$R_{2o} = \frac{v_{2o}}{i_{2o}} = R_{in} (1 + g_m r_o) + r_o$$

$$\tau_{2o} = (R_{in} (1 + g_m r_o) + r_o) C_{gd1}$$

Common-Source Amp w/ $OC\tau$

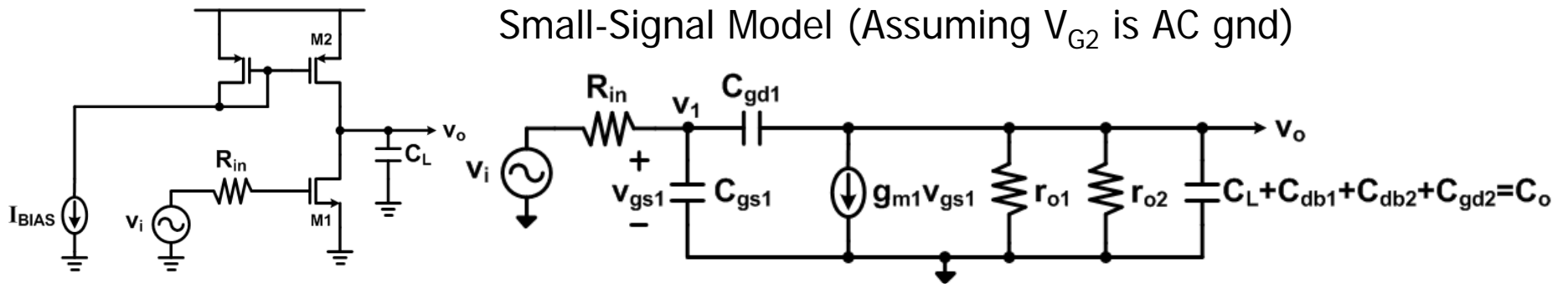


- For C_o

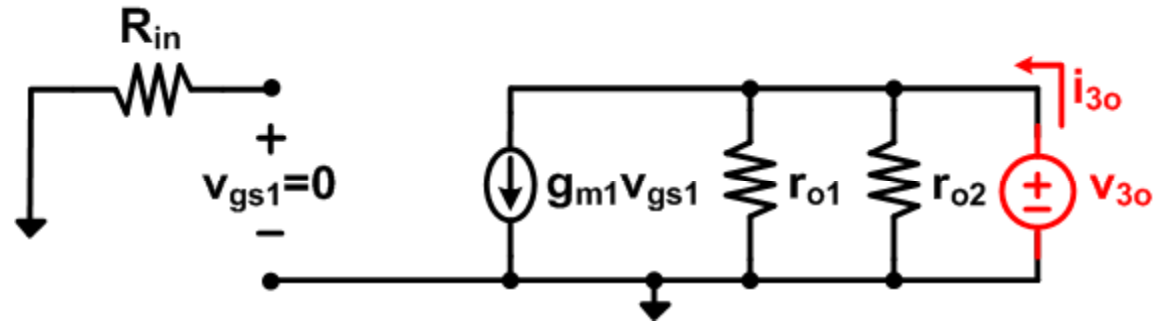

$$R_{3o} = \frac{v_{3o}}{i_{3o}} = \frac{v_{3o}}{\left(\frac{v_{3o}}{r_o}\right)} = r_o$$

$$\tau_{3o} = r_o C_o$$

Common-Source Amp w/ $OC\tau$

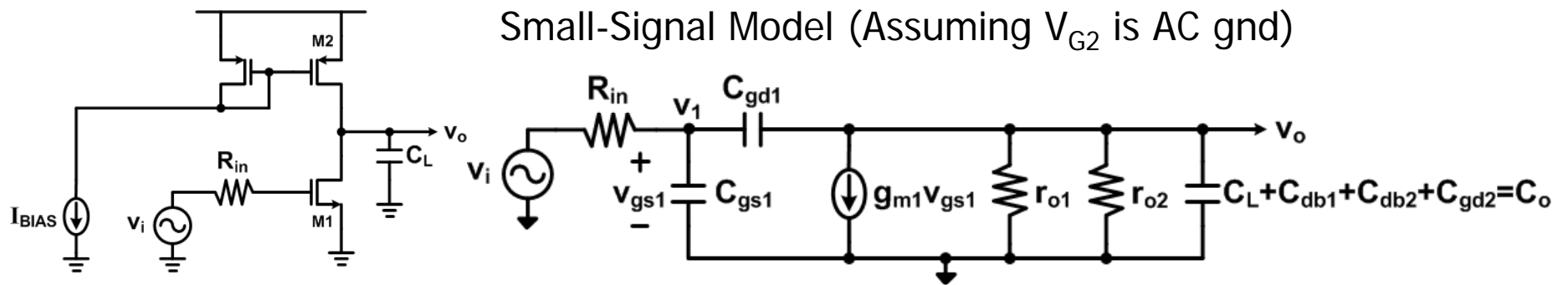

3 Time Constants : $\tau_{1o} = R_{in} C_{gs1}$, $\tau_{2o} = (R_{in}(1 + g_m r_o) + r_o) C_{gd1}$, $\tau_{3o} = r_o C_o$


$$b_1 = \sum_{i=1}^n \tau_i = R_{in} C_{gs1} + (R_{in}(1 + g_m r_o) + r_o) C_{gd1} + r_o C_o$$

$$\omega_{h,est} = \frac{1}{b_1} = \frac{1}{R_{in} C_{gs1} + (R_{in}(1 + g_m r_o) + r_o) C_{gd1} + r_o C_o}$$

Exactly the same as what we derived in Slide 6!

$$A(s) = \frac{v_o}{v_i} \cong \frac{-g_{m1} r_o}{1 + s(R_{in} [C_{gs1} + C_{gd1}(1 + g_{m1} r_o)] + r_o (C_{gd1} + C_o))}$$

Common-Source Amp w/ Large R_{in}

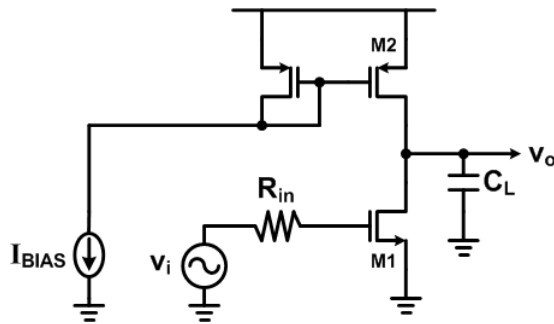

- Example: Using common-source output stage in a 2-stage OpAmp

$$A(s) = \frac{v_o}{v_i} \cong \frac{-g_{m1}r_o}{1 + s(R_{in}[C_{gs1} + C_{gd1}(1 + g_{m1}r_o)] + r_o(C_{gd1} + C_o))}$$


with $R_{in} \gg r_o$

$$A(s) = \frac{v_o}{v_i} \cong \frac{-g_{m1}r_o}{1 + sR_{in}[C_{gs1} + C_{gd1}(1 + g_{m1}r_o)]}$$

$$\omega_{p1} = -\frac{1}{R_{in}[C_{gs1} + C_{gd1}(1 + g_{m1}r_o)]}$$

- Dominant pole is formed by input resistance times transistor C_{gs} and C_{gd} which has been multiplied by $1 - A_{dc}$
 - $C_{gd}(1 - A_{dc})$ is called the Miller capacitance

Common-Source Amp w/ Large R_{in}

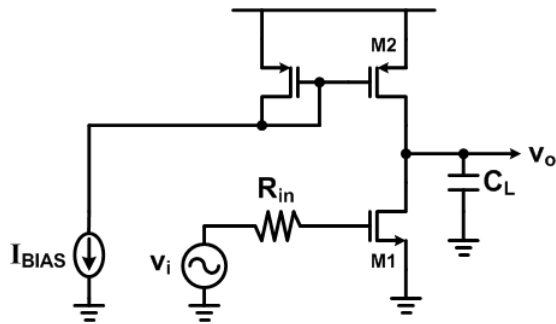

- What about the second pole?

Exact Transfer Function:
$$\frac{v_o}{v_i} = \frac{-g_m r_o \left(1 - s \frac{C_{gd1}}{g_{m1}}\right)}{1 + sa + s^2 b}$$

Denominator
$$D(s) = \left(1 - \frac{s}{\omega_{p1}}\right) \left(1 - \frac{s}{\omega_{p2}}\right) = 1 - s \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right) + \frac{s^2}{\omega_{p1} \omega_{p2}} \cong 1 - \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1} \omega_{p2}}$$


$$\frac{1}{\omega_{p1} \omega_{p2}} = b = R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)$$

$$\omega_{p2} = -\frac{1}{\omega_{p1} R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)} = -\frac{R_{in} [C_{gs1} + C_{gd1} (1 + g_{m1} r_o)]}{R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)}$$

Assuming that the Miller Cap, $C_{gd1} (1 + g_{m1} r_o)$, dominates

$$\omega_{p2} \cong -\frac{g_m C_{gd1}}{C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o}$$

Common-Source Amp w/ Small R_{in}

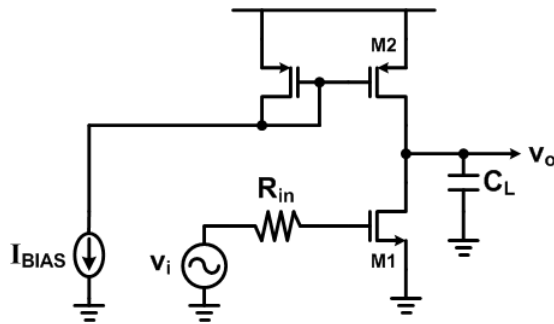

- Example: Source-follower driving the common-source amp

$$A(s) = \frac{v_o}{v_i} \cong \frac{-g_{m1}r_o}{1 + s(R_{in}[C_{gs1} + C_{gd1}(1 + g_{m1}r_o)] + r_o(C_{gd1} + C_o))}$$


with $r_o \gg R_{in}$

$$A(s) = \frac{v_o}{v_i} \cong \frac{-g_{m1}r_o}{1 + sr_o(C_{gd1} + C_o)}$$

$$\omega_{p1} = -\frac{1}{r_o(C_{gd1} + C_o)}$$

- Dominant pole is formed by output resistance times output capacitance plus transistor C_{gd}

Common-Source Amp w/ Small R_{in}

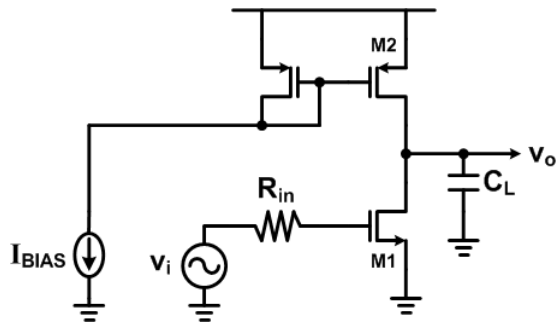

- What about the second pole?

Exact Transfer Function:
$$\frac{v_o}{v_i} = \frac{-g_m r_o \left(1 - s \frac{C_{gd1}}{g_{m1}}\right)}{1 + sa + s^2 b}$$


Denominator
$$D(s) = \left(1 - \frac{s}{\omega_{p1}}\right) \left(1 - \frac{s}{\omega_{p2}}\right) = 1 - s \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right) + \frac{s^2}{\omega_{p1} \omega_{p2}} \cong 1 - \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1} \omega_{p2}}$$

$$\frac{1}{\omega_{p1} \omega_{p2}} = b = R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)$$

$$\omega_{p2} = -\frac{1}{\omega_{p1} R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)} = -\frac{r_o (C_{gd1} + C_o)}{R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)}$$

$$\omega_{p2} = -\frac{C_{gd1} + C_o}{R_{in} (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)} \cong -\frac{1}{R_{in} (C_{gs1} + C_{gd1})} \quad \text{(with large } C_o)$$

Common-Source Amp Frequency Response

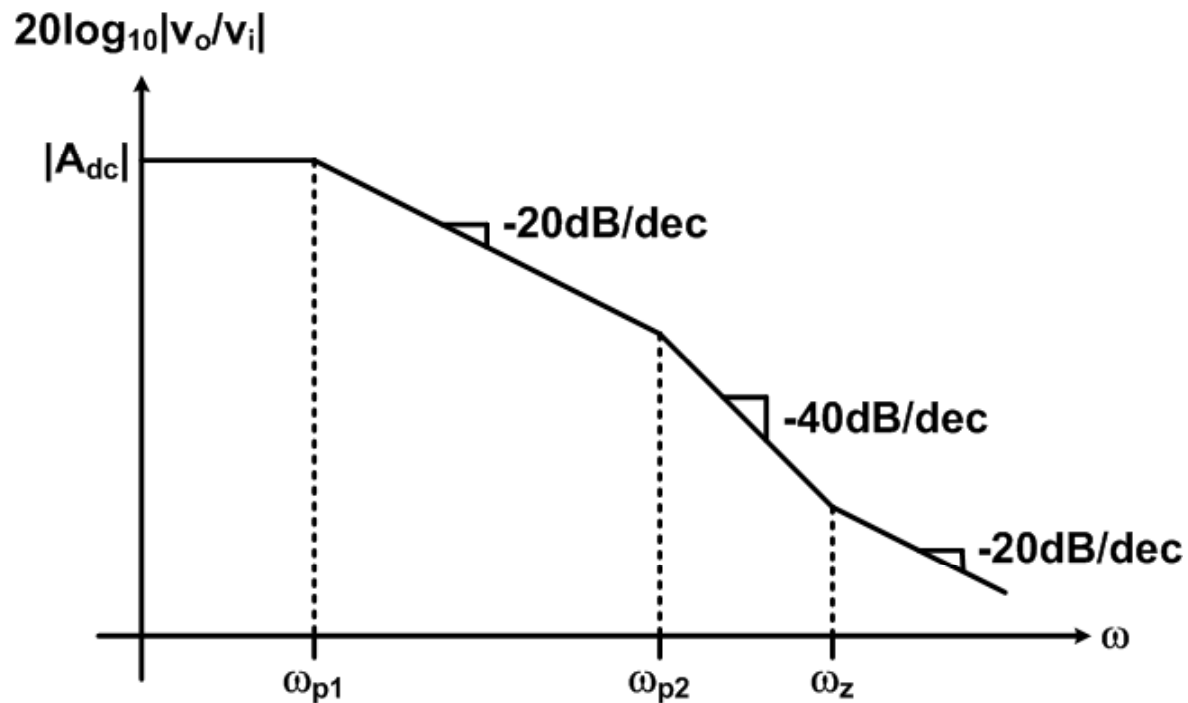

Large R_{in}

Small R_{in}

$$A_{dc} = -g_m r_o$$

$$\omega_z = \frac{g_{m1}}{C_{gd1}}$$

$$\omega_{p1} = -\frac{1}{R_{in} [C_{gs1} + C_{gd1} (1 + g_{m1} r_o)]}$$

$$\omega_{p2} \cong -\frac{g_{m1} C_{gd1}}{C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o}$$

$$\omega_{p1} = -\frac{1}{r_o (C_{gd1} + C_o)}$$

$$\omega_{p2} \cong -\frac{1}{R_{in} (C_{gs1} + C_{gd1})}$$

Next Time

- Single-Stage Amplifiers (cont.)
 - Common-Drain
 - Common-Gate
 - Cascode Stage
- Differential Pairs