


# Op Amps Conventional Topologies

Edgar Sánchez-Sinencio  
TI J. Kilby Chair Professor

Next we review the *conventional Op Amp Design frequency response compensation* techniques and also we introduced a simple LV Current-Mode based Op Amp using resistors as transconductors. Difference Differential Amplifiers are also introduced.



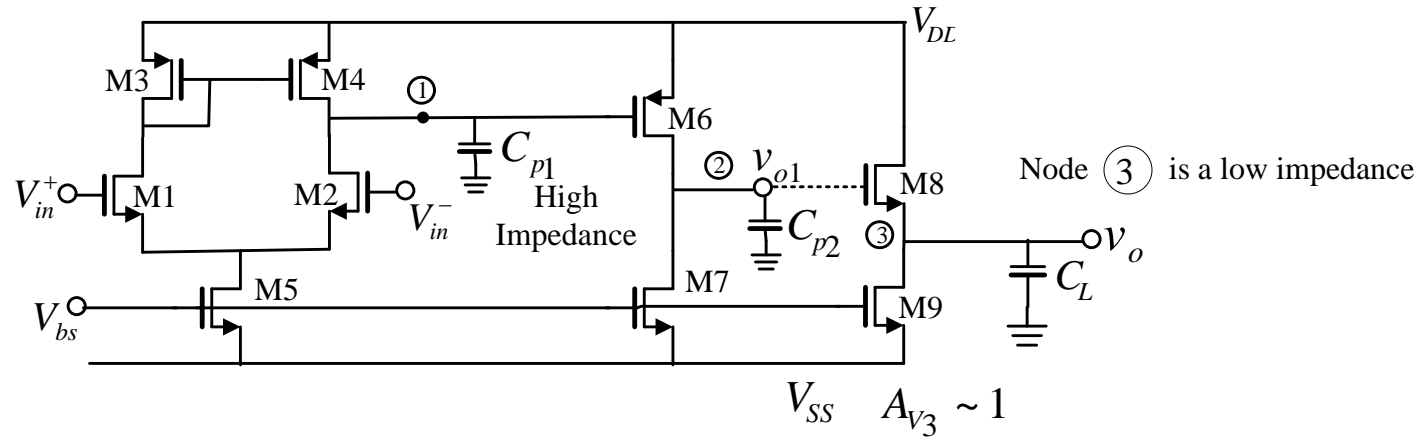
# UNCOMPENSATED CMOS OPERATIONAL AMPLIFIER



$$M1=M2; M3=M4$$

 


Ignoring zeros we can model this topology as:




$$A_{V1}(0) \cong \frac{g_{m1}}{g_{o1} + g_{o3}} \quad ; \quad A_{V2}(0) = \frac{-g_{m6}}{g_{o6} + g_{o7}} \quad ; \quad \omega_{p1} = \frac{g_{o2} + g_{o4}}{C_{p1}} \quad ; \quad \omega_{p2} = \frac{g_{o6} + g_{o7}}{C_{p2}}$$

$$A_{VT}(s) \cong \frac{A_{V1}(0)A_{V2}(0)A_{V3}(0)}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})(1 + s/\omega_{p3})} \quad ; \quad \omega_{p3} \cong \frac{g_{m8}}{C_L}$$

# *UNCOMPENSATED CMOS OPERATIONAL AMPLIFIER STABILITY ISSUES*

- The low frequency voltage gain is high enough for a number of applications. 
- The open loop poles are far from the origin, this can cause stability problems for closed loop applications. 
- Closed loop poles might end very close to the  $j\omega$  axis and some in the RHP. 
- How to tackle this stability problem will be discussed next.

# Two-Stage Uncompensated Amplifier

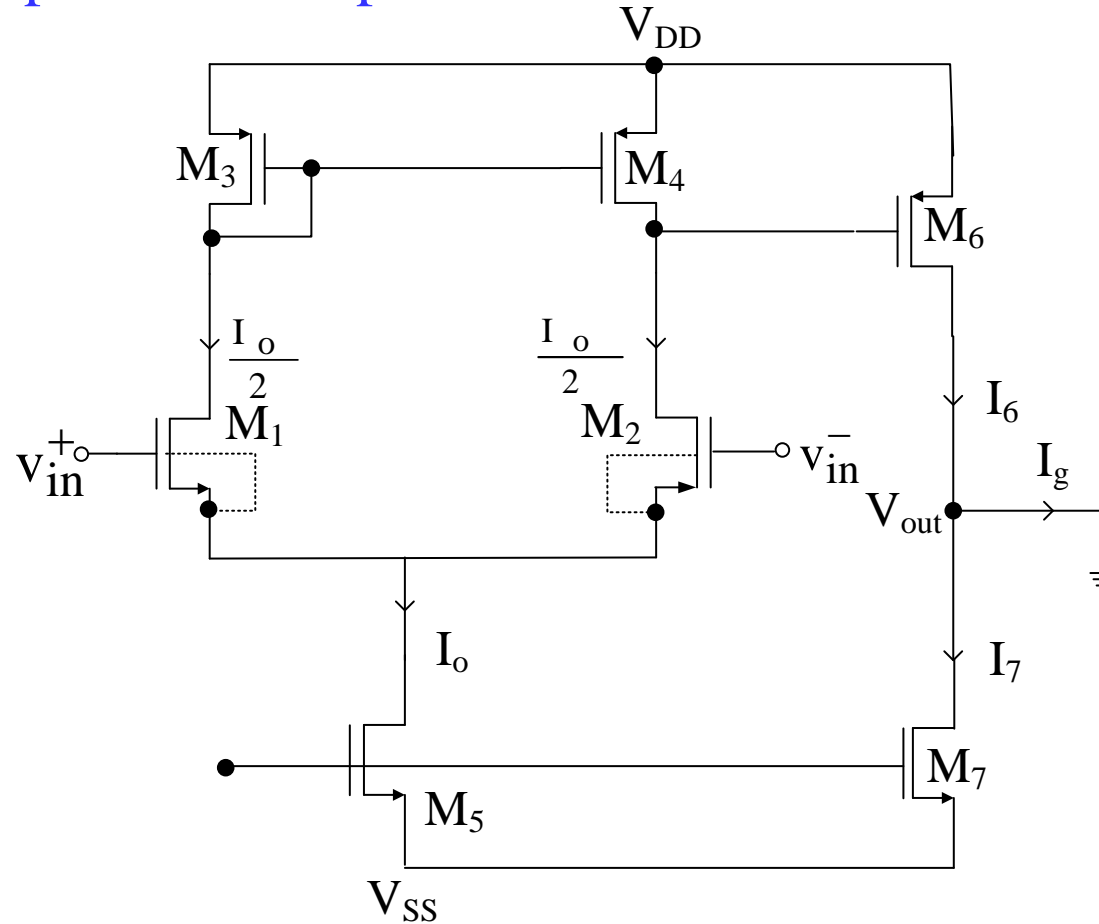

Uncompensated Operational Amplifier

–  $A_V = A_{V1}A_{V2} = \frac{g_{m2}}{g_{o2} + g_{o4}} \frac{g_{m6}}{g_{o6} + g_{o7}}$  Large voltage gain


– Poles are close to the  $j\omega$  axis causing stability problems







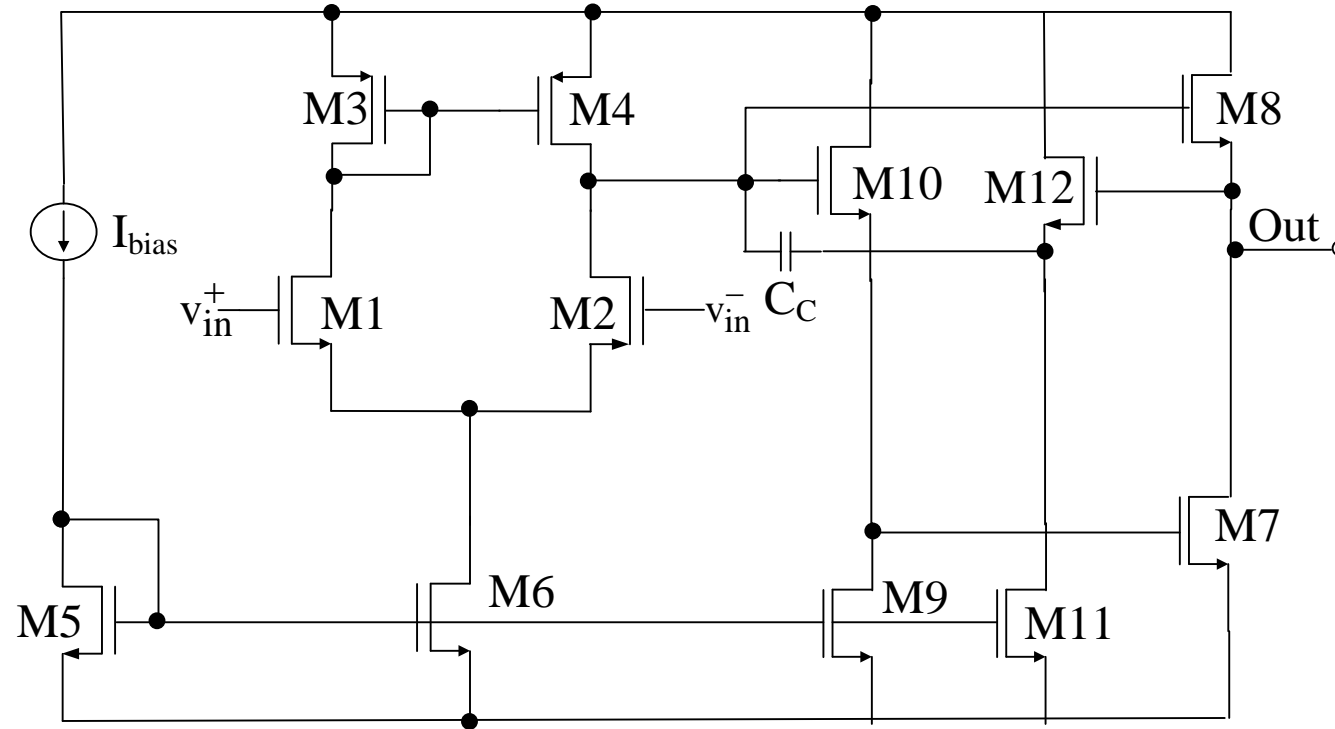
 
“Pole Splitting” can be carried out with a compensation capacitor feedback and a voltage buffer as shown below



Two-Stage amplifier with **source follower** compensation scheme

- Without M12 and M11 a zero in the PRH
- With buffer (**voltage follower**), zero is eliminated and pole sp  (due to  $C_C$ ) is kept.





# An Improved Frequency Compensation Technique for CMOS Operational Amplifiers using Current Buffers


**ECEN 607 (ESS)**

*Courtesy of Hatem Osman*

# Background.-
 
## Two-Stage Op-amp with Miller compensation

- The first stage is a differential-input/single-ended output stage, and the second stage is a class A or class AB inverting output stage.



- DC Gain**

$$A_{v,0} = -A_{v1}A_{v2}$$

$$A_{v1} = g_{m1}r_{o1}$$

$$A_{v2} = g_{m2}r_{o2}$$

- Transfer Function

- Pole/zero locations 
$$A_v = \frac{1 - \frac{C_c}{g_{m2}}s}{1 + (r_{o1}C_p + A_{v2}r_{o1}C_c + r_{o2}C_L)s + r_{o1}r_{o2}(C_pC_c + C_pC_L + C_cC_L)s^2}$$

$$s_z = \frac{g_{m2}}{C_c}$$

RHP zero

$$s_{p1} = -\frac{1}{r_{o1}C_p + A_{v2}r_{o1}C_c + r_{o2}C_L} \approx -\frac{1}{A_{v2}r_{o1}C_c}$$


Dominant Pole

$$s_{p2} = -\frac{r_{o1}C_p + A_{v2}r_{o1}C_c + r_{o2}C_L}{r_{o1}r_{o2}(C_pC_c + C_pC_L + C_cC_L)} \approx -\frac{g_{m2}}{C_L}$$

Non-dominant Pole

# Two-Stage Op-amp with Miller compensation

- Pole Splitting

 



- Pole/zero locations

$$S_z = \frac{g_{m2}}{C_c}$$

$$S_{p1} = -\frac{1}{A_{v2} r_{o1} C_c}$$

$$S_{p2} = -\frac{g_{m2}}{C_L}$$


- Pole-zero position diagram

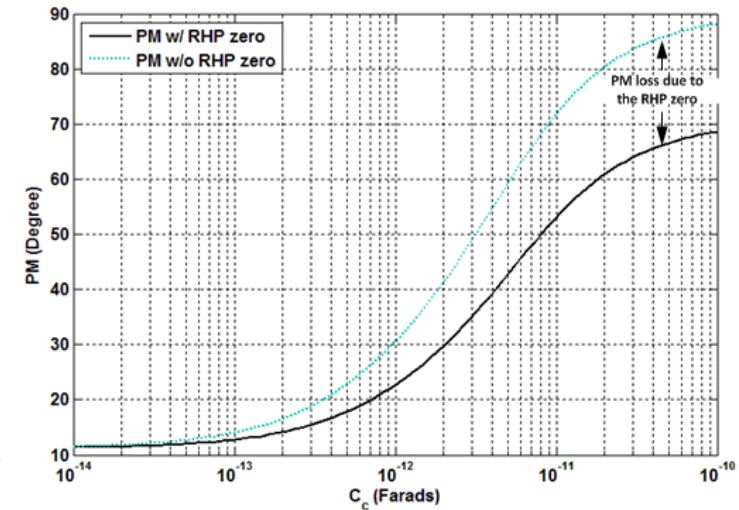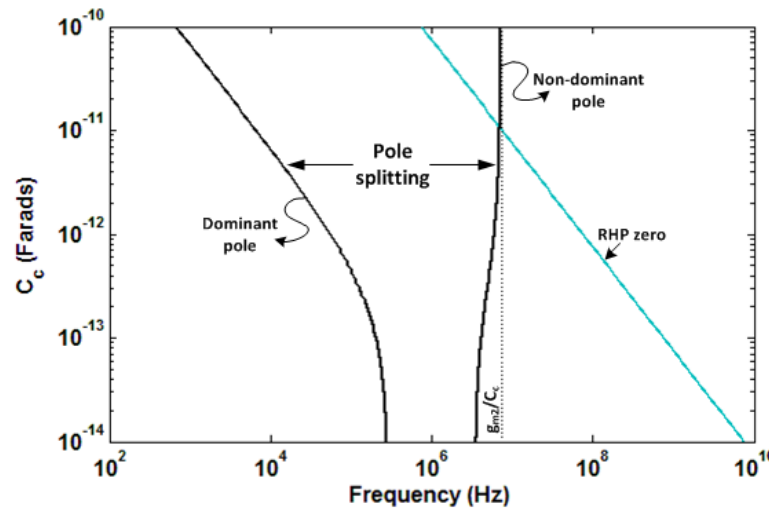

Increasing  $C_c$  achieves sufficient pole-splitting thus improving the PM. However, the larger  $C_c$  shifts the RHP zero to lower frequencies thus ruining the PM.
 
# Miller Op-amp with Nulling Resistance

- Introducing a small series resistance in series with  $C_c$  may cancel the RHP zero or shift it to the LHP.



- Pole/zero locations**

$$s_z = \frac{1}{\left(\frac{1}{g_{m2}} - R_c\right)C_c}$$

$$s_{p1} = -\frac{1}{A_{v2}r_{o1}C_c}$$

$$s_{p2} = -\frac{g_{m2}}{C_L}$$

$$R_c = 1/g_{m2}$$

No zero

$$R_c > 1/g_{m2}$$

LHP zero – Can be used to cancel the first non-dominant pole.


- Disadvantages:
  - To achieve a sufficient phase margin, second pole cross-over of the unity gain frequency should be avoided.

$$f_{p2} \gg GBW \rightarrow C_L \ll \frac{g_{m2}}{g_{m1}} C_c$$


Thus, the Op-amp stability is severely degraded for capacitive loads of the same order as compensation capacitor.
 
# Improved compensation technique

- The RHP zero is a result of the feed-forward path through  $C_c$ .



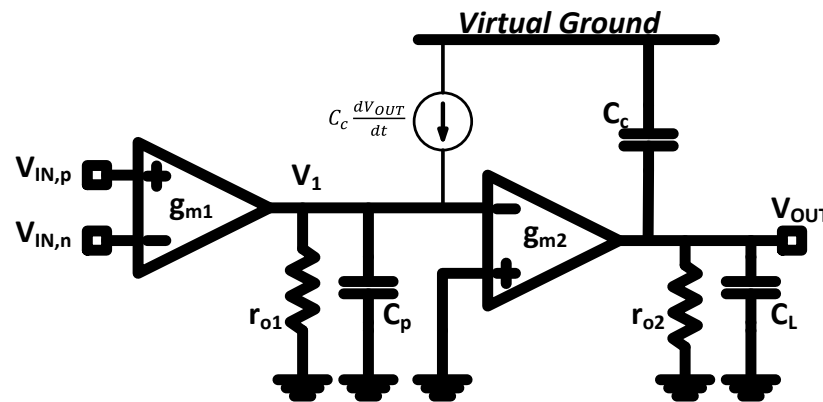
- The RHP zero can be eliminated if we cut the feed-forward path and make the compensation capacitor unidirectional.



An Improved Frequency Compensation  
Technique for CMOS Operational  
Amplifiers
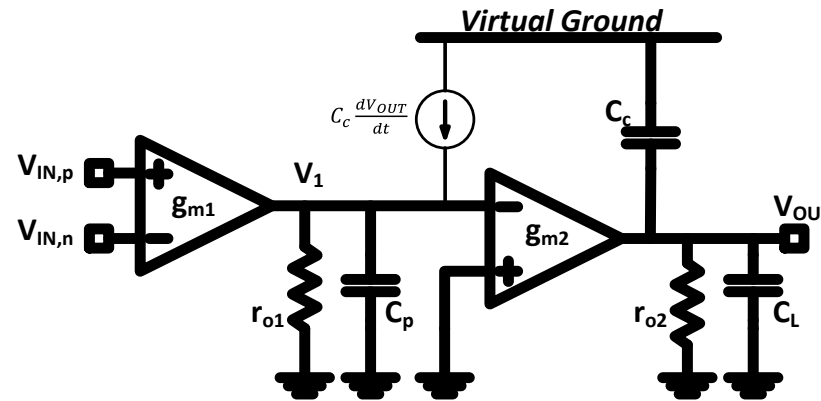
# Improved compensation technique

- The controlled current source injects AC current of  $C_c \frac{dV_{OUT}}{dt}$  to the output of the first stage.



- DC Gain**  
 $A_{v,0} = -A_{v1}A_{v2}$   
 $A_{v1} = g_{m1}r_{o1}$   
 $A_{v2} = g_{m2}r_{o2}$

- Transfer Function**

$$A_v = \frac{A_{v,0}}{1 + (r_{o1}C_p + A_{v2}r_{o1}C_c + r_{o2}(C_c + C_L))s + r_{o1}r_{o2}C_p(C_c + C_L)s^2}$$

- Pole/zero locations**

$$s_{p1} = -\frac{1}{r_{o1}C_p + A_{v2}r_{o1}C_c + r_{o2}(C_c + C_L)} \approx -\frac{1}{A_{v2}r_{o1}C_c} \quad \text{Dominant Pole}$$

$$s_{p2} = -\frac{r_{o1}C_p + A_{v2}r_{o1}C_c + r_{o2}(C_c + C_L)}{r_{o1}r_{o2}C_p(C_c + C_L)} \approx -\frac{g_{m2}C_c}{C_p(C_c + C_L)} \quad \text{Non-dominant Pole}$$

- To achieve sufficient PM**

$$f_{p2} \gg GBW \rightarrow C_L \ll \frac{g_{m2}C_c^2}{g_{m1}C_p}$$

# Improved compensation technique

- Numerical example

Miller compensation with nulling resistance	Improved compensation technique
<b>Dominant pole</b> $\omega_d = \frac{1}{g_{m2}r_{o1}r_{o2}C_c}$	<b>Dominant pole</b> $\omega_d = \frac{1}{g_{m2}r_{o1}r_{o2}C_c}$
<b>Non-dominant pole</b> $\omega_{nd} = \frac{g_{m2}}{C_L}$	<b>Non-dominant pole</b> $\omega_{nd} = \frac{g_{m2}C_c}{C_p(C_c+C_L)}$
<b>Gain-bandwidth product</b> $GBW = \frac{g_{m1}}{C_c}$	<b>Gain-bandwidth product</b> $GBW = \frac{g_{m1}}{C_c}$
<b>Phase margin</b> $PM = 90 - \tan^{-1}\left(\frac{GBW}{\omega_{nd}}\right)$	<b>Phase margin</b> $PM = 90 - \tan^{-1}\left(\frac{GBW}{\omega_{nd}}\right)$

- If  $\frac{g_{m2}}{g_{m1}} = 10$ ,  $C_c = 5 \text{ pF}$ ,  $C_p = 0.5 \text{ pF}$ , and  $\frac{\omega_{nd}}{GBW} \geq 4$  for  $PM > 75^\circ$


$$C_L \leq \frac{GBW}{\omega_{nd}} \frac{g_{m2}}{g_{m1}} C_c \rightarrow C_L \leq 12.5 \text{ pF}$$

$$C_L \leq \frac{GBW}{\omega_{nd}} \frac{g_{m2}}{g_{m1}} \frac{C_c^2}{C_p} \rightarrow C_L \leq 125 \text{ pF}$$


- The improved technique offers an order of magnitude improvement in capacitive load capability for the same performance.
 
# Circuit Implementation

- **Miller compensation with nulling resistance.**




- **Improved compensation technique.**

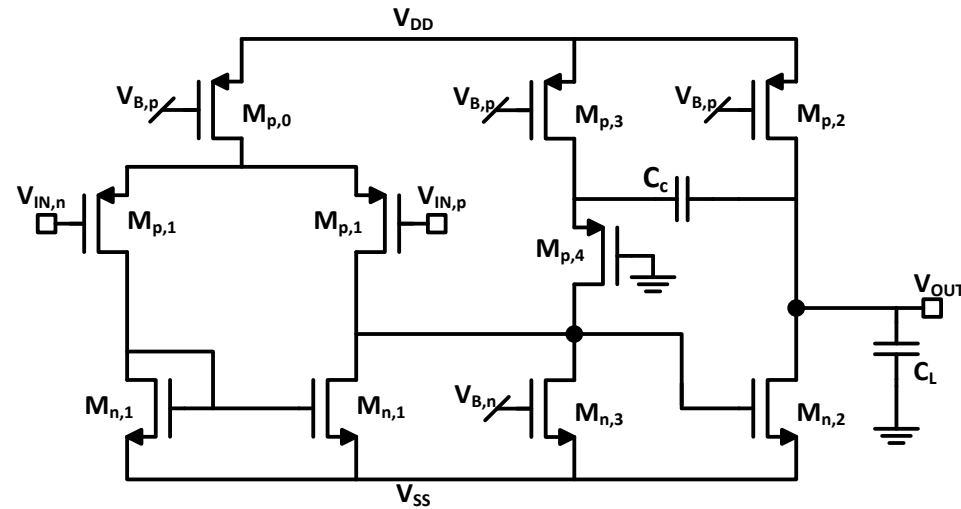



 
# Other performance parameters- PSR


- **Miller compensation with nulling resistance.**



 
$$\frac{V_{OUT}}{V_{SS}} = \frac{1 + sA_{v2}C_c r_{o1}}{g_{m1}g_{m2}r_{o1}r_{o2}}$$



- **Improved compensation technique.**

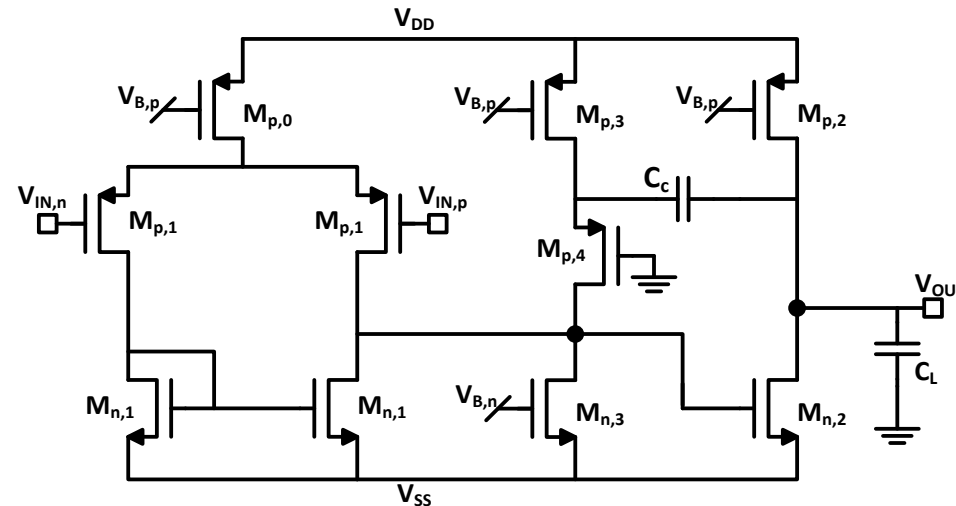

 
$$\frac{V_{OUT}}{V_{SS}} = \frac{1 + sC_p r_{o1}}{g_{m1}g_{m2}r_{o1}r_{o2} \left(1 + \frac{s}{GBW}\right)}$$



• **Better PSR at high frequencies.**
 
# Design Example – Miller Compensation

- Design an OTA with  $GBW > 5\text{MHz}$ ,  $C_L=10\text{pF}$ ,  $PM>70$ , and  $SR > 2\text{ V}/\mu\text{s}$ .



- Choose  $C_c=C_L/2=5\text{ pF}$ .
- $GBW > 5\text{MHz}$   
 $GBW = \frac{g_{m1}}{C_c} \rightarrow g_{m1} \geq 157\ \mu\text{S}$
- $SR > 2\text{ V}/\mu\text{S}$   
 $SR = \frac{I_{p,0}}{C_c} \rightarrow I_{p,0} \geq 20\ \mu\text{A}$
- $PM > 70^\circ$   
 $PM = 90 - \tan^{-1}\left(\frac{GBW}{\omega_{nd}}\right) \rightarrow \omega_{nd} \geq 2.7\text{GB}$

Let

$$\omega_{nd} = 3 \times GBW = \frac{g_{m2}}{C_L} \rightarrow \frac{g_{m2}}{g_{m1}} = 3 \frac{C_L}{C_c} = 6$$


Then

$$g_{m2} = 6g_{m1} \cong 1\text{ mS} \rightarrow I_{p,2} = 3I_{p,0}$$


- Choose  $R_c > 1/g_{m2}$

$$R_c \geq 1\text{ K}\Omega$$


# Design Example – Miller Compensation

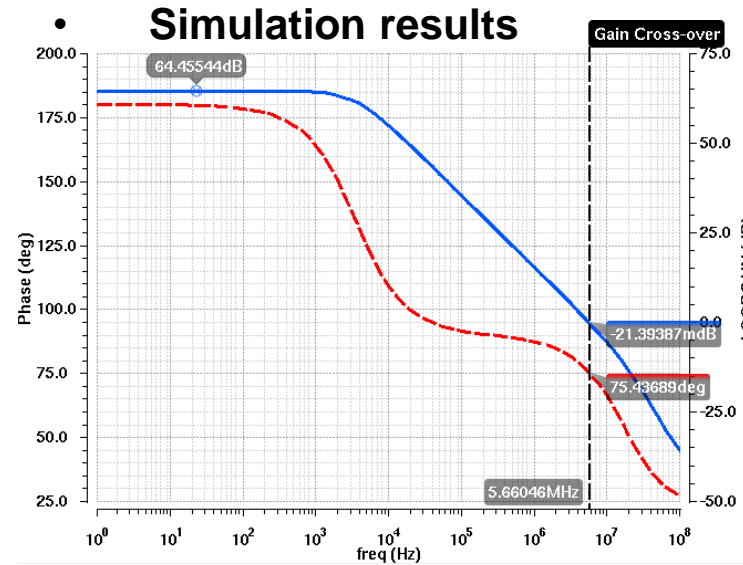


*OL Transfer function*

 

*Negative supply rejection*

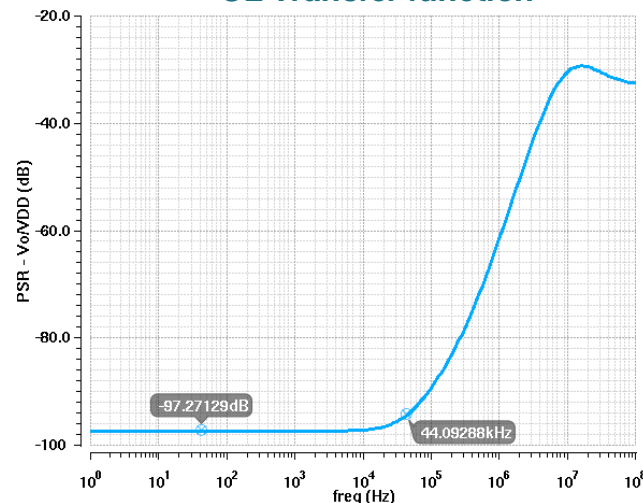


*Positive supply rejection*

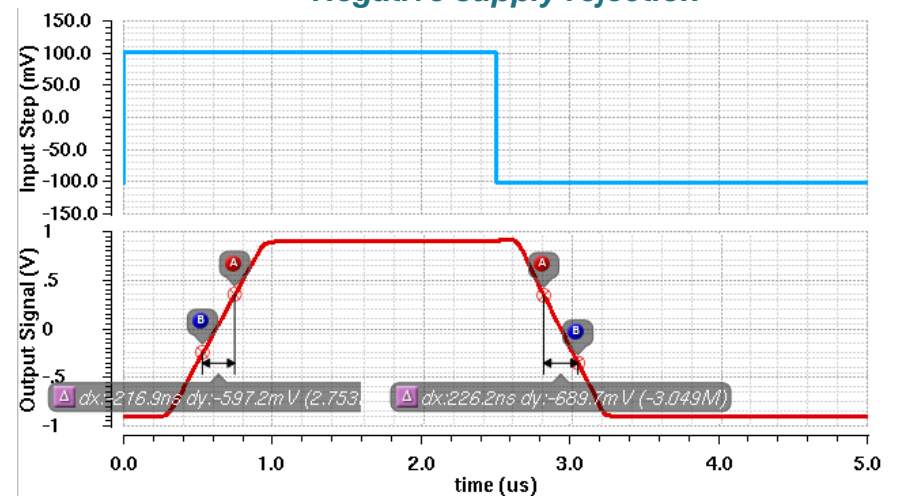

*Transient step response*

# Design Example – Miller Compensation


- Capacitive load driving capability

 

- $PM > 70^\circ$  for  $C_L < 15$  pF.
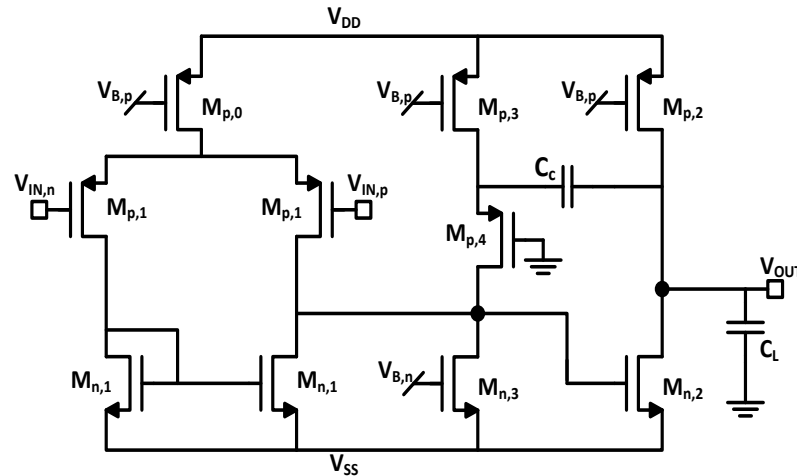
# Design Example – Improved Compensation

- Design an OTA with  $GBW > 5\text{MHz}$ ,  $C_L=10\text{pF}$ ,  $PM>70$ , and  $SR > 2\text{ V}/\mu\text{s}$ .



- Choose  $C_c=C_L/2= 5\text{ pF}$ .
- $GBW > 5\text{MHz}$

$$GBW = \frac{g_{m1}}{C_c} \rightarrow g_{m1} \geq 157 \mu\text{S}$$

- $SR > 2\text{ V}/\mu\text{s}$

$$SR = \frac{I_{p,0}}{C_c} \rightarrow I_{p,0} \geq 20 \mu\text{A}$$

In order to make the current transformer biased during slewing interval

$$I_{p3} > I_{p0} \rightarrow I_{p,3} = 30 \mu\text{A}$$

- $PM > 70^\circ$

$$PM = 90 - \tan^{-1} \left( \frac{GBW}{\omega_{nd}} \right) \rightarrow \omega_{nd} \geq 2.7GBW$$

Let


$$\text{Then } \omega_{nd} = 3 \times GBW = \frac{g_{m2}C_c}{C_p(C_c+C_L)} \rightarrow \frac{g_{m2}}{g_{m1}} = 0.3$$

$$g_{m2} = 0.3g_{m1} \cong 52 \mu\text{S} \rightarrow I_{p,2} = 0.3I_{p,0}$$


- ✓ Let's use  $g_{m2}=6g_{m1}$  like the miller Op-amp to make a comparison between the capacitive driving capability.
- ✓ For the same capacitive load driving capability, the second stage will consume less current making it suitable for low power applications

# Design Example – Improved Compensation


- Simulation results

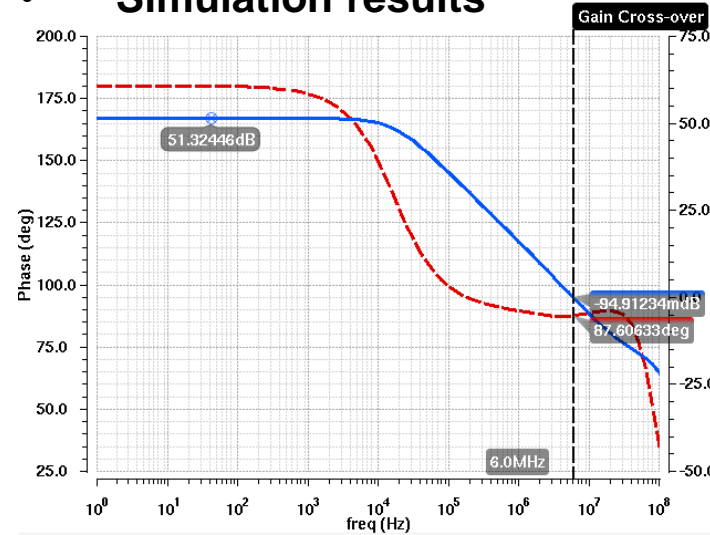


OL Transfer function

 

Negative supply rejection

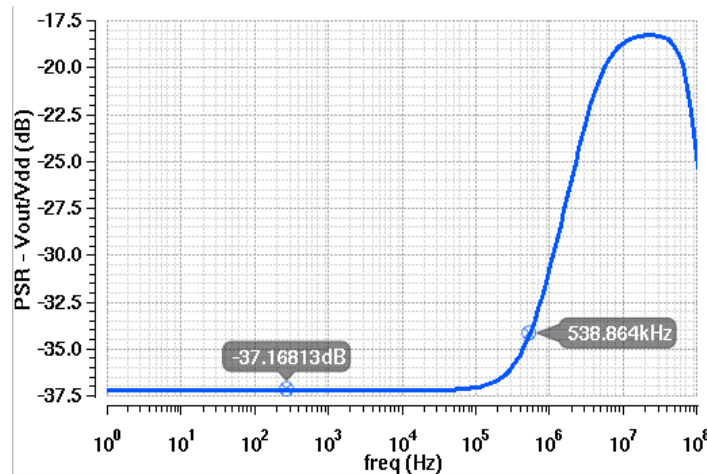


Positive supply rejection

 

Transient step response

# Design Example – Improved Compensation

- **Capacitive load driving capability**

 

- $PM > 70^\circ$  for  $C_L < 100$  pF.


# Design Example – Improved Compensation

- Summary of Simulation results

Parameter	Spec	Miller Compensation	Improved Compensation
GBW	> 5MHz	5.5 MHz	6 MHz
PM	> 70°	75°	87.6°
SR <sup>+</sup>	> 2 V/μs	2.75 V/μs	3 V/μs
SR <sup>-</sup>	> 2 V/μs	3 V/μs	3.15 V/μs
PSR <sup>-</sup>	-	-65.6 dB At (0-3.1 kHz)	-51.9 dB At (0-245.4 kHz)
PSR <sup>+</sup>	-	-97.2 dB At (0-44 kHz)	-37.2 dB At (0-538.9 kHz)
DC gain	-	64.5 dB	51.3 dB
Current consumption	-	80 μA	110 μA
Capacitive load driving capability	-	PM > 70° for C <sub>L</sub> < 15 pF	PM > 70° for C <sub>L</sub> < 100 pF



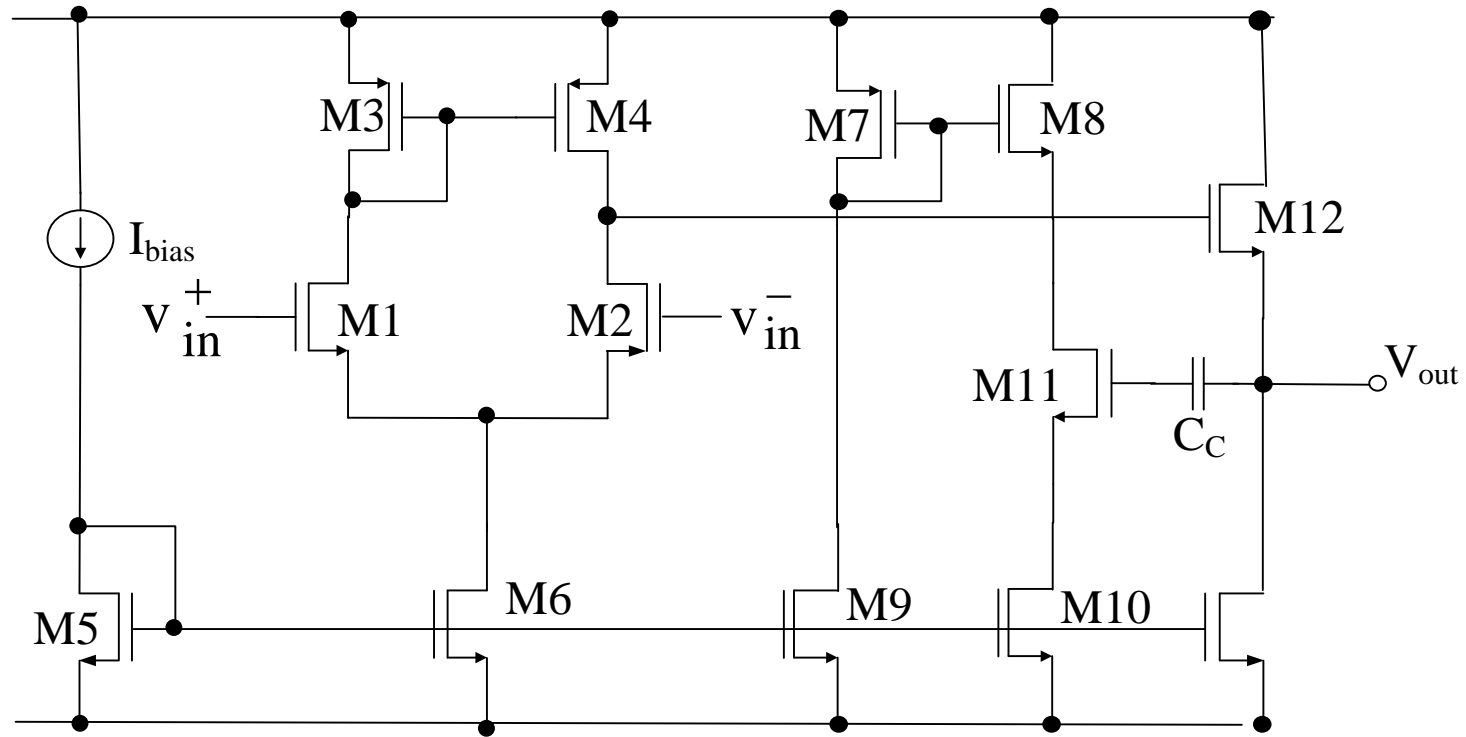
Using another **current buffer Op Amp topology**.



Two-Stage amplifier with Current Buffer compensation scheme.

- Improve SR at the expense of power consumption.
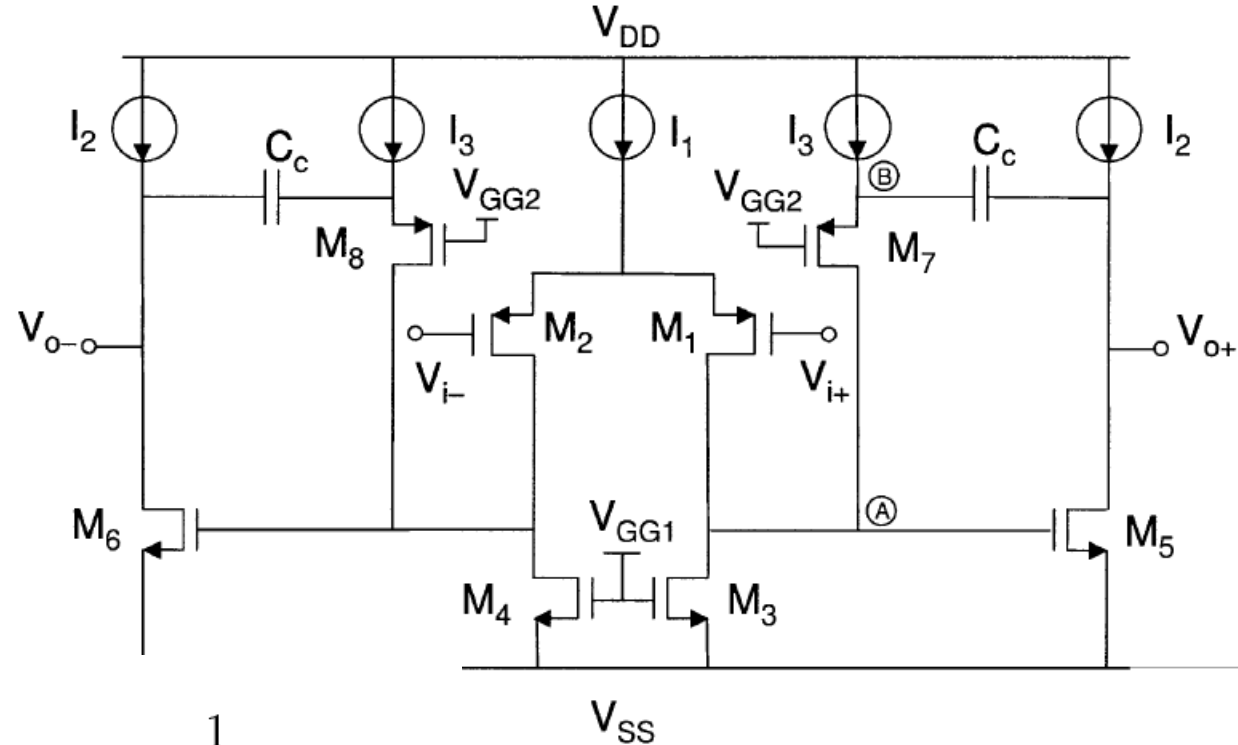
## Differential Output Two Stage Amp with a capacitor compensation with a current Buffer ( Common Gate)




$$p_1 \approx -\frac{1}{g_{m5} R_L R_{oA} C_c}$$

$$p_2 \approx -\frac{g_{m5}}{(C_L + C_c)} \frac{C_c}{C_A}$$

$$z \approx -\frac{g_{m7}}{C_B + C_c}$$

$$g_{m7} \rightarrow \infty \text{ then } p_3 \rightarrow \infty$$

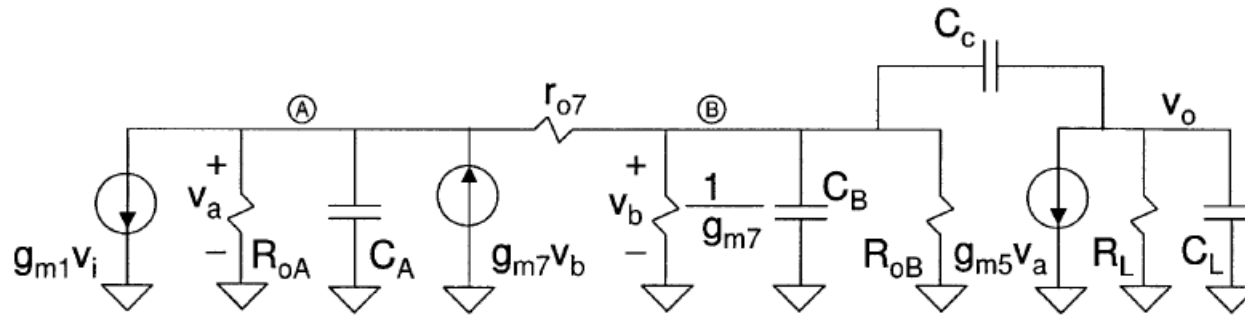
# Differential mode half circuit of previous topology



Element	Fig. 1(a)
$R_{oA}$	$r_{o1}    r_{o3}$
$C_A$	$C_{gs5} + C_{db1} + C_{db3} + C_{db7}$
$R_{oB}$	$\infty$ *
$C_B$	$C_{gs7} + C_{sb7}$ **
$R_L$ ***	$r_{o5}$
$C_L$ ****	$C_{db5}$

Note that this and previous structure are fully differential but this approach could be used for single output topologies.
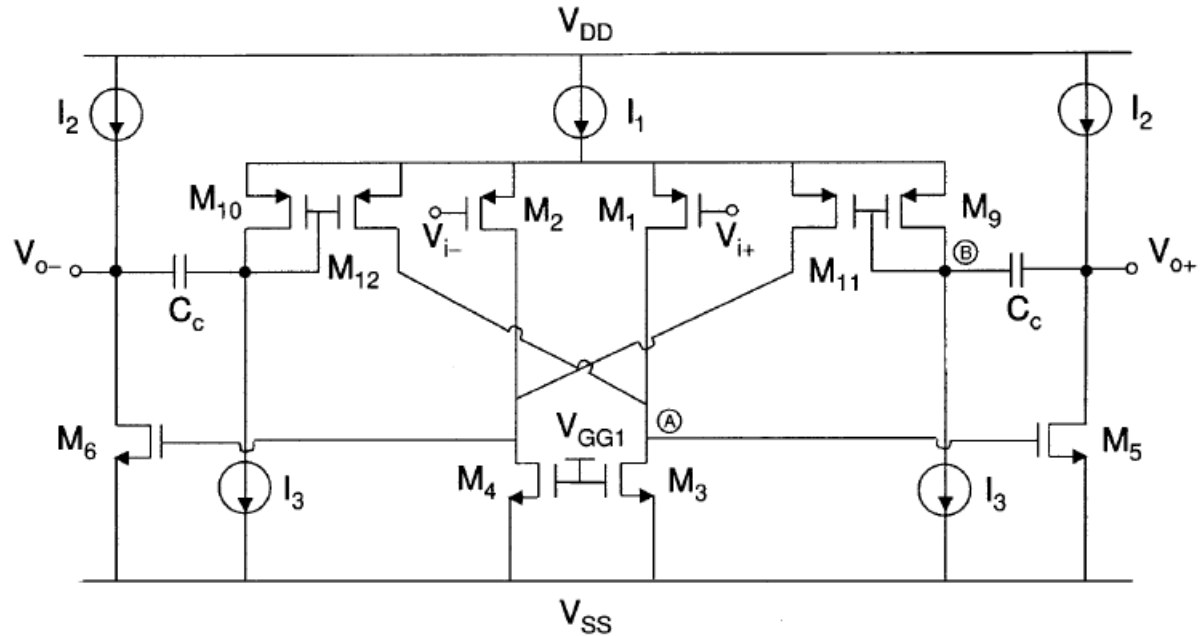
### Compensation using a current buffer ( current gain)



**Note that the current-mirror introduces an extra inversion which must be taken into consideration for the single ended version.**

P.J. Hurst, Lewis, S.H. ; Keane, J.P. ; Aram, F. ; Dyer, K.C.

“ Miller compensation using current buffers in fully differential CMOS two-stage operational amplifiers” *IEEE Transactions on Circuits and Systems I*, Volume: 51 , Issue: 2, Feb. 2004

Element	
$R_{oA}$	$r_{o1}    r_{o3}    r_{o11}$
$C_A$	$C_{gs5} + C_{db1} + C_{db3} + C_{db11}$
$R_{oB}$	$r_{o9}^*$
$C_B$	$C_{gs9} + C_{gs11} + C_{db9}^{**}$
$R_L^{***}$	$r_{o5}$
$C_L^{****}$	$C_{db5}$


$$z \approx -\frac{g_{m11}}{C_B + C_c}$$

Besides the above zero the amp has three poles


## Elements of Current-Mirror Cc compensated

*Note that the common-gate and current mirror topologies under ideal case are almost identical, however in practice the one using current-mirrors is more power hungry and has a larger parasitic capacitance  $C_B$*
 
# Summary for Two Stage Op Amp Architecture Designs




 - Roots close to the  $j\omega$  axis for uncompensated



- Potentially unstable for some values of  $C_L$

$$I_{\text{bias}} = C_L S_R * 2.5$$

 


- Improved output stage optimal bias of  $Q_6$  and  $Q_7$


- No significant change of pole locations.

$$A_V(0) \rightarrow +$$

$$A_V(\omega) \rightarrow -$$

 

 
Pole splitting  $\Rightarrow$  one dominant pole




$z_1$  Phase deteriorates phase margin

The good and the bad news

 Two possible solutions to cancel  $z_1$  and keeping  $s_{p2} > \omega_t = \text{GBW}$  and  $s_{p1}$  small



Internally Compensated  
with  $R_C C_C$

 

Internally Compensated  
with unity gain buffer  
( $Q_{10}, Q_{11}$ )

## Operational Amplifier (conventional) Architectures.

*Reader.- See the internally Op Amp compensated with current gain buffer in previous pages*

# Folded Cascode Op Amp

- ❑ Compared to two-stage Op Amp, **folded cascode Op Amp** has:
  - Improved input common-mode range (ICMR)
  - Improved power supply rejection (PSR)
  - Push-pull output stage
  - Self compensation


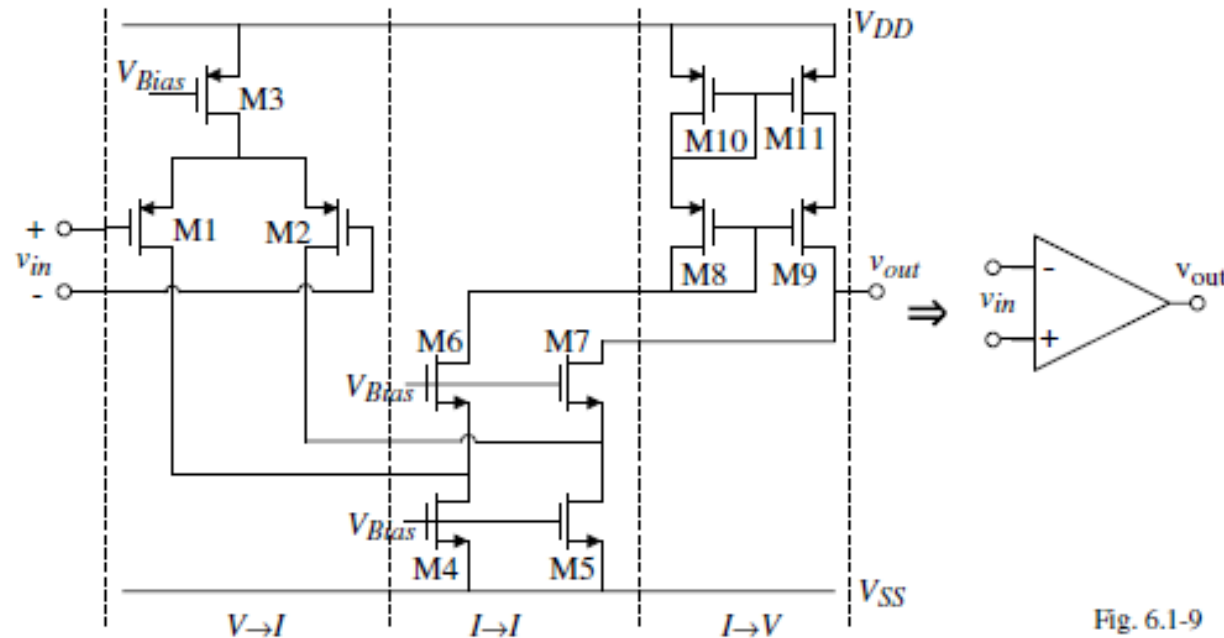


Fig. 6.1-9

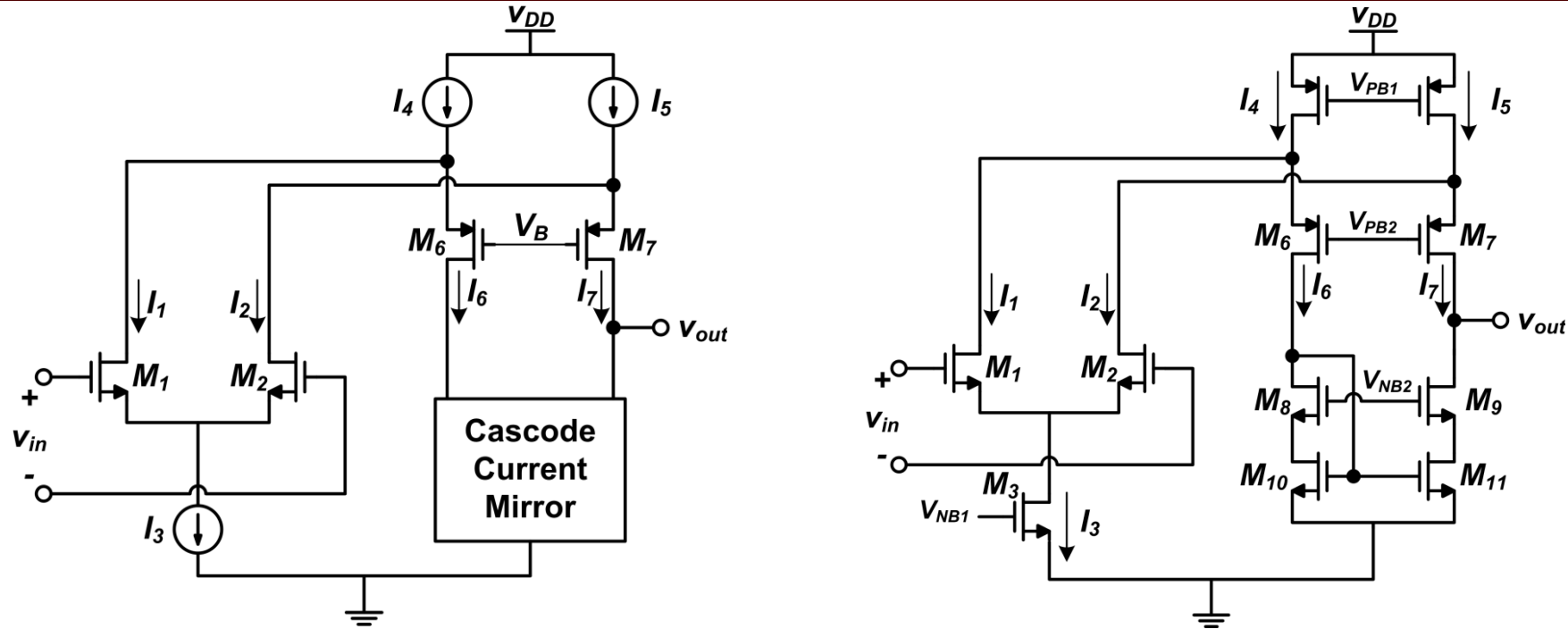**Folded-cascode Op Amp** broken into stages  
[Allen]




# Folded Cascode OpAmp



- The extended ICMR is achieved
- The bias currents  $I_4$  and  $I_5$  should be designed such that  $I_6$  and  $I_7$  never goes to zero (i.e.  $I_{4,5} = 1.2I_3 \rightarrow 1.5I_3$ )
- Poor noise performance: In addition to the input transistors, transistors  $M_{4,5}$  and  $M_{10,11}$  generate significant current noise

# Small Signal Analysis

 

$R_A$  and  $R_B$  are the resistances looking into the sources of  $M_6$  and  $M_7$

$$R_A = \frac{r_{ds6} + 1/g_{m10}}{1 + g_{m6}r_{ds6}} \approx \frac{1}{g_{m6}} \text{ and } R_B = \frac{r_{ds7} + R_{II}}{1 + g_{m7}r_{ds7}} \approx \frac{R_{II}}{g_{m7}r_{ds7}} \text{ where } R_{II} = g_{m9}r_{ds9}r_{ds11}$$

The currents  $i_7$  and  $i_{10}$  is expressed as

$$i_7 = \frac{g_{m2}(r_{ds2} \parallel r_{ds5})}{R_B + (r_{ds2} \parallel r_{ds5})} \frac{v_{in}}{2} = \frac{g_{m2}}{k+1} \frac{v_{in}}{2} \text{ where } k = \frac{R_B}{r_{ds2} \parallel r_{ds5}}$$

$$i_{10} = -\frac{g_{m1}(r_{ds1} \parallel r_{ds4})}{R_A + (r_{ds1} \parallel r_{ds4})} \frac{v_{in}}{2} \approx -g_{m1} \frac{v_{in}}{2}$$

Thus, the transfer function can be found as follows

$$\frac{v_{out}}{v_{in}} = \left( \frac{g_{m1}}{2} + \frac{g_{m2}}{2(k+1)} \right) R_{out} = \left( \frac{2+k}{2+2k} \right) g_{m1} R_{out}$$

Where

$$R_{out} = g_{m9}r_{ds9}r_{ds11} \parallel g_{m7}r_{ds7}(r_{ds2} \parallel r_{ds5})$$

Where  $k$  is the low-frequency unbalance factor

# Frequency Response

- The frequency response is dominated primarily by the output pole due to the high output impedance

$$P_{out} = \frac{-1}{R_{out}C_{out}}$$

- In order to have sufficient phase margin, all other pole should be located will above the GBW

Pole at source of  $M_6$  (Folding node)

$$P_A = -\frac{1}{R_A(C_{gs}+2C_{bd})} \approx -\frac{g_{m6}}{C_{gs}+2C_{bd}}$$

Pole at source of  $M_7$  (Folding node)

$$P_B = -\frac{1}{R_B(C_{gs}+2C_{bd})} \approx -\frac{g_{m7}}{C_{gs}+2C_{bd}}$$

Pole at drain of  $M_6$

$$P_6 = -\frac{g_{m10}}{2C_{gs}+2C_{bd}}$$

Pole at source of  $M_8$

$$P_8 = -\frac{g_{m8}r_{ds8}g_{m10}}{C_{gs}+C_{bd}}$$

Pole at source of  $M_9$

$$P_9 = -\frac{g_{m9}}{C_{gs}+C_{bd}}$$

- **Remarks:**

We assumed  $R_B \approx 1/g_{m7}$  because at high frequency, where this pole has influence,  $C_{out}$  shunts the drain of  $M_7$  to ground.

# Power Supply Rejection

□ The following model is used to calculate the negative PSR


- The gate, source and drain of  $M_{11}$  varies with  $V_{SS}$
- The gate, source of  $M_9$  varies with  $V_{SS}$

□ The transfer function  $V_{out}/V_{ss}$  can be found as

$$\frac{V_{out}}{V_{ss}} = \frac{sC_{gd9}R_{out}}{sC_{out}R_{out}+1}$$

□  $PSRR^-$  can be calculated


$$PSRR^- = \frac{A_v}{|V_{out}/V_{ss}|}$$

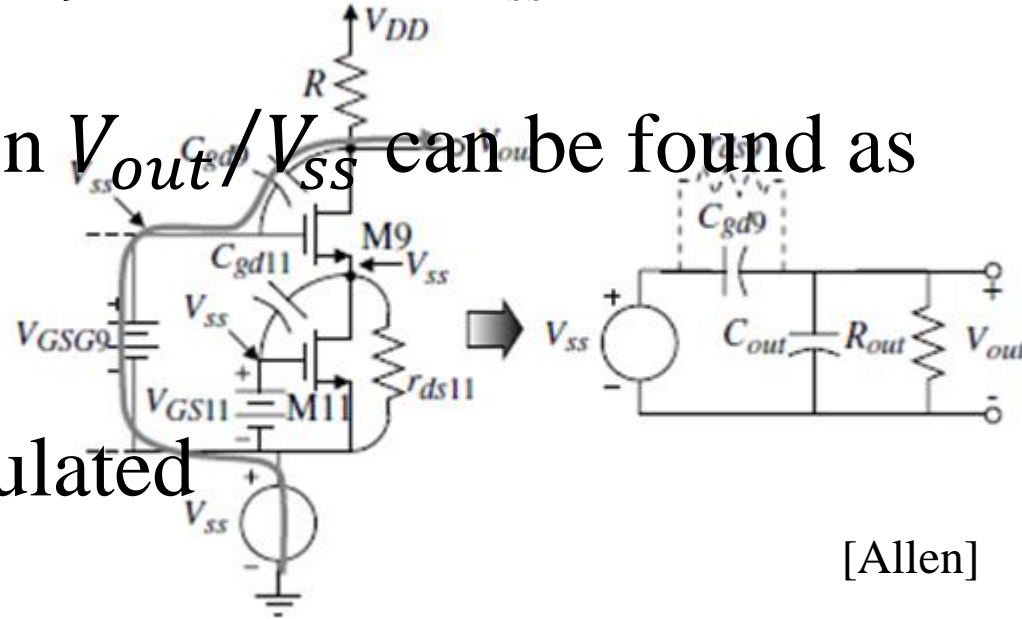

[Allen]



Output stage of folded cascode OpAmp

# Power Supply Rejection

 

- ❑ At low frequency, we assume that other source of  $V_{SS}$  injection becomes significant
- ❑ Low frequency  $PSRR^-$  is at least as large as the magnitude of the differential voltage gain  $A_v$
- ❑  $PSRR^+$  can be derived similarly: the primary source of injection is through

# Slew Rate

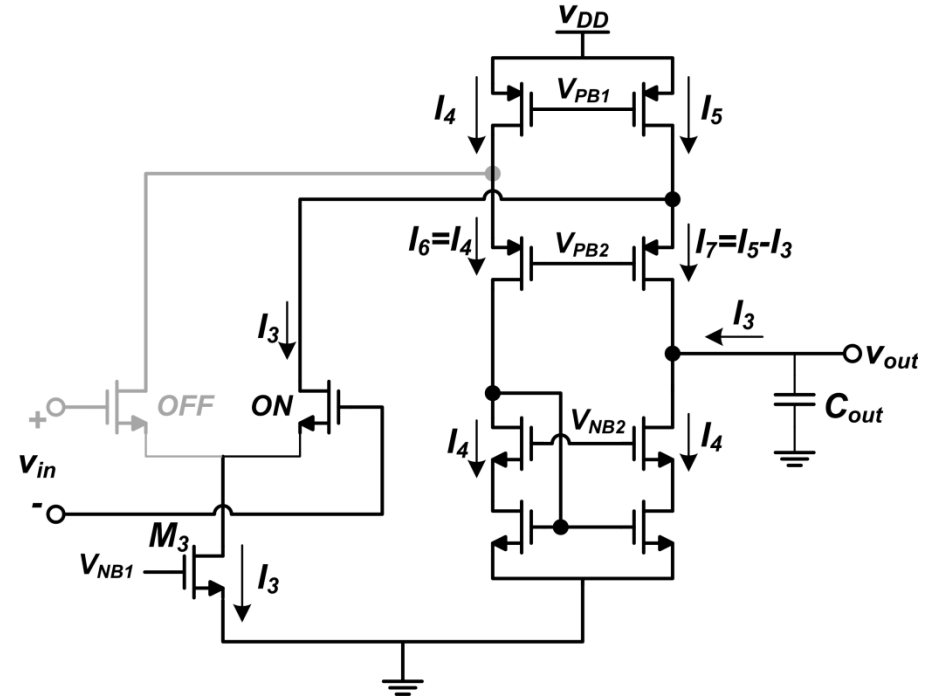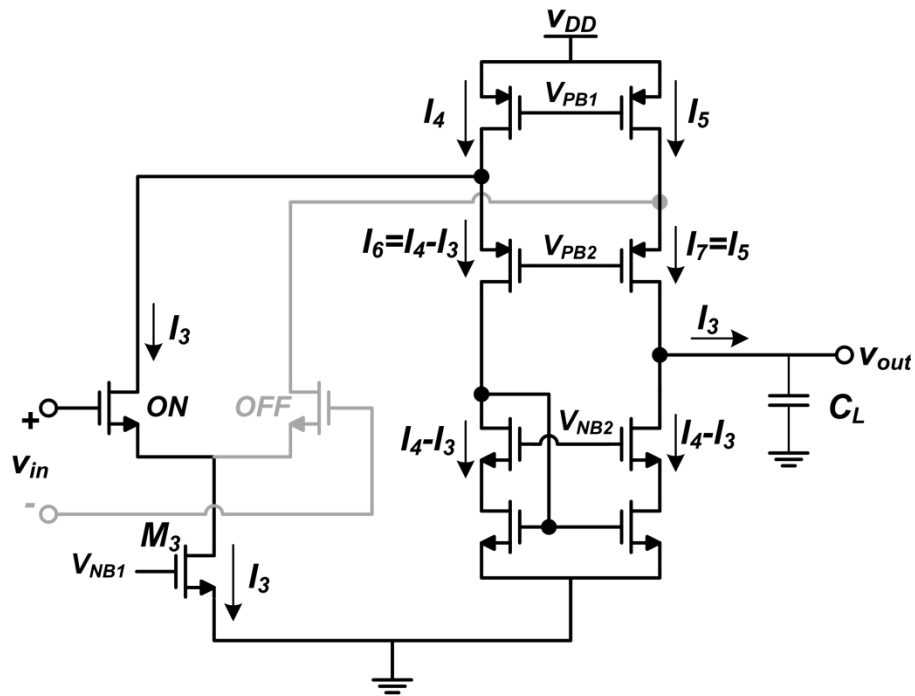


$$SR^+ = SR^- = \frac{I_3}{C_L}$$

□ The bias currents  $I_{4,5}$  should be designed such that  $I_{6,7}$  never goes to zero

$$I_{4,5} = 1.2I_3 \rightarrow 1.5I_5$$

# Maximum Available Output Swing

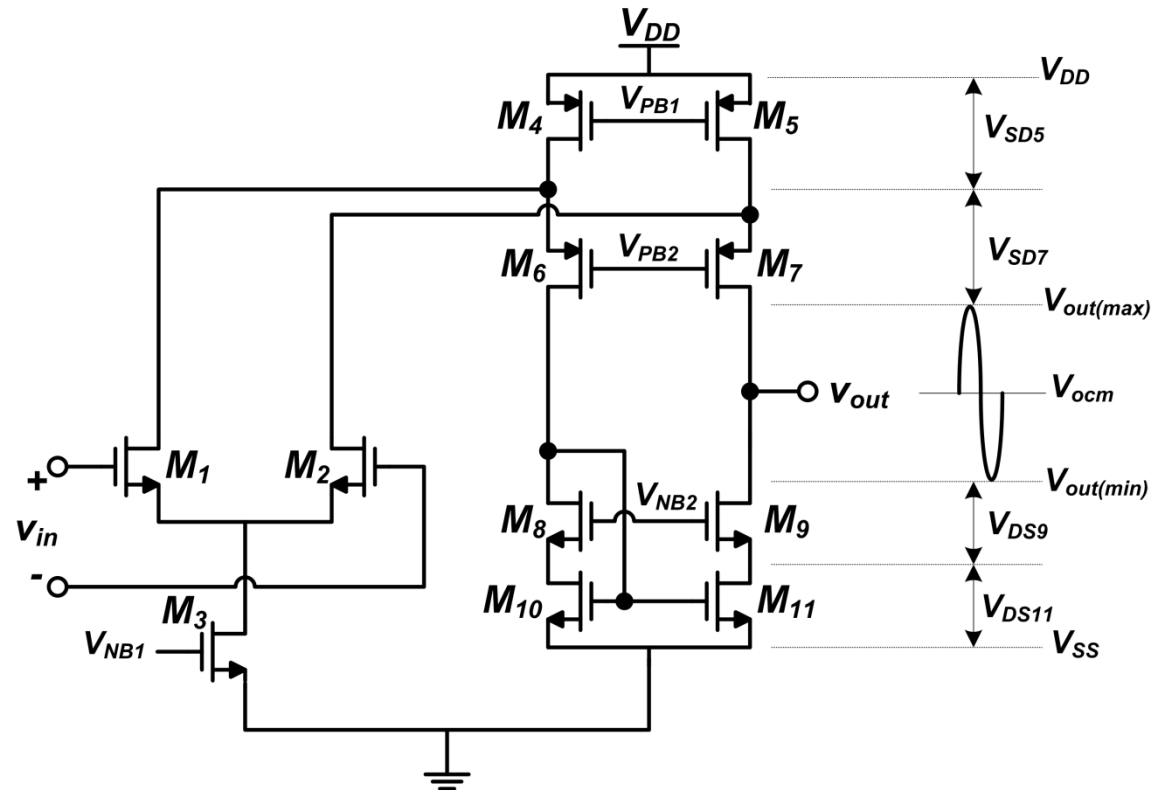

$$V_{out(max)} = V_{DD} - V_{SD5} - V_{SD7}$$

$$V_{out(min)} = V_{SS} + V_{DS9} + V_{DS11}$$

- The output common mode level  $V_{ocm}$  is often dictated by the circuit that interface with the amplifier (e.g.  $V_{ocm} = V_{DD}/2$ )


# Noise Analysis

- ❑ The noise current of  $M_1$ ,  $M_4$  and  $M_{10}$  goes directly to the output
- ❑ At low and medium frequencies, noise contribution of the cascode transistors ( $M_6$  and  $M_8$ ) can be neglected
- ❑ Total output noise current becomes

$$\overline{i_{out}^2} = 8KT\gamma(g_{m1} + g_{m4} + g_{m10})$$

- ❑ Input referred noise density
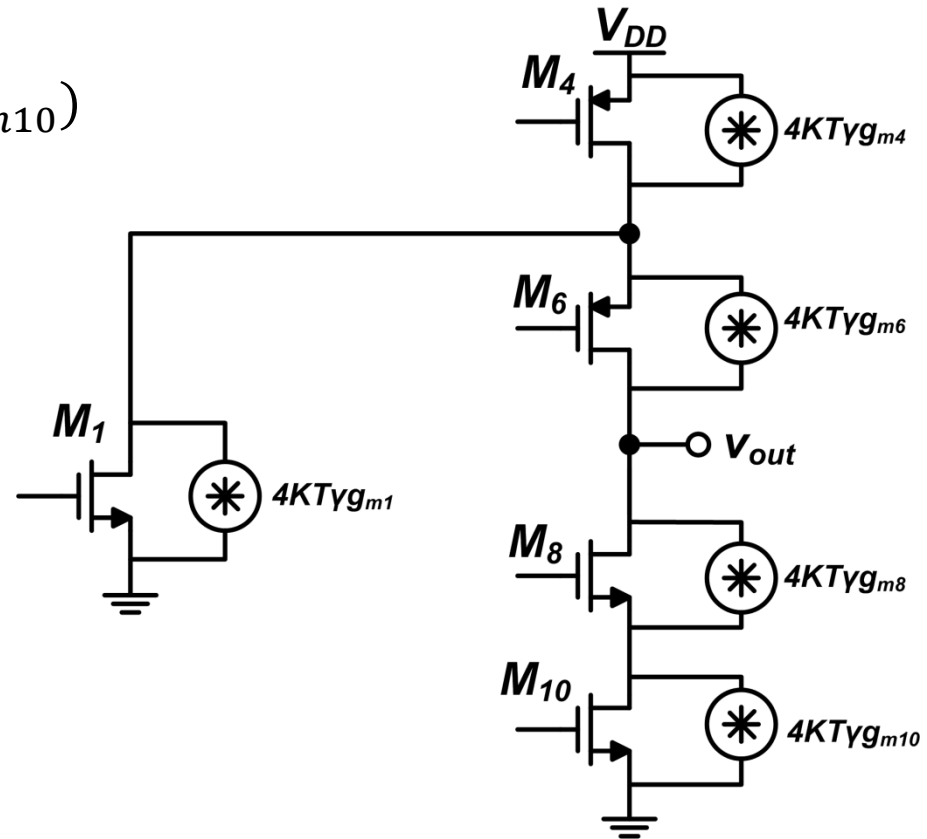
$$\overline{v_{n,in}^2} = \frac{8KT\gamma}{g_{m1}} \left( 1 + \frac{g_{m4}}{g_{m1}} + \frac{g_{m10}}{g_{m1}} \right)$$



Half circuit model



# Folded Cascode Op Amp Design Procedure

□ Design approach for the folded cascode Op Amp using long-channel model

Step	Relationship	Design Equation/Constraint	Comments
1	Slew Rate	$I_3 = SR \cdot C_L$	
2	Bias currents in output cascodes	$I_4 = I_5 = 1.2I_3$ to $1.5I_3$	Avoid zero current in cascodes
3	Maximum output voltage, $v_{out(max)}$	$S_5 = \frac{2I_5}{K_P \cdot V_{SD5}^2}$ , $S_7 = \frac{2I_7}{K_P \cdot V_{SD7}^2}$ , ( $S_4 = S_5$ and $S_6 = S_7$ )	$V_{SD5(sat)} = V_{SD7(sat)} = 0.5[V_{DD} - V_{out(max)}]$
4	Minimum output voltage, $v_{out(min)}$	$S_{11} = \frac{2I_{11}}{K_N \cdot V_{DS11}^2}$ , $S_9 = \frac{2I_9}{K_N \cdot V_{DS9}^2}$ , ( $S_{10} = S_{11}$ and $S_8 = S_9$ )	$V_{DS9(sat)} = V_{DS11(sat)} = 0.5[V_{out(min)} - V_{SS}]$
5	$GB = \frac{g_{m1}}{C_L}$	$S_1 = S_2 = \frac{g_{m1}^2}{K_N \cdot I_3} = \frac{GB^2 C_L^2}{K_N \cdot I_3}$	
6	Minimum input CM	$S_3 = \frac{2I_3}{K_N \cdot (V_{in(min)} - V_{SS} - \sqrt{(I_3/K_N \cdot S_1)} - V_{T1})^2}$	
7	Maximum input CM	$S_4 = S_5 = \frac{2I_4}{K_P \cdot (V_{DD} - V_{in(max)} + V_{T1})^2}$	$S_4$ and $S_5$ must meet or exceed value in step 3
8	Differential Voltage Gain	$\frac{v_{out}}{v_{in}} = \left( \frac{g_{m1}}{2} + \frac{g_{m2}}{2(1+k)} \right) R_{out} = \left( \frac{2+k}{2+2k} \right) g_{m1} R_{out}$	$k = \frac{R_{II}(g_{ds2} + g_{ds4})}{g_{m7} r_{ds7}}$
9	Power dissipation	$P_{diss} = (V_{DD} - V_{SS})(I_3 + I_{10} + I_{11})$	

# Design Example

---

- Design a folded cascode Op Amp to comply with the following specifications using 0.18 $\mu$ m CMOS technology

Parameter	Spec
Slew rate	$> 10 \text{ V}/\mu\text{s}$
Load Capacitor	10pF
Power Supply	$\pm 1 \text{ V}$
Max/Min Output Voltage	$\pm 0.5 \text{ V}$
GBW	$> 10 \text{ MHz}$
Min Input CM Voltage	$-0.3 \text{ V}$
Max Input CM Voltage	1 V
Differential Voltage Gain	$> 60 \text{ dB}$
Power Dissipation	$< 2 \text{ mW}$

## Design Example (Cont.)

### □ Solution:

- From the value of the slew rate we can get  $I_3$

$$I_3 = SR \times C_L > (10 \times 10^6)(10 \times 10^{-12}) \rightarrow I_3 \geq 100\mu\text{A}$$

Select  $I_3 = 120\mu\text{A}$

- $I_{4,5}$  will be designed such that  $I_{6,7}$  never goes to zero

$$I_4 = I_5 = 1.2I_3 \text{ to } 1.5I_3$$

Select  $I_4 = I_5 = 1.25I_3 = 150\mu\text{A}$

- Knowing  $I_4$  and  $I_3$ , we can get the quiescent, min, and max values of  $I_{6,7}$

$$I_{6,Q} = I_{7,Q} = I_4 - 0.5I_3 = 90\mu\text{A}$$


$$I_{6(\min)} = I_{7(\min)} = I_4 - I_3 = 20\mu\text{A}$$

$$I_{6(\max)} = I_{7(\max)} = I_4 = 150\mu\text{A}$$

- From the min and maximum output voltages we can get overdrive voltage of transistors  $M_{4-11}$

$$V_{SDsat(4-7)}|_{\max} = 0.5(V_{DD} - V_{out(\max)}) = 0.25\text{ V}$$

$$V_{DSsat(8-11)}|_{\max} = 0.5(V_{out(\min)} - V_{SS}) = 0.25\text{ V}$$

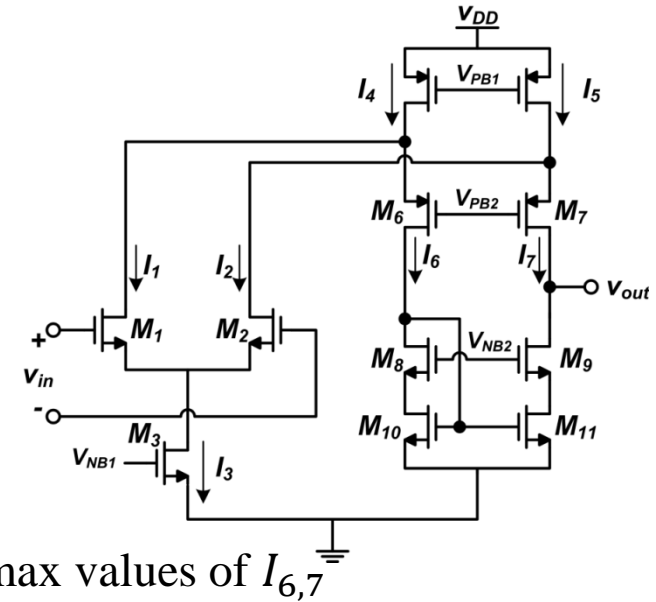

## Design Example (Cont.)

- The value of  $GB$  gives  $g_{m1,2}$

$$g_{m1,2} = GB \times C_L \geq 628.3 \mu A/V$$

Thus, choose  $g_{m1,2} = 700 \mu A/V$

From  $g_{m1,2}$  and  $I_{1,2}$ , we can obtain  $V_{DSSat(1,2)}$

$$V_{DSSat(1,2)} = \frac{2I_1}{g_{m1}} = \frac{I_3}{g_{m1}} = 0.17 V$$


- The minimum input common mode voltage defines  $V_{DSSat3}$

$$V_{icm(min)} = V_{SS} + V_{DSSat(3)} + V_{Tn} + V_{DSSat(1)}$$

Thus,  $V_{DSSat(3)} = 0.13 \mu A$  for  $V_{Tn} = 0.4 V$

- We need to check that the maximum input common mode voltage is satisfied
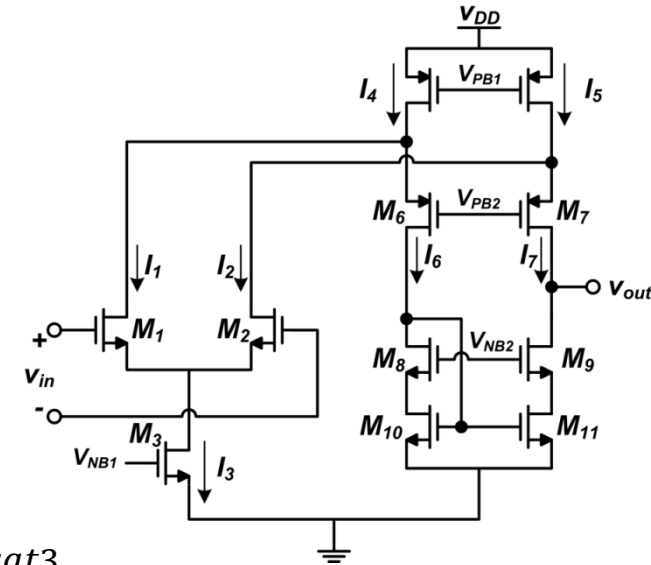
$$V_{icm(max)} = V_{DD} - V_{SDsat(4)} + V_{Tn} = 1.15 V \rightarrow \text{Meets the spec}$$



## Design Example (Cont.)

---

- ❑ Now, we have the bias currents  $I_D$  and overdrive voltage  $V_{DSSat}$  of all the transistors. Thus, we can obtain  $W/L$  of all the transistors from the ACM model or square-law model if long-channel transistors are used.
- ❑ The channel length of the transistors should be chosen to satisfy the specified voltage gain.
- ❑ The current flowing in transistors  $M_{6-11}$  can have any value from  $20 \mu A$  to  $150 \mu A$  depending on the amplitude and polarity of the differential input voltage. Therefore, they should be sized such that the worst case  $V_{DSSat}$  of each transistor meets the specified limits on the output voltages.
- ❑ Bias voltages of the cascode transistors  $V_{PB2}$  and  $V_{NB2}$  are chosen such that  $V_{PB2}$

# Simulation Results



---

## □ DC operating point

Transistor	$W/L$	$I_D$ ( $\mu A$ )	$V_{DSsat}$
$M_{1,2}$	18/1	120	0.13
$M_3$	24/1	60	0.16
$M_{4,5}$	72/1	150	0.23
$M_{6,7}$	72/1	90	0.23
$M_{8,9}$	12/1	90	0.24
$M_{10,11}$	12/1	90	0.24

# Simulation Results


## Input common-mode range

 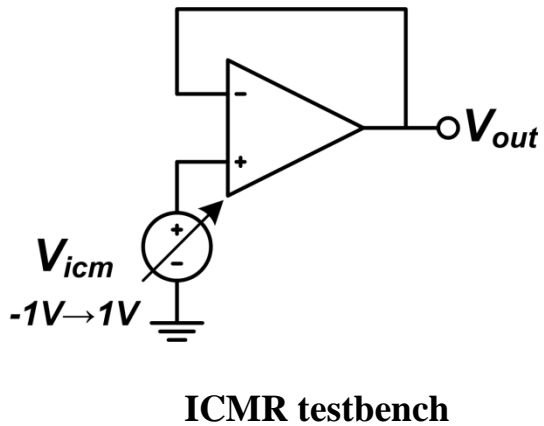


Minimum input common mode voltage is 0.28 V

# Simulation Results

## Output Swing

 

Output Swing Testbench


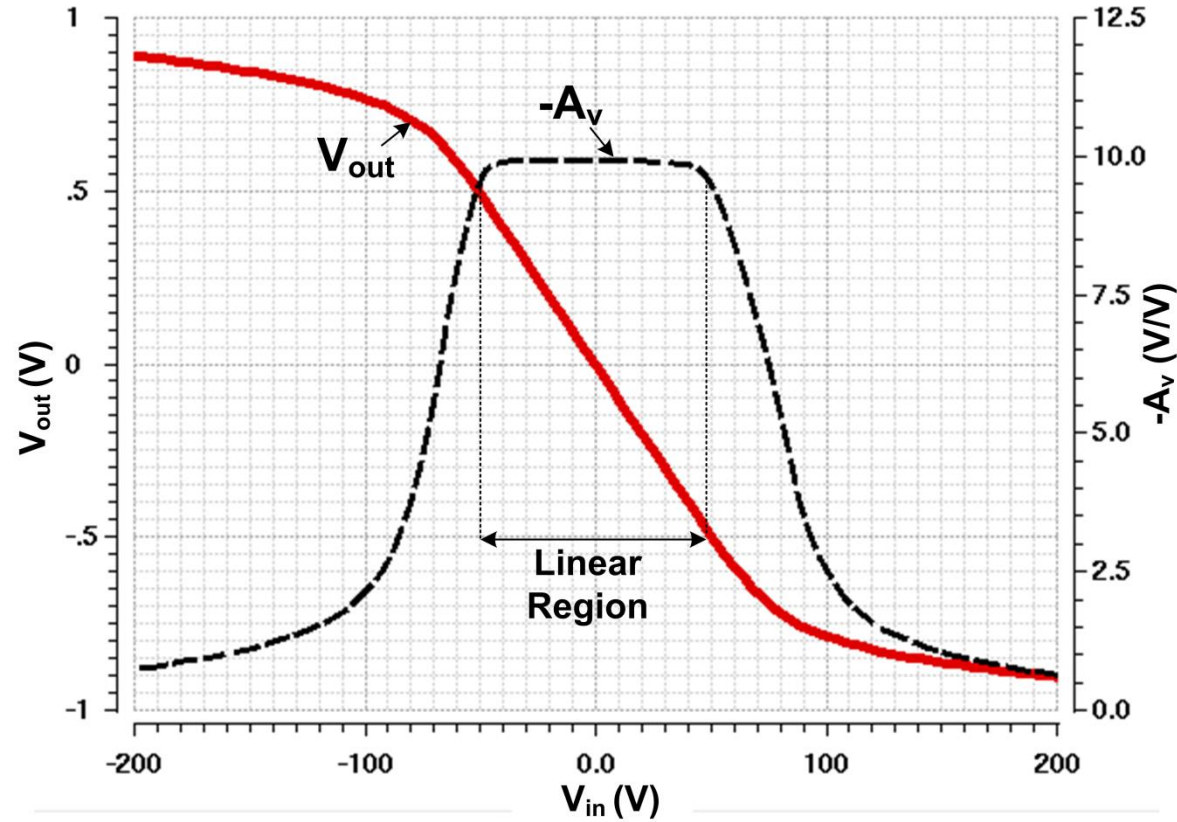


The gain is perfectly linear for  $-0.5 \leq V_{out} \leq 0.5$



# Simulation Results




## Open loop response

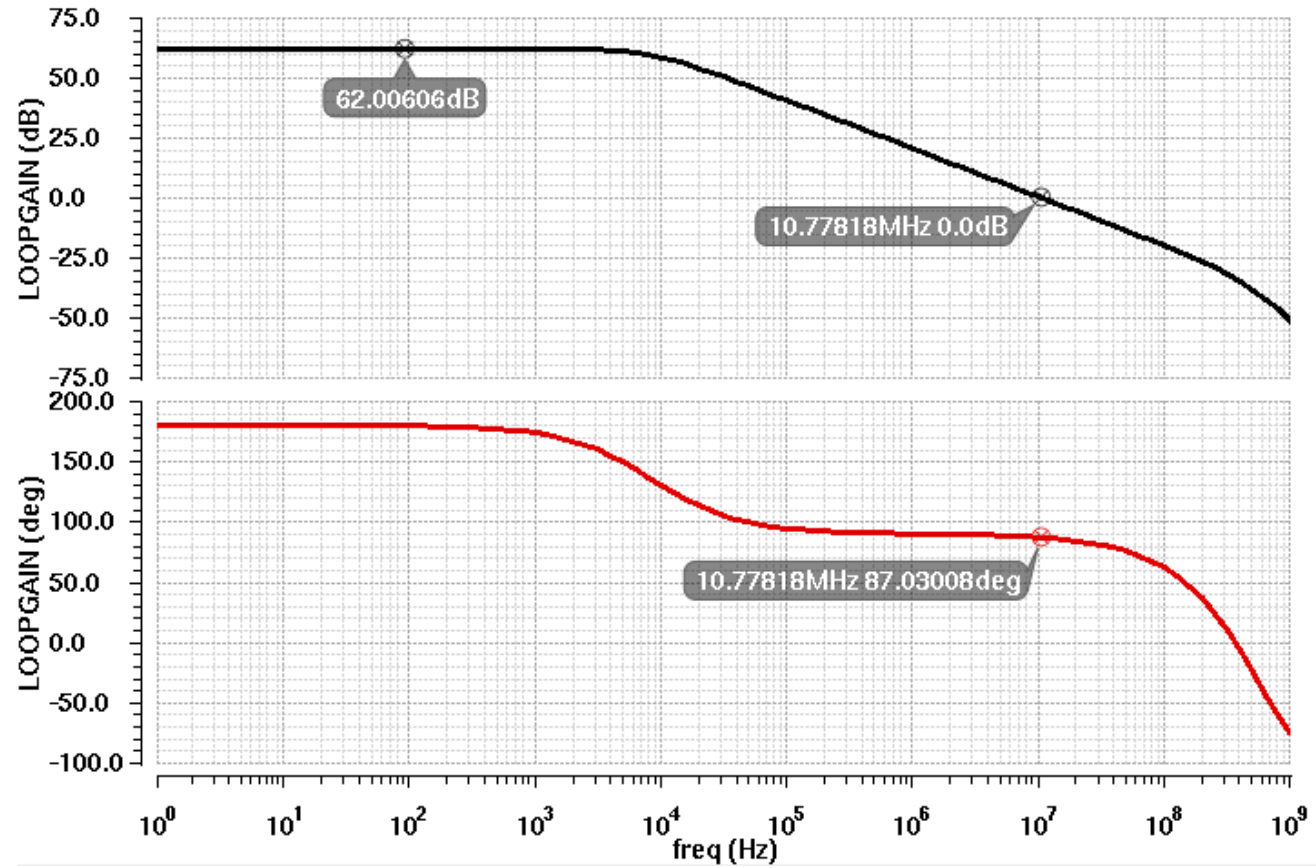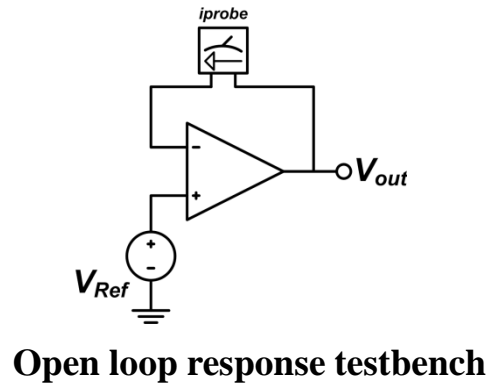

$A_v > 60 \text{ dB}$   
 $GB > 10 \text{ MHz}$

# Simulation Results


## □ Slew Rate

 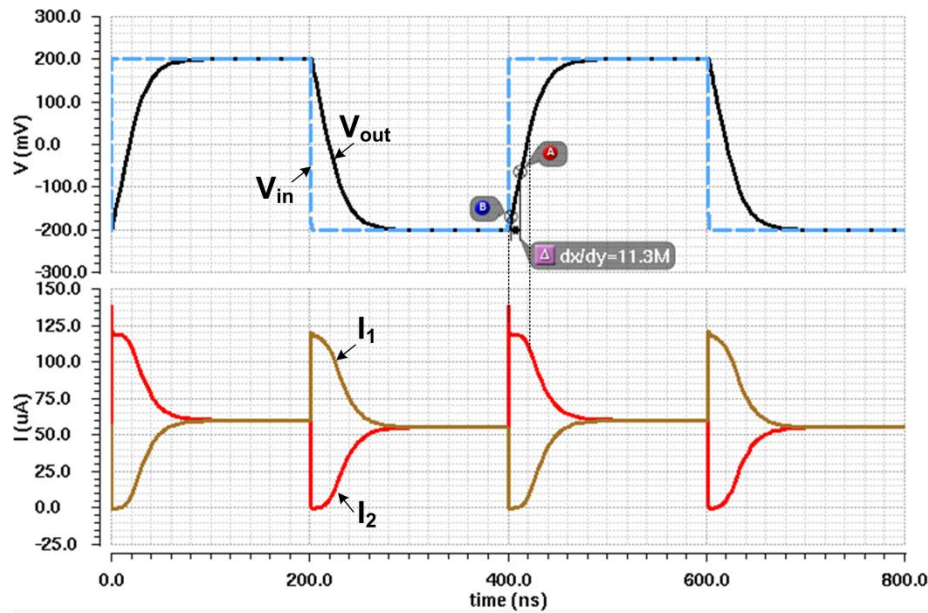 



$$SR^+, SR^- > 10 V/\mu s$$

# Simulation Results


## PSRR

 

PSRR+ testbench

  

PSRR- testbench

 


# Summary of Results

□ The following simulation results for  $C_L = 10pF$ ,  $V_{DD} = 1V$  and  $V_{SS} = -1V$

Parameter	Spec	Simulation
SR <sup>+</sup>	> 10 V/μs	11.3 V/μs
SR <sup>-</sup>	> 10 V/μs	11.18 V/μs
Max/Min Output Voltage	±0.5 V	-0.65 → 0.61 V
GBW	> 10 MHz	10.7 MHz
Min Input CM Voltage	-0.3 V	-0.28 V
Max Input CM Voltage	1 V	1 V
Differential Voltage Gain	> 60 dB	62 dB
PSRR <sup>+</sup>	-	65.64 dB
PSRR <sup>-</sup>	-	75.86 dB
Power Dissipation	< 2 mW	840 μW

 
# Techniques for Wideband Amplifiers

Focus the improvement in the load of the differential pair



Current Mirror  
at the output load

Conventional

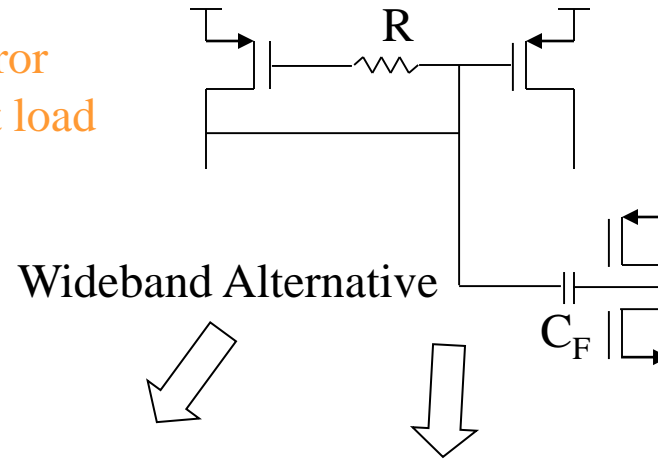


Wideband Alternative


Frequency Dependent  
Current Mirror (FDCM)

$$C_F \gg C_{gs}$$

$$0.1K < R < 1K$$

 


Low Frequency  
Behavior

 

High Frequency  
Behavior


An example of its use:

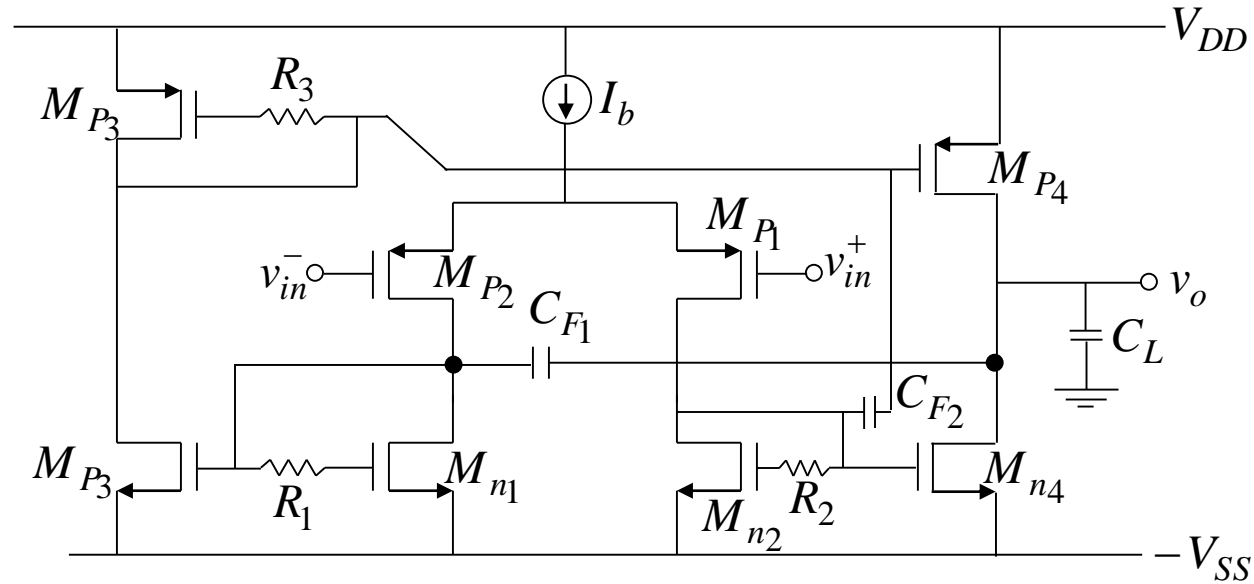
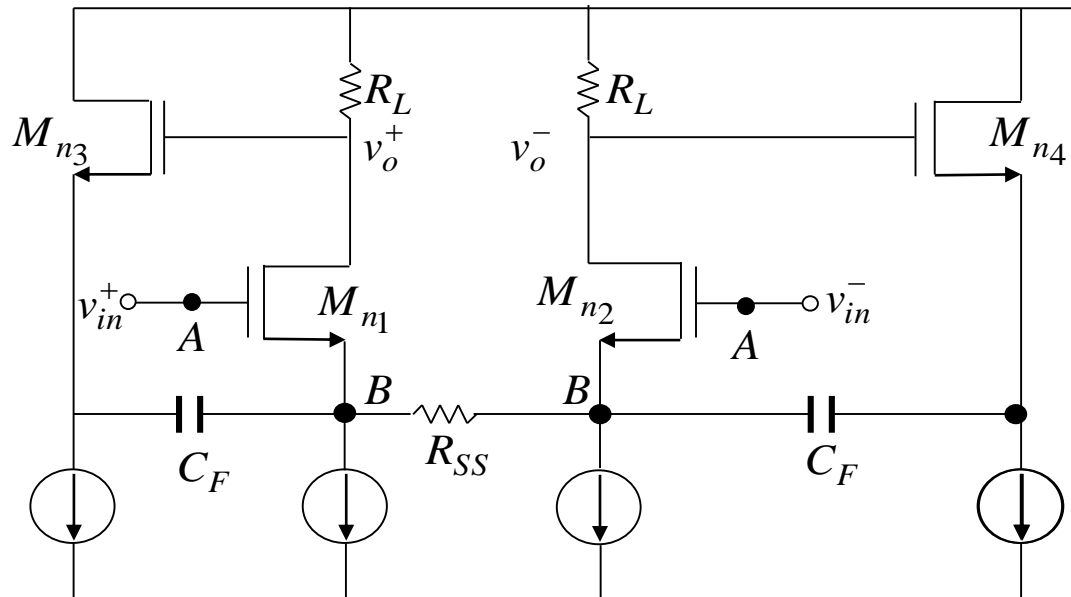
## Wideband Amplifier with Feedforward Technique

- What is the optimal value of  $R_1$  as a function of  $G_{mP3}$  ?
- $C_{F1}$  bypasses two current mirrors.
- $C_{F2}$  is fed forward to the input of another FDCM and signal is amplified.


Next, we discuss different families of wideband reported in the literature.




- An alternative is to connect  $C_F$  instead to nodes B to nodes A

F. Centurelli et al, "A Bootstrap Technique for Wideband Amplifiers," *IEEE Trans. on Circuits And System – I*, Vol. 49, No. 10, pp. 1474-1480, October 2002

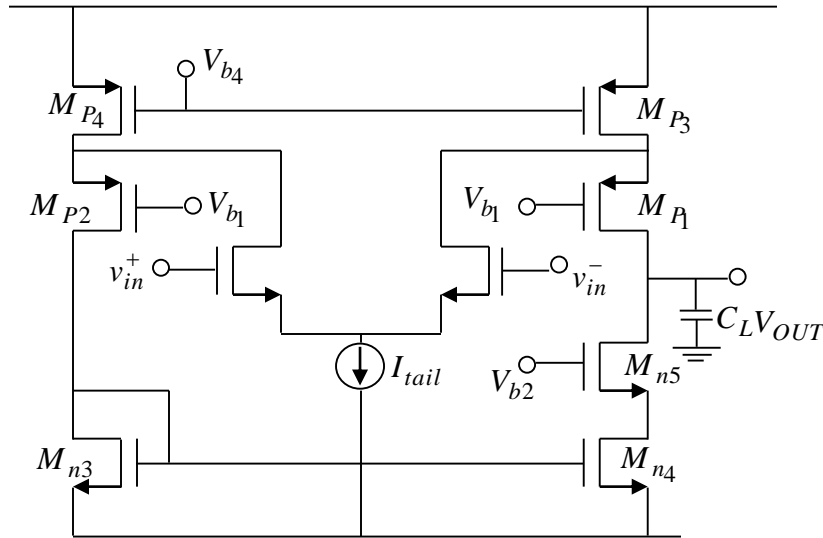
# FOLDED-CASCODE WIDEBAND AMPLIFIER ( See page 11 for cascode)



Conventional Folded-Cascode (FC)

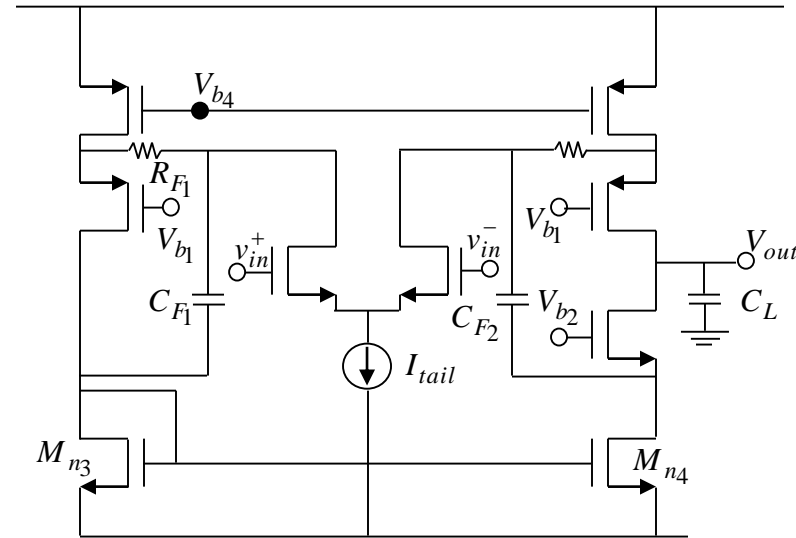

FC with Capacitive Feedforward

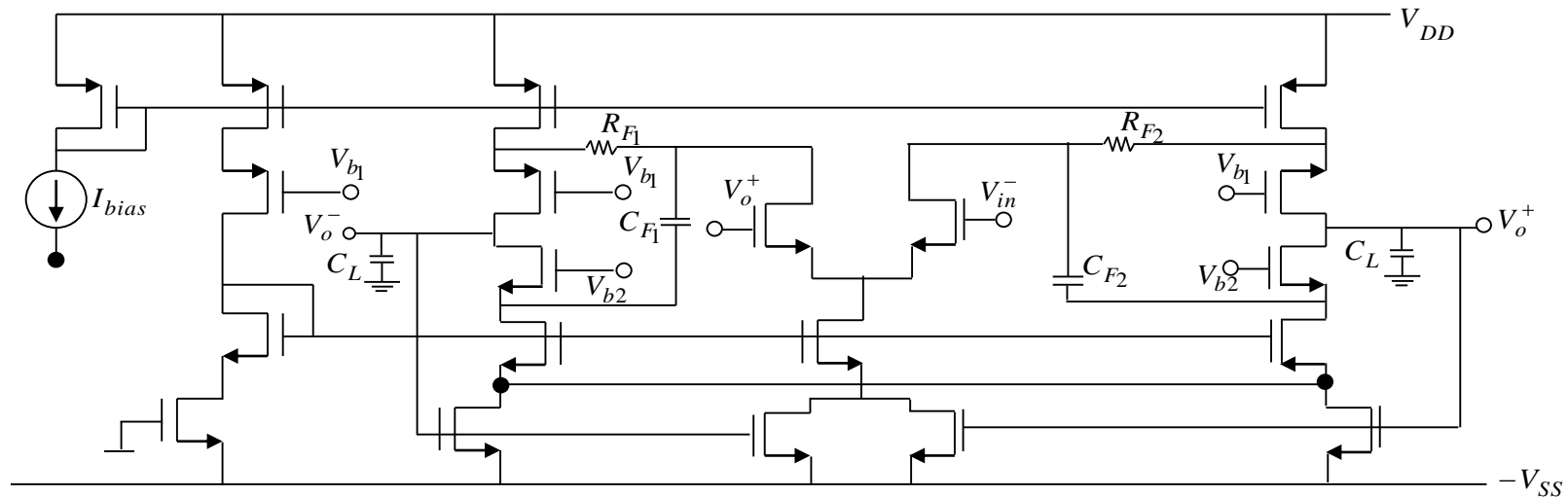

Differential Wideband Amplifier



# An example of LV techniques: Current-Mode based LV Op Amp

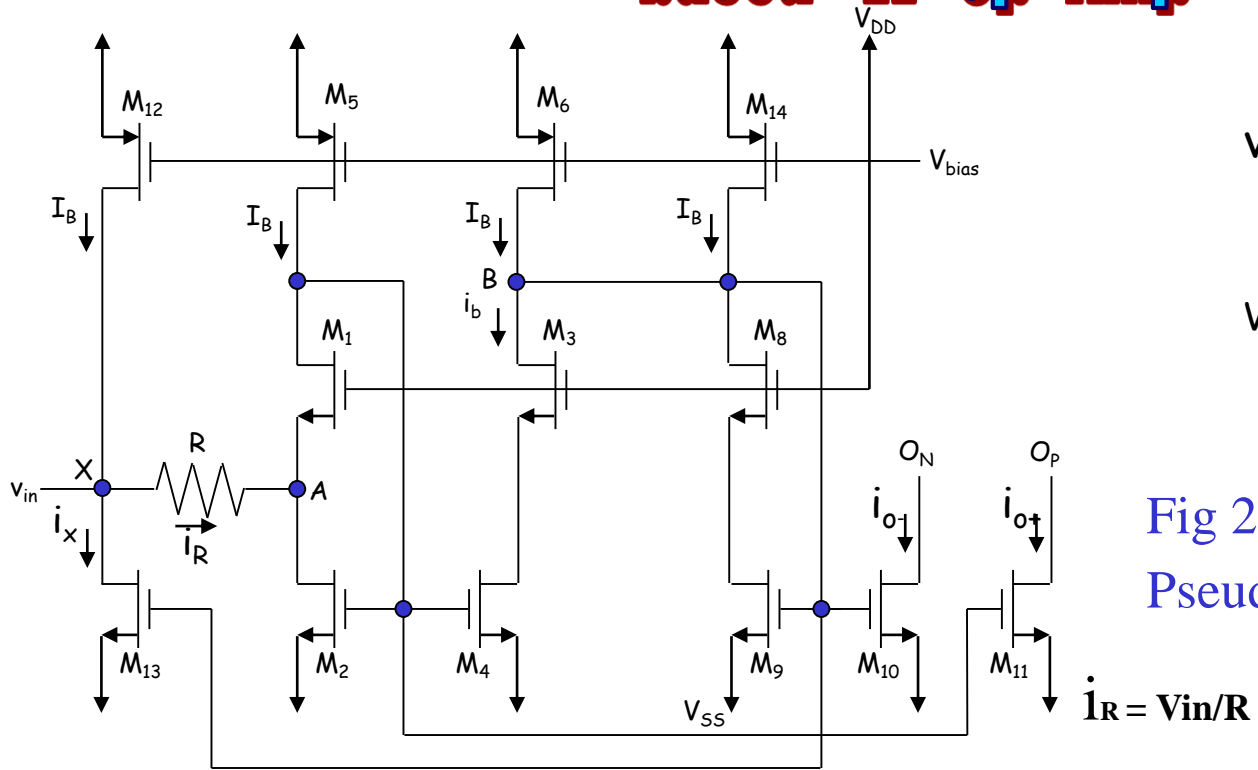


Fig. 1 Transconductance Amp  
Basic Structure based on current-mode

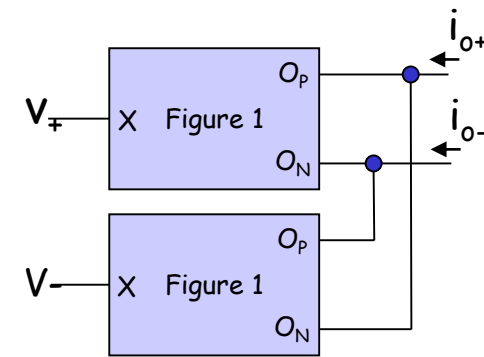


Fig 2  
Pseudo Differential Op Amp

$$i_R = v_{in}/R$$

$$i_X = -i_R$$

$$I_B > i_R$$

E.K.F. Lee, " Low-Voltage Opamp Design and Differential Difference Amplifier Design Using Linear Transconductor with Resistor Input ", " IEEE Trans. Circuits and Systems II, vol. 47, pp 776-778, Aug. 2000



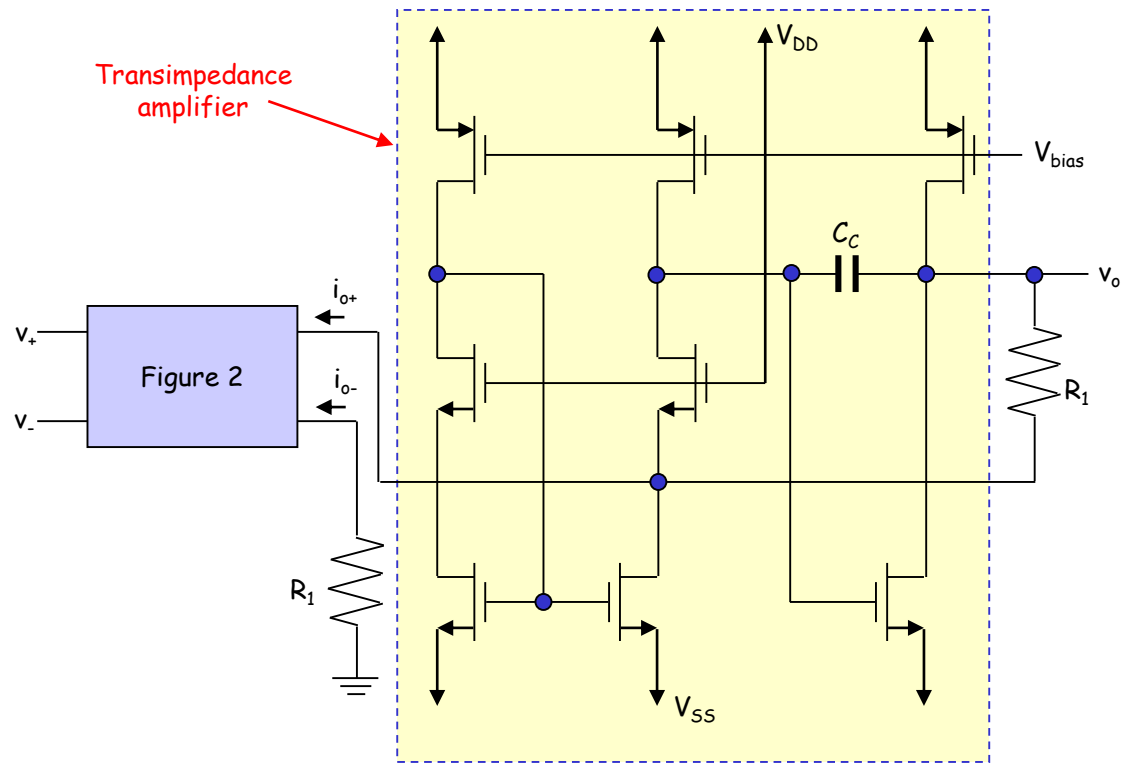



Fig 3 VCVS Amplifier: Op Amp

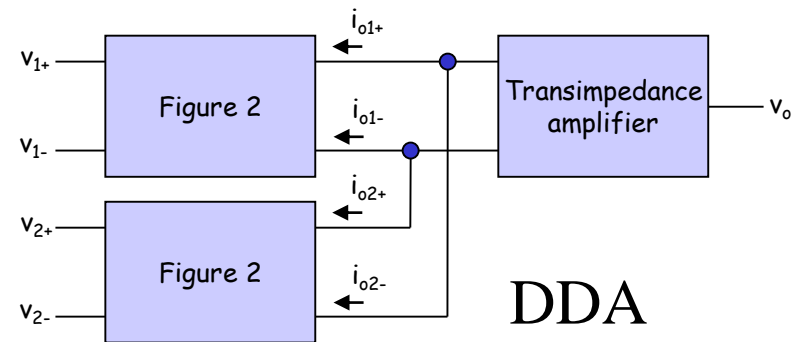

# References

 

- SS Rajput, SS Januar, Low voltage analog circuit design techniques, *IEEE Circuits and Systems Magazine*, pp. 24-42, 2002
- S. Yan and E. Sánchez-Sinencio, Low Voltage Analog Circuit Design Techniques: A Tutorial, *IEICE Trans. Fundamentals*, Vol. E83-A, No. 2, pp 179-196, February 2000
- E. Sánchez-Sinencio and Andreas G. Andreou, Eds. “ *Low-Voltage/Low-Power Integrated Circuits and Systems* “, IEEE Press, Piscataway, NJ 1999
- X. Xie, M.C. Schneider, E. Sanchez-Sinencio and S.H.K. Embabi, “ Sound Design of Low Power Nested Transconductance-Capacitance Compensation Amplifiers”, *IEE Electronics Letters*, Vol. 35, pp.956-958, June 1999.
- A. Rodriguez-Vazquez and E. Sánchez-Sinencio, Eds., Special Issue on Low-Voltage and Low-Power Analog and Mixed-Signal Circuits and Systems, *IEEE Trans. on Circuits and Systems I*, vol. 42, No. 11, November 1995
- J. Crols, J.; Steyaert, M.; Switched-opamp: an approach to realize full CMOS switched capacitor circuits at very low power supply voltages” *IEEE Journal of Solid-State Circuits*,, Volume: 29 , Issue: 8 , Aug. 1994 Pages:936 - 942

 

## **Very low-voltage analog signal processing based quasi-floating gate transistors,J**

Ramirez-Angulo, AJ Lopez-Martin, RG Carvajal, et all, *IEEE J. Solid-State Circuits*, pp 434- 442, **March 2004**

## **Low threshold CMOS circuits with low standby current**

*Stan, M.R.* Low Power Electronics and Design, 1998. Proceedings. 1998 International Symposium on , 10-12 Aug. 1998 Pages:97 - 99

## **A dynamic threshold voltage MOSFET (DTMOS) for ultra low voltage operation** *Assaderaghi, F.;*

*Sinitsky, D.; Parke, S.; Bokor, J.; Ko, P.K.; Chenming Hu;*

Electron Devices Meeting, 1994. Technical Digest., International , 11-14 Dec. 1994 Pages:809 - 812

## **Resizing rules for MOS analog-design reuse**

*Galup-Montoro, C.; Schneider, M.C.; Coitinho, R.M.;*

Design & Test of Computers, IEEE ,Volume: 19 , Issue: 2 , March-April 2002 Pages:50 - 58

## **An MOS transistor model for analog circuit design** .*Cunha, A.I.A.; Schneider, M.C.; Galup-*

*Montoro, C.;* Solid-State Circuits, IEEE Journal of ,Volume: 33 , Issue: 10 , Oct. 1998


Pages:1510 – 151

## **Series-parallel association of FET's for high gain and high frequency applications**

*Galup-Montoro, C.; Schneider, M.C.; Loss, I.J.B.;* Solid-State Circuits, IEEE Journal

of ,Volume: 29 , Issue: 9 , Sept. 1994 Pages:1094 - 1101

# References

 

**S. M. Mallya and J. H. Nevin, “ Design Procedures for a Fully Differential Folded Cascode CMOS Operational Amplifier”, *IEEE J. of Solid-State Circuits*, Vol 24, No. 6, pp1737-1740, December 1989.**

**D. B. Ribner, M. A. Copeland. and M. Milkovic, “80MHz low offset fully-differential and single-ended opamps,” in *Proc. IEEE Custom Integrated Circuits Con/.*, 1983, pp. 74-75.**

**This reference discusses three different Op Amp topologies:**

**S. Rabbii and B. A. Wooley, “ A 1.8V-V Digital Audio Sigma-Delta Modulator in 0.8-um CMOS”, *IEEE J. of Solid-State Circuits*, Vol. 32, No. 6, pp. 783-796, June 1997**

**CMOS Analog Circuit Design, P.E. Allen, D.R. Holberg, Oxford University Press, 3<sup>rd</sup> Edition, 2012**