

## ECEN 607 (ESS)

### HOW TO APPROXIMATE AN EXPRESSION FOR 3dB BANDWIDTH OF A MULTIPLE POLE SYSTEM?

Let us consider an all pole system

$$A(s) = \frac{A_o}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})(1 + s/\omega_{p3}) \cdots (1 + s/\omega_{pn})}$$
$$|A(j\omega)| = \frac{A_o}{\left\{ \left(1 + (\omega/\omega_{p1})^2\right) \left(1 + (\omega/\omega_{p2})^2\right) \left(1 + (\omega/\omega_{p3})^2\right) \cdots \right\}^{1/2}}$$

The 3dB cutoff frequency  $\omega_{3dB}$  is defined at magnitude value  $A_o/\sqrt{2}$ , therefore

$$2 = \left(1 + (\omega_{3dB} / \omega_{p1})^2\right) \left(1 + (\omega_{3dB} / \omega_{p2})^2\right) \left(1 + (\omega_{3dB} / \omega_{p3})^2\right) \cdots$$

Since  $\omega_{3dB} < \omega_{p1}, \omega_{p2} \cdots, \omega_{pn}$  one can approximate

$$2 \cong 1 + \omega_{3dB}^2 \left( \frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2} + \frac{1}{\omega_{p3}^2} + \cdots \right)$$


Hence

$$\omega_{3dB}^2 = \frac{1}{\frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2} + \frac{1}{\omega_{p3}^2} + \cdots}$$

$$\omega_{3dB}^2 \cong \frac{1}{\sum_{i=1}^n \frac{1}{\omega_{pi}^2}}$$

Another approach to obtain the  $\omega_{3dB}$  is by means of "The Time - Constant Method".

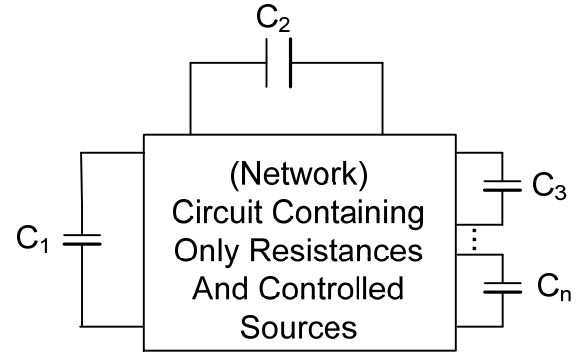Consider the network consisting of capacitors, resistors and depending sources



The transfer function of the network above can be expressed as

$$H(s) = \frac{N(s)}{1 + a_1s + a_2s^2 + \dots}$$


It can be proved that  $a_1$  is the sum of the time constants and  $a_2$  is the sum of the product of time constants.

Lets consider the case of three capacitors, thus

$$a_1 = R_{11}^o C_1 + R_{22}^o C_2 + R_{33}^o C_3$$

where  $R_{11}^o, R_{22}^o, R_{33}^o$  are the zero frequency resistances seen by  $C_1, C_2$  and  $C_3$  respectively.

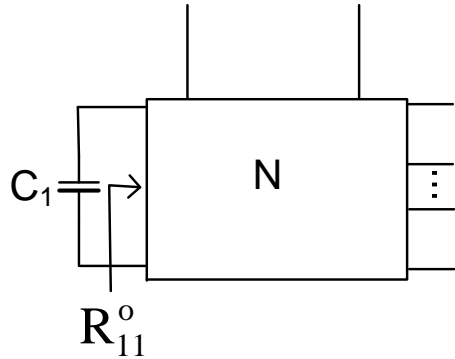For example to compute  $R_{11}^o$  the circuit shown is used



$$C_2 = C_3 = 0$$

Thus if we obtain  $R_{22}^o$  and  $R_{33}^o$  in a similar way, one can express  $a_1$  as

$$a_1 = \sum_{i=1}^n R_{ii}^o C_i = \sum_{i=1}^n \tau_i$$


$a_1$  can be seen as the sum of open - circuit time constants. Thus an approximation of  $\omega_{3dB}$  can be as

$$\omega_{3dB} \cong \frac{1}{a_1} = \frac{1}{\sum_{i=1}^n \tau_i} = \frac{1}{\sum_{i=1}^n \frac{1}{\omega_{pi}}}$$


For the sake of completeness let us discuss how to compute  $a_2$ .

$$a_2 = R_{11}^o C_1 R_{22}^1 C_2 + R_{11}^o C_1 R_{33}^1 C_3 + R_{22}^o C_2 R_{33}^2 C_3$$

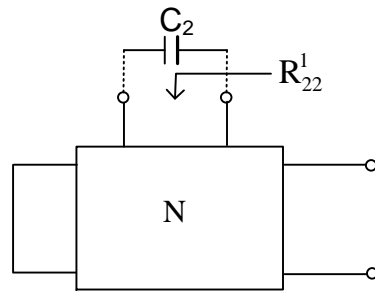
Where  $R_{ii}^j$  is the zero - frequency resistance seen by  $C_i$  when  $C_j$  is short - circuited.



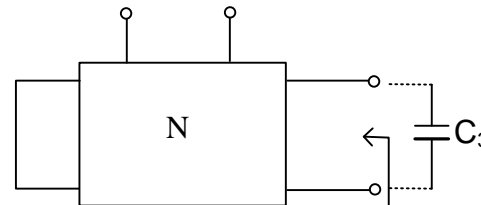$C_1$  is short-circuited  
 $C_3$  is open-circuited



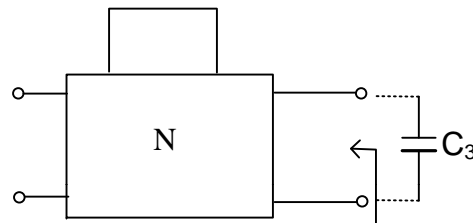$C_1$  is short-circuited  
 $C_2$  is open-circuited



$C_2$  is short-circuited  
 $C_1$  is open-circuited

### Notation Remarks

$R_{ii}^j$ , ii Indicates the terminals at which the resistance is computed  
 j denotes the capacitance that is shorted.


The general form of each term in  $a_2$  is

$$R_{ii}^0 C_i R_{jj}^1 C_j = R_{jj}^0 C_j R_{ii}^j C_i$$

For instance if  $R_{22}^0 C_2 R_{33}^2 C_3$  is replaced by  $R_{33}^0 C_3 R_{22}^3 C_2$  the value of  $a_2$  is not modified.

Ref. J. Millman and A. Grabel "Microelectronics", 2<sup>nd</sup> Edition, New York, 1987.

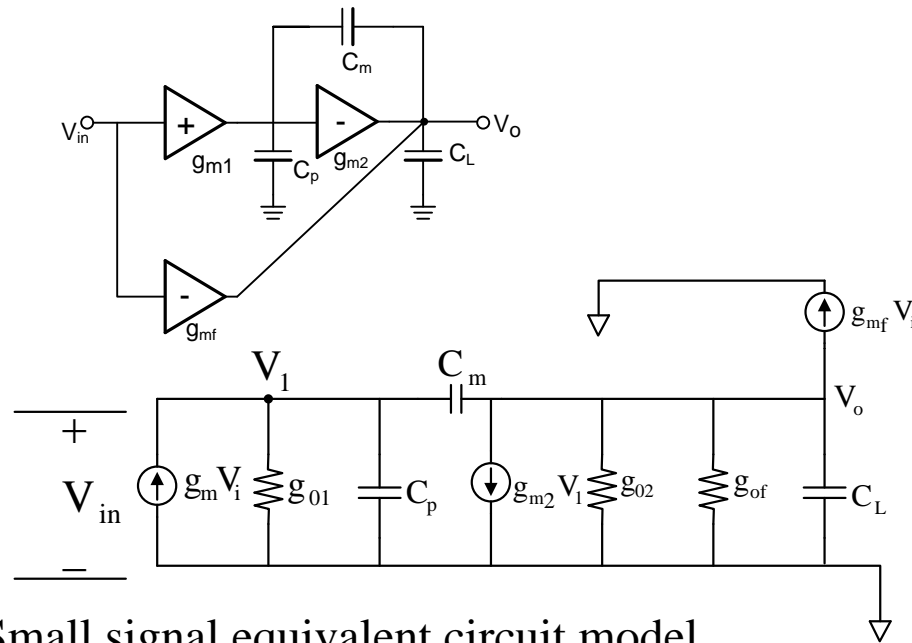
## OPEN – CIRCUIT TIME CONSTANT TECHNIQUE: A NESTED Gm-C EXAMPLE




Small signal equivalent circuit model

There are three capacitors, therefore 3 time constants.

First short-circuit  $v_{in}$

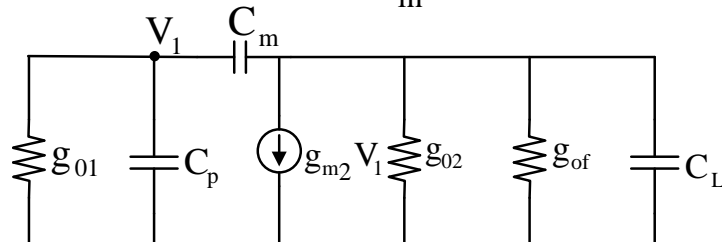


## Time Constant Associated With $C_p$

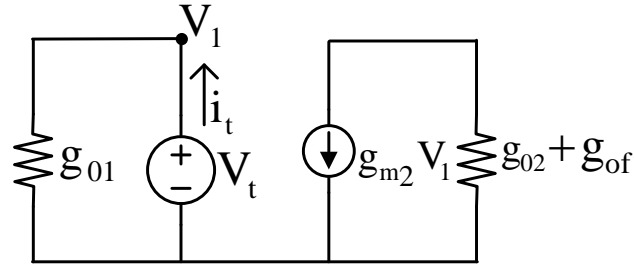

Therefore

$$R_t = R_{\text{thevenin}} = 1/g_{01} = R_p^o, \tau_p = C_p/g_{01}$$

## Time Constant Associated with $C_L$

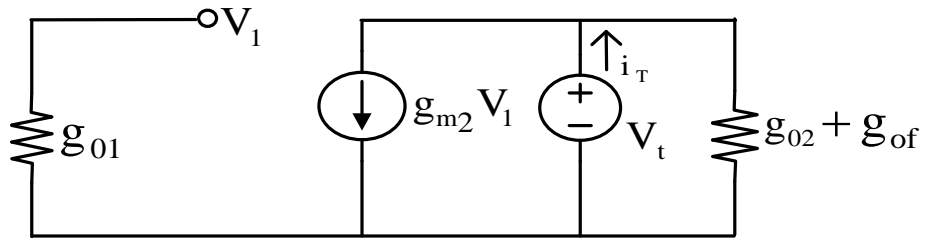


$$V_1 = 0$$

Thus 
$$R_T = \frac{1}{g_{02} + g_{of}}$$

$$\tau_L = \frac{C_L}{g_{02} + g_{of}}$$

## Time Constant Associated with $C_m$

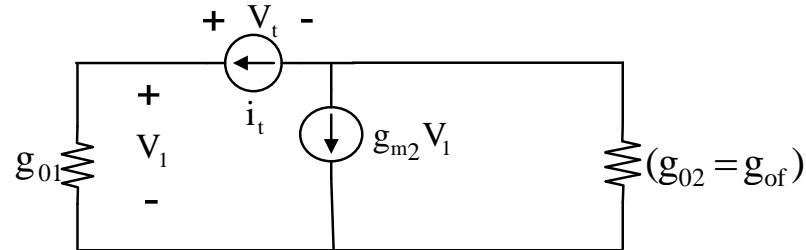

$$V_1 = i_t / g_{o1}$$

KVL

$$V_t = V_1 + (g_{m2} V_1 + i_t) / (g_{o2} + g_{of})$$

Thus

$$V_t = i_t \left\{ \left[ g_{o1}^{-1} + (g_{o2} + g_{of})^{-1} \right] + \frac{g_{m2}}{g_{o1}} \frac{1}{g_{o2} + g_{of}} \right\}$$

$$R_T = \frac{V_t}{i_t} = \frac{1}{g_{o1}} + \frac{1}{g_{o2} + g_{of}} \left( 1 + \frac{g_{m2}}{g_{o1}} \right) = R_m^o$$

$$\tau_m = C_m \left[ \frac{1}{g_{o1}} + \frac{1}{g_{o2} + g_{of}} \left( 1 + \frac{g_{m2}}{g_{o1}} \right) \right]$$

Thus the approximated  $\omega_{3dB}$  becomes

$$\omega_{3dB} = \frac{1}{\tau_p + \tau_L + \tau_m}$$

$$\omega_{3dB} = \frac{1}{\frac{C_m + C_p}{g_{o1}} + C_m \left[ \frac{1}{g_{o2} + g_{of}} \left( 1 + \frac{g_{m2}}{g_{o1}} \right) \right] + \frac{C_L}{g_{o2} + g_{of}}}$$

Note that  $\tau_p \ll \tau_m$ , thus one can approximate

$$\omega_{3dB} \cong \frac{1}{\tau_m + \tau_L}$$


Also

$$\omega_m = \frac{1}{\tau_m} \cong \frac{g_{o2} + g_{of}}{C_m \left( 1 + \frac{g_{m2}}{g_{o1}} \right)} \cong \frac{g_{o2} + g_{of}}{C_m \frac{g_{m2}}{g_{o1}}}$$


$$\omega_L = \frac{1}{\tau_L} = \frac{g_{o2} + g_{of}}{C_L}$$


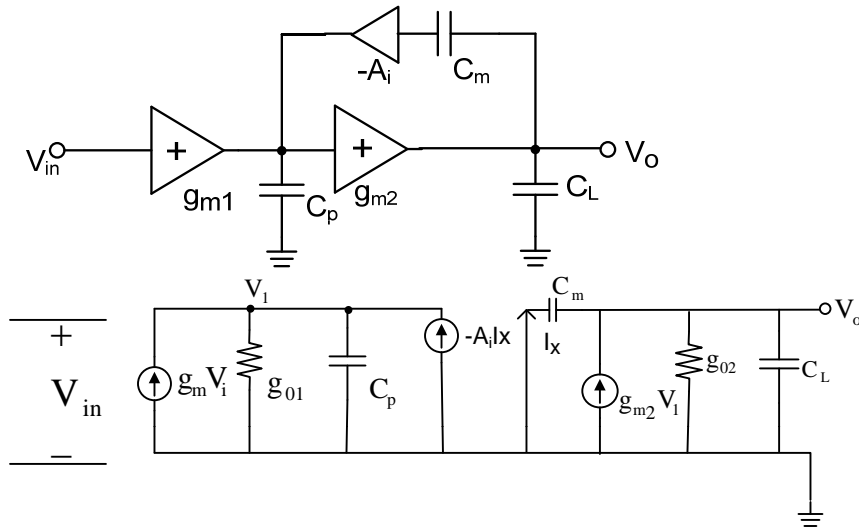
## Open-Circuit Time Constant for Amplifier with Current Buffer




First Short-Circuited  $V_{in}$

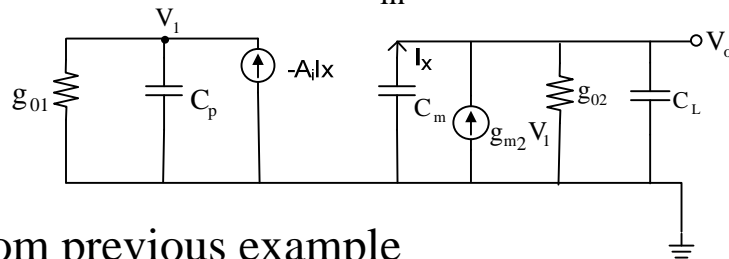

From previous example

$$\tau_L = \frac{C_L}{g_{o2}} \quad \text{and} \quad \tau_p = \frac{C_p}{g_{o1}}$$

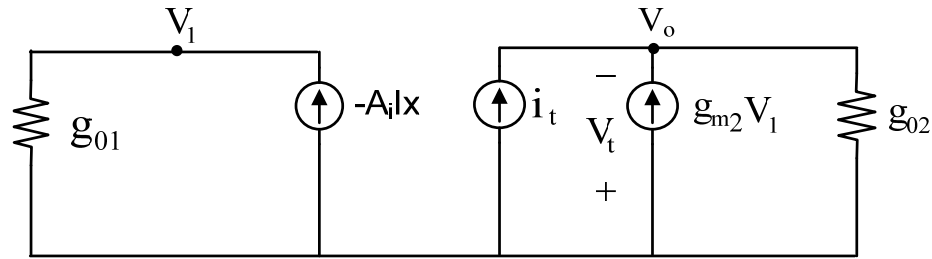Time Constant Associated with  $C_m$  is considered next



$$I_x = I_t \quad ; \quad V_o = -V_t$$

$$V_1 = +g_{01} A_i I_x$$

KCL

$$V_o g_{02} = g_{m2} V_1 + i_t$$

$$V_t g_{02} = g_{m2} g_{01} A_i i_t + i_t$$

$$V_t = (g_{m2} g_{01} A_i + 1) \frac{1}{g_{02}}$$

$$R_T = \frac{1 + g_{m2} g_{01} A_i}{g_{02}}$$

$$\tau_m = \frac{1 + g_{m2} g_{01} A_i}{g_{02}} C_m$$

$$\omega_m = \frac{g_{02}}{(1 + g_{m2} g_{01} A_i) C_m} \cong \frac{g_{02}}{g_{m2} g_{01} A_i C_m}$$

$$\omega_{3dB} \cong \frac{1}{1/\omega_m + 1/\omega_L} = \frac{1}{\tau_m + \tau_L}$$

$$\omega_{3dB} \cong \frac{g_{02}}{g_{m2} g_{01} A_i C_m + C_L}$$

Let us illustrate how to compute  $a_2$  using the amplifier shown in Figure of Slide 5. Thus for a two capacitor system\*


$$a_2 = R_p^o C_p R_m^p C_m = R_m^o C_m R_p^m C_p$$

The open-circuit resistances  $R_p^o$  and  $R_m^o$  are known since they were derived previously

$$R_m^o = \frac{1}{g_{o1}} + \frac{1}{g_{o2} + g_{of}} \left( 1 + \frac{g_{m2}}{g_{o1}} \right)$$

$$R_p^o = \frac{1}{g_{o1}}$$

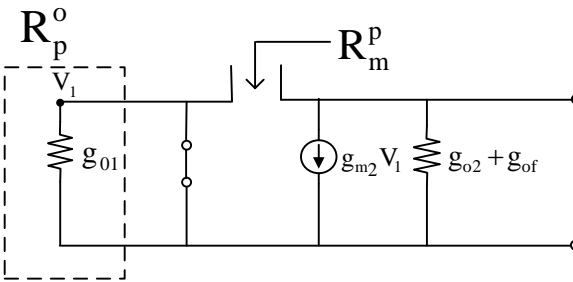To illustrate the analysis we will obtain  $R_m^p$  and  $R_p^m$  using the following circuits




$$V_1 = 0, \text{ thus } R_m^p = \frac{1}{g_{o2} + g_{of}}$$

Therefore

$$a_2 = \frac{1}{g_{o1}} C_p \frac{C_m}{g_{o2} + g_{of}} = \frac{C_p C_m}{g_{o1} (g_{o2} + g_{of})}$$

\* We will ignore initially  $C_L$

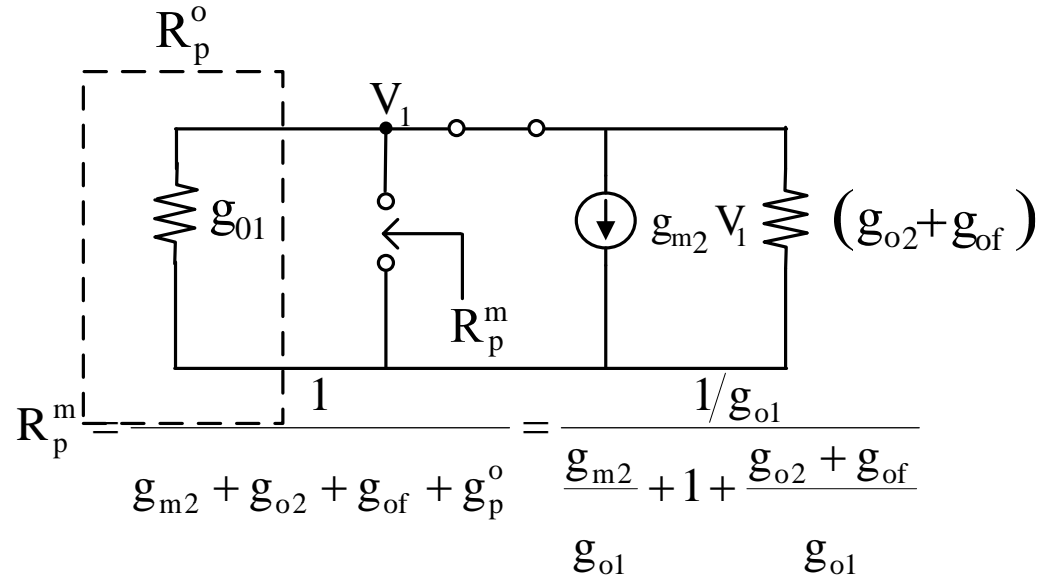


Thus

$$a_2 = R_m^o C_m R_p^m C_p$$

$$a_2 = \left[ \frac{1}{g_{o1}} + \frac{1}{g_{o2} + g_{of}} \left( 1 + \frac{g_{m2}}{g_{o1}} \right) \right] C_m \frac{1/g_{o1}}{1 + \frac{g_{m2}}{g_{o1}} + \frac{g_{o2} + g_{of}}{g_{o1}}} C_p$$

$$a_2 \cong \frac{C_p C_m}{g_{o1} (g_{o2} + g_{of})}$$

Let us consider  $C_L$

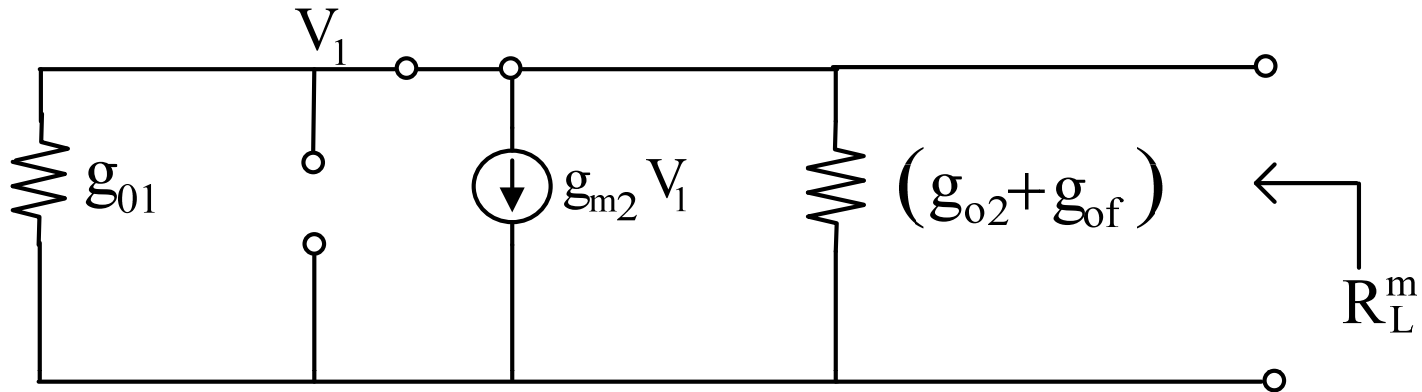

$$\text{Note } R_L^m = R_p^m = \frac{1}{g_{m2} + g_{o2} + g_{of} + g_{o1}}$$

Thus

$$a_2 = R_m^o C_m R_p^m C_p + R_m^o C_m R_L^m C_L + R_m + R_p^o C_p R_L^p C_L$$

The dominant term of  $a_2$  when  $C_p \ll C_L, C_m$  becomes

$$a_2 \cong R_m^o R_L^m C_m C_L$$

Thus

$$a_2 = \left\{ \frac{1}{g_{o1}} + \frac{1}{g_{o2} + g_{of}} \left( 1 + \frac{g_{m2}}{g_{o1}} \right) \right\} \frac{\frac{1}{g_{o1}}}{1 + \frac{g_{m2}}{g_{o1}} + \frac{g_{o2} + g_{of}}{g_{o1}}} C_m C_L$$

$$a_2 \cong \frac{C_m C_L}{g_{o1} (g_{of} + g_{o2})}$$

Ref. 2:

R.T. Howe and C.G. Sodini, "Microelectronics An Integrated Approach", Prentice Hall, Upper Saddle 1997