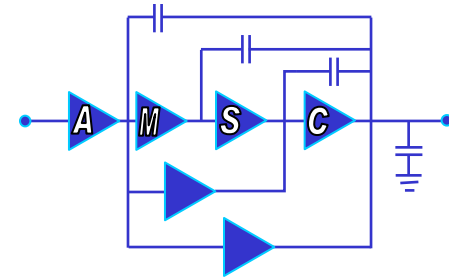




# Noise




**Edgar Sánchez-Sinencio**  
**Department of Electrical and Computer Engineering**  
**Analog and Mixed-Signal Center**  
**Texas A&M University**  
<http://amsc.tamu.edu/>


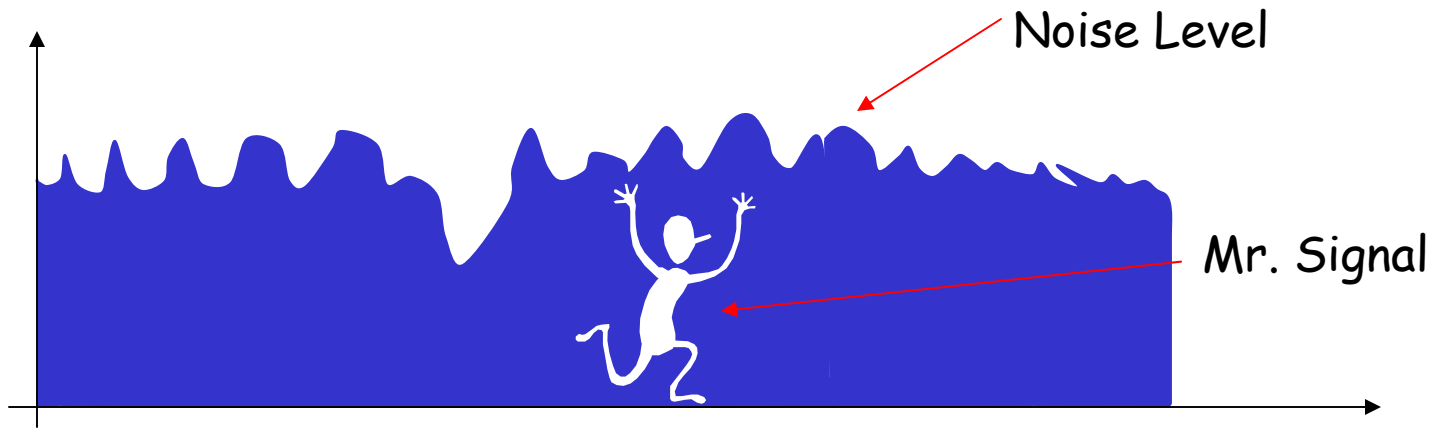
# NOISE

- **NOISE** limits the minimum signal level that a circuit can process with acceptable quality.



Can you identify the signal buried in the noise?

How does the minimal signal must be with respect to the noise level?

- Let us consider the street noise, can one predict the (exact) noise at any time?


No, because it is a random process

- If you decide to blow your car's horn every 5 minutes, then you can say this signal is deterministic.
- So, how can we incorporate noise in circuit design?
  - Observe the noise for a long time
  - Construct a "statistical model"
- The average power noise is predictable
- Most noise sources in circuits exhibit a constant average power

- Average power delivered by a periodic voltage  $v(t)$ , of period  $T$ , to a load resistance  $R_L$  is given by

$$P_{\text{av}} = \frac{1}{T} \int_{-T/2}^{T/2} \frac{v^2(t)}{R_L} dt = \frac{1}{T} \int_{-T/2}^{T/2} v(t)i(t) dt$$

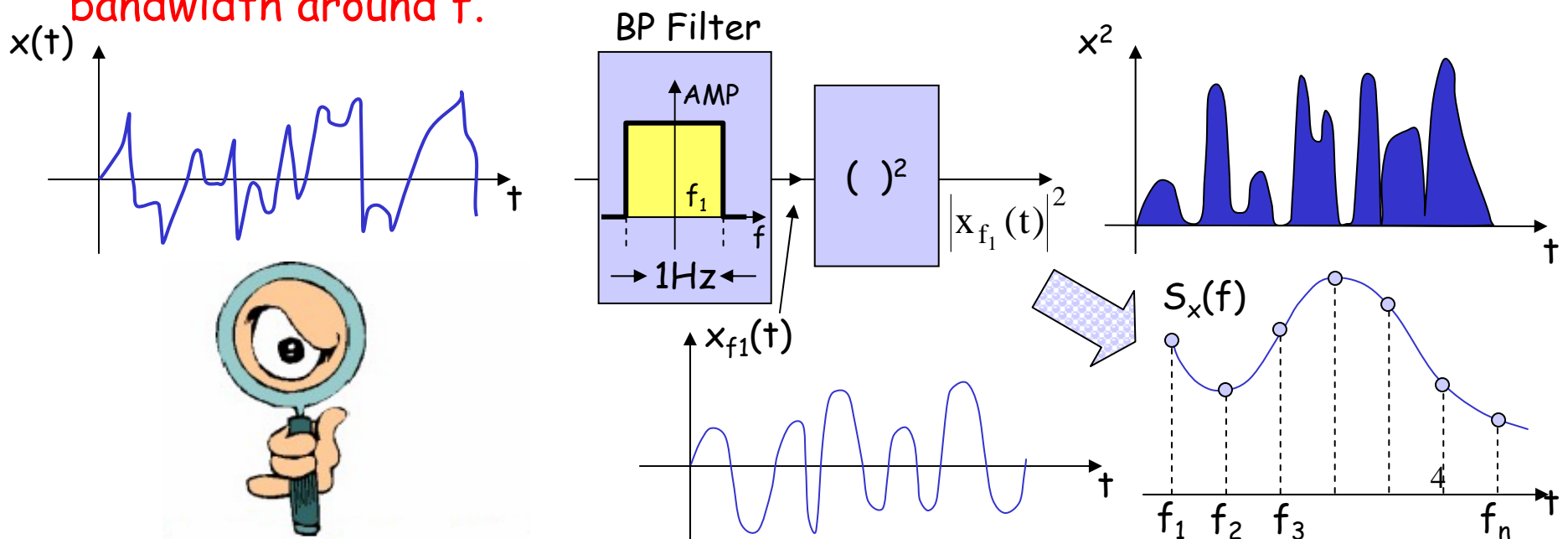
- For non-periodic signals,  $T$  becomes a large quantity
- How much power a signal carries at each frequency is defined by the "power spectral density" (PSD) ( $S_x(f)$ )
- $S_x(f)$  is defined as the average power carried by  $x(t)$  in a one-hertz bandwidth around  $f$ .




- $S_x(f)$  is expressed in  $V^2/\text{Hz}$  rather than  $\text{VI}/\text{Hz} = \text{w}/\text{Hz}$ , in fact  $\{S_x(f)\}^{1/2} = \text{v}/\text{Hz}^{-1/2}$  is often used. Say a filter at 1MHz is equal to 1.414  $\text{nV}/\text{Hz}^{-1/2}$ , means an average power in a 1-Hz bandwidth at 1MHz is equal to  $(1.414 \times 10^{-9})^2 \text{V}^2 = 2 \times 10^{-18} \text{V}^2$

- Another spectrum is the "White Spectrum" or white noise


In practice is band limited.

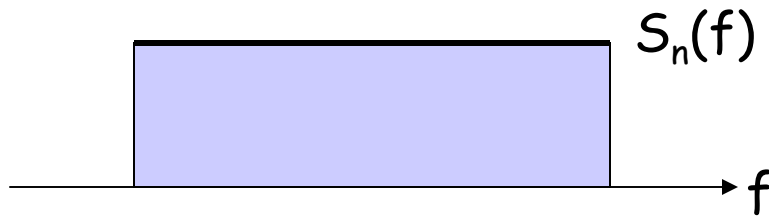

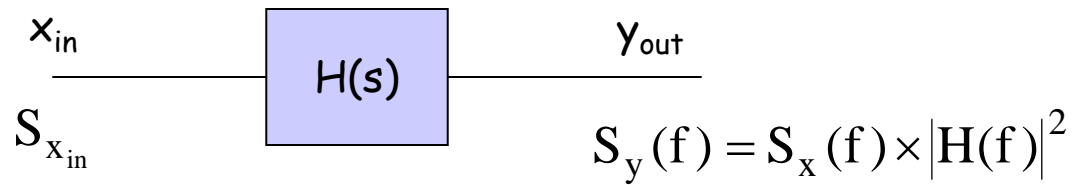- How do you determine the output spectrum of a linear, time-invariant system with transfer function,  $H(s)$ ?




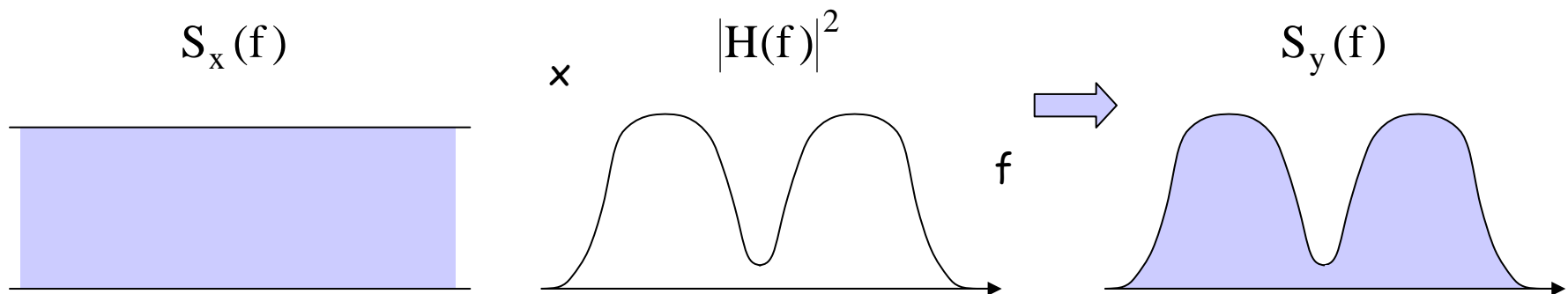- How is the shape of the output spectrum?




- A practical example is the telephone bandwidth, where BW of  $S_{x_{in}}(f)$  is between 0-20KHz, BW of  $H(f)$  is 4KHz and consequently BW of  $S_{y_{out}}(f)$  is 4 KHz.

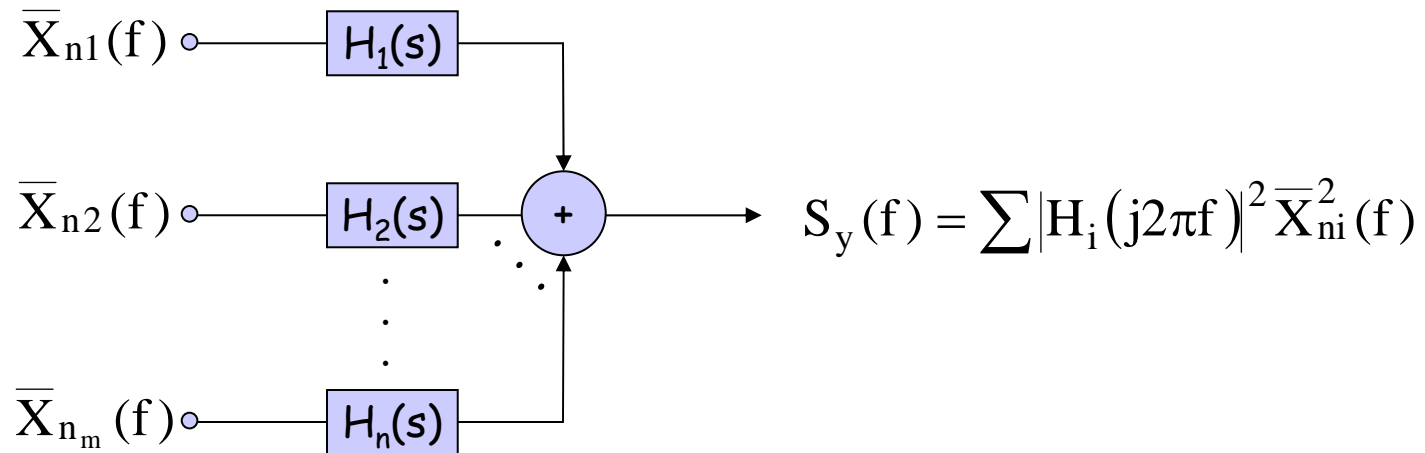If there are more than two noise sources, how do you compute their total effects?





$\bar{x}_{n1}(f), \bar{x}_{n2}(f), \dots$  are uncorrelated noise sources

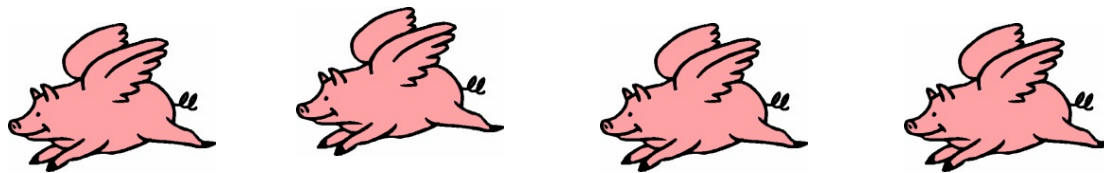Superposition is applied to obtain the total output spectrum.



# Noise Bandwidth

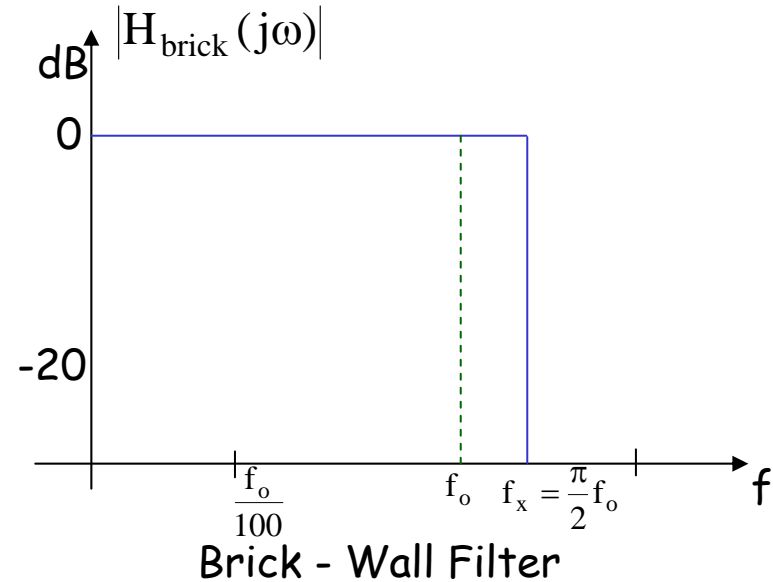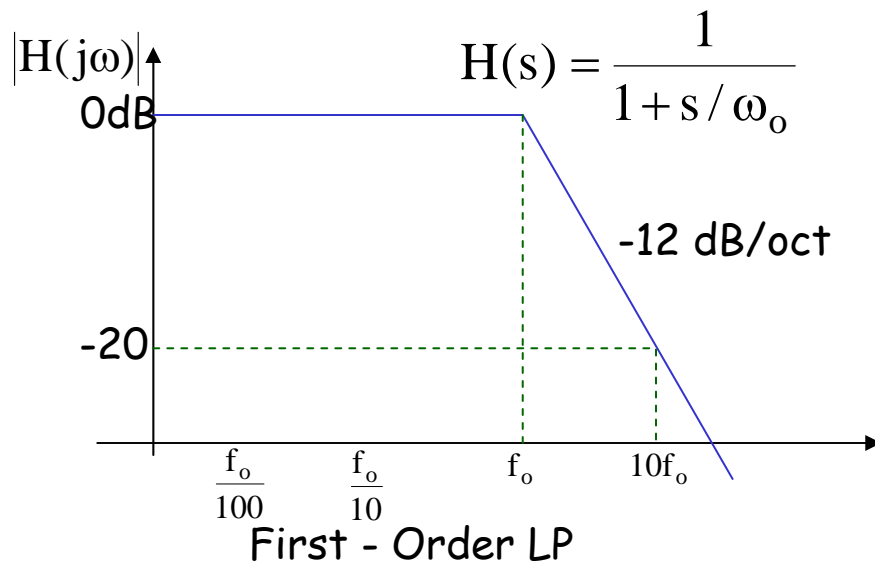

Assume an input signal,  $V_{ni}(f) = V_{nw}$  (constant)

$$\bar{V}_{n,out(rms)}^2 = \int_0^\infty \bar{V}_{ni}^2(f) |H(2\pi f j)|^2 df = \int_0^\infty \frac{\bar{V}_{nw}^2}{1 + \left(\frac{f}{f_o}\right)^2} df = \bar{V}_{nw} f_o \tan^{-1}\left(\frac{f}{f_o}\right) \Bigg|_0^\infty = \frac{\bar{V}_{nw} \pi f_o}{2}$$

If this same input signal,  $V_{nw}$ , is applied to the (brick-wall) filter

$$\bar{V}_{brick(rms)}^2 = \int_0^{f_x} \bar{V}_{nw}^2 df = \bar{V}_{nw}^2 f_x \quad , \quad \text{since } V_{n,out} = V_{brick} \quad , \quad \text{then } f_x = \frac{\pi f_o}{2}$$



# Equivalent Noise Bandwidth

$$\Delta f = \frac{1}{A_{vo}^2} \int_0^{\infty} |A_v(f)|^2 df$$





## Examples

$$A_v(f) = \frac{1}{1 + j \frac{f}{f_{3dB}}} \quad , \quad \Delta f = \int_0^{\infty} \frac{df}{1 + \left( \frac{f}{f_{3dB}} \right)^2} = 1.571 f_{3dB}$$

$$A_v(f) = \left| \frac{1}{1 + j \frac{f}{f_{3dB}}} \right|^2 \quad , \quad \Delta f = \int_0^{\infty} \left| \frac{1}{1 + \left( \frac{f}{f_{3dB}} \right)^2} \right| df = 1.22 f_a = 1.22 \times 0.6436 f_{3dB}$$

- Amplitude Distribution of Noise

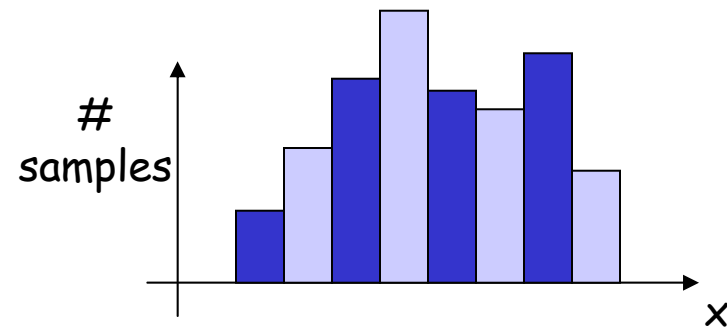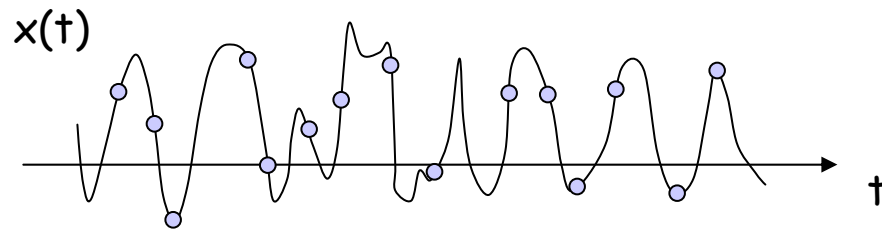

Probability Density Function (PDF), the distribution of  $x(t)$  is

$$p_x(x)dx = \text{probability of } x < X < x + dx$$

- An important example of PDFs is the Gaussian (or normal) Distribution.

$$p_x(x) = \frac{1}{\sigma\sqrt{2\pi}} \exp\left\{-\frac{(x-m)^2}{2\sigma^2}\right\}$$

Where  $\sigma$  and  $m$  are the standard deviation and mean of the distribution, respectively.

- How do you determine the total average power due to two or more noise sources?

$$P_{av} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} [x_1(t) + x_2(t)]^2 dt = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} (x_1^2(t) + x_2^2(t) + 2x_1(t)x_2(t)) dt$$

$$P_{av} = P_{av_1} + P_{av_2} + \underbrace{\lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} 2x_1(t)x_2(t) dt}_{= 0? \text{ When?}}$$

If noise sources are uncorrelated the third term is zero.



Example of uncorrelated and correlated noises is that of spectators in a sports stadium.





# Noise Types

- Device Electronics Noise
- Environmental Noise

## • Thermal Noise

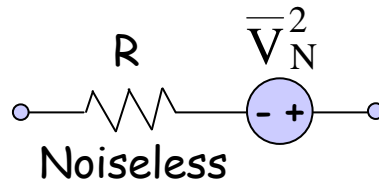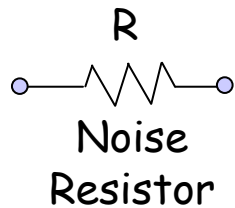


$$\bar{V}_N^2 = 4KTR$$

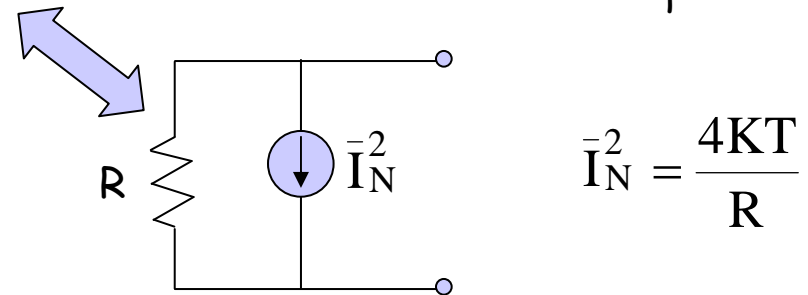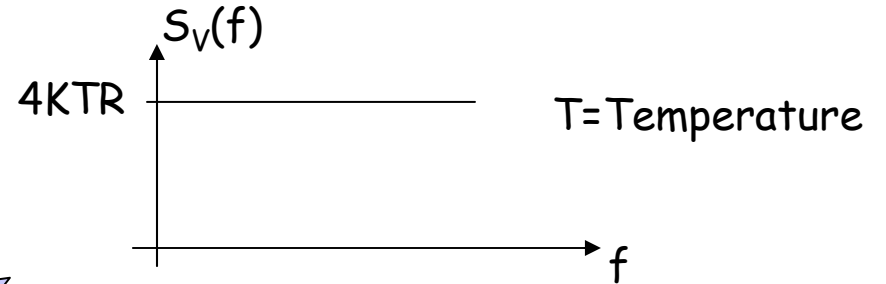
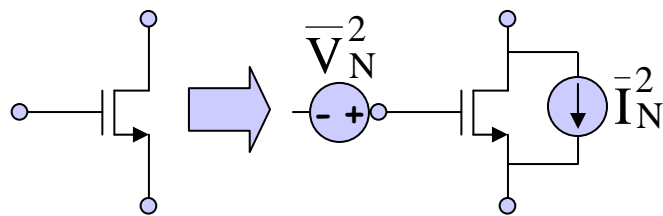
## Example

$$R = 50\Omega \quad T = 300^\circ\text{K} \Rightarrow \bar{V}_N^2 = 8.28 \times 10^{-19} \text{V}^2/\text{Hz} \Rightarrow (0.91 \text{ nV}/\sqrt{\text{Hz}})^2$$




Noisy

$$\bar{I}_N^2 = 4KT \left( \frac{2}{3} \right) g_m \Rightarrow \text{Thermal (White) Noise}$$

$$\bar{V}_N^2 = \frac{K_{\text{dev}}}{WLC_{\text{ox}} f} \Rightarrow \text{Flicker Noise}$$

# Noise Voltage

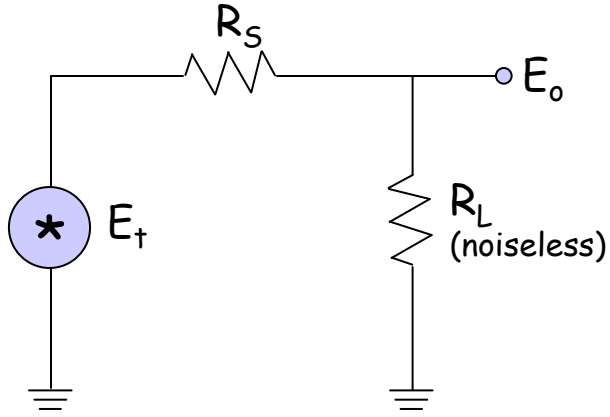

## Power Supplied to $R_L$ is



$$P_t = I_o E_o = \frac{E_o^2}{R_L}$$

$$P_t \left| \begin{array}{l} = \frac{E_t^2}{4R} = KT\Delta f \\ R_S = R_L = R \end{array} \right. , \quad E_o = \frac{E_t}{2R} R = \frac{E_t}{2}$$

Then

$$E_t = \sqrt{4kTR\Delta f} \quad (V_{\text{rms}})$$

$$E_t \left| \begin{array}{l} R = 1K\Omega \\ \Delta f = 1\text{Hz} \end{array} \right. = 4\text{n} \text{ V}_{\text{rms}}$$

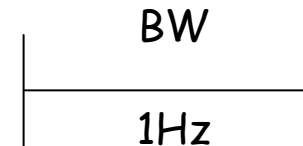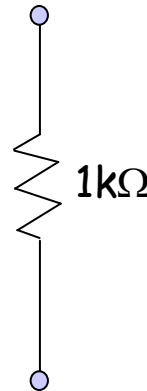


- Flicker or 1/f Noise

PSD is given by

$$\overline{V_n^2}(f) = \frac{K_V^2}{f} = \left( \frac{K_V}{\sqrt{f}} \right)^2 = \frac{K}{C_{ox} WL f}$$

for a CMOS

$$K \sim 10^{-25} V^2 F$$

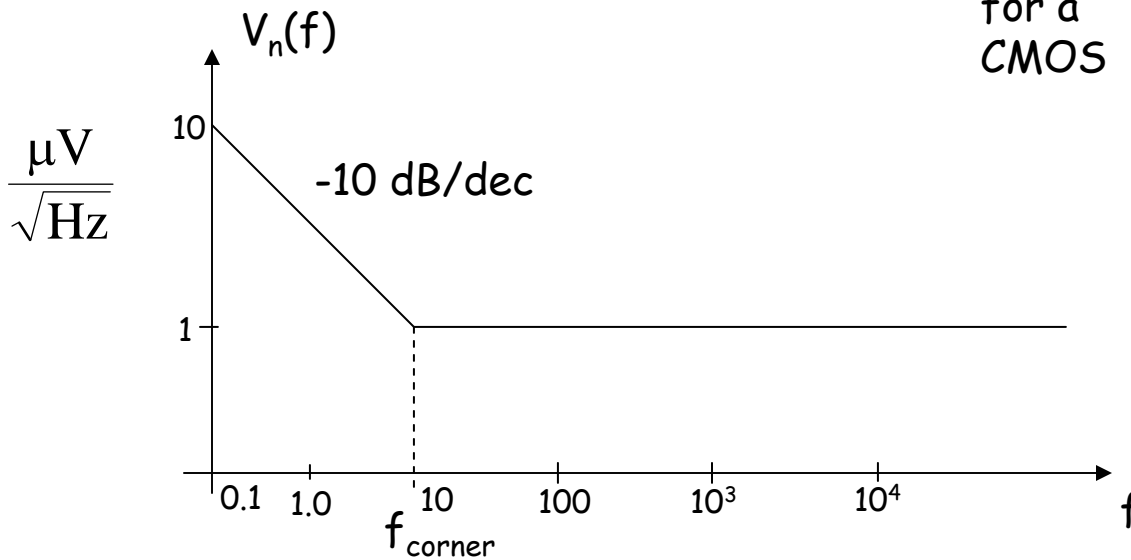

1/f noise dominates

white noise dominates

Low Frequency



High Frequency

Equating output currents

$$4KT \left( \frac{2}{3} g_m \right) = \frac{K}{C_{ox} WL f_c} g_m^2$$

$$f_c = \frac{K}{C_{ox} WL} g_m \frac{3}{8KT} \quad 14$$

# Noise Considerations

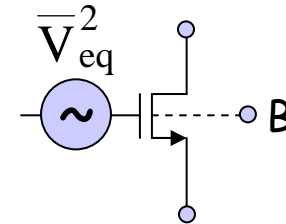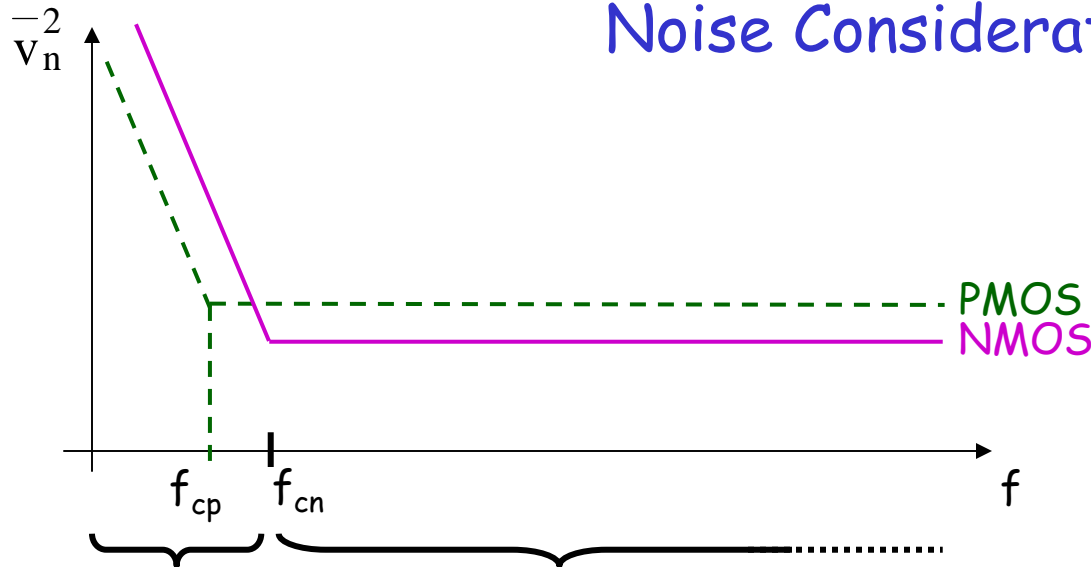

$$\eta = \frac{g_{mb}}{g_m}$$

Flicker Noise

Thermal or Johnson Noise (White Noise)

$$\overline{V}_N^2 = \overline{V}_{eq}^2 = \underbrace{\left\{ \frac{KF \cdot \Delta f}{2fC_{ox} K_p WL} \right\}}_{\text{Flicker Noise}} + \underbrace{\frac{8kT(1+\eta)}{3g_m} \Delta f}_{\text{White Noise}}$$

- To reduce Flicker Noise:

Increase  $W * L$  (Area)

To keep same bias point keep same ( $W/L$ )

i.e.,

$$KF_p = 2.7 \times 10^{-21} \text{ A}$$

$$KF_n = 4.3 \times 10^{-21} \text{ A}$$

Flicker Noise

White Noise

- To reduce White Noise

Increase  $g_m$ . Since  $g_m \cong \sqrt{2K_p I_D \left( \frac{W}{L} \right)} = K_p (V_{gs} - V_T) \frac{W}{L}$

(a)  $(W/L) \uparrow$  and  $(I_D) \uparrow$  will increase  $g_m$ , power consumption ( $I_D$ ), and area


(b)  $(W/L) \uparrow$  and modify the bias to keep  $I_D$  same as before increasing  $g_m$ .

How to compute the total output noise due to individual noise sources?

How to compute the input-referred noise?

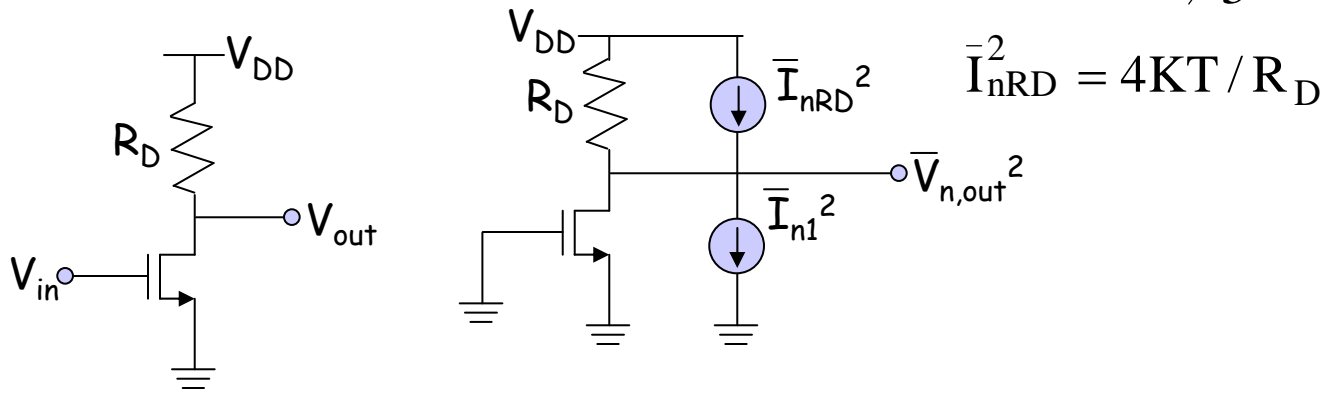Example.\_\_\_\_\_

$$\bar{I}_{n1}^2 = 4KT \left( \frac{2}{3} \right) g_m + K g_m^2 / (C_{ox} W L f)$$



$$\bar{I}_{nRD}^2 = 4KT / R_D$$


$$\bar{V}_{n,out}^2 = \left( 4KT \frac{2}{3} g_m + \frac{K}{C_{ox} W L f} g_m^2 + \frac{4KT}{R_D} \right) R_D^2 \quad \text{in 1Hz at frequency } f$$

$$\bar{V}_{n,in}^2 = \frac{\bar{V}_{n,out}^2}{A_V^2} \cong \frac{1}{g_m^2 R_D} \left( \bar{V}_{n,out}^2 \right)$$

$$\bar{V}_{n,in}^2 = 4KT \frac{2}{3g_m} + \frac{K}{C_{ox} W L f} + \frac{4KT}{g_m^2 R_D} \quad \longrightarrow \quad \text{Good performance parameter}$$



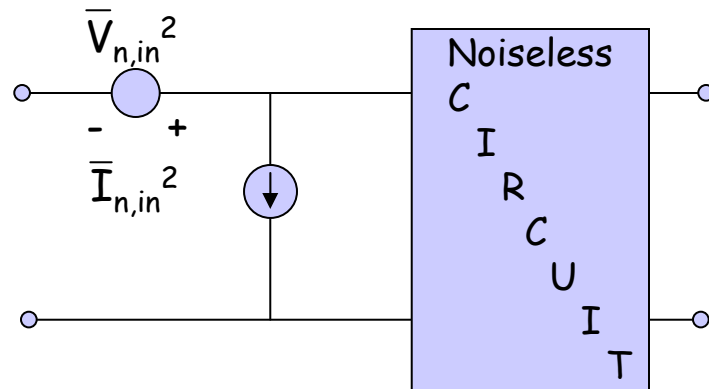- Can we always use the input-referred noise by a single voltage source in series with the input?



A necessary and sufficient representation




- Simplifications

- For zero source impedance,  $\bar{I}_{n,in}^2$  not affecting the output
- For infinite source impedance, then  $\bar{V}_{n,in}^2$  has no effect

- Note that both sources will not count the noise twice.

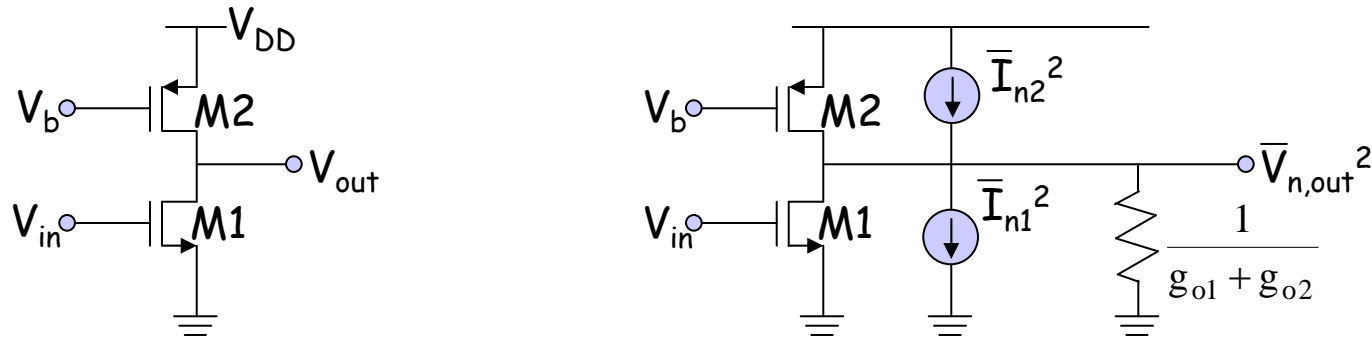For the following amplifier and from the point of view, of minimum noise, how the values of  $g_{m1}$  and  $g_{m2}$  should be set?



Considering the thermal noise:

$$\overline{V_{n,out}^2} = 4KT \left( \frac{2}{3} g_{m1} + \frac{2}{3} g_{m2} \right) \frac{1}{(g_{o1} + g_{o2})^2}$$

$$A_v = \frac{g_{m1}}{g_{o1} + g_{o2}}$$


$$\overline{V_{n,inp}^2} = \frac{\overline{V_{n,out}^2}}{A_v^2} = 4KT \left( \frac{2}{3g_{m1}} + \frac{2}{3} \frac{g_{m2}}{g_{m1}^2} \right)$$

$$\overline{V_{n,inp}^2} \downarrow g_{m1} \uparrow g_{m2} \downarrow (\text{current - source})$$

Trade-offs of increasing  $g_{m1}$ ?



# Noise Analysis, p driver, n load.

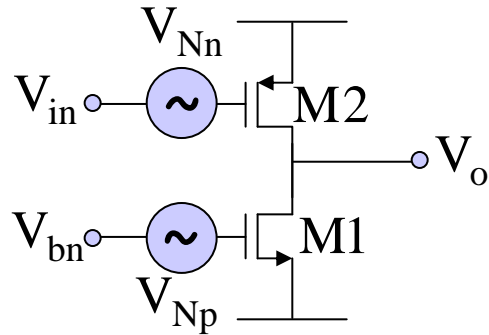

Make  $V_{in}$  and  $V_{bn}$  null

$$v_{oN}^2 = \left( \frac{g_{m2}}{g_{o1} + g_{o2}} \right)^2 \bar{V}_{Nn}^2 + \left( \frac{g_{m1}}{g_{o1} + g_{o2}} \right) \bar{V}_{Np}^2$$

$$A_V^2 = \frac{g_{m2}^2}{(g_{o1} + g_{o2})^2}$$

Equivalent input-noise spectral density

$$\bar{V}_{N_{INP}}^2 = \frac{\bar{v}_{oN}^2}{A_V^2} = \frac{(g_{o1} + g_{o2})^2}{g_{m2}^2} \left[ \frac{g_{m2}^2 \bar{V}_{Nn}^2}{(\quad)^2} + \frac{g_{m2}^2 \bar{V}_{Np}^2}{(\quad)^2} \right]$$

$$\bar{V}_{N_{INP}}^2 = \bar{V}_{Nn}^2 + \frac{g_{m1}^2}{g_{m2}^2} \bar{V}_{Np}^2$$

To reduce the equivalent input-noise spectral

$g_{m1}$  ↓  
for bias device


$g_{m2}$  ↑  
for signal (driver) device



To compute the rms output noise:

(i) Compute the frequency response bandwidth  $f_{3dB}$

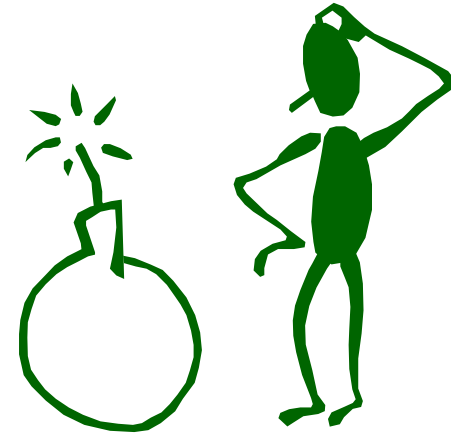(ii) Compute the noise bandwidth,  $\Delta f$




$$\Delta f = 1.571 * f_{3dB} \quad (\text{assuming a single pole})$$


(iii) 
$$V_{\text{out,noise}} = \left\{ \overline{V}_{\text{n,out}}^2 \cdot \Delta f \right\}^{1/2} V_{\text{rms}}$$

where  $\overline{V}_{\text{n,out}}^2$  is the spectral density value of the output noise at low frequency.


# Issues about noise sources

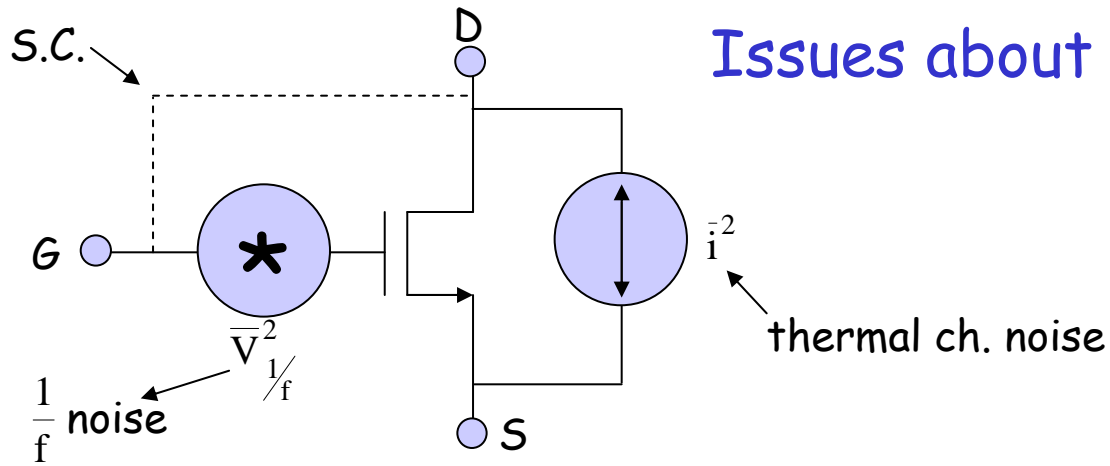

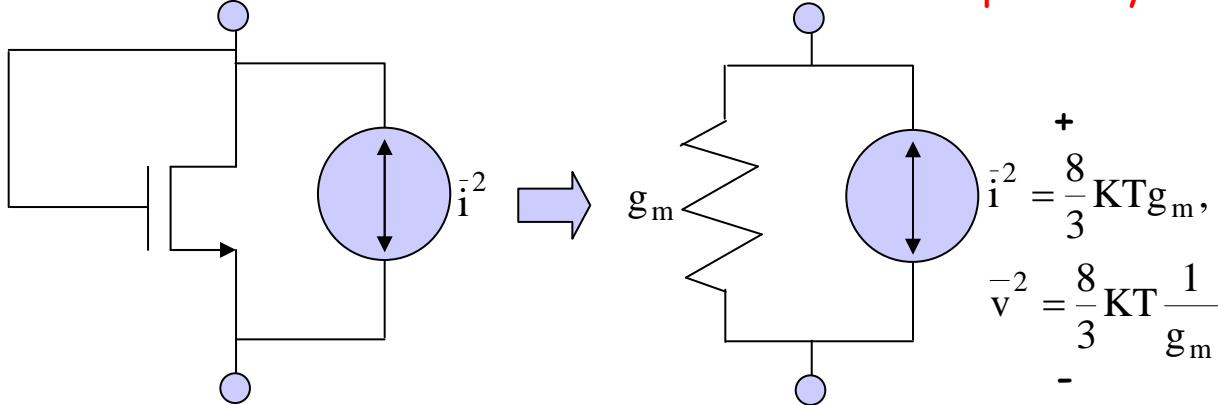If thermal channel noise is considered separately




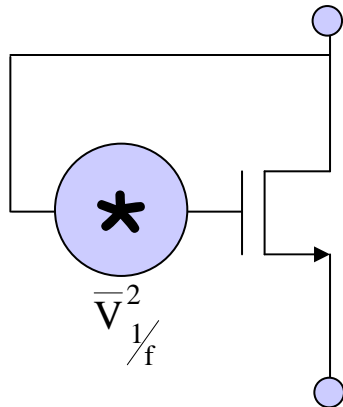If the 1/f noise is considered separately



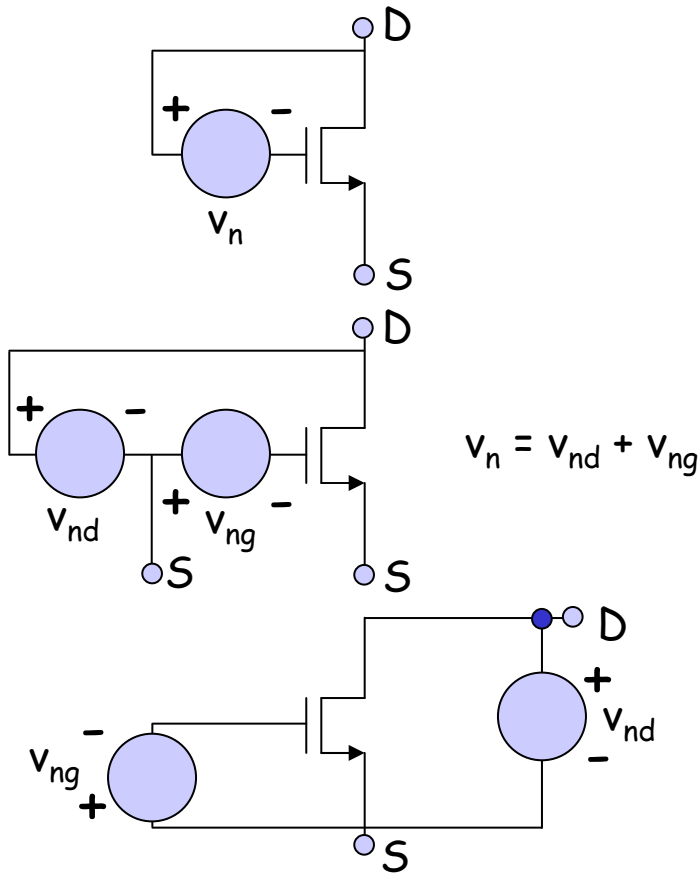The noise can be seen as a drain-source noise voltage source equal to  $v_{1/f}^2$  (see next page)





$$v_{nd} = g_m r_o v_{ng} \text{ (must be satisfied)}$$


$$v_n = v_{nd} + v_{ng}$$

$$= v_{ng} (1 + g_m r_o)$$

or

$$v_n = v_{nd} (1 + 1/g_m r_o)$$

$$v_n \approx v_{nd} = v_{ds}$$

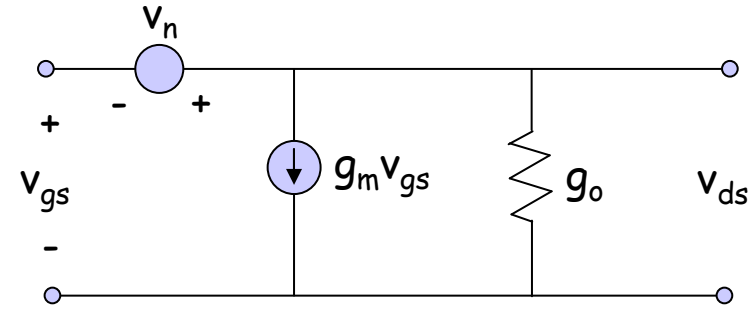

$$V_{gs} = V_d + V_n - V_s$$

$$= V_{ds} + V_n$$

$$V_{ds} = -\frac{g_m V_{gs}}{g_o}$$

$$\therefore V_{ds} = \frac{V_n}{(1 + g_m r_o)}$$


$$\& V_{ds} = -\frac{g_m r_o}{1 + g_m r_o} v_n$$

$$\text{or } \overline{V_{gs}^2} = \frac{\overline{V_n^2}}{(1 + g_m r_o)^2} \cong \frac{\overline{V_n^2}}{(g_m r_o)^2}$$


$$\& \overline{V_{ds}^2} = \frac{\overline{V_n^2} \times (g_m r_o)^2}{(1 + g_m r_o)^2} \cong \overline{V_n^2}$$

So for a diode the  $1/f$  noise shows up as a noise voltage (shrinking the diode) of value equal to  $\overline{v_n^2}$ .

## Noise in an op amp macromodel

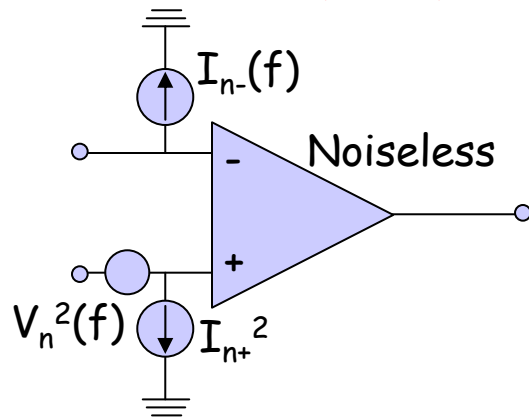

### Particular Cases:

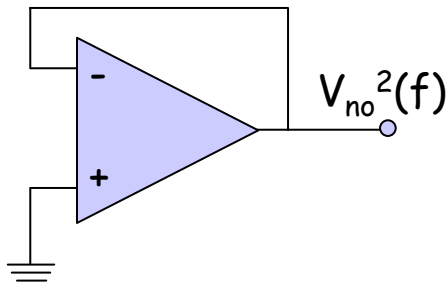


If  $\bar{V}_n^2(f)$  ignored:

$$\bar{V}_{no}^2 = 0$$

Actual:

$$\bar{V}_{no}^2 = \bar{V}_n^2$$

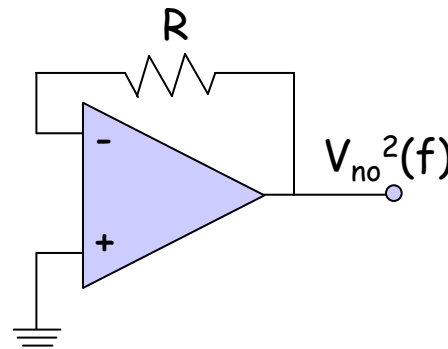


If  $I_n(f)$  ignored:

$$\bar{V}_{no}^2 = \bar{V}_n^2$$

Actual:
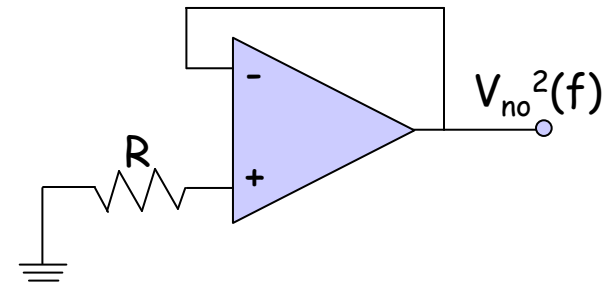
$$\bar{V}_{no}^2 = \bar{V}_n^2 + (I_{n-}R)^2$$



If  $I_{n+}(f)$  ignored:


$$\bar{V}_{no}^2 = \bar{V}_n^2$$

Actual:

$$\bar{V}_{no}^2 = \bar{V}_n^2 + (I_{n+}R)^2$$

- Ideal capacitors and inductors do not generate noise, but accumulate.
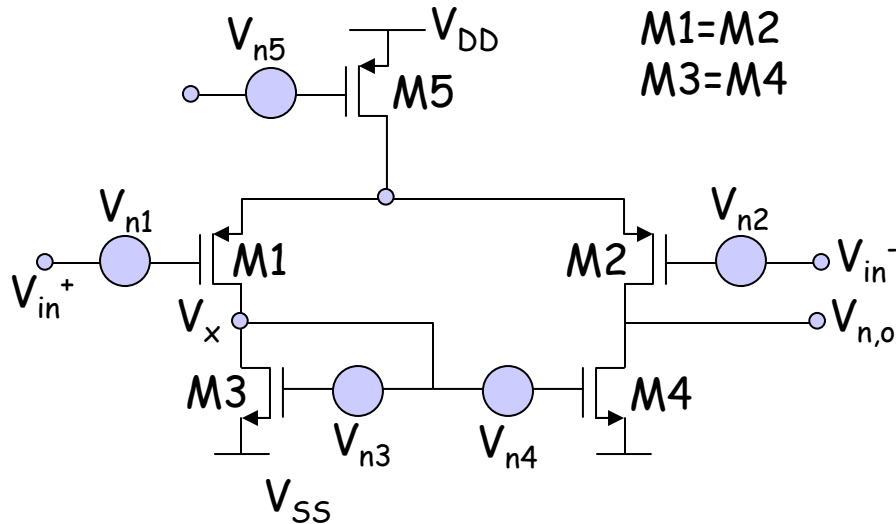
# CMOS Simple OTA: Noise Analysis Example



M1=M2  
M3=M4

- First determine the gain from the noise sources to the output

$$\left| \frac{V_{n,o}}{V_{n1}} \right| = \left| \frac{V_{n,o}}{V_{n2}} \right| = g_{m1} R_o \stackrel{?}{=} \left| \frac{V_n}{V_{in}^+ - V_{in}^-} \right| = A_V$$

$$\left| \frac{V_{n,o}}{V_{n4}} \right| = g_{m4} R_o$$

Assuming  $V_x = V_{n,o}$  ;  $R_{ox} \cong \frac{1}{g_{m3}}$

$$\left| \frac{V_{n,o}}{V_{n5}} \right| = \frac{g_{m5}}{2g_{m3}} \quad (\text{small})$$

since  $V_{gs3} = V_{gs4} \Rightarrow V_{n3} = V_{n4}$ , then

$$\left| \frac{V_{n,o}}{V_{n3}} \right| = g_{m4} R_o$$

$$V_{n,o}^2(f) = 2(g_{m1} R_o)^2 V_{n1}^2(f) + 2(g_{m3} R_o)^2 V_{n3}^2(f)$$

$$V_{n,input}^2(f) = 2V_{n1}^2(f) + 2V_{n3}^2 \left( \frac{g_{m3}}{g_{m1}} \right)^2$$

$$V_{n,input}^2(f) \Big|_{\text{white part}} = \left( \frac{16}{3} \right) kT \left( \frac{1}{g_{m1}} \right) + \left( \frac{16}{3} \right) kT \left( \frac{g_{m3}}{g_{m1}} \right)^2 \frac{1}{g_{m3}} \quad ; \quad V_{n,input}^2(f) \downarrow \quad g_{m1} \uparrow$$

1 <  $g_{m1} / g_{m3}$  < 4 ? 24



For the white noise portion of  $V_{ni}(f)$  and  $V_{n3}(f)$

$$V_{ni}^2 = 4KT \left( \frac{2}{3} \right) \left( \frac{1}{g_{m1}} \right) \quad i = 1, 3$$

Yielding

$$V_{n,input}^2 (f) = \left( \frac{16}{3} \right) KT \left( \frac{1}{g_{m1}} \right) + \left( \frac{16}{3} \right) KT \left( \frac{g_{m3}}{g_{m1}} \right) \left( \frac{1}{g_{m3}} \right) \quad ; \quad g_{m1} \uparrow ?$$

On the other hand, for the 1/f noise

$$V_{n,input}^2 (f) \left| \begin{array}{l} = 2V_{n1}^2 + 2V_{n3}^2 (f) \frac{\mu_n \left( \frac{W}{L} \right)_3}{\mu_p \left( \frac{W}{L} \right)_1} \\ g_m = \{ 2\mu_j C_{ox} \left( \frac{W}{L} \right)_j I_{Dj} \} \end{array} \right.$$

Yielding

$$V_{n,input}^2 (f) = \frac{2}{C_{ox} f} \left[ \frac{K_1}{W_1 L_1} + \left( \frac{\mu_n}{\mu_p} \right) \left( \frac{K_3 L_1}{W_1 L_3^2} \right) \right]$$

For  $V_{ni}^2 (f) = \frac{K_i}{W_i L_i C_{ox} f}$

$L_3 \uparrow V_{n,input}^2 \downarrow$  but signal swing  $\downarrow$

By integrating from  $f_1$  to  $f_2$

$$V_{n,input}^2 (rms) = 2 \left[ \frac{a_p}{W_1 L_1} + a_n \left( \frac{\mu_n}{\mu_p} \right) \frac{L_1}{L_3^2 W_1} \right] \quad ; \quad a_i = \frac{K_i}{C_{ox}} \ln \left( \frac{f_2}{f_1} \right)$$

## How do you simulate noise in SPICE?

- Noise is associated with AC analysis
- Noise V(N) VIN
- AC DEC FI FSTEP FFINAL

Reader.\_\_\_\_\_



Simulate both examples dealing with two transistors, plot frequency responses and noise spectrum, as well as the total noise at each frequency (total rms noise)

Obtain the signal to noise ratio

$$\frac{S}{N} = 20 \log \frac{\text{signal for \% THD (rms)}}{\text{Total Noise (rms)}}$$

# References

1. B. Razavi, "*Design of Analog CMOS Integrated Circuits*", Preview Edition, Mcgraw Hill, 2000.
2. D.A. Johns and K. Martin, *Analog Integrated Circuit Design*, New York; Wiley, 1997.
3. M.S. Gupta, "*Selected papers on Noise in Circuits and Systems*", IEEE Press 1998.
4. P.E. Allen and D. R. Holberg, "*CMOS Analog Circuit Design*" 2<sup>nd</sup> Edition. Chapter 7.5, New York, Oxford University Press 2002