

FALL 2011
ELEN 622 (ESS)

Name KEY

EXAM #1

This is a closed book and notes exam. One information page allowed for this exam. This exam is worth 25% of your total grade. One extra credit point is added.

Problem	Maximum	Yours
1	7	
2	6	
3	6	
4	6	
Extra Credit	1	
Total	26	

Problem 1. Write a block diagram implementation and obtain the $H(s) = \frac{V_{out}(s)}{V_{in}(s)}$

Sketch its frequency response for different R_1/R_K ratios.


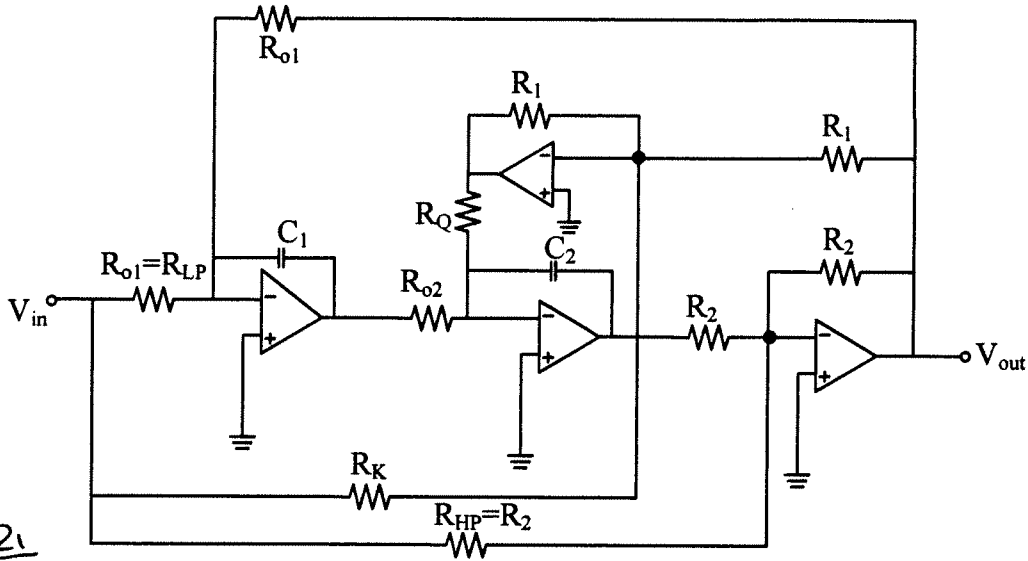
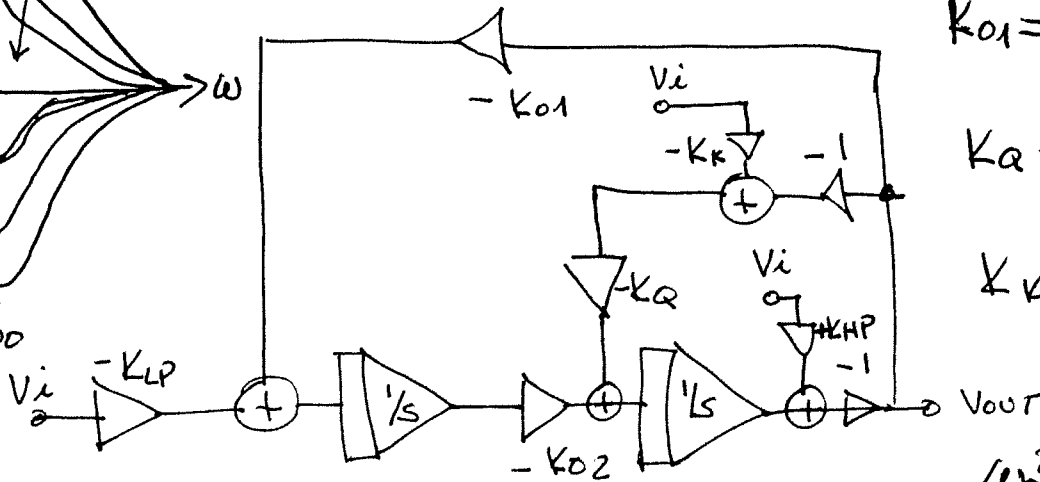


Figure 1 Magnitude Equalizer Circuit Diagram

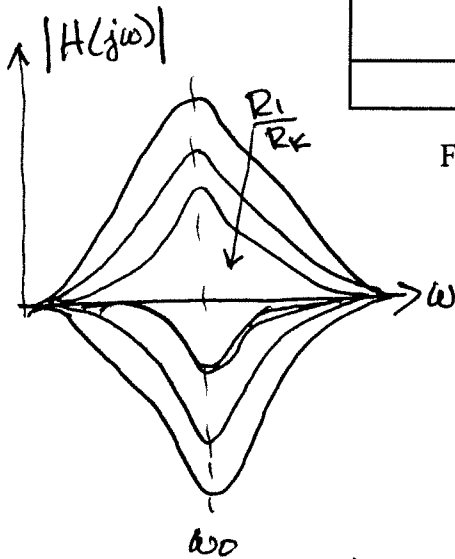

$$K_{o1} = \frac{1}{R_{o1} C_1}$$

$$K_a = \frac{1}{R_Q C_2}$$

$$K_K = \frac{R_1}{R_K}$$


$$\omega_0^2 = \frac{1}{R_{o1} R_{o2} C_1 C_2}$$

$$H(s) = \frac{K_{o1} K_{o2} + \frac{-K_K K_a}{s} - K_{HP}}{1 + \frac{K_{o1} K_{o2}}{s^2} + \frac{K_a}{s}}$$


$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{K_{HP} s^2 + K_K K_a s + K_{o1} K_{o2}}{s^2 + s K_a + K_{o1} K_{o2}}$$

NOTE THAT $K_{HP} = 1$

Problem 2.

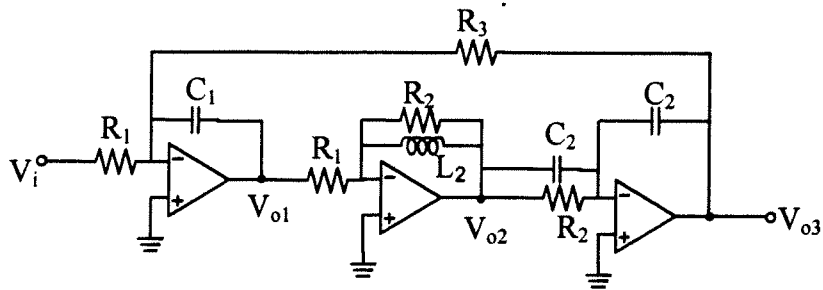

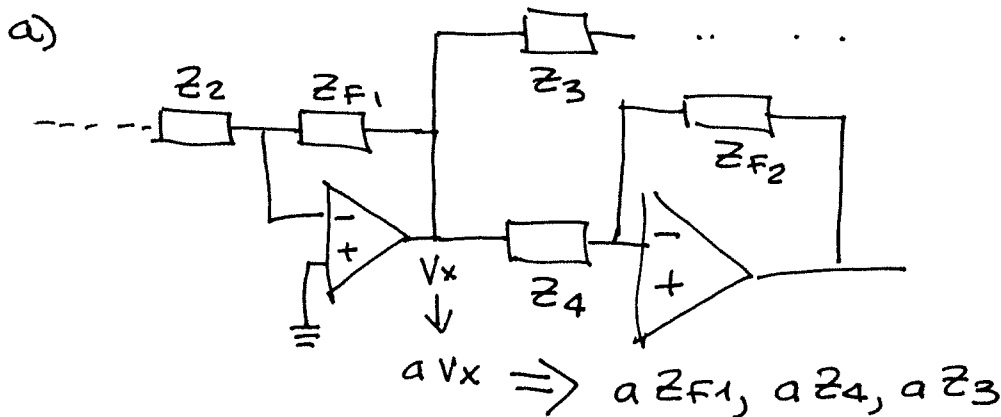
- a) Assume we want to increase V_{02} to aV_{02} but keep V_{01} and V_{03} unchanged. Determine the components to be modified and how.
- $R_2 \rightarrow aR_2, L_2 \rightarrow aL_2, C_2 \rightarrow C_2/a, R_2 \rightarrow aR_2$
- b) Assume the circuit shown above is normalized to a cut-off frequency $\omega_c=1$ and we want to scale to ω_s , show what elements and how need to be scaled.
- c) Do an impedance scaling by a factor R_s . Indicate how the elements are modified.



- b) $Z(s) \rightarrow Z(\omega_s \cdot s) \Rightarrow$ NO CHANGE FOR R'S
- $C_i \rightarrow \omega_s C_i$ OR $C_i = \frac{C_{ni}}{\omega_s}$ — NORMALIZED CAPACITOR
- $L_i \rightarrow \omega_s L_i$ OR $L_i = \frac{L_{ni}}{\omega_s}$ — NORMALIZED INDUCTOR


- c) $Z(s) \rightarrow R_s Z(s)$
- $R_i \rightarrow R_s R_i$
- $C_i \rightarrow C_i / R_s$
- $L_i \rightarrow R_s L_i$

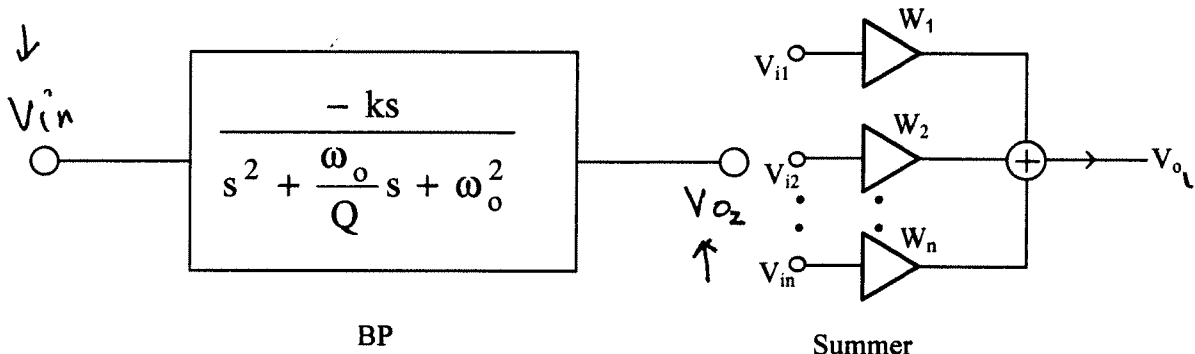Problem 3. You have been hired by a small company and your first job is to design a symmetric notch filter. However, you only have in your company stock a commercial bandpass filter and a (resistance) summer. How would you combine the BP and summer to yield a symmetric notch filter? Specify the optimal value of k yielding the symmetric notch.



SOLUTION:
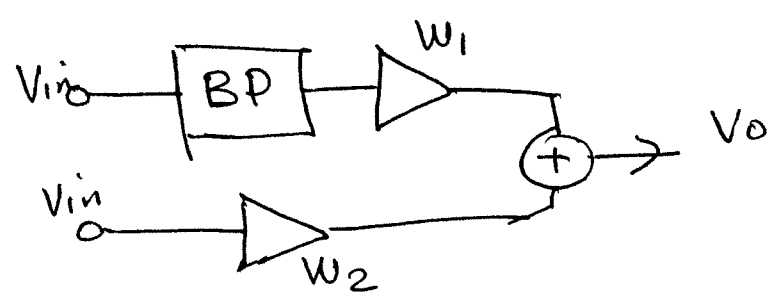
$$k = \frac{W_2}{W_1} \frac{\omega_0}{Q}$$




DETAILS:

$$V_o = \frac{-ks \cdot W_1 + W_2 s^2 + W_2 s \frac{\omega_0}{Q} + W_2 \omega_0^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} V_{in}$$

$$H(s) = \frac{V_o}{V_{in}} = \frac{W_2 s^2 + s(W_2 \frac{\omega_0}{Q} - kW_1) + W_2 \omega_0^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

NOTE THAT FOR $k = \frac{W_2}{W_1} \frac{\omega_0}{Q}$, $H(s)$ YIELDS OR $W_1 = \frac{k \omega_0}{Q}$ (if $W_2 = 1$)

$$H(s) \Big|_{k = \frac{W_2 \omega_0}{Q}} = W_2 \frac{s^2 + \omega_0^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

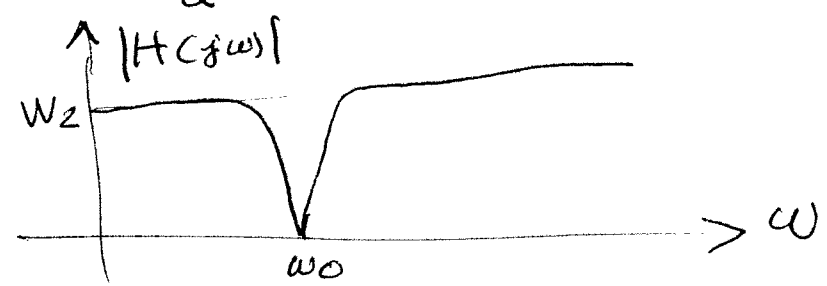

Problem 4. An OTA with three current-mirrors has an input impedance equal to

$R_{in} // (1/sC_{in})$, an output impedance $Z_o = \frac{1}{\frac{1}{R_o} + sC_o}$. The voltage gain amplifier has the




following transfer function:

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{GB}{s} \frac{1 + s/\omega_z}{(1 + s/\omega_{n2})(1 + s/\omega_{n3})(1 + s/\omega_{n4})}$$


Note that Z_{in} and Z_o should not affect $H(s)$.

Propose an OTA macromodel implementing Z_{in} , Z_o and $H(s)$ using SPICE primitive elements i.e., R, C, L, and dependent sources.

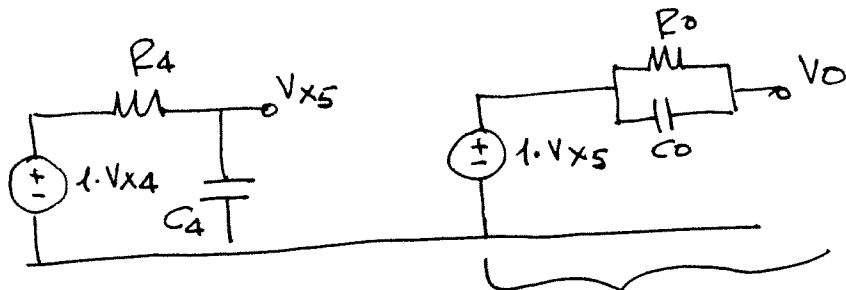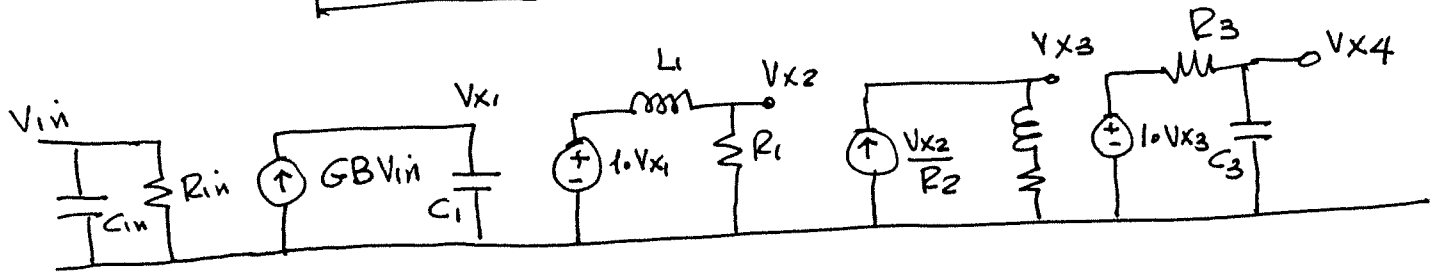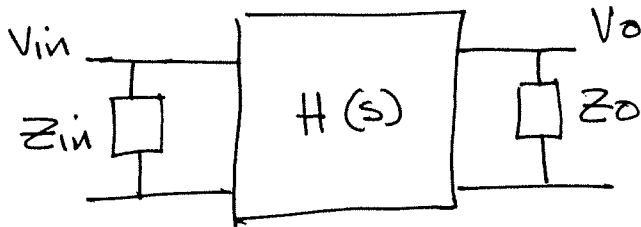
THERE ARE MANY WAYS TO SATISFY THE ABOVE REQUIREMENTS,
AN EXAMPLE FOLLOWS.



OR

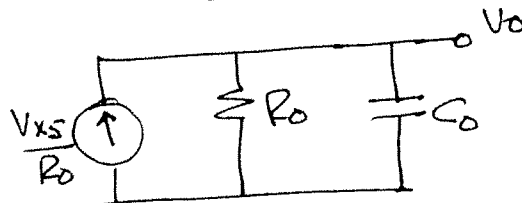

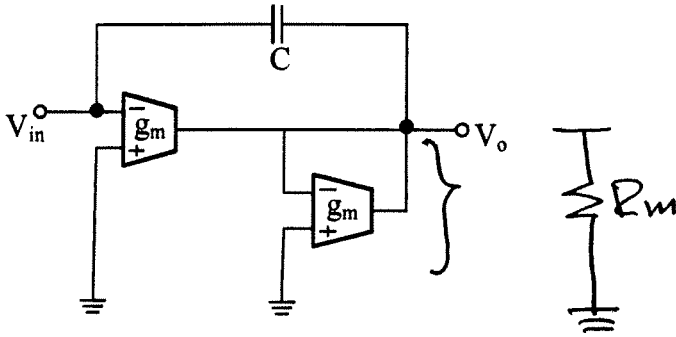EXTRA CREDIT (No partial credit). — Obtain $H(s)$ and identify the type of filter.



$$V_o \left(\frac{1}{R_m} + sC \right) - V_{in} sC - g_m V_{in} = 0$$

$$V_o = \frac{(-g_m + sC) V_{in}}{g_m + sC} = \frac{-1 + sC/g_m}{1 + sC/g_m} V_{in}$$

$$\frac{V_o}{V_{in}} = \frac{-1 + as}{1 + as} = \frac{1 - as}{1 + as} \quad \text{A.P.}$$

$$\text{where } a = \frac{C}{g_m}$$