

Operational Transconductance - C (OTA-C) and Current-Mode Filter Structures and Practical Issues

- **OTA-C Filter Topologies**
- **OTA-C Filter Non-idealities**
- **Pseudo Differential OTA**
- **OTA-C BP Least Mean Square Tuning Scheme**
- **How to use a conventional OTA as a filter by adding capacitances at the internal nodes.**



Applications for continuous time filters



Read channel of disk drives --
for phase equalization and
smoothing the wave form

Top view of a 36 GB, 10,000 RPM,
IBM SCSI server hard disk, with its
top cover removed.



Receivers and Transmitters in wireless applications -- used in PLL and for image rejection




6185i digital cell phone from Nokia.




CMP-35 portable MP3 player

All multi media
applications --Anti
aliasing before ADC and
smoothing after DAC

LOSSY OTA-C INTEGRATORS

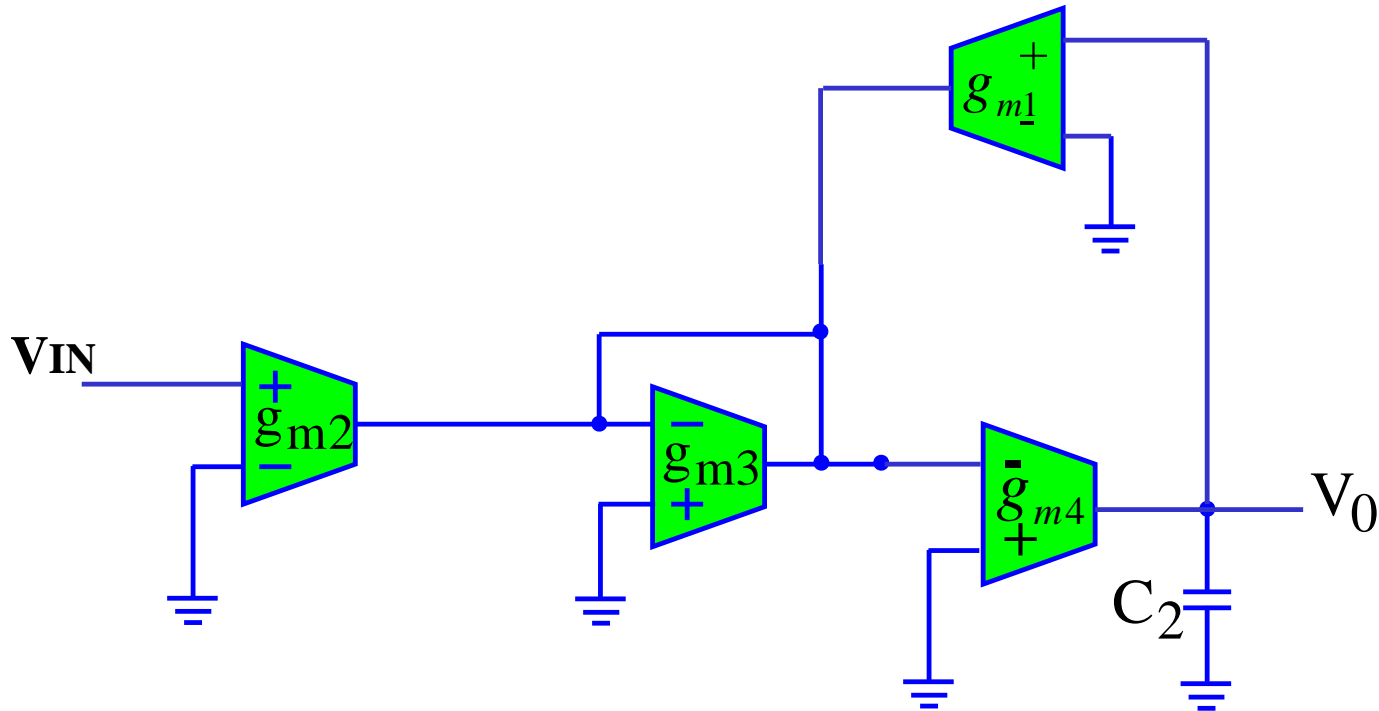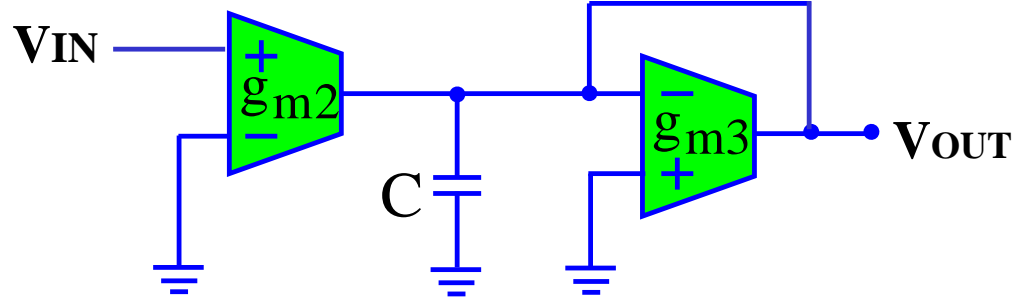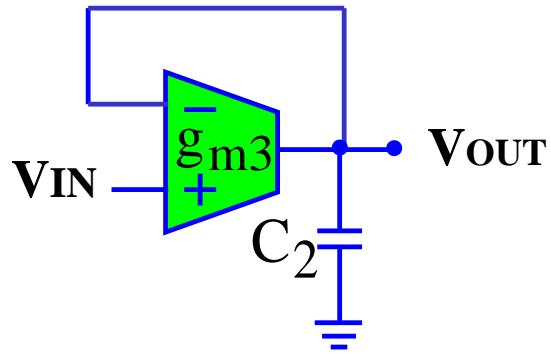


OTA-C Two Integrator Loop Filters

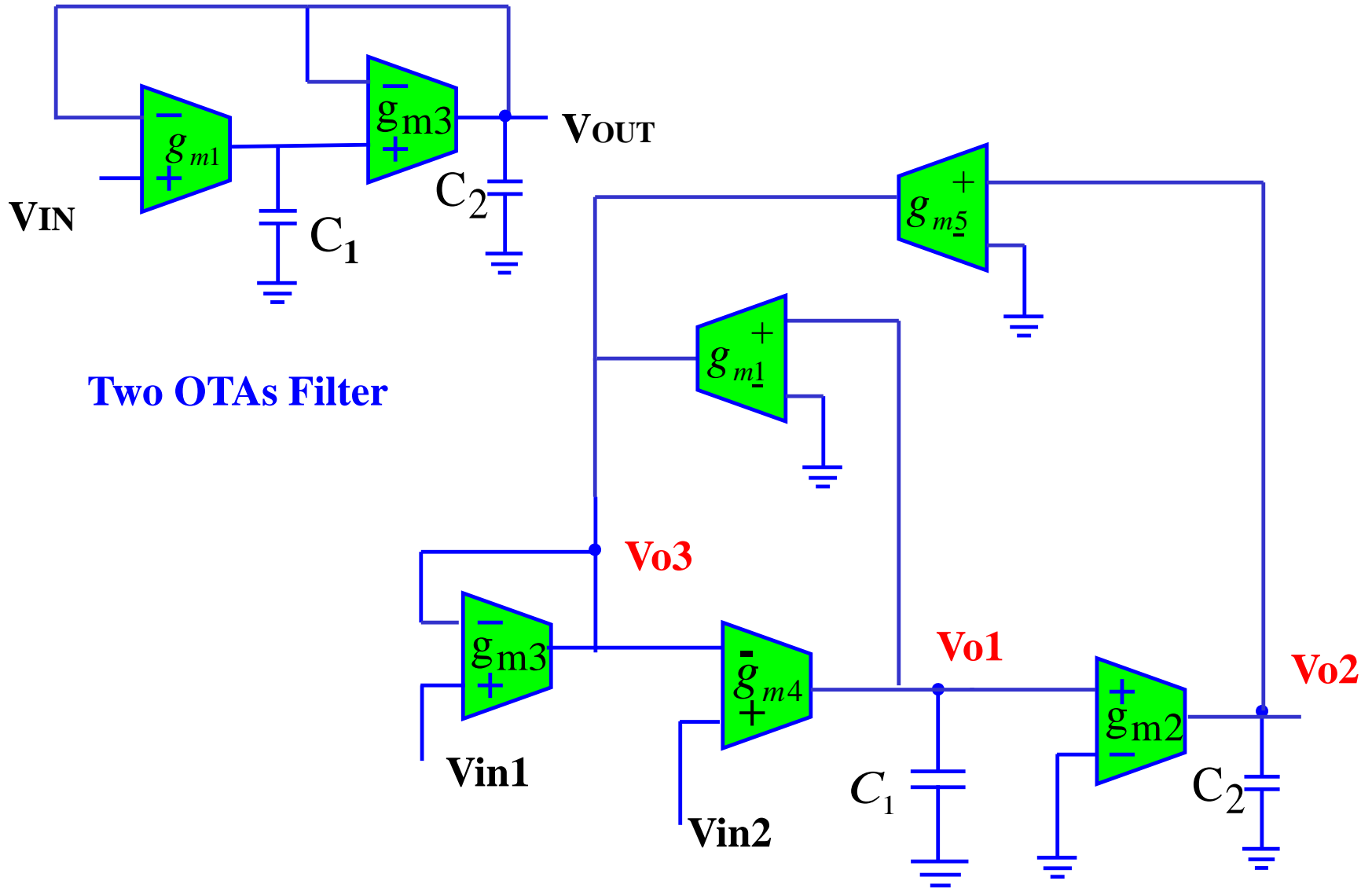

KHN OTA-C Version


How to generate the zeros of the filter ?

Canonic OTA-C Biquad

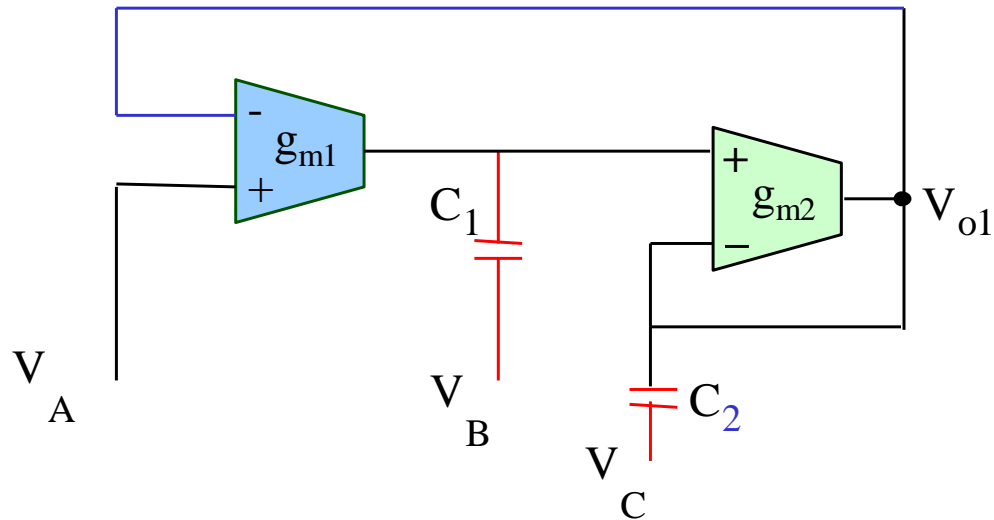

$$V_{o1} = \frac{s^2 C_1 C_2 V_C + s C_1 g_{m2} V_B + g_{m1} g_{m2} V_A}{s^2 C_1 C_2 + s C_1 g_{m2} + g_{m1} g_{m2}}$$

Analog and Mixed-Signal Center

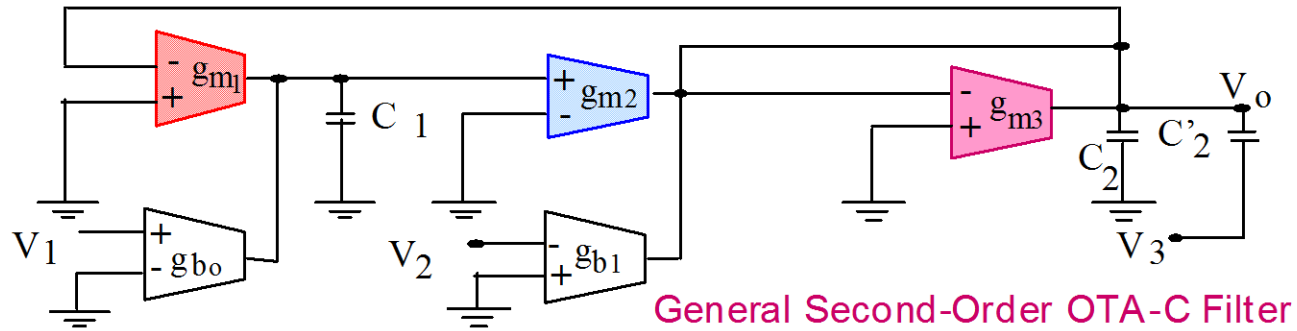

For $V_1=V_2=V_3$

$$H(s) = \frac{C_2}{C_2 + C'_2} \frac{s^2 - s \frac{g b_1}{C_2} + \frac{g b_0 g m_2}{C_1 C_2}}{s^2 + s \frac{g m_3}{(C_2 + C'_2)} + \frac{g m_1 g m_2}{C_1 (C_2 + C'_2)}}$$


$$\omega_0^2 = \frac{g m_1 g m_2}{C_1 (C_2 + C'_2)} \quad ; \quad \omega_z^2 = \frac{g b_0 g m_2}{C_1 C_2}$$

$$\frac{\omega_0}{Q} = \frac{g m_3}{(C_2 + C'_2)} \quad ; \quad \frac{\omega_z}{Q_z} = \frac{g b_1}{C_2}$$

$$|H(0)| = \frac{g b_0}{g m_1} \quad ; \quad |H(\infty)| = \frac{C_2}{C_2 + C'_2}$$

Analog and Mixed-Signal Center


INTERNAL VOLTAGE SCALING

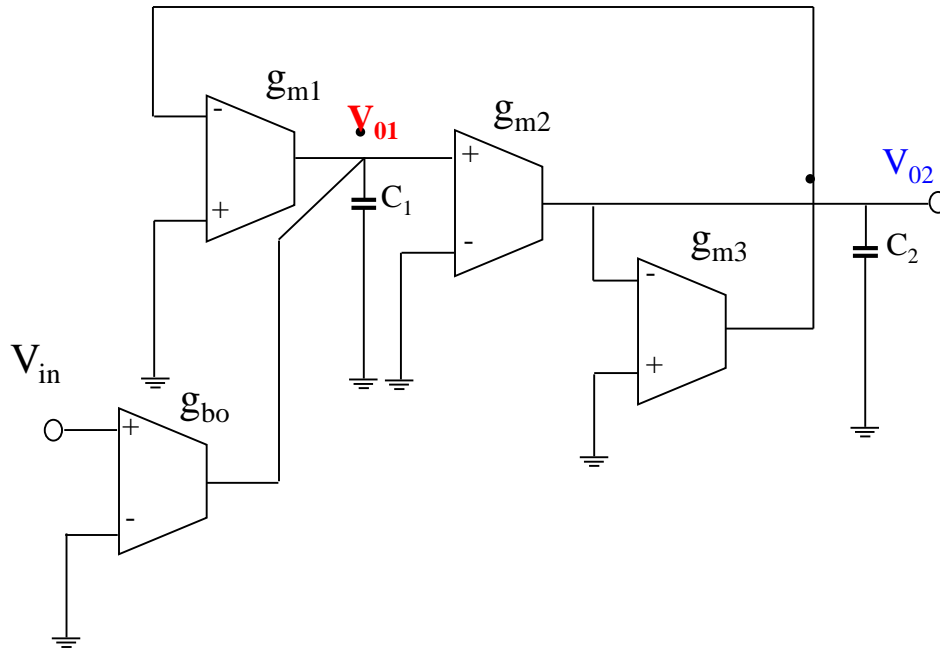

Assume the voltage V_{01} needs to be scaled by a factor “a” without changing the other node voltages:

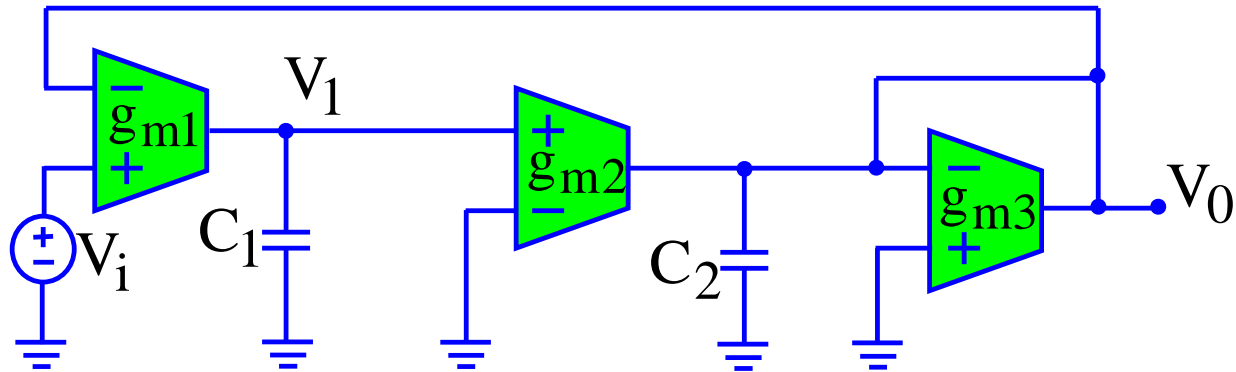1. The impedance at the node under consideration must be increased by “a”. In this case C_1 becomes C_1/a .
2. Multiply all the transconductances leaving that node by the factor “a”. In this case g_{m2} becomes ag_{m2} ,

OTA-C Three OTA Filter: Transfer Function Derivation taking into Account the OTA non-idealities.



Assume ideal OTAs first, then :

$$V_1 = \frac{1}{sC_1} g_{m1} (V_i - V_0) \quad (1)$$

$$V_0 = (g_{m2} V_1 - g_{m3} V_0) \frac{1}{sC_2} \quad (2)$$

(1) into (2)

$$(sC_2)V_0 = \left[g_{m2} \frac{g_{m1}}{sC_1} (V_i - V_0) - g_{m3} V_0 \right]$$

$$V_0 \left[sC_2 + \frac{g_{m1}g_{m2}}{sC_1} + g_{m3} \right] = \frac{g_{m1}g_{m2}}{sC_1} V_i$$

$$H_{LP}(s) = \frac{V_0}{V_i} = \frac{g_{m1}g_{m2}}{s^2C_1C_2 + sC_1g_{m3} + g_{m1}g_{m2}} = \frac{\frac{g_{m1}g_{m2}}{C_1C_2}}{s^2 + s\frac{g_{m3}}{C_2} + \frac{g_{m1}g_{m2}}{C_1C_2}}$$

$$\omega_0^2 = \frac{g_{m1}g_{m2}}{C_1C_2} \quad , \quad BW = \frac{\omega_0}{Q} = \frac{g_{m3}}{C_2}$$

$$Q = \frac{1}{g_{m3}} \sqrt{\frac{g_{m1}g_{m2}C_2}{C_1}} = \frac{C_2\omega_0}{g_{m3}}$$

Now let's assume the transconductance is characterized by:

$$g_m = g_{m0} e^{-s/\omega_p} \cong g_{m0} \left(1 - s/\omega_p\right) \text{ for } \omega_p \ll \omega_o.$$

Under this condition the excess phase can be expressed as $\phi_E \cong \omega_o / \omega_p$.

Note that ideally $\phi_E = 0^0$.

then,

$$H_{LP}(s) = \frac{g_{m01}g_{m02}(1 - s/\omega_{p1})(1 - s/\omega_{p2})}{s^2C_1C_2 + sC_1g_{m03}(1 - s/\omega_{p3}) + g_{m01}g_{m02}(1 - s/\omega_{p1})(1 - s/\omega_{p2})}$$

$$D(s) = s^2C_1C_2 + sC_1g_{m03} - s^2 \frac{C_1g_{m03}}{\omega_{p3}} + g_{m01}g_{m02} \left(1 - s \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) + \frac{s^2}{\omega_{p1}\omega_{p2}} \right)$$

$$D(s) = s^2 \left\{ C_1C_2 - \frac{C_1g_{m03}}{\omega_{p3}} + \frac{g_{m01}g_{m02}}{\omega_{p1}\omega_{p2}} \right\} + s \left\{ C_1g_{m03} - \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) g_{m01}g_{m02} \right\} + g_{m01}g_{m02}$$

Then the actual ω_{oa} and BW_a become

$$\omega_{oa}^2 = \frac{g_{m01}g_{m02}}{C_1C_2 + \frac{g_{m01}g_{m02}}{\omega_{p1}\omega_{p2}} - \frac{C_1g_{m03}}{\omega_{p3}}}$$

$$BW_a = \frac{\omega_{oa}}{Q_a} = \frac{C_1g_{m03} - \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) g_{m01}g_{m02}}{C_1C_2 - \frac{C_1g_{m03}}{\omega_{p3}} + \frac{1}{\omega_{p1}\omega_{p2}}}$$

Let us also assume that $\omega_{p1} = \omega_{p2} = \omega_p$, then $\omega_{oa} \cong \omega_o$, thus,

$$BW_a = \frac{\omega_{oa}}{Q_a} = \frac{C_1 g_{mo3} - \frac{2}{\omega_{p1}} g_{m01} g_{m02}}{C_1 C_2 - \frac{C_1 g_{mo3}}{\omega_p} + \frac{1}{\omega_p^2}} \cong \frac{C_1 g_{mo3} - \frac{2}{\omega_p} g_{m01} g_{m02}}{C_1 C_2}$$

$$BW_a \cong \frac{g_{mo3}}{C_2} - \frac{g_{m01} g_{m02}}{C_1 C_2} \frac{2}{\omega_{p1}} = BW - \omega_{oa}^2 \cdot \frac{2}{\omega_{p1}} = BW - \frac{2\omega_{oa}^2}{\omega_{p1}}$$

$$Q_a = \frac{\omega_{oa}}{BW_a} \cong \frac{1 \cdot \omega_{oa}}{\frac{g_{mo3}}{C_2} - \omega_{oa}^2 \frac{2}{\omega_{p1}}}$$

$$Q_a = \frac{\frac{C_2 \omega_{oa}}{g_{m3}}}{1 - \frac{C_2 \omega_{oa}}{g_{m3}} \frac{2\omega_{oa}}{\omega_{p1}}} = \frac{Q}{1 - \frac{Q 2\omega_{oa}}{\omega_{p1}}} = \frac{Q}{1 - \frac{2\omega_{oa}}{\omega_{p1}} Q}$$

Alternatively, Q_a can be expressed in terms of the excess phase $\phi_E = \tan^{-1} \frac{\omega_o}{\omega_p} \cong \frac{\omega_o}{\omega_p}$ then

$$Q_a \cong \frac{Q}{1 - 2\phi_E Q} \cong Q(1 + 2\phi_E Q)$$

$$BW_a = BW - 2\omega_{oa} \phi_E$$

Furthermore, if $A_{vo} = g_m R_o$ is taken into account, then

$$Q_a = \frac{Q}{1 + \frac{2Q}{A_{vo}}}$$

If $A_{vo} = 500$

$$Q_a = \frac{Q}{1 + 4 \times 10^{-3} Q}$$

Note that :


$Q_a \downarrow$ when $A_{vo} \downarrow$
 $BW_a \downarrow$ $Q_a \uparrow$ when $\phi_E \uparrow$

Q	Q_a
1	0.996
5	4.902
10	9.6
50	41.667


$$Q_a \cong \frac{Q}{1 - 2\phi_E Q} \cong Q(1 + 2\phi_E Q)$$

$$BW_a = BW - 2\omega_{oa} \phi_E$$

Two-integrator biquad with gain control

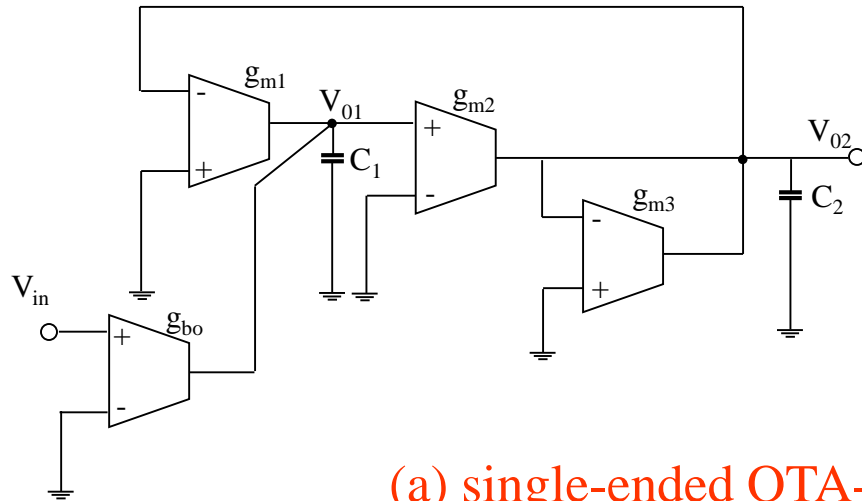

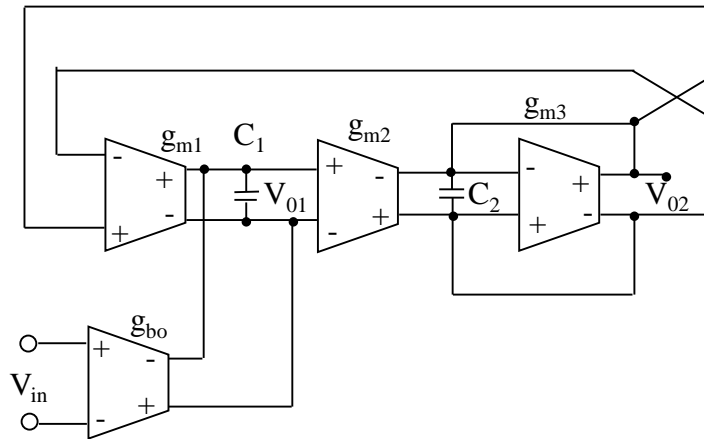(a) single-ended OTA-C Biquad with one input



(b)

Fully differential OTA-C Biquad


Assuming a one pole OTA model

Table OTA finite parameters effects for biquad on the resonant frequency and bandwidth

Poles frequency*	$\sqrt{\frac{g_{m1}g_{m2}}{C_1C_2}} \left[\sqrt{1 + \left(\frac{g_{o1}}{g_{m1}}\right)\left(\frac{g_{m3} + g_{o2} + g_{o3}}{g_{m2}}\right)} - \left(\frac{g_{m1}}{C_1}\right)\left(\frac{g_{m2}}{C_2}\right) \right]$
Bandwidth*	$BW_{ideal}(1 - error) \cong \left(\frac{g_{m3}}{C_1}\right)\left(1 - \frac{g_{o1} + g_{o2} + g_{o3}}{g_{m3}} - 2Q\frac{\omega_0}{\omega_{P1,2}}\right)$

* $\omega_{P1,2}$ and $g_{o1,2}$ are the non-dominant pole and output conductance, respectively.


Lossy Integrator With Positive Feedback

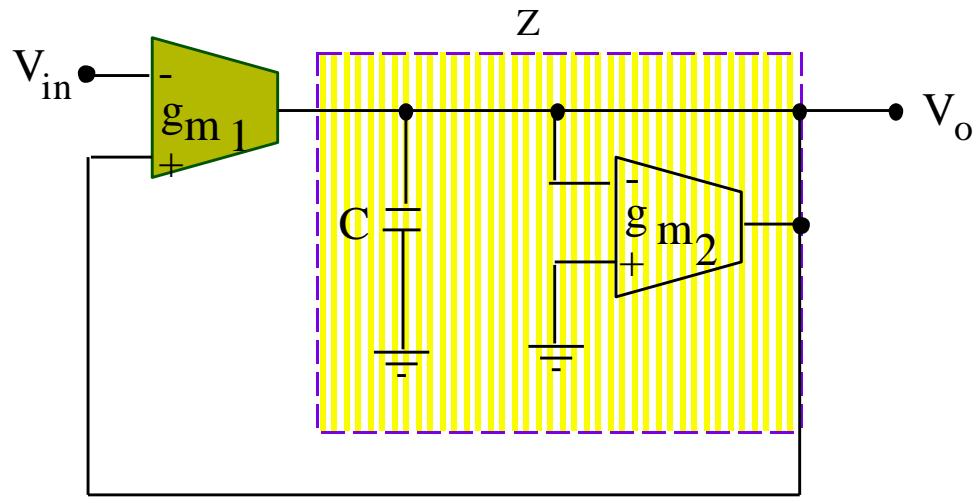

$$\frac{V_o}{V_{in}} = \frac{-g_{m1} Z}{1 - g_{m1} Z} = - \frac{g_{m1}}{sC + (g_{m2} - g_{m1})}$$

Analog and Mixed-Signal Center


Low-Frequency, High-Q OTA-C Biquad

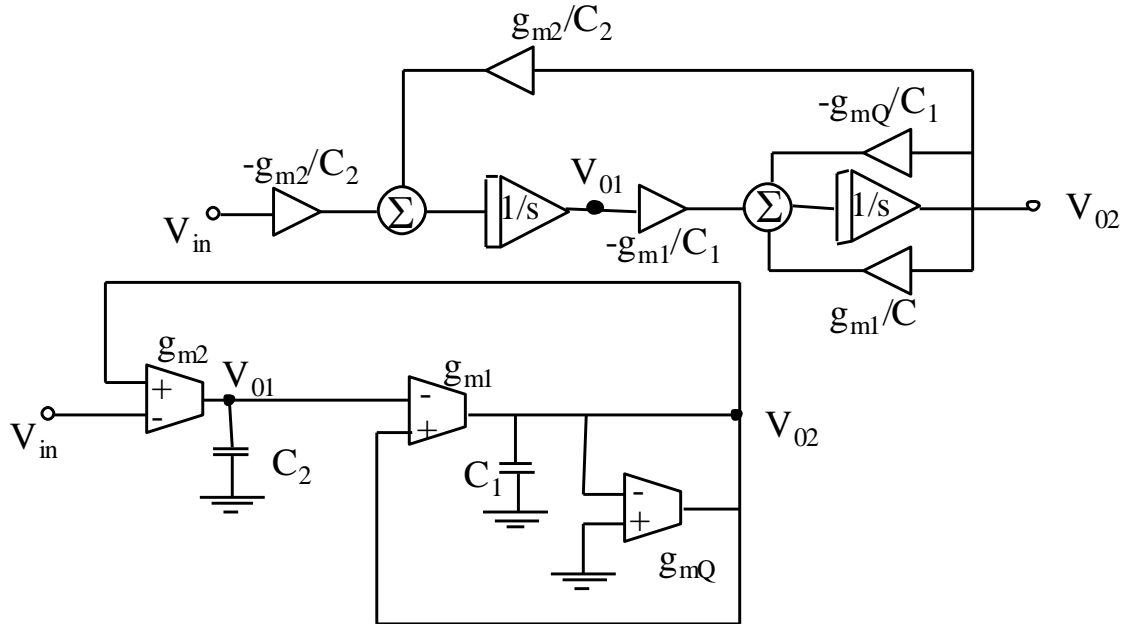

$$\frac{V_{02}}{V_{in}} = \frac{g_{m1}g_{m2}/C_1C_2}{s^2 + s(g_{m1} - g_{m2})/C_1 + g_{m1}g_{m2}/C_1C_2} = \frac{g_{m1}g_{m2}/C_1C_2}{D(s)} \quad \text{LP}$$

$$\frac{V_{01}}{V_{in}} = \frac{g_{m1}/C_2(s + (g_{m2} - g_{mQ})/C_1)}{D(s)} \quad \text{Resonator}$$

OTA Excess Phase Compensation

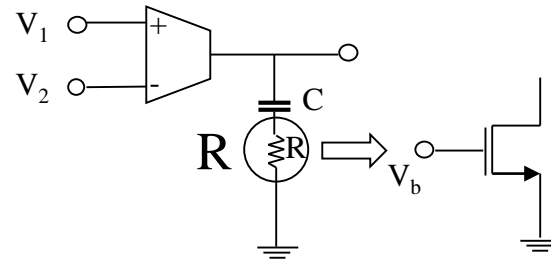

- . Phase compensation techniques: **passive for integrators.**


How to determine the value of RC ?

The R is implemented with a transistor operating in the triode (ohmic) region.

The zero generated by the RC should cancel the dominant pole of $G_m(s)$.

Active Frequency Compensation Transconductor

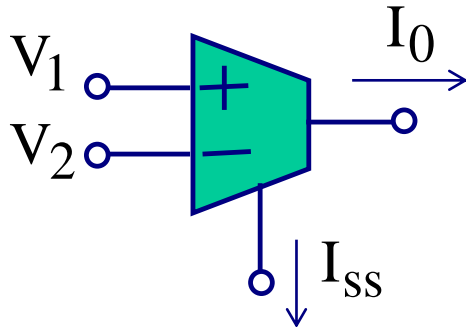
[J. Ramirez-Angulo and E. Sanchez-Sinencio, "Active Compensation of Operational Transconductance Amplifier Filters Using Partial Positive Feedback," IEEE Journal of Solid-State Circuits, vol. 25, No. 4, pp. 1024-1028, August 1990]



$$I_0 = g_m(V_1 - V_2)$$

$$g_m(s) = g_{m0} \left(1 - \frac{s}{\omega} \right)$$

ω depends on I_{SS}

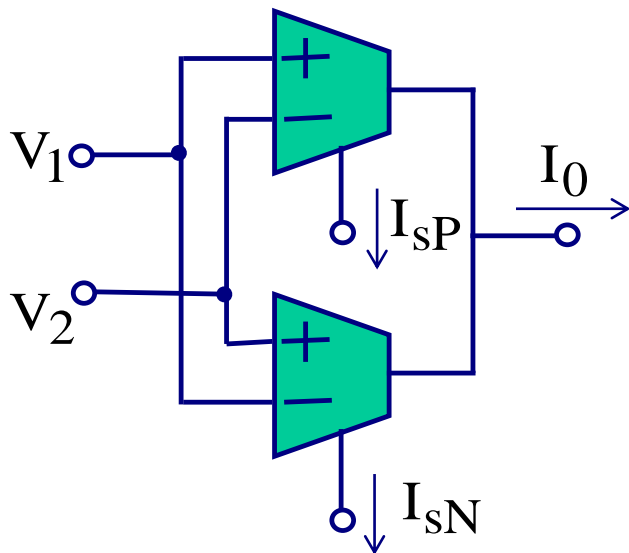

$$I_0 = (g_{mp}(s) - g_{mN}(s))\Delta V = g_{meff}(s)\Delta V$$

$$g_{meff}(s) = g_{meff0} \left[1 - \frac{s}{\omega_{eff}} \right]$$

$$g_{meff0} = g_{mP0} - g_{mN0} \quad , \quad \omega_{eff} = \frac{g_{meff0}}{\frac{g_{mP0}}{\omega_P} - \frac{g_{mN0}}{\omega_N}}$$



It is possible to make

$$\omega_{eff} \gg \omega_P, \omega_N$$

Phase compensation techniques

In a Biquad:
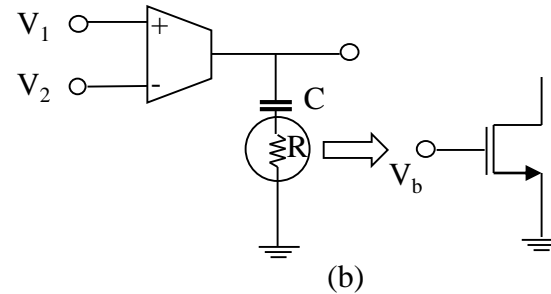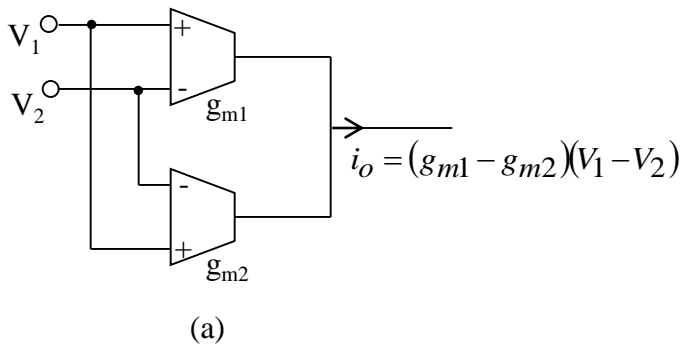
$$Q_a = \frac{Q}{1 + 2\left(\frac{1}{A_{vo}} - \phi_E\right)Q}$$




(a) active; and (b) passive for integrators.


Recall that

$$g_m = \frac{g_{mo}}{1 + s/\omega_p} \cong g_{mo} \left(1 - s/\omega_p\right) \cong g_{mo} e^{-s/\omega_p}$$


Behavior of symmetric circuits

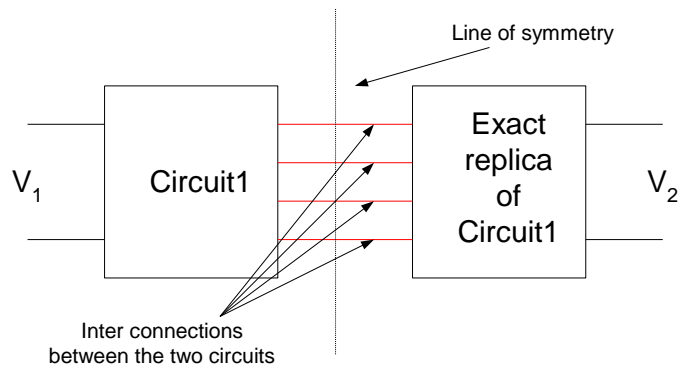

An example of fully symmetric circuit

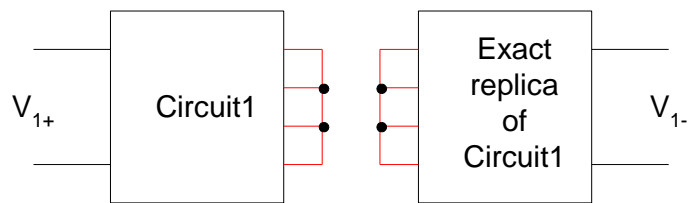


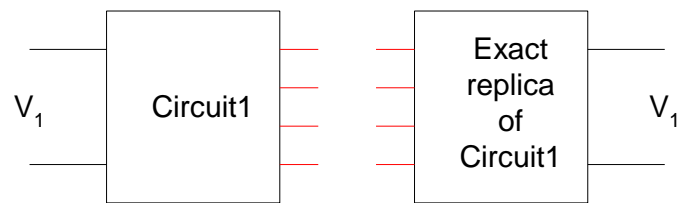Equivalent circuit for fully differential input




Equivalent circuit for common mode input



Derivation of CMFF OTA

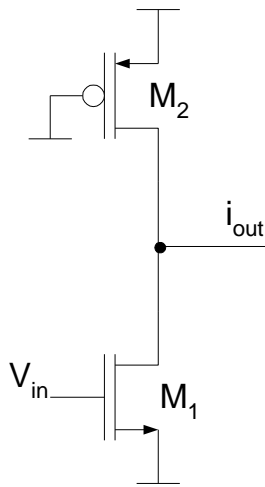


Single ended OTA circuit

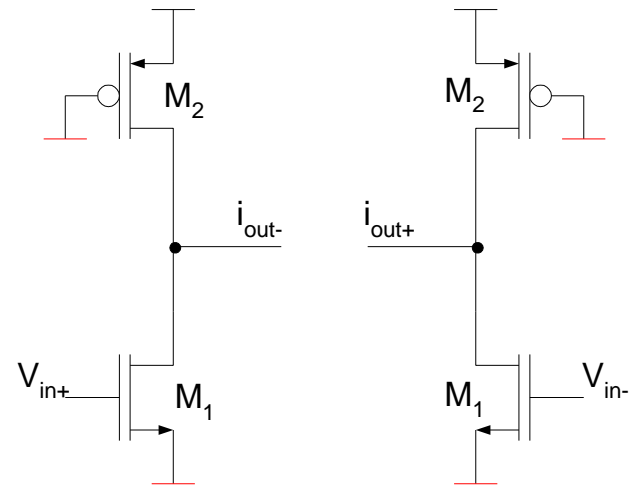


Circuit of OTA for differential input

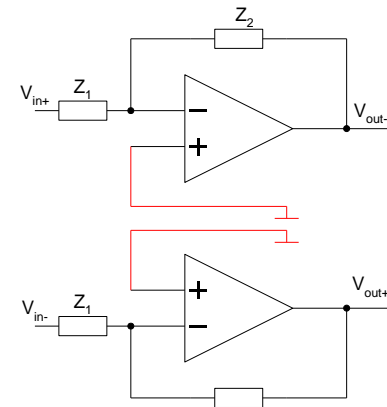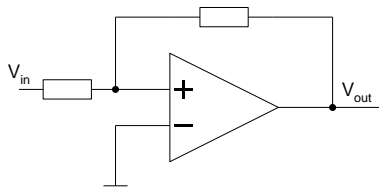


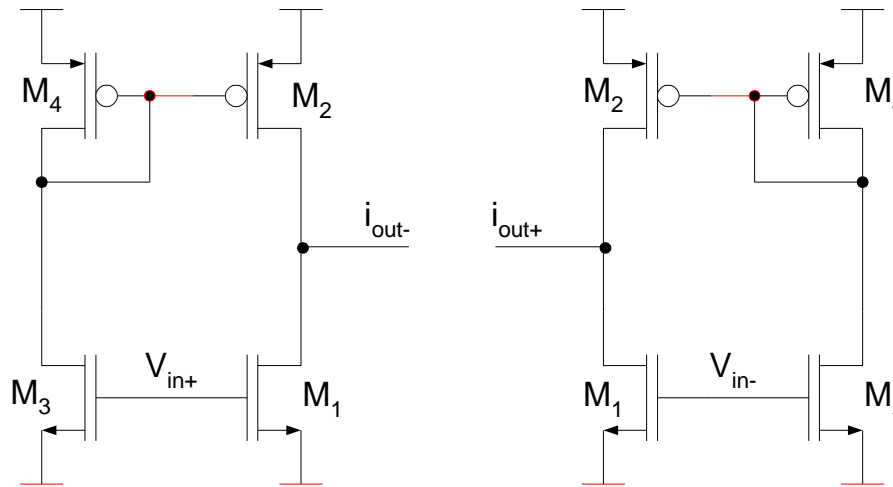


Circuit of OTA for common mode signals

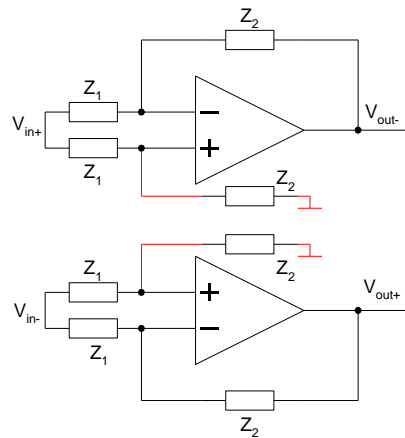


Note.- Independent trajectories, poor CMRR

Fully-balanced, fully-symmetric CMFF OTA

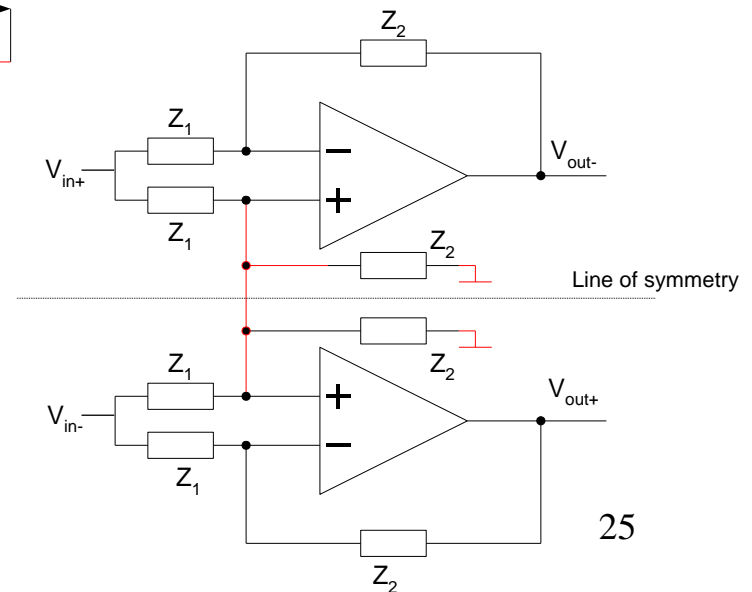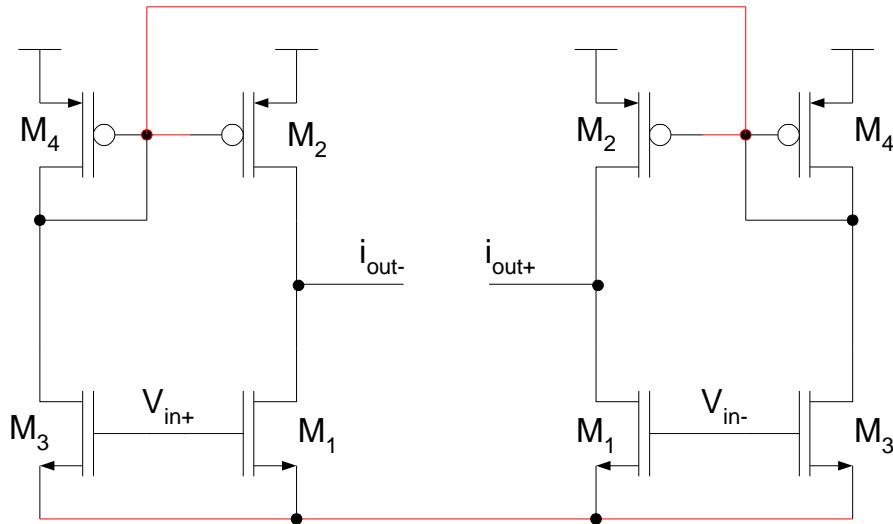


OTA with improved flexibility

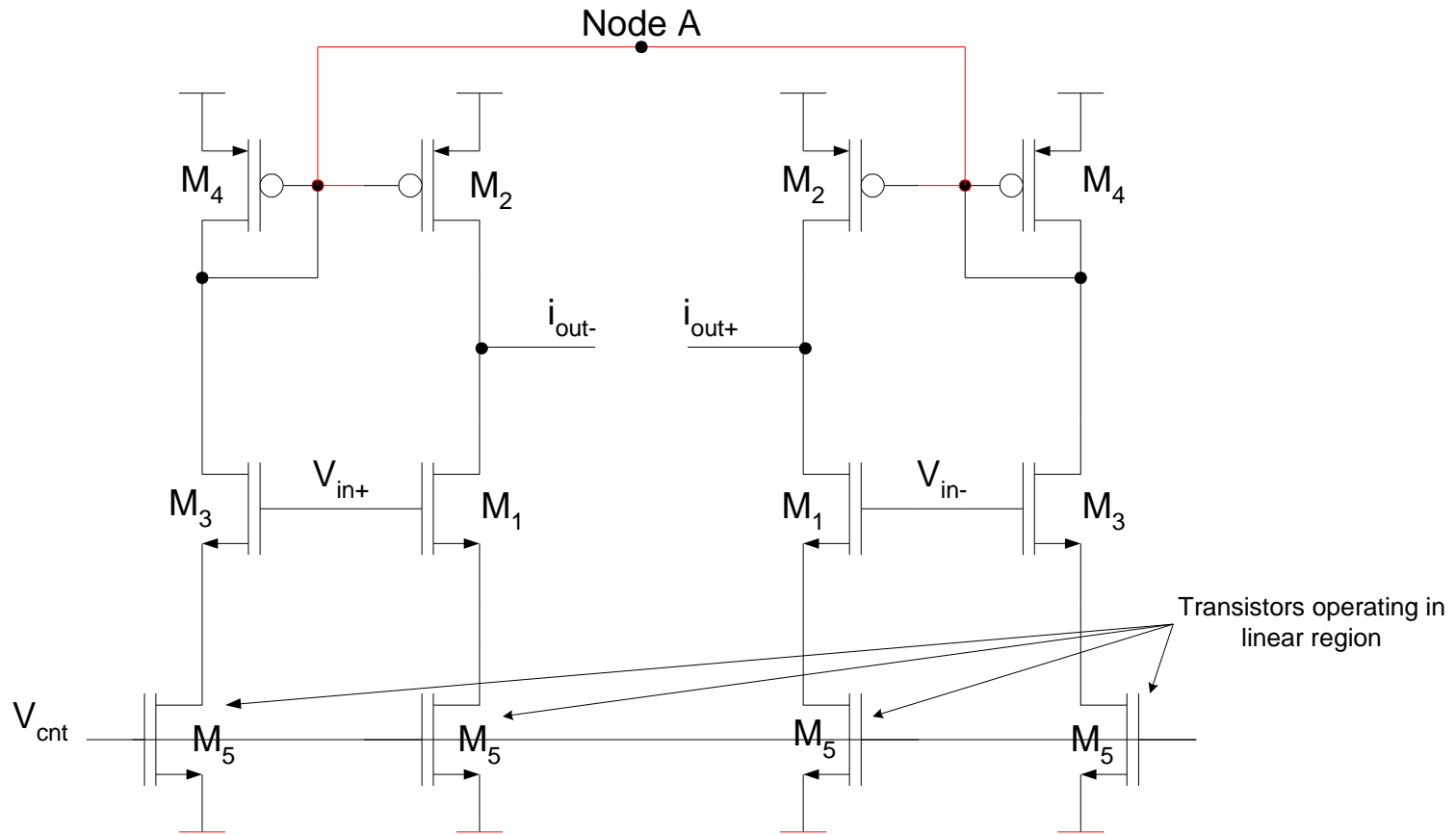


Fully-balanced, fully-symmetric, pseudo differential CMFF OTA

Two integrator loop

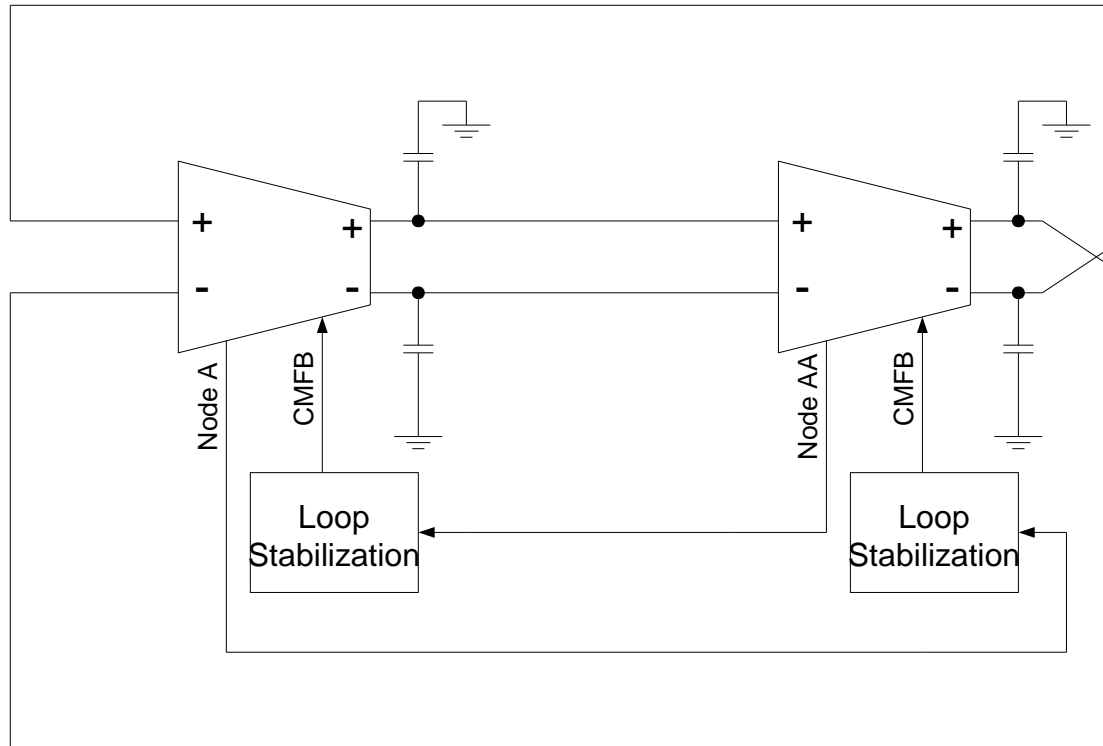


Two integrator loop using CMFF OTA

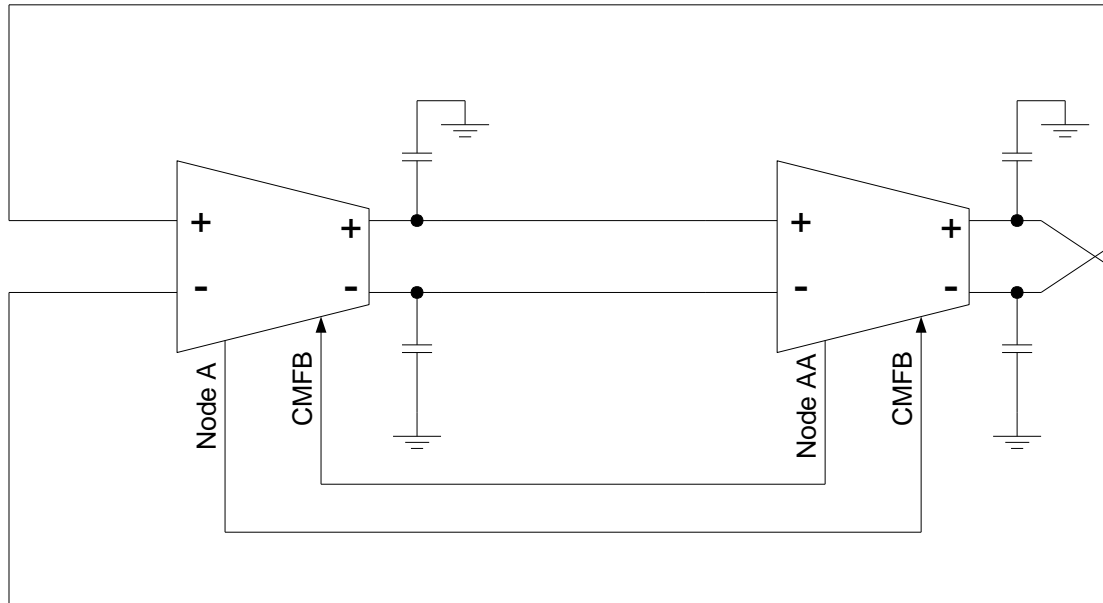

Two integrator loop using CMFF+CMFB OTA

(CMFF + CMFB) OTA

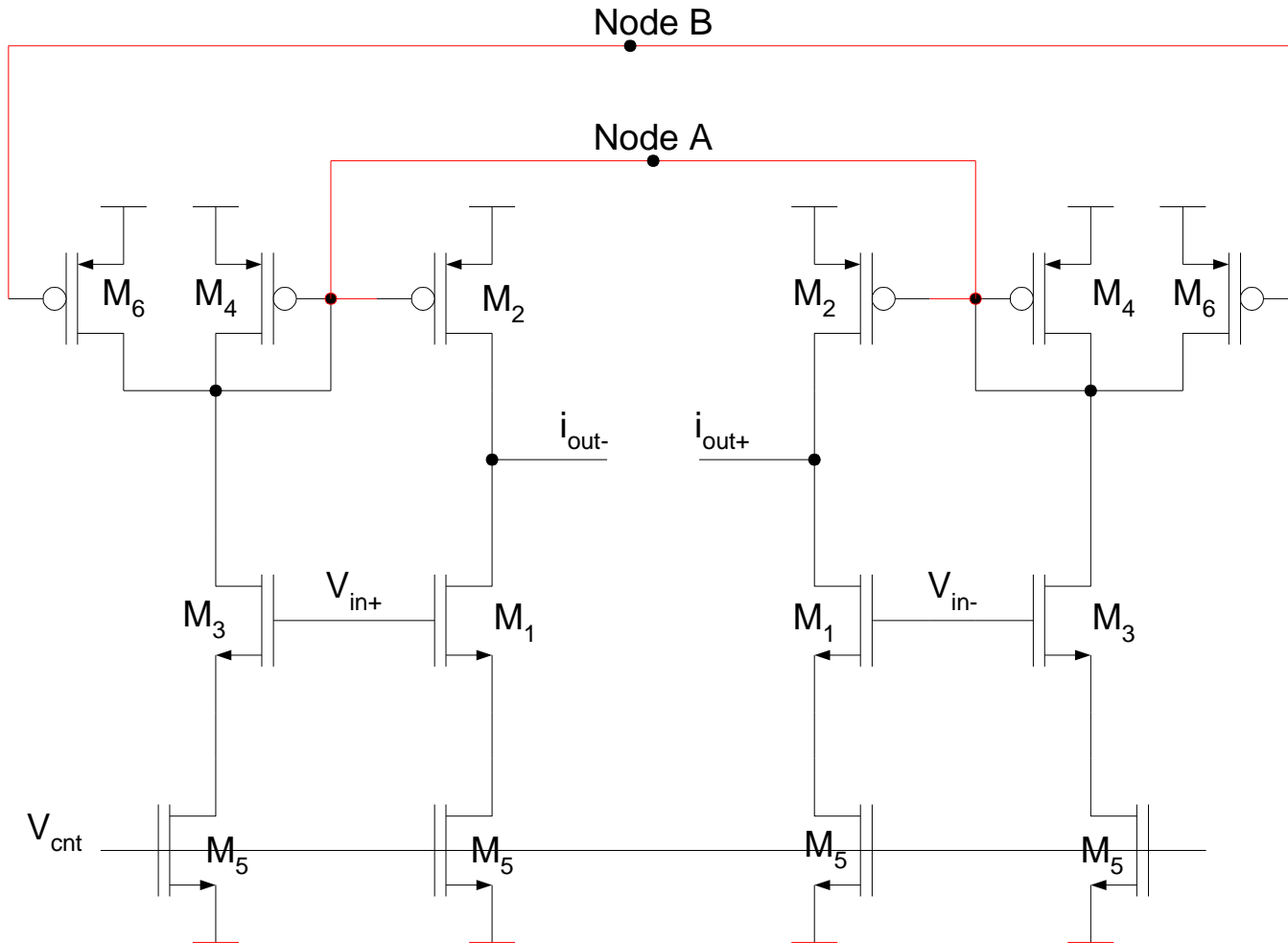

Fully-balanced, fully-symmetric, pseudo differential (CMFF+CMFB) OTA

Characteristics of the OTA

- Let the total capacitance at 'node A' be C_{int}
- Let the capacitance used in two integrator loop be

C_{ext}

- Effective transconductance =
$$g_{m1\text{eff}} = \frac{g_{m1}}{1 + \frac{g_{m1}}{g_{ds5}}}$$

- CMFB loop gain =
$$\frac{g_{m1\text{eff}} \cdot g_{m6} \cdot g_{m2}}{g_{m4} \cdot g_{m4} \cdot g_{ds2}} \cdot \frac{1}{\left(1 + \frac{sC_{int}}{g_{m4}}\right)^2 \left(1 + \frac{sC_{ext}}{g_{ds2}}\right)}$$

- Gain (I_o/V_i) = $g_{ds5} \left\{ 2 - \left(1 + \frac{4\beta_1}{g_{ds5}} (V_G - V_T) \right)^{-\frac{1}{2}} \right\}$

- Gain(I_o/V_i^3) = $\frac{12\beta_1^2}{g_{ds5}} \left[1 + \frac{4\beta_1}{g_{ds5}} (V_G - V_T) \right]^{-\frac{5}{2}} = \frac{12\beta_1^2 g_{ds5}^{3/2}}{[g_{ds5} + 4\beta_1 (V_G - V_T)]^{5/2}}$

- To improve linearity, use larger resistor for source degeneration.

- Differential gain = $\frac{g_{m1,eff}}{g_{ds2}}$

- Common mode gain = $\left[1 - \frac{1}{1 + \frac{sC_{int}}{g_{m4}}} \right] \times \frac{g_{m1,eff}}{g_{ds2}} + \frac{g_{m1,eff}}{g_{m4}}$

- $CMRR_{(DC)} = \frac{g_{m4}}{g_{ds2}}$

- Gain from +ve supply=1
- Gain from -ve supply= $\left[1 - \frac{1}{1 + \frac{sC_{int}}{g_{m4}}} \right] \times \frac{g_{m1,eff}}{g_{ds2}} + \frac{g_{m1,eff}}{g_{m4}}$

- Gain from VSS is less than gain from VDD. So, output should be measured wrt VDD
- PSRR is same as CMRR


Output noise current=

$$\begin{aligned}
 & i_{n1}^2 \times \left(\frac{1}{1 + \frac{g_{m1}}{g_{ds5}}} \right)^2 + 4KTg_{ds5} + 4KTg_{ds5} \times \left(\frac{g_{m2}}{g_{m4} \left(1 + \frac{sC_{\text{int}}}{g_{m4}} \right)} \right)^2 \\
 & + i_{n2}^2 + i_{n4}^2 \times \left(\frac{g_{m2}}{g_{m4}} \right)^2 + i_{n6}^2 \times \left(\frac{g_{m2}}{g_{m4} \left(1 + \frac{sC_{\text{int}}}{g_{m4}} \right)} \right)^2
 \end{aligned}$$


Simplified noise expression

$$KT \left\{ \frac{8g_{m1}}{3 \left(1 + \frac{g_{m1}}{g_{ds5}} \right)^2} + 4g_{ds5} + \frac{4g_{ds5}}{\left(1 + \frac{sC_{int}}{g_{m4}} \right)^2} + \frac{8g_{m2}}{3} + \frac{8g_{m2}}{3 \left(1 + \frac{sC_{int}}{g_{m4}} \right)^2} \right\}$$

Two integrator loop

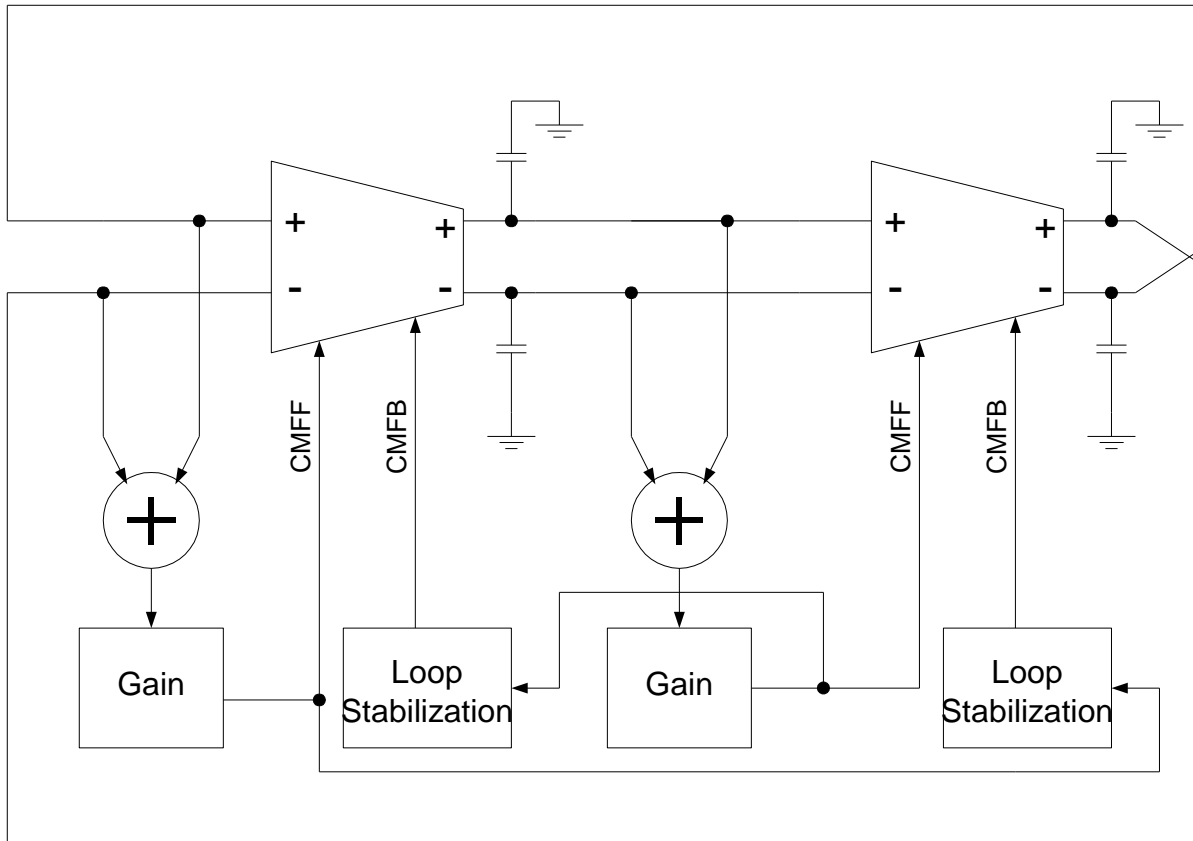

Band pass filter

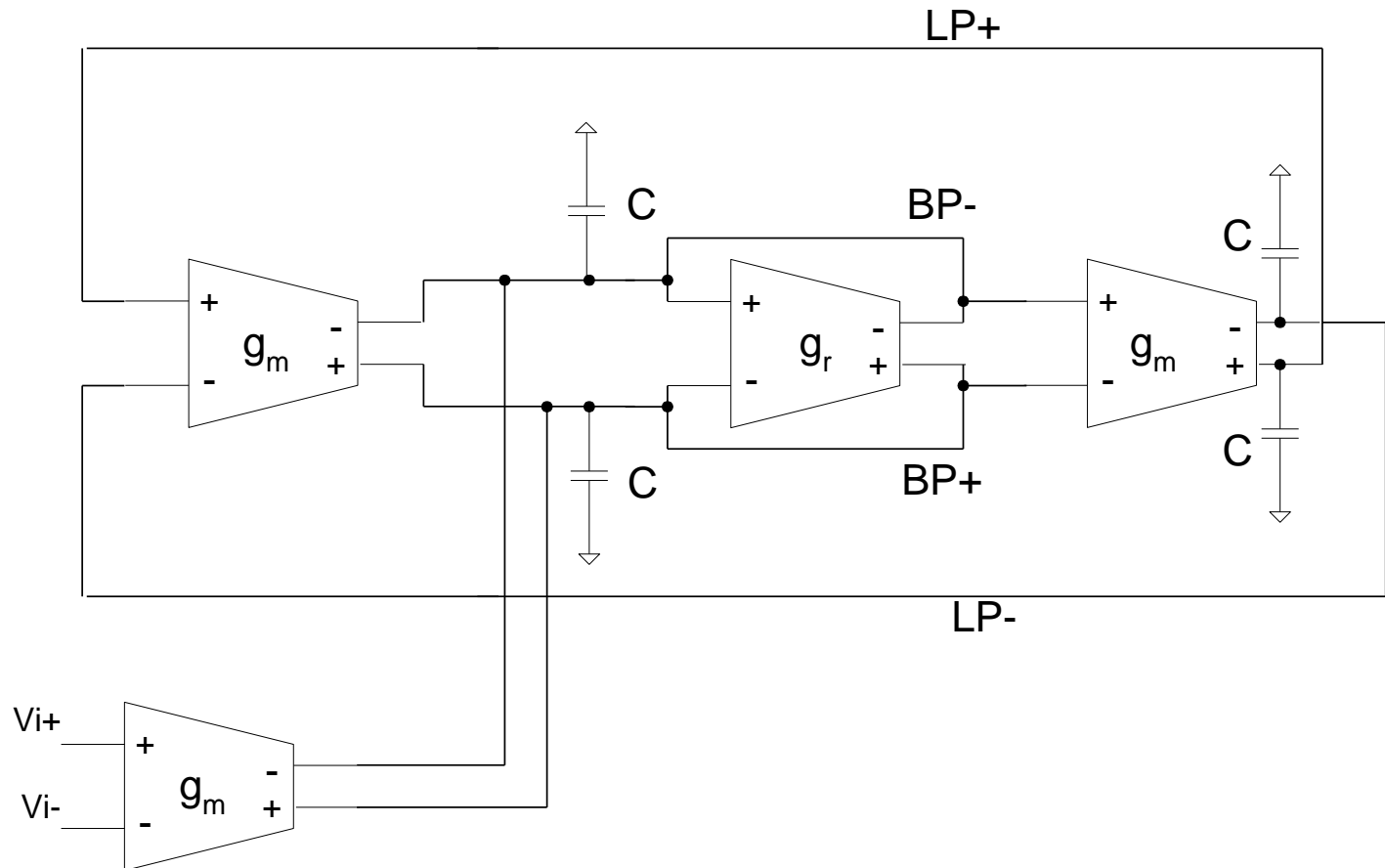

Design of a new high frequency OTA and a Filter Tuning Scheme



Praveen Kallam

Advisor: Dr. E. Sanchez Sinencio

How to build a filter

- OpAmps - Low frequency, high linearity
- OTAs - Medium high frequencies, medium linearity
- Passive components - High frequency
- Transmission lines - Extremely high frequency

NMOS VS PMOS

	NMOS	PMOS
Speed	Faster	Slower
Device noise	Low thermal noise	Low flicker noise
Linearity	Bulk effect degrades linearity	No bulk effect
Substrate noise	Higher due to common substrate	Can be better shielded

Advantages of differential Circuits

- Double the signal swings
- Better power supply and substrate noise rejection
- Higher output impedance with conductance cancellation schemes
- Better linearity due to cancellation of even harmonics
- Partial cancellation of systematic errors using layout techniques
- Availability of already inverted signals


Disadvantages of differential Circuits

- Duplication of circuit requires double the area and power
- Additional circuitry to tackle common mode issues

Common mode issues


- Output DC common mode voltage should be stabilized (otherwise, the voltage may hit the rails)
- Common mode gain should be small (otherwise, positive feedback in a two integrator loop becomes stronger)

Common Mode Feed Forward

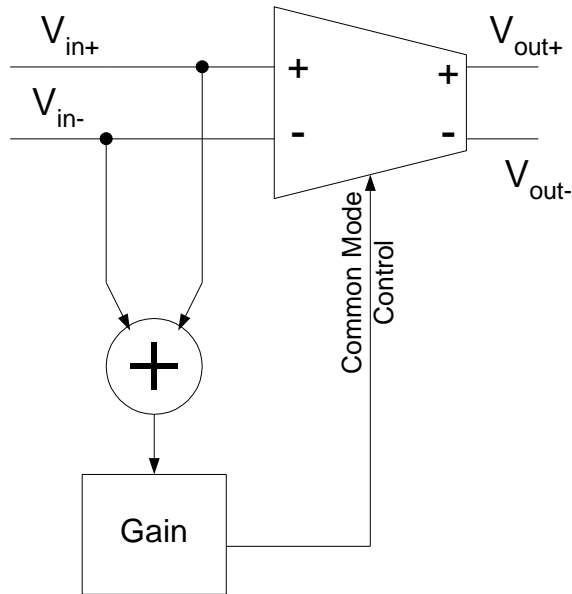


- Can decrease common mode gain even at higher frequencies
- Does not have stability problems
- Cannot stabilize the output DC voltage

Common Mode Feed Back

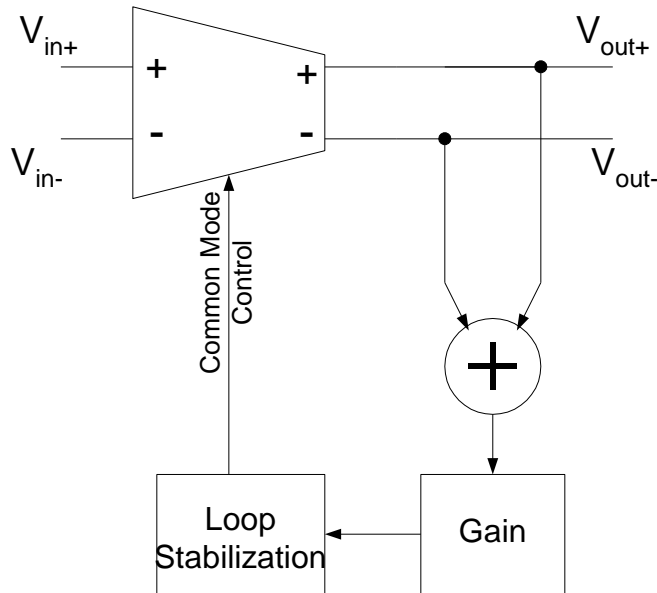


- Stabilizes output DC voltage
- Feedback stability issues make the circuit slow and bulky


CMFF + CMFB

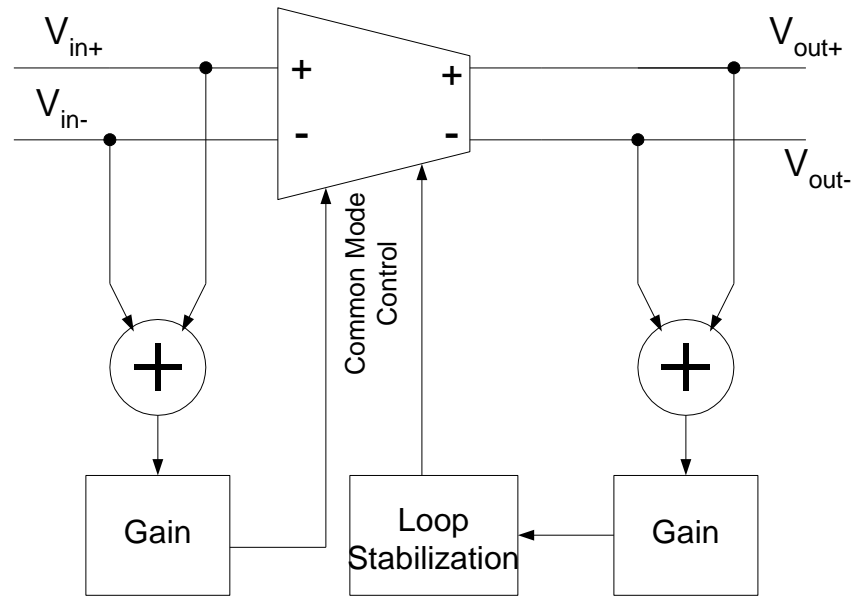

Two integrator loop

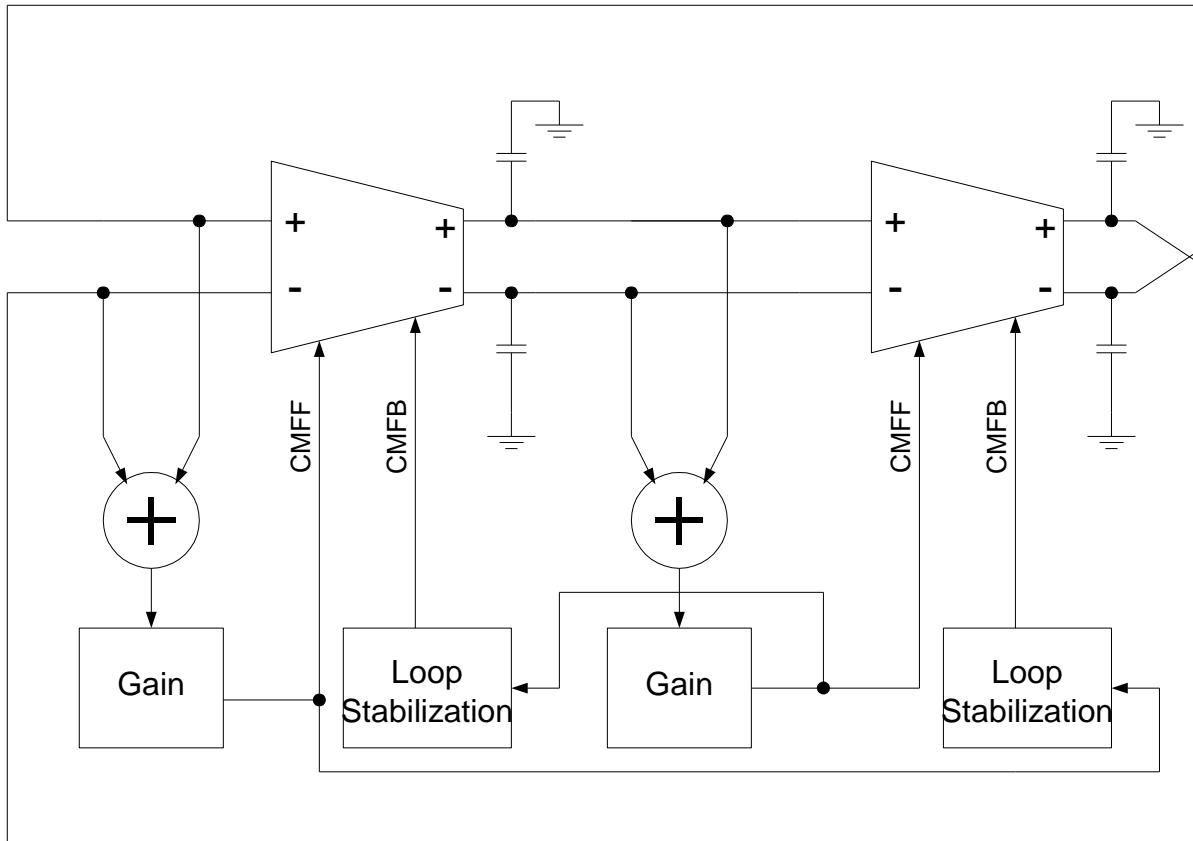

Band pass filter

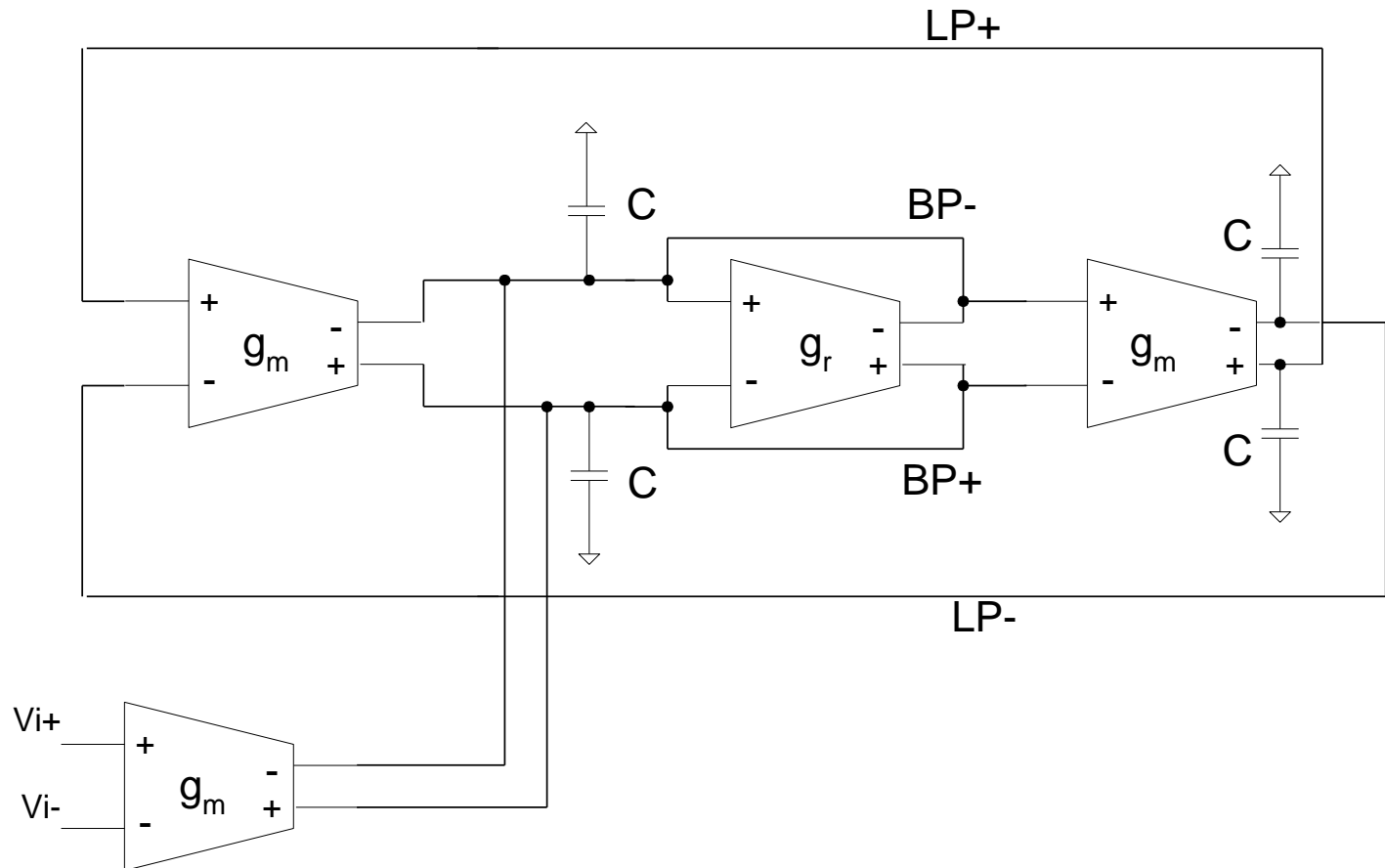

Need for tuning

- Process parameters can change by 10%
- Parameters also change with temperature and time(aging)
- Another solution for low-frequency is using Switch Capacitor filters

Methods of tuning

- Master-Slave
- Pre-tuning
- Burst tuning
- Switching between two filters

Frequency Tuning

PLL

- Most widely used scheme
- Accurate (less than 1% error is reported)
- **Square wave input reference**
- Only XOR and LPF are the additional components

- Usually used only for filters with $Q > 10$
- Large area overhead

Q tuning

Modified LMS

- Accurate
- **Square wave input**
- Independent of frequency tuning

- Not very robust
- Large area overhead



The most accurate scheme so far

- Stevenson, J.M.; Sanchez-Sinencio, E “An accurate quality factor tuning scheme for IF and high-Q continuous-time filters”. Solid-State Circuits, IEEE Journal of Volume: 33 12 , Dec. 1998 , Page(s): 1970 -1978
- Combines Master-Slave, PLL and modified LMS
- Less than 1% error in both f-tuning and Q-tuning

LMS Algorithm Derivation.- The mean square error (MSE) is defined as $E(t)=0.5[e(t)]^2 = 0.5[d(t)-y(t)]^2$ where $d(t)$ is the desired output signal, and $y(t)$ is the actual output signal. The steepest descent algorithm is defined as:

$$\frac{dW}{dt} = -\mu \frac{\partial E}{\partial W}$$

$$\frac{dW}{dt} = -\mu \frac{\partial E}{\partial y} \frac{\partial y}{\partial W}$$

$$\frac{dW}{dt} = -\mu \frac{\partial [0.5\{d(t) - y(t)\}^2]}{\partial y} \frac{\partial y}{\partial W}$$

$$\frac{dW}{dt} = \mu [d(t) - y(t)] \frac{\partial y(t)}{\partial W}$$

$$\dot{W} = \mu [d(t) - y(t)] G(t) = \mu e(t) G(t)$$

Linear System case.

$$y(t) = \sum_{i=0}^n w_i x_i,$$

where:

x_i is the input signal.

Therefore:


$$\frac{dW}{dt} = \mu[d(t) - y(t)] \frac{\partial \sum_{i=0}^n w_i x_i}{\partial W} = \mu[d(t) - y(t)] x_i$$


$$\dot{W} = \mu e(t) x_{xi}$$

Adaptive LMS Algorithm

$$\dot{w}_i = \mu [d(t) - y(t)] g_i(t)$$

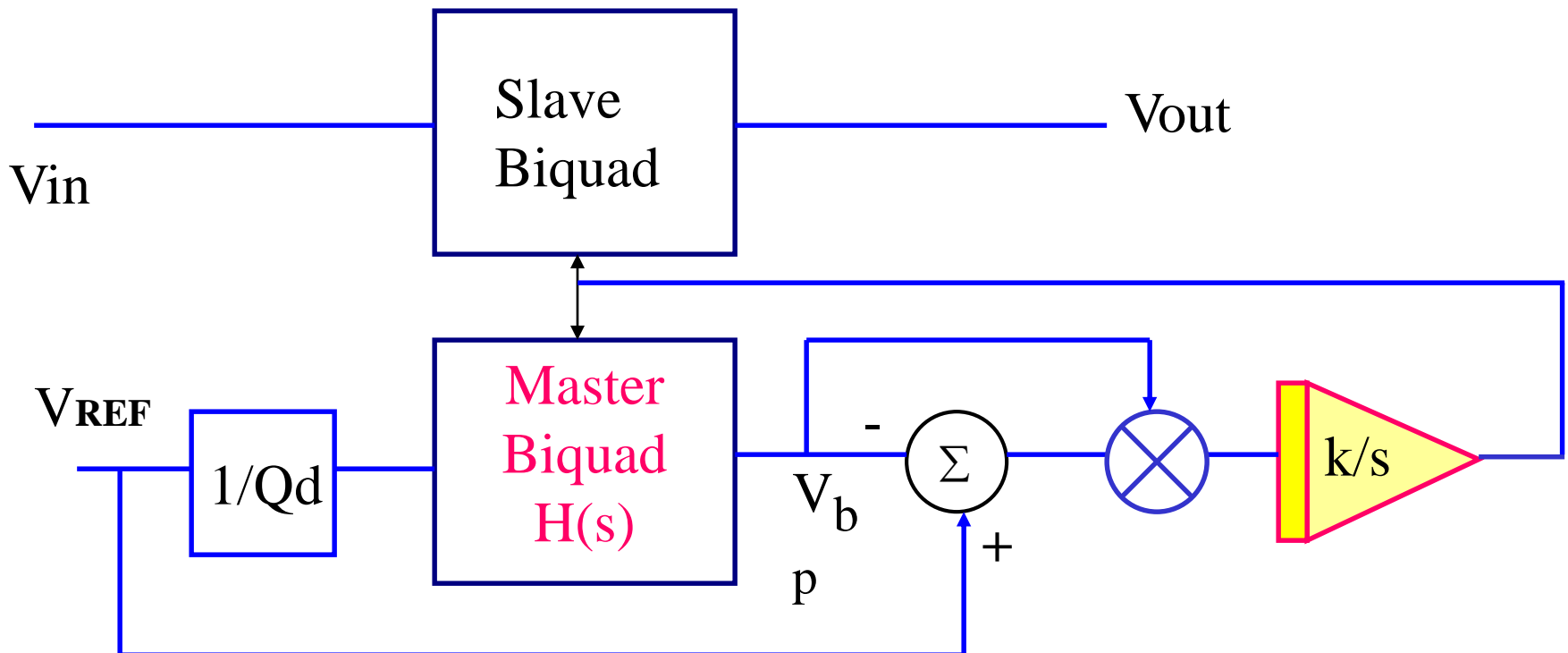
Where μ is the tuning signal, $d(t)$ is the desired response, $y(t)$ is the actual response, and $g_i(t)$ is the gradient signal (that is the direction of tuning).



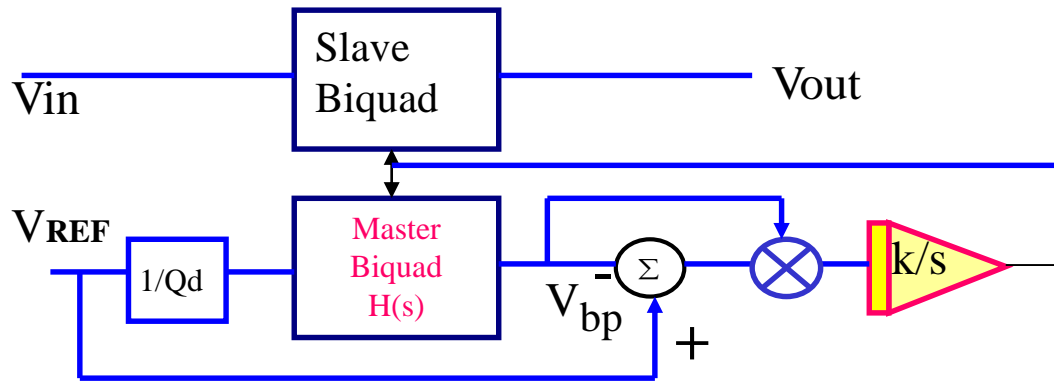

Block Diagram Solution




The tuning scheme implemented before

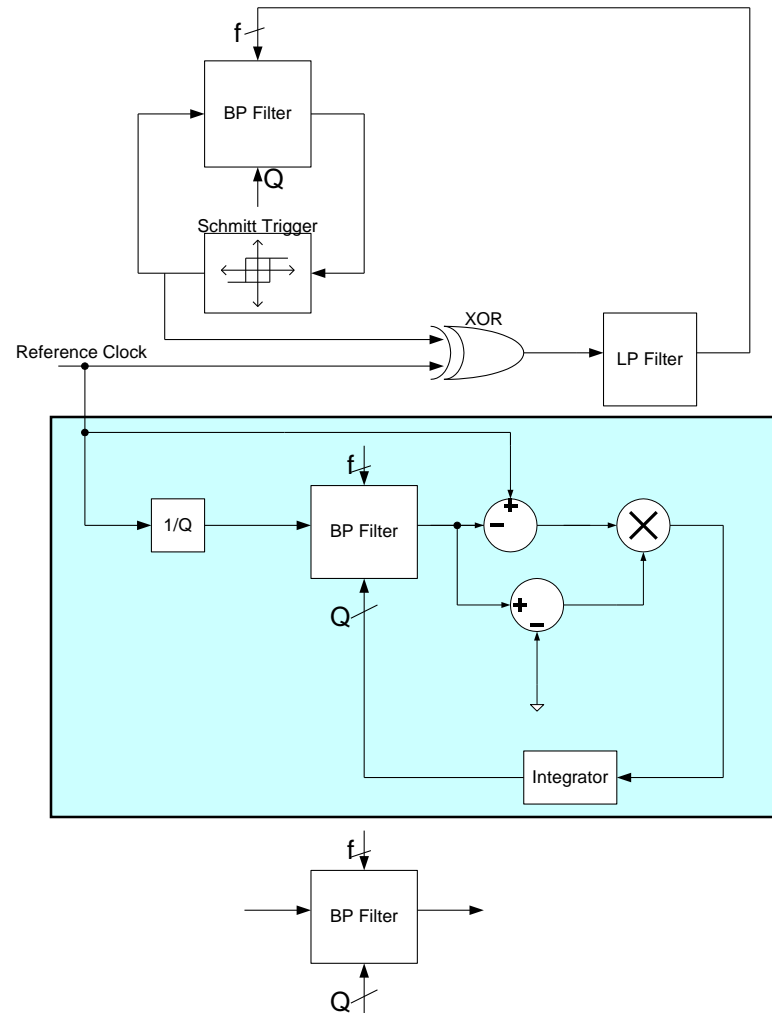


Problems in the previous scheme

- Large area overhead (may run into matching problems)
- Power hungry
- Not very robust (very low offsets required.)
- Loses accuracy at low $Q_s (< 10)$ and very high Q_s (~ 100)
- Applies only to Band-Pass filters

PLL

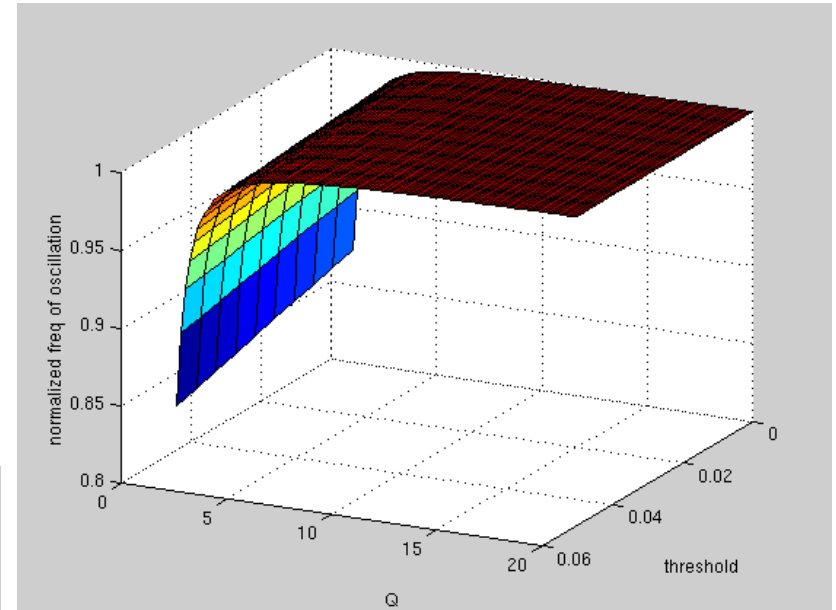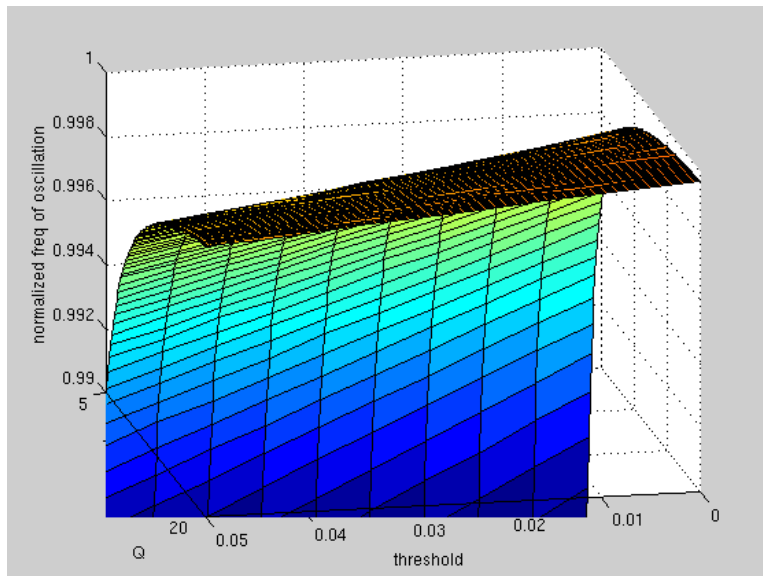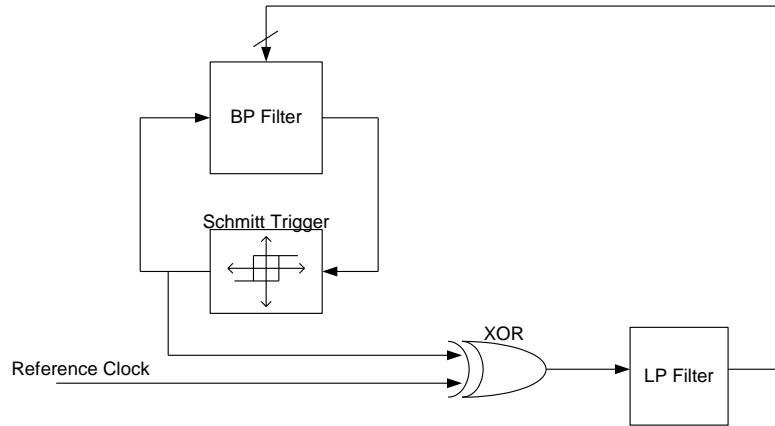

Proposed Q-tuning scheme

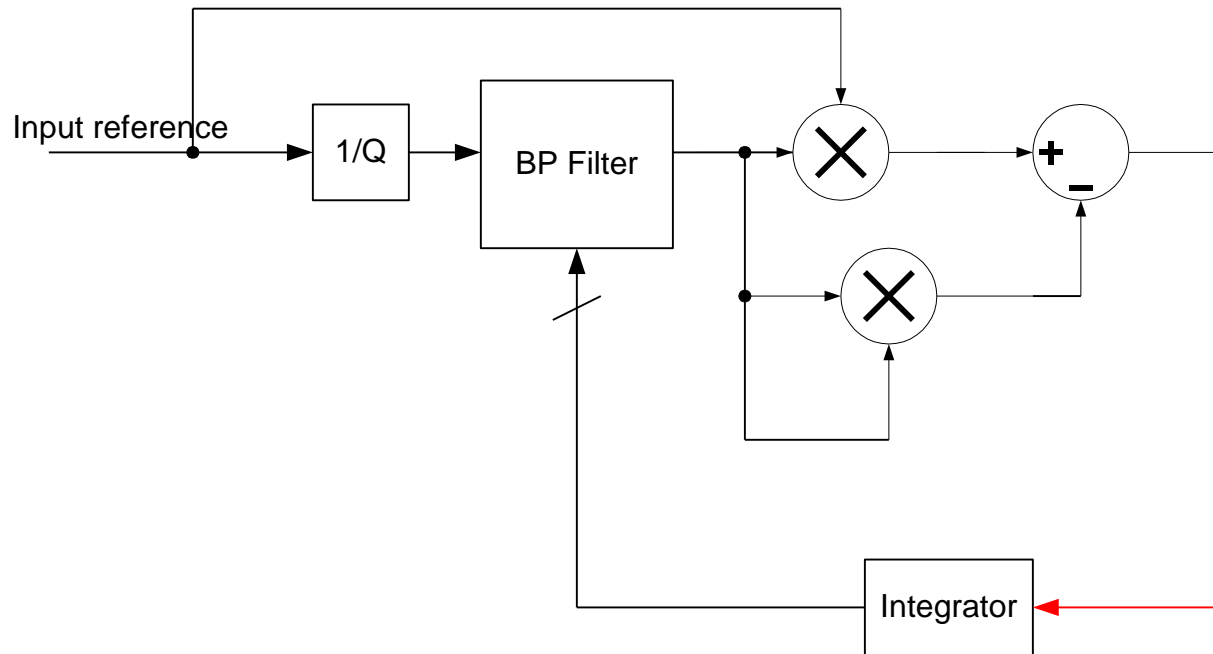

New implementation of modified-LMS Q-tuning scheme

Tuning is independent of the shape of reference waveform

$$V_o(t) = A \times \frac{Q_a}{Q_D} \times G \times \sin\{wt + \theta\} \quad \Rightarrow \quad V_o(t) = A \times \frac{Q_a}{Q_D} \times \cos(\theta) \times \sin(wt + \theta)$$

$$G = \left| \frac{jw / w_a Q_a}{1 + jw / w_a Q_a - w^2 / w_a^2} \right| \quad \theta = \text{Arg} \left(\frac{jw / w_a Q_a}{1 + jw / w_a Q_a - w^2 / w_a^2} \right)$$

$$V_i(t) = \sum_i A_i \sin(w_i t) \quad \Rightarrow \quad V_o(t) = \sum_i A_i \frac{Q_a}{Q_D} \cos(\theta_i) \sin(w_i t + \theta_i)$$


When this input and output is processed by the tuning scheme,

$$\left\{ \frac{Q_a}{Q_D} \sum_i A_i^2 \cos^2(\theta) - \left(\frac{Q_a}{Q_D} \right)^2 \sum_i A_i^2 \cos^2(\theta) \right\} = 0$$

Improved Offset performance


$$\text{Previous offset} = G_{mul} G_{sum}^2 (O_{in} - O_{BP}) O_{BP} + G_{mul} G_{sum} O_{in} O_{sum} + G_{mul} O_{sum}^2 + O_{mul}$$
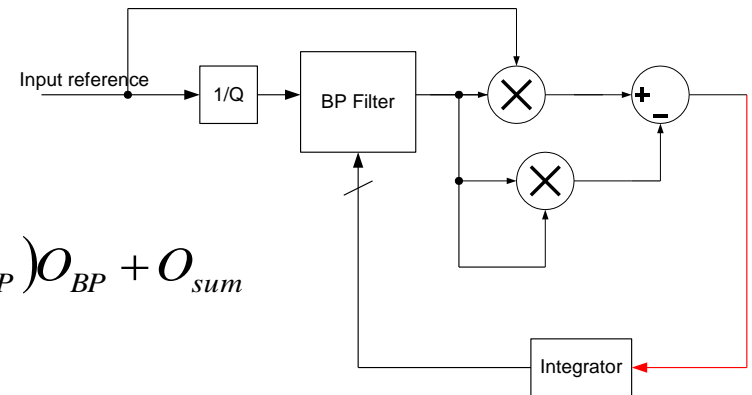
$$\text{Present Offset} = G_{mul} G_{sum} (O_{in} - O_{BP}) O_{BP} + O_{sum}$$



- Reduced offset \Rightarrow improved accuracy

The new tuning scheme

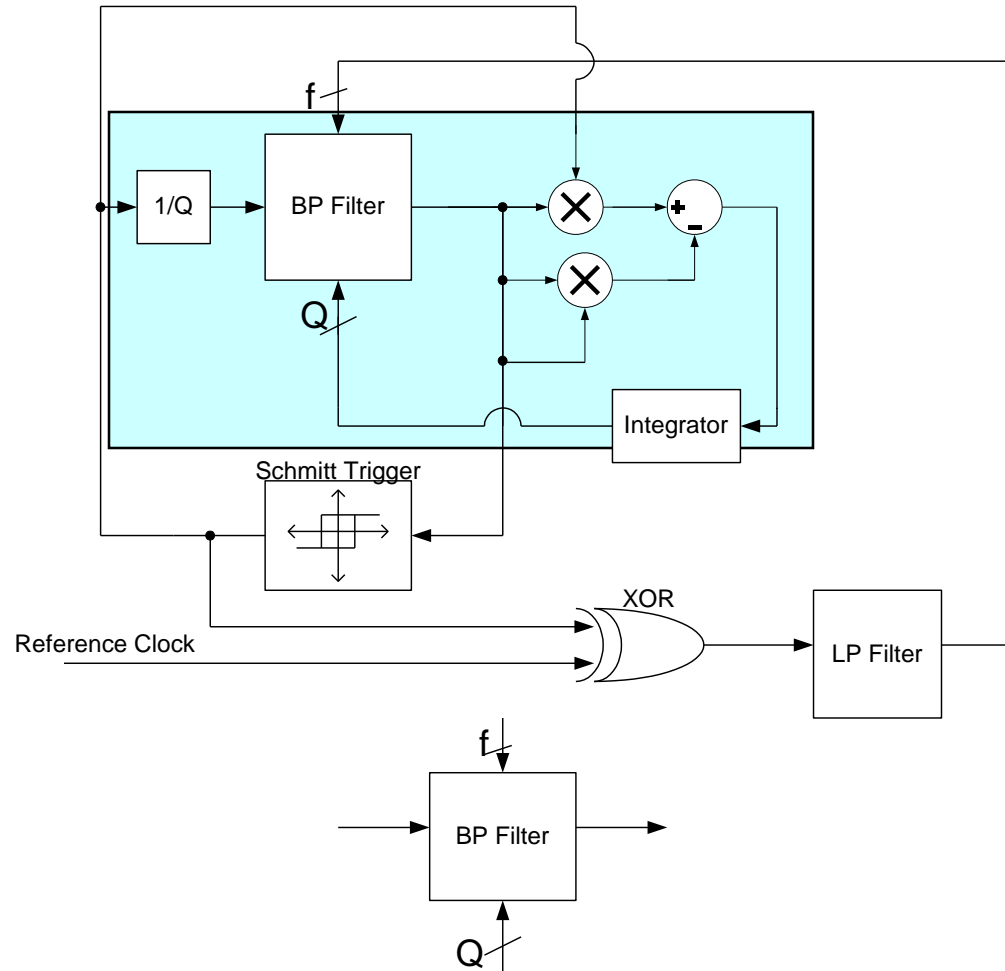

Improvements over the previous tuning scheme

- Area overhead decreased

(Previous scheme => 2 extra filters

New scheme => 1 extra filter)


- Eases the matching restrictions

(Previous tuning scheme => match 3 filters

New tuning scheme => match 2 filters)

- Improves accuracy of tuning

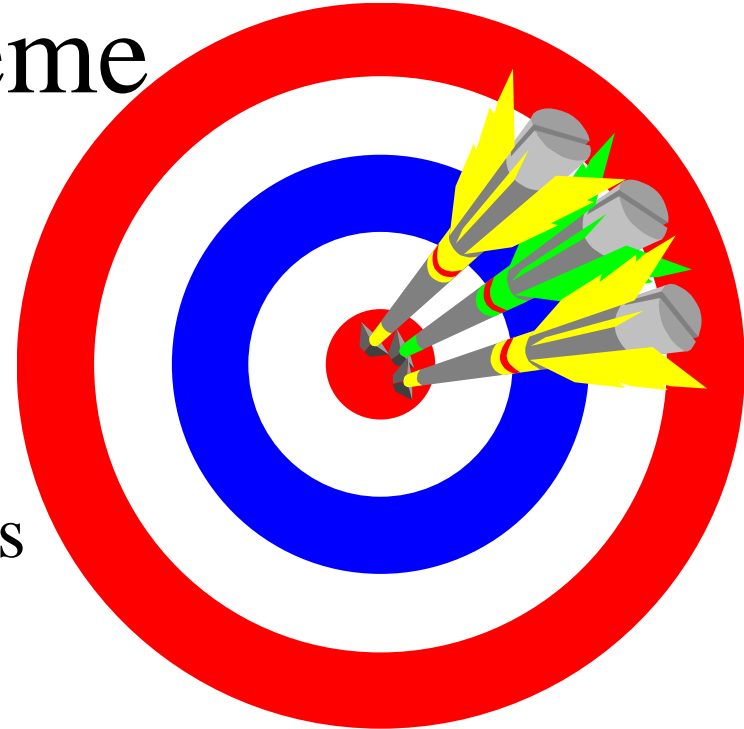(New tuning scheme is more tolerant to offsets than the previous one)




Circuits to be designed


- Comparator
 - Attenuator
 - Multiplier
 - LPF \longrightarrow outside the IC using Opamp
 - Differential difference adder
 - Integrator \longrightarrow outside the IC using Opamp
- (Both macro model & transistor level are used in simulations for the OpAmp)

Comparator

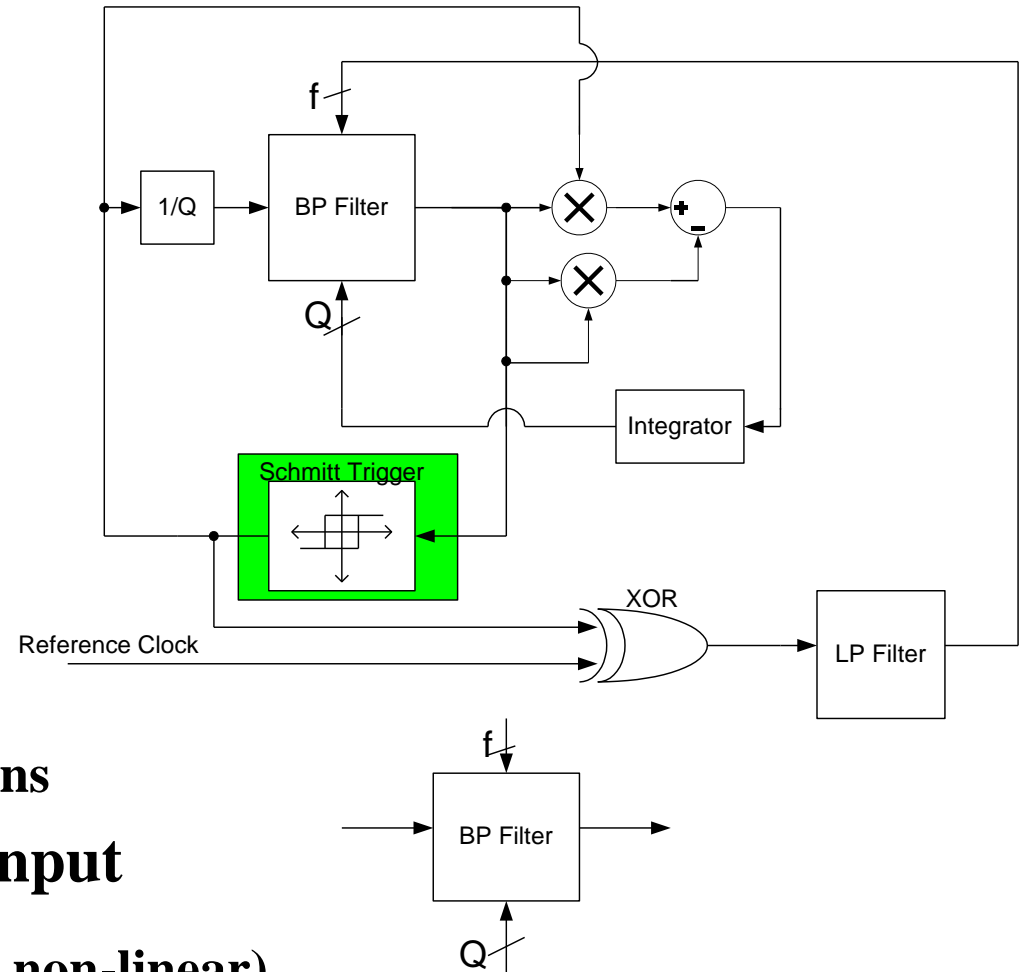- **Non-linear amplifier**
 - Gain should be as close to unity to improve THD
 - If less than unity, no oscillations
- **Rate of change of gain wrt input should be high (should be very non-linear)**
 - cannot use complex circuits
 - **DIODE**




Circuit of differential comparator

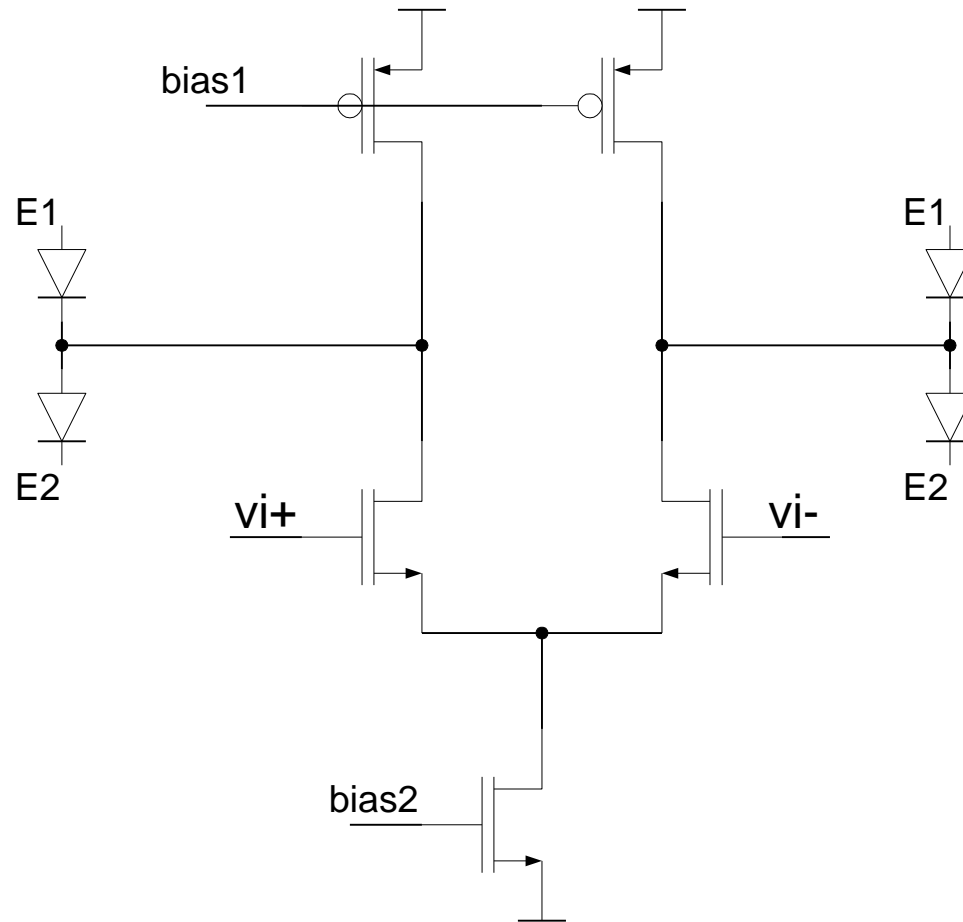

Comparator characteristics


proj_2 fQ_tun1 schematic : Dec 4 23:51:02 2000

Transient Response

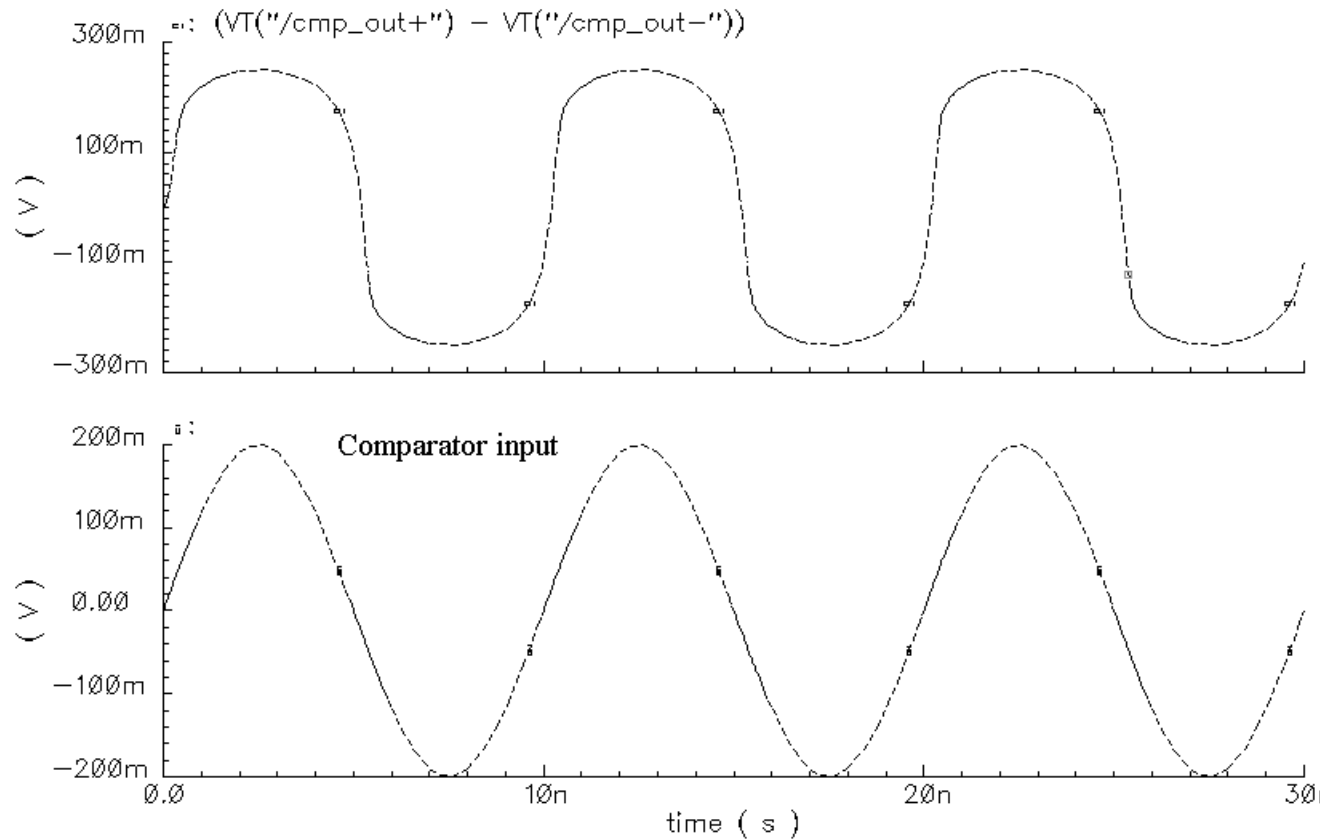

Attenuator

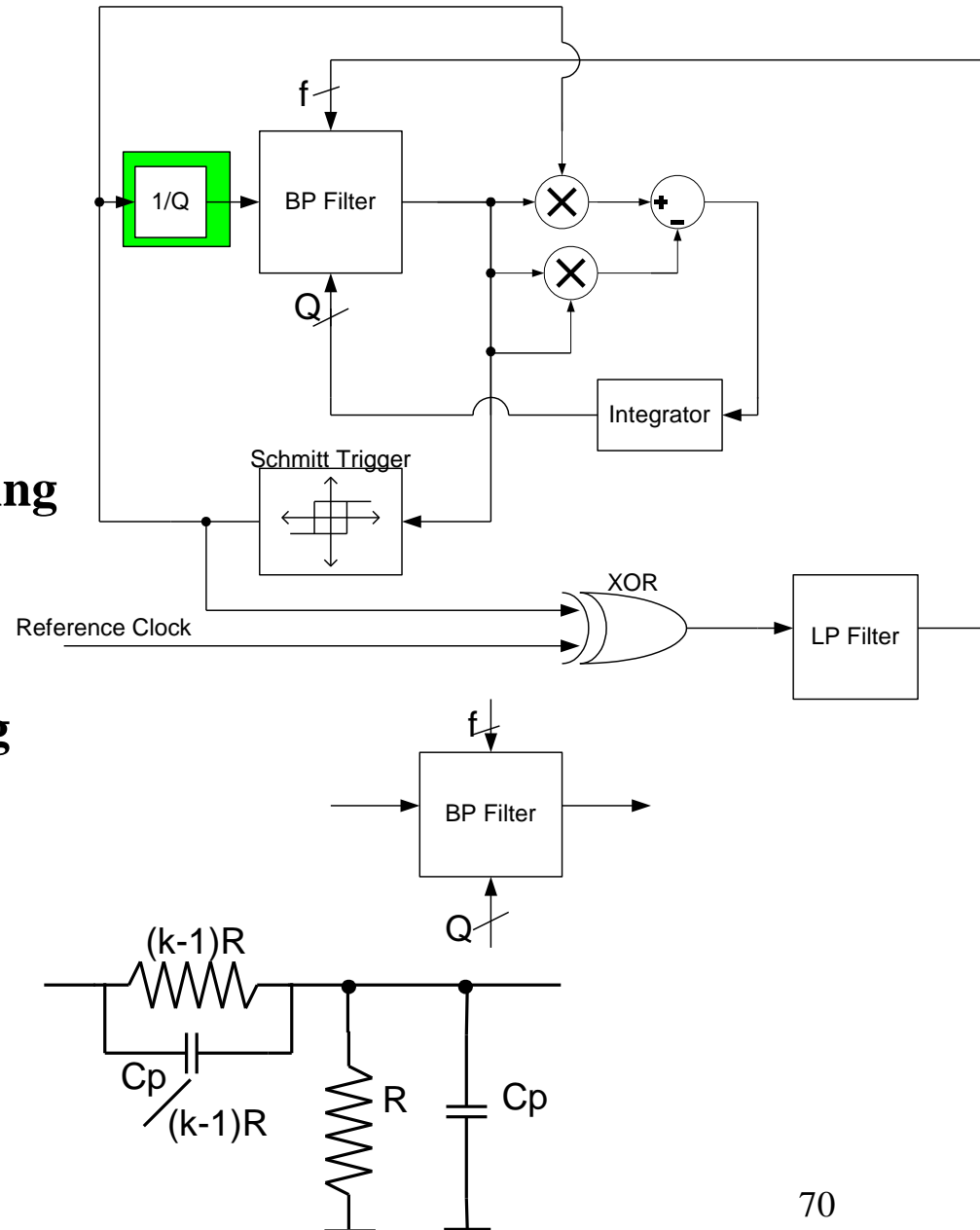
- **Capacitor**
 - Large capacitors for matching
 - Large capacitors → Large loading
- **Resistor**
 - Larger resistors for matching
 - Large resistors → Small loading
 - Should take parasitic capacitor into consideration




Multiplier

- Constraints

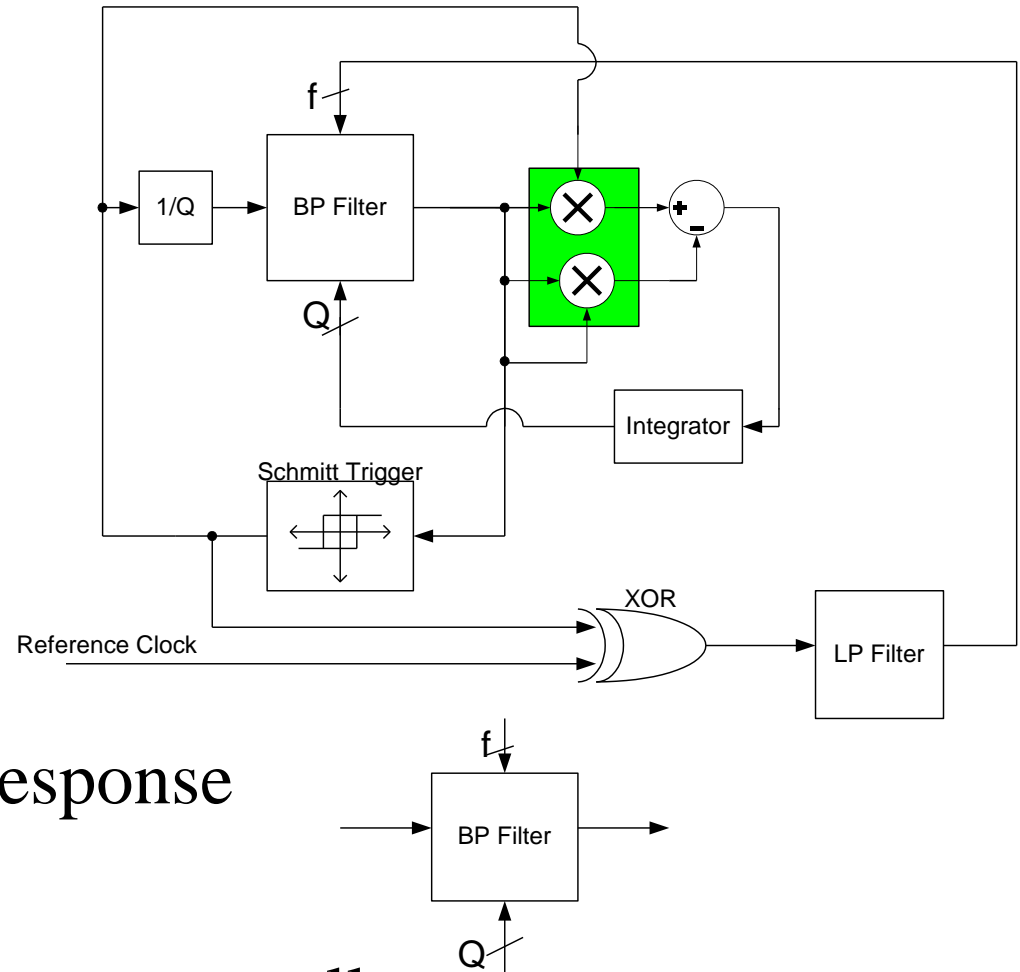- Symmetric
- Good frequency response
- Good CMRR
- Gain should not be very small




Multiplier

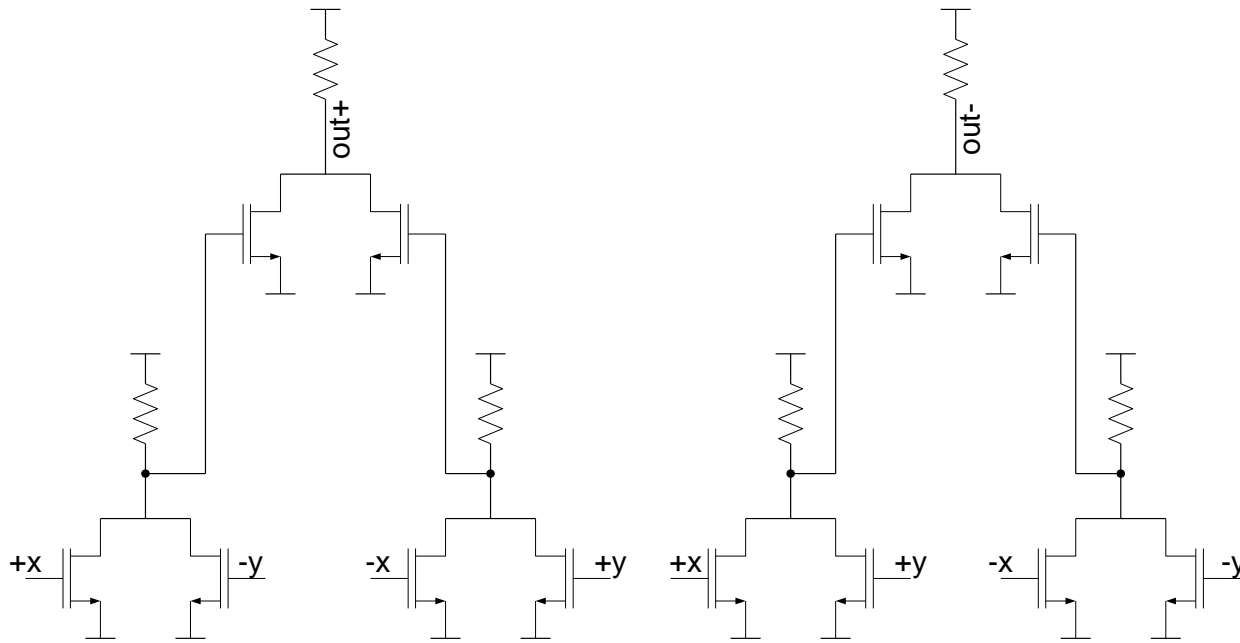

$$\text{Multiplier gain} = \frac{-32 V_{DD}^3}{(V_1 - V_T)^3}$$

$$\text{CM gain} = \frac{4 V_{DD}^2}{(V_1 - V_T)^2}$$

LPF

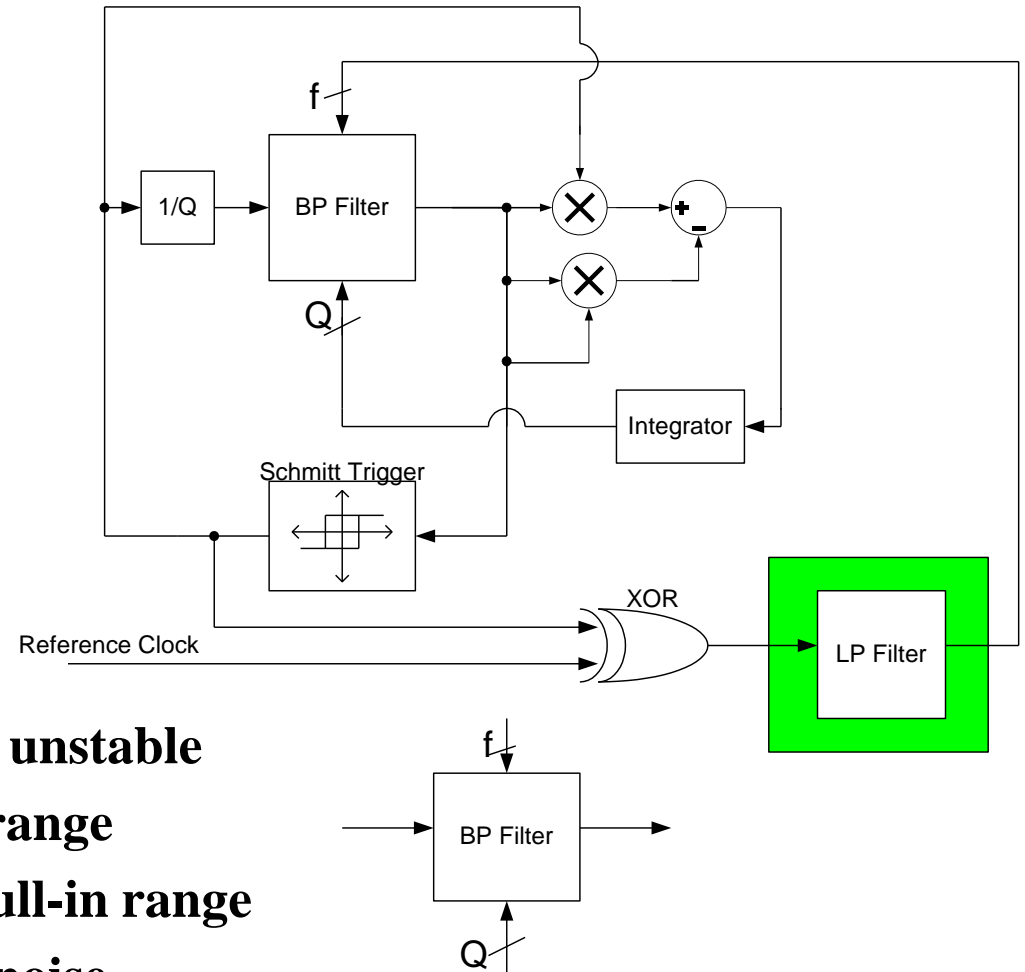


- **Constraints**

- High gain \Rightarrow PLL might be unstable
- Low gain \Rightarrow small pull-in range
- low cut-off freq \Rightarrow small pull-in range
- High cut-off freq \Rightarrow Jitter noise
- Single ended output

- **Built using external components for good control**

Differential difference adder

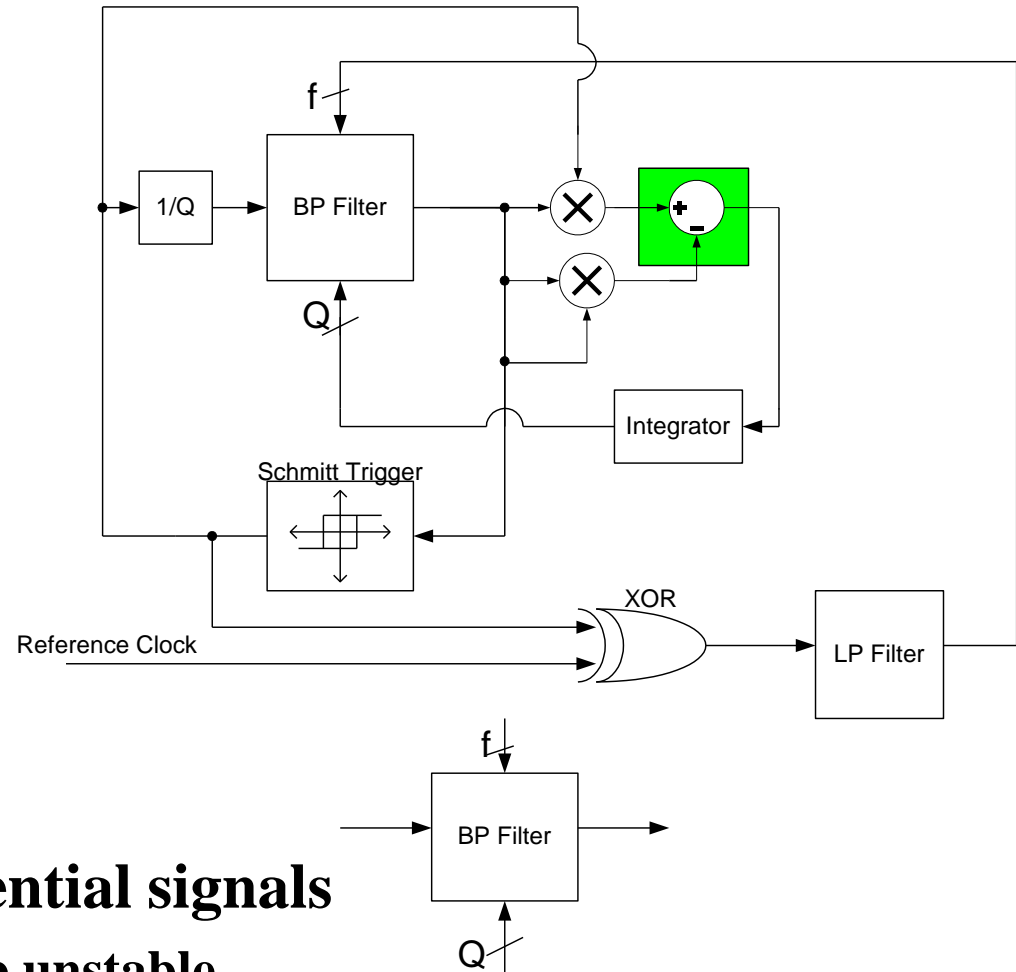


- **Add/Subtract two differential signals**
 - High gain $\Rightarrow Q$ tuning loop unstable
 - Low gain \Rightarrow Lesser accuracy
 - Need not have a good frequency response

Integrator


- Very high gain required to minimize Q tuning errors
- Frequency compensated Op-Amp in open loop can be used
- 3dB frequency should be as small as possible
- Phase margin as large as possible

Built using external components

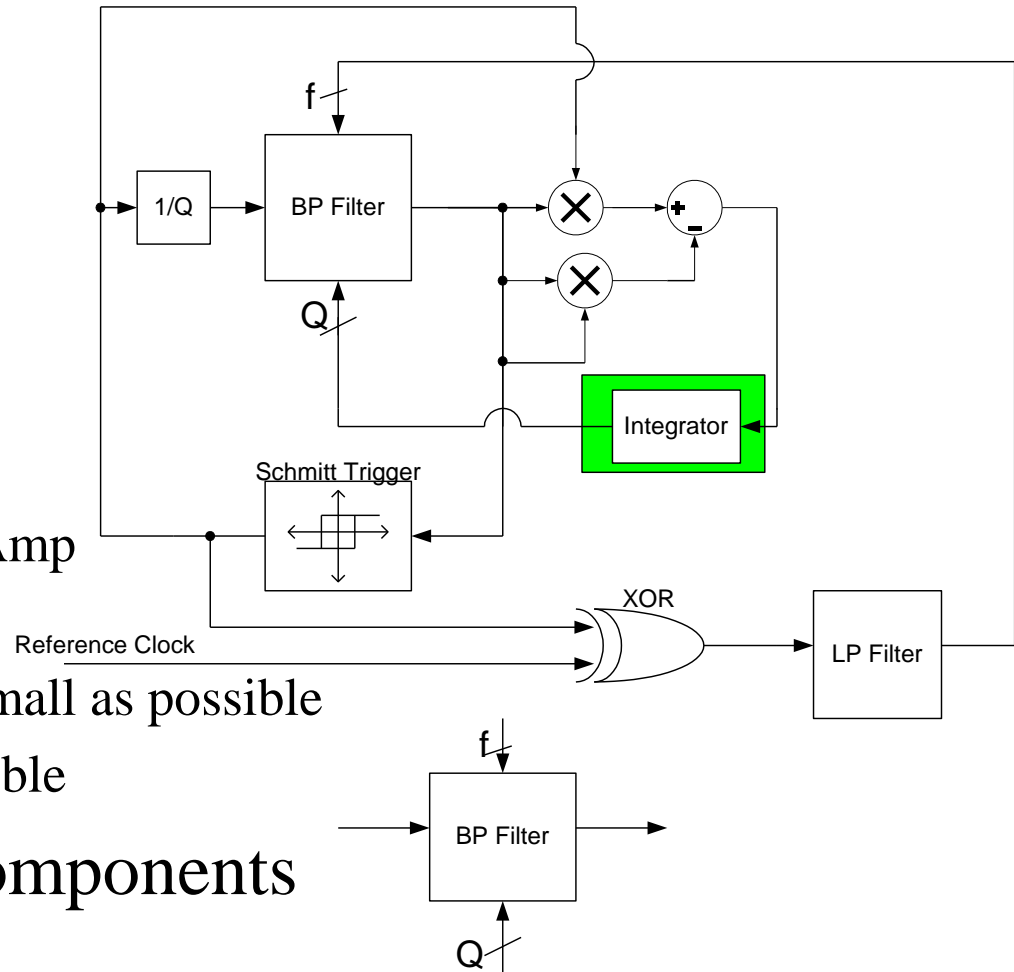


Simulated results for tuning scheme

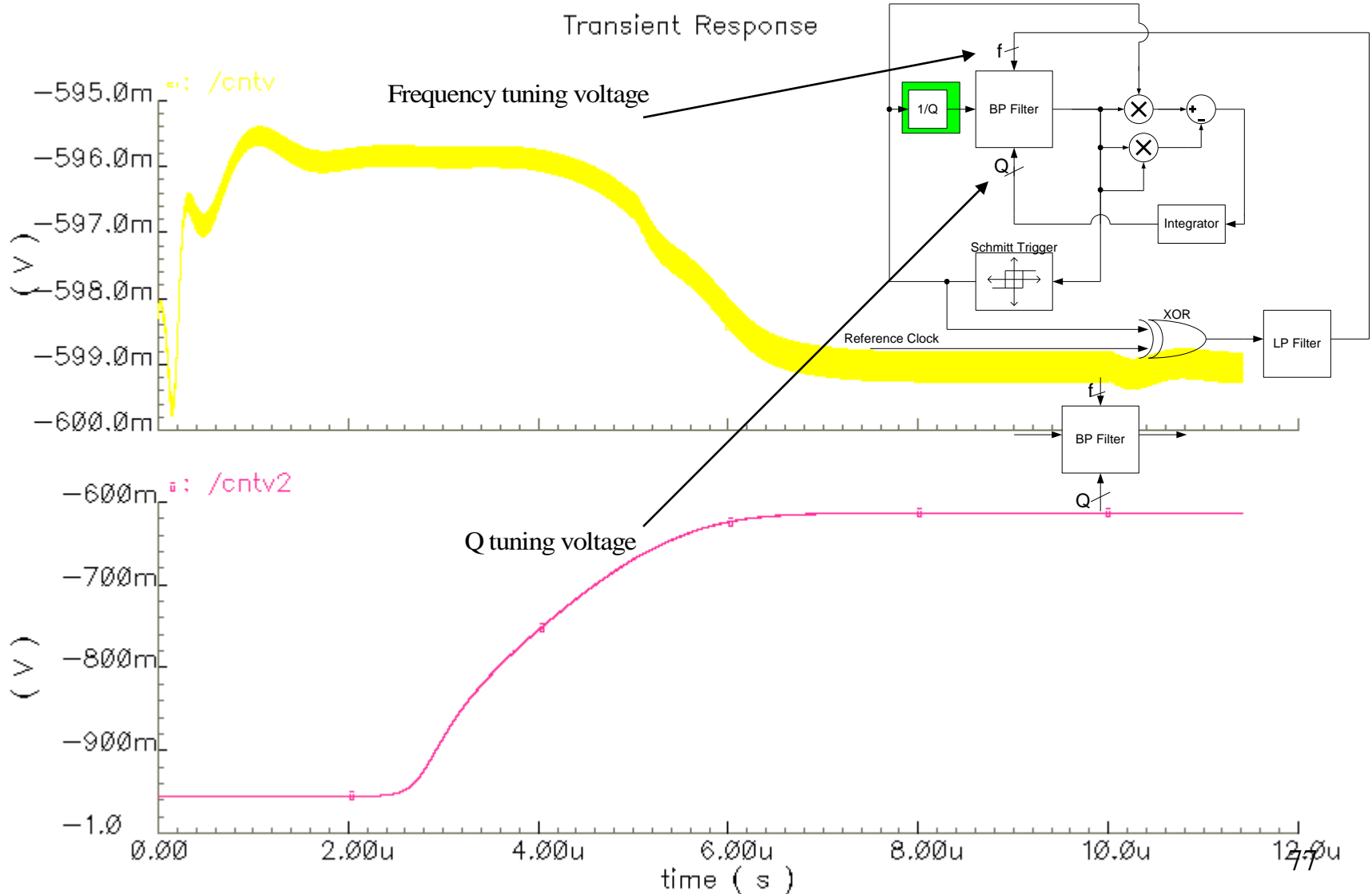proj_2 fQ_tun1 schematic : Dec 4 23:51:02 2000




Die Photograph

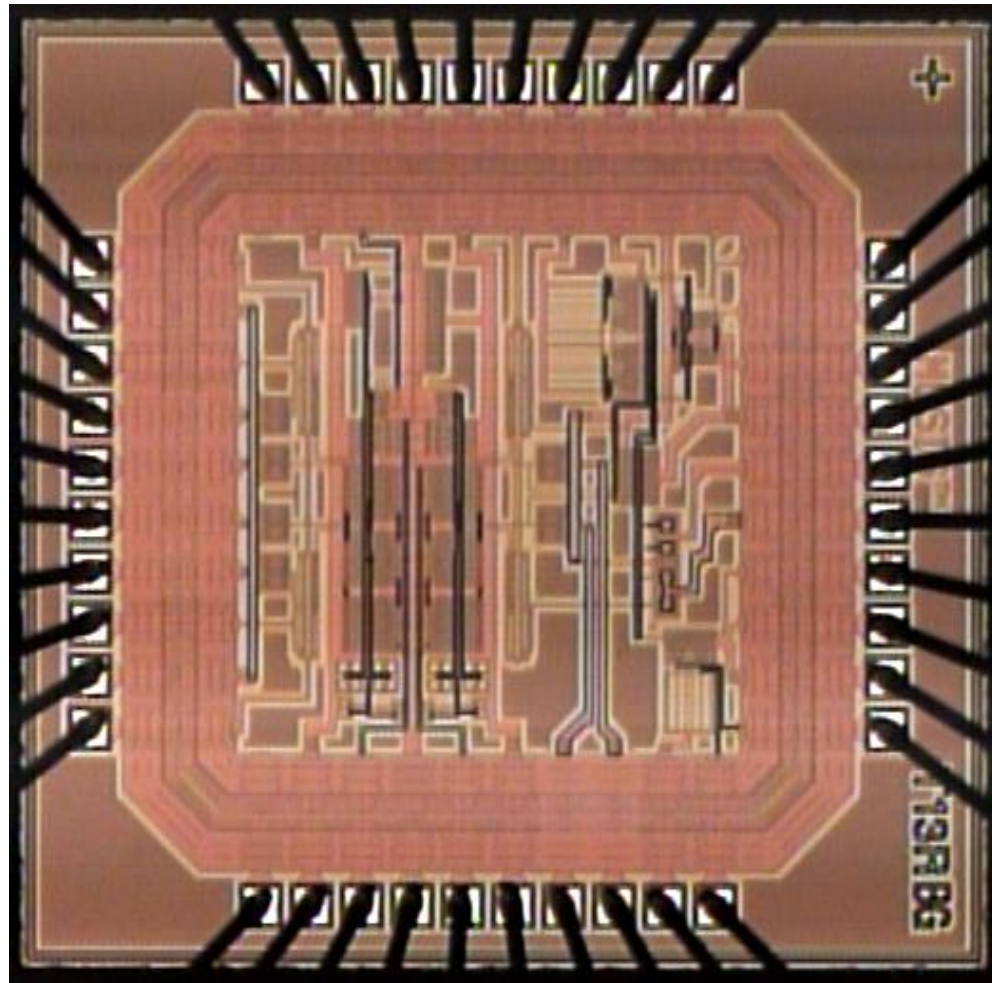

900um


900um

Experimental results on

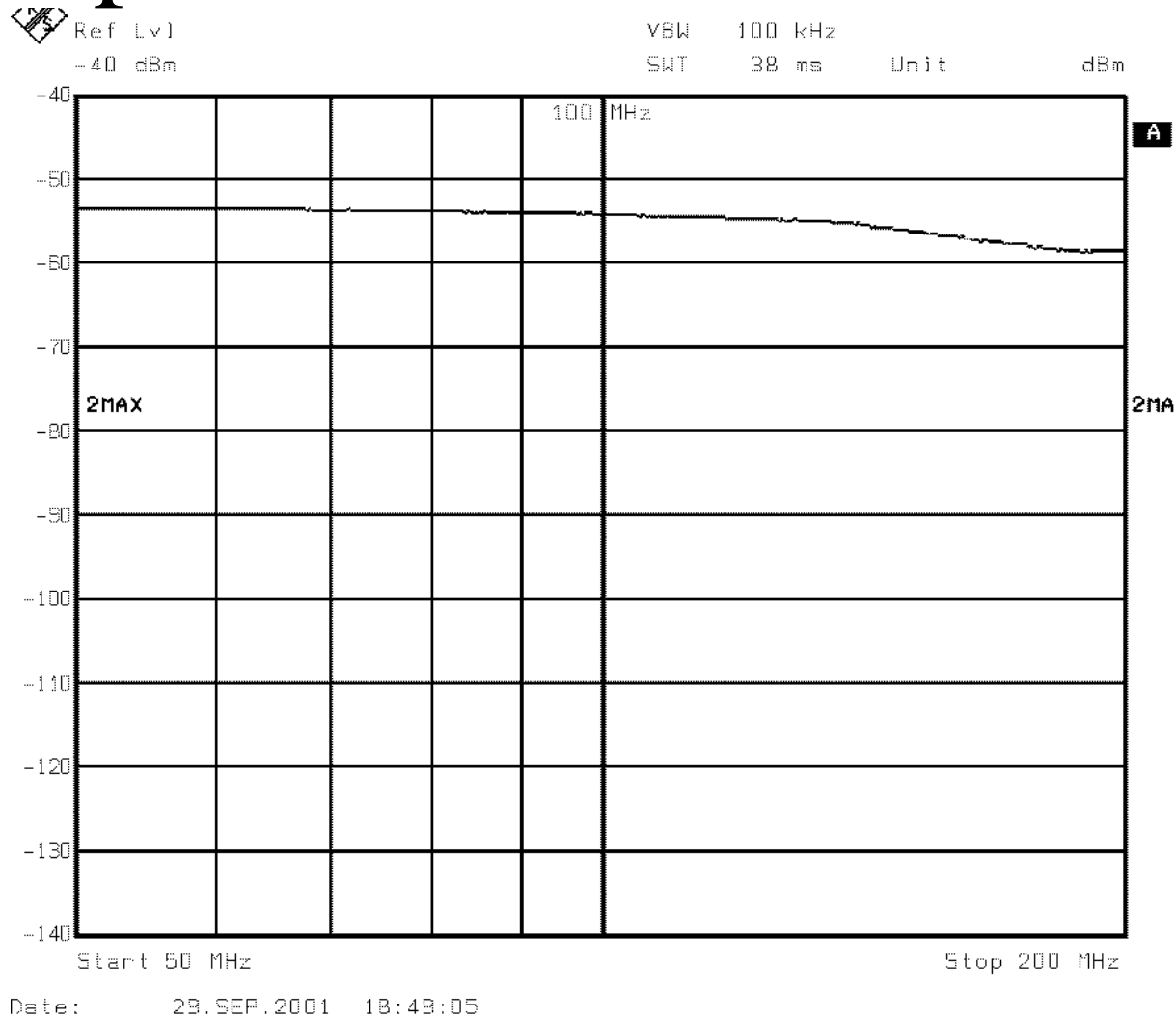


This response should be subtracted from other plots to get actual response

Filter response

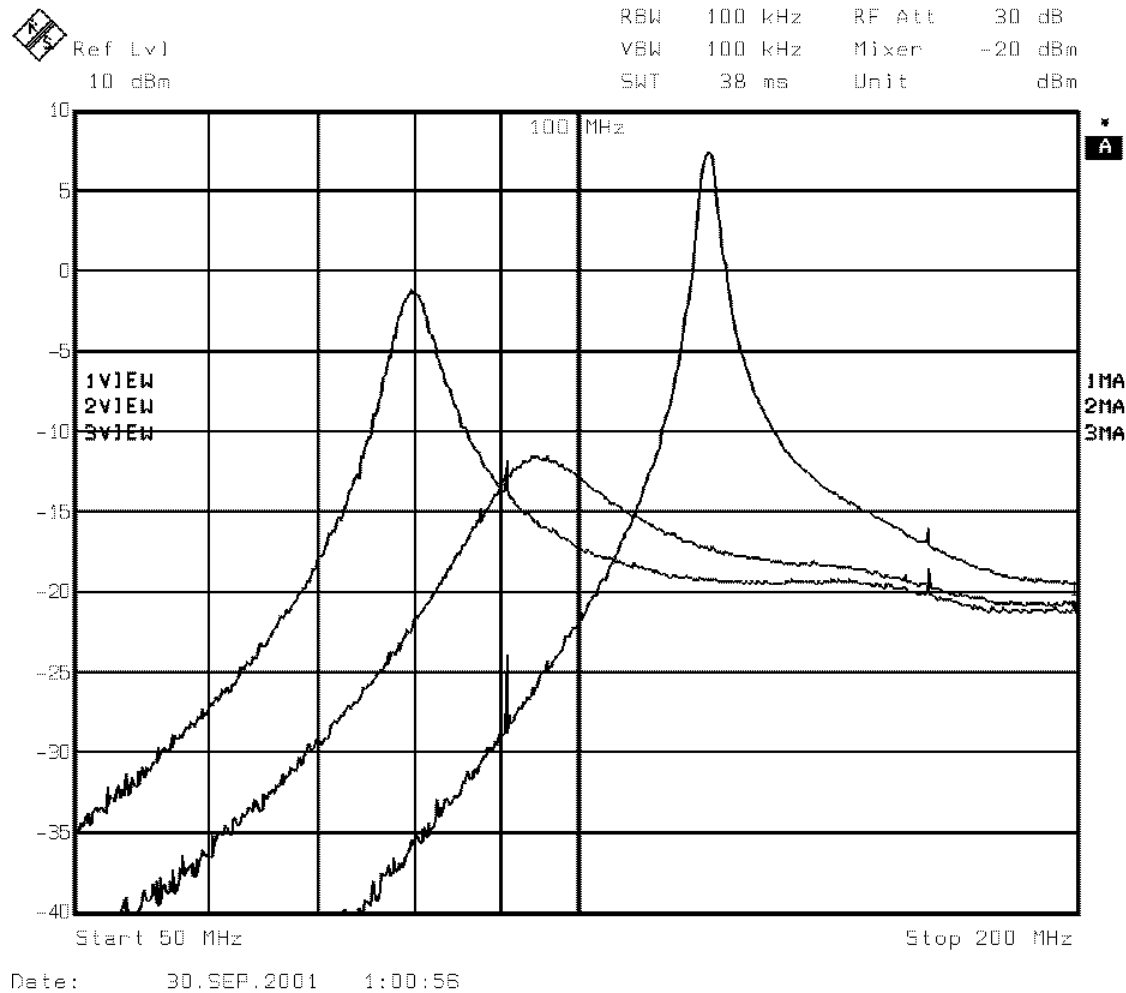


- Qs of 16, 5 and 40 at 80,95 and 110 MHz

DM-CM response of the filter

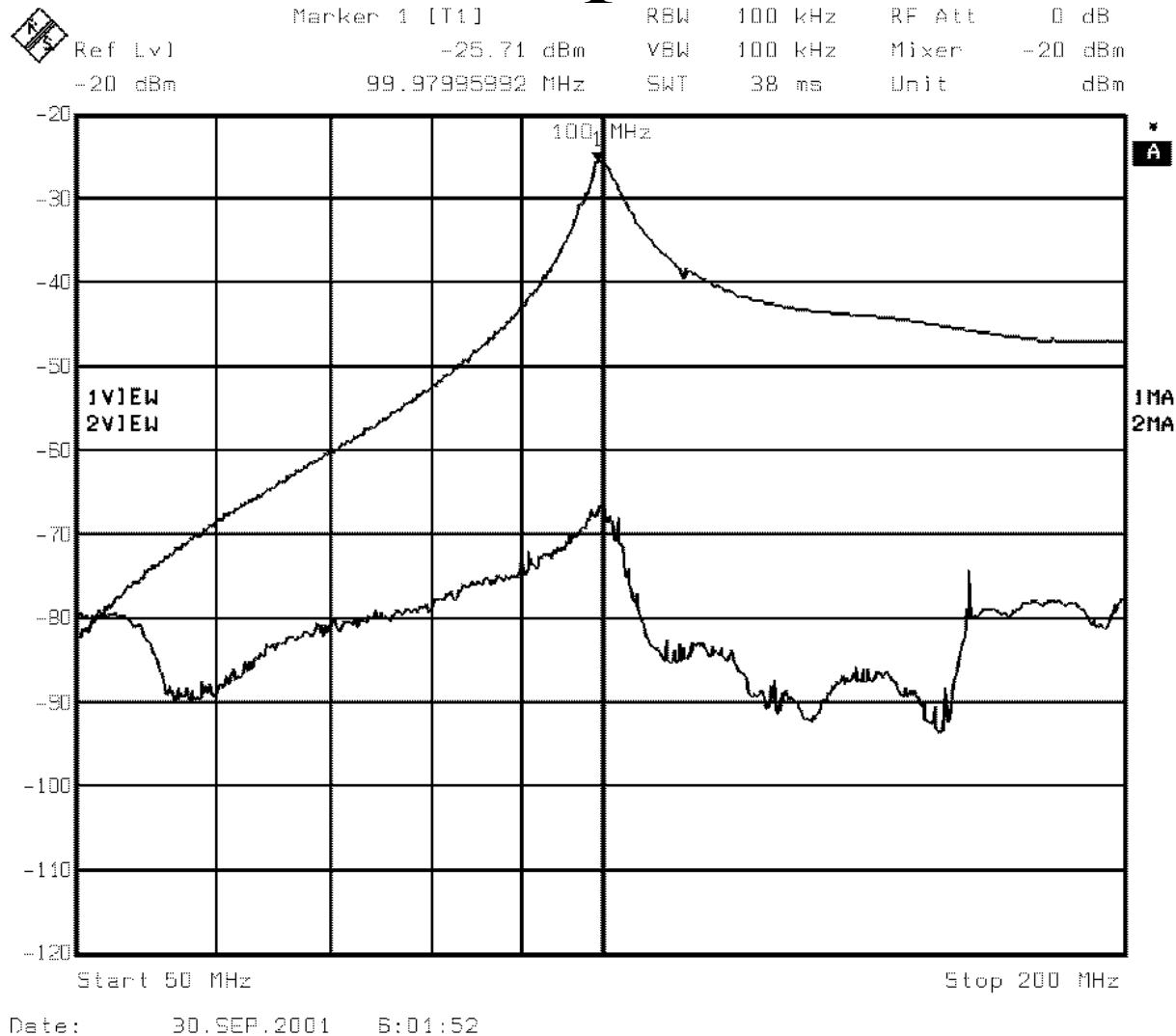


- CMRR is more than 40dB in the band of interest

Supply response of the filter

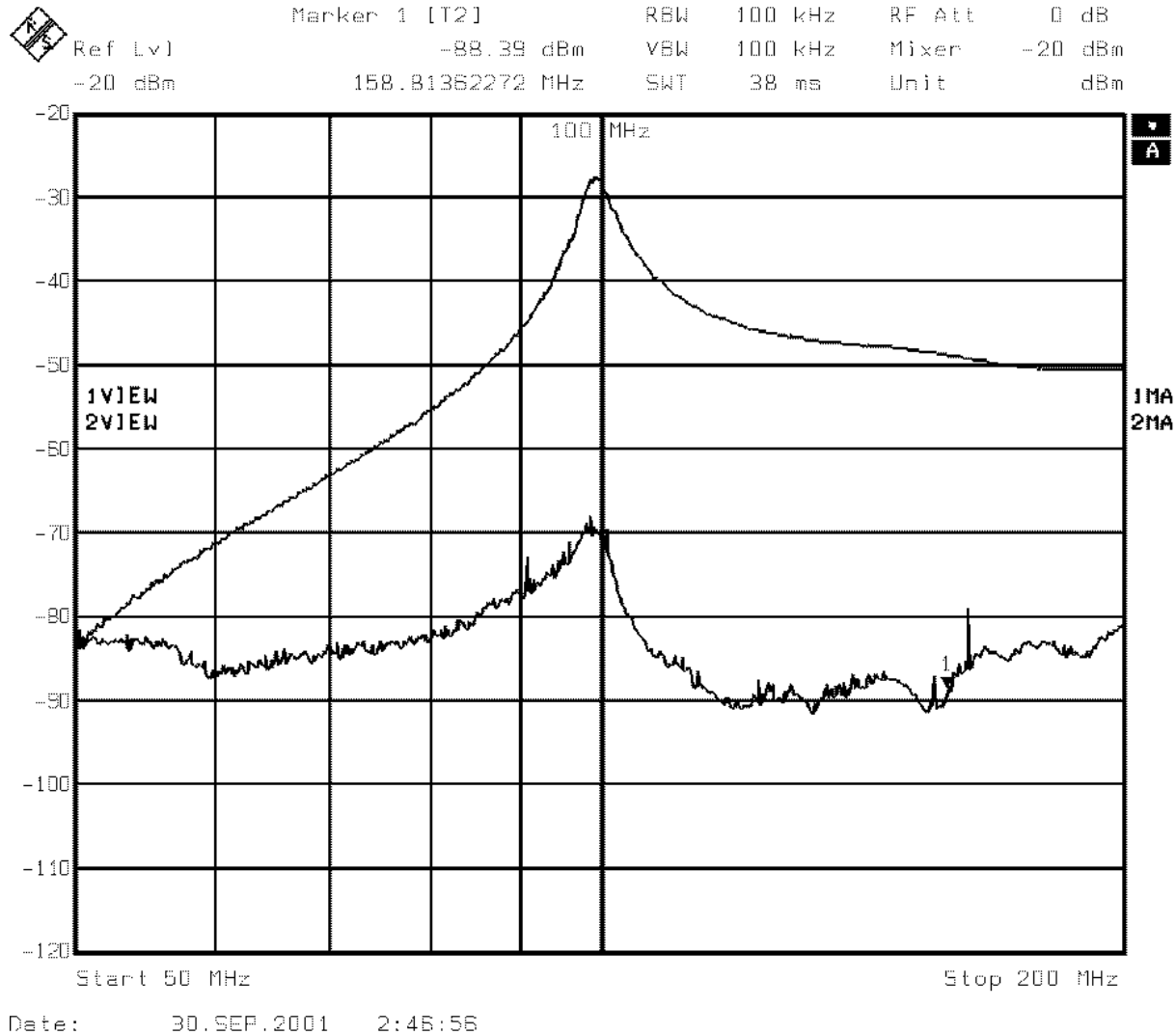


- PSRR is more than 40dB in the band of interest

Noise response of the filter

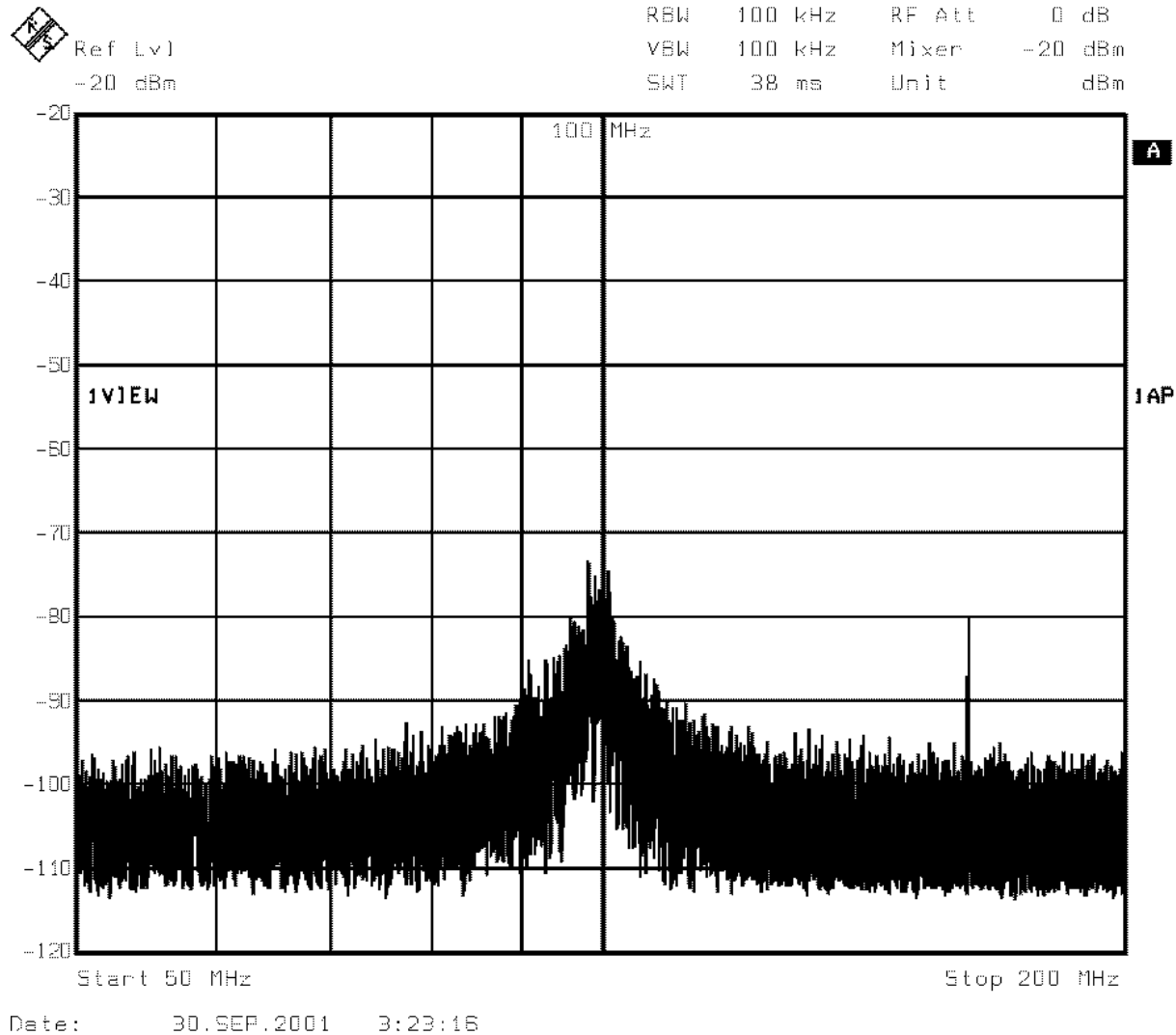


- Total integrated noise power at the output= -60dBm

Two-tone inter-modulation test

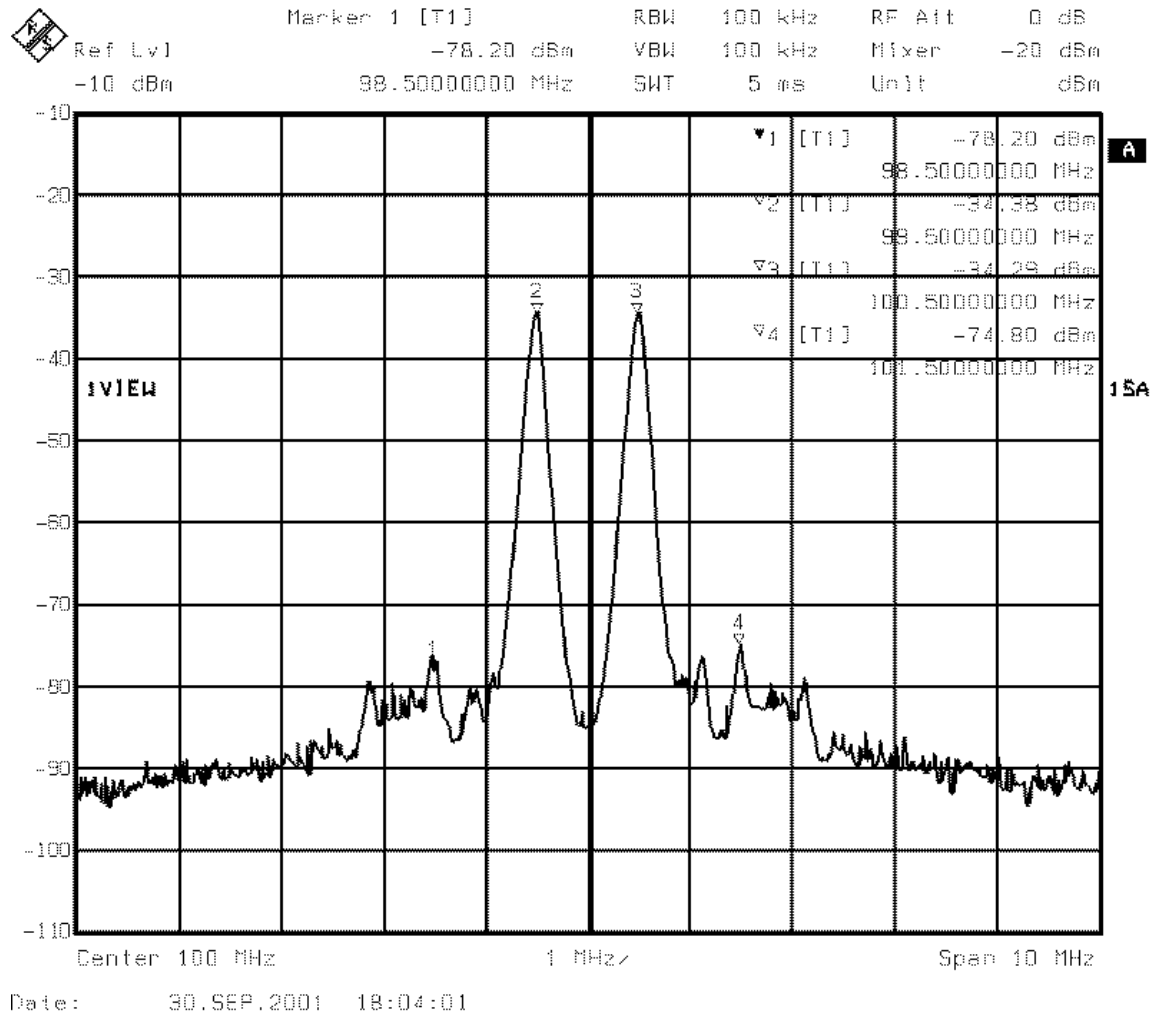


- IM_3 of 45dB when the input signal is 44.6mV

Filter response when tuned to Q=20

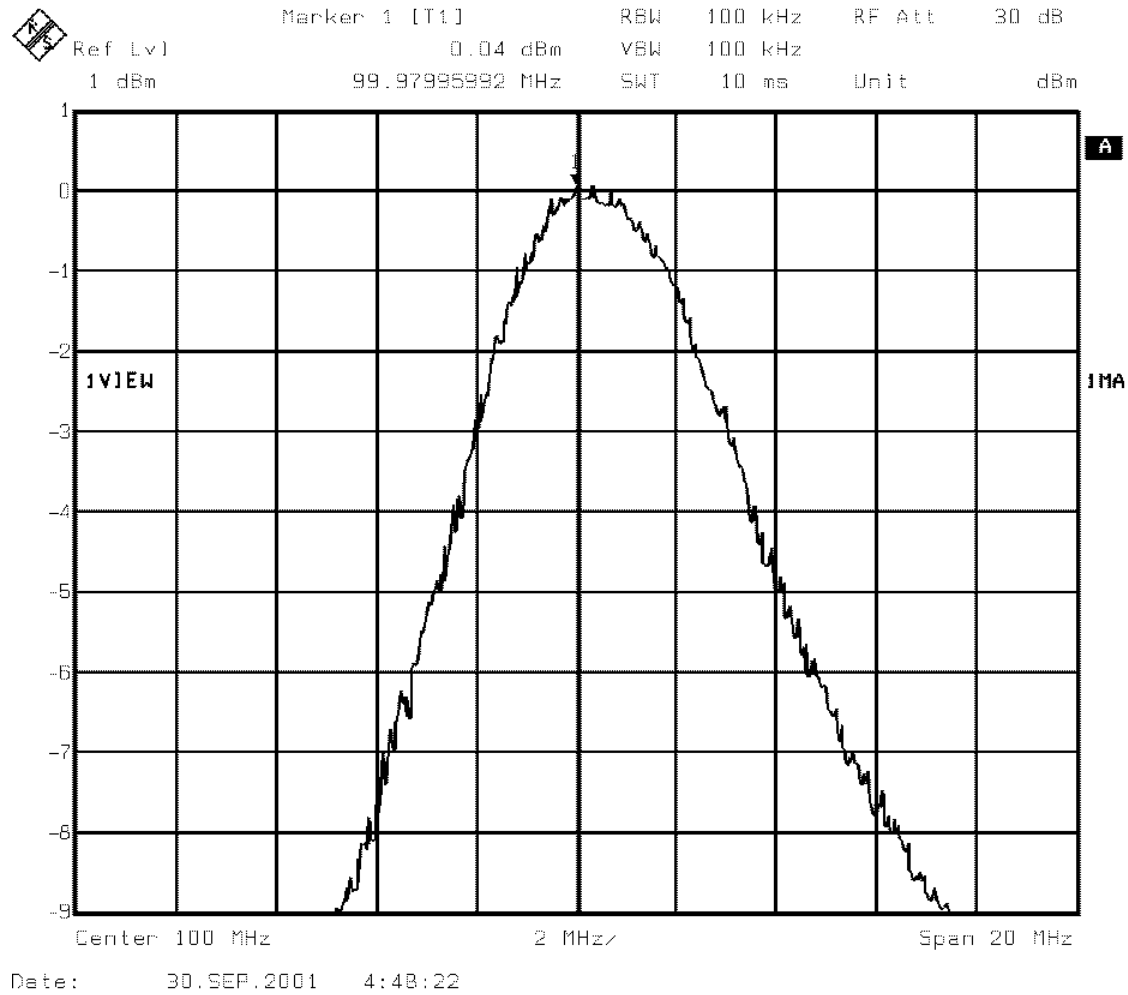


Both bandwidth and gain corroborate that accuracy of tuning is around 1%

Filter response for four different ICs

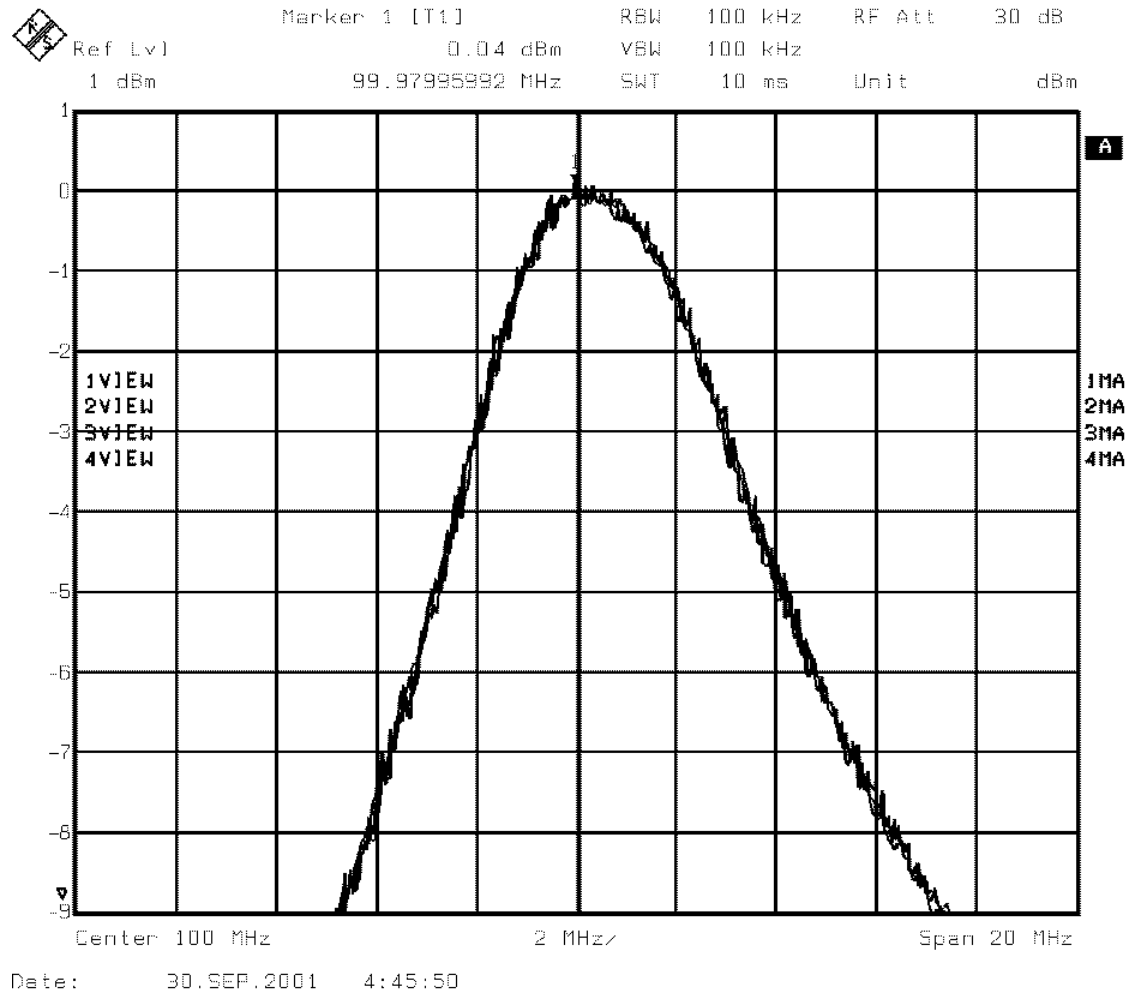

- Tuning accuracy is around 1%

Filter response for four different ICs

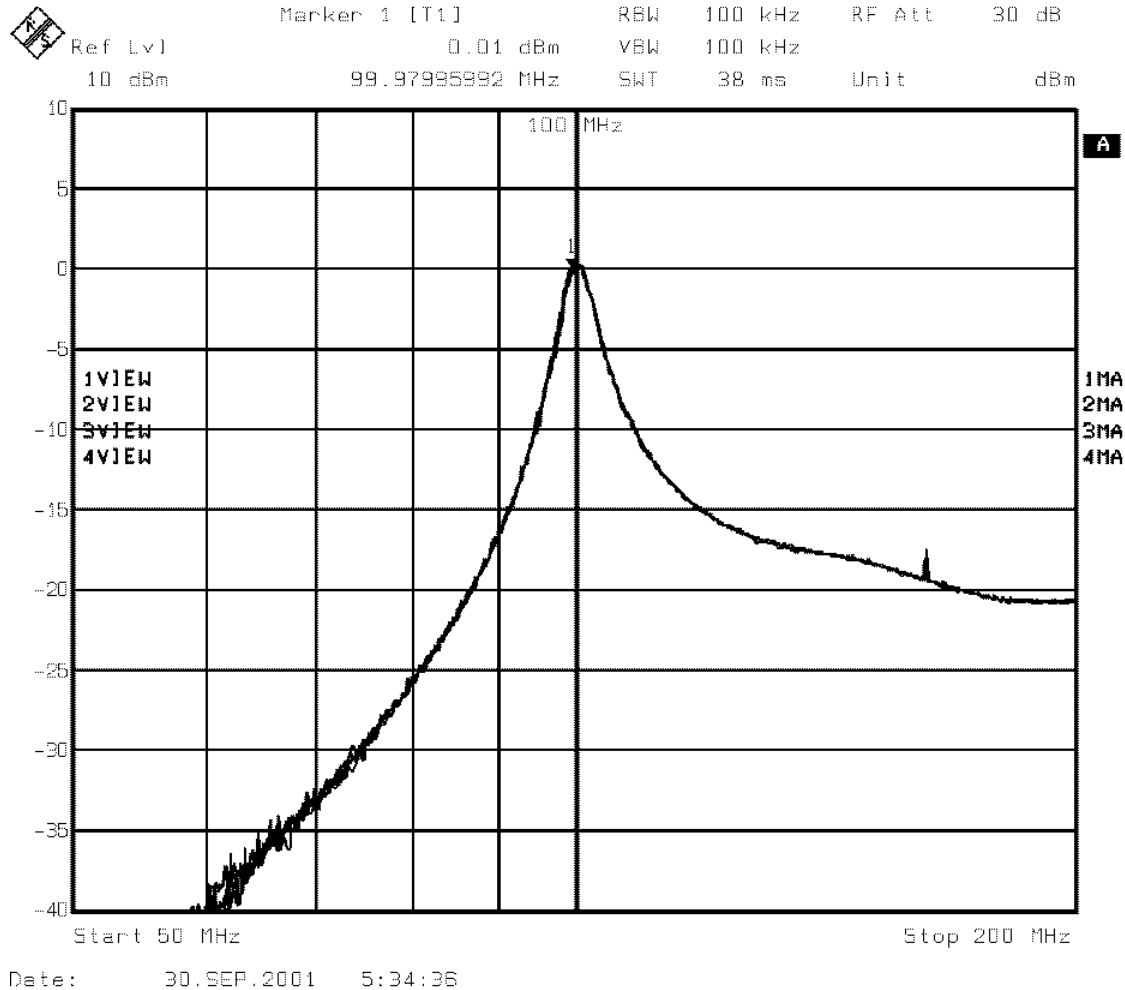

- The tuning works!

Conclusions

- A new high-frequency fully-differential OTA is designed.
- A band pass filter with $f=100\text{MHz}$ and $Q=20$ is designed using the new OTA in AMI0.5 μm
- A new tuning scheme for BP filters that overcomes many of the problems faced by previous scheme is implemented.

References

- Stevenson, J.M.; Sanchez-Sinencio, E “An accurate quality factor tuning scheme for IF and high-Q continuous-time filters”. Solid-State Circuits, IEEE Journal of Volume: 33 12 , Dec. 1998 , Page(s): 1970 -1978
- Class notes on converting a single ended Op-Amp circuit to a fully symmetric, fully differential circuit.
- Shuo-Yuan Hsiao and Chung-Yu Wu “a 1.2V CMOS Four-Quadrant Analog Multiplier” IEEE international symposium on Circuits and Systems, June 1997 Pages: 241: 244
- G.T Uehara, and P.R. Gray, “A 100 MHz output rate analog to digital interface for PRML magnetic-disk read channel in 1.2 μ m CMOS” Solid-State Circuits Conference, 1994. Digest of Technical Papers. 41st ISSCC. IEEE International. Page(s): 280 -281
- D.D.Kumar and B.J.Hunsinger “ACT-enabled 100MHz equalizer for 100MHz application” Magnetics, IEEE Transactions on Volume: 27 6 2 , Nov. 1991 , Page(s): 4799 -4803
- Philpott, R.A. Kertis, R.A. Richetta, R.A. Schmerbeck, T.J. and Schulte, D.J. “A 7 MBytes/s (65MHz) mixed signal magnetic recording channel DSP using partial response signaling with maximum likelihood detection” Solid-State Circuits, IEEE Journal of
Volume: 29 3 , March 1994 , Page(s): 177 -184
- Tao Hai and J.M. Khoury “A 190MHz IF, 400Msamples/s CMOS direct conversion band-pass $\Sigma\Delta$ modulator” Solid-State Circuits Conference, 1999. Digest of Technical Papers. ISSCC. IEEE International , Page(s): 60 -61
- J.Franca and Y.Tsividis (editors) *Design of analog-digital VLSI circuits for tele-communications and signal processing* Prentice Hall 1994, chapter 7-9

- F.Krummenachar and N.Joehl, “A 4-MHz CMOS continuous time filter with on chip automatic tuning”, *IEEE Journal of Solid-State Circuits*, vol. 23, pp. 750-758, June 1988.
- F.Krummenachar and N.Joehl, “A 4-MHz CMOS continuous time filter with on chip automatic tuning”, *IEEE Journal of Solid-State Circuits*, vol. 23, pp. 750-758, June 1988.
- H.Khorramabadi and P.Gray, “High-frequency CMOS continuous time filters”, *IEEE Journal of Solid-State Circuits*, vol. SC-19, pp. 939-948, December 1984.
- J. Silva-Martinez, M. Steyaert, and W. Sansen, “A 10.7-MHz 68-dB SNR CMOS CMOS continuous time filter with on chip automatic tuning”, *IEEE Journal of Solid-State Circuits*, vol. 27, pp. 1843-1853, December 1992.
- S.Pavan and Y.P.Tsividis, “An analytical solution for a class of oscillators, and its application to filter tuning”, *IEEE Transactions on Circuits and Systems I*, vol. 45, pp. 547 -556 May 1998
- O.Shana'a and R.Schaumann “Low-voltage high-speed current-mode continuous-time IC filters with orthogonal w-Q tuning” *IEEE Transactions on Circuits and Systems II*, vol. 46 pp. 390 -400, April 1999.
- O.H.W.Chou, J.E.Franca, R.P.Martins, J.C.Vital and C.A.Leme, “A 21.4 MHz Gm-C bandpass filter in 0.8um digital CMOS with on-chip frequency and Q-factor tuning”, 2nd IEEE-CAS Region 8 Workshop on Analog and Mixed IC Design, pp. 87 -90, 1997.
- C.Plett and M.A.Copeland, “A study of tuning for continuous-time filters using macromodels” *IEEE Transactions on Circuits and Systems II*, vol. 39, pp. 524 -531, Aug, 1992.

- J. Van der Plas, “MOSFET-C filter with low excess noise and accurate automatic tuning”, IEEE *Journal of Solid-State Circuits*, vol. 26, pp. 922-929, July 1991.
- T. Kwan and K. Martin, “A notch filter based frequency-difference detector and its applications”, in 1990 IEEE ISCAS Proceedings, pp. 1343-1346, 1990.
- A.I.Karsilayan and R.Schaumann “Automatic tuning of high-Q filters based on envelope detection” in 1999 IEEE ISCAS Proceedings, vol.2, pp. 668 -671, 1999.
- R. Schaumann, M. Ghauri and K.Laker, *Design of Analog Filters*, ch. 7. Englewood Cliffs, New Jersey: Prentice-Hall, 1990.
- B. Widrow, M.lehr, F.Beaufays, E.Wan and M.Bilello, “Learning algorithms for adaptive signal processing and control”, in 1993 IEEE ISCAS Proceedings, pp. 1-8, 1993.
- B.Nauta, “A CMOS transconductance-C filter technique for very high frequencies”, IEEE *Journal of Solid-State Circuits*, vol. 27, pp. 142 -153, Feb, 1992.
- V.Gopinathan, Y.P.Tsividis, K.S.Tan, and R.K.Hester, “Design considerations for high-frequency continuous-time filters and implementation of an antialiasing filter for digital video” IEEE *Journal of Solid-State Circuits*, vol. 25, pp. 1368 -1378, Dec, 1990.
- Gunhee Han and E.Sanchez-Sinencio, “CMOS transconductance multipliers: a tutorial”, IEEE *Transactions on Circuits and Systems II*, vol. 45, pp. 1550 -1563, Dec. 1998.
- J.Ramirez-Angulo and E.Sanchez-Sinencio, “Active compensation of operational transconductance amplifier filters using partial positive feedback”, IEEE *Journal of Solid-State Circuits*, vol. 25, pp. 1024 -1028, Aug, 1990.