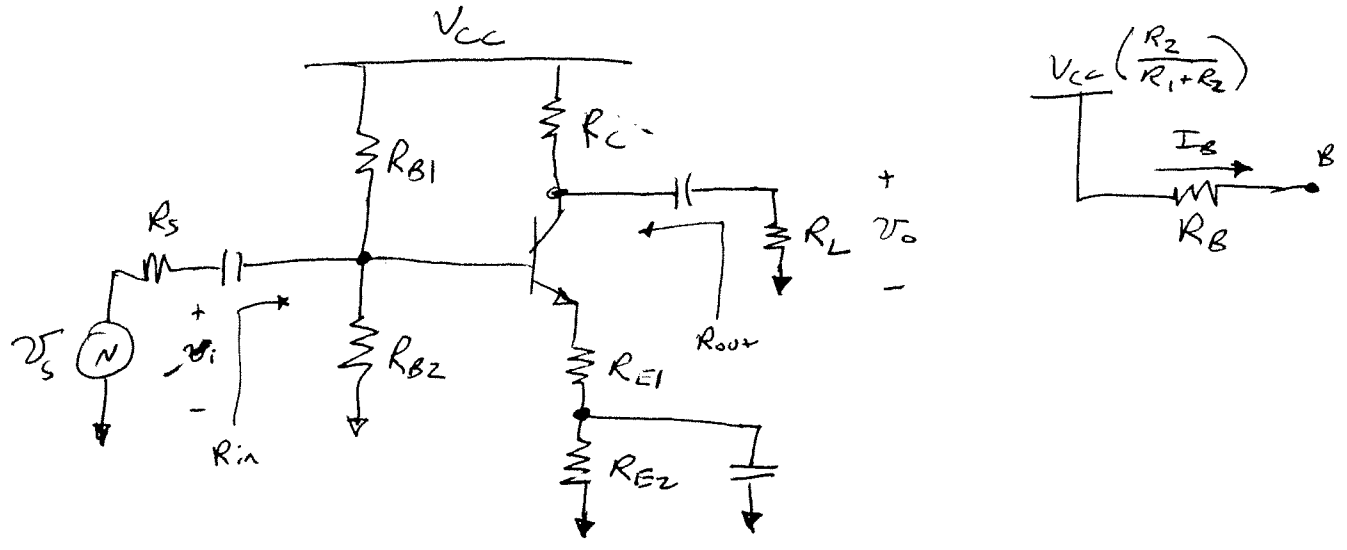



Common Emitter w/ Emitter Resistance



Why $R_E = R_{E1} + R_{E2}$?

The emitter resistor provides a DC bias point + more robust to variations in β and temperature. This comes at the cost of reduced gain.


* DC Biasing

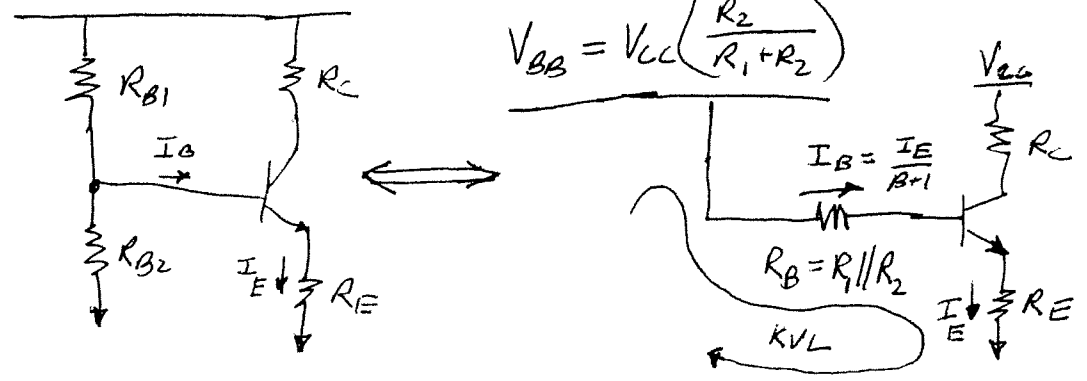

$$KVL: -V_{CC} \left(\frac{R_2}{R_1 + R_2} \right) + \frac{I_E R_B}{\beta + 1} + I_E R_E = 0$$

$$\Rightarrow I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}}$$

AC Equivalent Circuit (w/ T model)

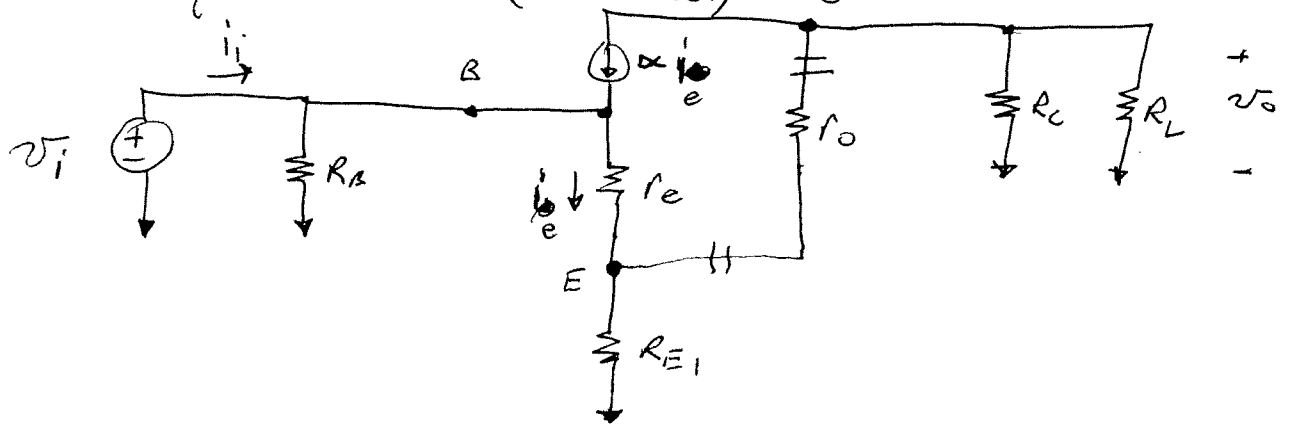

Neglecting r_o to simplify analysis

$$v_o = -\alpha i_e (R_C \parallel R_L)$$

$$i_e = \frac{v_i}{r_e + R_{E1}}$$

$$\Rightarrow A_V = \frac{v_o}{v_i} = -\frac{\alpha (R_C \parallel R_L)}{r_e + R_{E1}}$$


using $r_e = \frac{\alpha}{g_m}$

$$A_V = -\frac{\alpha (R_C \parallel R_L)}{\frac{\alpha}{g_m} + R_{E1}} = -\frac{g_m (R_C \parallel R_L)}{1 + \frac{g_m R_{E1}}{\alpha}}$$

A_V
reduced by
roughly
 $1 + g_m R_{E1}$

so, if $g_m R_{E1} \gg 1 \Rightarrow$ gain approaches $-\frac{R_C}{R_{E1}}$
(and R_L big)

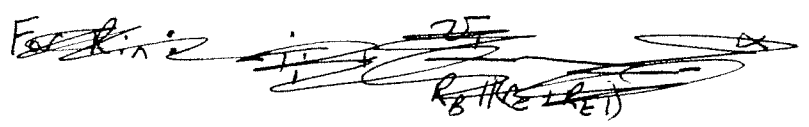\Rightarrow with Emitter cap can get both stable DC bias and high AC gain



* For R_{in} : KCL @ Base

$$-i_i + \frac{v_i}{R_B} + \frac{v_i}{r_e + R_{E1}} - \frac{\alpha v_i}{r_e + R_{E1}} = 0$$

~~$$v_i \left[\frac{1}{R_B} + \frac{1-\alpha}{r_e + R_{E1}} \right] = i_i$$~~

$$v_i \left[\frac{1}{R_B \parallel \left(\frac{r_e + R_{E1}}{1-\alpha} \right)} \right] = i_i$$

$$R_{in} = \frac{v_i}{i_i} = R_B \parallel \left[\frac{r_e + R_{E1}}{1-\alpha} \right] = R_B \parallel (\beta+1)(r_e + R_{E1})$$

using $\beta+1 = \frac{1}{1-\alpha}$

$$= R_B \parallel (r_{\pi} + (\beta+1)R_{E1})$$

if R_B is large $\Rightarrow R_{in}$ increases by roughly $(\beta+1)R_{E1}$

Using $\beta = g_m r_{\pi}$

$$R_{in} = R_B \parallel (r_{\pi} + (g_m r_{\pi} + 1)R_{E1})$$


$$\approx R_B \parallel r_{\pi} (1 + g_m R_{E1})$$

$\Rightarrow R_{in}$ has increased by roughly $1 + g_m R_{E1}$


* For R_o : w/ $v_i = 0, i_e = 0$

(Not affected much)


$$R_{out} = R_c$$

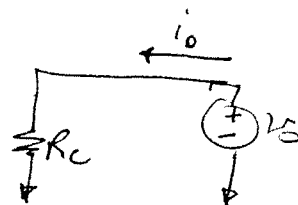

Common Collector

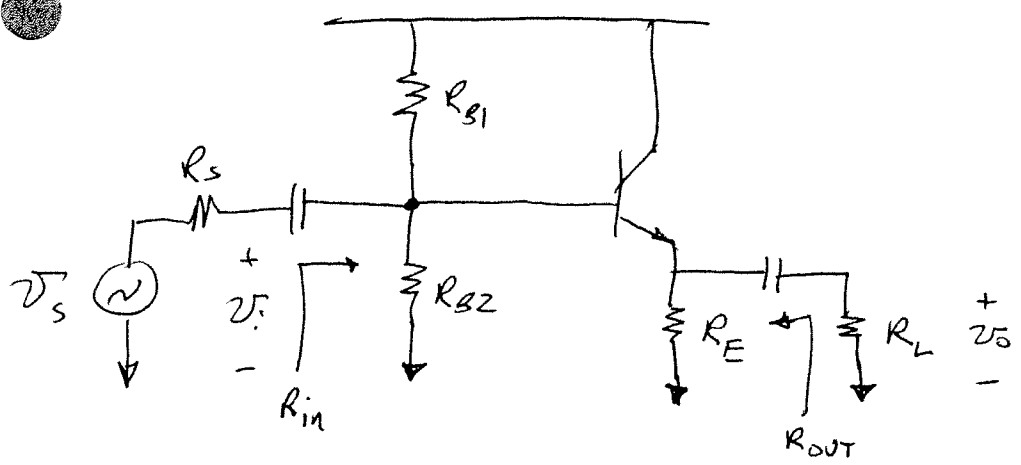

AC Equivalent Circuit (neglecting r_o)

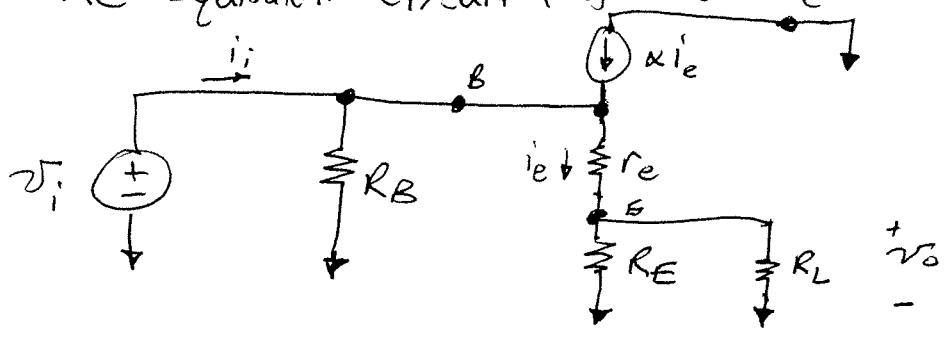

$$v_o = i_e (R_E \parallel R_L)$$


$$= \frac{v_i (R_E \parallel R_L)}{r_e + R_E \parallel R_L}$$


$$A_v = \frac{v_o}{v_i} = \frac{R_E \parallel R_L}{r_e + R_E \parallel R_L} \quad (< 1)$$

For R_{in} : Same as CE, but w/ $R_E \parallel R_L$



$$R_{in} = R_B \parallel \left[r_{\pi} + (\beta + 1)(R_E \parallel R_L) \right] \quad \left(\begin{matrix} \text{High} \\ R_{in} \end{matrix} \right)$$

For R_{out}

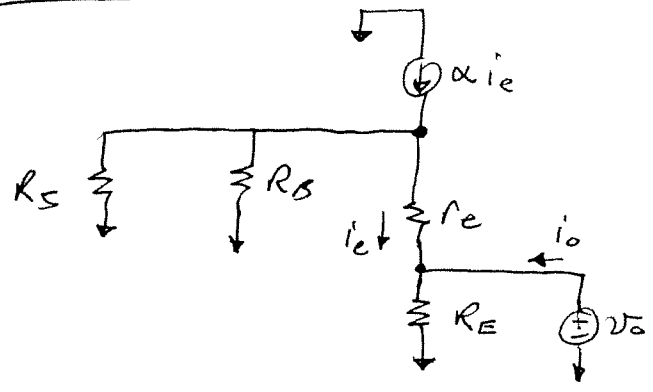

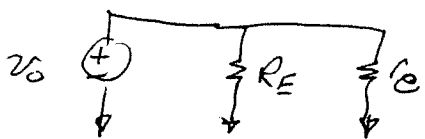IF $R_S = 0 \Rightarrow v_o$  $R_{out} = R_E || r_e$

W/ R_S

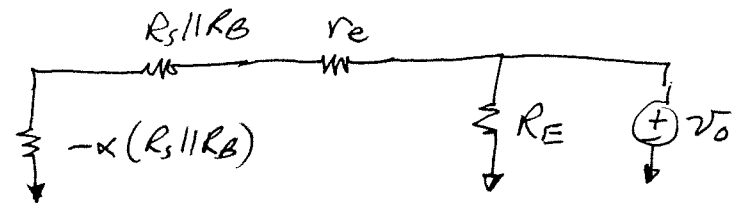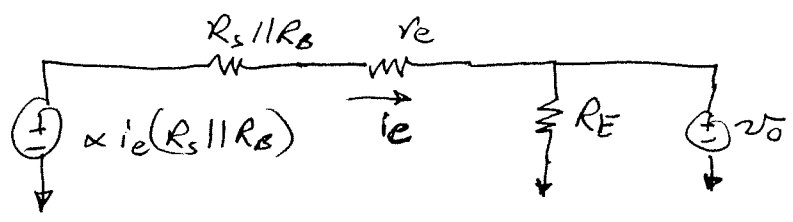


$$R_{out} = R_E || \left[r_e + (R_S || R_B)(1 - \alpha) \right]$$

$$R_{out} = R_E || \left[r_e + \frac{R_S || R_B}{\beta + 1} \right]$$


(Low)
 $\approx r_e$

* While this circuit has $A_v < 1$, it has high R_{in} and low $R_{out} \Rightarrow$ Useful as a buffer or output stage

Common Base

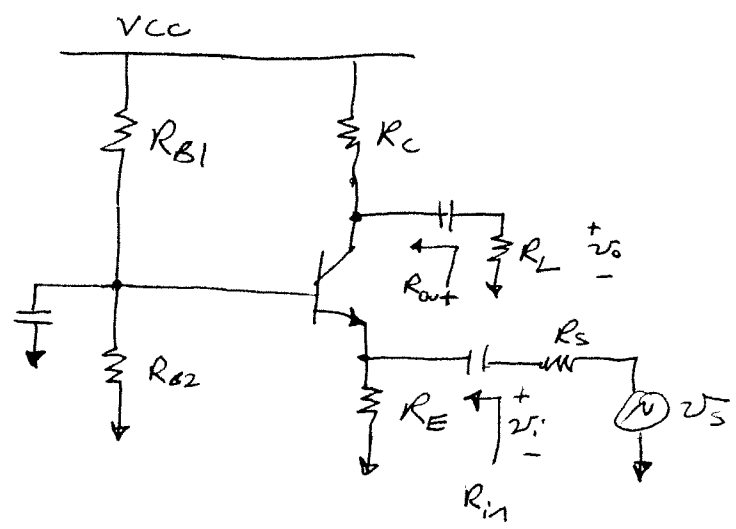

AC Equivalent Circuit (Neglecting r_e)

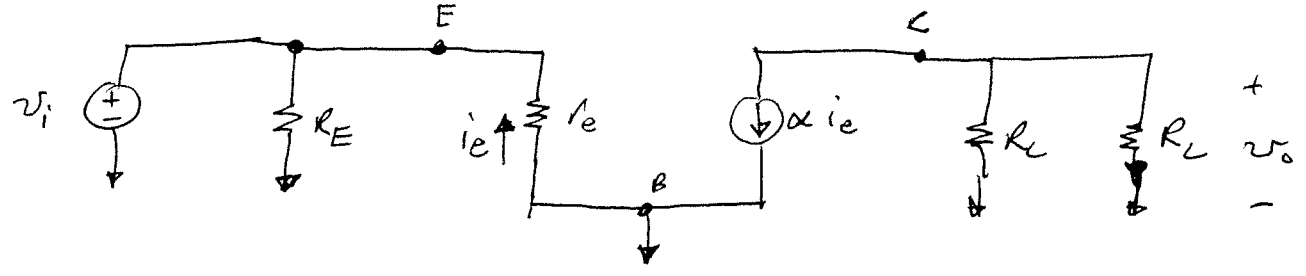

$$v_o = -\alpha i_e (R_c \parallel R_L)$$


$$i_e = -\frac{v_i}{r_e}$$

$$A_v = \frac{v_o}{v_i} = \frac{\alpha (R_c \parallel R_L)}{r_e} = g_m (R_c \parallel R_L)$$

(Medium gain)
(Non-Inv)

$$R_{in} = R_E \parallel r_e \quad (\text{low})$$

For R_{out}

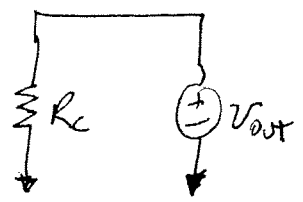

$$R_{out} = R_c \quad (\text{High})$$