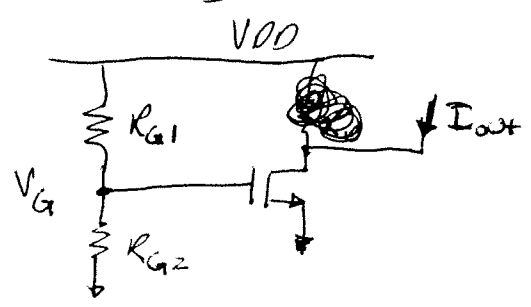


Single Stage Amplifier Comparison

	CS	CG	CD
Input/Output Phase	180°	0°	0°
R _{in}	High	Low	High
R _{out}	High	High	Low
A _v	Medium	Medium	< 1
Application	Voltage Amp	I-V Amp (TIA)	Buffer

Current Mirrors/Biasing^{DC}

* Resistive Biasing



Assuming Saturation

$$I_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_G - V_{TN})^2$$

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left(\frac{R_{G2}}{R_{G1} + R_{G2}} V_{DD} - V_{TN} \right)^2$$

I_{out} is sensitive to:

Supply : V_{DD}


Process : V_T can vary by ~ 100mV from wafer to wafer

B (μ_nC_{ox} $\frac{W}{L}$) can vary by ~ 5-15%


Temperature : μ_n and V_T sensitive to temp

* Current Mirrors

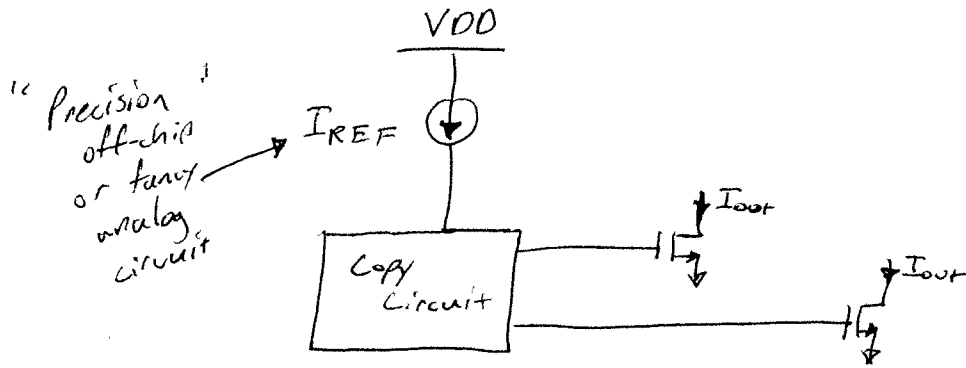In ~~the~~ IC design we assume that we have one precise current source and we copy its value to our circuits.



* Basic Current Mirror

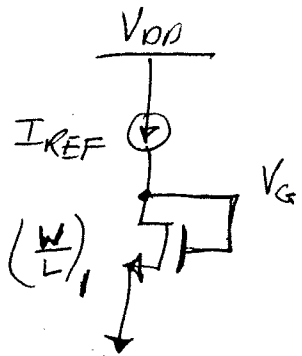


What is V_G ?

$$I_D = \frac{K_{PN}}{2} \left(\frac{W}{L}\right)_1 (V_G - V_{TN})^2$$

$$V_G = \sqrt{\frac{2I_{REF}}{K_{PN} \left(\frac{W}{L}\right)_1}} + V_{TN}$$

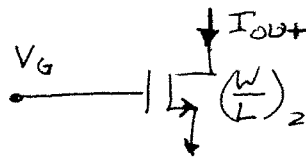
If I apply this V_G to another transistor



$$I_{out} = \frac{K_{PN}}{2} \left(\frac{W}{L}\right)_2 \left(\sqrt{\frac{2I_{REF}}{K_{PN} \left(\frac{W}{L}\right)_1}} + V_{TN} - V_{TN} \right)^2$$

$$I_{out} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} I_{REF}$$


Example

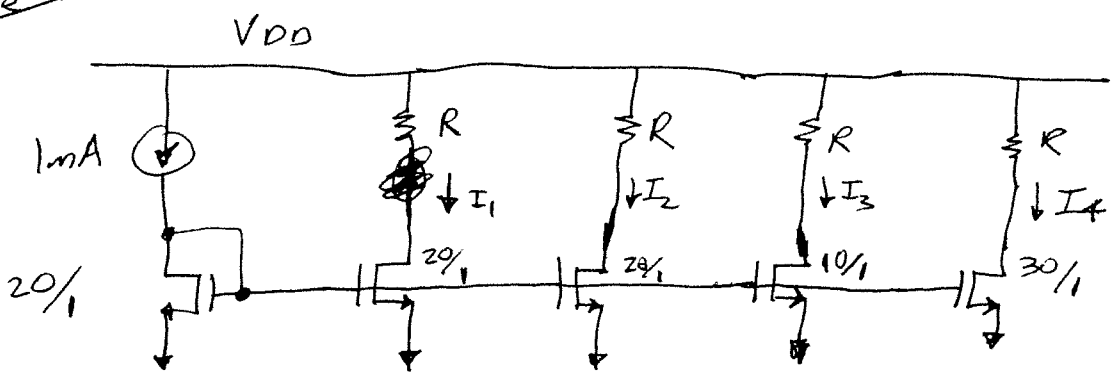

$I_1 = 1mA$
 $I_2 = 1mA$
 $I_3 = 0.5mA$
 $I_4 = 1.5mA$

This bias scheme reduces sensitivity to PVT.

Common-Source Amp w/ Current Source

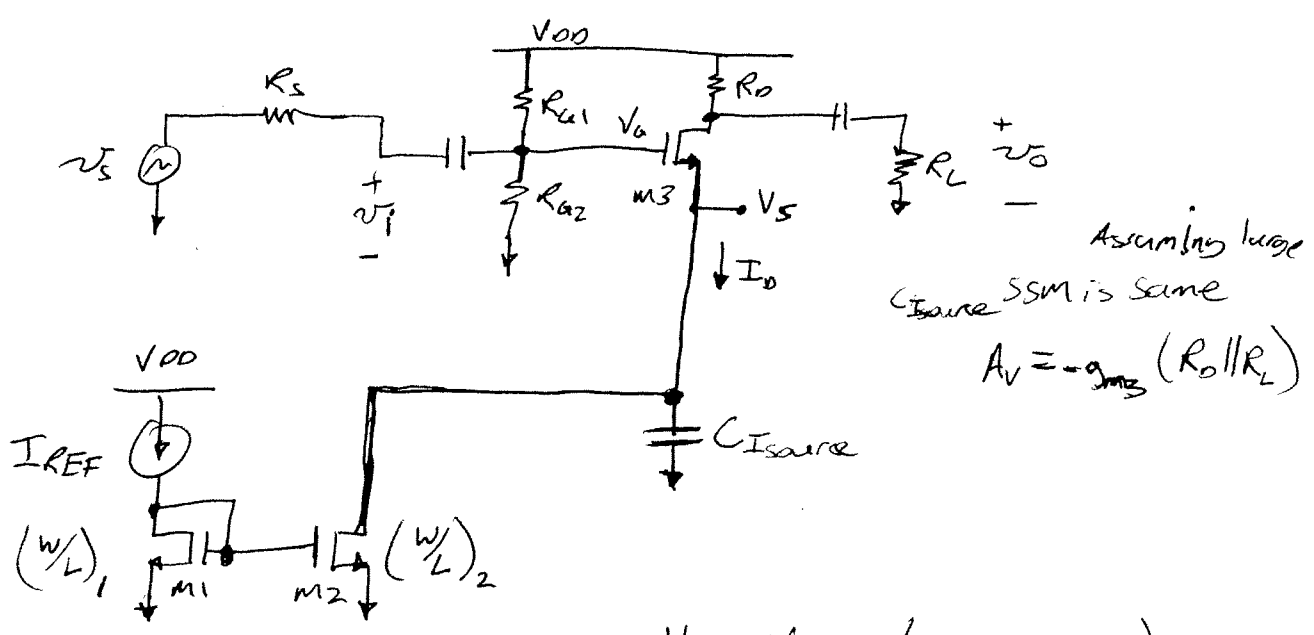

Assuming large $C_{issource}$ SSN is same
 $A_v = -g_{m3} (R_D || R_L)$


$V_s = V_g - (V_{DD} + V_{TN})$

$I_D = \frac{(W/L)_2}{(W/L)_1} I_{REF}$

$$V_s = \left(\frac{R_{g2}}{R_{g1} + R_{g2}} \right) V_{DD} - \left(\sqrt{\frac{2I_D}{K_{PN} (W/L)}} + V_{TN} \right)$$

(check that current source M2 is sat.)

PMOS Review / SSM

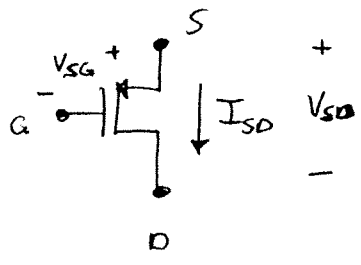

For Saturation: $V_{SD} \geq V_{SG} - |V_{TP}|$

$$I_{SD} = \frac{1}{2} K_P \frac{W}{L} (V_{SG} - |V_{TP}|)^2 (1 + \lambda_P V_{SD})$$

For AC Small-Signal Analysis

$$i_{sd} = \underbrace{\frac{\partial I_{SD}}{\partial V_{SG}}}_{g_m} v_{sg} + \underbrace{\frac{\partial I_{SD}}{\partial V_{SD}}}_{g_o} v_{sd}$$


$$g_m = \left. \frac{\partial I_{SD}}{\partial V_{SG}} \right|_Q = K_P \frac{W}{L} (V_{SG} - |V_{TP}|) \quad \left(\text{neglect } 1 + \lambda_P V_{SD} \text{ here} \right)$$

$$g_o = \left. \frac{\partial I_{SD}}{\partial V_{SD}} \right|_Q = \lambda_P \frac{1}{2} K_P \frac{W}{L} (V_{SG} - |V_{TP}|)^2 = \lambda_P I_D$$


(where I_D is w/o $1 + \lambda_P V_{SD}$ term)

Formal SSM

π -model

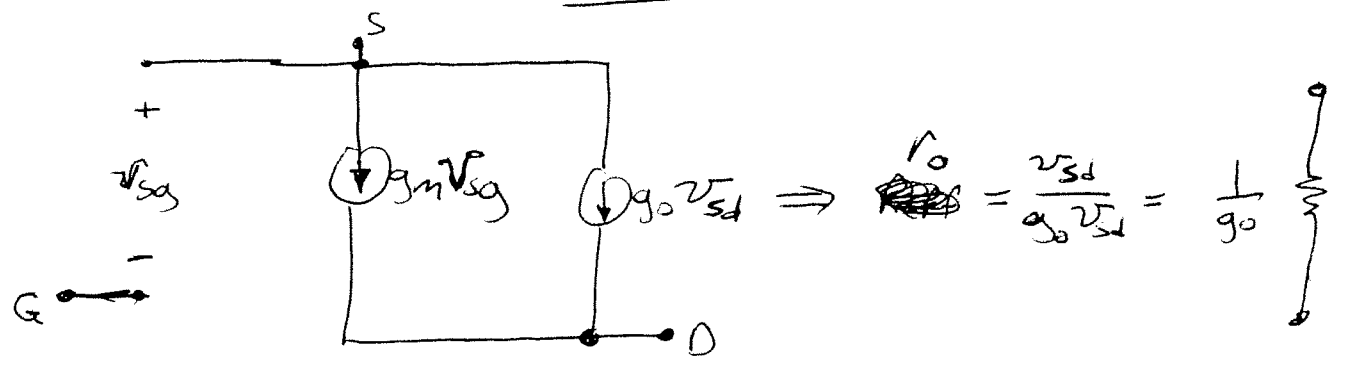


If we use V_{gs} instead of V_{sg}

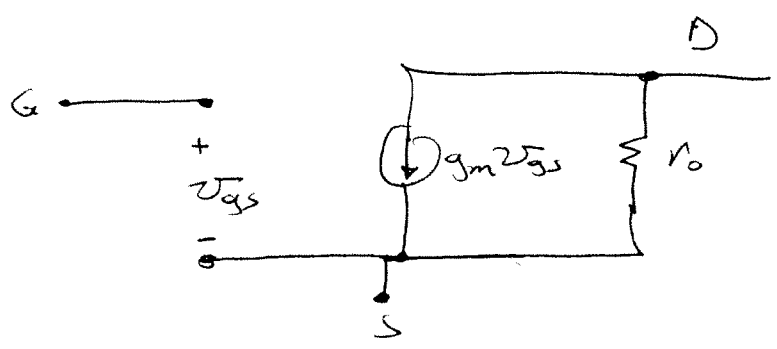


⇒ Same model as NMOS

π-model

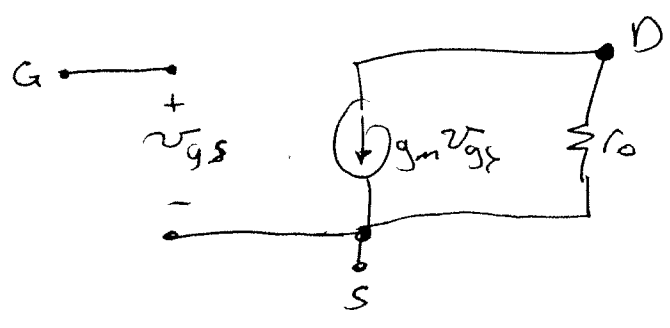

T-model

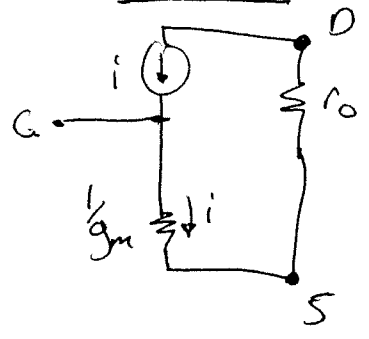

NMOS: $g_m = \frac{\partial I_{D0}}{\partial V_{gs}} = K_{PN} \frac{W}{L} (V_{gs} - V_{TN}) = K_{PN} \frac{W}{L} V_{OD}$


$g_o = \frac{\partial I_{D0}}{\partial V_{ds}} = \lambda_N I_{D0}$

PMOS: $g_m = \frac{\partial I_{S0}}{\partial V_{sg}} = K_{PP} \frac{W}{L} (V_{sg} - |V_{TP}|) = K_{PP} \frac{W}{L} V_{OD}$

$g_o = \frac{\partial I_{S0}}{\partial V_{sd}} = \lambda_P I_{D0}$

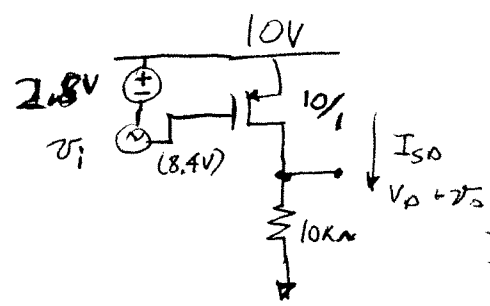Example

$K_P = 30 \mu A/V^2$ $V_{TP} = -1V$ $\lambda = 0.02V^{-1}$



$$I_{SD} = \frac{1}{2} K_P \frac{W}{L} (V_{SG} - |V_{TP}|)^2$$


$$I_{SD} = \frac{1}{2} (30 \mu A/V^2) (10) (2.8 - 1)^2 = 0.486 \text{ mA}$$

$$V_D = 4.86 \text{ V} \Rightarrow V_{SD} = 5.14 \text{ V}$$

$$\geq V_{SG} - |V_{TP}| = 1.8 \text{ V} \quad (sat) \checkmark$$

$$g_m = \frac{\partial I_{SD}}{\partial V_{SG}} = K_P \frac{W}{L} (V_{SG} - |V_{TP}|) = (30 \mu A/V^2) (10) (2.8 - 1) = 540 \mu A/V$$
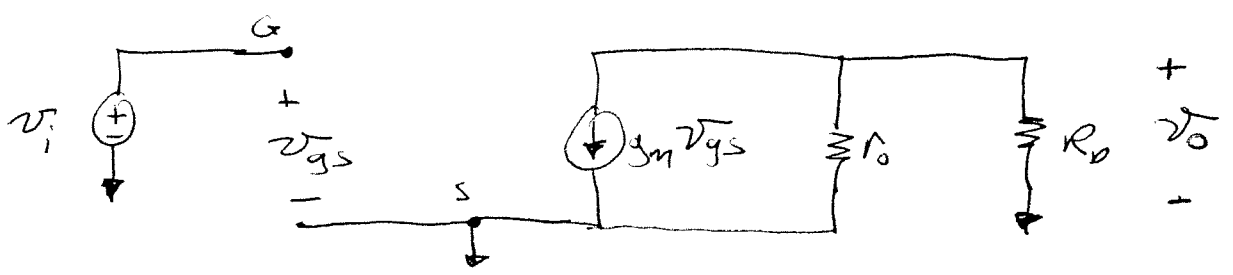
$$g_o = \lambda I_D = 0.02 V^{-1} (0.486 \text{ mA}) = 9.76 \mu A/V \Rightarrow r_o = 103 \text{ k}\Omega$$



$$A_V = -g_m (R_D || r_o) = -540 \mu A/V (10 \text{ k}\Omega || 103 \text{ k}\Omega)$$

$$A_V = -4.92 \text{ V/V}$$