

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 325 – Electronics

Fall 2022

Exam #1

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are **6** pages in your exam
- Good Luck!

Problem	Score	Max Score
1		30
2		25
3		25
4		20
Total		100

Name: SAM PALERMO

UIN: _____

Problem 1 (30 points)

Plot the magnitude and phase response of the following transfer function. Label key points and slopes.

$$H(s) = \frac{(s + 10^4)(s + 10^6)}{10^2 s^2}$$



DC gain = $\frac{10^0}{0} = \infty = \infty \text{ dB}$
 HF gain = $\frac{s^2}{10^2 s^2} = \frac{1}{100} = -40 \text{ dB}$

$z_1 = -10^4 \quad z_2 = -10^6$

$p_1 = p_2 = 0$

LF Phase \Rightarrow 2 DC poles
 $= 2(-90^\circ)$
 $= -180^\circ$

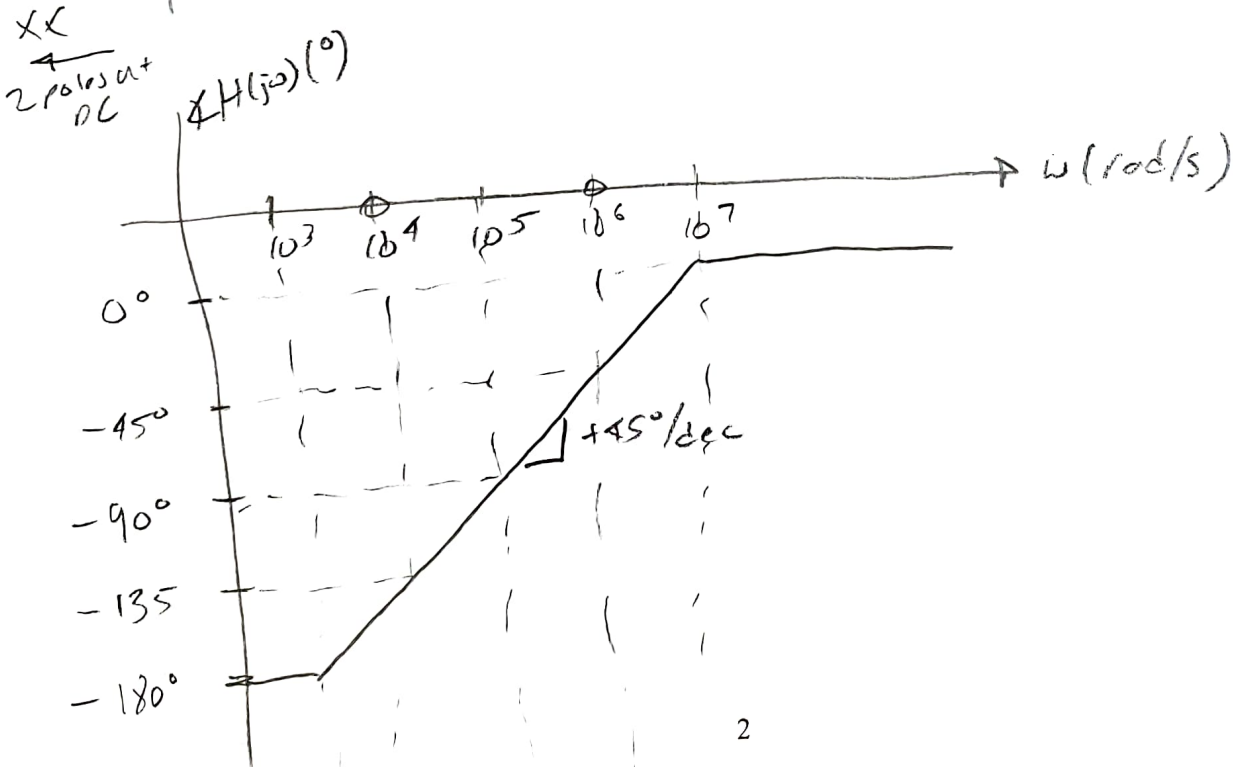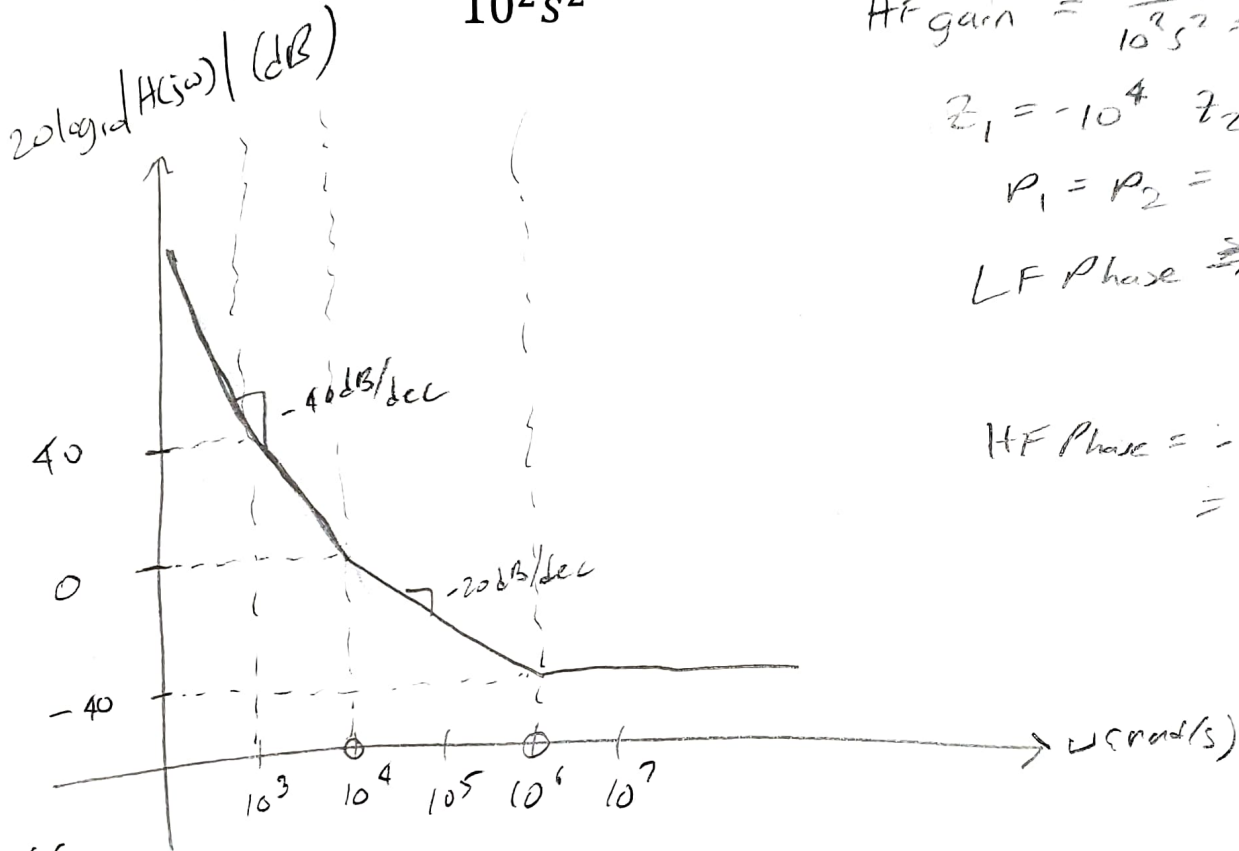HF Phase = $-180^\circ + 2(90^\circ)$
 $= 0^\circ$




Problem 2 (25 points)

Assume for Problem 2 circuits that all operational amplifiers are ideal.

For the following circuit:

- Obtain the transfer function, $v_o(s)/v_i(s)$
- Set the component values to achieve a $1\text{k}\Omega$ high-frequency input resistance, 20dB high-frequency gain (magnitude), and a pole frequency of $|\omega_p| = 10\text{krad/s}$.

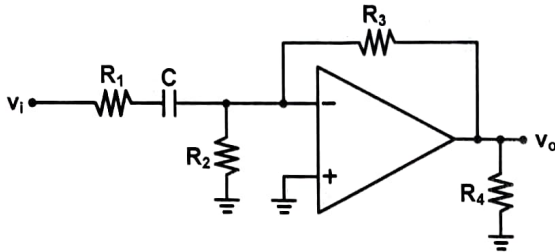

$$\frac{V_o(s)}{V_i(s)} = - \frac{Z_{R3}}{Z_{R1} + Z_C} = - \frac{R_3}{R_1 + \frac{1}{sC}} = \frac{-R_3/R_1 s}{s + \frac{1}{R_1 C}}$$

$$\boxed{\frac{V_o(s)}{V_i(s)} = \frac{-\frac{R_3}{R_1} s}{s + \frac{1}{R_1 C}}}$$

$$\text{HF } R_{in} = R_1 = 1\text{k}\Omega$$

$$|\text{HF Gain}| = \frac{R_3}{R_1} = 10 \Rightarrow R_3 = 10R_1 = 10\text{k}\Omega$$


$$|\omega_p| = \frac{1}{R_1 C} \Rightarrow C = \frac{1}{R_1 |\omega_p|} = \frac{1}{(1\text{k}\Omega)(10\text{k})} = 100\text{nF}$$

$$\boxed{\begin{aligned} R_1 &= 1\text{k}\Omega \\ R_3 &= 10\text{k}\Omega \\ C &= 100\text{nF} \end{aligned}}$$

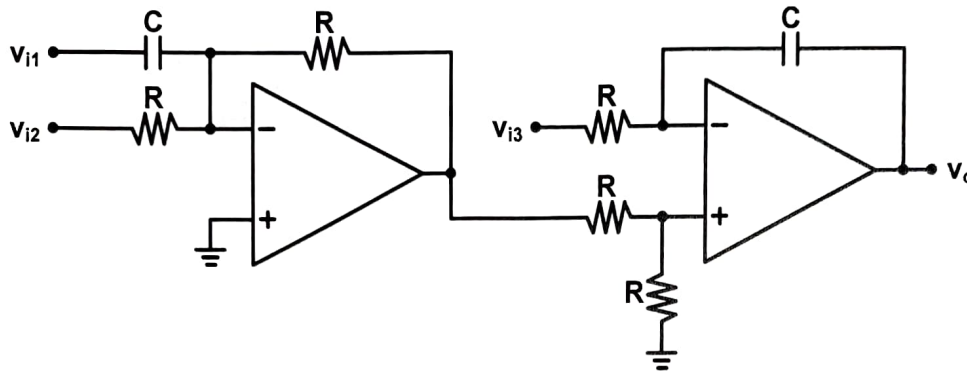Problem 3 (25 points)

Assume for Problem 3 circuits that all operational amplifiers are ideal.

For the following circuit obtain the expression for v_o as a function of v_{i1} , v_{i2} , and v_{i3} . Assume ideal opamps. Hint: apply superposition.



$$V_o = \left(-\frac{z_R}{z_C}\right) \left(\frac{1}{2}\right) \left(1 + \frac{z_C}{z_R}\right) V_{i1} + (-1) \left(\frac{1}{2}\right) \left(1 + \frac{z_C}{z_R}\right) V_{i2} - \frac{z_C}{z_R} V_{i3}$$

$$= \left(-\frac{1}{2}\right) \left(\frac{z_R}{z_C} + 1\right) V_{i1} - \frac{1}{2} \left(1 + \frac{z_C}{z_R}\right) V_{i2} - \frac{z_C}{z_R} V_{i3}$$



$$V_o = -\frac{1}{2} (1 + sRC) V_{i1} - \frac{1}{2} \left(1 + \frac{1}{sRC}\right) V_{i2} - \frac{1}{sRC} V_{i3}$$

Problem 4 (20 points)

The operational amplifier used in the remainder of the problem has the following **open-loop** transfer function

$$A(s) = \frac{10^4}{1 + \frac{s}{10^2}}$$

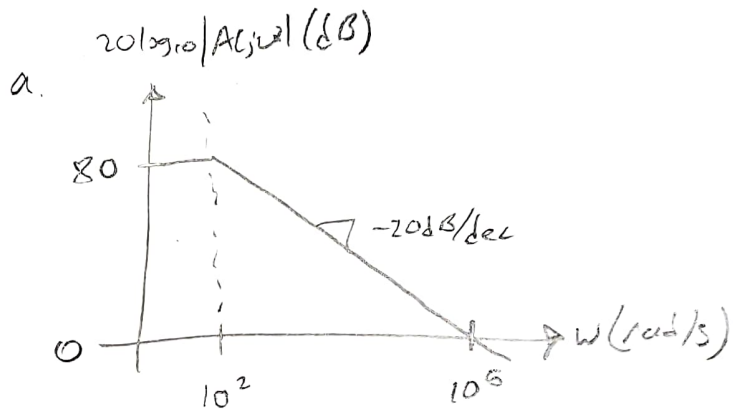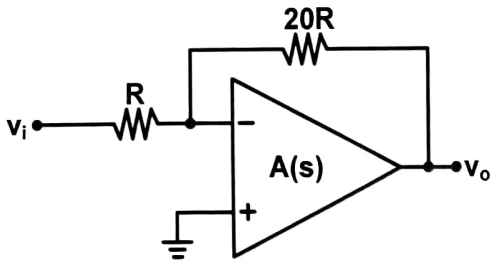- a) Sketch the **open-loop** magnitude response of the operational amplifier. **Make sure to label the unity-gain frequency.**
- b) The finite gain-bandwidth operational amplifier from part (a) is used in the following amplifier circuit. Find the expression for the **closed-loop** transfer function (v_o/v_i).
- c) What is the **closed-loop** -3dB frequency (bandwidth) of the total amplifier circuit?
- d) Sketch the **closed-loop** magnitude response of the amplifier circuit. **Make sure to label the unity-gain frequency.**



b.

$$\frac{V_o(s)}{V_i(s)} = \frac{-20}{1 + \frac{s}{10^6/21}}$$

c.

$$\omega_{CL} = \frac{10^6}{21} \text{ rad/s}$$

