

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 325 – Electronics

Spring 2020

Exam #1

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are **5** pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		30
2		50
3		20
Total		100

Name: SAM PALERMO

UIN: _____

Problem 1 (30 points)

Plot the magnitude and phase response of the following transfer function. Label key points and slopes.

$$F(s) = \frac{10(s + 10^6)(s + 10^9)}{(s + 10^7)(s + 10^8)}$$

$$DC \text{ gain} = \frac{10(10^6)(10^9)}{(10^7)(10^8)} = \frac{10^{16}}{10^{15}} = 10$$



$$\Rightarrow 20 \text{ dB}$$

$$HF \text{ gain} = 10 \Rightarrow 20 \text{ dB}$$

$$z_1 = -10^6, \quad z_2 = -10^9$$

$$p_1 = -10^7, \quad p_2 = -10^8$$

$$LF \text{ Phase} = 0^\circ$$

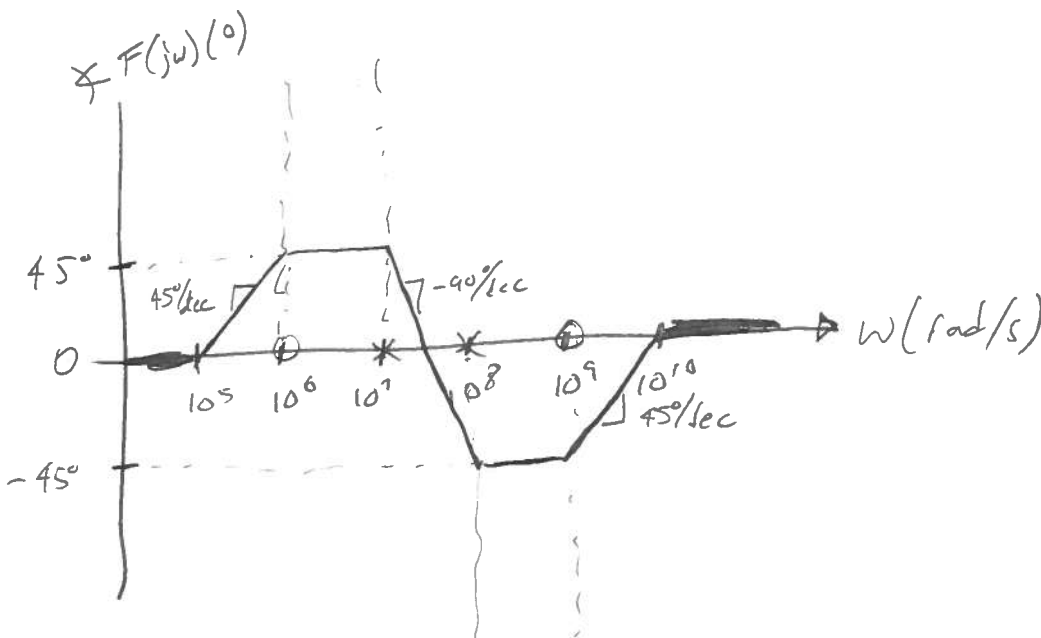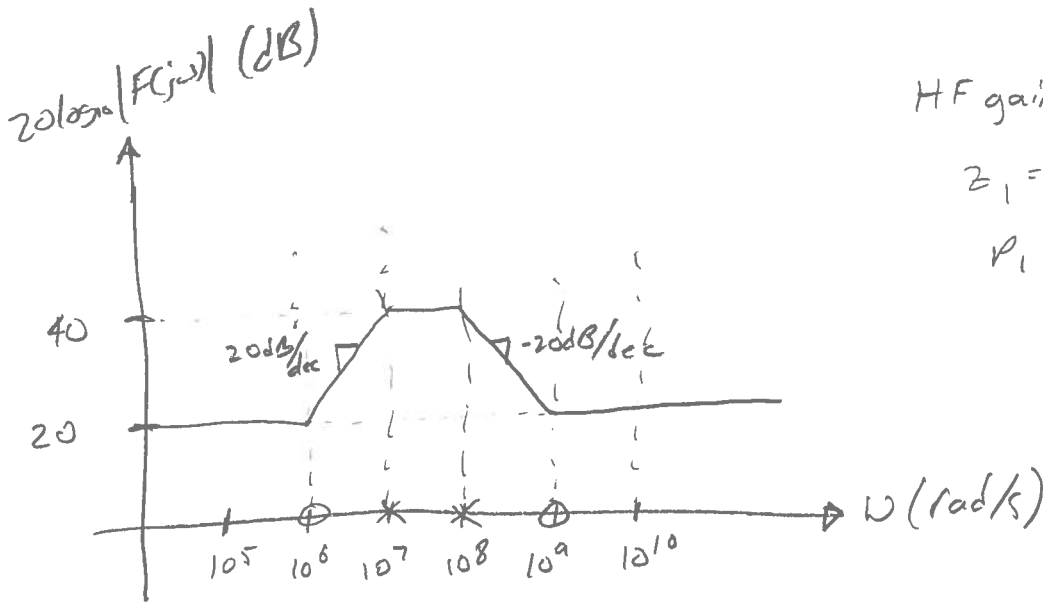


Problem 2 (50 points)

Assume for problem 2 circuits that all operational amplifiers are ideal.

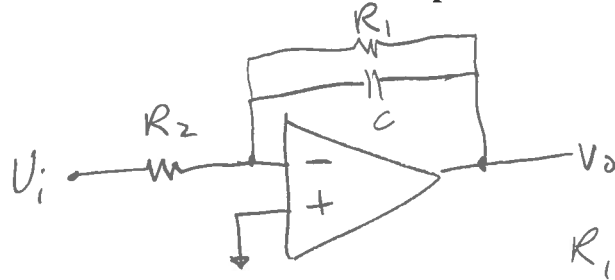a) Design an operational amplifier circuit to implement the following transfer function.

$$\frac{V_o(s)}{V_i(s)} = -\frac{100}{1 + \frac{s}{10^6}}$$

The circuit should have a **100Ω input resistance**. (25 points)



$$R_1 = 10\text{ k}\Omega$$

$$R_2 = 100\ \Omega$$


$$C = 100\ \mu\text{F}$$

$$R_1 C = \frac{1}{10^6}$$

$$\frac{V_o}{V_i} = \frac{-\frac{R_1}{R_2}}{1 + sR_1 C} \quad C = \frac{1}{10^6 R_1} = \frac{1}{10^6 (10\text{ k}\Omega)} = 100\ \mu\text{F}$$

$$R_{in} = R_2 = 100\ \Omega \Rightarrow R_1 = 100 R_2 = 10\text{ k}\Omega$$

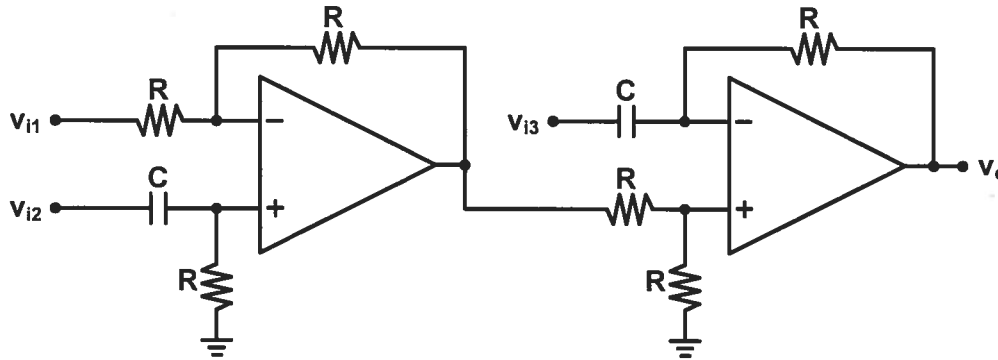b) For the following circuit obtain the expression for v_o as a function of v_{i1} , v_{i2} , and v_{i3} . Assume ideal opamps. Hint: apply superposition. (25 points)



$$V_o = (-1)\left(\frac{1}{2}\right)\left(1 + \frac{ZR}{ZC}\right)V_{i1} + \left(\frac{ZR}{ZC + ZR}\right)(2)\left(\frac{1}{2}\right)\left(1 + \frac{ZR}{ZC}\right)V_{i2} - \frac{ZR}{ZC}V_{i3}$$



$$V_o = -\frac{1}{2}(1 + sRC)V_{i1} + sRCV_{i2} - sRCV_{i3}$$

Problem 3 (20 points)

The operational amplifier used in the remainder of the problem has the following **open-loop** transfer function

$$A(s) = \frac{10^5}{1 + \frac{s}{10}}$$

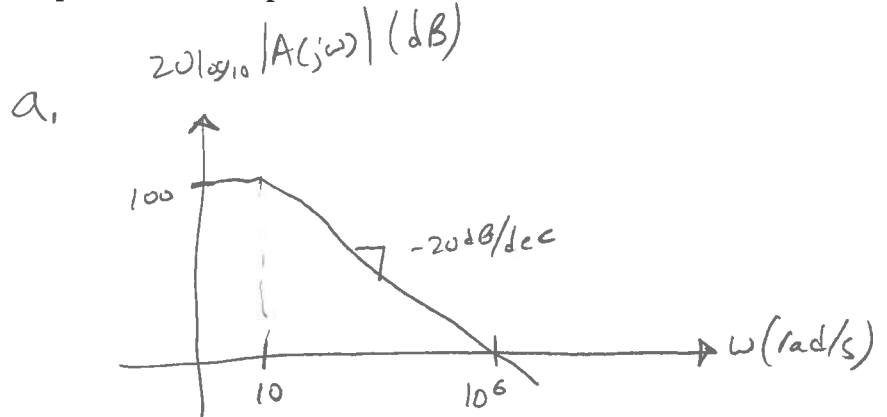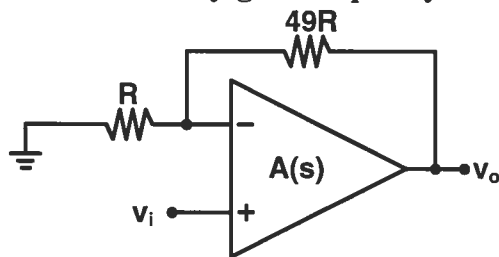
- a) Sketch the **open-loop** magnitude response of the operational amplifier. **Make sure to label the unity-gain frequency.**
- b) The finite gain-bandwidth operational amplifier from part (a) is used in the following amplifier circuit. Find the expression for the **closed-loop** transfer function (v_o/v_i).
- c) What is the **closed-loop** -3dB frequency (bandwidth) of the total amplifier circuit?
- d) Sketch the **closed-loop** magnitude response of the amplifier circuit. **Make sure to label the unity-gain frequency.**



b.

$$\frac{V_o(s)}{V_i(s)} \approx \frac{50}{1 + \frac{s}{10^6/50}}$$

c. $\omega_{cl} = \frac{10^6}{50}$

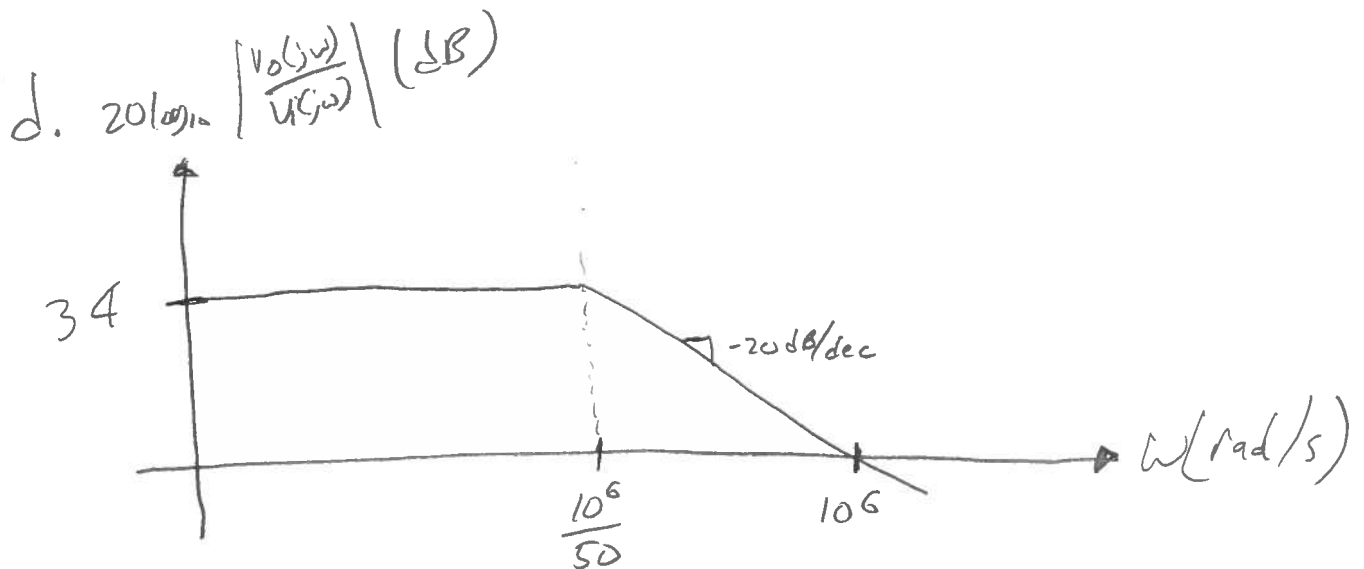

Scratch Paper