

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 325 – Electronics

Spring 2021

Exam #2

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are **5** pages in your exam
- Good Luck!

Problem	Score	Max Score
1		30
2		35
3		35
Total		100


Name: _____ SAM PALERMO _____

UIN: _____

Problem 1 (30 points)

For all the circuits below, use the constant-voltage-drop diode model ($V_D=0.7V$), $V_T=25.9mV$, and $n=1$.

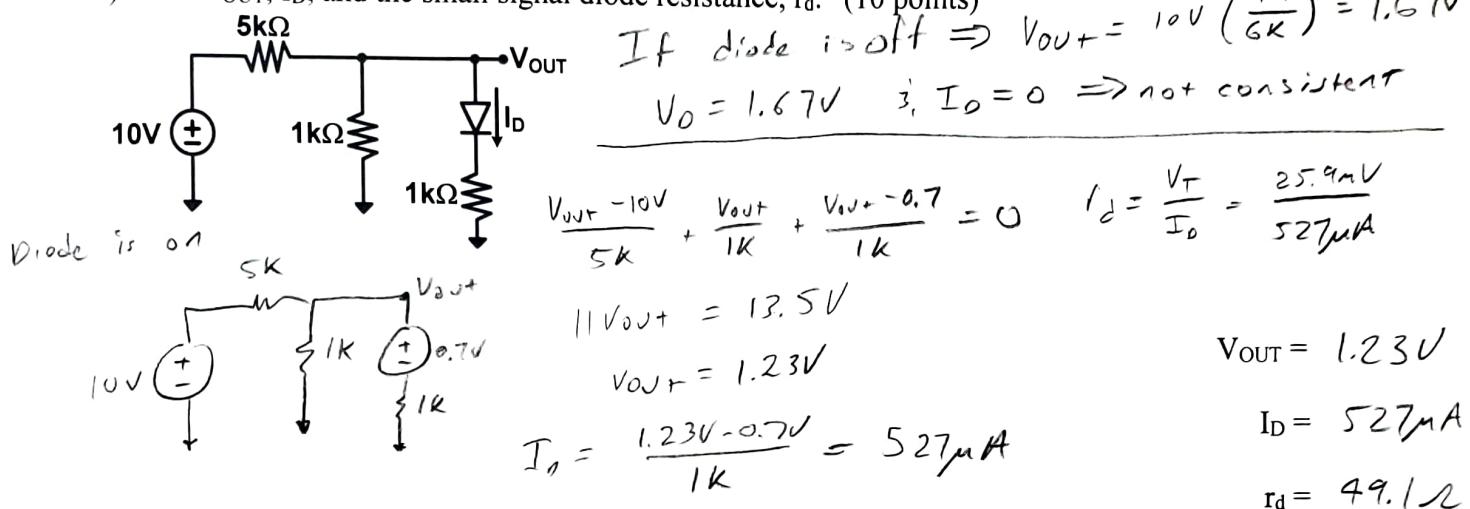
- a) Find V_{OUT} , I_D , and the small signal diode resistance, r_d . (10 points)



Assume for the following circuit that the diode is forward biased and there is a small-signal AC signal, $v_{i,AC}$, in series with a DC voltage.

- b) Derive the small-signal AC transfer function $v_{o,AC}(s)/v_{i,AC}(s)$. (10 points)

- c) Assume that $R_s=1k\Omega$, $C=1\mu F$. Calculate the value of I_D and V_S necessary to set the magnitude of the pole frequency of the AC transfer function, $|\omega_p|$, equal to 10krad/s. (10 points)

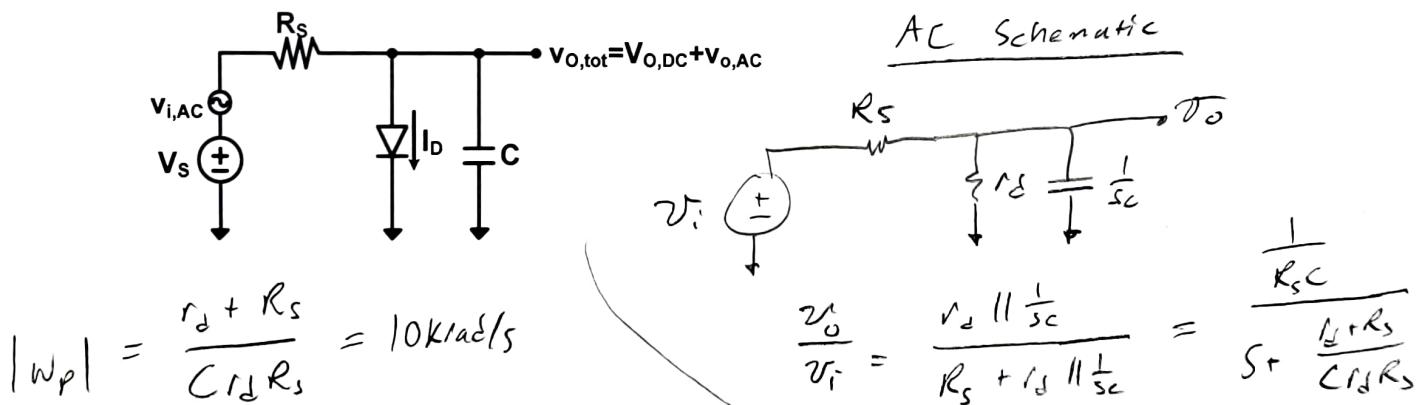

$$\frac{r_d + 1k}{(1\mu F)r_d(1k)} = 10k$$

$$r_d + 1k = 10r_d$$

$$r_d = 111\Omega$$

$$I_D = \frac{V_T}{r_d} = \frac{25.9mV}{111\Omega} = 233\mu A$$

$$\frac{V_S - 0.7V}{1k} = 233\mu A$$

$$V_S = 0.933V$$

$$I_D = 233\mu A$$

$$V_S = 0.933V$$

AC Transfer Function:


$$\frac{1}{R_s C}$$

$$\frac{1}{s + \frac{r_d + R_s}{C r_d R_s}}$$

Problem 2 (35 points)

Assume for Problem 2 that the transistor $\beta=150$, $V_{BE}=0.7V$, and $V_{th}=25.9mV$.

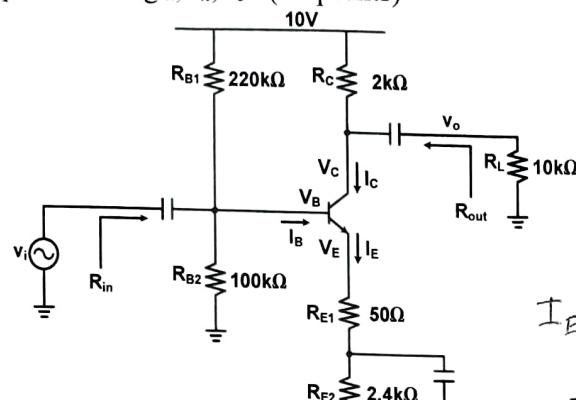- a) Calculate the DC values for V_C , V_B , V_E , I_C , I_B , and I_E . Compute the AC small signal parameters g_m , r_π , r_e . (18 points)




$$V_C = 10V - 2k(829\mu A) = 8.34V$$

$$V_E = 835\mu A(2.45k) = 2.05V$$

$$V_B = 2.75V$$

$$g_m = \frac{I_c}{V_T} = \frac{829\mu A}{25.9mV} = 32mA/V$$
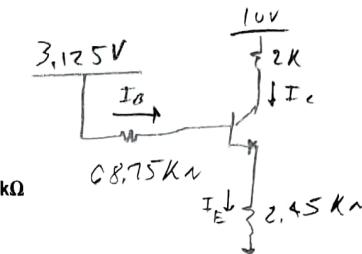
$$r_\pi = \frac{V_T}{I_B} = \frac{25.9mV}{5.5\mu A} = 4.71k\Omega$$



$$I_E = \frac{3.125V - 0.7V}{2.45k + 68.75k} = 835\mu A$$

$$I_B = \frac{I_E}{\beta+1} = 5.5\mu A, I_c = I_E \left(\frac{\beta}{\beta+1}\right) = 829\mu A$$

$$I_C = 829\mu A$$

$$I_B = 5.5\mu A$$

$$I_E = 835\mu A$$

$$V_C = 8.34V$$

$$V_B = 2.75V$$

$$V_E = 2.05V$$


$$g_m = 32mA/V$$

$$r_\pi = 4.71k\Omega$$


$$r_e = 31\Omega$$

- b) Sketch the small-signal model of the circuit. Assume that the capacitors act as AC shorts and that the transistor's r_o is infinite. Only ONE version of the model (π or T) is required (11 points)

w/T-model

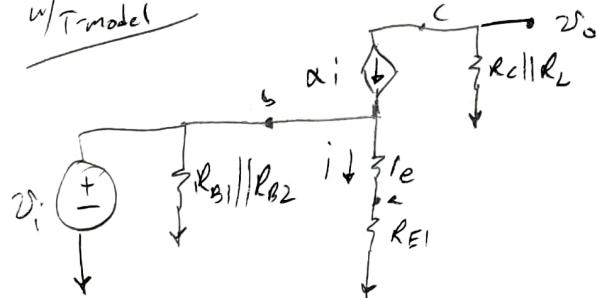

w/π-model

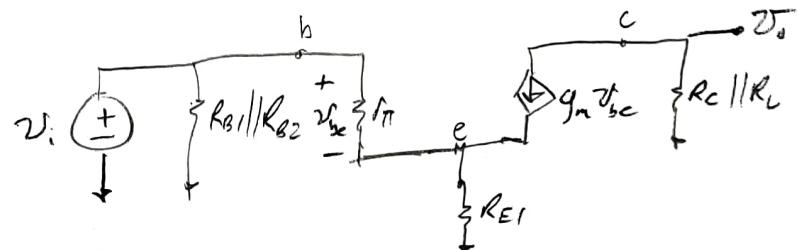

- c) Calculate the small signal gain $A_v = v_o/v_i$, the input resistance R_{in} , the output resistance R_{out} . (6 points)

$$A_v = \frac{-g_m (R_c || R_L)}{1 + \frac{g_m R_{E1}}{\alpha}} = - \frac{(32mA/V)(2k || 10k)}{1 + \frac{32mA/V(50)}{0.993}} = -20.4V/V$$

$$A_v = -20.4V/V$$

$$R_{in} = R_B || [r_\pi + (\beta+1)R_{E1}] = 68.75k || [4.71k + 151(50)] = 10.4k$$

$$R_{in} = 10.4k\Omega$$


$$R_{out} = 2k\Omega$$

$$R_{out} = R_L = 2k$$

Problem 3 (35 points)

Assume for Problem 3 that the transistor $\beta=150$, $V_{BE}=0.7V$, and $V_{th}=25.9mV$.

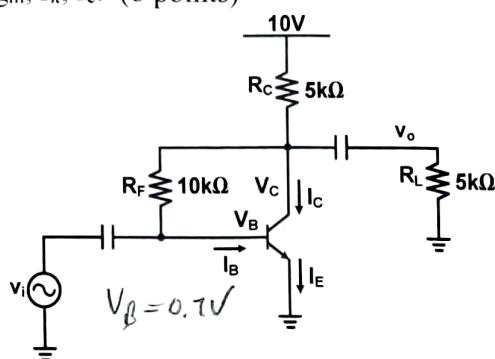- a) Calculate the DC values for V_C , V_B , I_C , I_B , and I_E . Compute the AC small signal parameters g_m , r_π , r_e . (8 points)



$$I_F = I_B + I_C = \frac{10V - 0.822V}{5k} = 1.84mA$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{1.94mA}{151} = 12.2\mu A, \quad I_C = \beta I_B = 1.82mA \quad I_{IT} = \frac{V_T}{I_B} = \frac{25.9mV}{12.2\mu A}$$

$$I_m = \frac{I_c}{V_T} = \frac{1.82mA}{25.9mV} = 70.4mA/V$$

Assume that the capacitors act as

b) Sketch the small-signal model of the circuit. Assume that the capacitors act as AC shorts and that the transistor's r_o is infinite. Only **ONE** version of the model (π or T) is required (15 points)

c) Using the small-signal model in (b), derive an expression for the small signal gain $A_v = v_o/v_i$ in terms of R_F , R_C , R_L and the transistor small signal parameters (variables only, no numbers). Then compute A_v with the parameters from part (a). (12 points)

Using Π mode!

$$KCL @ 25_0: \frac{V_o - V_i}{R_E} + g_m V_i + \frac{V_o}{R_o || R_L} = 0$$

$$V_o \left[\frac{1}{R_F} + \frac{1}{R_c || R_L} \right] = -V_i \left[g_m - \frac{1}{R_F} \right]$$

$$A_v \text{ Expression: } \frac{V_o}{V_i} = - \left[g_m - \frac{1}{R_F} \right] (R_F || R_C || R_L)$$

$$A_v = -141 \text{ V/V}$$

$$= - \left[70.4_m - \frac{1}{10k} \right] (10k || 5k || 5k) = - 141\%$$