

**Texas A&M University
Department of Electrical and Computer Engineering**

ECEN 325 – Electronics

Spring 2024

Exam #2

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 5 pages in your exam
- Good Luck!

Problem	Score	Max Score
1		10
2		20
3		35
4		35
Total		100


Name: SAM PALERMO

UIN: _____

Problem 1 (10 points)

For all the circuits below, use the constant-voltage-drop diode model ($V_D=0.7V$), $V_{th}=25.9mV$, and $n=1$.

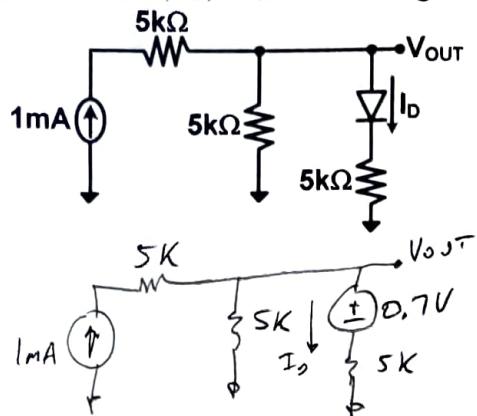- a) Find V_{OUT} , I_D , and the small signal diode resistance, r_d . (10 points)



If diode is OFF $\Rightarrow V_{OUT} = 5V = V_D \Rightarrow$ inconsistent

Diode is ON

KCL @ V_{OUT}

$$-1mA + \frac{V_{OUT}}{5k\Omega} + \frac{V_{OUT} - 0.7V}{5k\Omega} = 0$$

$$2V_{OUT} = 5.7V$$

$$V_{OUT} = 2.85V$$


$$I_D = \frac{2.85V - 0.7V}{5k\Omega} = 430\mu A$$

$$r_d = \frac{25.9mV}{430\mu A} = 60.2\Omega$$

Problem 2 (20 points)

The following circuit has a small-signal AC signal, $v_{i,AC}$, in series with a DC voltage.

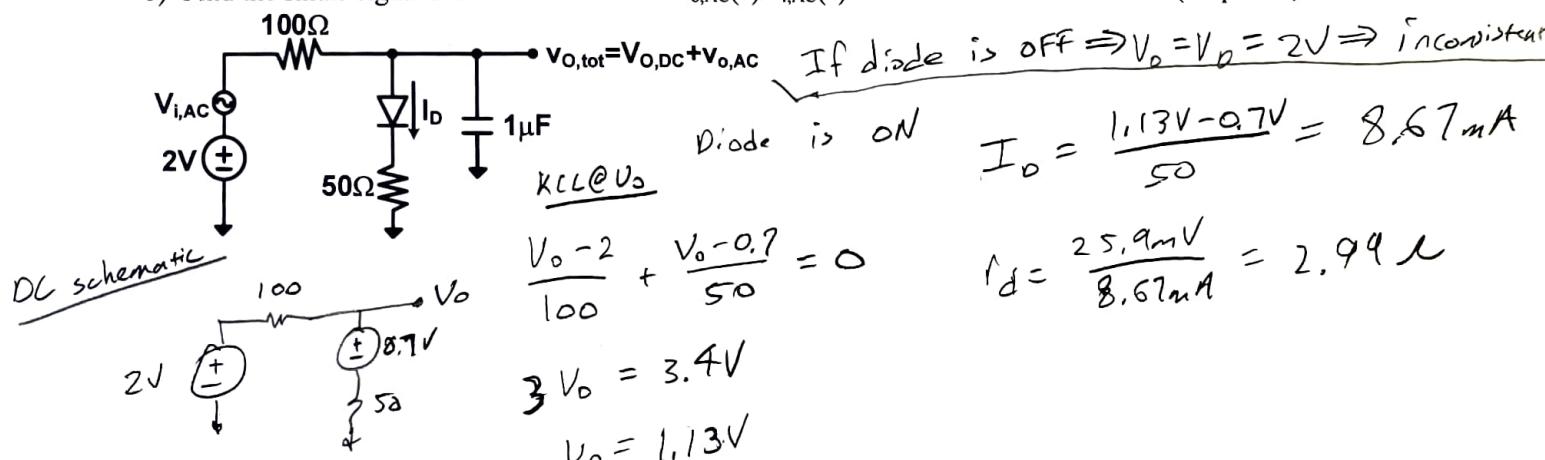- a) Find the DC output voltage, $V_{O,DC}$, DC diode current I_D , and small-signal diode r_d (10 points)
- b) Find the small-signal AC transfer function $v_{o,AC}(s)/v_{i,AC}(s)$ (10 points)



AC Transfer Function:

$$\frac{V_o}{V_i} = \frac{\frac{Z_C}{R_1 + Z_C} \parallel [r_d + R_2]}{R_1 + r_d + R_2}$$

$$= \frac{r_d + R_2}{R_1 + r_d + R_2}$$

$$= \frac{1}{1 + sC[R_1 \parallel (r_d + R_2)]}$$



$$= \frac{0.346}{1 + s(3.46 \times 10^{-5})}$$

$$= \frac{\frac{2.99 + 50}{100 + 2.99 + 50}}{1 + s(1\mu F)(100 \parallel (2.99 + 50))}$$

Problem 3 (35 points)

Assume for Problem 3 that the transistor $\beta=150$, $V_{BE}=0.7V$, and $V_T=25.9mV$.

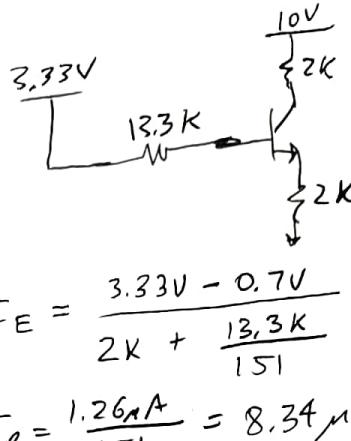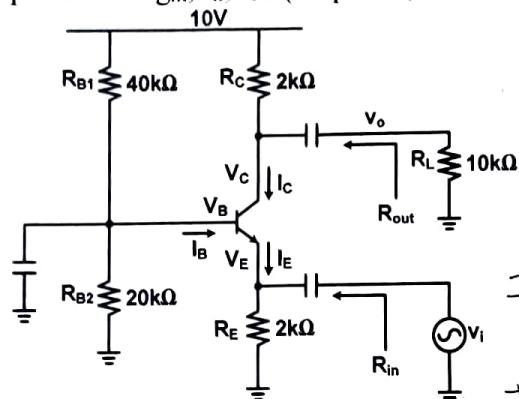- a) Calculate the DC values for V_C , V_B , V_E , I_C , I_B , and I_E . Compute the AC small signal parameters g_m , r_π , r_e . (18 points)



$$V_E = 1.26mA (2k) = 2.52V$$

$$V_B = 2.52V + 0.7V = 3.22V$$

$$V_C = 10V - 1.25mA (2k) = 7.5V$$

$$r_\pi = \frac{25.9mV}{8.34\mu A} = 3.11k\Omega$$

$$I_E = \frac{3.33V - 0.7V}{2k + \frac{13.3k}{151}} = 1.26mA$$

$$I_B = \frac{1.26mA}{151} = 8.34\mu A$$



$$I_C = 8.34\mu A (150) = 1.25mA$$

$$g_m = \frac{1.25mA}{25.9mV} = 48.3 mA/V$$

$$r_e = \frac{25.9mV}{1.26mA} = 20.6\Omega$$

- b) Sketch the small-signal model of the circuit. Assume that the capacitors act as AC shorts and that the transistor's r_0 is infinite. Only ONE version of the model (π or T) is required (11 points)

w/T-model

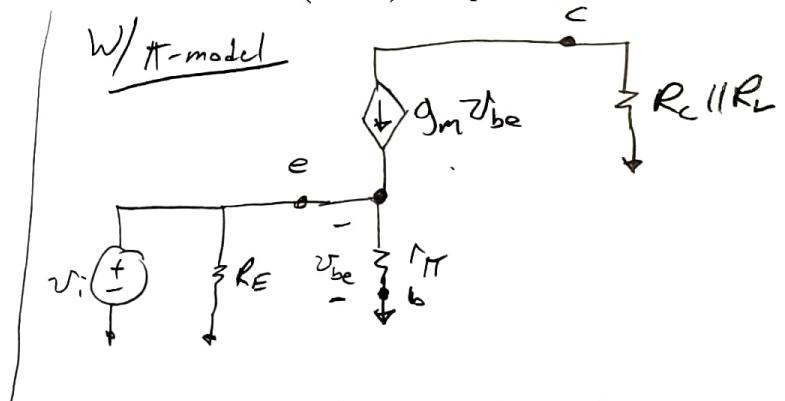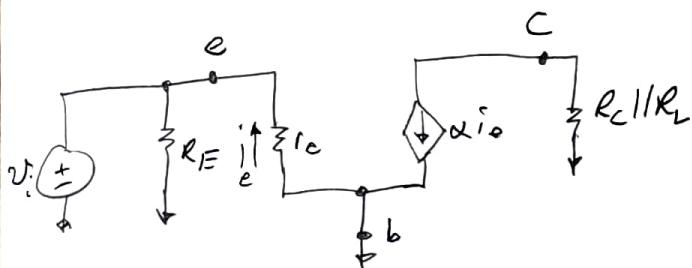

- c) Calculate the small signal gain $A_v = v_o/v_i$, the input resistance R_{in} , the output resistance R_{out} . (6 points)

$$A_v = g_m (R_C || R_L) = 48.3 mA/V (2k || 10k) = 80.5 V/V$$

$$R_{in} = R_E // r_e = 2k // 20.6 = 20.4 \Omega$$

$$R_{out} = R_C = 2k$$


$$A_v = 80.5 V/V$$

$$R_{in} = 20.4 \Omega$$

$$R_{out} = 2k$$

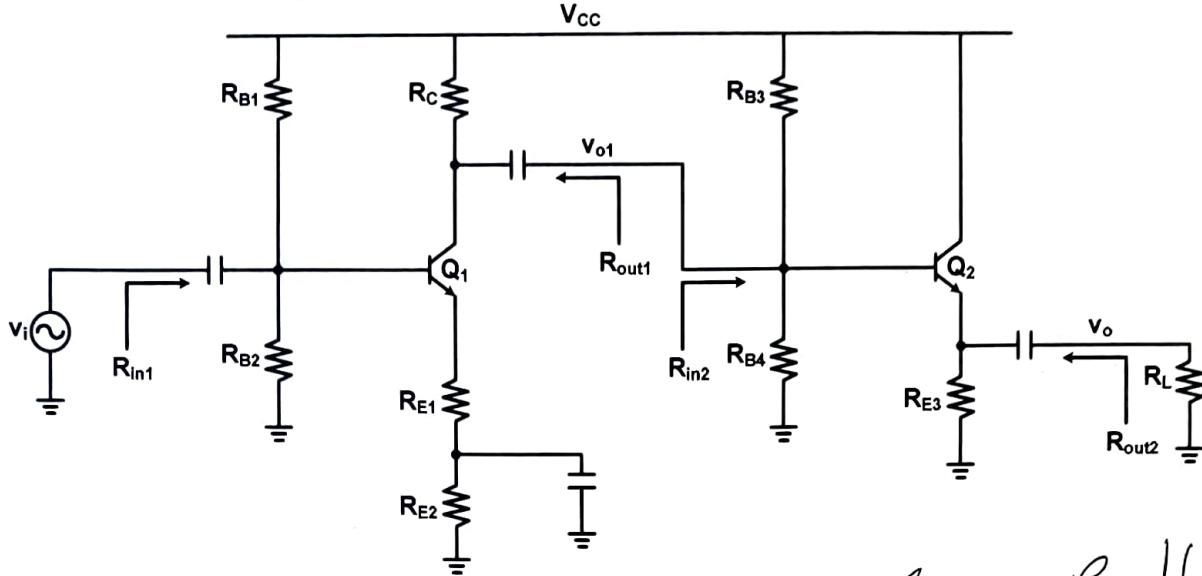Problem 4 (35 points)

Assume for Problem 4 that **the transistors are operating in active mode** and that the capacitors act as AC shorts and that the transistors' r_o is infinite (can be neglected). For the 2-stage amplifier below, give expressions for the small signal parameters requested below.



$$\text{where } R_{B12} = R_{B1} \parallel R_{B2}$$

$$R_{in1} = R_{B12} \parallel [r_{\pi1} + (\beta+1)R_{E1}]$$

$$R_{B34} = R_{B3} \parallel R_{B4}$$

$$R_{out1} = R_C$$

$$R_{in2} = R_{B34} \parallel [r_{\pi2} + (\beta+1)(R_{E3} \parallel R_L)]$$

$$R_{out2} = R_{E3} \parallel [r_{e3} + \frac{R_C \parallel R_{B34}}{\beta+1}]$$

$$A_{v1} = v_{o1}/v_i = \frac{-g_m1 (R_C \parallel R_{in2})}{1 + \frac{g_m1 R_{E1}}{\alpha}} = \frac{-\alpha (R_C \parallel R_{in2})}{r_{e1} + R_{E1}}$$

$$A_{v2} = v_o/v_{o1} = \frac{R_{E3} \parallel R_L}{r_{e2} + R_{E3} \parallel R_L}$$

$$\text{Total } A_v = v_o/v_i =$$

$$A_{v1} \cdot A_{v2}$$