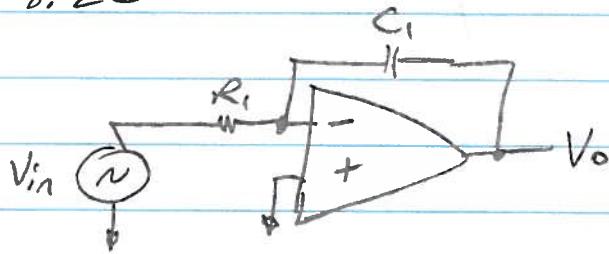


(19) From eq (8.31),

$$\begin{aligned}V_{out} &= -\frac{1}{R, C,} \int V_{in} dt \\&= -\frac{1}{R, C,} \int V_0 \sin \omega t dt \\&= \frac{V_0}{R, C, \omega} \cos \omega t\end{aligned}$$

$$\therefore \text{Amplitude of output} = \frac{V_0}{R, C, \omega} //$$

8.20



$$\frac{V_o(s)}{V_{in}(s)} = -\frac{1}{sR_iC_1}$$

$$\left| \frac{V_o(j\omega)}{V_{in}(j\omega)} \right| = \frac{1}{\omega R_i C_1} = 10$$

$$\omega = \frac{1}{10R_iC_1} = \frac{1}{10(10\text{ns})} = 10\text{M rad/s}$$

$$\boxed{\omega = 10\text{M rad/s} = 1.59\text{MHz}}$$

(24) $\because A_0 = \infty$

$$|A_v| = \frac{R_i}{\frac{1}{\omega C_i}}$$

$$= \omega R_i C_i$$


$$= 5$$

$$\therefore R_i C_i = \frac{5}{\omega}$$

$$= \frac{5}{2\pi \times 10^6}$$

$$= 7.958 \times 10^{-7}$$

(48)

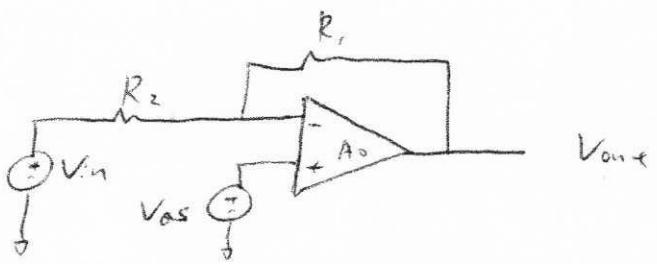

By KCL,

$$\frac{V_{in} - V_{os}}{R_2} = - \frac{V_{out} - V_{os}}{R_1}$$

$$V_{out} = - \frac{R_1}{R_2} (V_{in} - V_{os}) + V_{os}$$

(49)

In Fig. (8.25),

Assuming input is zero.

$$V_x = 10 \times V_{os,A_1}$$


$$= 30 \text{ mV}$$

$$\therefore V_{out} = 10 \times (V_{os,A_2} + V_x)$$

$$= 330 \text{ mV}$$

Thus, the maximum offset error is 330 mV.

8.55

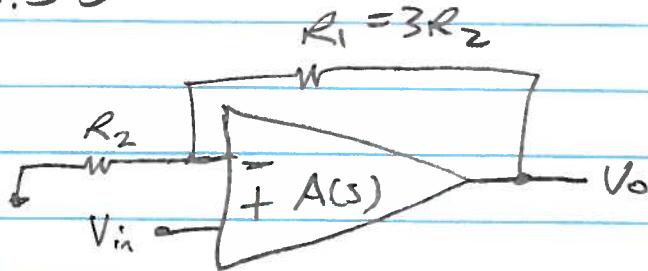

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_p}}$$

$$\frac{V_o}{V_{in}} = \frac{1 + \frac{R_1}{R_2}}{\frac{s}{\omega_p} \left(\frac{1 + \frac{R_1}{R_2}}{A_0} \right) + 1 + \frac{R_1}{R_2}} \underset{\text{W/ high } A_0}{\approx} \frac{1 + \frac{R_1}{R_2}}{1 + \frac{s}{\omega_{PNI}}}$$

$$\text{where } \omega_{PNI} = \frac{\omega_p}{1 + \frac{R_1}{R_2}}$$

$$\text{a. } A_0 = 1000, f_i = 50 \text{ Hz} \Rightarrow \omega_{PNI} = \frac{2\pi(50 \text{ Hz})}{4} = 2\pi(12.5 \text{ kHz})$$

Find Magnitude Response at $\omega = 2\pi(100 \text{ MHz})$

$$\left| \frac{V_o(j2\pi100M)}{V_{in}(j2\pi100M)} \right| \underset{\omega = 2\pi(100M)}{\approx} \frac{4}{\sqrt{1 + \left(\frac{2\pi(100M)}{2\pi(12.5M)} \right)^2}} = 5 \times 10^{-4}$$

\Rightarrow This is much less than 4 !!


$$\text{b. } A_0 = 500, f_i = 1 \text{ MHz} \Rightarrow \omega_{PNI} = \frac{2\pi(500 \text{ Hz})}{4} = 2\pi(125 \text{ MHz})$$

$$\left| \frac{V_o(j2\pi100M)}{V_{in}(j2\pi100M)} \right| \underset{\omega = 2\pi(100M)}{\approx} \frac{4}{\sqrt{1 + \left(\frac{2\pi(100M)}{2\pi(125M)} \right)^2}} = 3.12 \Rightarrow \text{Much closer to ideal gain of 4}$$

We should use OpAmp (b) with

$$A_0 = 500, f_i = 1 \text{ MHz} \Rightarrow f_u = 500 \text{ MHz}$$

8.56

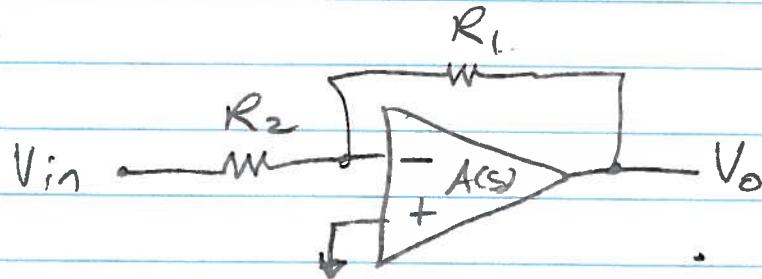

$$\text{Open-Loop OpAmp: } A(s) = \frac{A_0}{1 + \frac{s}{\omega_1}}$$

Closed-Loop Amplifier Transfer Function

$$\frac{V_o}{V_{in}} = \frac{-\frac{R_1}{R_2}}{1 + \frac{1 + \frac{R_1}{R_2}}{A(s)}} = \frac{-\frac{R_1}{R_2}}{1 + \frac{1 + \frac{R_1}{R_2}}{A_0} \left(1 + \frac{s}{\omega_1}\right)}$$

$$\frac{V_o}{V_{in}} = \frac{-\frac{R_1}{R_2}}{\frac{s}{\omega_1} \left(\frac{1 + \frac{R_1}{R_2}}{A_0}\right) + 1 + \frac{1 + \frac{R_1}{R_2}}{A_0}}$$


The bandwidth of the closed-loop amplifier is equal to the pole frequency.

$$|w_{PI, \text{closed}}| = \left(1 + \frac{A_0}{1 + \frac{R_1}{R_2}}\right) \omega_1 \underset{\text{if } A_0 \text{ is very large}}{\approx} \frac{A_0 \omega_1}{1 + \frac{R_1}{R_2}}$$

59

Nominal gain = 4
Slew Rate = 1V/ns

$$V_p = 0.5 \text{ V}$$

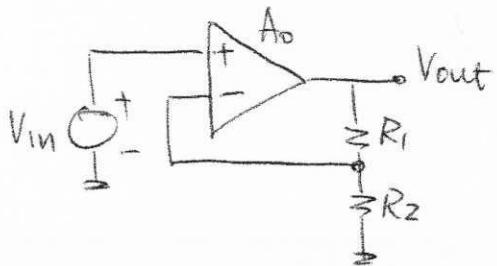

$$= 4$$

$$V_{in}(t) = 0.5 \sin \omega t \Rightarrow V_{out} = 0.5 \times \left(1 + \frac{R_1}{R_2}\right) \sin \omega t.$$

$$\frac{dV_{out}}{dt} = 0.5 \left(1 + \frac{R_1}{R_2}\right) \omega \cos \omega t.$$

= Maximum when $\cos \omega t = 1$

$$\Rightarrow \frac{dV_{out}}{dt} \Big|_{\max} = 0.5 \omega \left(1 + \frac{R_1}{R_2}\right) = 2 \omega$$

\therefore Highest frequency $\Rightarrow 2\omega = 1 \text{ V/ns}$

$$\Rightarrow \omega = 0.5 \text{ rad/ns} \Rightarrow f_{\max} \approx 79.6 \text{ MHz}$$