


ECEN 325
Homework #4

Due: March 21, 2024, 11:59PM


Homeworks will not be received after due.

Instructor: Sam Palermo

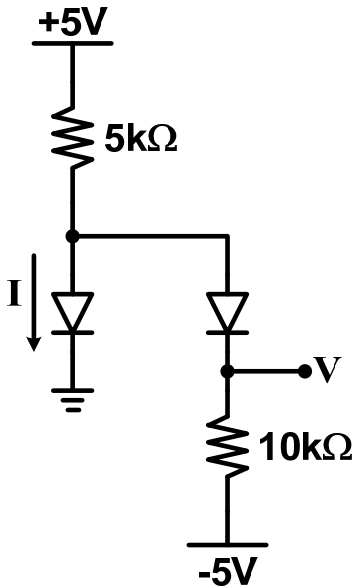1. (20 points) For the 2 following circuits solve for the labeled current I and voltage V . Use the constant-voltage-drop diode model ($V_D=0.7V$).




(a)

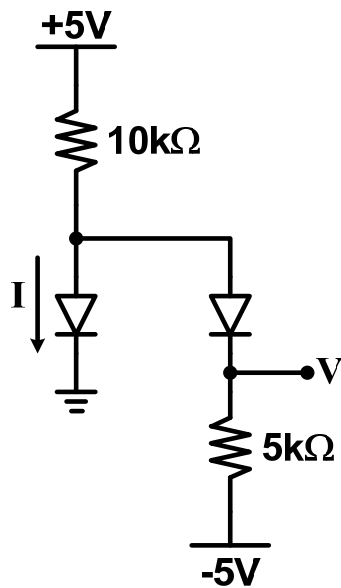


(b)

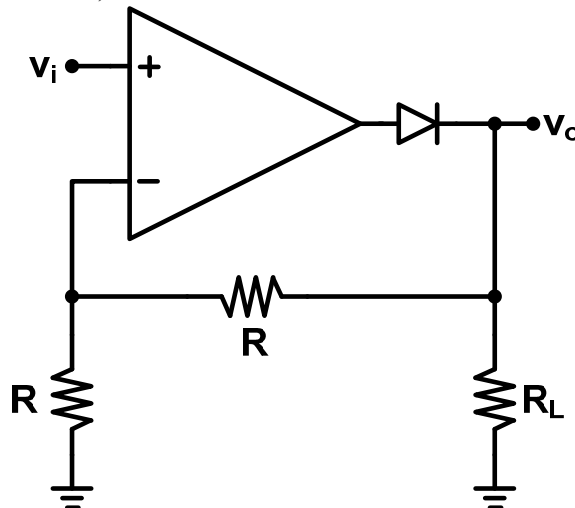2. (20 points) In the following circuit, the op-amp is ideal except that the op-amp output saturates at $\pm 6V$. Sketch the circuit's transfer characteristic, v_o vs v_i , for v_i ranging from $\pm 10V$. Use the constant-voltage-drop diode model ($V_D=0.7V$).



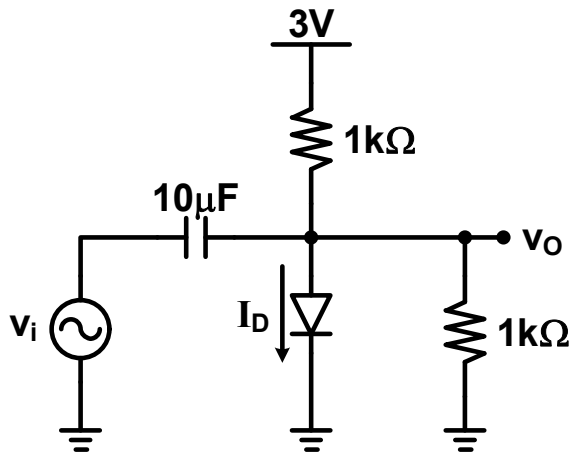3. (20 points) For the circuit below:

- Find the DC diode current (I_D) and the DC output voltage (V_O).
- Find the small-signal AC transfer function $v_o(s)/v_i(s)$. Assume $n=1$ for the diode.
- Find the total output voltage $v_{O,total}$ for $v_i(t)=0.001 \sin(2\pi \cdot 10^5 t)$.




4. (40 points) Design an AC adapter with the following specifications using a single-ended transformer. Choose an appropriate rectifier to minimize the capacitance.

Input voltage: $120V_{rms}, 60Hz$
 Output voltage: $5V$
 Maximum ripple: 5%
 Load current range: $0-500mA$

Determine the minimum specs for the diode (I_P , reverse breakdown voltage), primary/secondary ratio (N_P/N_S) of the transformer, and the load resistor and capacitor value.

Recall for a sinusoidal signal: $V_{rms} = \frac{V_P}{\sqrt{2}}$

Also, for a transformer

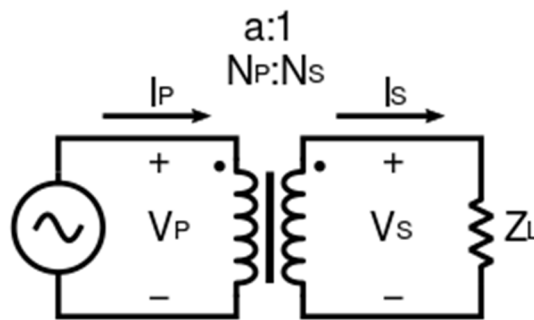

$$\frac{V_P}{V_S} = \frac{I_S}{I_P} = \frac{N_P}{N_S}$$

[Wikipedia]