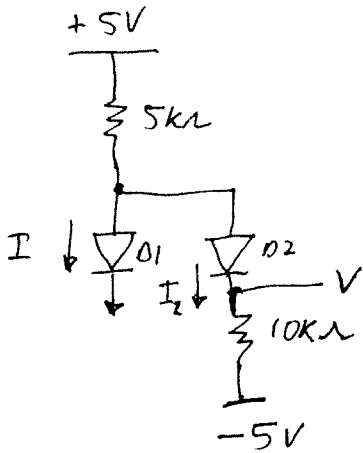


1. a.




Case $\emptyset\emptyset \Rightarrow D1 \nmid D2$ "OFF"

$V_{D1} = 5V, V_{D2} = 10V$

$I = 0A \quad I_2 = 0A$

\Rightarrow Not consistent w/ diode model

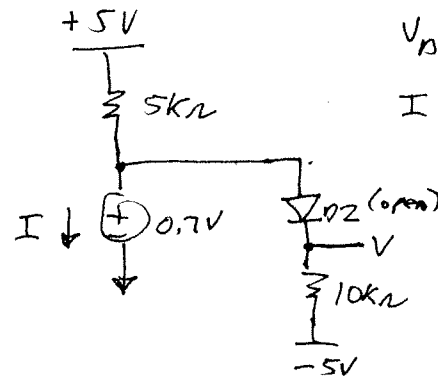Case $\emptyset 1 \Rightarrow D1$ "ON" $\nmid D2$ "OFF"



$V_{D1} = 0.7V$


$I = \frac{5-0.7}{5k} = 0.86mA$

$V_{D2} = 5.7V$

$I_2 = 0$

D2 not consistent w/ diode model

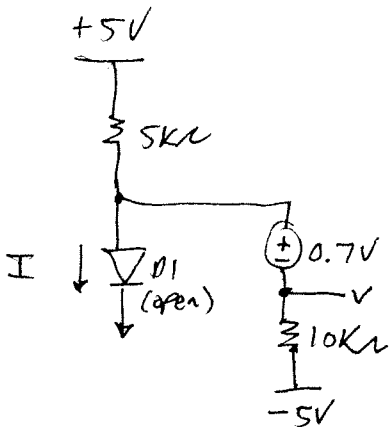Case $1\emptyset \Rightarrow D1$ "OFF" $\nmid D2$ "ON"



$\frac{V+0.7-5}{5k} + \frac{V+5}{10k} = 0 \Rightarrow V = 1.2V$

$V_{D1} = 1.9V$


$V_{D2} = 0.7V$

$I = 0A$

$I = 0.82mA$

D1 not consistent w/ diode model

Case II $\Rightarrow D1 \nmid D2$ "ON"

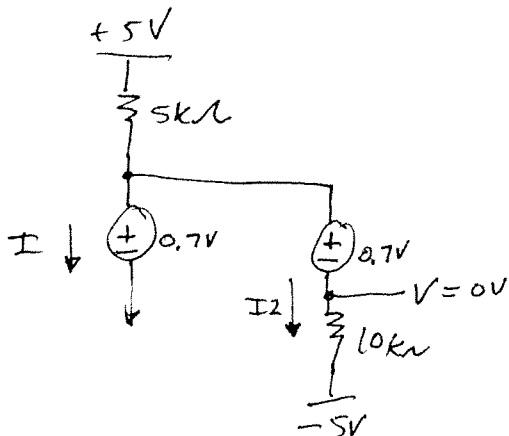

$V_{D1} = V_{D2} = 0.7V$

$I = 0.36mA$
 $V = 0V$


~~$\frac{0.7-5}{5k} + I + \frac{0+5}{10k} = 0$~~

$I = 0.36mA$

$I_2 = 0.5mA$

\Rightarrow Both consistent w/ diode model (Done)

1. b.

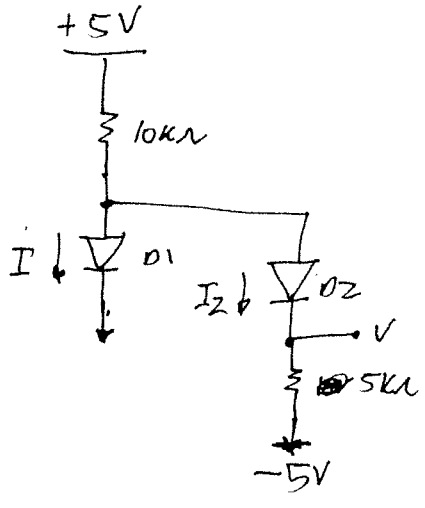


Case $\phi\phi \Rightarrow D1 \text{ \&D2 "OFF"}$

$V_{D1} = 5V, V_{D2} = 10V$

$I = 0A, I_2 = 0A$

\Rightarrow Both not consistent w/ diode model

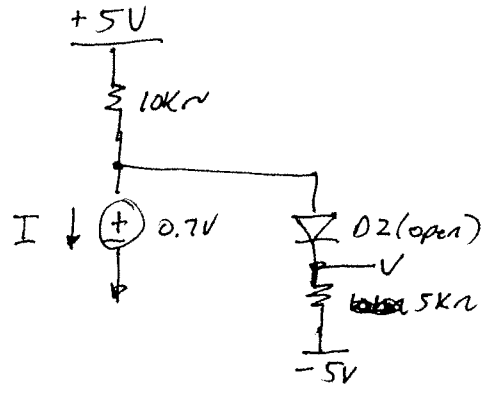Case $\phi 1 \Rightarrow D1 \text{ "ON" \&D2 "OFF"}$



$V_{D1} = 0.7V$


$I = \frac{5-0.7}{10k} = 0.43mA$

$V_{D2} = 5.7V$

$I_2 = 0$

$D2$ not consistent w/ diode model

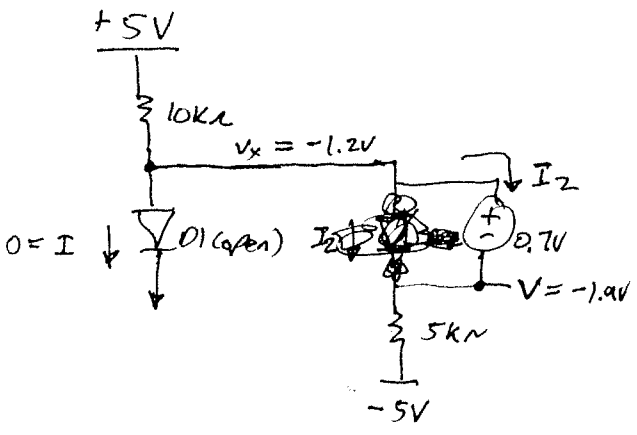Case $1\phi \Rightarrow D1 \text{ "OFF" \&D2 "ON"}$



$\frac{V+0.7-5}{10k} + \frac{V+5}{5k} = 0 \Rightarrow V = -1.9V$

$I_2 = \frac{5+1.9}{10k} = \cancel{0.69mA} 0.62mA$

$V_{D1} = -1.2V, V_{D2} = 0.7V$


$I = 0, I_2 = 0.62mA$

\Rightarrow Both consistent w/ diode model (Done)

No need to compute Case II

$I = \phi mA$
 $V = -1.9V$

2.

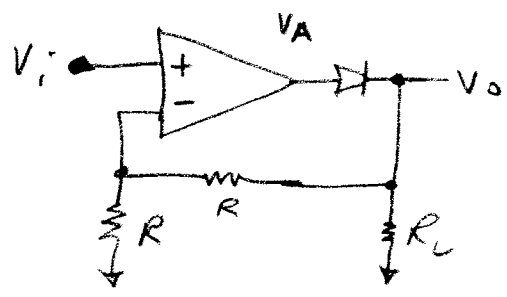


w/o diode


$$V_o = \left(1 + \frac{R}{R}\right) V_i = 2V_i$$

* If $V_i < 0V$, normal non-inverting amp would force a negative V_o , which implies current flowing into the opamp. However, the diode blocks this current and the opamp is in "open-loop" with V_A saturating at $-6V$ and $V_o = 0V$.


* If $V_i > 0V$, if the diode is "off" then the "open-loop" opamp will saturate $\Rightarrow V_A = 6V$. However, this voltage ~~also~~ the diode to be forward-biased up until $V_o = 5.3V$, which corresponds to $V_i = \frac{5.3V}{2}$.

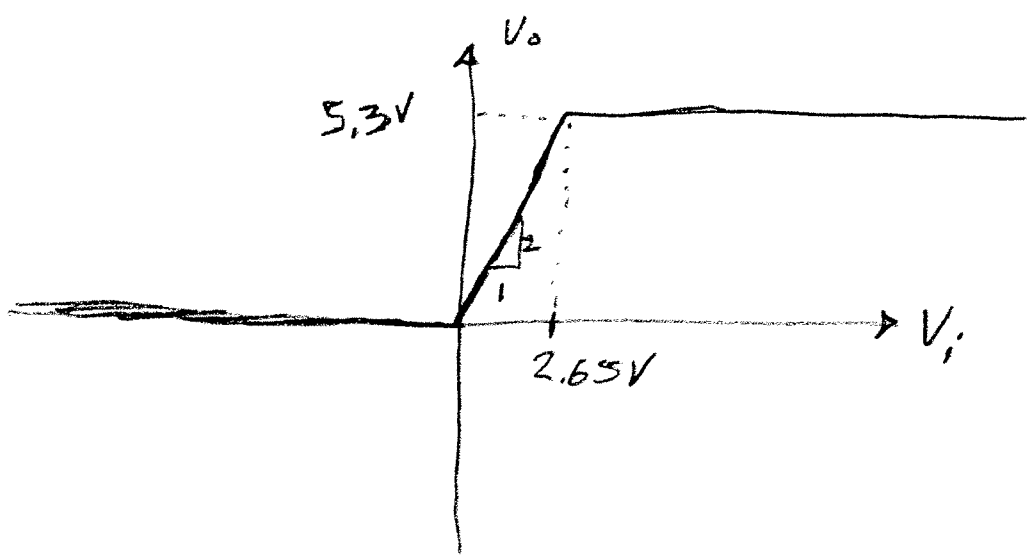Thus, from $0 \leq V_o \leq 2.65V$ the circuit operate with a linear gain of $2V/V$. For $V_i \geq 2.65V$, V_o saturates at $5.3V$.



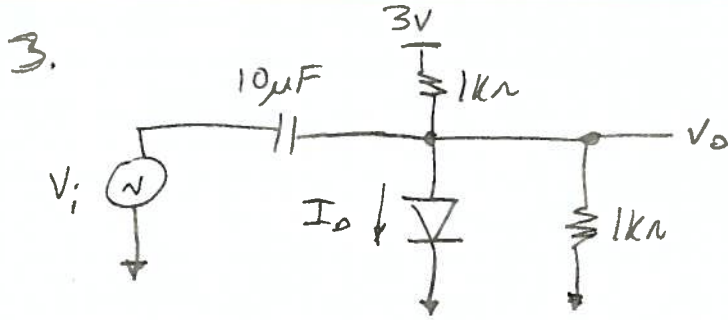

a. "DC" schematic

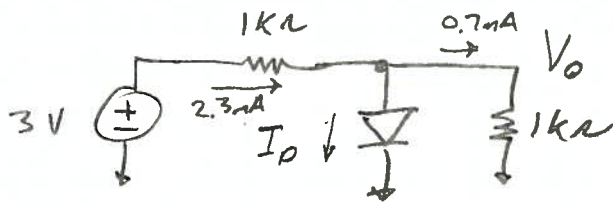


$$V_o = 0.7V$$

$$I_D = 1.6mA$$

b. Diode $r_d = \frac{n V_{th}}{I_D} = \frac{25.9mV}{1.6mA} = 16.2\Omega$

"AC" schematic

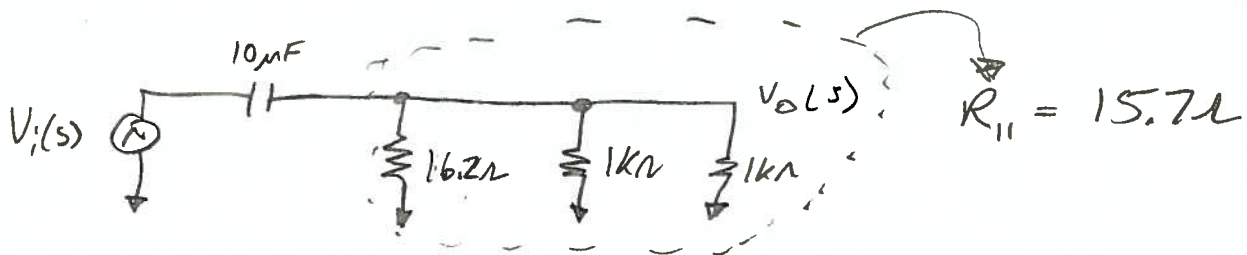

$$\frac{V_o(s)}{V_i(s)} = \frac{R_{11}}{\frac{1}{sC} + R_{11}} = \frac{s}{s + \frac{1}{R_{11}C}} = \frac{s}{s + 6.37 \times 10^3}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{s}{s + 6.37 \times 10^3}$$

c. At $\omega = 2\pi \times 10^5$


$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{j 2\pi \times 10^5}{j 2\pi \times 10^5 + 6.37 \times 10^3} \Rightarrow \left| \frac{V_o(j 2\pi \times 10^5)}{V_i(j 2\pi \times 10^5)} \right| = 0.999 \approx 1$$

$$\angle \frac{V_o(j 2\pi \times 10^5)}{V_i(j 2\pi \times 10^5)} = 0.581^\circ \approx 0^\circ$$

Thus,

$$V_{o, total} \approx 0.7V + 0.001 \sin(2\pi \times 10^5 t)$$

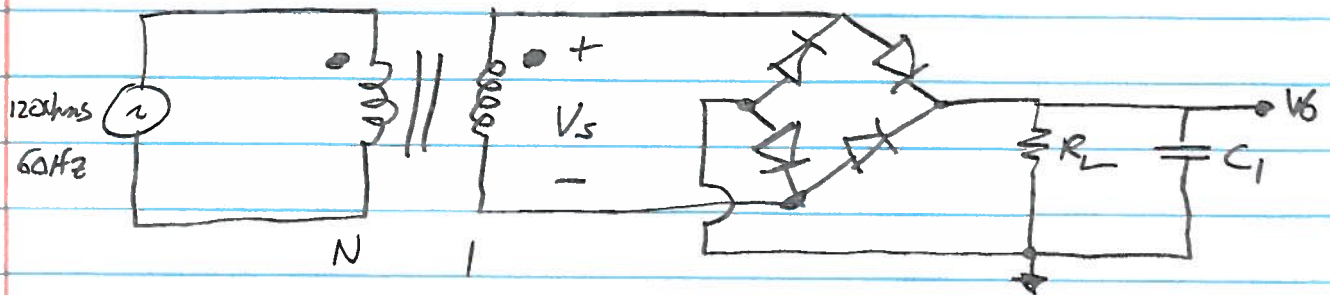4. To minimize capacitance w/ a single-ended transformer use a Bridge Rectifier.



To get output voltage = 5V

$$V_{o, \text{peak}} = V_{s, \text{peak}} - 1.4V = 5V$$

$$V_{s, \text{peak}} = 6.4V$$

Requires transformer ratio

$$\frac{120\sqrt{2}}{N} = \frac{6.4}{1} \Rightarrow N = 26.5$$

Load Current Range requires R_L

$$R_L = \frac{V_{\text{max}}}{I_{\text{max}}} = \frac{5V}{500\text{mA}} = 10\Omega$$

$$V_R = 5\% \text{ of } 5V = 0.25V$$

$$C_1 = \frac{V_{s, \text{peak}} - 2V_{D, \text{on}}}{2R_L f \Delta V_R} = \frac{6.4V - 1.4V}{2(10\Omega)(60\text{Hz})(0.25V)}$$

$$C_1 = 16.7\text{mF}$$

$$\text{Diode Maximum Reverse Voltage} = V_p - V_{\text{on}} = 6.4V - 0.7V = 5.7V$$

Diode Peak Current


$$I_p = \frac{V_p}{R_L} \left(R_L C_1 \omega \sqrt{\frac{2V_R}{V_p} + 1} \right)$$

Here it is more accurate to use $V_p = 5V$

$$I_p = \frac{5V}{10\Omega} \left((10\Omega)(16.7mF)(2\pi \cdot 60Hz) \sqrt{\frac{2(0.25V)}{5V} + 1} \right)$$

$I_p = 10.5A$, but will also accept $I_p = 11.9A$
if you use $V_p = 6.4V$

Summary

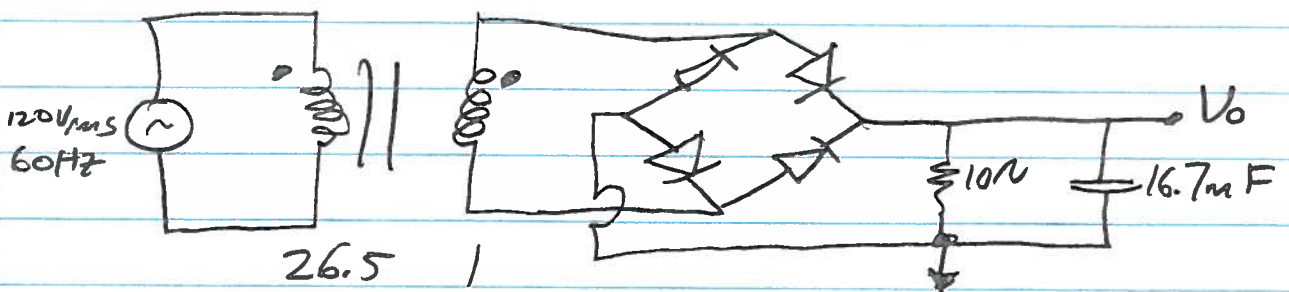

$$|\text{Diode Breakdown Voltage}| > 5.7V$$

$$I_p = 10.5A \quad (\text{or } 11.9A)$$