

ECEN326: Electronic Circuits


Spring 2022

Lab 1 Graphical Design Approach



Sam Palermo
Analog & Mixed-Signal Center
Texas A&M University

Common Emitter Amp w/ Emitter Resistor

 

$$A_v = -\frac{\alpha(R_C \parallel R_L)}{r_e + R_E \parallel R_G} = -\frac{g_m(R_C \parallel R_L)}{1 + \frac{g_m(R_E \parallel R_G)}{\alpha}}$$

$$R_{in} = kR_B \parallel (1-k)R_B \parallel [(\beta + 1)(r_e + R_E \parallel R_G)]$$

Typical Design Specifications


- Loaded voltage gain, A_v
- Max output swing, V_{omax}
 - This must be satisfied at a given linearity (total harmonic distortion)
- Input resistance, R_{in}
- Power Supply, V_{CC}
- Min Emitter Voltage for β robustness, V_E

How to set DC Biasing Conditions?

- In order to meet all design specifications, the DC biasing conditions (I_C , R_C) must be set appropriately
- Can transform design specifications into functions of I_C & R_C and graph them to find acceptable solution space

R_{in} , V_{CC} , & Neg. v_{omax} Specifications

- R_{in} Spec

 

$$R_{in} = kR_B \parallel (1-k)R_B \parallel [(\beta + 1)(r_e + R_E \parallel R_G)] \approx \beta(R_E \parallel R_G)$$

$$R_E \parallel R_G \approx \frac{R_{in}}{\beta}$$

- Input resistance is primarily set by $R_E \parallel R_G$


R_{in} , V_{CC} , & Neg. $v_{o\max}$ Specifications

- Need a minimum V_{CE} to keep transistor in active mode with maximum negative swing

Set $V_{CE\min} = 300mV$

* Note if the specs are relaxed enough, it is often good to set $V_{CE\min} = 500mV$ for margin.

- V_{CC} Spec (w/ max negative swing)

 


$$V_{CC} = V_E + V_{CE\min} + v_{o\max} + I_C R_C$$

$$V_{CE\min} = V_{CC} - I_C R_C - v_{o\max} - V_E \geq 300mV$$

R_{in} , V_{CC} , & Neg. $v_{o\max}$ Specifications

- Can solve for I_C

 

$$I_C \leq \frac{V_{CC} - v_{o\max} - 0.3V - V_E}{R_C}$$


- Minimum negative AC Swing constraint sets an upper bound on I_C

Pos. $v_{o\max}$ Specification

- Need to insure with a positive swing that the output signal doesn't clip the power supply

$$V_{CC} - I_C R_C + v_{o\max} \leq V_{CC}$$


$$I_C \geq \frac{v_{o\max}}{R_C}$$

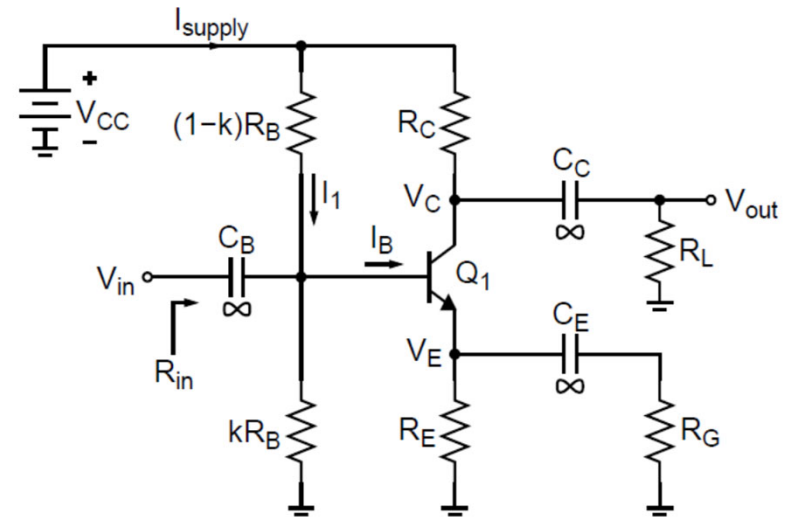

- Positive AC Swing constraint sets a lower bound on I_C
- Additional linearity constraint (harmonic distortion) generally sets a tighter bound

Gain Specification

$$|A_v| = \left| \frac{v_o}{v_i} \right| \leq \frac{g_m (R_C \parallel R_L)}{1 + \frac{g_m (R_E \parallel R_G)}{\alpha}} = \frac{\frac{I_C}{V_{th}} (R_C \parallel R_L)}{1 + \left(\frac{I_C}{V_{th}} \right) \frac{(R_E \parallel R_G)}{\alpha}}$$

 


$$I_C \geq \frac{|A_v| V_{th}}{R_C \parallel R_L - \frac{|A_v| (R_E \parallel R_G)}{\alpha}} = \frac{|A_v| V_{th}}{R_C \parallel R_L - \frac{|A_v| R_{in}}{\alpha \beta}}$$

- Gain constraint sets a lower bound on I_C

Harmonic Distortion Specification

 - Need a minimum amount of bias current to insure that the AC swing doesn't distort



Model a as a system which distorts

$$i_c = av_{be} = a_1v_{be} + a_2v_{be}^2 + a_3v_{be}^3 + \dots$$


$$\text{where } a_1 = g_m, \quad a_2 = \frac{1}{2} \frac{I_{CQ}}{V_{th}^2}, \quad \dots$$

$$\text{Here } v_{be} = v_b - v_e \approx v_b - f i_c$$

$$\text{where } f = R_E$$

***This analysis is for a general CE Amp, in our specific circuit $R_C \Rightarrow R_C || R_L$ and $R_E \Rightarrow R_E || R_G$**

Harmonic Distortion Specification

 

We want to express i_c as a function of v_b because that is our input

$$i_c = bv_b = b_1v_b + b_2v_b^2 + b_3v_b^3 + \dots$$

Can show that*

$$b_1 = \frac{g_m}{1 + g_m R_E}, \quad b_2 = \frac{1}{2} \frac{I_{CQ}}{V_{th}^2 (1 + g_m R_E)^3}, \quad \dots$$

- For single-ended amplifiers with low-distortion, HD2 will dominate the distortion terms

The second - order harmonic distortion is

$$HD2 = \frac{1}{2} \frac{b_2}{b_1^2} i_{c \max} = \frac{1}{4} \left(\frac{1}{1 + g_m R_E} \right) \left(\frac{i_{c \max}}{I_{CQ}} \right)$$

*This analysis is for a general CE Amp, in our specific circuit $R_C \Rightarrow R_C || R_L$ and $R_E \Rightarrow R_E || R_G$

Harmonic Distortion Specification

To satisfy a given HD2 specification

$$i_{c\max} \leq 4HD2(1 + g_m R_E) I_{CQ}$$

$$I_C \geq \frac{\frac{v_{o\max}}{R_C}}{4HD2(1 + g_m R_E)} \approx \frac{\frac{v_{o\max}}{R_C}}{4HD2 \left(\frac{I_C}{V_{th}} \right) R_E}$$

$$I_C \geq \frac{1}{2} \sqrt{\frac{V_{th} v_{o\max}}{R_C R_E HD2}}$$

Using $R_E \approx \frac{R_{in}}{\beta}$

$$I_C \geq \frac{1}{2} \sqrt{\frac{V_{th} v_{o\max} \beta}{(R_C \parallel R_L) R_{in} HD2}}$$

*This analysis is for a general CE Amp, in our specific circuit $R_C \Rightarrow R_C \parallel R_L$ and $R_E \Rightarrow R_E \parallel R_G$

- HD2 will dominate, but is not the only distortion term, so you need to use a slightly larger current or put some margin in the HD2 value relative to the THD spec

Key CE Amp Design Equation Summary

$$\text{Neg. Swing, } R_{in}, V_{CC} : I_C \leq \frac{V_{CC} - v_{o\max} - 0.3V - V_E}{R_C}$$

$$\text{Pos. Swing : } I_C \geq \frac{v_{o\max}}{R_C}$$


$$\text{Gain : } I_C \geq \frac{|A_v|V_{th}}{R_C \parallel R_L - \frac{|A_v|R_{in}}{\alpha\beta}}$$

$$\text{Harmonic Distortion : } I_C \geq \frac{1}{2} \sqrt{\frac{V_{th}v_{o\max}\beta}{(R_C \parallel R_L)R_{in}HD2}}$$

Design Example - Specifications

- $|A_v| \geq |-20|$
- $R_{in} \geq 10k\Omega$
- $R_L = 20k\Omega$
- $V_{omax} = 1V_{pk}$ w/ THD $\leq 5\%$ (-26.0dB)
- $V_{CC} = 5V$
- $V_E \geq 0.5V$
- $I_{supply} \leq 1.5mA$
- Nominal operation at 5kHz



Design Equation Plots

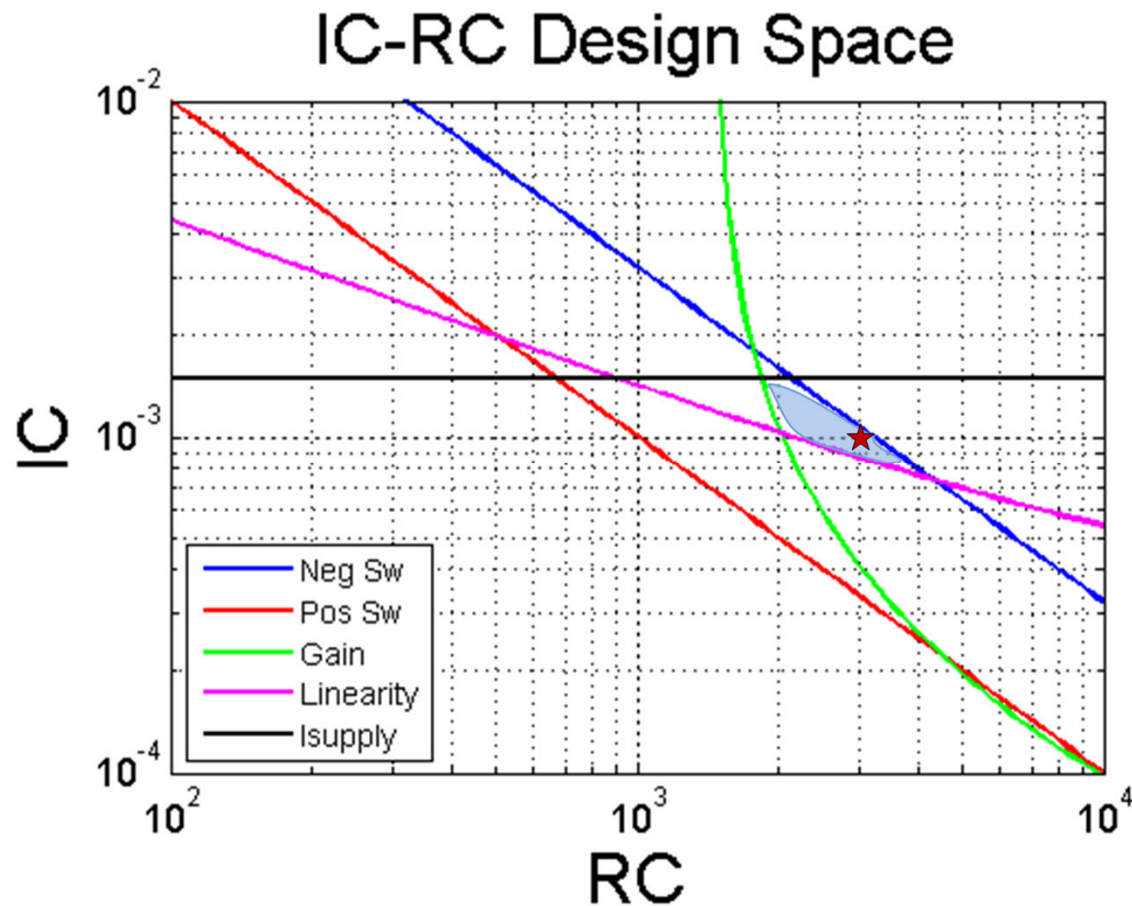

Plots done with $\beta=150$


- Chosen design point is $I_C=1\text{mA}$, $R_C=3\text{k}\Omega$

DC Operating Points

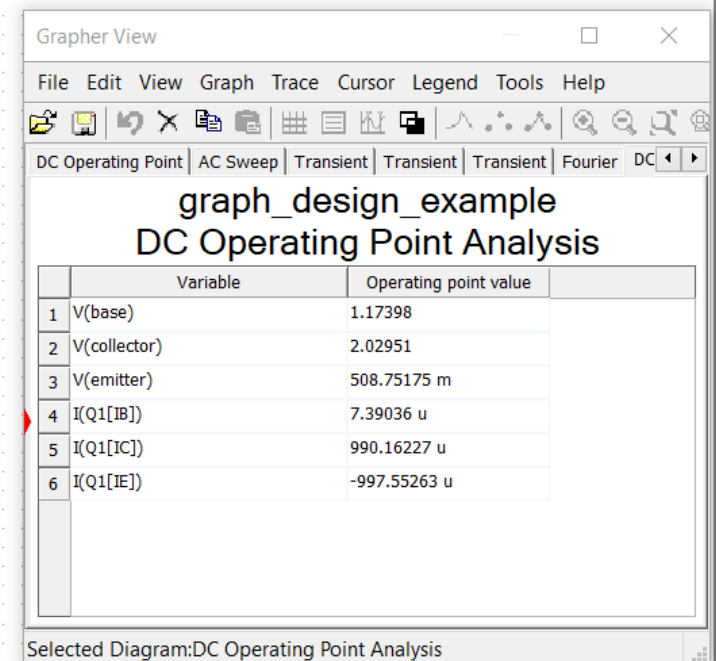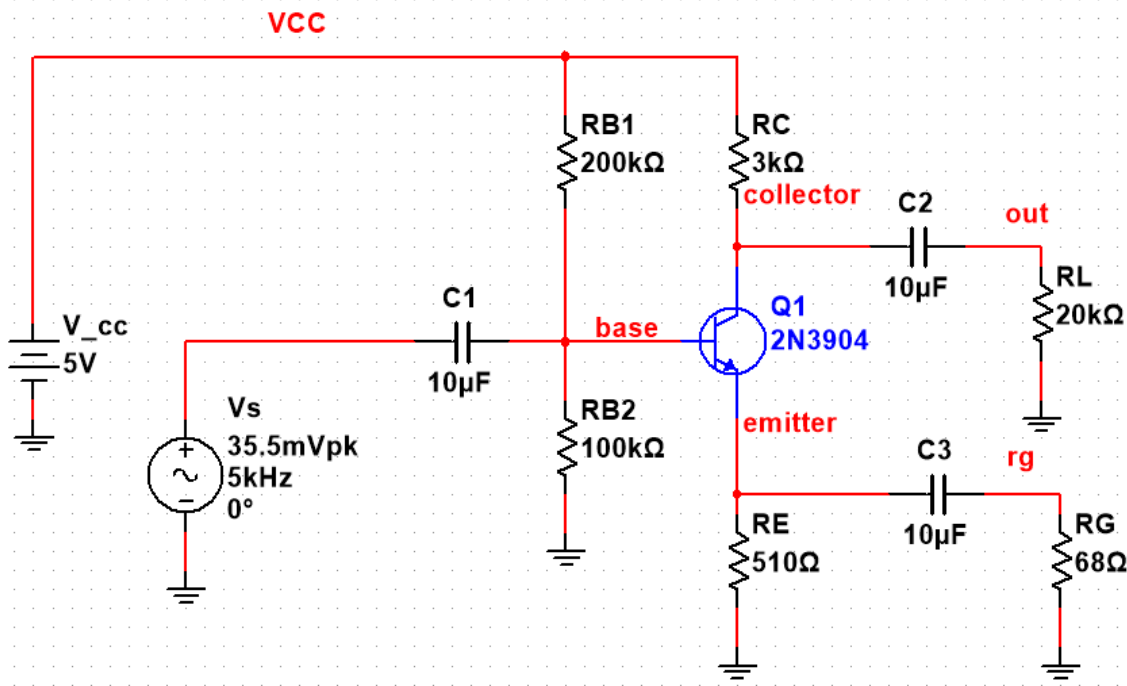


- R_E is set with $V_E = I_E R_E$
- R_G is set as R_{in} / β
- DC bias points must be reasonable for the circuit to work as designed!

AC Gain

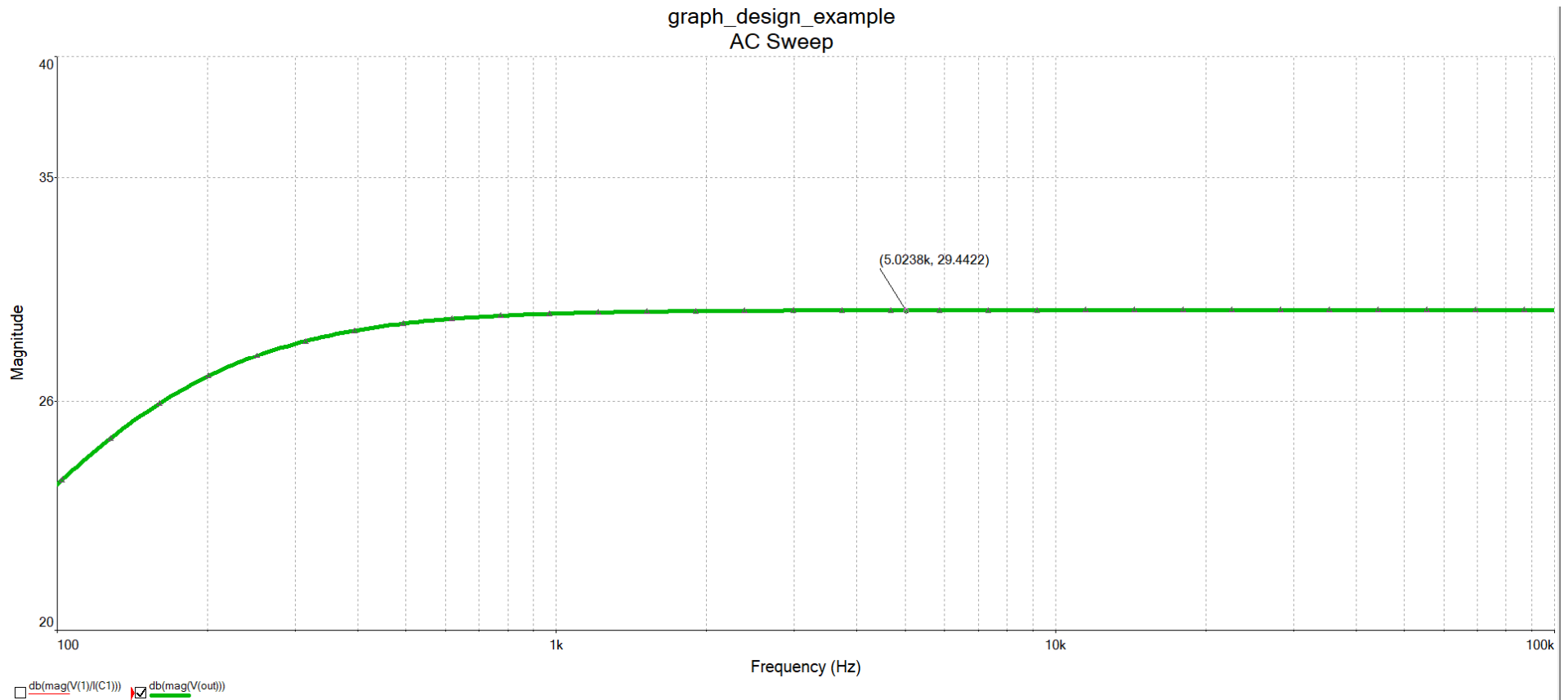


- $|A_v| = 29.4\text{dB} = 29.5\text{V/V}$

R_{in}

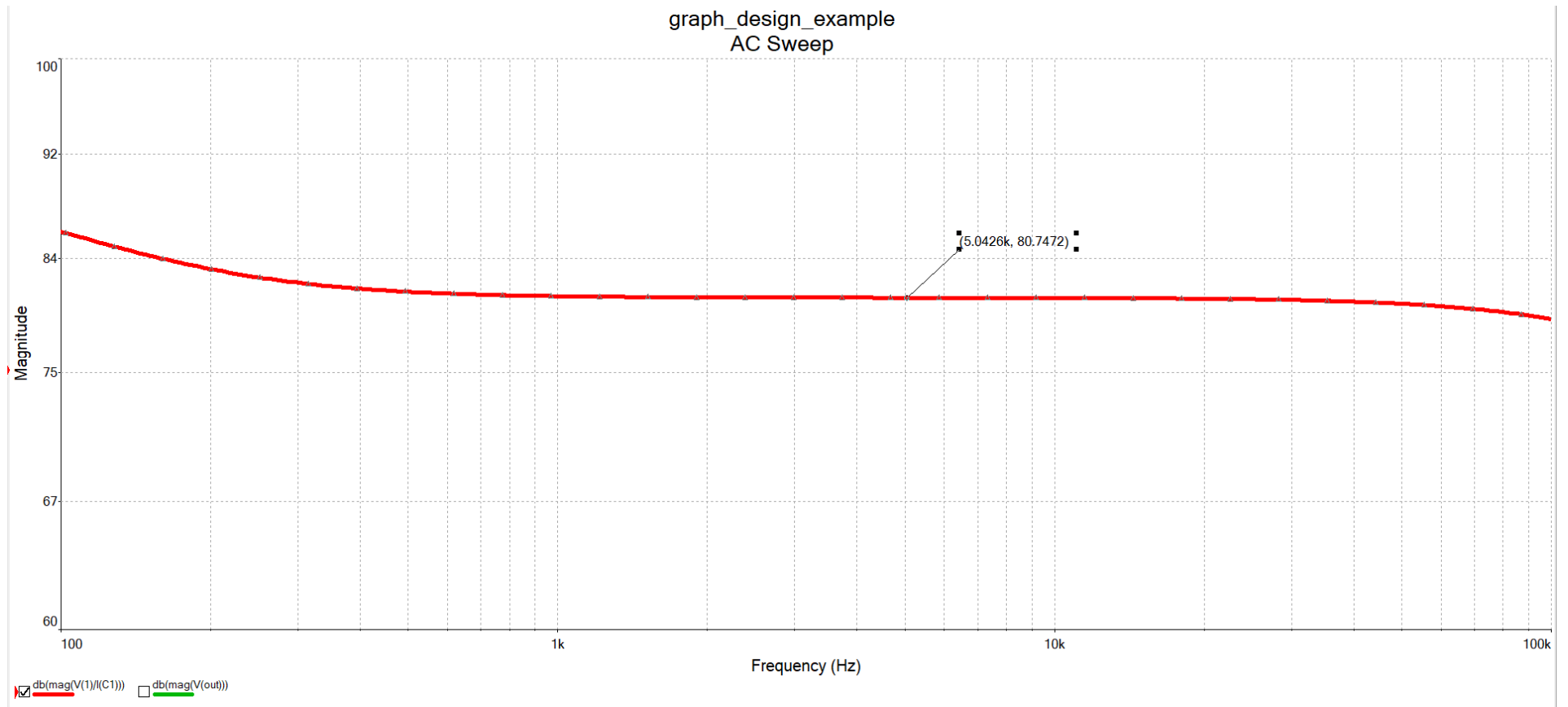

- $R_{in} = 80.7\text{dB}\Omega = 10.8\text{k}\Omega$

Transient Response

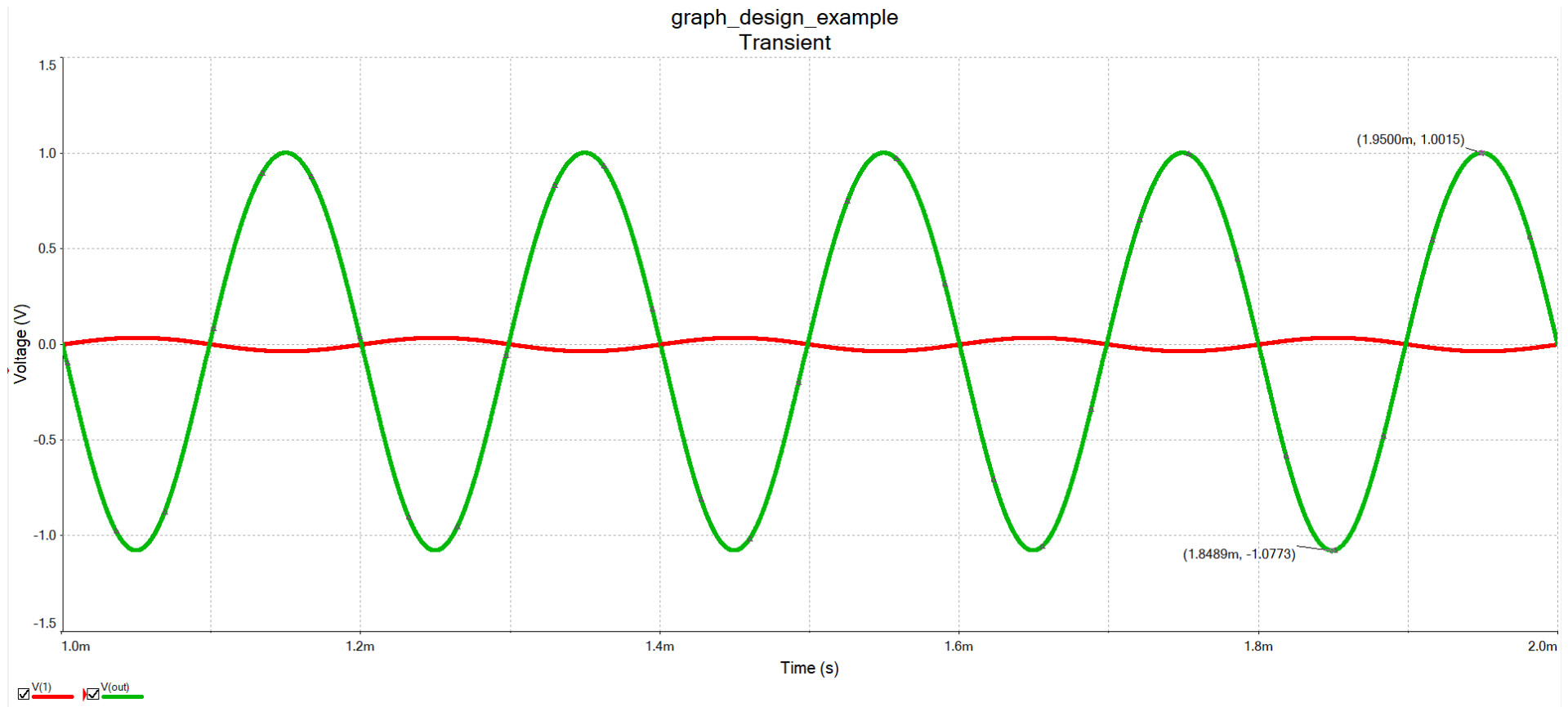


- Response with 35.5mV_{pk} input signal
- Signal is beginning to compress

Total Harmonic Distortion

graph_design_example


Harmonic	Frequency	Magnitude	Phase	Norm. Mag	Norm. Phase
0	0	0.00476869	0	0.00457648	0
1	5000	1.042	-178.38	1	0
2	10000	0.0328185	93.9458	0.0314957	272.327
3	15000	0.00245989	-175.03	0.00236074	3.34859
4	20000	0.000150432	-84.251	0.000144369	94.1302
5	25000	8.29323e-006	10.0916	7.95896e-006	188.473
6	30000	4.13012e-006	-6.1577	3.96365e-006	172.224
7	35000	3.15322e-006	1.56041	3.02612e-006	179.942

Fourier Analysis

 

- THD = 3.16% = -30dB

R_{out}

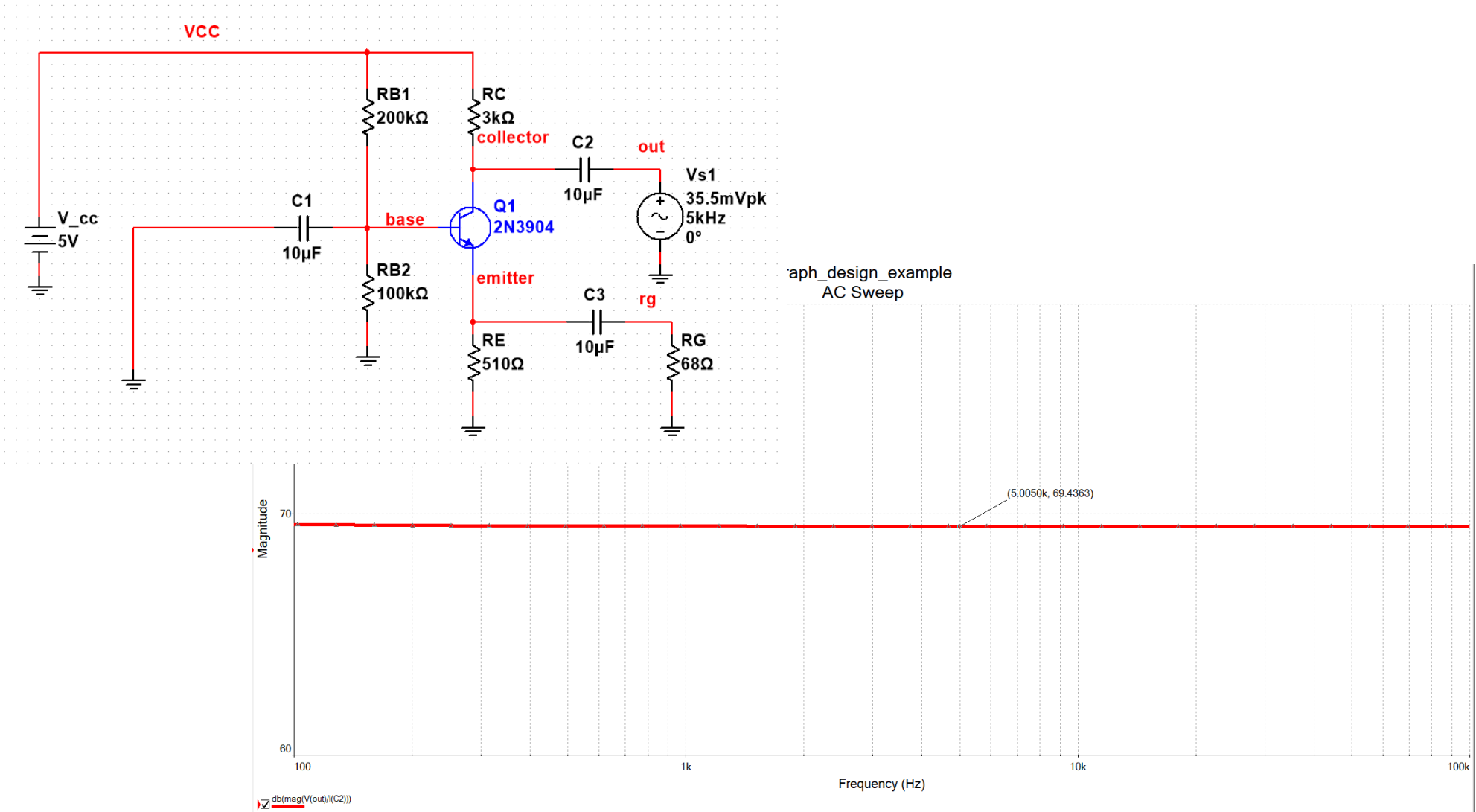

- $R_{out} = 69.4\text{dB}\Omega = 2.95\text{k}\Omega \approx R_C$

Lab1 Design Specs

- $|A_v| \geq |-15|$
- $R_{in} \geq 5k\Omega$
- $R_L = 10k\Omega$
- $V_{omax} = 1V_{pk}$ w/ THD $\leq 5\%$ (-26.0dB)
- $V_{CC} = 5V$
- $V_E \geq 0.5V$
- $I_{supply} \leq 4mA$
- Nominal operation at 5kHz