

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 326 – Electronic Circuits

Fall 2015

Exam #1

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 5 pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		40
2		60
Total		100



Name: SAM PALERMO

UIN: _____

Problem 1 (40 points)


For the circuit shown below, assume that all transistors are operating in the active region and that $V_A = \infty$ for all transistors. Obtain expressions for the following:

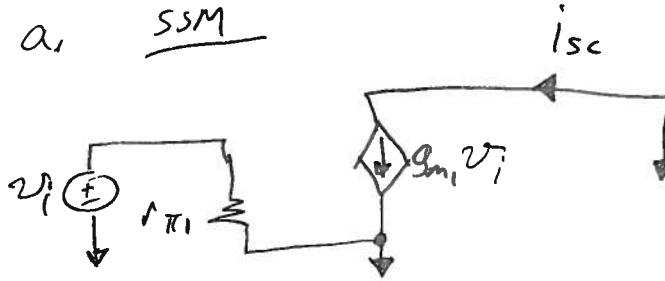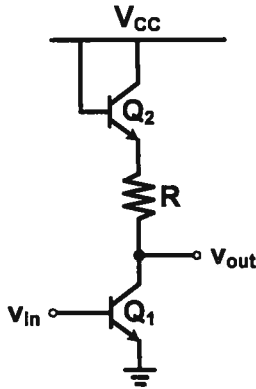- a) Short-circuit transconductance, G_m . Here use the book convention where i_{sc} flowing into the circuit is positive.
- b) Output resistance, R_{out}
- c) Small-signal gain, $A_v = v_{out}/v_{in}$
- d) Input resistance, R_{in}



$$G_m = \frac{i_{sc}}{v_i} = \frac{g_{m1} v_i}{v_i} = g_{m1}$$


b. SSM

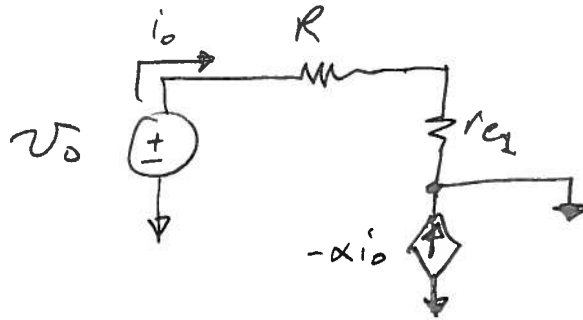

$$R_{out} = \frac{v_o}{i_o} = R + r_{e2}$$

c. $A_v = -G_m R_{out} = -g_{m1} (R + r_{e2})$

d. SSM

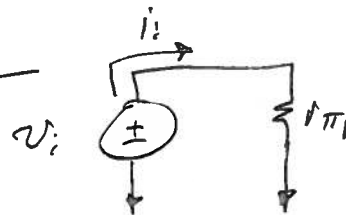

$$R_{in} = r_{\pi 1}$$

Problem 2 (60 points)


For the circuit shown below, assume that all transistors are operating in the saturation region.

Use the following transistor parameters

$$K_{PN} = \mu_n C_{ox} = 200 \mu A/V^2, V_{TH,N} = 0.4V$$

$$\lambda_1 = \lambda_2 = 0$$

$$\lambda_3 = \lambda_4 = 0.1 V^{-1}$$

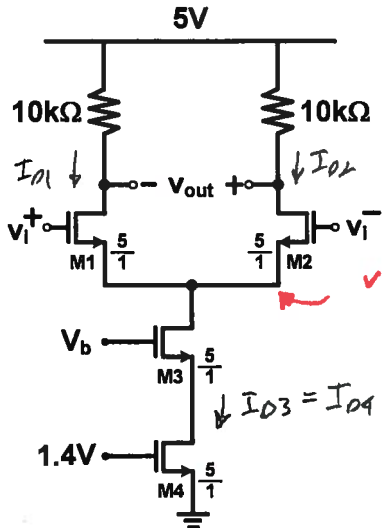

$$I_{D1} = I_{D2} = \frac{I_{D3}}{2} = 250 \mu A$$

virtual gnd

$$I_{D3} = I_{D4} = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 = \frac{200 \mu}{2} \left(\frac{5}{1}\right) (1.4 - 0.4)^2 = 500 \mu A$$

- a) Calculate the DC current flowing through the transistors. Here assume that V_b and the input common-mode is sufficient to keep all the transistors operating in the saturation region. Also, you can neglect λ effects for this part.

$$I_{D1} = 250 \mu A$$

$$I_{D2} = 250 \mu A$$

$$I_{D3} = 500 \mu A$$

$$I_{D4} = 500 \mu A$$


- b) Calculate the small-signal differential mode gain, $A_{DM} = v_{out}/(v_i^+ - v_i^-)$. Include λ effects, if necessary.

$$A_{DM} = g_{m1} R_D$$

$$g_{m1} = \sqrt{\mu C_{ox} \frac{W}{L} 2 I_D} = \sqrt{200 \mu \left(\frac{5}{1}\right) (2) (250 \mu A)} = 707 \mu A/V$$

$$A_{DM} = (707 \mu A/V) (10k\Omega) = 7.07 V/V$$

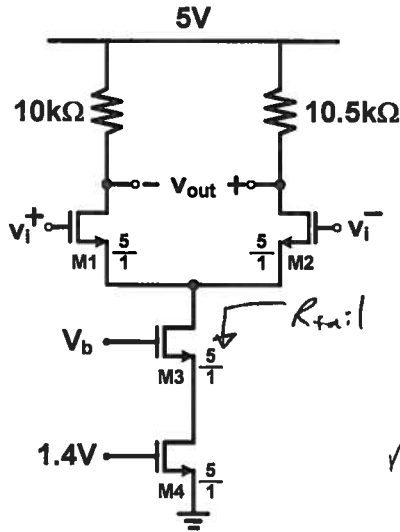- c) As shown in the circuit below, during manufacturing a mismatch appears in the load resistors. Calculate the common-mode to differential-mode conversion gain, A_{CM-DM} . Include λ effects, if necessary.



$$A_{CM-DM} = \frac{\Delta R_o}{\frac{1}{g_{m1}} + 2R_{tail}}$$

$$R_{tail} = r_{o3} + r_{o4} + g_{m3} r_{o3} r_{o4}$$

$$r_{o3} = r_{o4} = \frac{1}{\lambda I_D} = \frac{1}{(0.1)(500\mu)} = 20k\Omega$$

$$g_{m3} = \sqrt{\mu_{ox} \frac{w}{L} 2I_D} = \sqrt{(200\mu)(\frac{5}{1})2(500\mu)} = 1 \text{ mA/V}$$

$$A_{CM-DM} = \frac{500}{\frac{1}{707\mu A/V} + 2(20k + 20k + (1m)(20k)^2)} = 567 \times 10^{-6}$$

$$A_{CM-DM} = 567 \times 10^{-6} = -64.9 \text{ dB}$$

- d) Calculate the common-mode rejection ration, $CMRR = (A_{DM}/A_{CM-DM})$. Here you can use the A_{DM} calculated in part (b).

$$CMRR = \frac{A_{DM}}{A_{CM-DM}} = \frac{7.07}{567 \times 10^{-6}} = 12.5 \times 10^3 = 81.9 \text{ dB}$$

Scratch Paper