

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 326 – Electronic Circuits

Fall 2015

Exam #3

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 5 pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		35
2		35
3		30
Total		100


Name: _____ SAM PALERMO _____

UIN: _____

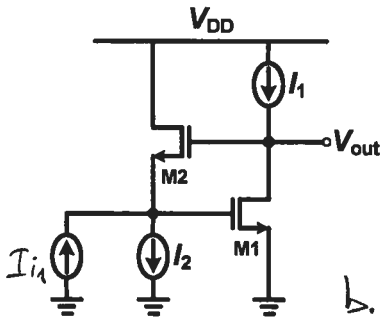Problem 1 (35 points)


For the circuit shown below, assume that all transistors are operating in the saturation region and that $\lambda > 0$.

- What type of feedback is present in the circuit?
- Give expressions for the **open-loop** gain (V_{out}/I_{in}), input resistance, and output resistance. Make sure to include feedback loading effects.
- What is the feedback factor, K ?
- Give expressions for the **closed-loop** gain (V_{out}/I_{in}), input resistance, and output resistance.



a. Voltage - Current Feedback
(Sensing) (Return) or Shunt-Shunt
(FB) (sensing)

b. Breaking Loop

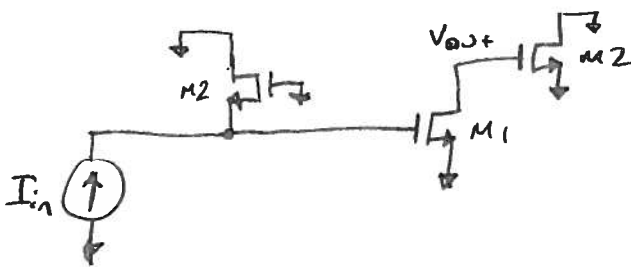


$$R_{OL} = \frac{V_{out}}{I_{in}} = \left(\frac{1}{g_{m2} \parallel r_{o2}} \right) (-g_{m1} r_{o1})$$

$$R_{in,OL} = \left(\frac{1}{g_{m2} \parallel r_{o2}} \right)$$

$$R_{out,OL} = r_{o1}$$

For K :

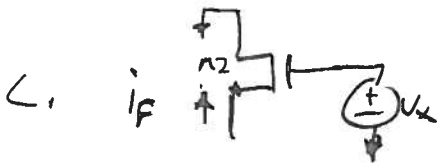

$$K = \frac{i_f}{V_x} = -g_{m2}$$

$$d. \quad R_{CL} = \frac{R_{OL}}{1 + K R_{OL}} = \frac{-g_{m1} r_{o1} \left(\frac{1}{g_{m2} \parallel r_{o2}} \right)}{1 + g_{m1} r_{o1} g_{m2} \left(\frac{1}{g_{m2} \parallel r_{o2}} \right)}$$

$$R_{in,CL} = \frac{R_{in,OL}}{1 + K R_{OL}} = \frac{\left(\frac{1}{g_{m2} \parallel r_{o2}} \right)}{1 + g_{m1} r_{o1} g_{m2} \left(\frac{1}{g_{m2} \parallel r_{o2}} \right)}$$

$$R_{out,CL} = \frac{R_{out,OL}}{1 + K R_{OL}} = \frac{r_{o1}}{1 + g_{m1} r_{o1} g_{m2} \left(\frac{1}{g_{m2} \parallel r_{o2}} \right)}$$

Problem 2 (35 points)


For the circuit shown below, assume that all transistors are operating in the saturation region. Also assume that the amplifier is well-designed with one dominant pole and that we can neglect any zero effects.

Calculate the following using these transistor parameters.

$$K_{PN} = \mu_n C_{ox} = 200 \mu A/V^2, V_{TH,N} = 0.4V, \lambda_N = 0.1V^{-1}$$

$$K_{PP} = \mu_p C_{ox} = 100 \mu A/V^2, V_{TH,P} = -0.4V, \lambda_P = 0.1V^{-1}$$

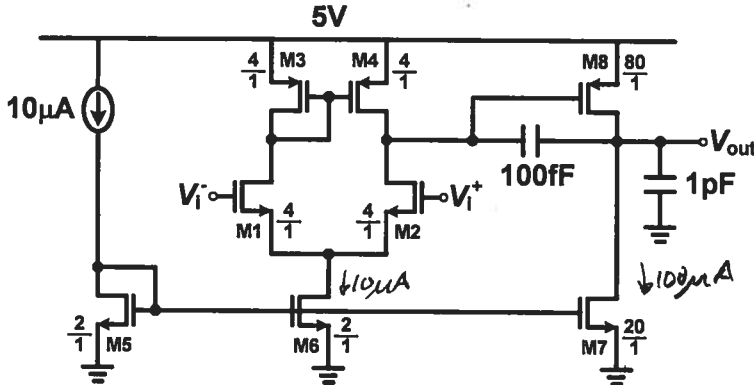Low-frequency gain ($A_{DC} = V_{out}/(V_i^+ - V_i^-)$), dominant pole (ω_{p1}), second pole (ω_{p2}), unity-gain frequency (ω_{GX}), and worst-case phase margin (PM).



$$A_{DC} = \left(\frac{-g_{m2}}{g_{o2} + g_{o4}} \right) \left(\frac{-g_{m8}}{g_{o7} + g_{o8}} \right)$$

$$g_{m2} = \sqrt{(200 \mu)(\frac{4}{1})(2)(5 \mu)} = 89.4 \mu A/V$$

$$g_{o2} = g_{o4} = \lambda I = (0.1V^{-1})(5 \mu A) = 0.5 \mu$$

$$g_{m8} = \sqrt{(100 \mu)(\frac{80}{1})(2)(100 \mu)} = 1.26 mA/V \quad g_{o7} = g_{o8} = (0.1V^{-1})(100 \mu A) = 10 \mu$$

$$A_{DC} = \left(\frac{89.4 \mu}{0.5 \mu + 0.5 \mu} \right) \left(\frac{1.26 mA}{10 \mu + 10 \mu} \right) = 5.63 \times 10^3$$

$$\omega_{p1} = - \frac{(g_{o2} + g_{o4})(g_{o7} + g_{o8})}{g_{m8} C_C} = - \frac{(0.5 \mu + 0.5 \mu)(10 \mu + 10 \mu)}{(1.26 mA)(100f)} = -159 Krad/s = -25.3 KHz$$

$$\omega_{p2} = - \frac{g_{m8}}{C_L} = - \frac{1.26 mA}{1p} = -1.26 G rad/s = -201 MHz$$

$$\omega_{GX} = \frac{g_{m2}}{C_L} = \frac{89.4 \mu}{100f} = 894 M rad/s = 142 MHz$$

$$PM = \tan^{-1} \left(\frac{\omega_{p2}}{\omega_{GX}} \right) = \tan^{-1} \left(\frac{201 MHz}{142 MHz} \right) = 54.8^\circ$$

$$A_{DC} = 5.63 \times 10^3$$

$$\omega_{p1} = -159 Krad/s$$


$$\omega_{p2} = -1.26 Grad/s$$

$$\omega_{GX} = 894 M rad/s$$

$$PM = 54.8^\circ$$

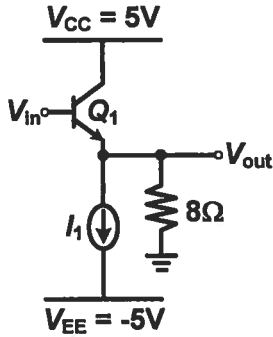Problem 3 (30 points)

The circuit shown below should be designed to deliver 1W into an 8Ω load resistor with minimal distortion. Determine I_1 , the average power consumed by Q_1 , and the average power consumed by I_1 .



$$P_{avg} = \frac{V_p^2}{2R_L}$$

$$V_p = \sqrt{2R_L P_{avg}} = \sqrt{2(8\Omega)(1W)} = 4V$$

$$I_p = \frac{V_p}{R_L} = \frac{4V}{8\Omega} = 0.5A \Rightarrow I_1 = 0.5A$$

$$P_{avg, Q1} = I_1 \left(V_{cc} - \frac{V_p}{2} \right) = 0.5A \left(5V - \frac{4V}{2} \right) = 1.5W$$

$$P_{avg, I1} = -I_1 V_{EE} = -(0.5A)(-5V) = 2.5W$$

$$I_1 = 0.5A$$

$$P_{av, Q1} = 1.5W$$

$$P_{av, I1} = 2.5W$$

Scratch Paper