


ECEN 326

Electronic Circuits


Feedback

Dr. Aydın İlker Karşılıyan

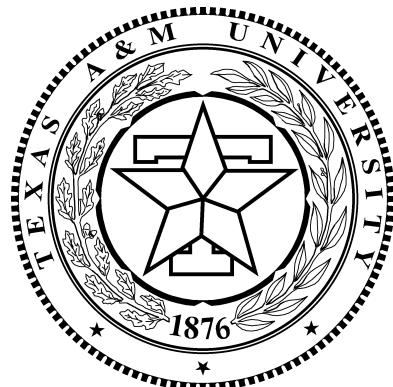Texas A&M University
Department of Electrical and Computer Engineering



Ideal Feedback Configuration

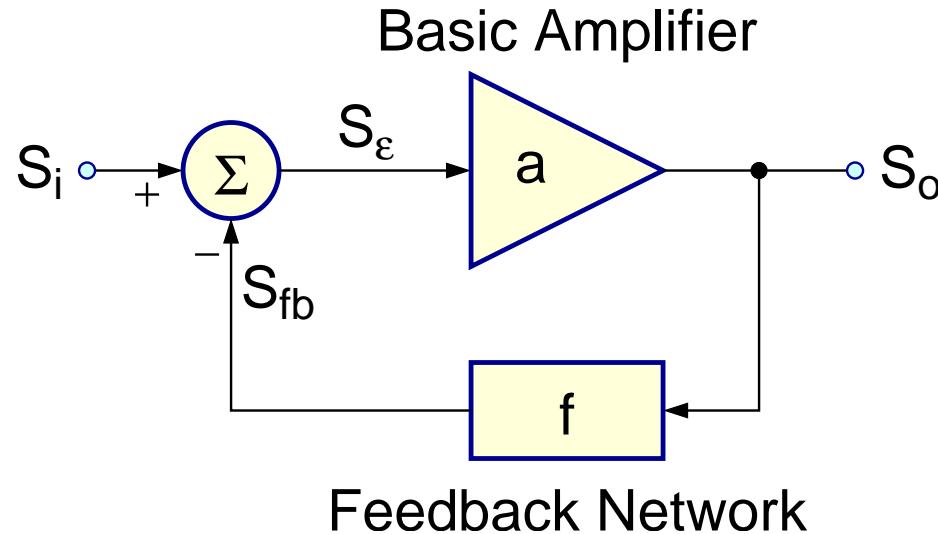

$$\frac{S_o}{S_i} = A = \frac{a}{1 + \tau} , \quad \tau = af$$

$$\frac{S_\varepsilon}{S_i} = \frac{1}{1 + \tau} , \quad \frac{S_{fb}}{S_i} = \frac{\tau}{1 + \tau}$$

Effect of Feedback

Gain sensitivity

Gain of the basic amplifier (**a**) usually depends on temperature, operating conditions and process parameters.


$$\frac{dA}{da} = \frac{(1 + af) - af}{(1 + af)^2} = \frac{1}{(1 + af)^2}$$

$$\delta A = \frac{\delta a}{(1 + af)^2} \Rightarrow \frac{\delta A}{A} = \frac{1 + af}{a} \frac{\delta a}{(1 + af)^2}$$

$$\frac{\delta A}{A} = \frac{\frac{\delta a}{a}}{1 + af} = \frac{\delta a}{a} \frac{1}{1 + T}$$

Effect of Feedback


Distortion

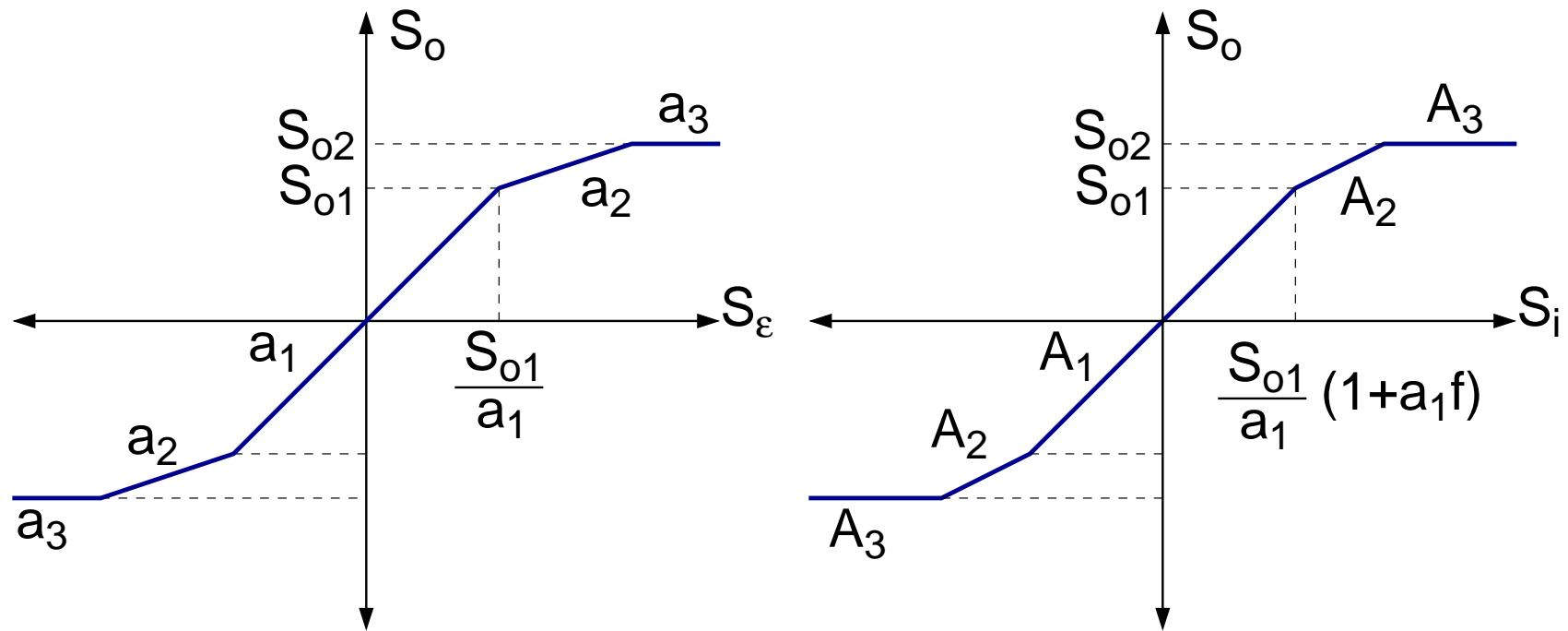

$$A_1 = \frac{a_1}{1 + a_1 f} \approx \frac{1}{f}, \quad A_2 = \frac{a_2}{1 + a_2 f} \approx \frac{1}{f}$$

Two-Port Networks

y parameters

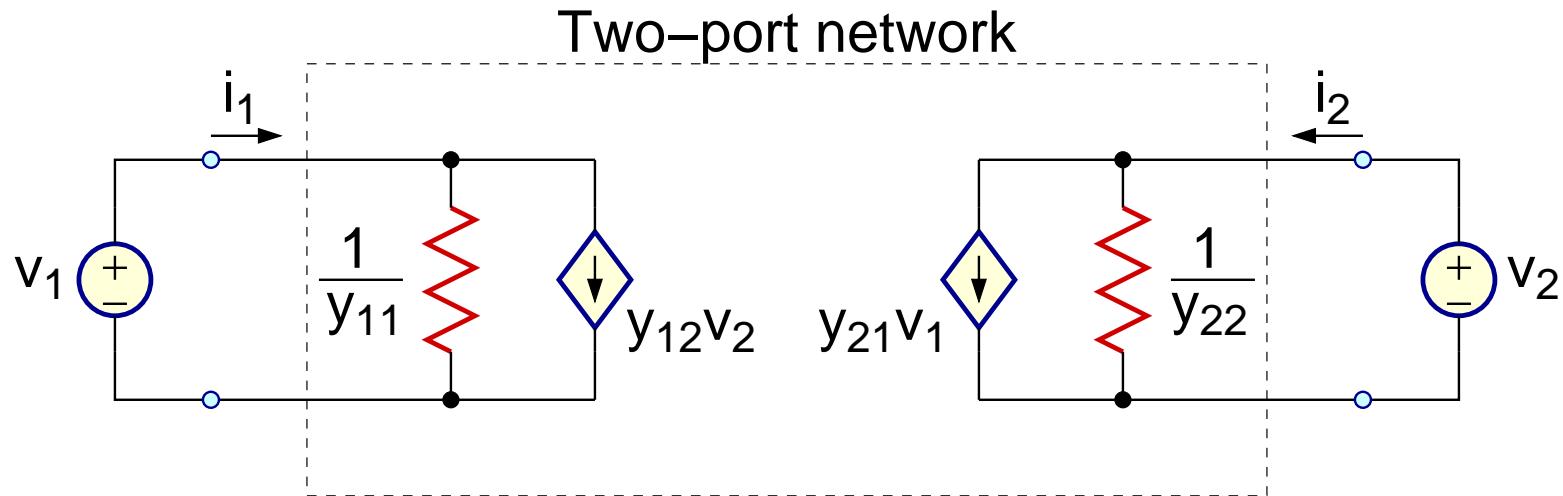


$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0}, \quad y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0}$$

$$y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0}, \quad y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0}$$

Two-Port Networks

z parameters

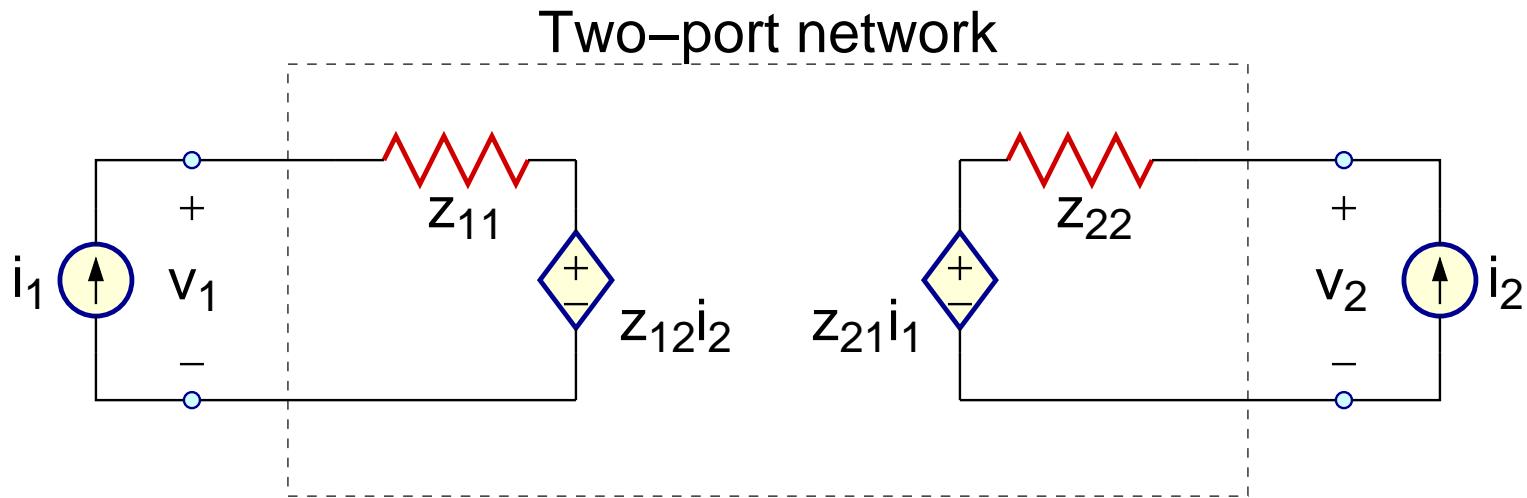

$$v_1 = z_{11}i_1 + z_{12}i_2$$


$$v_2 = z_{21}i_1 + z_{22}i_2$$

$$z_{11} = \left. \frac{v_1}{i_1} \right|_{i_2=0}, \quad z_{12} = \left. \frac{v_1}{i_2} \right|_{i_1=0}$$

$$z_{21} = \left. \frac{v_2}{i_1} \right|_{i_2=0}, \quad z_{22} = \left. \frac{v_2}{i_2} \right|_{i_1=0}$$

Two-Port Networks

h parameters

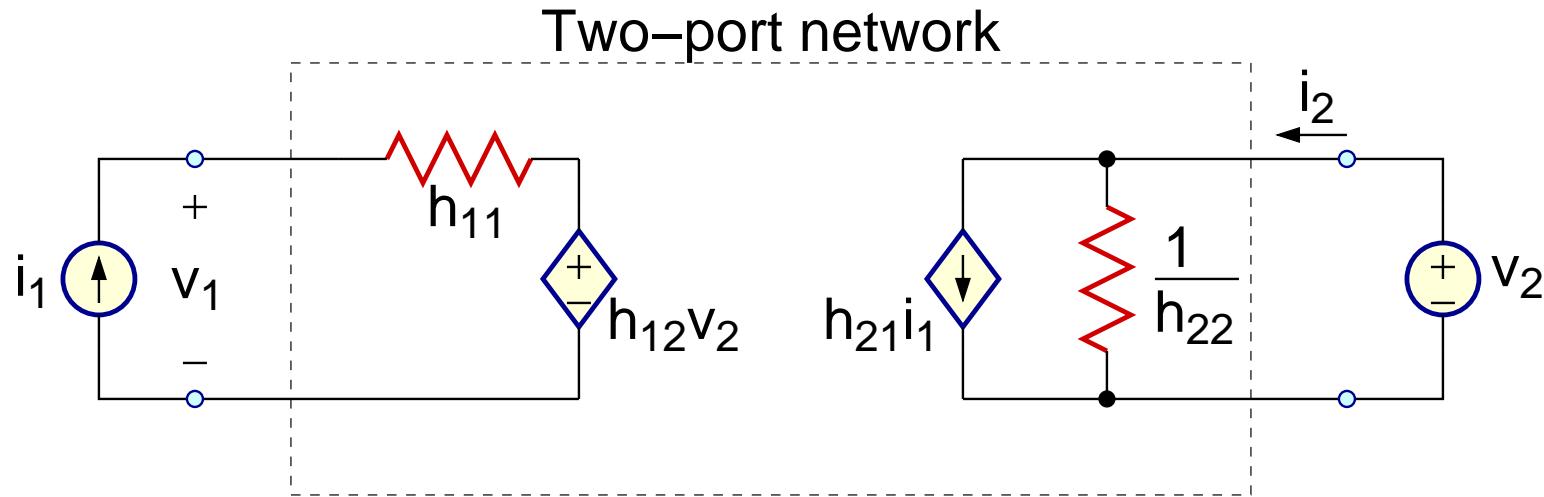

$$v_1 = h_{11}i_1 + h_{12}v_2$$


$$i_2 = h_{21}i_1 + h_{22}v_2$$

$$h_{11} = \left. \frac{v_1}{i_1} \right|_{v_2=0}, \quad h_{12} = \left. \frac{v_1}{v_2} \right|_{i_1=0}$$

$$h_{21} = \left. \frac{i_2}{i_1} \right|_{v_2=0}, \quad h_{22} = \left. \frac{i_2}{v_2} \right|_{i_1=0}$$

Two-Port Networks

g parameters

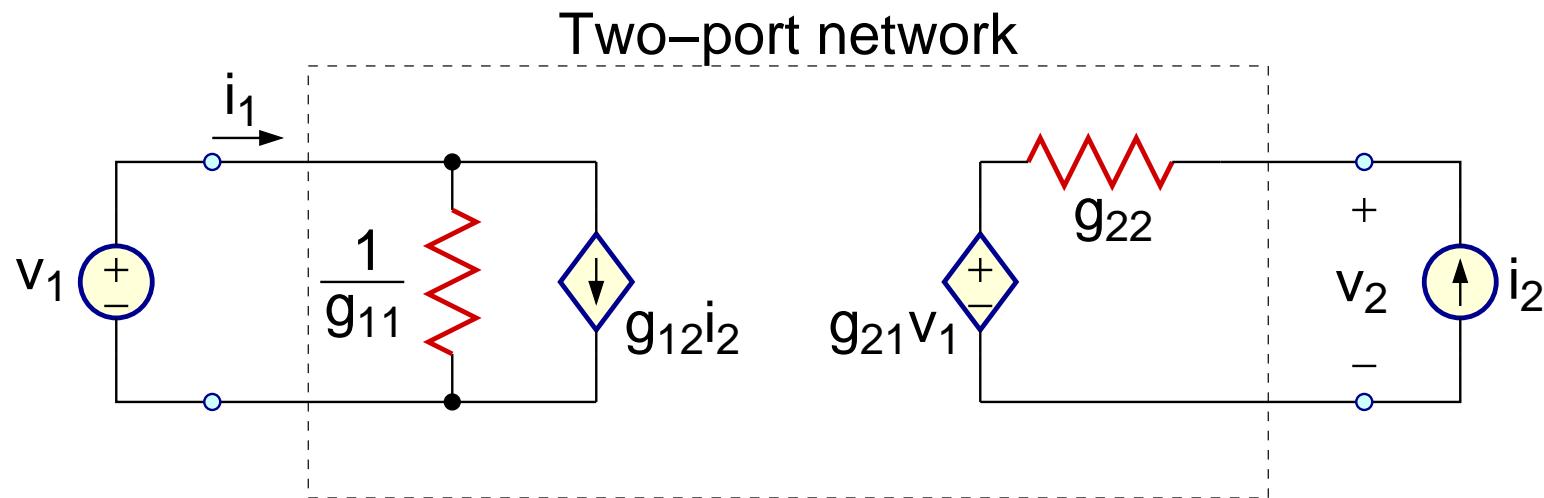

$$i_1 = g_{11}v_1 + g_{12}i_2$$

$$v_2 = g_{21}v_1 + g_{22}i_2$$

$$g_{11} = \left. \frac{i_1}{v_1} \right|_{i_2=0}, \quad g_{12} = \left. \frac{i_1}{i_2} \right|_{v_1=0}$$

$$g_{21} = \left. \frac{v_2}{v_1} \right|_{i_2=0}, \quad g_{22} = \left. \frac{v_2}{i_2} \right|_{v_1=0}$$

Feedback Configurations

According to whether the output signal \mathbf{S}_o is a current or a voltage and whether the feedback signal \mathbf{S}_{fb} is a current or a voltage, four feedback configurations exist:

- Series-Shunt Feedback

$\mathbf{S}_{fb} = v_{fb}$ (voltage), $\mathbf{S}_o = v_o$ (voltage)

- Shunt-Shunt Feedback

$\mathbf{S}_{fb} = i_{fb}$ (current), $\mathbf{S}_o = v_o$ (voltage)

- Shunt-Series Feedback


$\mathbf{S}_{fb} = i_{fb}$ (current), $\mathbf{S}_o = i_o$ (current)

- Series-Series Feedback

$\mathbf{S}_{fb} = v_{fb}$ (voltage), $\mathbf{S}_o = i_o$ (current)

Series-Shunt


Ideal

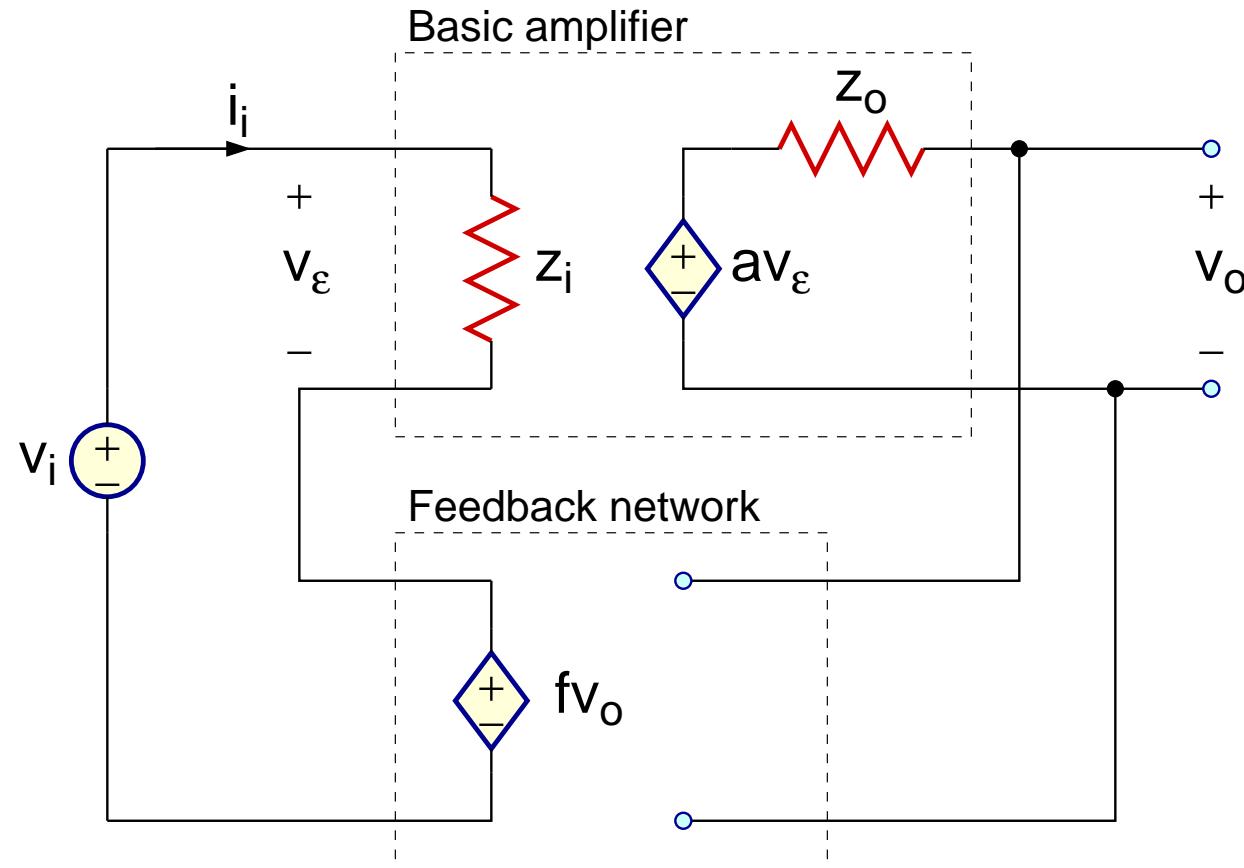

$$\frac{v_o}{v_i} = \frac{a}{1 + af} \quad z_i = (1 + af)z_i \quad z_o = \frac{z_o}{1 + af}$$

Series-Shunt

h-parameter representation

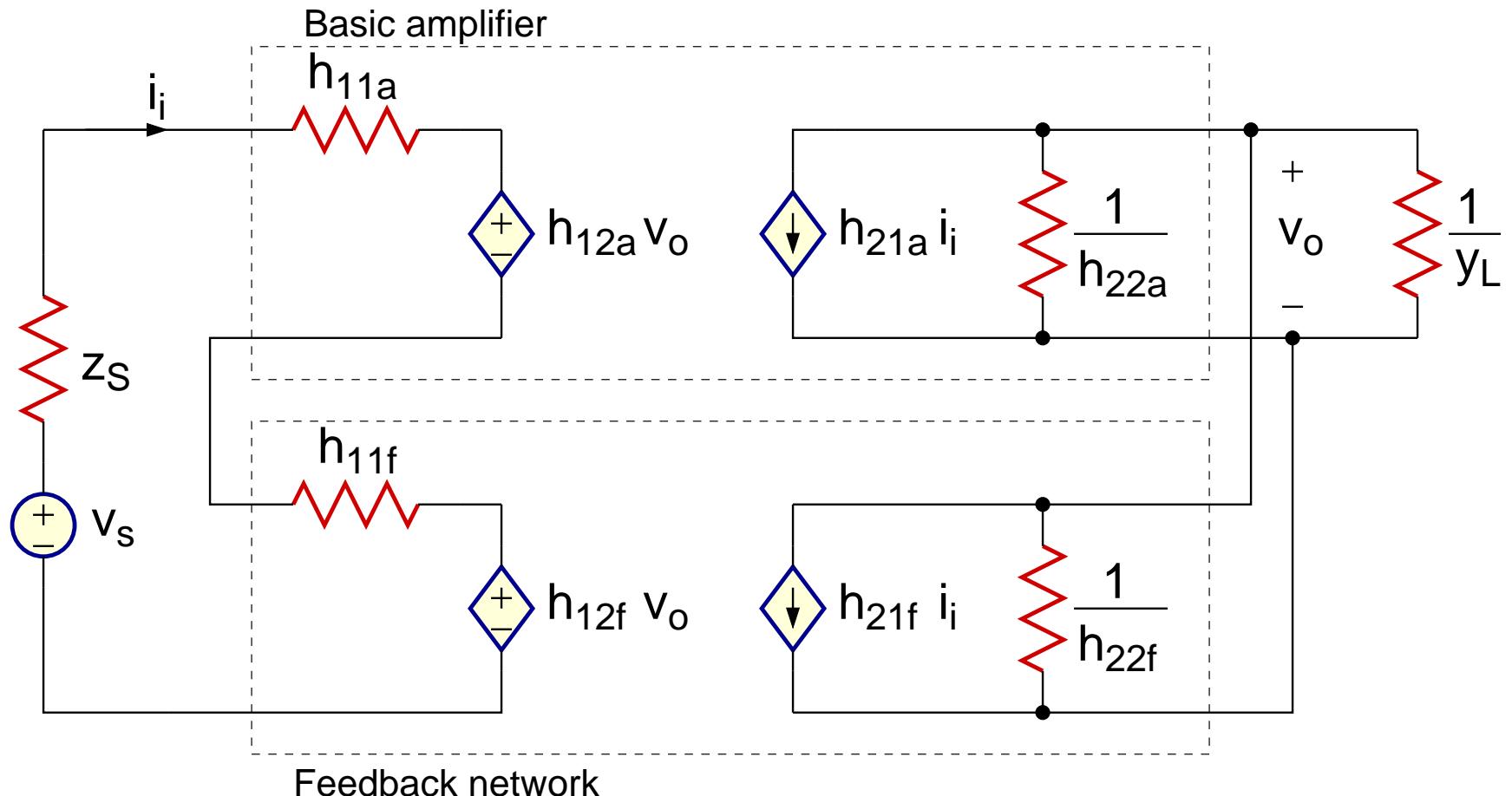


$$|h_{12f}| \gg |h_{12a}|$$

$$|h_{21a}| \gg |h_{21f}|$$

Series-Shunt

h-parameter representation - simplified

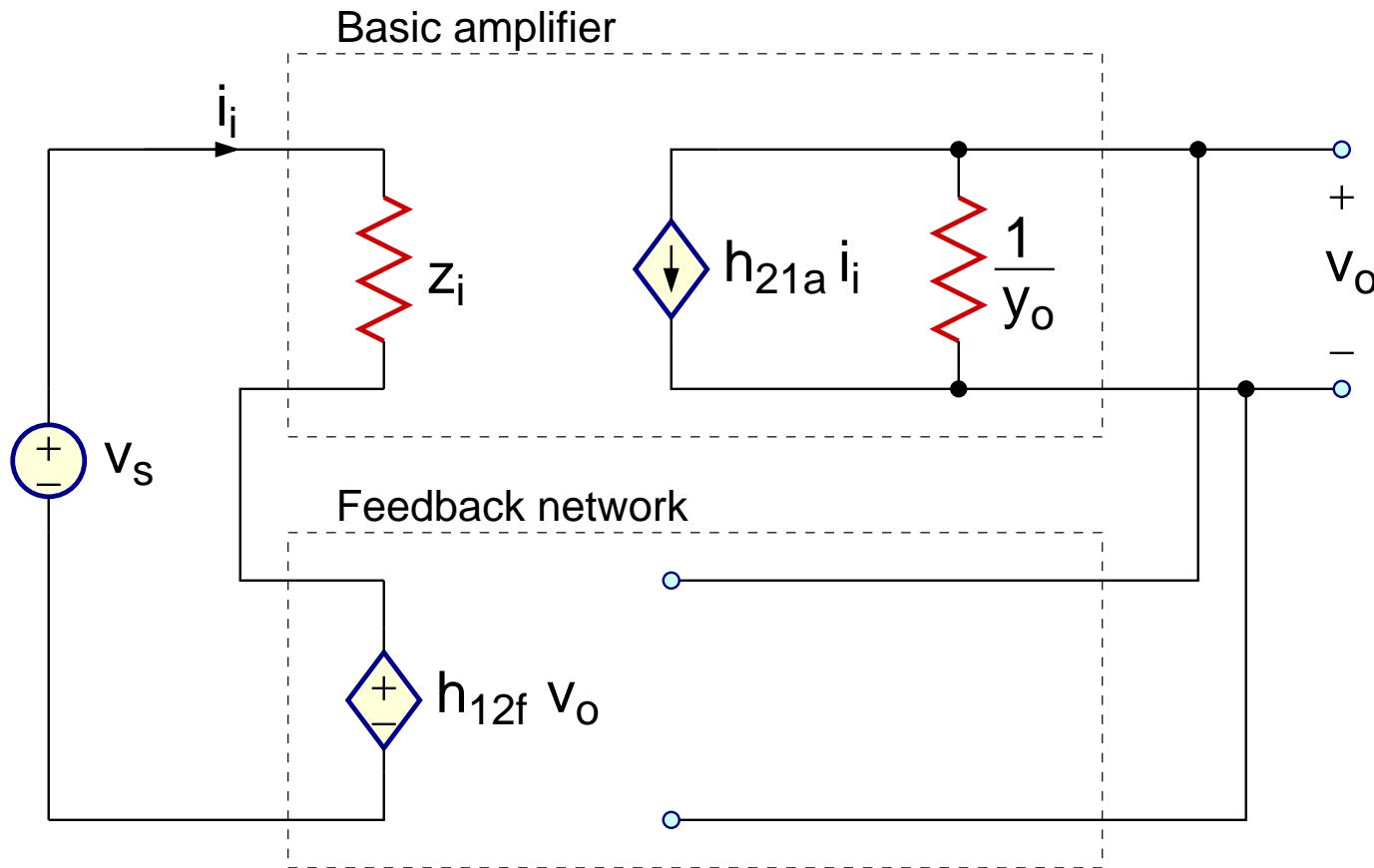


$$z_i = z_s + h_{11a} + h_{11f}$$

$$y_o = y_L + h_{22a} + h_{22f}$$

Series-Shunt

h-parameter representation - simplified

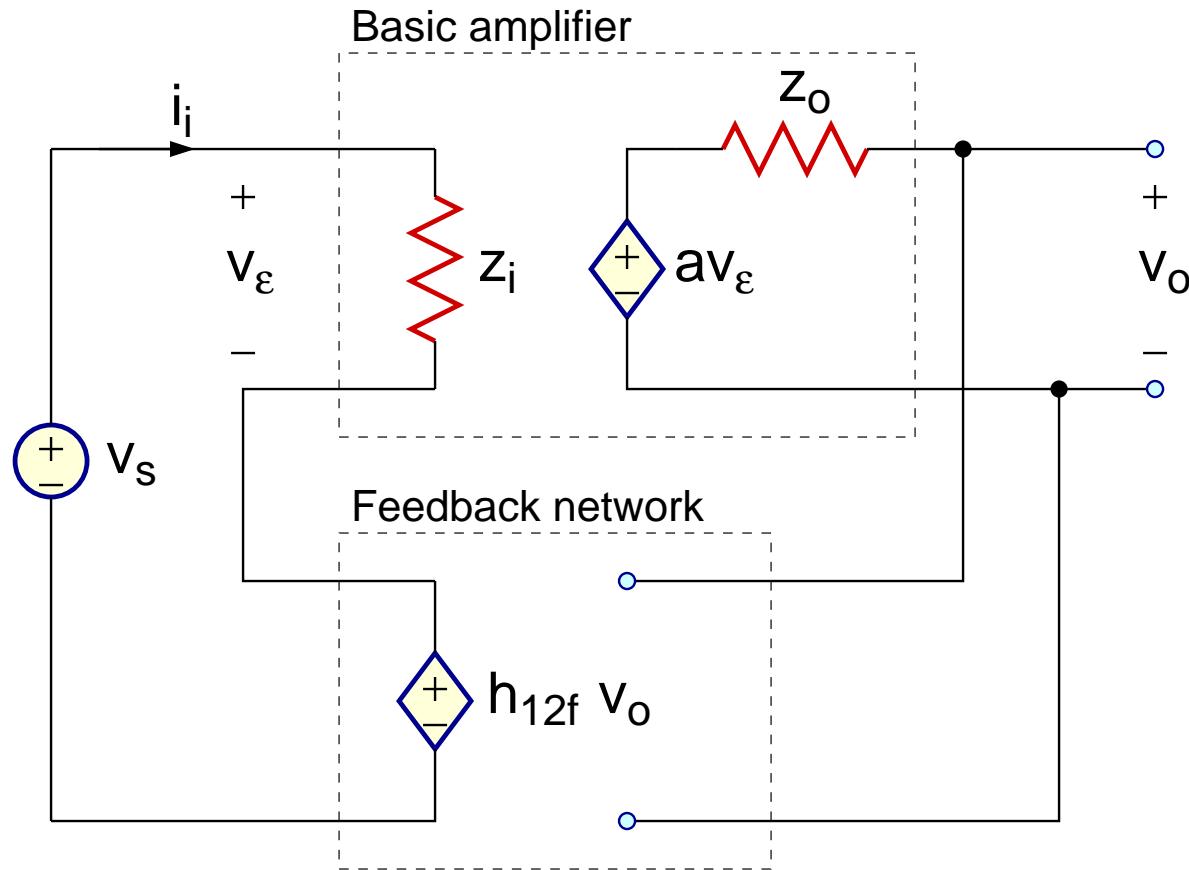


$$a = -\frac{h_{21a}}{z_i y_o}$$

$$f = h_{12f}$$

$$z_o = \frac{1}{y_o}$$

Series-Shunt

Example

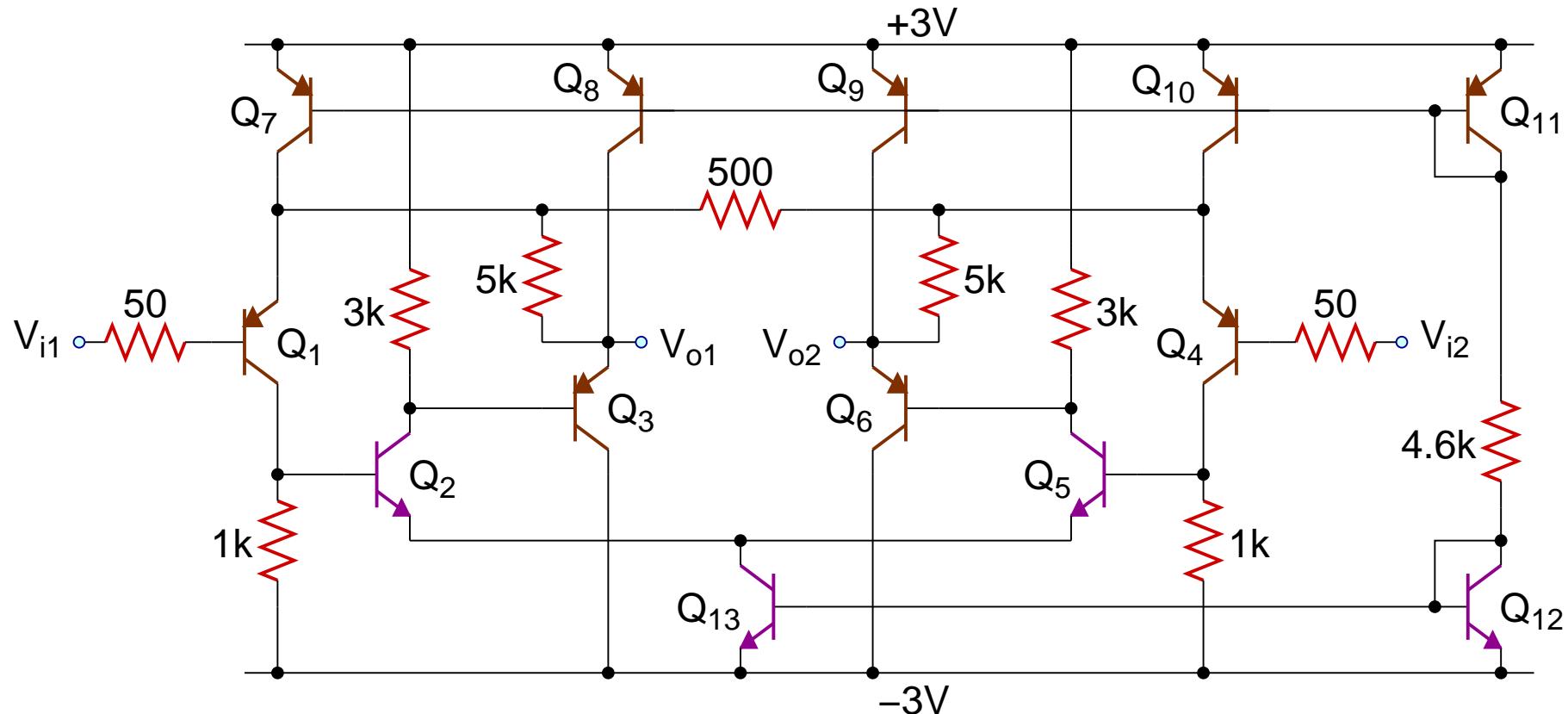


$$V_{i1,dc} = V_{i2,dc} = 0, \quad V_A = \infty, \quad V_T = 25mV, \quad \beta = 100$$

Series-Shunt

Example


Differential-mode AC half circuit:

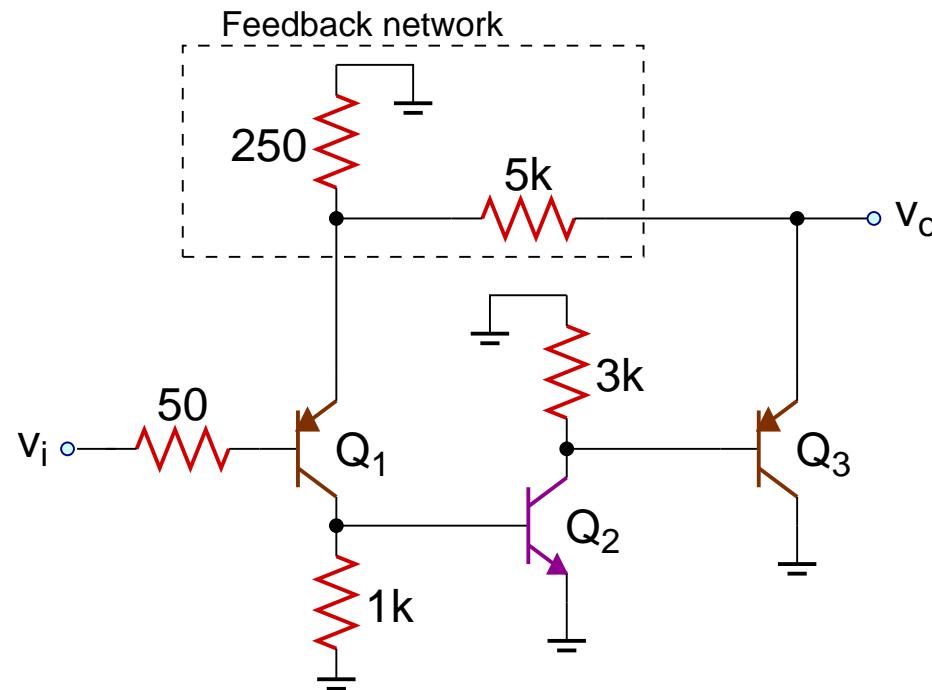

Input: Voltage
Output: Voltage


$$\begin{aligned}I_{C1} &= 1.3 \text{ mA} \\I_{C2} &= 0.5 \text{ mA} \\I_{C3} &= 0.7 \text{ mA}\end{aligned}$$

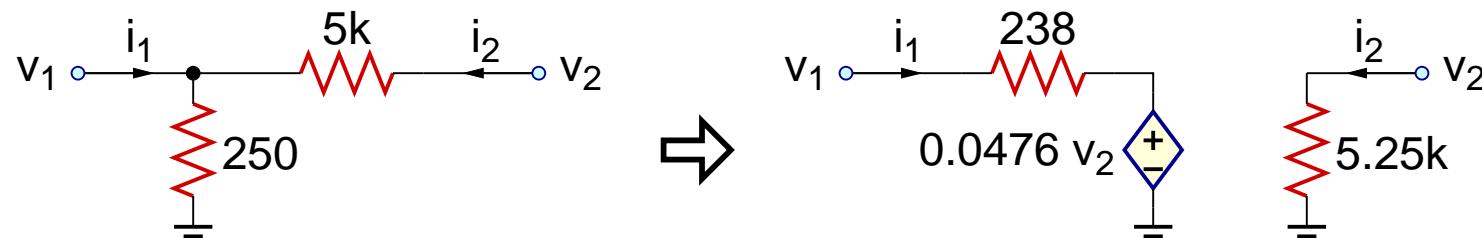h-parameter representation of the feedback network:




Series-Shunt

Example

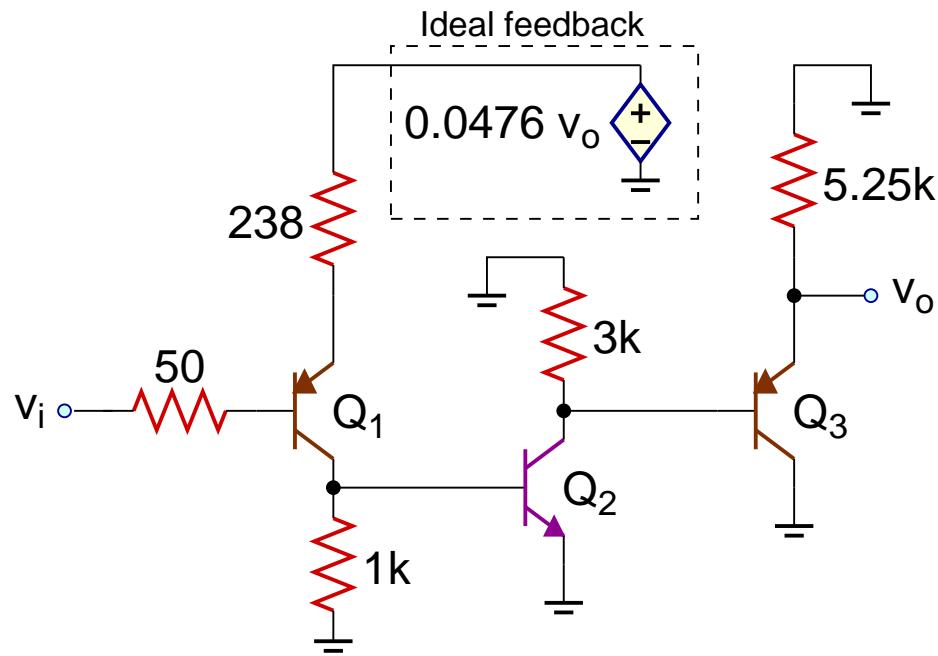

$$f = 0.0476$$

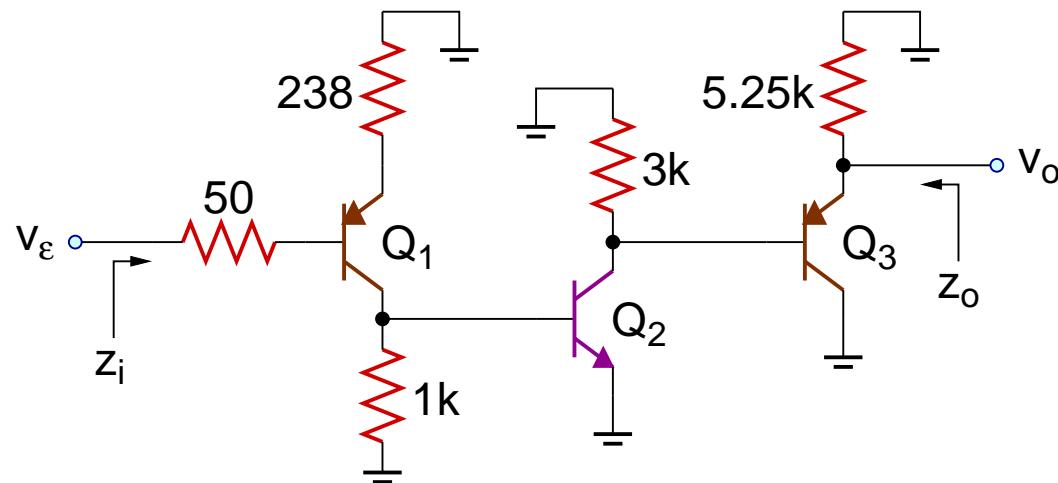


$$a = \frac{v_o}{v_e} = 192$$

$$z_i = 26 \text{ k}\Omega$$


$$z_o = 64.6 \Omega$$

Series-Shunt

Example

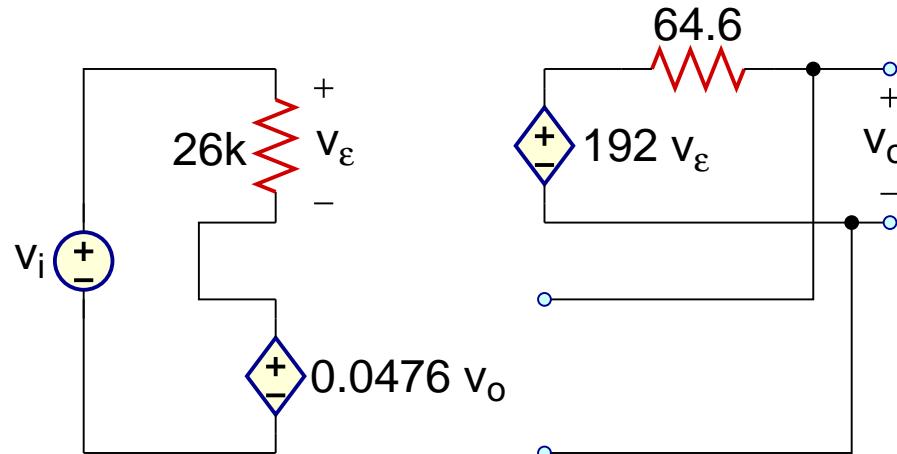
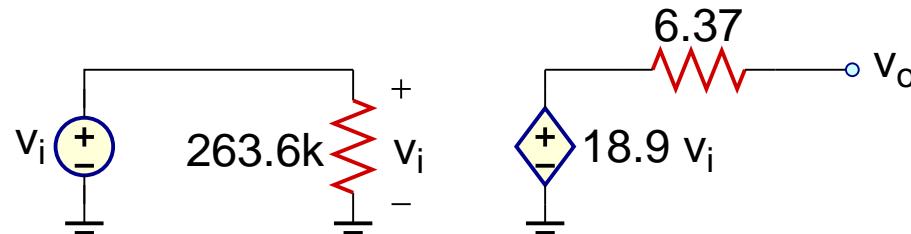
$$\begin{aligned} a &= 192 \\ f &= 0.0476 \\ z_i &= 26 \text{ k}\Omega \\ z_o &= 64.6 \Omega \end{aligned}$$



$$A = \frac{v_o}{v_i} = \frac{a}{1+af} = 18.9$$

$$Z_i = z_i(1+af) = 263.6 \text{ k}\Omega \quad Z_o = \frac{z_o}{1+af} = 6.37 \Omega$$


$$A_{dm} = 18.9$$

$$R_{id} = 2 \times 263.6 \text{ k} = 527.2 \text{ k}\Omega$$

$$R_{od} = 2 \times 6.37 = 12.7 \Omega$$

Shunt-Shunt

Ideal

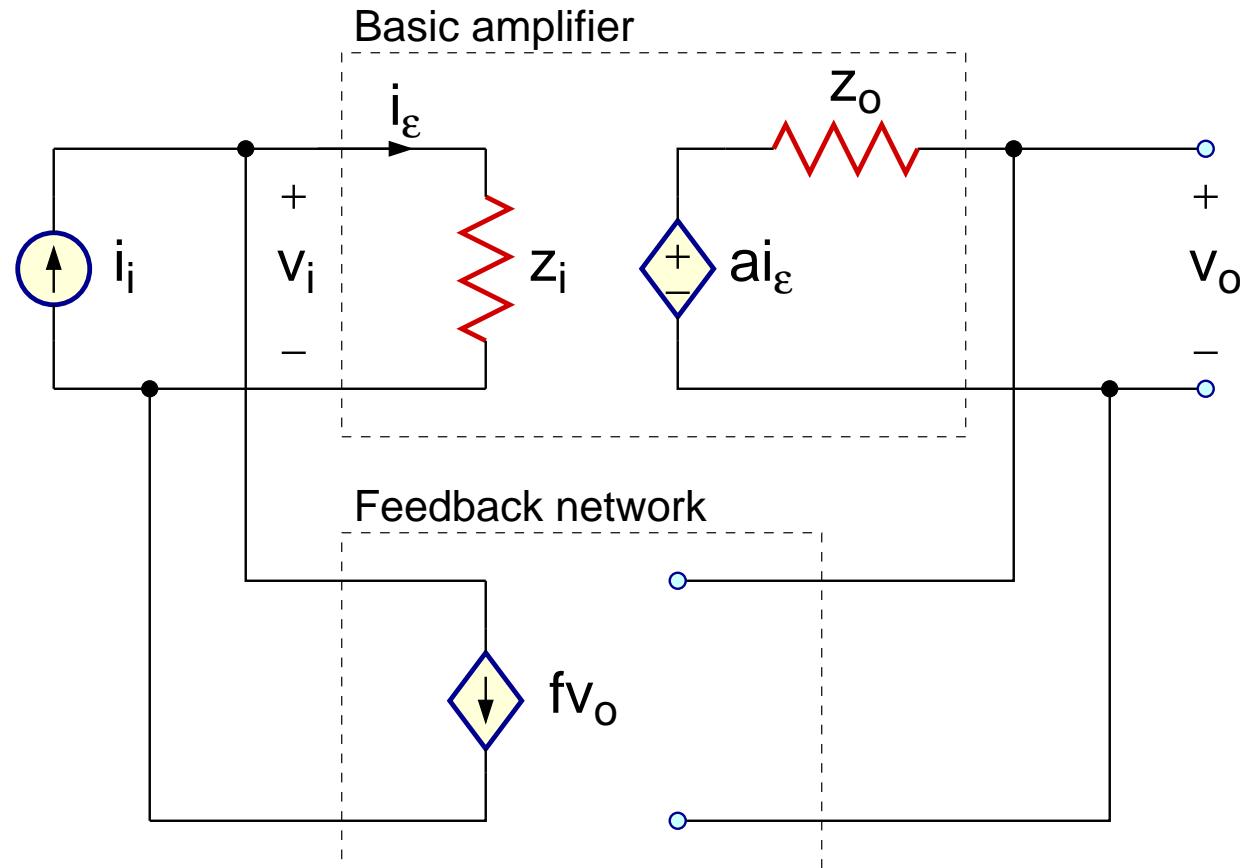


$$\frac{v_o}{i_i} = \frac{a}{1 + af}$$

$$z_i = \frac{z_i}{1 + af}$$

$$z_o = \frac{z_o}{1 + af}$$

Shunt-Shunt

y-parameter representation

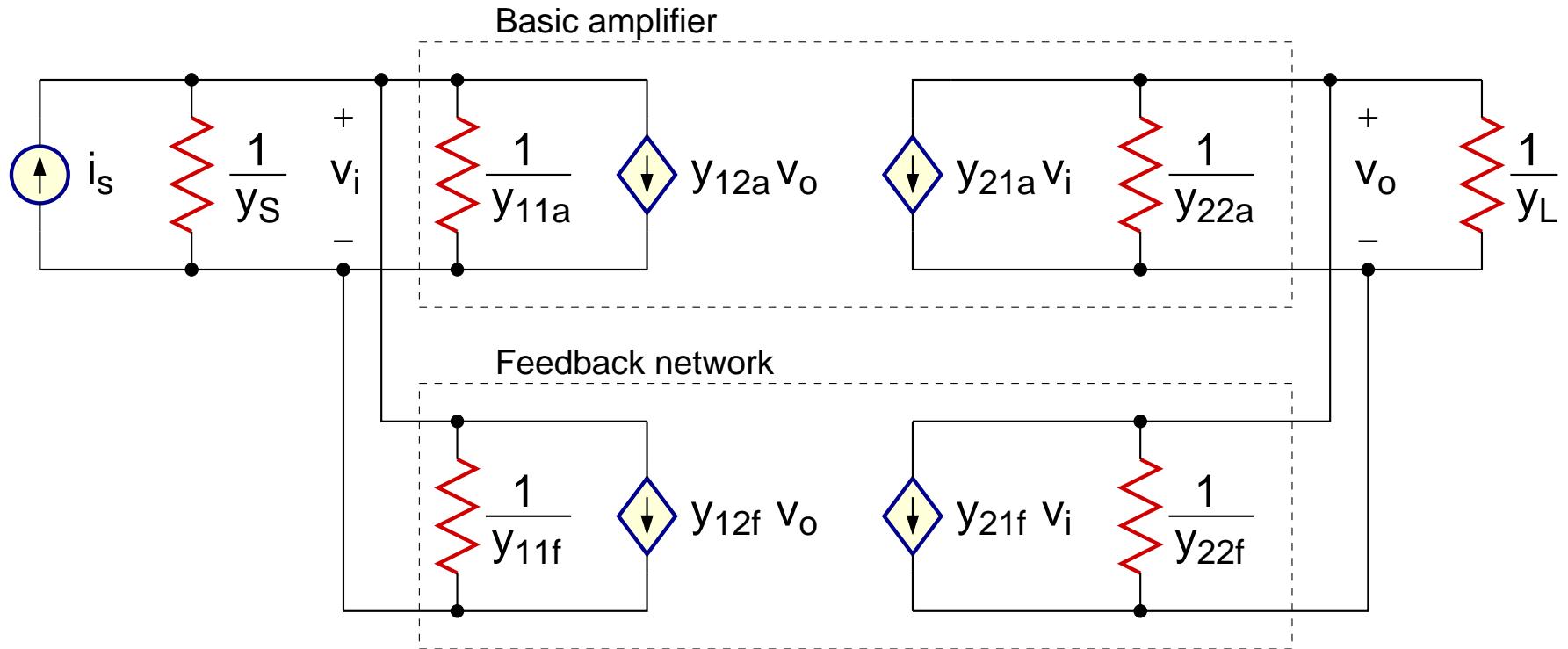


$$|y_{12f}| \gg |y_{12a}|$$

$$|y_{21a}| \gg |y_{21f}|$$

Shunt-Shunt

y-parameter representation - simplified

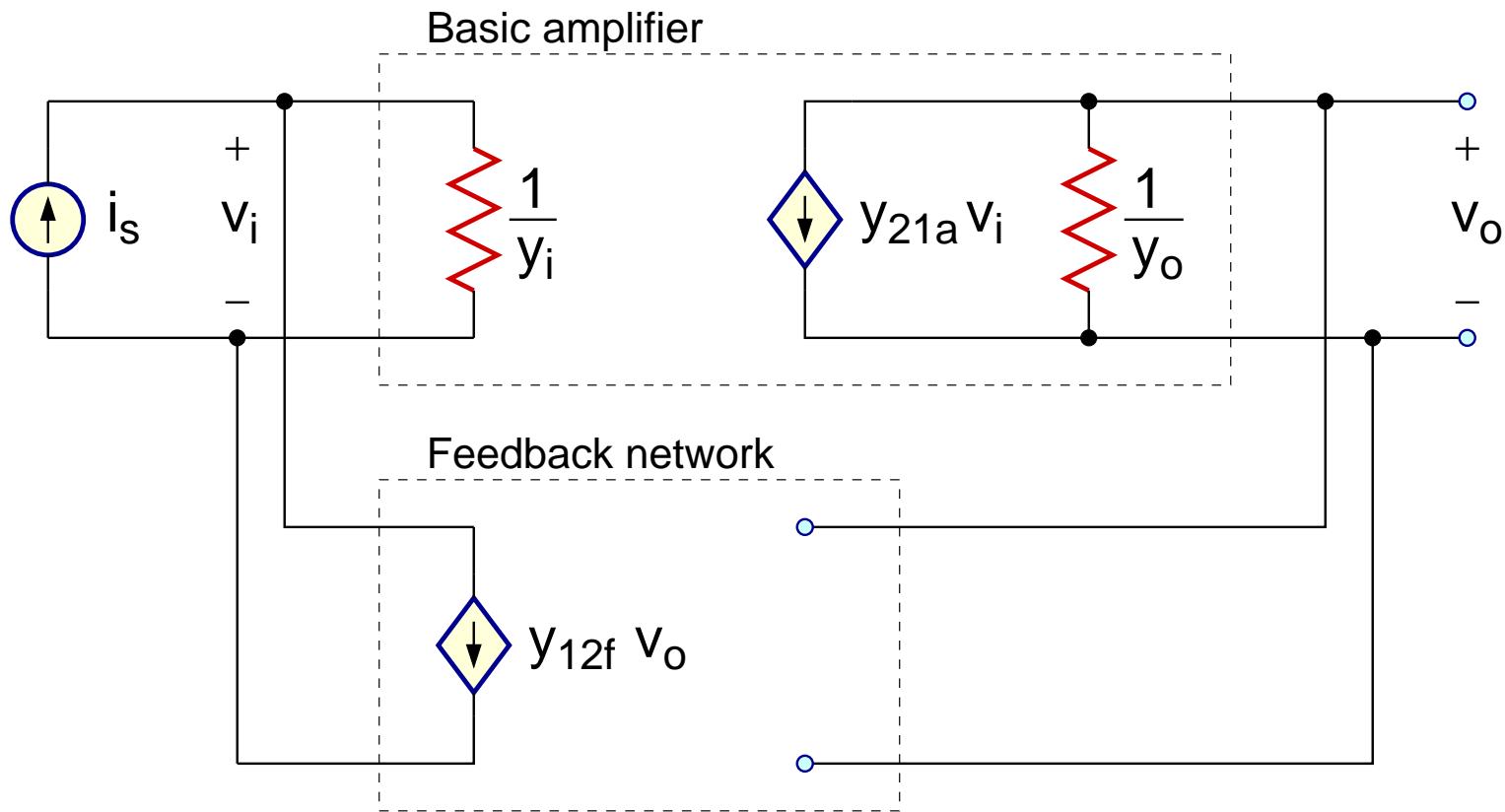


$$y_i = y_s + y_{11a} + y_{11f}$$

$$y_o = y_L + y_{22a} + y_{22f}$$

Shunt-Shunt


y-parameter representation - simplified

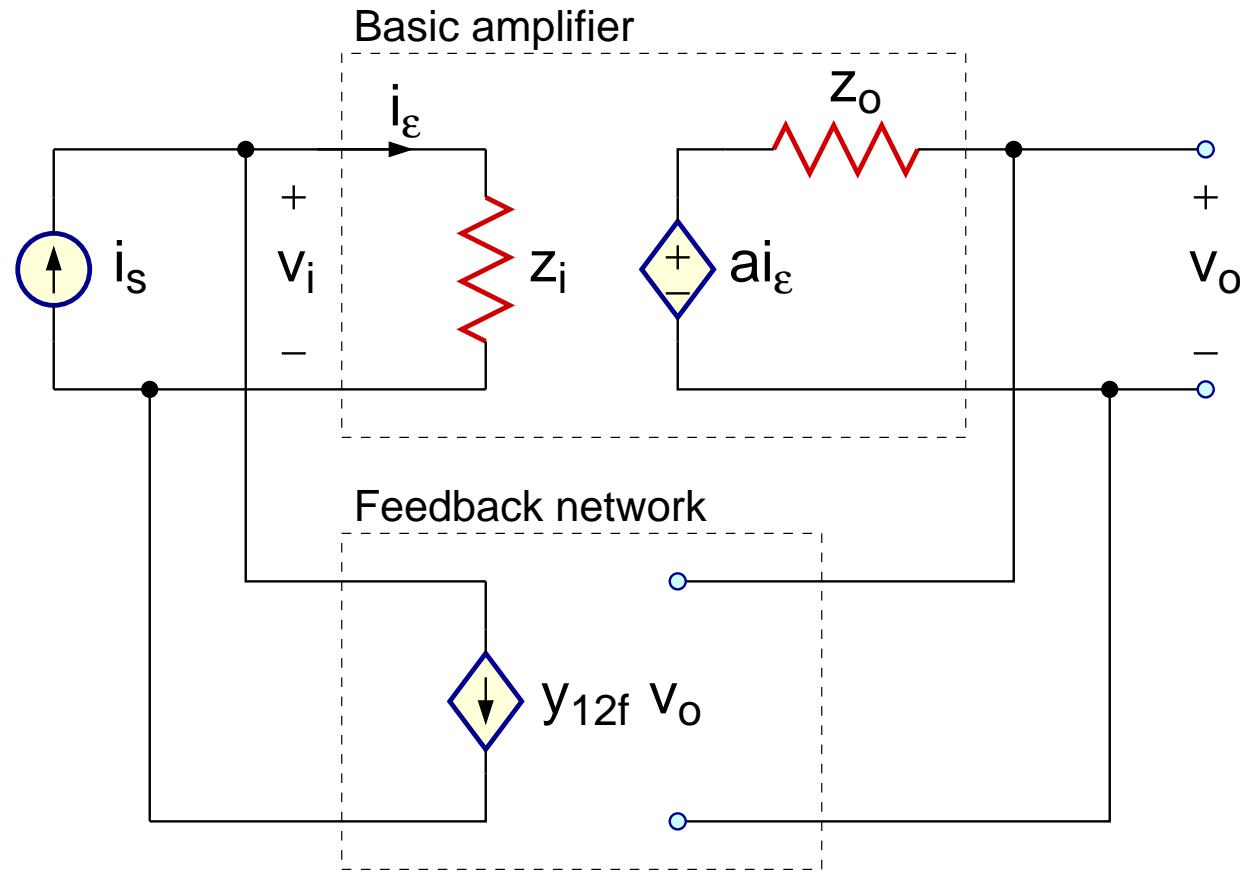

$$a = -\frac{y_{21a}}{y_i y_o} \quad f = y_{12f} \quad z_i = \frac{1}{y_i} \quad z_o = \frac{1}{y_o}$$

Shunt-Shunt

Example

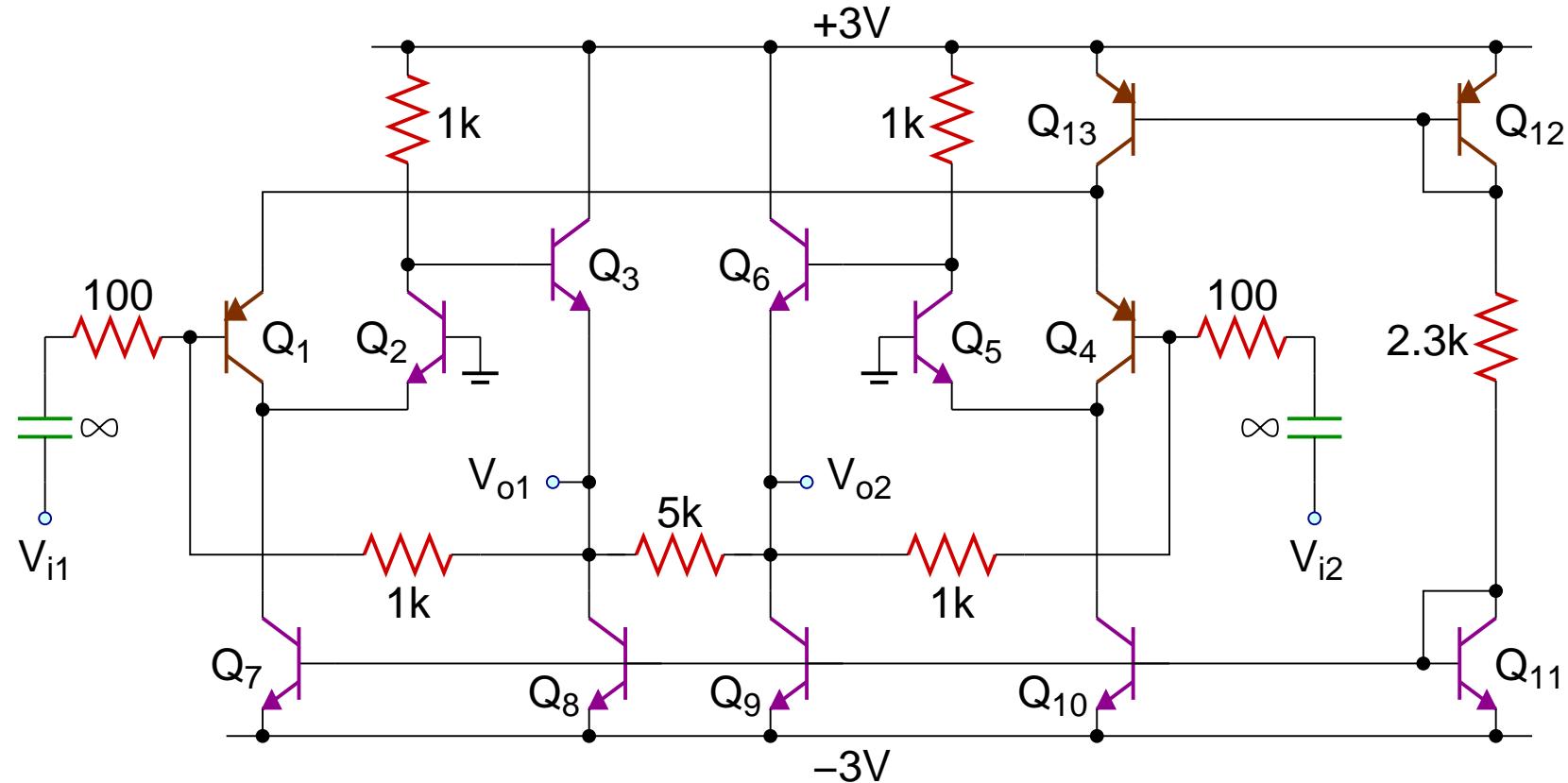


$$V_{i1,dc} = V_{i2,dc} = 0, \quad V_A = \infty, \quad V_T = 25mV, \quad \beta = 100$$

Shunt-Shunt

Example

Differential-mode AC half circuit:

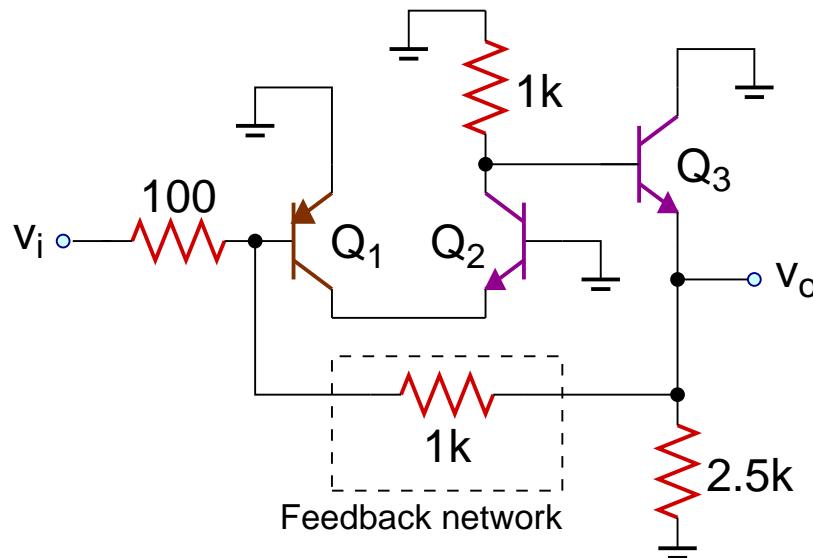

Input: Current


Output: Voltage

$$I_{C1} = 1 \text{ mA}$$

$$I_{C2} = 1 \text{ mA}$$


$$I_{C3} = 2 \text{ mA}$$

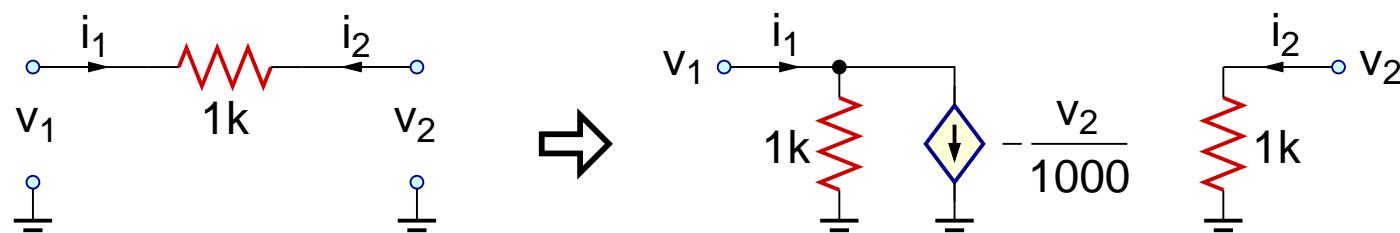y-parameter representation of the feedback network:




Shunt-Shunt

Example

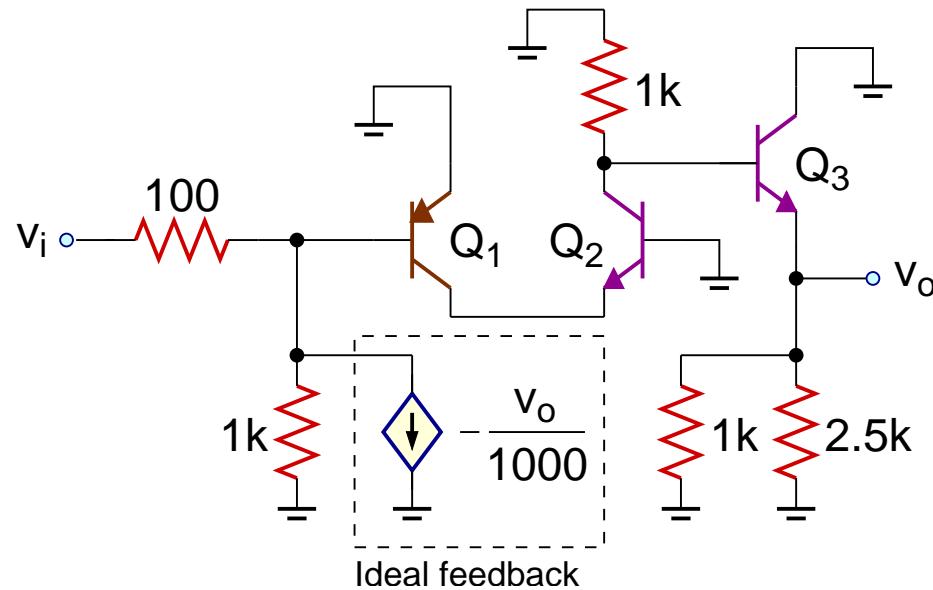

$$f = -0.001$$

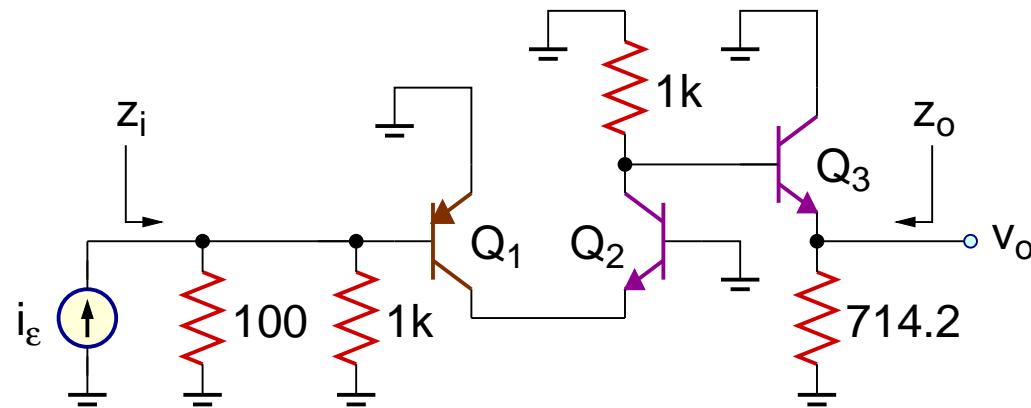



$$a = \frac{v_o}{i_e} = -3403$$

$$z_i = 87.7 \Omega$$

$$z_o = 21.7 \Omega$$

Shunt-Shunt

Example

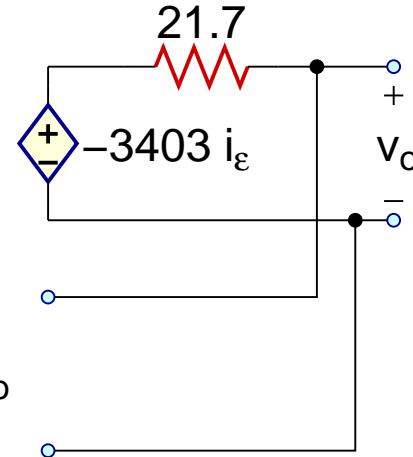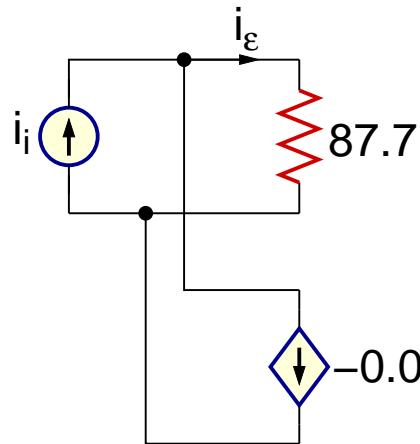


$$i_i = \frac{v_i}{100}$$

$$a = -3403$$

$$f = -0.001$$

$$z_i = 87.7 \Omega$$

$$z_o = 21.7 \Omega$$

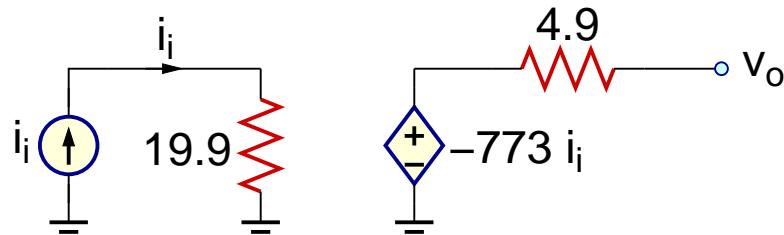

$$A = \frac{v_o}{i_i} = \frac{a}{1+af} = -773$$


$$z_i = \frac{z_i}{1+af} = 19.9 \Omega$$

$$z_o = \frac{z_o}{1+af} = 4.9 \Omega$$

Shunt-Shunt

Example

Voltage-mode equivalent circuit:

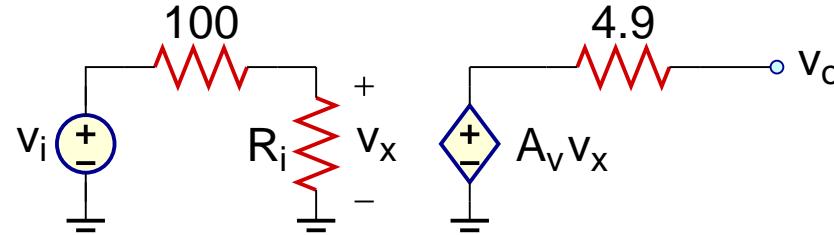

$$100 \parallel R_i = Z_i \Rightarrow \frac{1}{100} + \frac{1}{R_i} = \frac{1}{Z_i} \Rightarrow R_i = 24.8 \Omega$$

$$i_i = \frac{v_i}{100}, \quad v_o = -773 i_i \Rightarrow \frac{v_o}{v_i} = -7.73$$

$$v_o = -7.73 v_i = A_v \frac{R_i}{R_i + 100} v_i \Rightarrow A_v = -38.9$$


$$A_{dm} = -7.73$$

$$R_{id} = 2 \times (100 + 24.8) = 249.6 \Omega$$

$$R_{od} = 2 \times 4.9 = 9.8 \Omega$$

Shunt-Series


Ideal

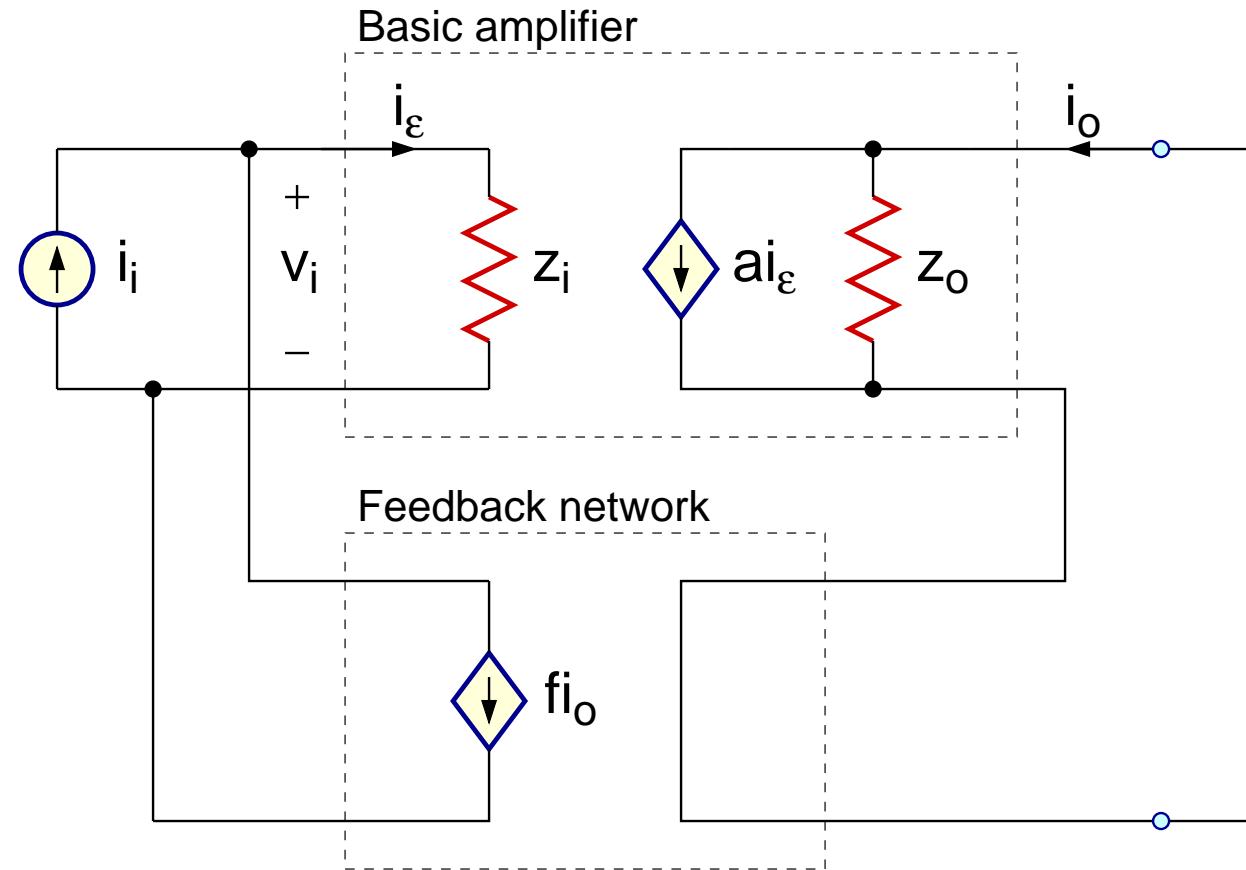

$$\frac{i_o}{i_i} = \frac{a}{1 + af} \quad Z_i = \frac{Z_i}{1 + af} \quad Z_o = Z_o(1 + af)$$

Shunt-Series

g-parameter representation

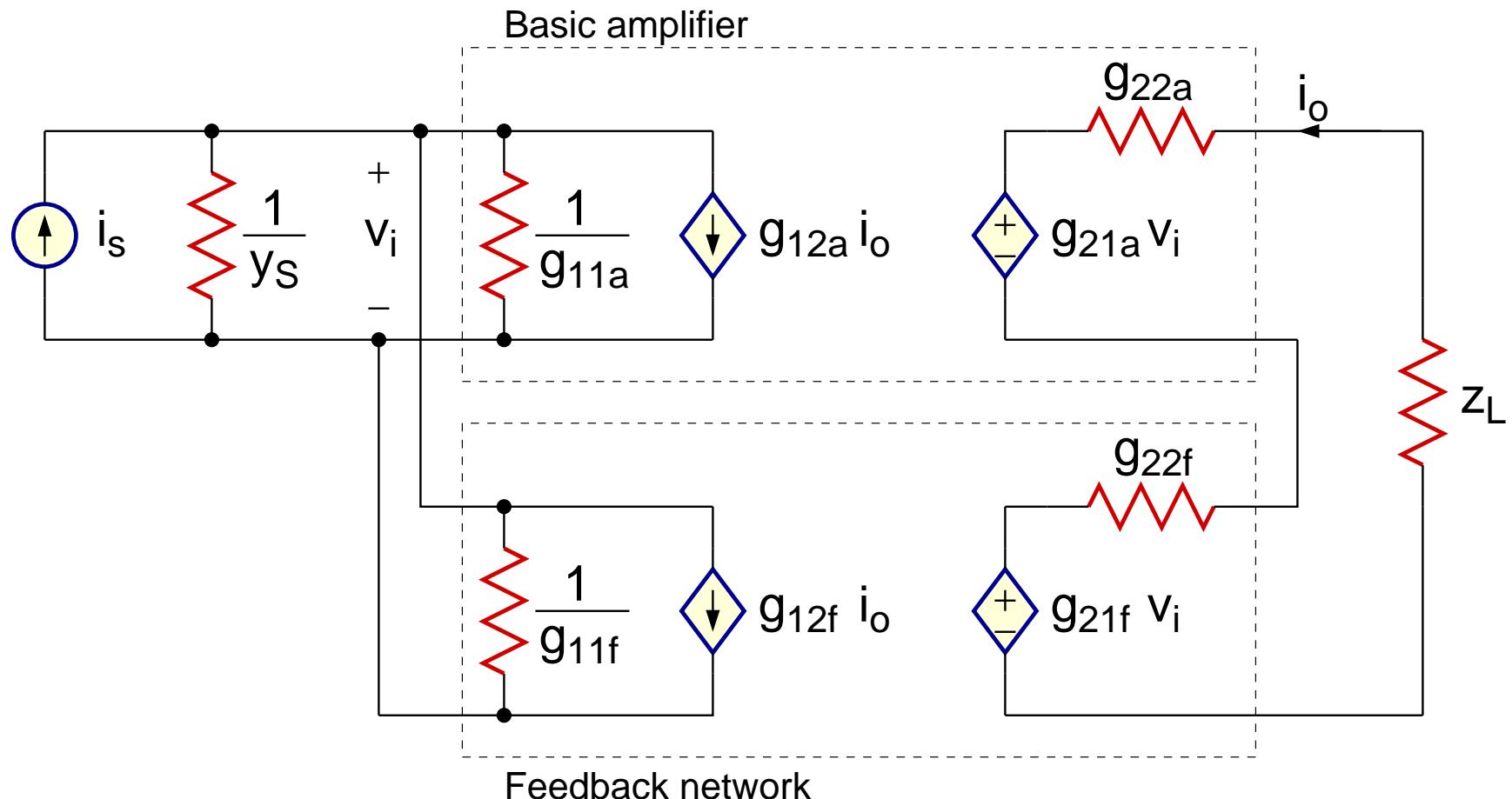


$$|g_{12f}| \gg |g_{12a}|$$

$$|g_{21a}| \gg |g_{21f}|$$

Shunt-Series

g-parameter representation - simplified

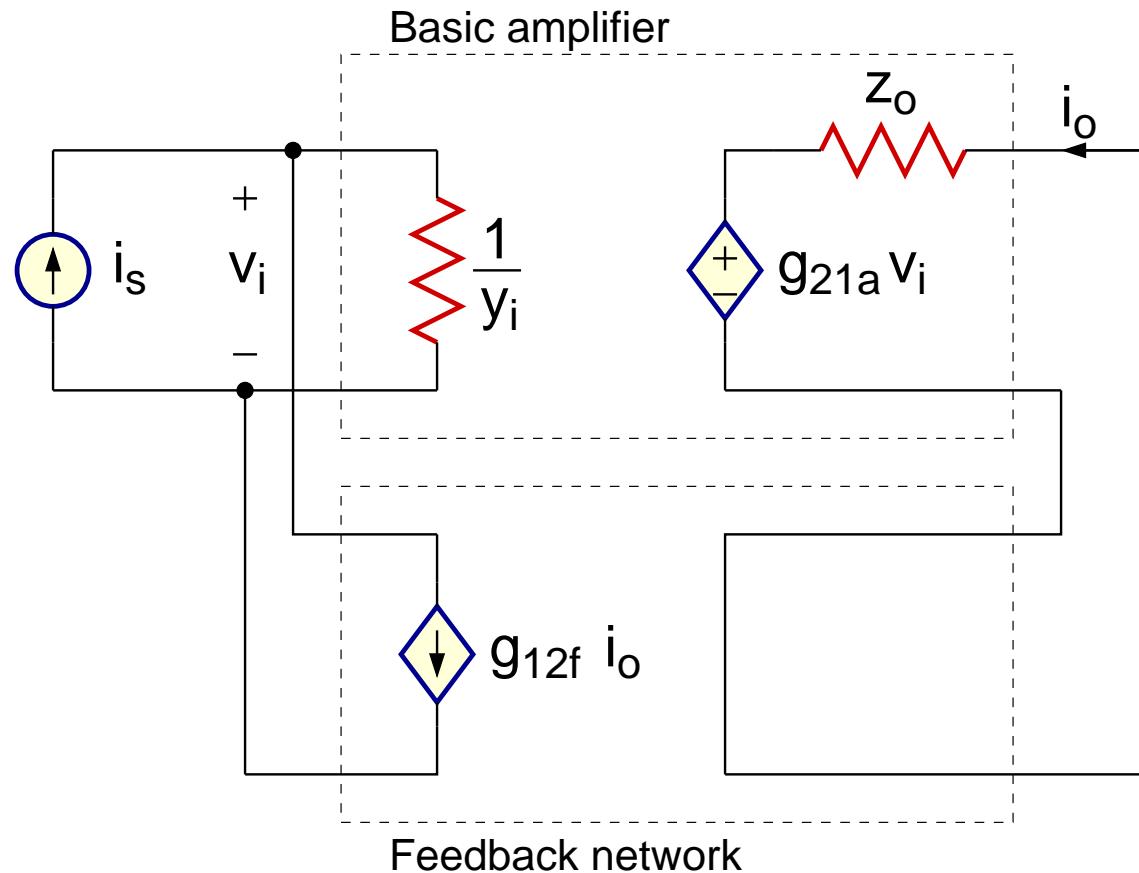


$$y_i = y_s + g_{11a} + g_{11f}$$

$$z_o = z_L + g_{22a} + g_{22f}$$

Shunt-Series


g-parameter representation - simplified

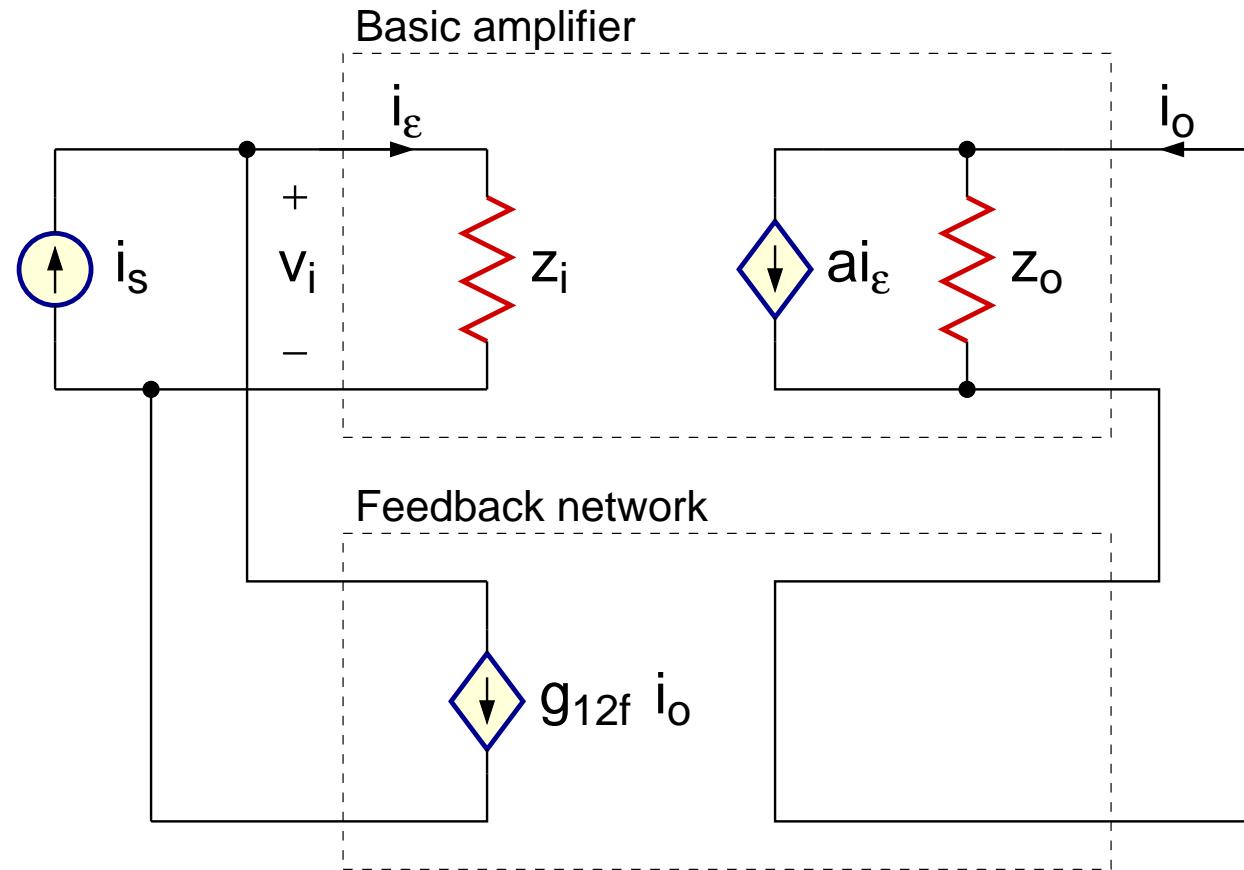

$$a = -\frac{g_{21a}}{y_i z_o} \quad f = g_{12f} \quad z_i = \frac{1}{y_i}$$

Shunt-Series

Example

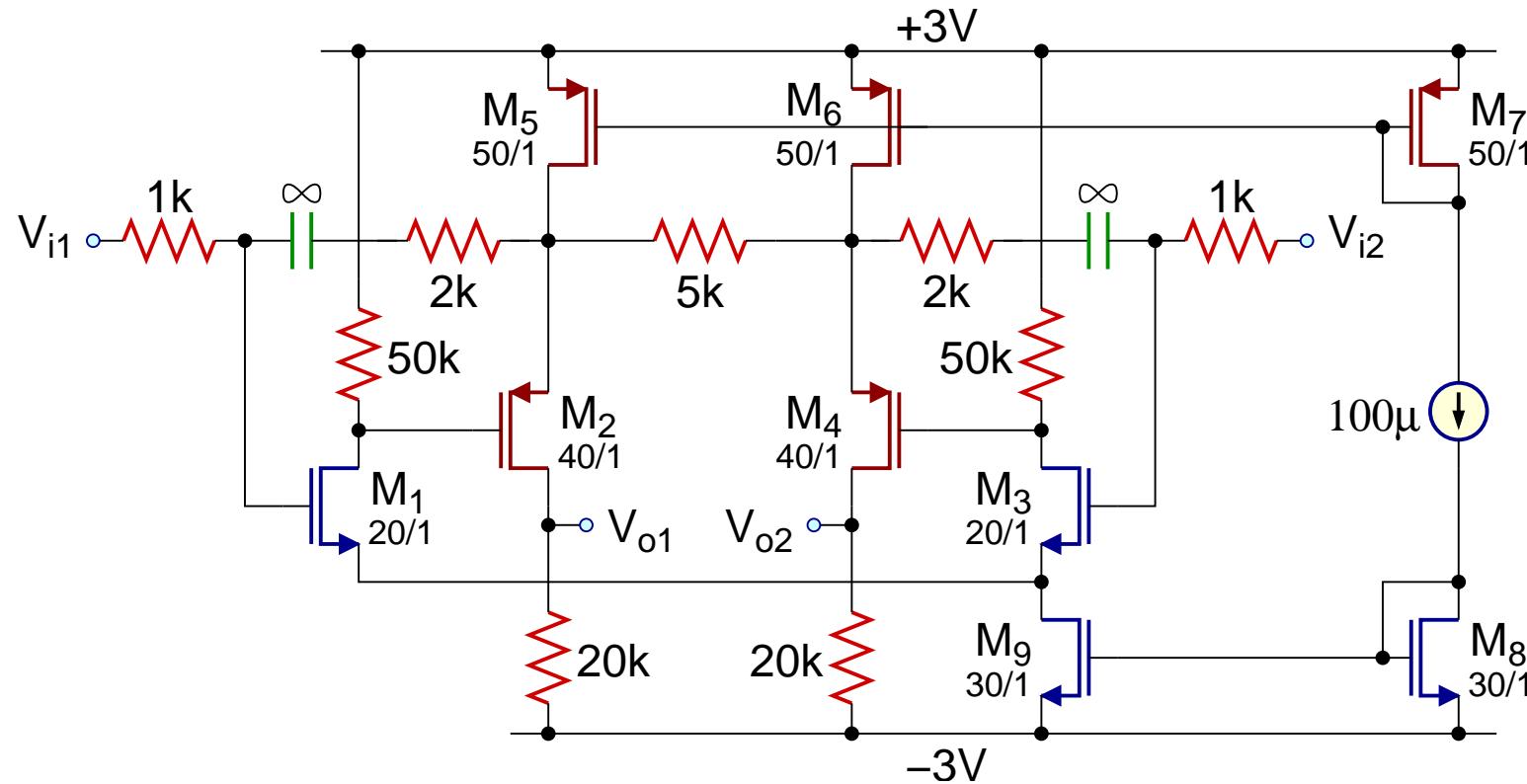


$$k'_n = 190 \text{ } \mu\text{A/V}^2, \text{ } k'_p = 110 \text{ } \mu\text{A/V}^2, \text{ } \lambda_n = \lambda_p = 0$$

$$V_{tn} = 1.5 \text{ V}, V_{tp} = -1.6 \text{ V}, \chi = 0$$

Shunt-Series

Example


Differential-mode AC half circuit:

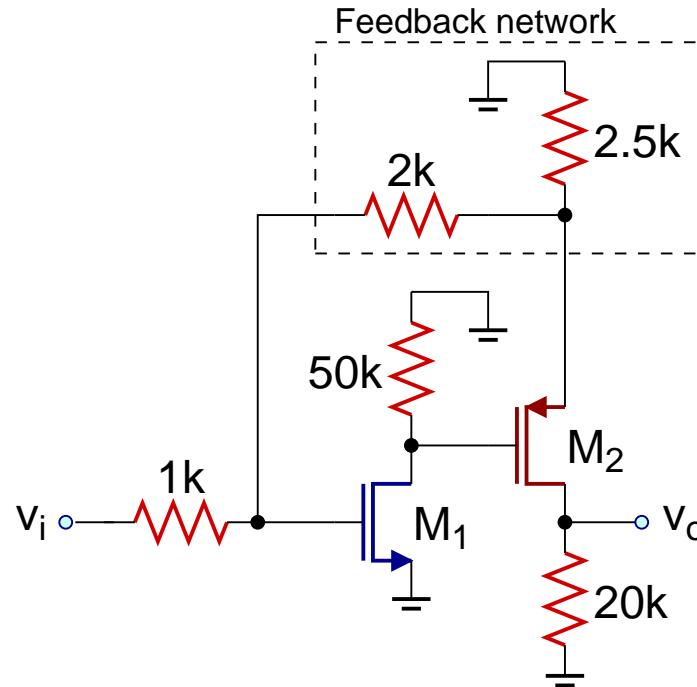

Input: Current
Output: Current


$$I_{D1} = 50 \mu\text{A}$$
$$I_{D2} = 100 \mu\text{A}$$

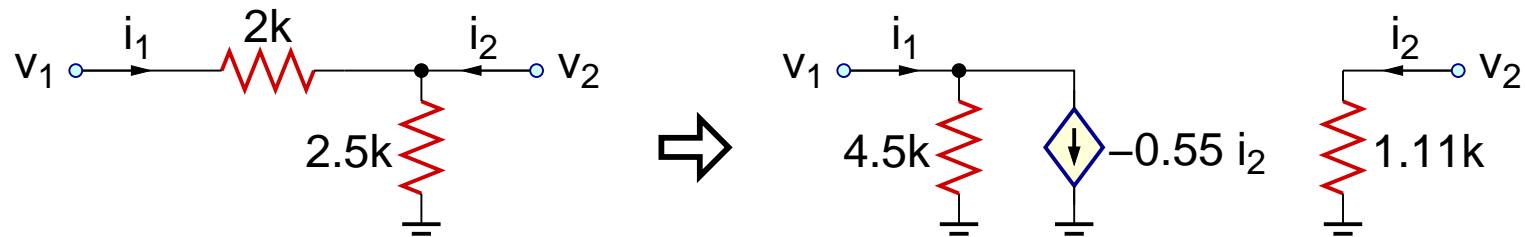g-parameter representation of the feedback network:




Shunt-Series

Example

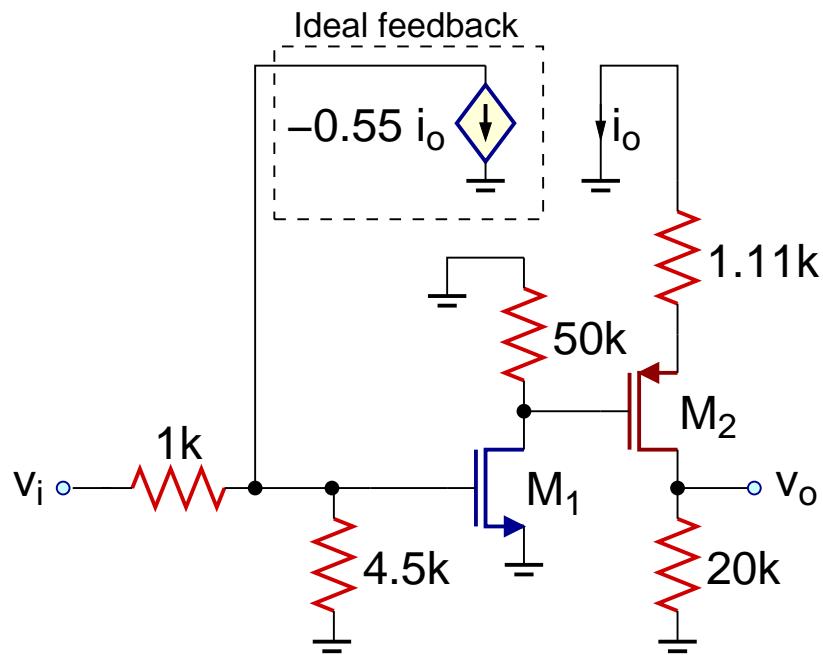

$$f = -0.55$$

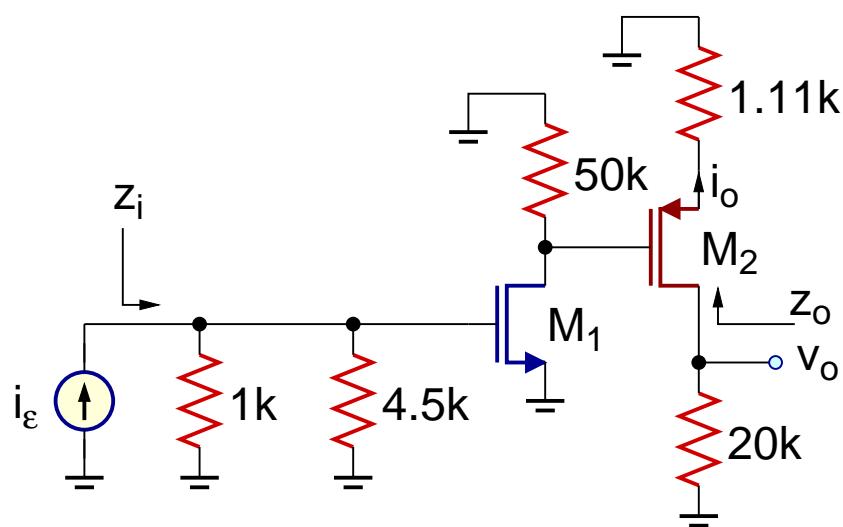


$$a = \frac{i_o}{i_e} = -11.6$$

$$z_i = 818.2 \Omega$$

$$z_o = \infty$$

Shunt-Series

Example

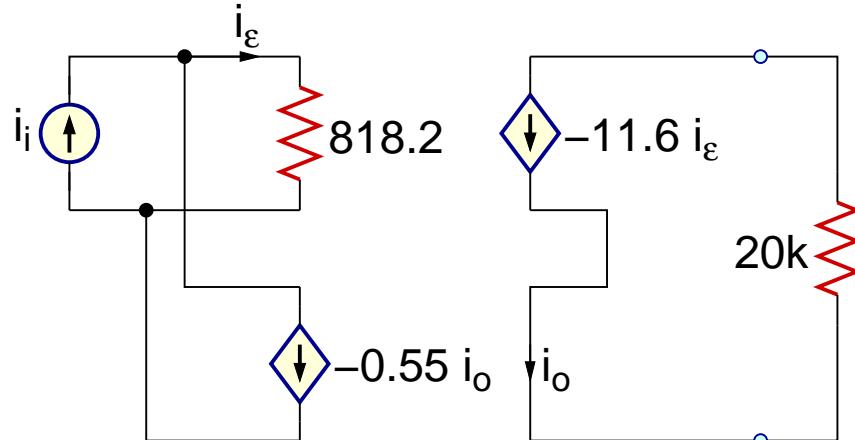


$$i_i = \frac{v_i}{1k}$$

$$a = -11.6$$

$$f = -0.55$$

$$z_i = 818.2 \Omega$$

$$z_o = \infty$$

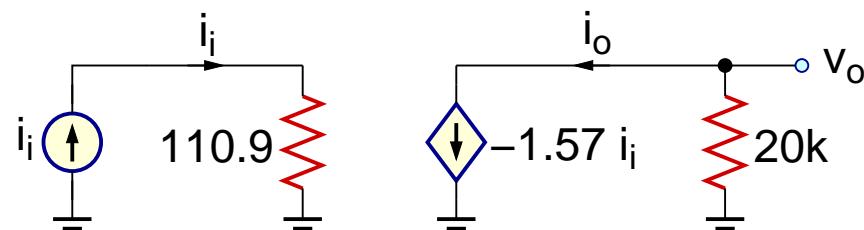

$$A = \frac{i_o}{i_i} = \frac{a}{1+af} = -1.57$$


$$z_i = \frac{z_i}{1+af} = 110.9 \Omega$$

$$z_o = \infty$$

Shunt-Series

Example

Voltage-mode equivalent circuit:

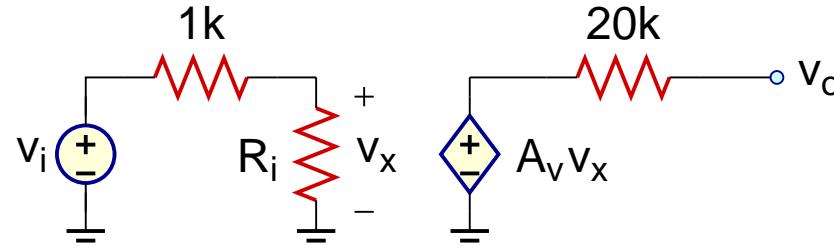

$$1k \parallel R_i = Z_i \Rightarrow \frac{1}{1k} + \frac{1}{R_i} = \frac{1}{Z_i} \Rightarrow R_i = 124.7 \Omega$$

$$i_i = \frac{v_i}{1k}, \quad v_o = -(20k)(-1.57i_i) \Rightarrow \frac{v_o}{v_i} = 31.4$$

$$v_o = 31.4v_i = A_v \frac{R_i}{R_i + 1k} v_i \Rightarrow A_v = 283.2$$


$$A_{dm} = 31.4$$

$$R_{id} = 2 \times (1k + 124.7) = 2.25 \text{ k}\Omega$$

$$R_{od} = 2 \times 20k = 40 \text{ k}\Omega$$

Series-Series


Ideal

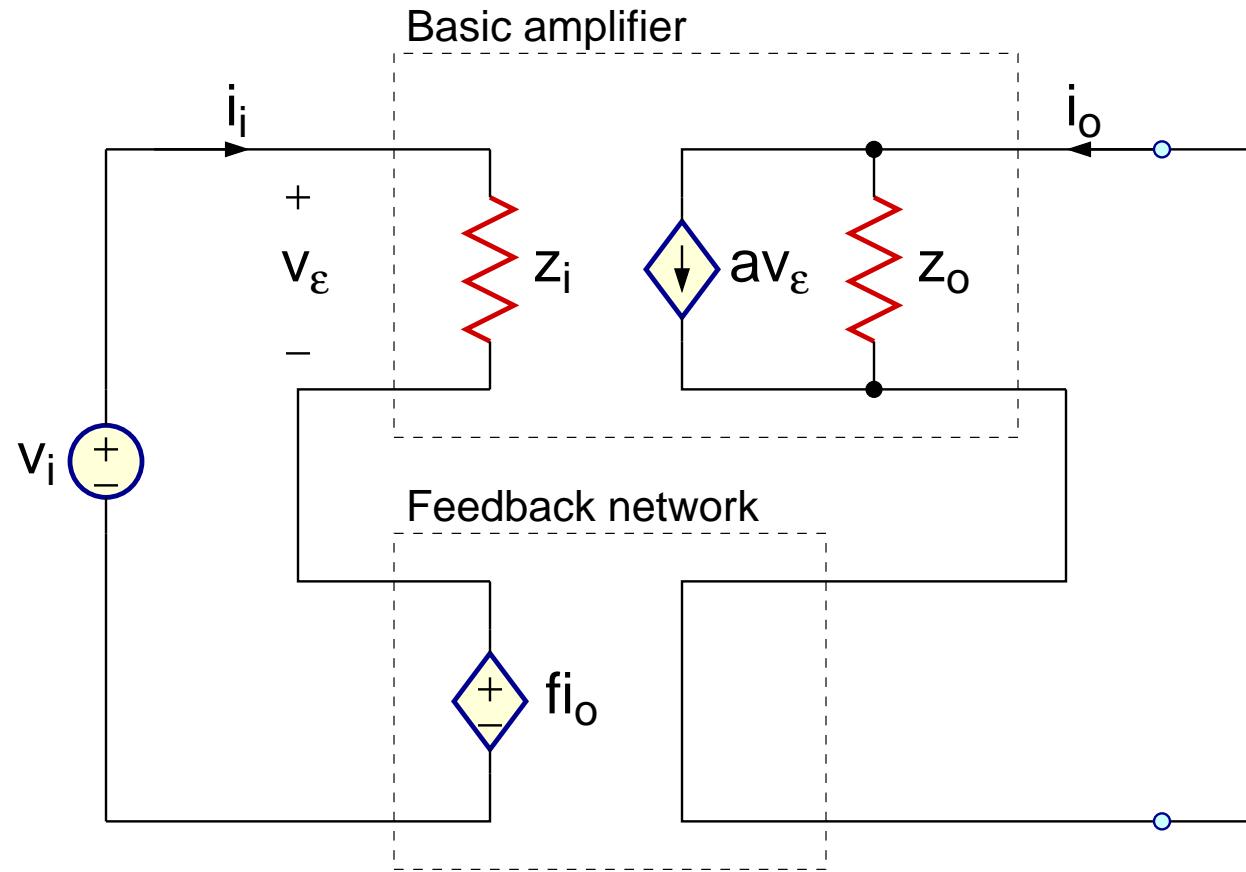

$$\frac{i_o}{v_i} = \frac{a}{1 + af} \quad z_i = z_i(1 + af) \quad z_o = z_o(1 + af)$$

Series-Series


z-parameter representation

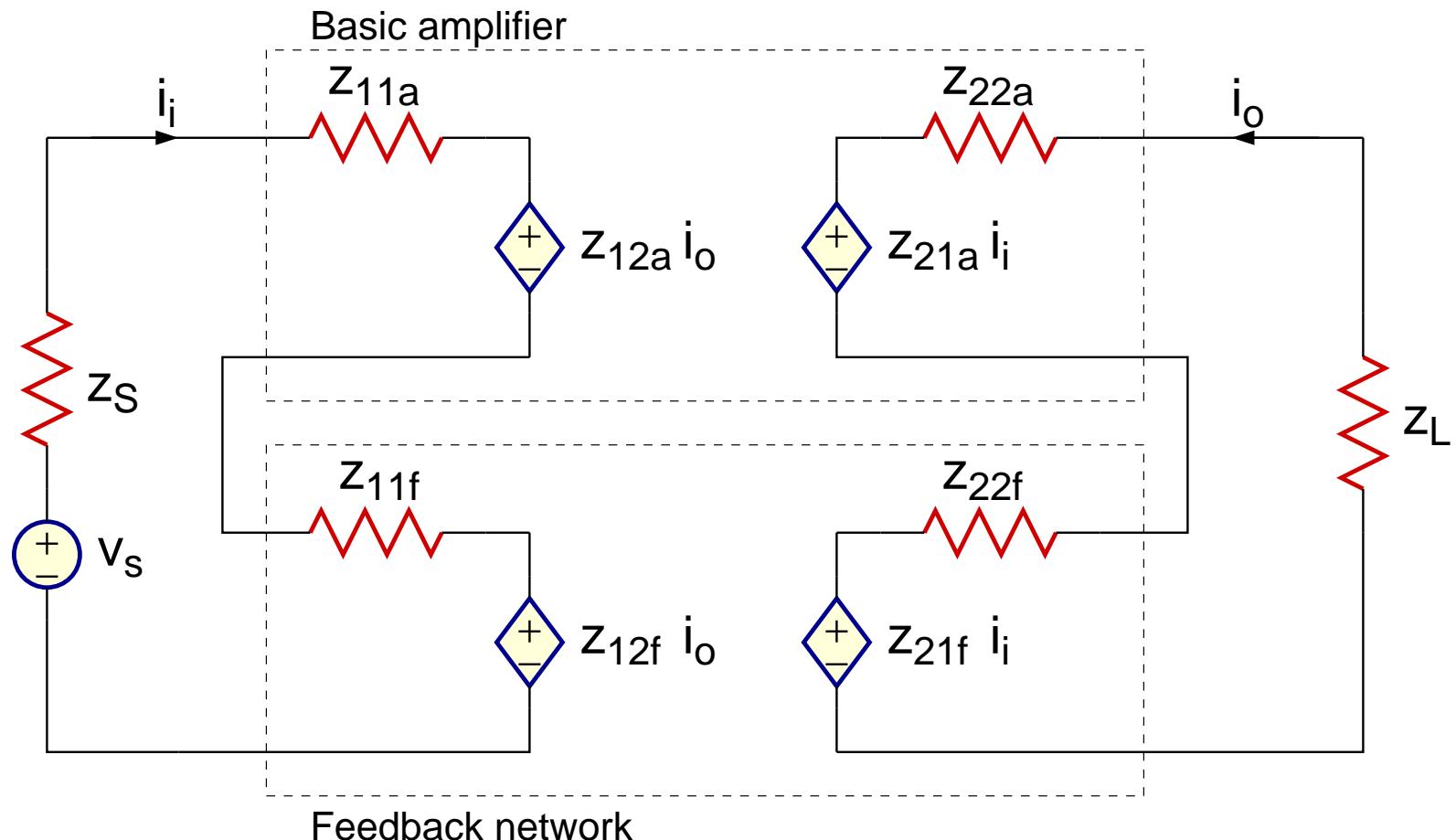

$$|z_{12f}| \gg |z_{12a}| \quad |z_{21a}| \gg |z_{21f}|$$

Series-Series

z-parameter representation - simplified

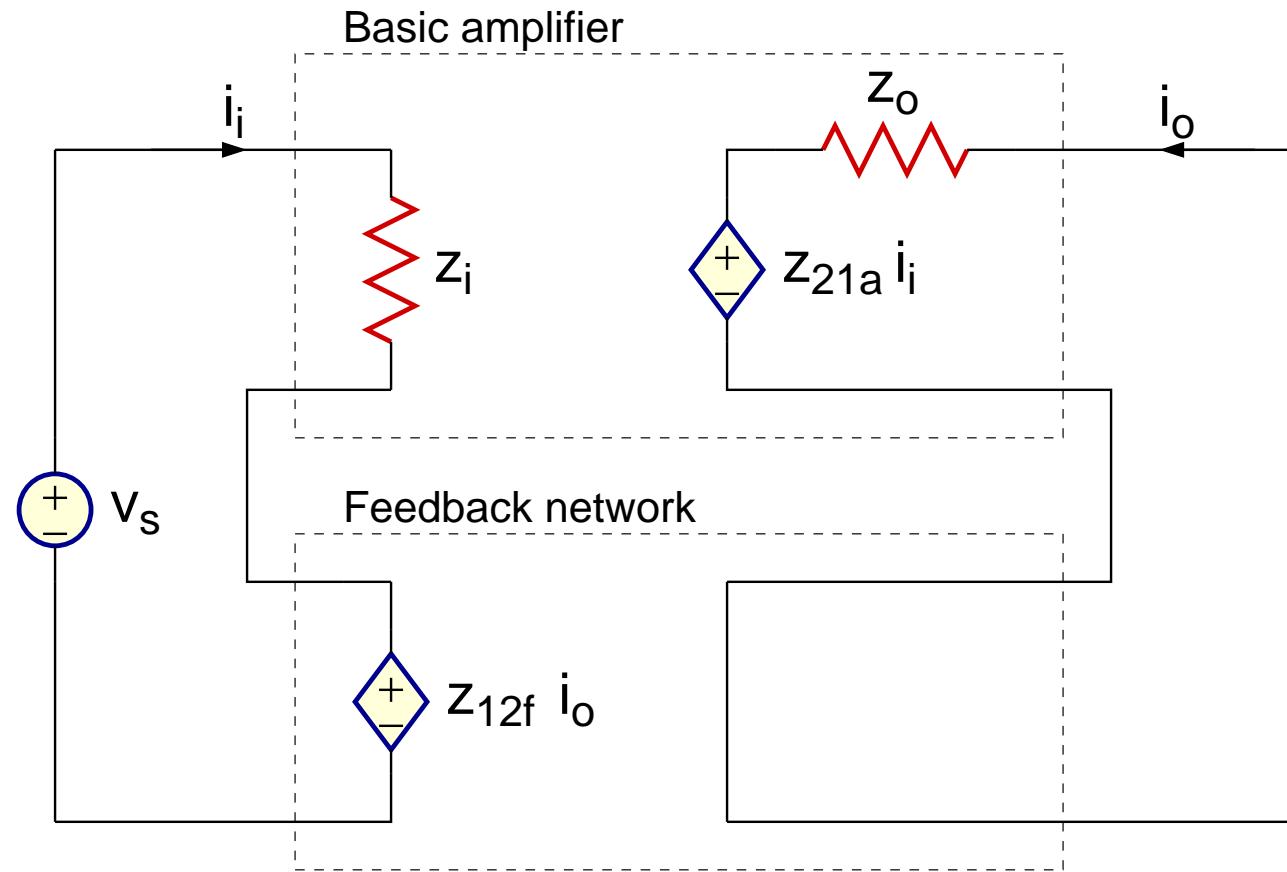


$$z_i = v_s + z_{11a} + z_{11f}$$

$$z_o = z_L + z_{22a} + z_{22f}$$

Series-Series


z-parameter representation - simplified

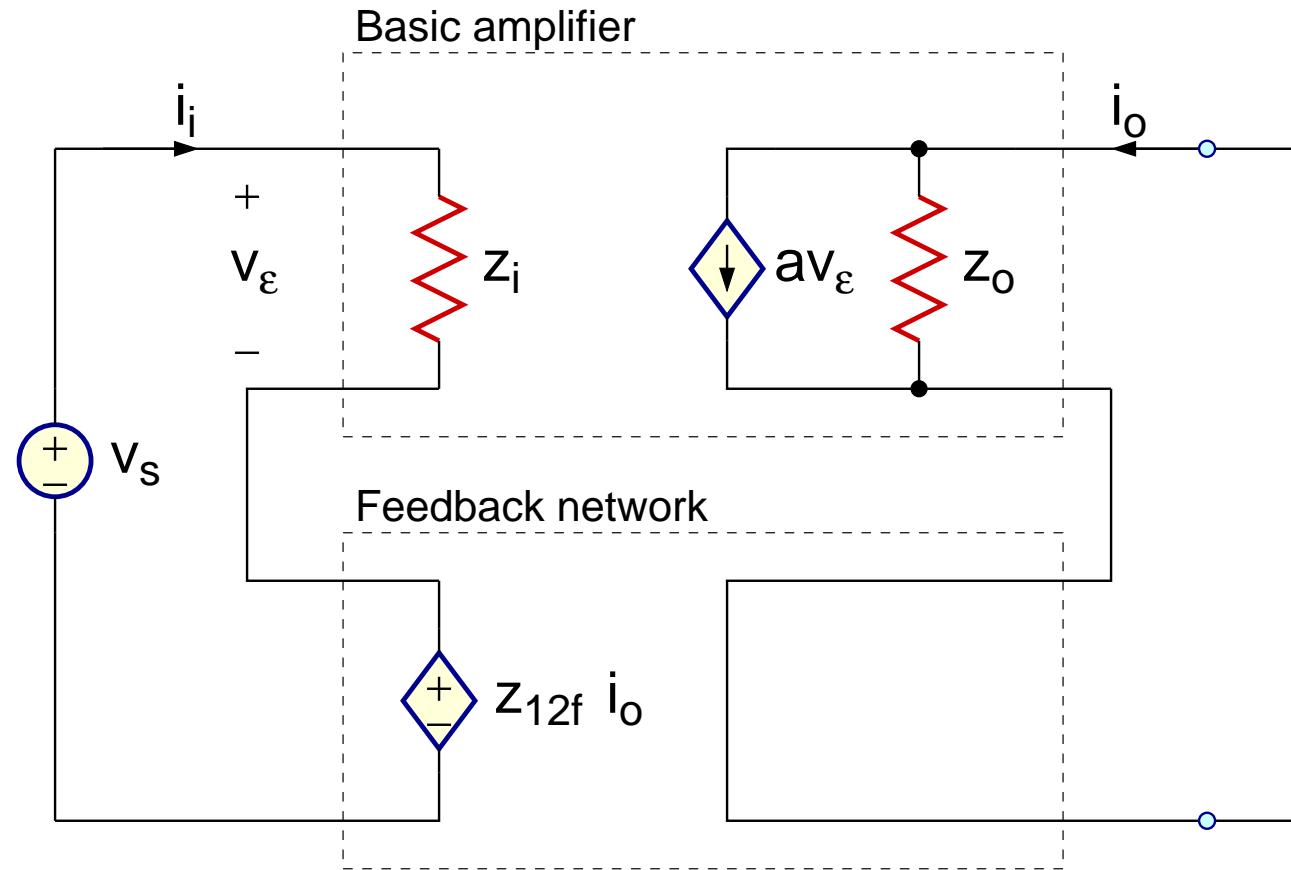

$$a = -\frac{z_{21a}}{z_i z_o} \quad f = z_{12f}$$

Series-Series

Example

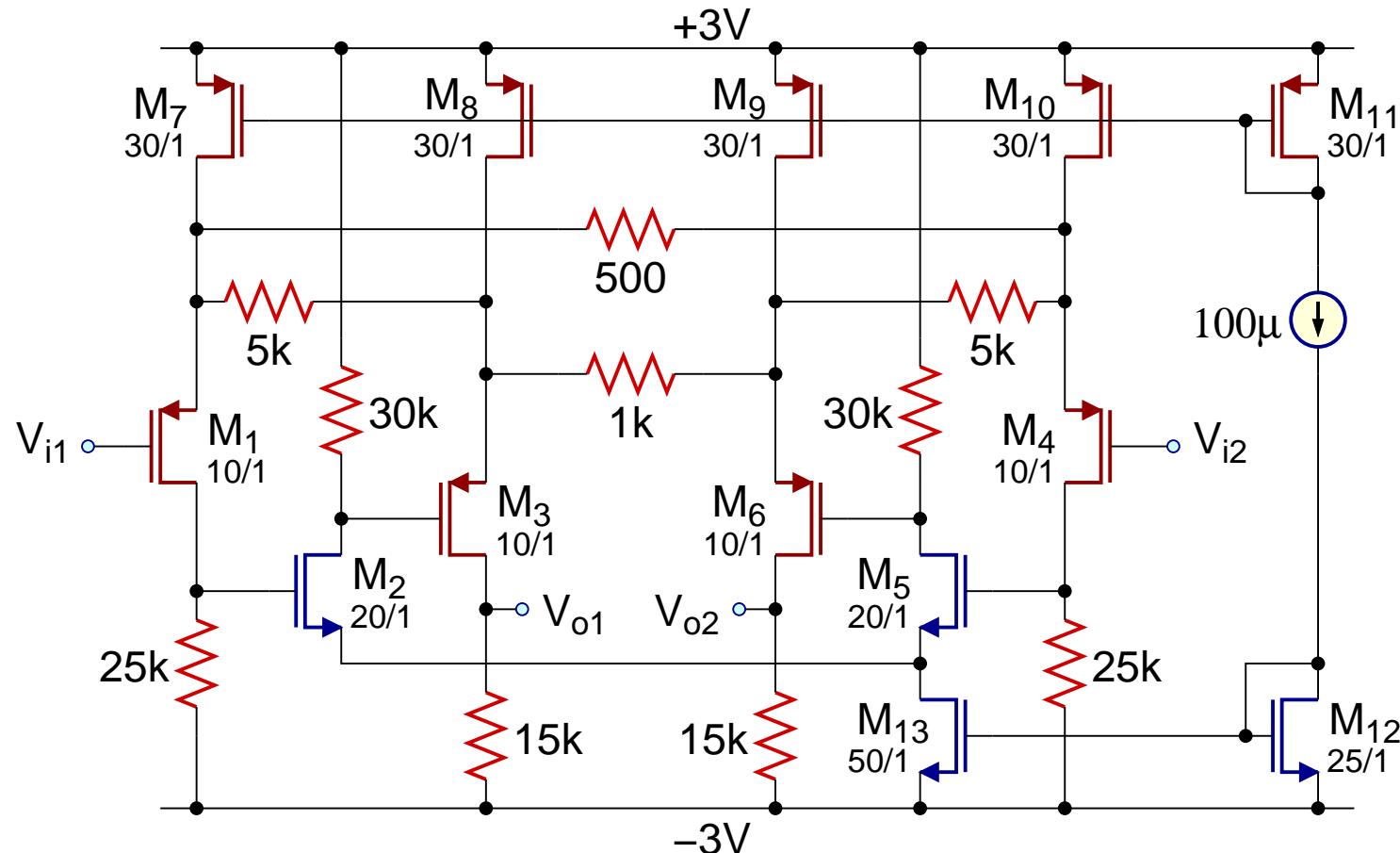


$$k'_n = 190 \mu\text{A}/\text{V}^2, k'_p = 110 \mu\text{A}/\text{V}^2, \lambda_n = \lambda_p = 0$$

$$V_{tn} = 1.5 \text{ V}, V_{tp} = -1.6 \text{ V}, \chi = 0$$

Series-Series

Example

Differential-mode AC half circuit:

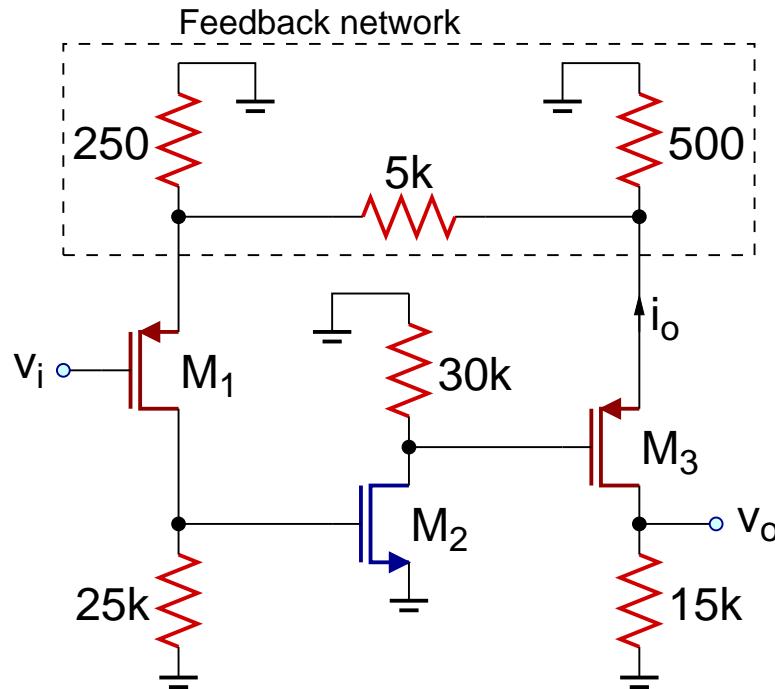


Input: Voltage
Output: Current

$$I_{D1} = 100 \mu\text{A}$$

$$I_{D2} = 100 \mu\text{A}$$


$$I_{D3} = 100 \mu\text{A}$$

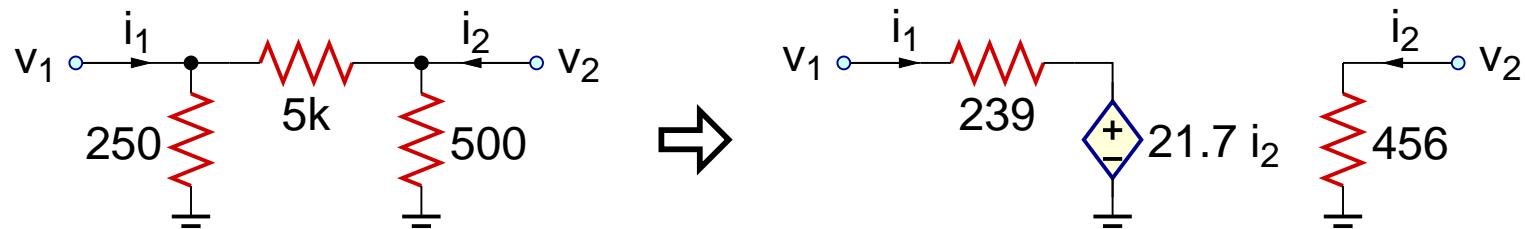Z -parameter representation of the feedback network:




Series-Series

Example

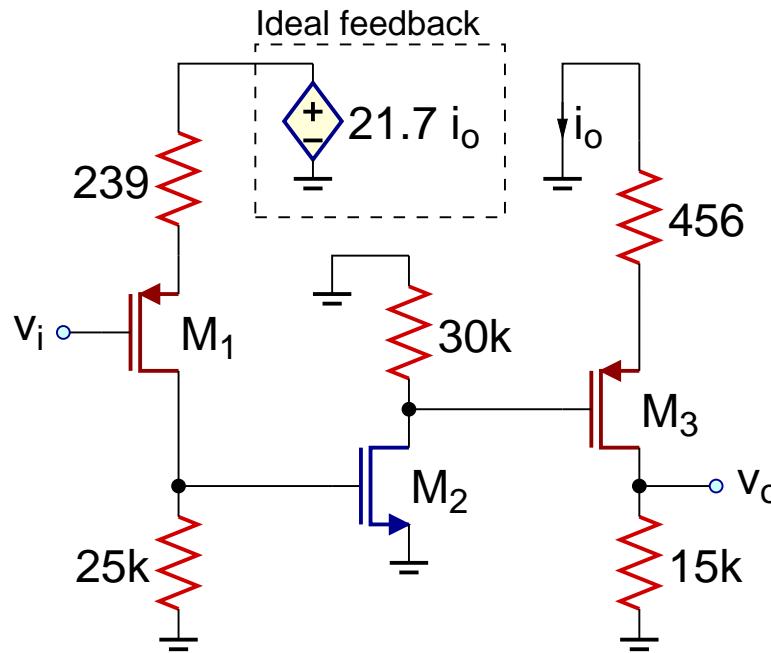

$$f = 21.7$$

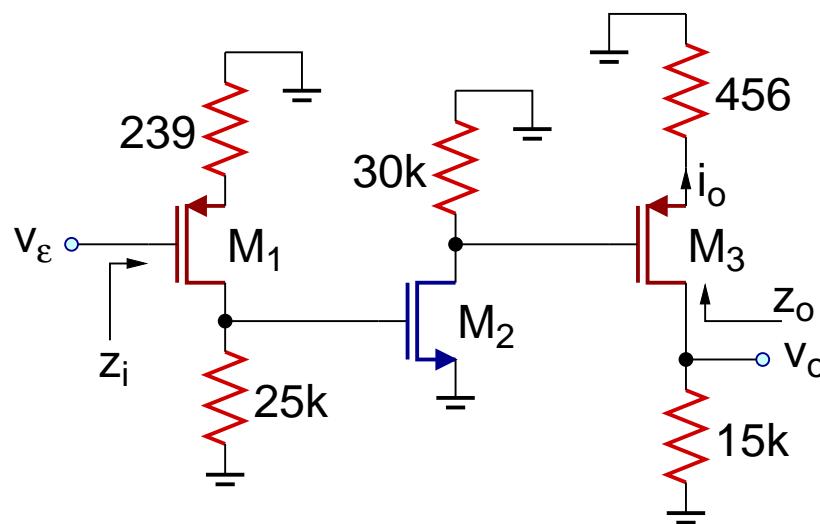


$$a = \frac{i_o}{v_e} = 0.106$$

$$z_i = \infty$$

$$z_o = \infty$$

Series-Series

Example

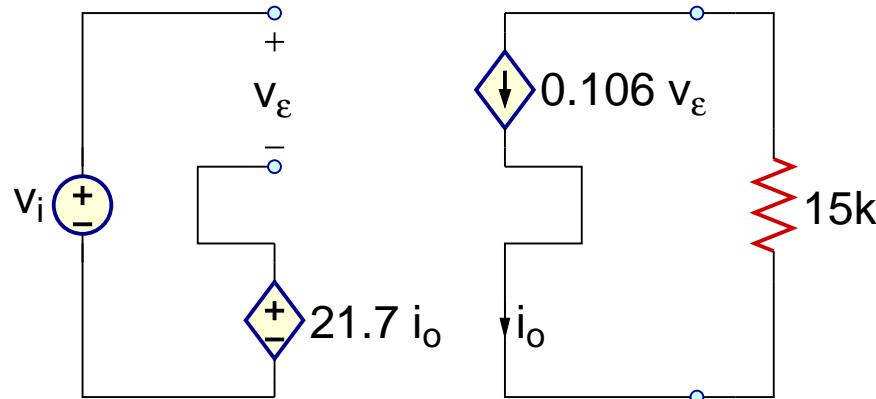


$$a = 0.106$$

$$f = 21.7$$

$$z_i = \infty$$

$$z_o = \infty$$

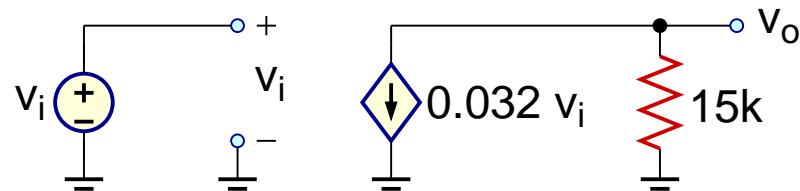

$$A = \frac{i_o}{v_i} = \frac{a}{1+af} = 0.032$$


$$z_i = \infty$$

$$z_o = \infty$$

Series-Series

Example

Voltage-mode equivalent circuit:

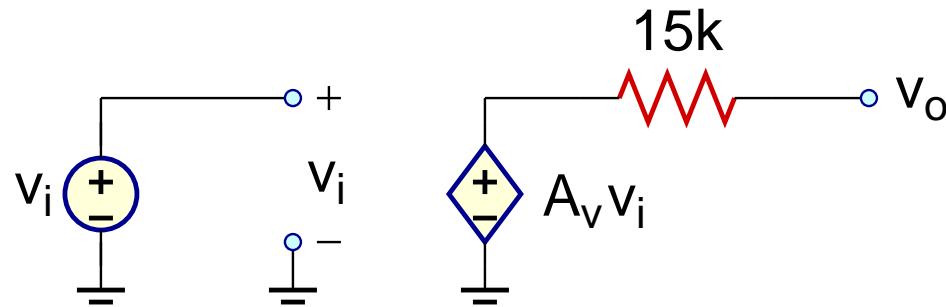

$$v_o = -(15k)(0.032v_i) = A_v v_i \Rightarrow A_v = -480$$

$$A_{dm} = -480$$

$$R_{id} = \infty$$

$$R_{od} = 2 \times 15k = 30 \text{ k}\Omega$$