


# **ECEN 326**

## **Electronic Circuits**

Frequency Response


*Dr. Aydın İlker Karşılıyan*

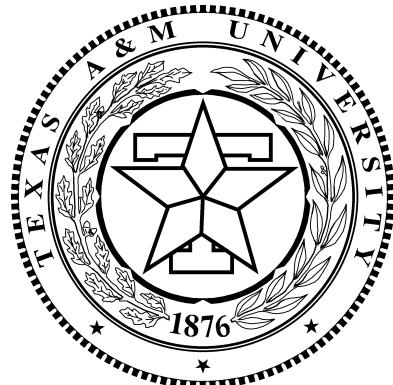Texas A&M University  
Department of Electrical and Computer Engineering



# High-Frequency Model

BJT & MOS

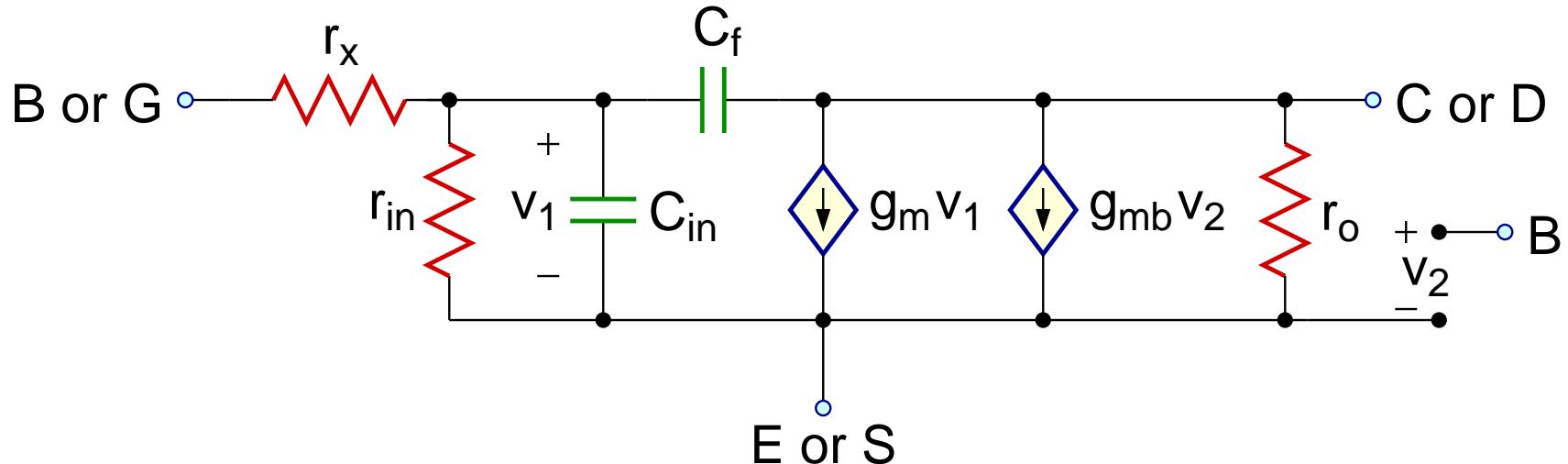

General	BJT	MOS
$r_x$	$r_b$	0
$r_{in}$	$r_\pi$	$\infty$
$C_{in}$	$C_\pi$	$C_{gs}$
$C_f$	$C_\mu$	$C_{gd}$
$r_o$	$r_o$	$r_o$
$g_m$	$g_m$	$g_m$
$g_{mb}$	0	$g_{mb}$

$$\text{BJT: } C_\pi = C_b + C_{je} = \tau_F g_m + C_{je}$$

$$C_\mu = \frac{C_{\mu o}}{\left(1 - \frac{V}{\psi_o}\right)^n}$$

$$C_\pi \gg C_\mu$$




$$\text{MOS: } C_{gs} = \frac{2}{3}WL C_{ox}$$

$C_{gd}$  : Overlap capacitance

$$C_{gs} \gg C_{gd}$$

# Transition Frequency, $f_T$

BJT & MOS

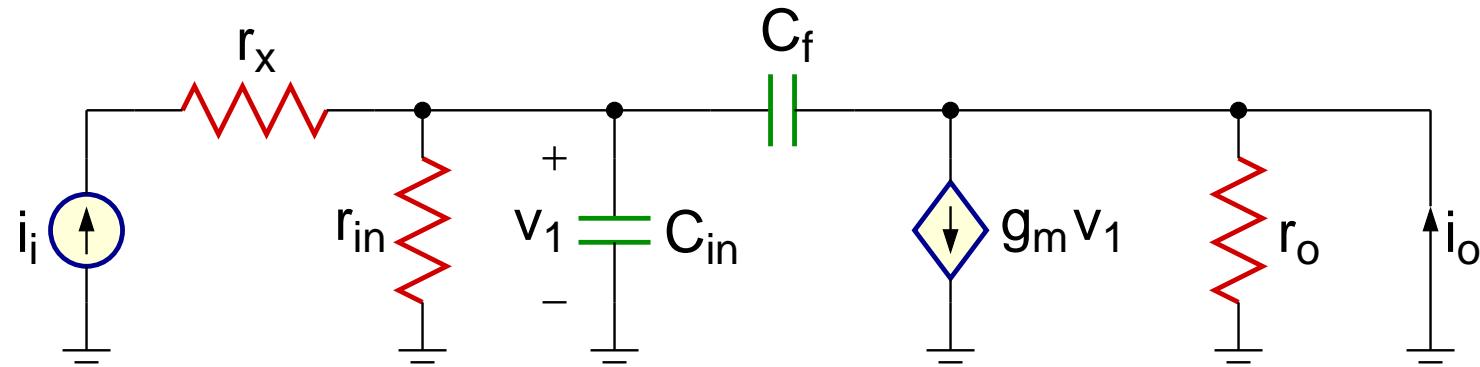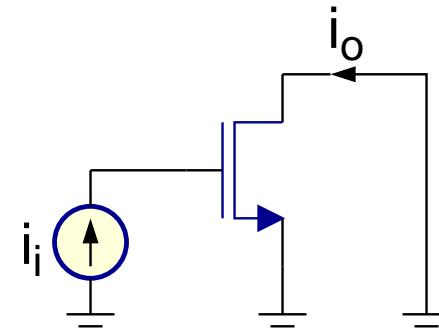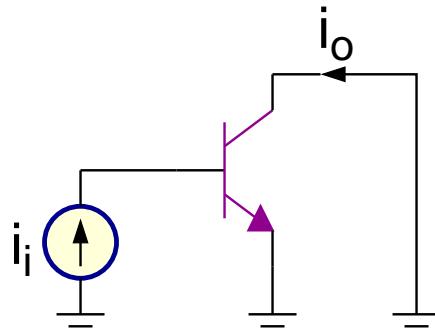

$$\frac{i_o(s)}{i_i} \approx \frac{g_m r_{in}}{1 + r_{in}(C_{in} + C_f)s}$$

# Transition Frequency, $f_T$

BJT & MOS

$$\frac{i_o}{i_i}(j\omega) \approx \frac{g_m r_{in}}{1 + r_{in}(C_{in} + C_f)j\omega}$$

At high frequencies:




$$\frac{i_o}{i_i}(j\omega) \approx \frac{g_m}{(C_{in} + C_f)j\omega}$$

$$\left| \frac{i_o}{i_i}(j\omega) \right|_{\omega=\omega_T} = 1 \Rightarrow \frac{g_m}{(C_{in} + C_f)\omega_T} = 1$$

$$\boxed{\omega_T = \frac{g_m}{C_{in} + C_f}, \quad f_T = \frac{\omega_T}{2\pi}}$$

$$\text{BJT: } \omega_T = \frac{g_m}{C_\pi + C_\mu}$$
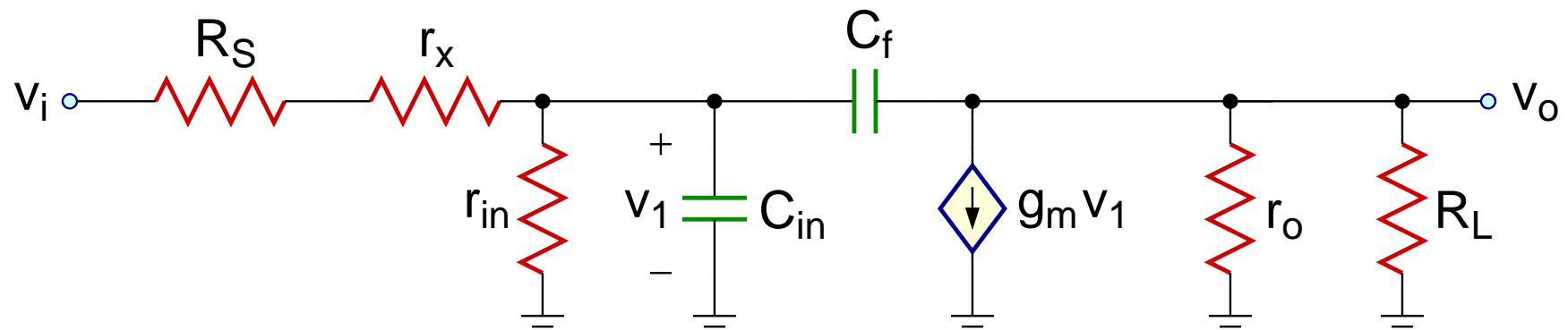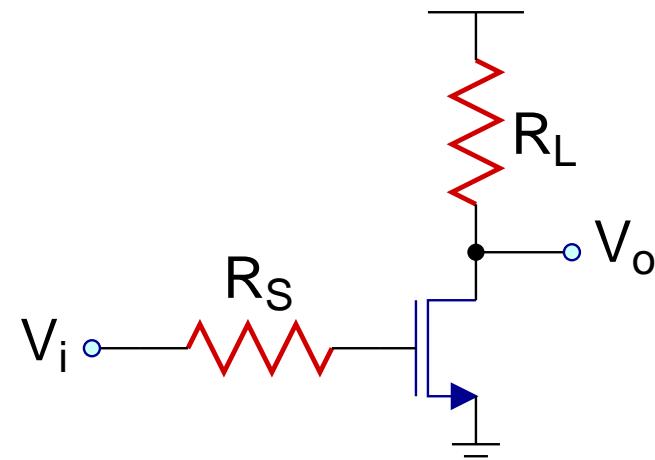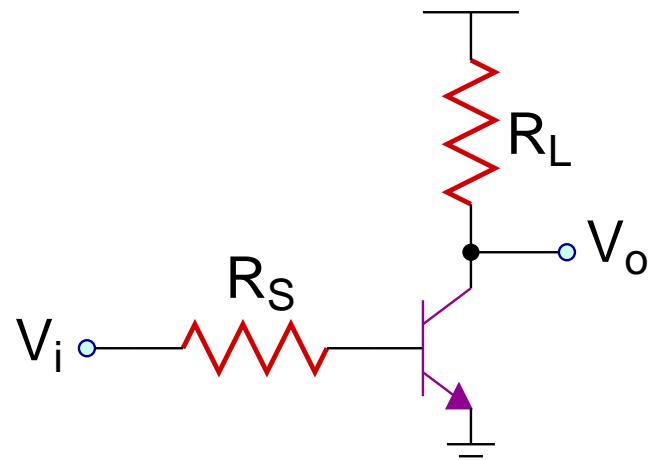
$$\text{MOS: } \omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$



$$\frac{v_o}{v_i}(s) = K \frac{1 - s \frac{C_f}{g_m}}{1 + a_1 s + a_2 s^2}$$

$$K = -\frac{g_m R_{OL} R}{R_s + r_x} = -g_m R_{OL} \frac{r_{in}}{R_s + r_x + r_{in}}$$

$$a_1 = C_f R_{OL} + C_f R + C_{in} R + g_m R_{OL} R C_f$$

$$a_2 = R_{OL} R C_f C_{in}$$

$$R = (R_s + r_x) \parallel r_{in}$$

$$R_{OL} = r_o \parallel R_L$$

$$D(s) = 1 + a_1 s + a_2 s^2 = \left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right)$$


$$|p_2| \gg |p_1| \Rightarrow p_1 \approx -\frac{1}{a_1}, \quad p_2 \approx -\frac{a_1}{a_2}$$

$$p_1 = -\frac{1}{R \left( C_{in} + C_f \left( 1 + g_m R_{OL} + \frac{R_{OL}}{R} \right) \right)}$$

$$p_2 = -\left( \frac{1}{R_{OL} C_f} + \frac{1}{R C_{in}} + \frac{1}{R_{OL} C_{in}} + \frac{g_m}{C_{in}} \right)$$

$$N(s) = 1 - \frac{s}{z_1} \Rightarrow z_1 = \frac{g_m}{C_f}$$


# Miller Approximation

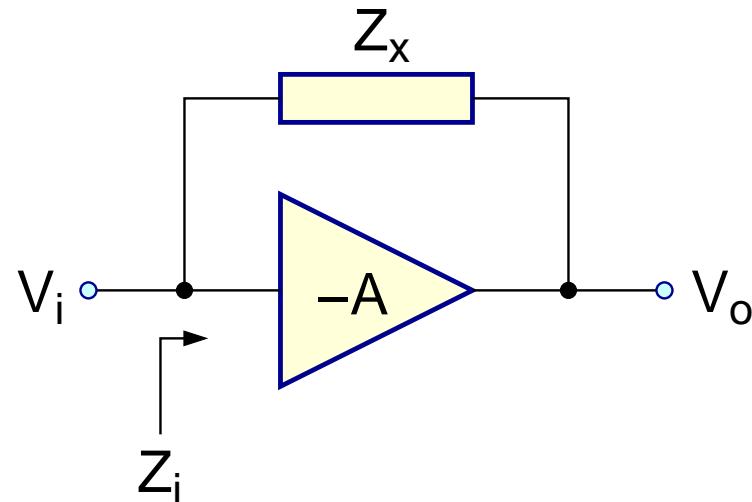


$$Z_i = \frac{V_i}{I_i} = \frac{V_i}{V_i - V_o} = \frac{V_i}{V_i - (-AV_i)} = \frac{Z_x V_i}{Z_x + (A+1)V_i} = \frac{Z_x}{(A+1) + Z_x/A}$$

$$Z_x = \frac{1}{sC} \Rightarrow Z_i = \frac{1}{s(A+1)C} = \frac{1}{sC'} , \quad C' = (A+1)C$$


# Miller Capacitance

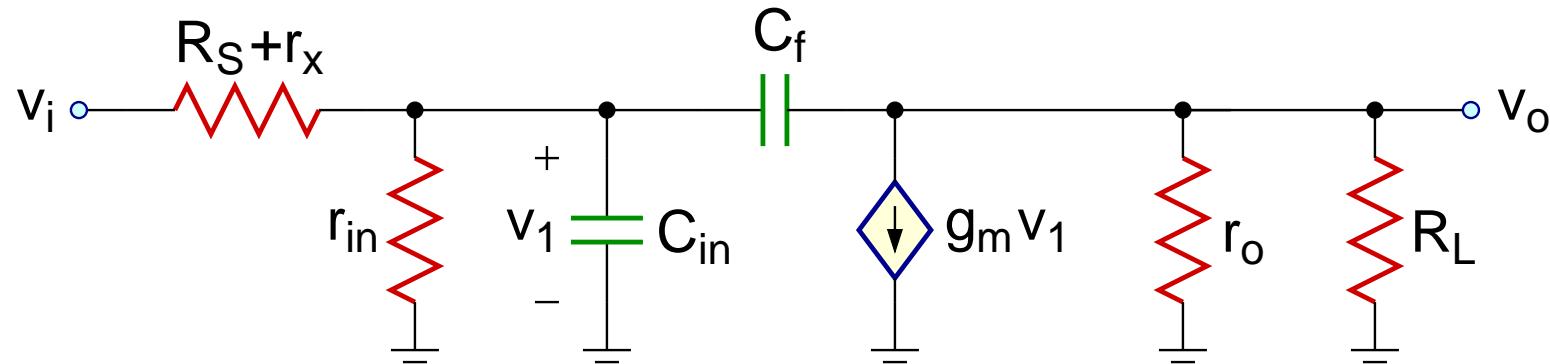

↓ Miller Approximation ↓

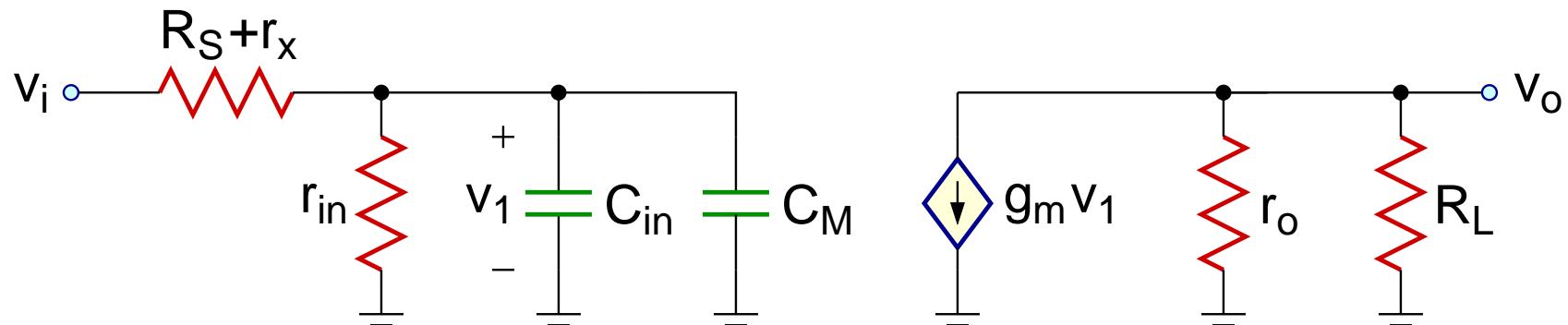
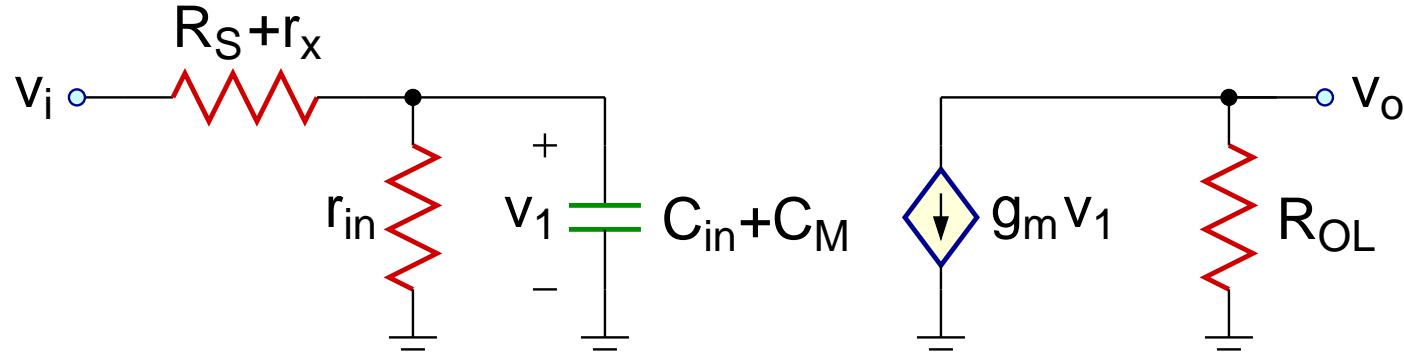
$$C_M = (A + 1)C_f \quad , \quad A = -\frac{V_o}{V_1} = g_m(r_o \parallel R_L)$$



$$\begin{aligned}
 \frac{V_o}{V_i} &= -g_m R_{OL} \frac{\frac{r_{in}}{R_s + r_x + \left( r_{in} \parallel \frac{1}{s(C_{in} + C_M)} \right)}}{\frac{1}{r_{in} \parallel \frac{1}{s(C_{in} + C_M)}}} \\
 &= -g_m R_{OL} \frac{r_{in}}{R_s + r_x + r_{in}} \frac{1}{1 + s(C_{in} + C_M)R}
 \end{aligned}$$

$$R = (R_s + r_x) \parallel r_{in}, \quad R_{OL} = r_o \parallel R_L$$

## Approximate vs. Exact Solution

---

Miller approximation:

$$p_1 = -\frac{1}{R(C_{in} + C_f(1 + g_m R_{OL}))}$$

Exact derivation:

$$p_1 = -\frac{1}{R \left( C_{in} + C_f \left( 1 + g_m R_{OL} + \frac{R_{OL}}{R} \right) \right)}$$

$$p_2 = - \left( \frac{1}{R_{OL} C_f} + \frac{1}{R C_{in}} + \frac{1}{R_{OL} C_{in}} + \frac{g_m}{C_{in}} \right)$$

$$z_1 = \frac{g_m}{C_f}$$

$$p_1 = -\frac{1}{((R_S + r_b) \parallel r_\pi) \left( C_\pi + C_\mu \left( 1 + g_m R_{OL} + \frac{R_{OL}}{R} \right) \right)}$$

$$p_2 = -\left( \frac{1}{R_{OL}C_\mu} + \frac{1}{RC_\pi} + \frac{1}{R_{OL}C_\pi} + \frac{g_m}{C_\pi} \right)$$

$$z_1 = \frac{g_m}{C_\mu}$$

$$\omega_T = \frac{g_m}{C_\pi + C_\mu}$$

$$|p_2| \gg |p_1| \quad , \quad |p_2| > \omega_T \quad , \quad |z_1| > \omega_T$$

$$p_1 = -\frac{1}{R_S \left( C_{gs} + C_{gd} \left( 1 + g_m R_{OL} + \frac{R_{OL}}{R_S} \right) \right)}$$

$$p_2 = -\left( \frac{1}{R_{OL} C_{gd}} + \frac{1}{R_S C_{gs}} + \frac{1}{R_{OL} C_{gs}} + \frac{g_m}{C_{gs}} \right)$$


$$z_1 = \frac{g_m}{C_{gd}}$$

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$

$$|p_2| \gg |p_1| , \quad |p_2| > \omega_T , \quad |z_1| > \omega_T$$

# BJT & MOS Differential Pair

DM

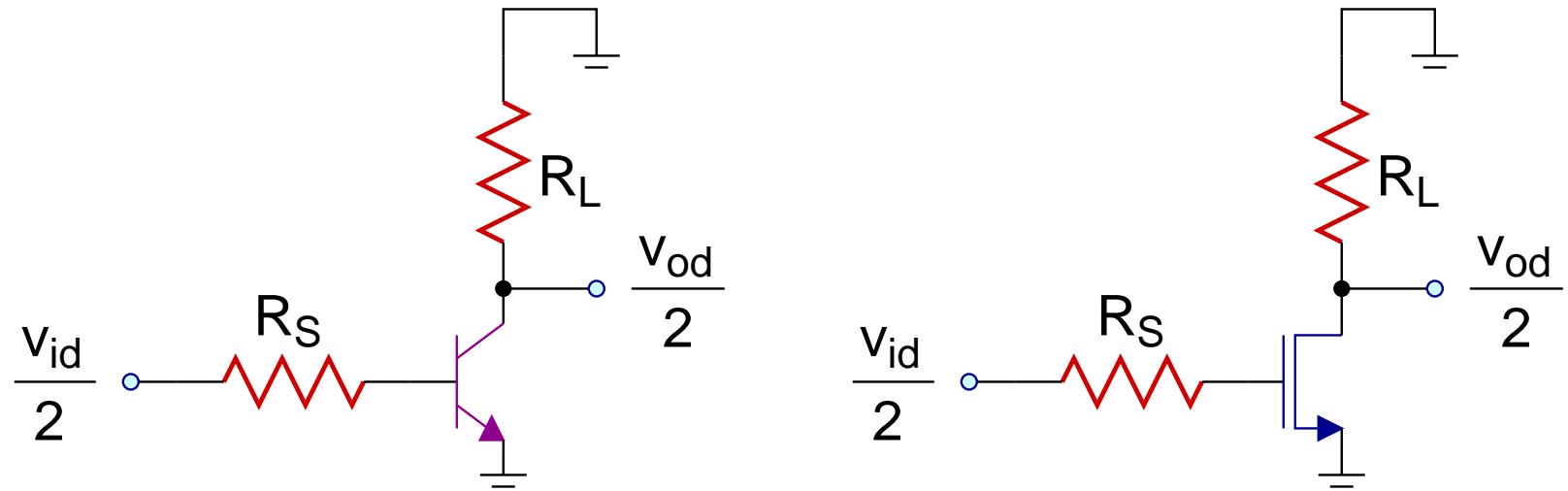


Dominant pole of  $\frac{V_{od}}{V_{id}}(s)$ :

$$p_1 = -\frac{1}{R \left( C_{in} + C_f \left( 1 + g_m R_{OL} + \frac{R_{OL}}{R} \right) \right)}$$

$$R = (R_s + r_x) \parallel r_{in} , \quad R_{OL} = r_o \parallel R_L$$

# BJT & MOS Differential Pair

CM

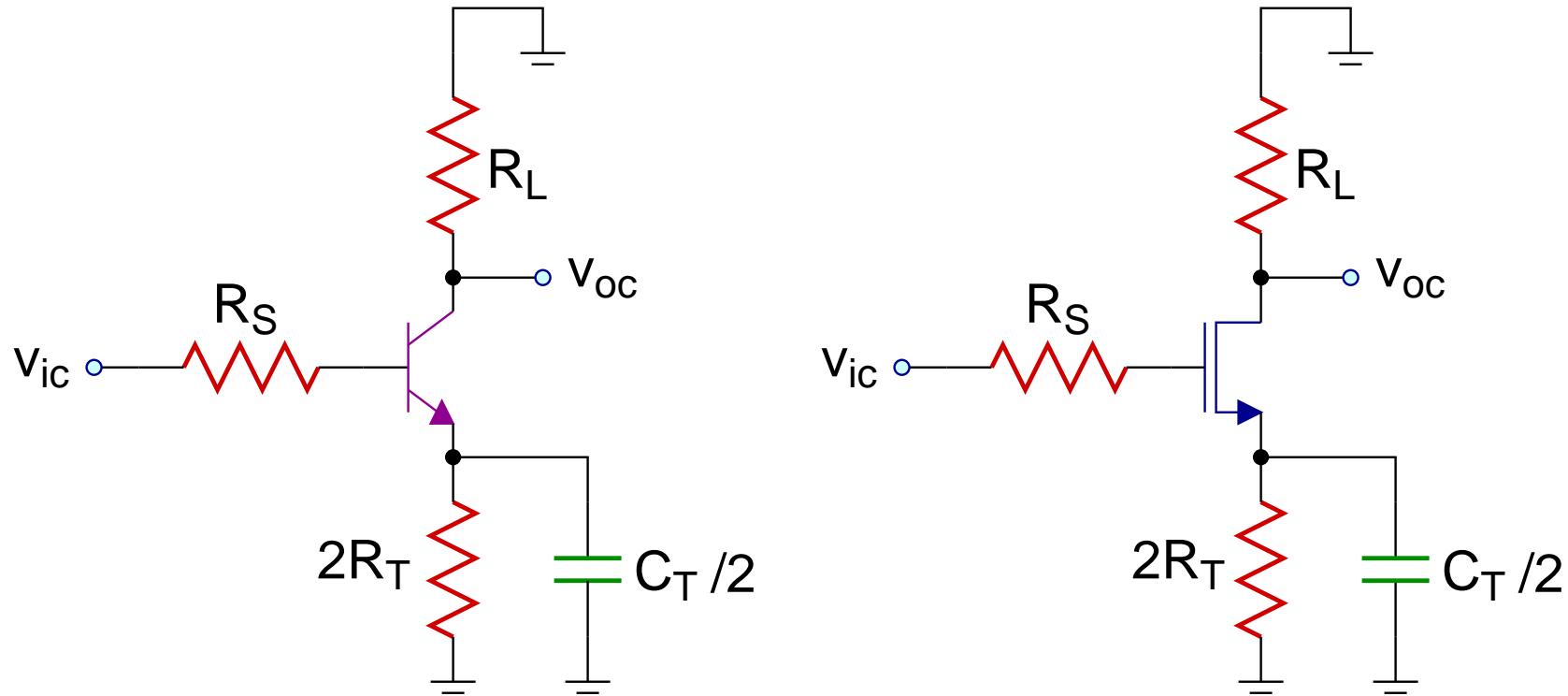


$$A_{cm}(s) \approx -\frac{R_L}{Z_T}, \quad Z_T = 2R_T \parallel \frac{1}{sC_T/2} = \frac{2R_T}{1 + sC_T R_T}$$

$$A_{cm}(s) \approx -\frac{R_L}{2R_T} (1 + sC_T R_T)$$

# BJT & MOS Differential Pair

CMRR



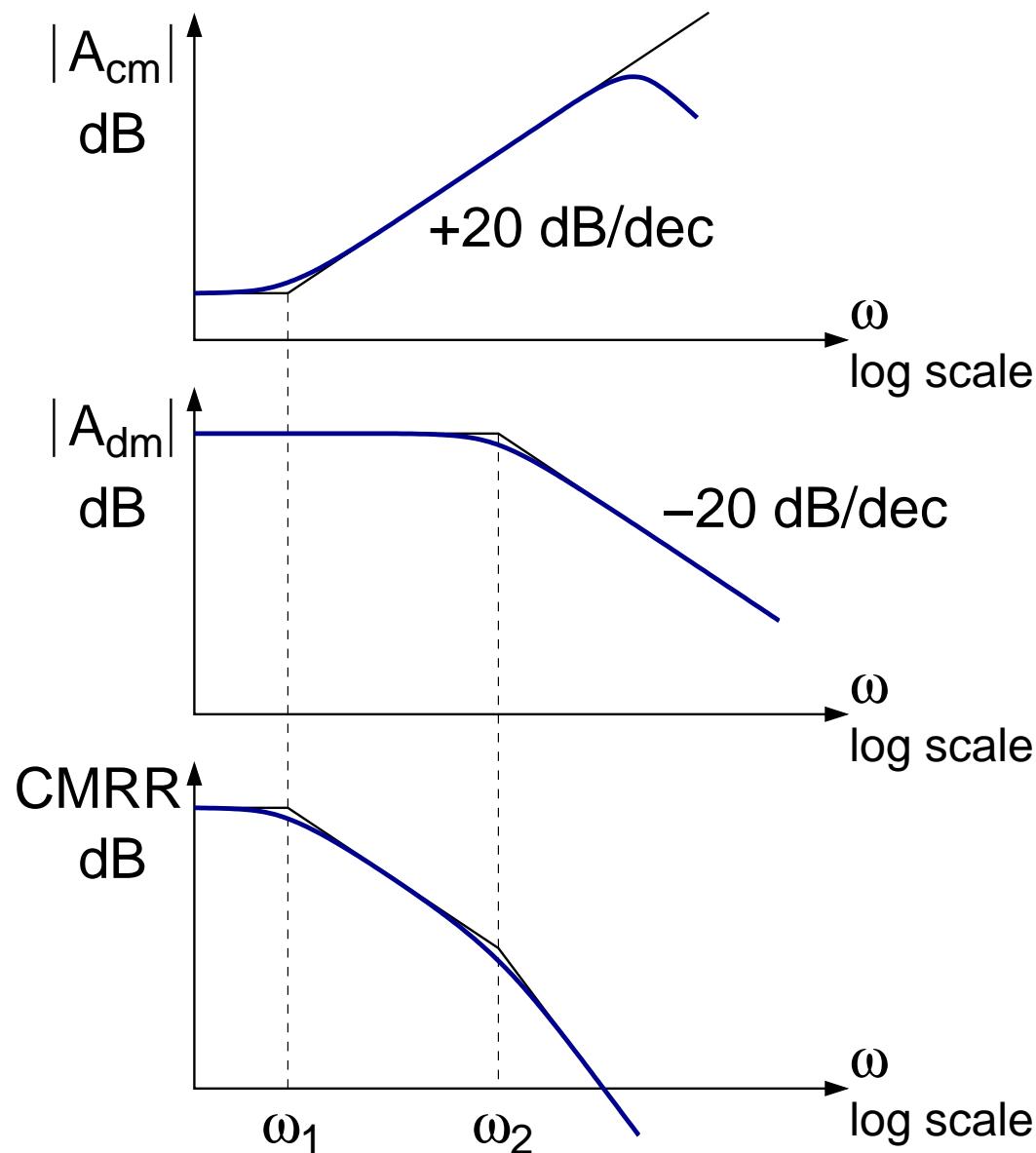


$$\omega_1 \approx \frac{1}{R_T C_T}$$

$$\omega_2 \approx \frac{1}{R(C_{in} + C_M)}$$

# BJT-CC & MOS-CD

Small-signal circuit

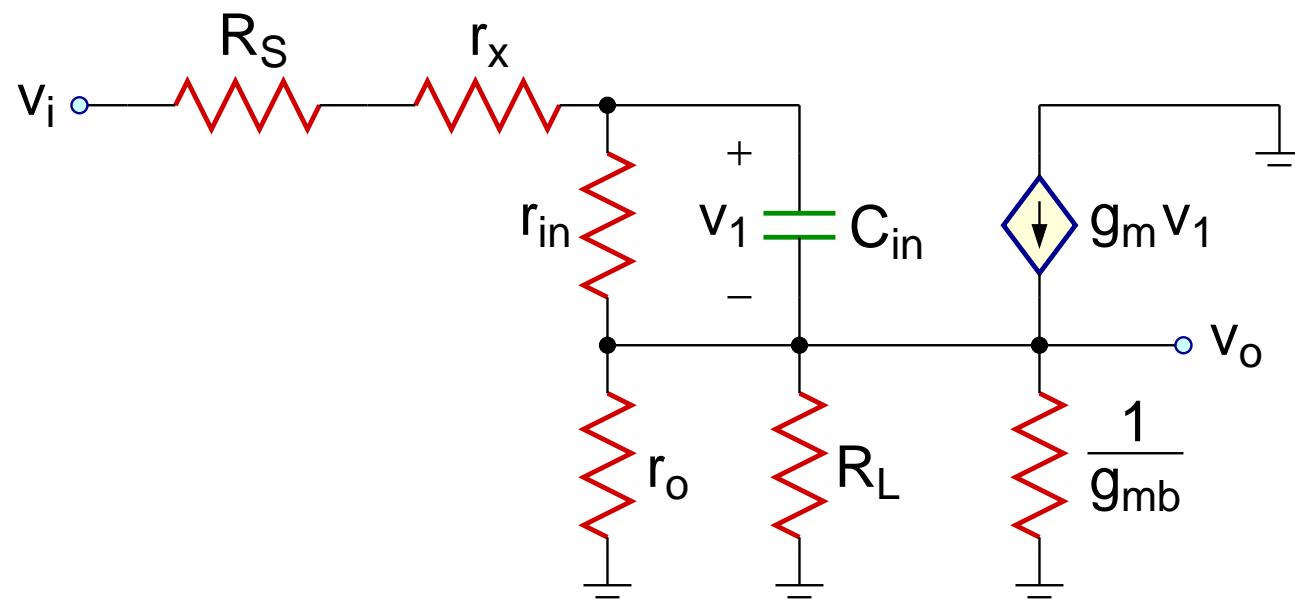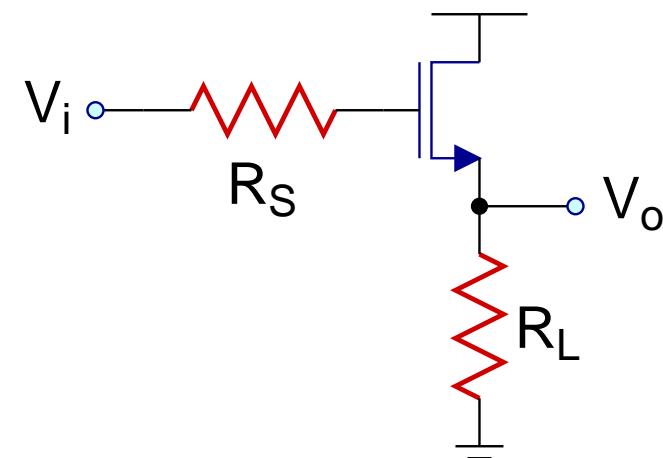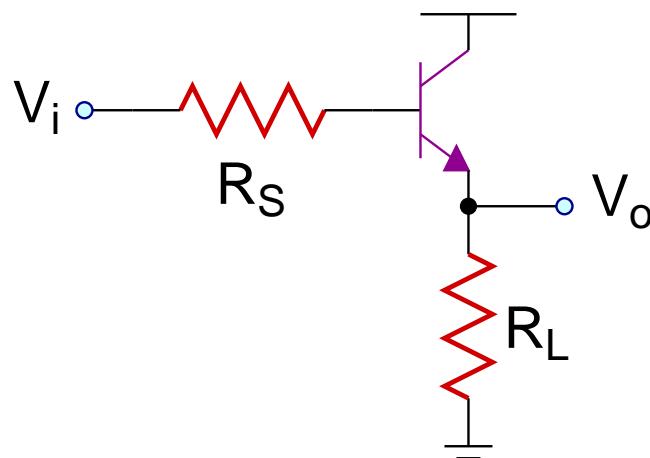

$$\frac{v_o}{v_i}(s) = \frac{g_m R'_L + \frac{R'_L}{r_{in}}}{1 + g_m R'_L + \frac{R'_S + R'_L}{r_{in}}} \frac{1 - \frac{s}{z_1}}{1 - \frac{s}{p_1}}$$

$$p_1 = -\frac{1}{R_1 C_{in}}, \quad z_1 = -\frac{g_m + \frac{1}{r_{in}}}{C_{in}}$$

$$R'_S = R_S + r_x$$

$$R'_L = r_o \parallel R_L \parallel \frac{1}{g_{mb}}$$

$$R_1 = r_{in} \parallel \frac{R'_S + R'_L}{1 + g_m R'_L}$$

$$z_1 = -\frac{g_m + \frac{1}{r_\pi}}{C_\pi} \approx -\frac{g_m}{C_\pi} \approx -\omega_T$$

$$p_1 = -\frac{1}{R_1 C_\pi}, \quad R_1 = r_\pi \parallel \frac{R'_S + R'_L}{1 + g_m R'_L}$$

$$R'_S = R_S + r_b, \quad R'_L = r_o \parallel R_L$$

Typically,  $|z_1|$  is slightly larger than  $|p_1|$ .

If  $g_m R'_L \gg 1$  and  $R'_S \ll R'_L$ , then  $R_1 \approx 1/g_m$  and  $p_1 \approx -\omega_T$ .

If  $R'_S$  is large (compared to  $R'_L$ ), then  $|p_1|$  will be significantly less than  $\omega_T$ .

$$z_1 = -\frac{g_m}{C_{gs}} \approx -\omega_T$$

$$p_1 = -\frac{1}{R_1 C_{gs}}, \quad R_1 = \frac{R_s + R'_L}{1 + g_m R'_L}$$

$$R'_L = r_o \parallel R_L \parallel \frac{1}{g_{mb}}$$



Typically,  $|z_1|$  is slightly larger than  $|p_1|$ .

If  $g_m R'_L \gg 1$  and  $R_s \ll R'_L$ , then  $R_1 \approx 1/g_m$  and  $p_1 \approx -\omega_T$ .

If  $R_s$  is large (compared to  $R'_L$ ), then  $|p_1|$  will be significantly less than  $\omega_T$ .

# BJT-CC & MOS-CD

Input impedance

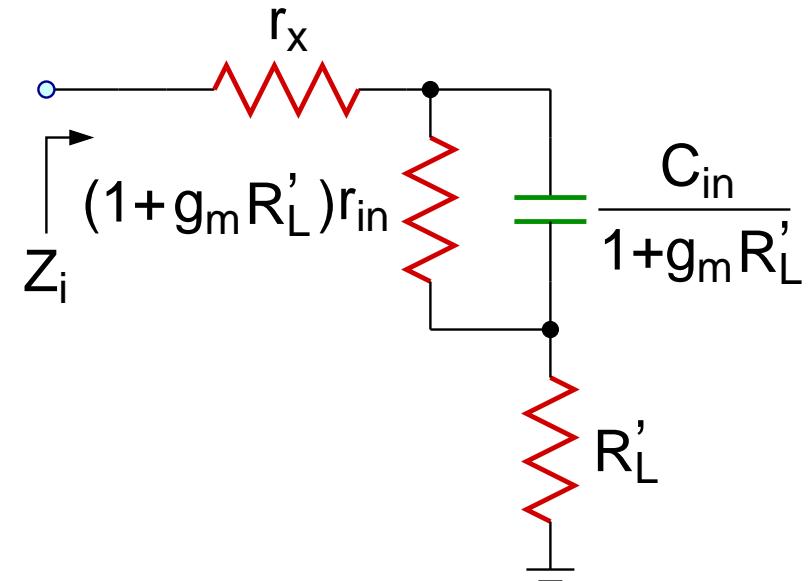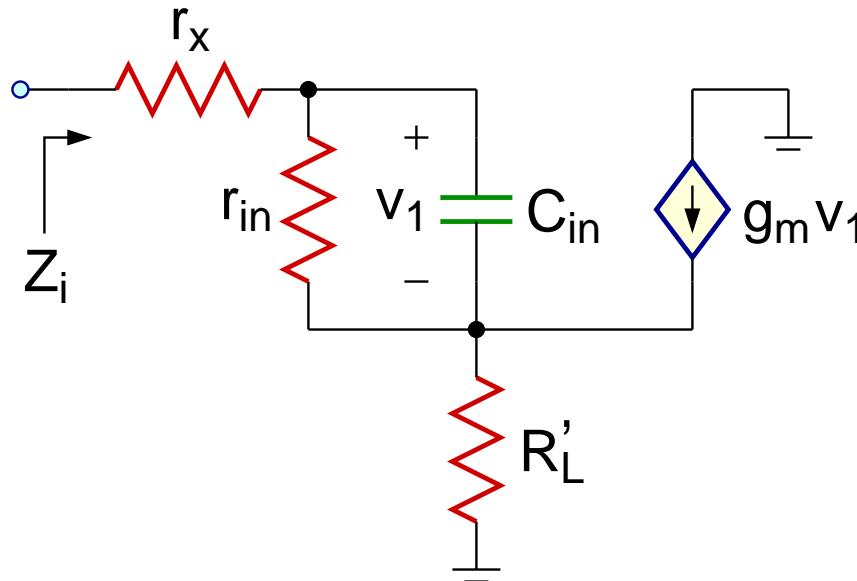

$$Z_i = r_x + \left( R \parallel \frac{1}{sC} \right) + R'_L$$

$$R = (1 + g_m R'_L) r_{in} , \quad C = \frac{C_{in}}{1 + g_m R'_L}$$

$$R'_L = r_o \parallel R_L \parallel \frac{1}{g_{mb}}$$

BJT:

$$Z_i = r_b + \left( R \parallel \frac{1}{sC} \right) + R'_L$$

$$R = (1 + g_m R'_L) r_\pi , \quad C = \frac{C_\pi}{1 + g_m R'_L}$$


$$R'_L = r_o \parallel R_L$$

MOS:

$$Z_i = \frac{1}{sC} + R'_L$$

$$C = \frac{C_{gs}}{1 + g_m R'_L}$$
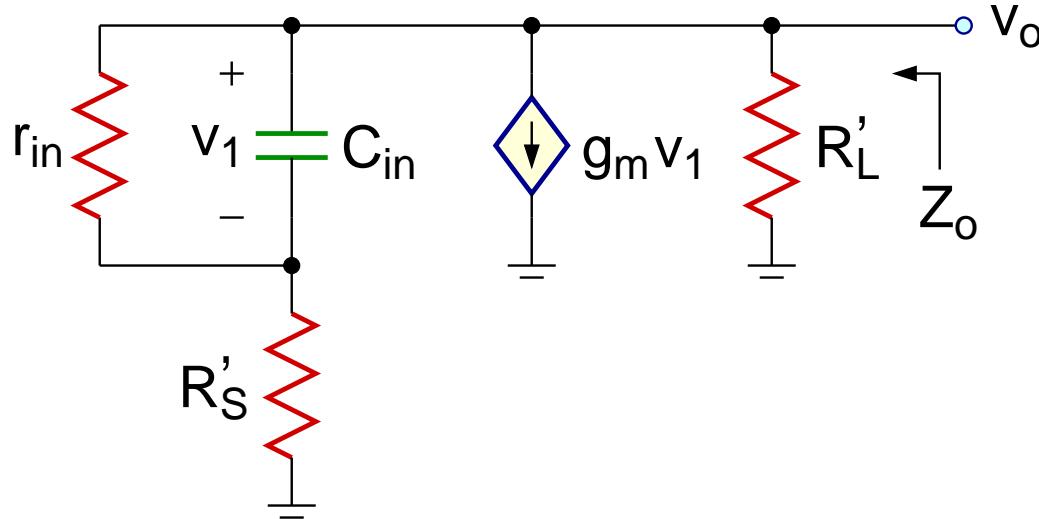
$$R'_L = r_o \parallel R_L \parallel \frac{1}{g_{mb}}$$



$$v_1 = \frac{z_{in}}{z_{in} + R'_S} v_o , \quad z_{in} = r_{in} \parallel \frac{1}{sC_{in}}$$

$$Z_o = (z_{in} + R'_S) \parallel \left( \frac{z_{in} + R'_S}{g_m z_{in}} \right) \parallel R'_L = \frac{z_{in} + R'_S}{1 + g_m z_{in}} \parallel R'_L$$

$$R'_S = R_S + r_x , \quad R'_L = r_o \parallel R_L \parallel \frac{1}{g_{mb}}$$

$$Z_o = R'_L \parallel \left[ \frac{r_{in} + R'_S}{1 + g_m r_{in}} \frac{1 + sC_{in}(R'_S \parallel r_{in})}{1 + sC_{in}\left(\frac{1}{g_m} \parallel r_{in}\right)} \right]$$

$\frac{1}{g_m} > R'_S \Rightarrow Z_o$  is capacitive

$\frac{1}{g_m} < R'_S \Rightarrow Z_o$  is inductive

$\frac{1}{g_m} = R'_S \Rightarrow Z_o$  is resistive




Practical design goals:  $r_x \ll R_S$  ,  $\frac{1}{g_m} = R_S$

BJT:

$$Z_o = r_o \parallel R_L \parallel \left[ \frac{r_\pi + R_S + r_b}{\beta + 1} \frac{1 + sC_\pi((R_S + r_b) \parallel r_\pi)}{1 + sC_\pi \left( \frac{1}{g_m} \parallel r_\pi \right)} \right]$$

MOS:
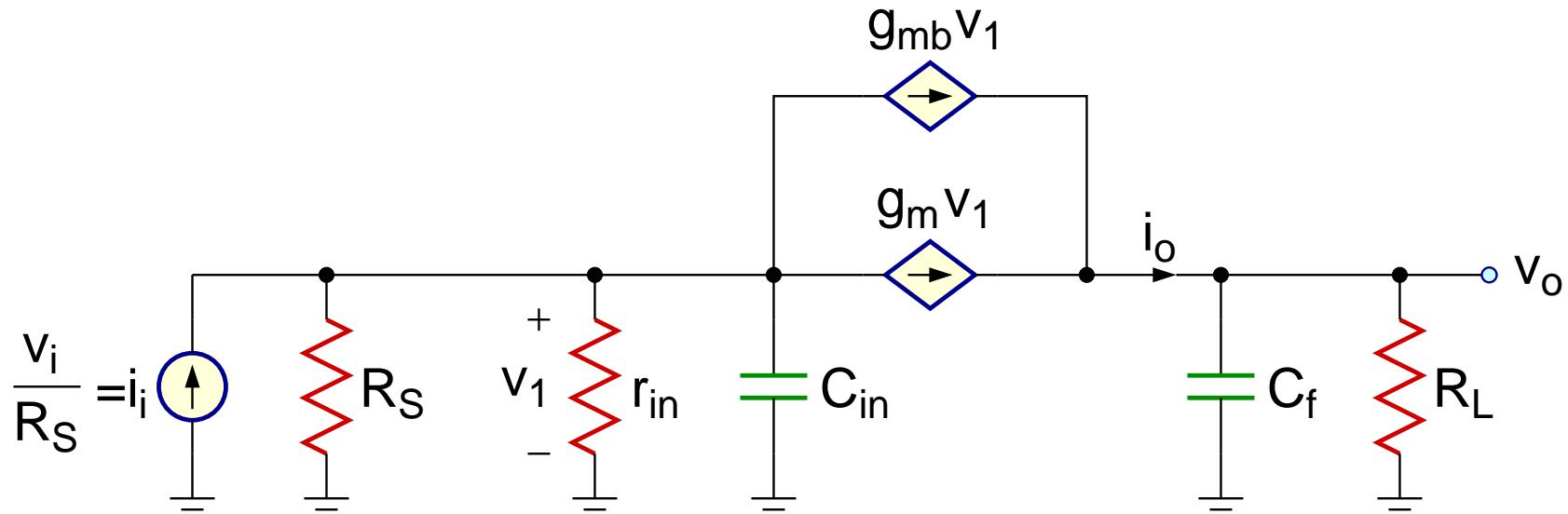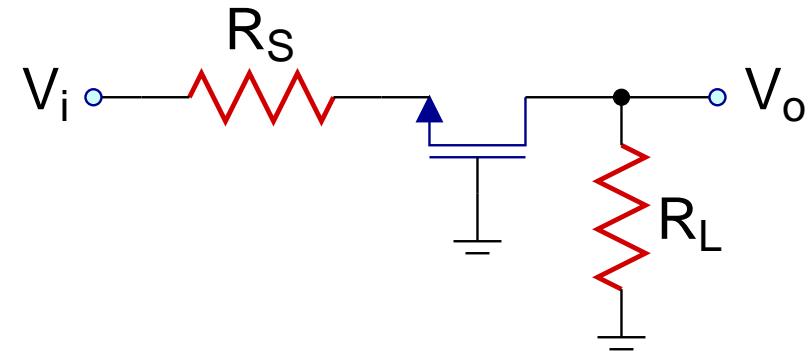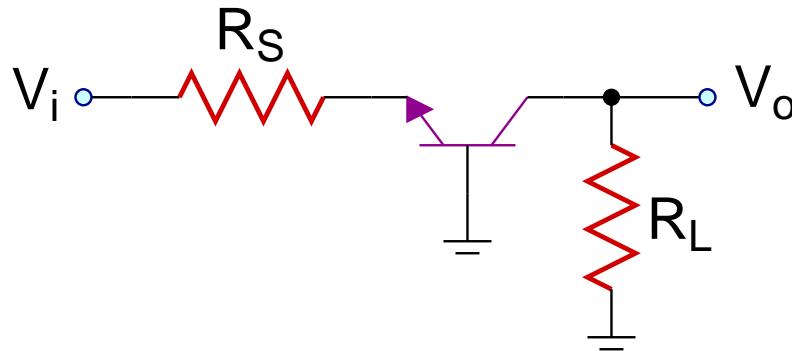
$$Z_o = r_o \parallel R_L \parallel \frac{1}{g_{mb}} \parallel \left[ \frac{1}{g_m} \frac{1 + sC_{gs}R_S}{1 + s\frac{C_{gs}}{g_m}} \right]$$



$$\frac{i_o}{i_i}(s) = K \frac{1}{1 - \frac{s}{p_1}}$$

$$\frac{v_o}{v_i}(s) = \frac{R_L}{R_S} K \frac{1}{1 - \frac{s}{p_1}} \frac{1}{1 - \frac{s}{p_2}}$$

$$K = \frac{g_m + g_{mb}}{g_m + g_{mb} + \frac{1}{R_S} + \frac{1}{r_{in}}}$$

$$p_1 = -\frac{g_m + g_{mb} + \frac{1}{R_S} + \frac{1}{r_{in}}}{C_{in}}, \quad p_2 = -\frac{1}{C_f R_L}$$

BJT:

$$\frac{v_o}{v_i}(s) = \frac{R_L}{R_S} \frac{g_m}{\frac{g_m}{\alpha} + \frac{1}{R_S}} \frac{1}{1 - \frac{s}{p_1}} \frac{1}{1 - \frac{s}{p_2}}$$

$$p_1 = -\frac{\frac{g_m}{\alpha} + \frac{1}{R_S}}{C_\pi}, \quad p_2 = -\frac{1}{C_\mu R_L}$$

MOS:

$$\frac{v_o}{v_i}(s) = \frac{R_L}{R_S} \frac{g_m + g_{mb}}{g_m + g_{mb} + \frac{1}{R_S}} \frac{1}{1 - \frac{s}{p_1}} \frac{1}{1 - \frac{s}{p_2}}$$

$$p_1 = -\frac{g_m + g_{mb} + \frac{1}{R_S}}{C_{gs}}, \quad p_2 = -\frac{1}{C_{gd} R_L}$$

$$\begin{aligned}
 A(s) &= \frac{\kappa}{1 + b_1 s + b_2 s^2 + \cdots + b_n s^n} \\
 &= \frac{\kappa}{\left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right) \cdots \left(1 - \frac{s}{p_n}\right)} \\
 b_1 &= \sum_{i=1}^n \left(-\frac{1}{p_i}\right)
 \end{aligned}$$

If  $|p_1| \ll |p_2|, |p_3|, \dots$  then


$$b_1 \approx \left| \frac{1}{p_1} \right| , \quad |A(j\omega)| \approx \frac{\kappa}{\sqrt{1 + \left(\frac{\omega}{p_1}\right)^2}}$$

The higher 3-dB frequency is

$$\omega_H \approx |p_1| \approx \frac{1}{b_1}$$
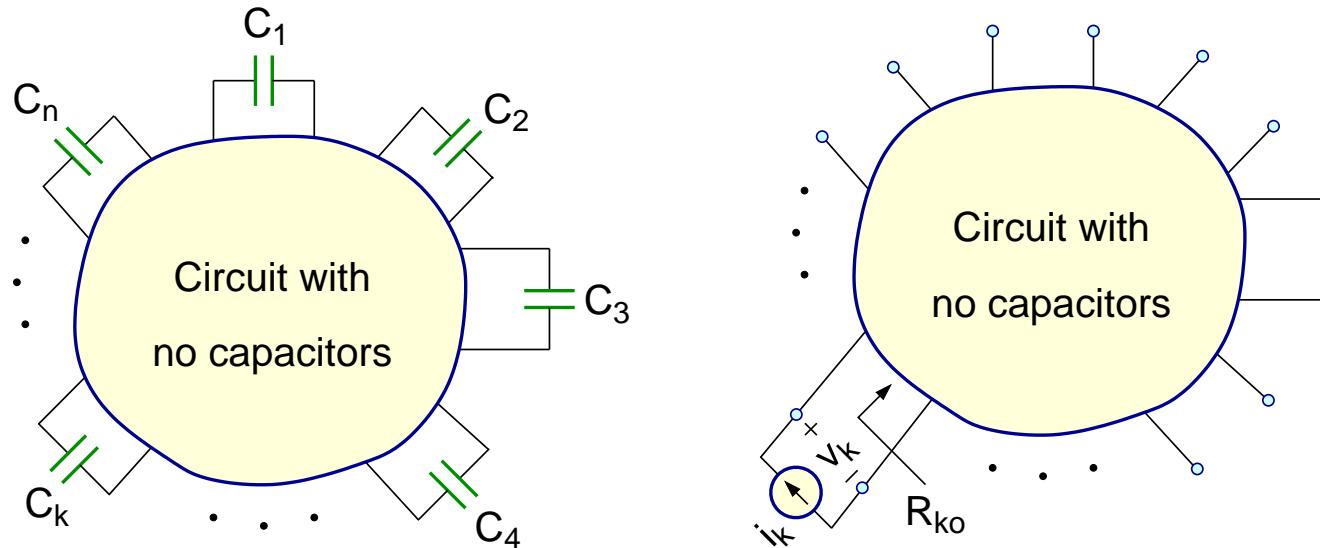
# Open-Circuit Time Constant Analysis

Also known as Zero-Value Time Constant Analysis. Can be used to estimate the higher 3-dB frequency ( $\omega_H$ ).




$$R_{ko} = \frac{V_k}{i_k}, \quad T_{ko} = R_{ko}C_k$$

$$b_1 = \sum_{k=1}^n R_{ko}C_k = R_{1o}C_1 + R_{2o}C_2 + \dots + R_{no}C_n$$

$$\omega_H \approx |p_1| \approx \frac{1}{b_1} \approx \frac{1}{\sum_k T_{ko}}$$
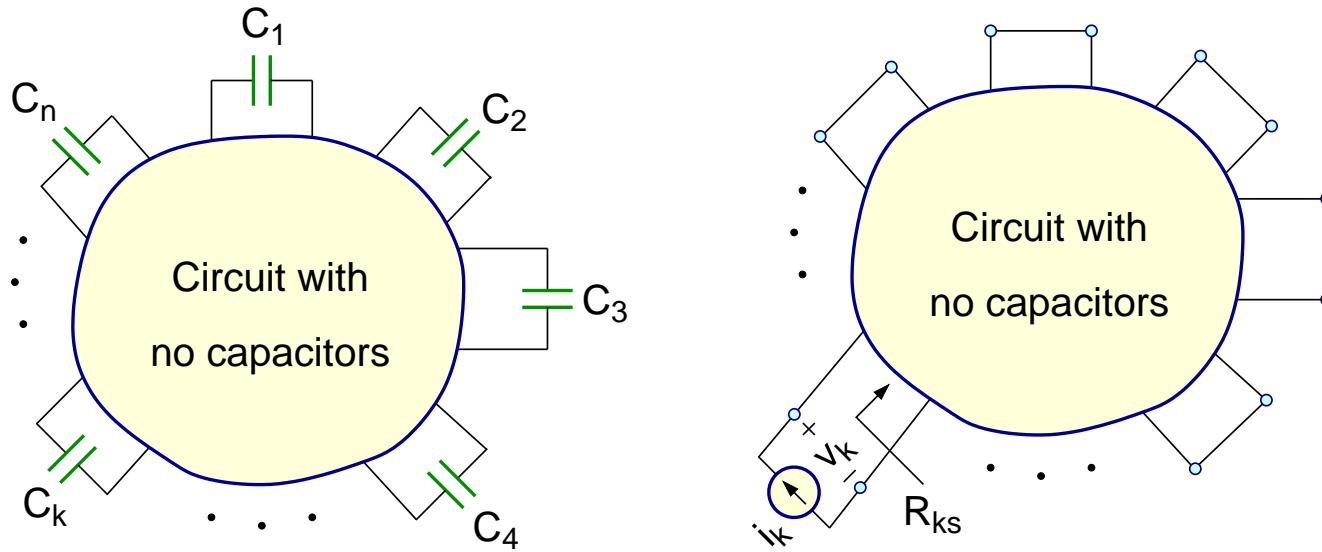
# Short-Circuit Time Constant Analysis

Can be used to estimate the lower 3-dB frequency ( $\omega_L$ ) of AC-coupled amplifiers.




$$R_{ks} = \frac{v_k}{i_k}, \quad \tau_{ks} = R_{ks} C_k$$

$$\omega_L \approx \sum_{k=1}^n \frac{1}{\tau_{ks}}$$
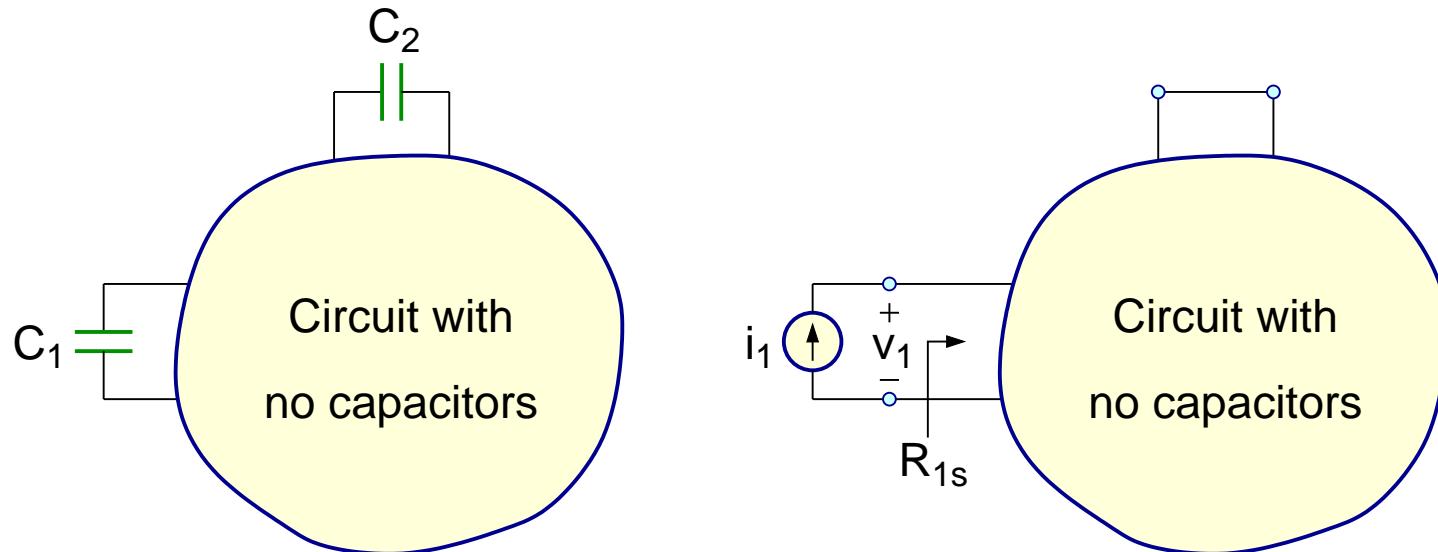
# Short-Circuit Time Constant Analysis



Can be used to estimate the nondominant pole ( $p_2$ ) in DC-coupled amplifiers that have only two widely-spaced real poles.



$$R_{ks} = \frac{v_k}{i_k} , \quad \tau_{ks} = R_{ks} C_k , \quad k = 1, 2$$

$$p_2 \approx - \sum_{k=1}^2 \frac{1}{\tau_{ks}}$$

# Cascode Frequency Response

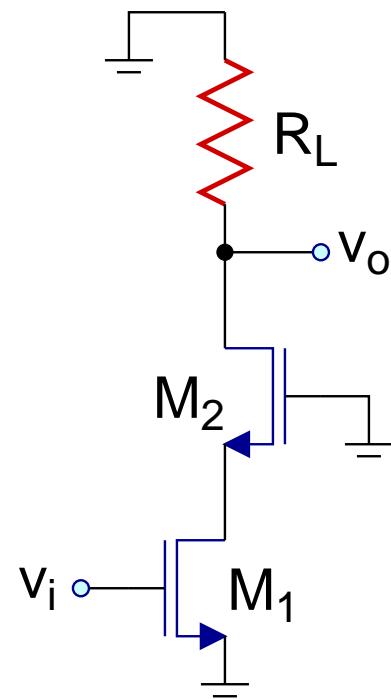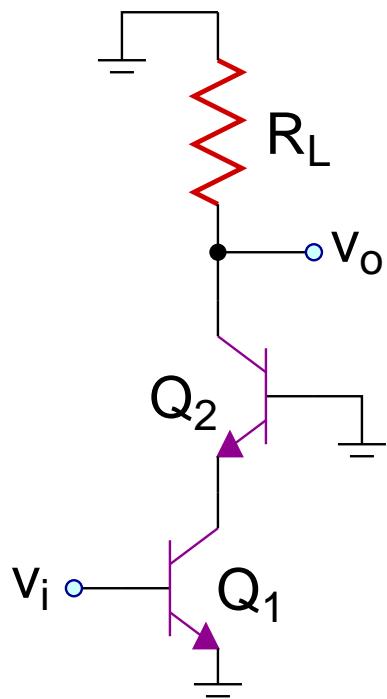

# Differential Pair

Current mirror load

