

January 21, 2022

ECEN 326

Homework #1

Due: 02-01-2022, 11:59PM

Homeworks will not be received after due.

Instructor: Sam Palermo

Solve the following problems from the Razavi text:

5.5, 5.9, 5.12(a), 5.16(a), 5.28, 5.46, 5.52, 5.56, 5.58, 5.73, 5.83

In the above problems that require DC operating point calculations (5.9, 5.12, ...), assume that $V_{BE}=0.7V$ for the BJTs. Note, in some of the given problems, Razavi gives you an I_S value and wants you to iterate and find a more exact V_{BE} . I don't think that is worth your time, so again just use $V_{BE}=0.7V$.

Problem Edits

5.9 – Use $\beta=50$

5.12 – Assume the transition between Active and Saturation modes is with $V_{CE}=0.3V$. Don't do part (b).

5.16 – Don't do part (b)