
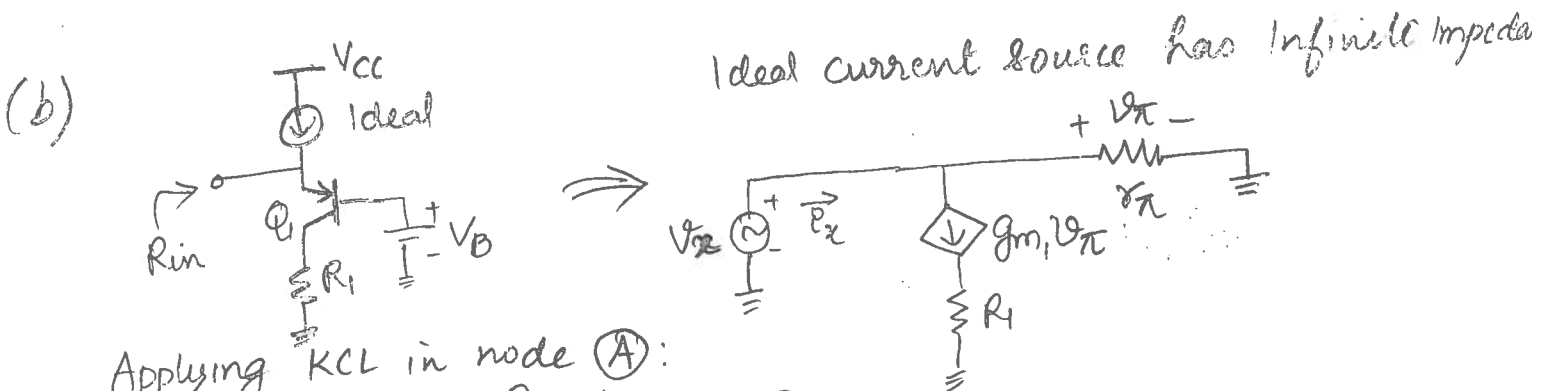


ECEN 326.

Home work 1

Solutions

5.5) Find R_{in}

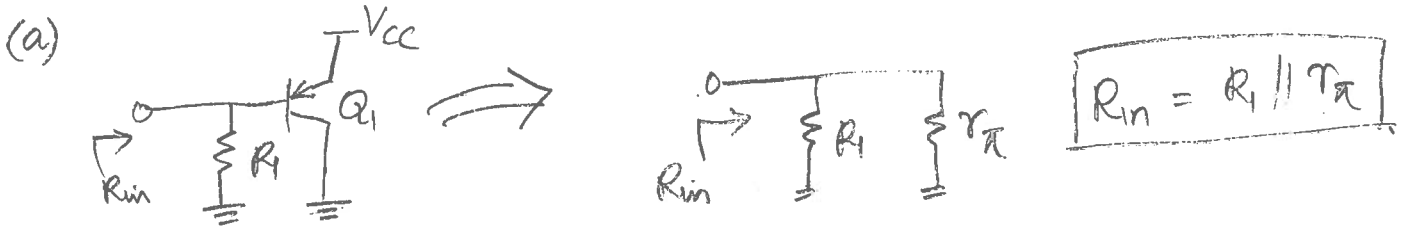

Applying KCL in node (A):

$$i_x = \frac{v_x}{r_{\pi}} + g_{m1}v_{\pi} \quad \text{--- (1)}$$

Also $v_x = v_{\pi} \quad \text{--- (2)}$



Using (1) & (2),

$$i_x = \frac{v_x}{r_{\pi}} + g_{m1}v_x$$

$$\therefore R_{in} = \frac{v_x}{i_x} = \frac{1}{\frac{1}{r_{\pi}} + g_{m1}}$$

$R_{in} = r_{\pi} \parallel \frac{1}{g_{m1}}$

c)

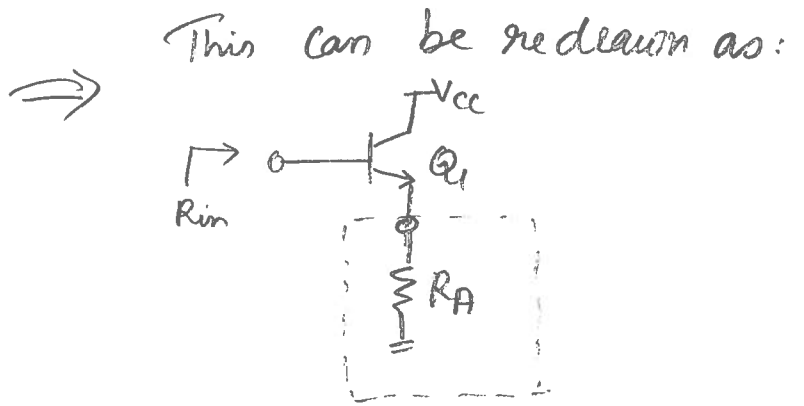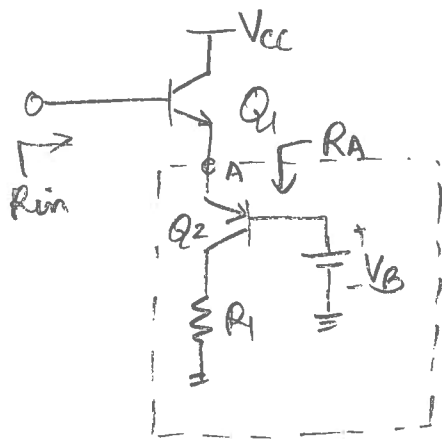

We already know from 5.5 (b) that $R_A = r_{\pi 2} \parallel \frac{1}{g_{m2}}$

We have:

$$V_A = v_x - v_{\pi 1}$$

$$\text{or } V_A = v_x - \beta_1 v_{\pi 1} \quad \text{--- (1)}$$

Also,

$$v_A = R_A (\beta_1 i_x + g_{m1} v_{\pi 1})$$

$$= R_A (\beta_1 i_x + g_{m1} \beta_1 v_{\pi 1})$$

$$\Rightarrow v_A = R_A \beta_1 i_x (1 + g_{m1} r_{\pi 1}) \quad \text{--- (2)}$$

Using (1) & (2): $R_A \beta_1 i_x (1 + g_{m1} r_{\pi 1}) = v_x - \beta_1 v_{\pi 1}$

$$\text{or } \beta_1 [R_A (1 + g_{m1} r_{\pi 1}) + r_{\pi 1}] i_x = v_x$$


$$\text{or } R_{in} = \frac{v_x}{i_x} = r_{\pi 1} + R_A (1 + g_{m1} r_{\pi 1})$$

$$\text{or } R_{in} = r_{\pi 1} + (1 + g_{m1} r_{\pi 1}) \left[r_{\pi 2} \parallel \frac{1}{g_{m2}} \right]$$


$$\text{or } R_{in} = r_{\pi 1} + (1 + \beta_1) \left[r_{\pi 2} \parallel \frac{1}{g_{m2}} \right] = r_{\pi 1} + (\beta + 1) r_{e2}$$

(2)

(d)

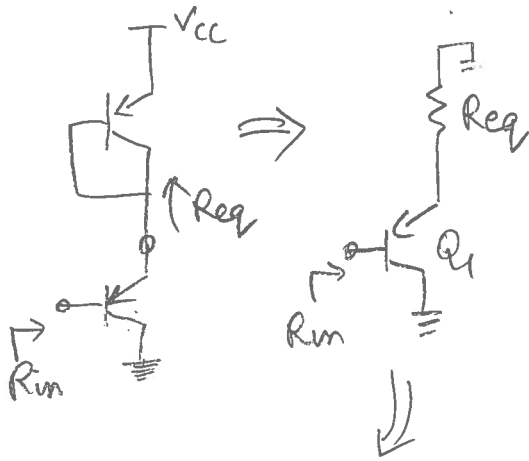


Where

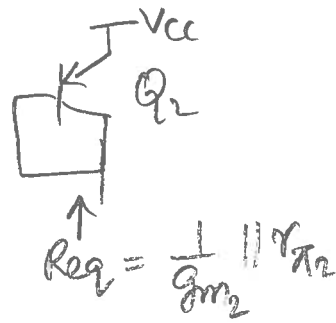

$$R_{in} = r_{\pi_1} + (1+\beta)R_{eq} \Rightarrow R_{in} = r_{\pi_1} + (1+\beta) \left[\frac{1}{g_{m_2}} \parallel r_{\pi_2} \right]$$

$$= r_{\pi_1} + (\beta+1)r_{e_2}$$

(e)

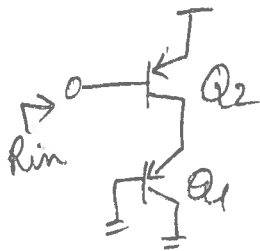


$$R_{in} = r_{\pi_2}$$

Since Q_1 is connected to the collector of Q_2 , Q_1 plays no role in the input impedance of the circuit.

5.9)

(a)

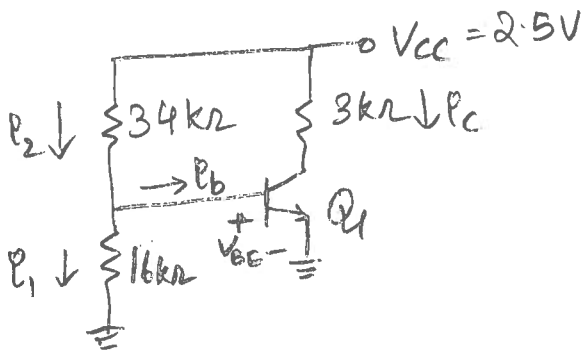

$$V_{BE} = 0.7V ; \beta = 50$$

$$I_c = \beta I_b = 100 I_b$$

$$I_1 = \frac{V_{BE}}{16k} = \frac{0.7V}{16k} = \underline{\underline{43.75\mu A}}$$

$$I_2 = \frac{V_{cc} - V_{BE}}{34k} = \frac{2.5 - 0.7}{34k} = \underline{\underline{52.94\mu A}}$$

$$I_b = I_2 - I_1 = 52.94\mu A - 43.75\mu A$$

$$\Rightarrow \underline{\underline{I_b = 9.19\mu A}}$$


$$\therefore I_c = 9.19\mu A \times 50 \Rightarrow \boxed{I_c = 459.5\mu A}$$

$$V_{CE} = V_{cc} - I_c \times 3k \Rightarrow V_{CE} = 2.5V - 1.3785V$$

$$\text{or } \boxed{V_{CE} = 1.1215V}$$

Q_1 is in forward active (3)

(b)

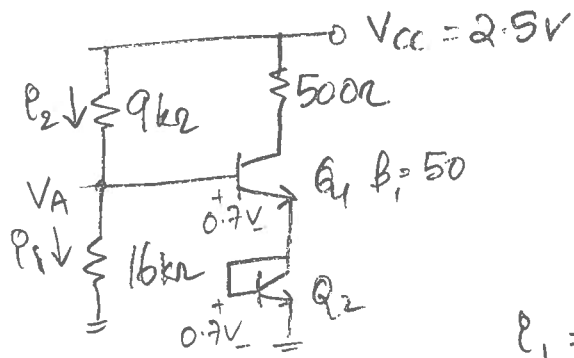

$$V_A = V_{BE1} + V_{BE2}$$

$$= 0.7 + 0.7 \Rightarrow \underline{\underline{V_A = 1.4V}}$$

$$I_1 = \frac{V_A}{16k} = \frac{1.4V}{16k} = \underline{\underline{87.5\mu A}}$$

$$I_2 = \frac{V_{CC} - V_A}{9k} = \frac{2.5 - 1.4}{9k} = \frac{1.1}{9k} = \underline{\underline{122.22\mu A}}$$

$$\therefore I_{B1} = I_2 - I_1 = \underline{\underline{34.72\mu A}}$$

$$I_{C1} = \beta I_{B1} = 50 \times 34.72\mu A \therefore \boxed{I_{C1} = 1.736mA}$$

$$\text{Since } I_{E1} = I_{E2} \Rightarrow I_{C1} = I_{C2} \therefore \boxed{I_{C2} = 1.736mA}$$

$$\boxed{V_{CE2} = V_{BE2} = 0.7V}$$


$$V_{CE1} = V_{CC} - I_{C1}(500\Omega) - V_{CE2}$$

$$= 2.5V - 1.736mA \times 0.5k - 0.7V$$

$$\Rightarrow \boxed{V_{CE1} = 0.932V}$$

\therefore Both Q_1 & Q_2 are in forward active region of transistor operation.

(C)

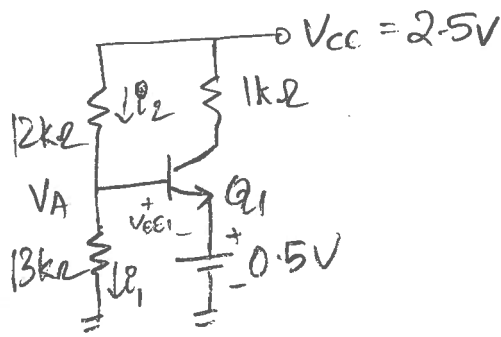

$$V_{BE1} = 0.7V, \beta = 50 \text{ (given)}$$

$$V_A = V_{BE1} + 0.5V = 0.7 + 0.5 = 1.2V$$


$$I_B = I_2 - I_1 = \frac{2.5V - 1.2V}{12k\Omega} - \frac{1.2V}{13k\Omega}$$

$$I_B = 16\mu A \Rightarrow I_C = 0.8mA$$

$$V_{CE1} = 2.5V - (0.8mA \times 1k\Omega) - 0.5V \Rightarrow V_{CE1} = 1.2V$$

$\therefore Q_1$ is in forward active.

5.12) a)

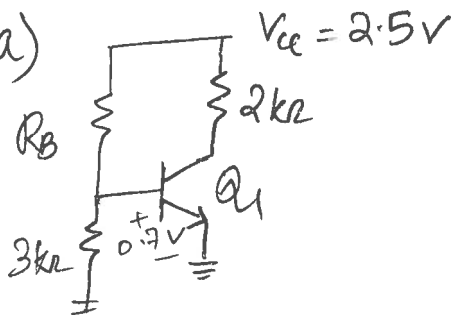

To operate in active mode,

$$V_{CE} \geq 0.3V$$

$$\therefore V_{CC} - I_C \times 2k\Omega = V_{CE} \geq 0.3V$$

$$\text{or } I_C \leq \frac{V_{CC} - 0.3V}{2k\Omega} = 1.1mA$$

\therefore To operate in active mode

$$I_C \leq 1.1mA \Rightarrow \beta I_B \leq 1.1mA$$

$$\text{or } I_B \leq 11\mu A \text{ (with } \beta = 100)$$

$$\text{We know that } I_B = \frac{2.5V - 0.7V}{R_B} - \frac{0.7V}{3k\Omega} = \frac{1.8V}{R_B} - 233.33\mu A$$

$$\therefore \frac{1.8}{R_B} - 233.33\mu A \leq 11\mu A \text{ or } \frac{1.8}{R_B} \leq 244.33\mu A$$

$$\Rightarrow R_B \geq \frac{1.8}{244.33\mu A}$$


$$\Rightarrow R_B \geq 7.36k\Omega$$

(5)

$$R_{Bmin} = 7.36k\Omega$$

To guarantee active mode in Q_1

5.16)
a)

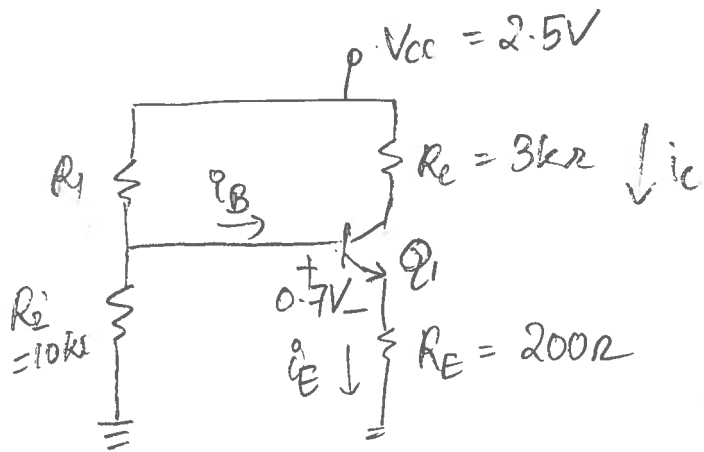

Given

$$P_C = 0.25 \text{ mW}$$

or

$$250 \mu\text{A}$$

$$\beta = 100$$

$$\therefore I_B = 2.5 \mu\text{A}$$

$$V_A = V_{BE} + I_E R_E = V_{BE} + 101 I_B R_E$$

$$\therefore V_A = 0.7 + 25 \times 2.5 \mu\text{A} \times 200 = 0.7505 \text{ V}$$

KCL at node A:

$$\frac{V_{CC} - 0.7505}{R_1} = \frac{0.7505}{R_2} + I_B$$

$$\frac{2.5 - 0.7505}{R_1} = \frac{0.7505}{10\text{k}} + 2.5 \mu\text{A}$$


$$\Rightarrow \frac{1.7495}{R_1} = 77.55 \mu\text{A}$$

$$\text{or } R_1 = 22.56 \text{ k}\Omega$$

6

5.28)

(a)

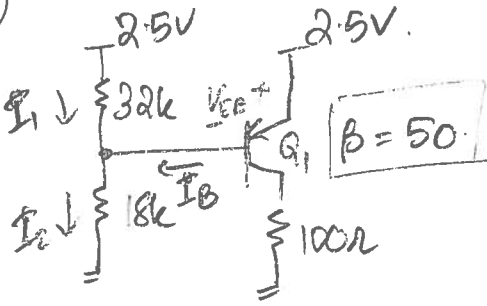

$$I_B = I_2 - I_1$$

$$V_{EB} = 0.7 \text{ Given/assum}$$

$$= \frac{V_{CC} - V_{EB}}{18k} - \frac{V_{EB}}{32k}$$

$$\Rightarrow I_B = \frac{2.5 - 0.7}{18k} - \frac{0.7}{32k} = \frac{1.8}{18k} - \frac{0.7}{32k}$$

$$= 100\mu A - 21.875\mu A$$


$$\therefore I_B = 78.125\mu A$$

$$I_C = 50 \times 78.125\mu A \Rightarrow I_C = 3.9\text{mA}$$

$$V_{EC} = V_{CC} - I_C \times 100 \Rightarrow V_{EC} = 2.5 - (3.9\text{mA} \times 0.1k)$$

$$\text{or } V_{EC} = 2.11\text{V}$$

(b)

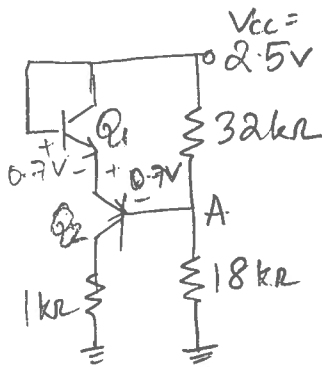

$$V_A = V_{CC} - V_{BE1} - V_{BE2}$$

$$= 2.5\text{V} - 0.7\text{V} - 0.7\text{V}$$

$$\Rightarrow V_A = 1.1\text{V}$$

Given:

$$\beta_1 = 100$$

$$\beta_2 = 50$$

$$V_{BE1} = V_{BE2} = 0.7\text{V}$$

$$I_{B2} = \frac{V_A}{18k} - \frac{V_{CC} - V_A}{32k} = \frac{1.1}{18k} - \frac{1.4}{32k} \Rightarrow I_{B2} = 17.36\mu A$$

$$I_{C2} = \beta_2 \cdot I_{B2} = 50 \times 17.36\mu A$$

$$\Rightarrow I_{C2} = 868\mu A$$

$$V_{CE1} = V_{CE2} = 0.7\text{V}$$

$$V_{CE2} = V_{CC} - V_{BE1} - (I_{C2} \times 1k) = 2.5\text{V} - 0.7\text{V} - (868\mu A \times 1k)$$

$$\Rightarrow V_{CE2} = 0.932\text{V}$$


(7)

$$I_{E1} = I_{C2} = (1 + 50) 17.36\mu A \Rightarrow I_{E1} = 885.36\mu A \Rightarrow I_{C1} = \frac{I_{E1} \times 100}{101}$$

$$\text{or } I_{C1} = 876.59\mu A$$

5.46)

(a)

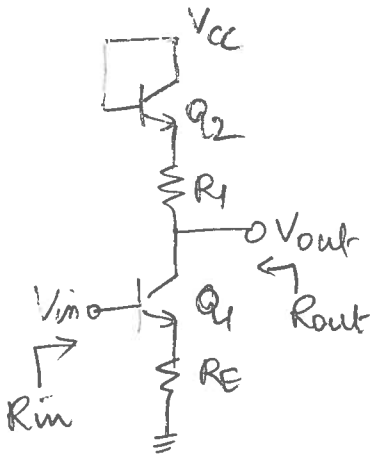


$$R_{in} = r_{\pi 1} + (1 + \beta_1) R_E$$

$$R_{out} = R_1 + \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$A_v = - \frac{R_1 + \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)}{R_E + \frac{1}{g_{m1}}} = - \frac{\alpha (R_1 + r_{e2})}{R_E + r_{e1}}$$

(b)

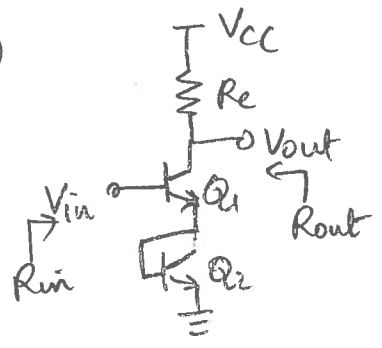


$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left[\frac{1}{g_{m1}} \parallel r_{\pi 2} \right]$$

$$R_{out} = R_C$$

$$A_v = - \frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2}} = - \frac{\alpha R_C}{r_{e1} + r_{e2}}$$

(c)

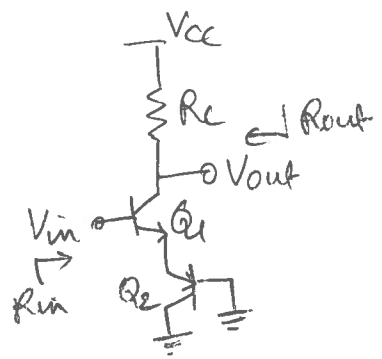


$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left[\frac{1}{g_{m2}} \parallel r_{\pi 2} \right]$$

$$R_{out} = R_C$$

$$A_v = \frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2}} = - \frac{\alpha R_C}{r_{e1} + r_{e2}}$$

(d)

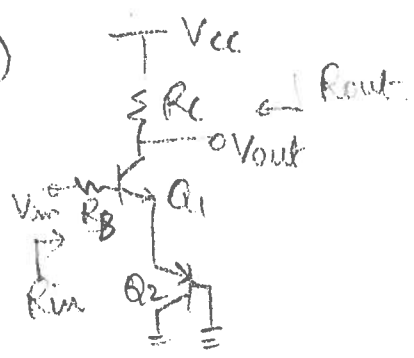


$$R_{in} = R_B + r_{\pi 1} + (1 + \beta_1) \left[\frac{1}{g_{m2}} \parallel r_{\pi 2} \right]$$

$$R_{out} = R_C$$

$$A_v = \frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2} + \frac{R_B}{1 + \beta_1}} = - \frac{\alpha R_C}{r_{e1} + r_{e2} + \frac{R_B}{\beta + 1}}$$

8

(e)

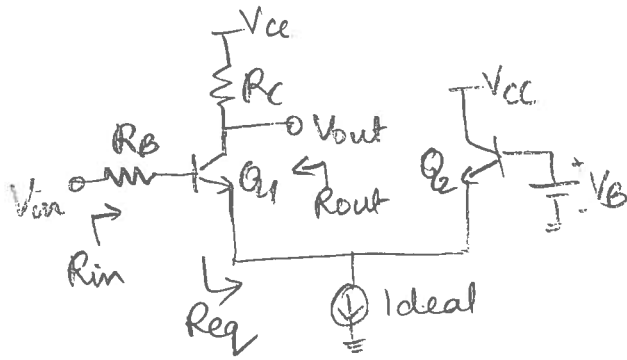

$$R_{in} = R_B + r_{\pi 1} + (1 + \beta_1) R_{eq}$$


$$\text{where } R_{eq} = \frac{1}{g_{m2}} \parallel r_{\pi 2} = r_{e2}$$

$$R_{out} = R_C$$

$$A_v = - \frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2} + \frac{R_B}{\beta + 1}} = - \frac{\alpha R_C}{r_{e1} + r_{e2} + \frac{R_B}{\beta + 1}}$$

5-52)

(a)

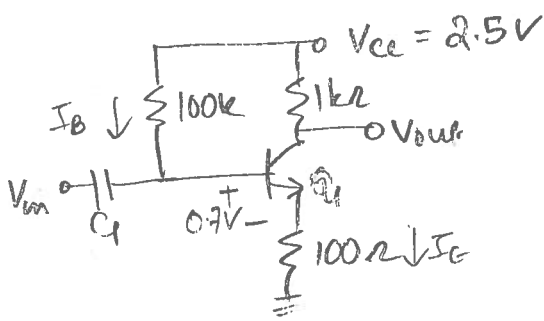

$$|A_v| = \frac{R_C}{\frac{1}{g_{m1}} + R_E} = \frac{1k}{100 + \frac{1}{g_{m1}}}$$

To find g_{m1} we analyse the DC operating point I_C for Q_1

Assume $V_{BE1} = 0.7V$ & $\beta = 100$. Then,

$$V_{CC} - I_B \times 100k - 0.7V - I_E \times 100\Omega = 0$$

$$2.5V - 0.7V = I_B [100k + (100 + 1)100] \quad \text{Using } I_E = (\beta + 1)I_B$$

$$\text{or } \boxed{I_B = 16.35 \mu A} \Rightarrow I_C = 100 \times 16.35 \mu A$$

$$\text{or } \boxed{I_C = 1.635 \text{ mA}}$$



$$\therefore g_{m1} = \frac{I_C}{V_T} = \frac{1.635 \text{ mA}}{25 \text{ mV}}$$

$$\text{or } \boxed{g_{m1} = 0.0654 \text{ S}^{-1}}$$

$$\therefore |A_v| = \frac{1k}{100 + \frac{1}{0.0654}} \Rightarrow \boxed{|A_v| = 8.674}$$

(9)

(b)

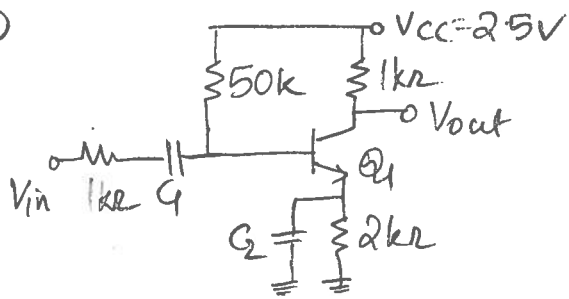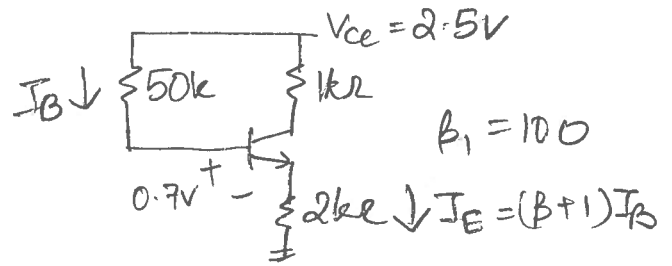DC Analysis (C_1, C_2 open)


$$V_{cc} - 0.7V - I_B \times 50k - 101 \times I_B \times 2k = 0$$

$$\text{or } I_B = \frac{2.5 - 0.7}{50k + 202k} = \underline{\underline{7.143 \mu A}}$$

$$\therefore I_C = \beta \times I_B = \underline{\underline{714.3 \mu A}}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.7143 \text{ mA}}{25 \text{ mV}} = \underline{\underline{0.02852 \text{ S}}}$$

$$r_\pi = \frac{\beta}{g_m} \text{ or } r_\pi = \underline{\underline{3.57k\Omega}}$$

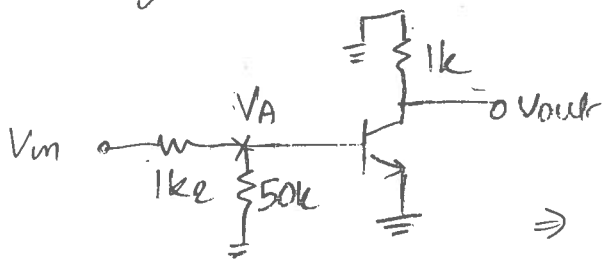AC Analysis: (C_1, C_2 short)

$$|A_v| = \frac{|V_{out}|}{|V_{in}|} = \frac{|V_{out}|}{|V_A|} \cdot \frac{|V_A|}{|V_{in}|}$$

$$\Rightarrow \frac{|V_A|}{|V_{in}|} = \frac{50k \parallel r_\pi}{1k + 50k \parallel r_\pi} = 0.769$$


$$\frac{|V_{out}|}{|V_A|} = g_m \times 1k = 28$$

$$\therefore |A_v| = 28 \times 0.769 \Rightarrow \boxed{|A_v| = 21.532}$$

(c)

DC Analysis:

Given $\beta = 100$
 $V_{BE} = 0.7V$

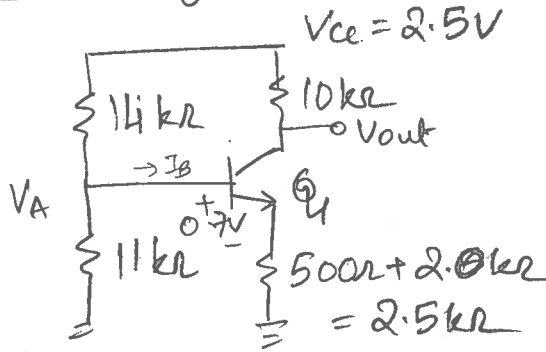

$$V_A = 0.7 + (\beta + 1) I_B \times 2.5k$$

$$V_A = 0.7 + 2.5k \times 101 \times I_B$$

$$I_B = \frac{V_{cc} - V_A}{14k} - \frac{V_A}{11k} = \frac{2.5 - 0.7}{14k} - \frac{2.5k \times 101 I_B}{14k} - \frac{0.7}{11k} - \frac{2.5k \times 101 I_B}{11k}$$

$$\Rightarrow I_B \left[1 + \frac{2.5 \times 101}{14} + \frac{2.5 \times 101}{11} \right] = \frac{2.5}{14k} - \frac{0.7}{11k} = 51.29 \mu$$

$$I_B \times 41.99 = 51.29 \mu \quad \text{or} \quad \boxed{I_B = 1.2215 \mu A}$$


$$I_C = \beta I_B \Rightarrow \boxed{I_C = 122.15 \mu A}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.12215 \text{ mA}}{25 \text{ mV}} = \underline{\underline{0.00489 \Omega^{-1}}}$$

$$r_\pi = \frac{\beta}{g_m} = \underline{\underline{20.5 k\Omega}}$$

AC Analysis:

$$(A_V) = \frac{|V_{out}|}{|V_{in}|} = \frac{|V_{out}|}{|V_A|} \cdot \frac{|V_A|}{|V_{in}|}$$

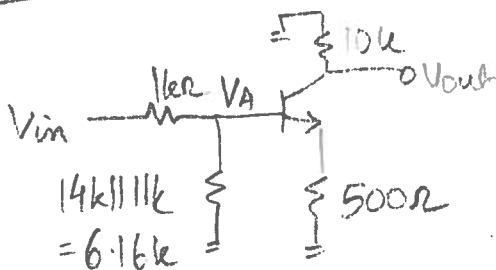

$$\frac{|V_A|}{|V_{in}|} = \frac{6.16k \parallel (r_\pi + (\beta + 1)0.5k)}{1k + 6.16k \parallel (r_\pi + (\beta + 1)0.5k)}$$


$$\frac{|V_A|}{|V_{in}|} = 0.86$$

$$\frac{|V_{out}|}{|V_A|} = \frac{10k}{0.5k + \frac{1}{g_m}} = 14.2$$

$$\Rightarrow |A_V| = 14.2 \times 0.86 \Rightarrow \boxed{|A_V| = 12.2}$$

(11)


5.56) (a)

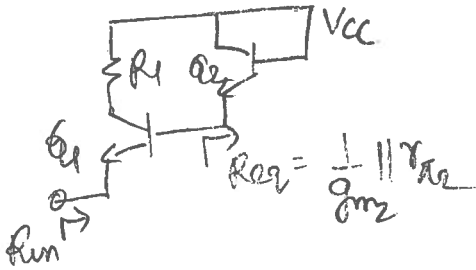

$$R_{in} = \frac{r_{\pi 1} + R_{eq}}{\beta_1 + 1}$$

$$= \text{or } R_{in} = \frac{r_{\pi 1} + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\beta_1 + 1} = r_{e1} + \frac{r_{e2}}{\beta_1 + 1}$$

(b)

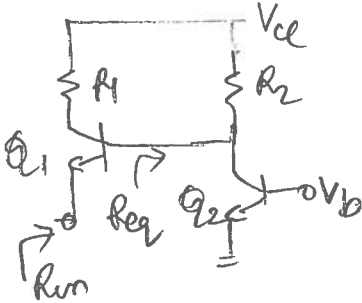


$$R_{eq} = R_2$$

$$R_{in} = \frac{r_{\pi 1} + R_{eq}}{\beta_1 + 1}$$

$$\Rightarrow R_{in} = \frac{r_{\pi 1} + R_2}{\beta_1 + 1} = r_{e1} + \frac{R_2}{\beta_1 + 1}$$

(c)

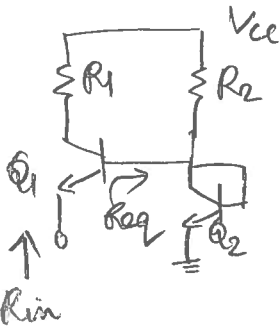


$$R_{eq} = R_2 \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$R_{in} = \frac{r_{\pi 1} + R_{eq}}{\beta_1 + 1}$$

$$\Rightarrow R_{in} = \frac{r_{\pi 1} + R_2 \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\beta_1 + 1} = r_{e1} + \frac{R_2 \parallel r_{e2}}{\beta_1 + 1}$$

(d)

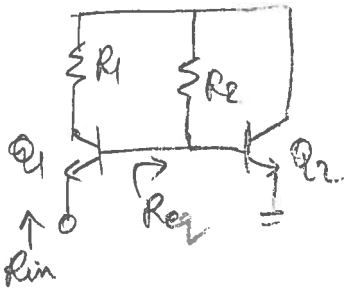


$$R_{eq} = R_2 \parallel r_{\pi 2} \quad R_{in} = \frac{r_{\pi 1} + R_{eq}}{\beta_1 + 1}$$

$$\Rightarrow R_{in} = \frac{r_{\pi 1} + R_2 \parallel r_{\pi 2}}{\beta_1 + 1} = r_{e1} + \frac{R_2 \parallel r_{\pi 2}}{\beta_1 + 1}$$

5.58) (a)

DC Analysis:

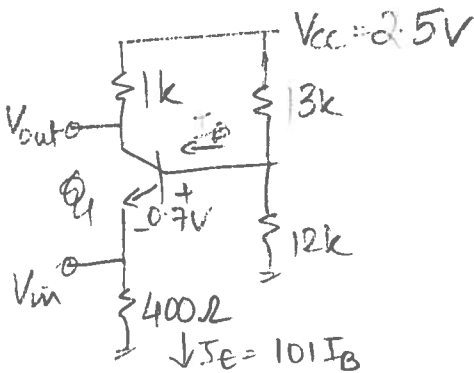

Given $V_{BE} = 0.7V$ & $\beta = 100$

$$I_B = \frac{V_{cc} - 0.7 - (101 I_B \times 0.4k)}{13k} = \frac{0.7 + 101 I_B \times 0.4}{12k}$$

$$\Rightarrow I_B = \frac{1.8}{13k} - \frac{0.7}{12k} - I_B \left[\frac{101 \times 0.4}{13} + \frac{101 \times 0.4}{12} \right]$$

$$\Rightarrow I_B = \frac{80 \mu A}{7474} \Rightarrow \boxed{I_B = 10.7 \mu A}$$

$$I_c = 100 I_b \Rightarrow \boxed{I_c = 1.07 \text{ mA}}$$


$$g_m = \frac{I_c}{V_T} = \frac{1.07 \text{ mA}}{25 \text{ mV}} \Rightarrow \boxed{g_m = 0.0428 \text{ S}}$$

$$r_{\pi} = \frac{\beta}{g_m} \Rightarrow \boxed{r_{\pi} = 2.336 \text{ k}\Omega}$$

$$V_{CE} = 2.5 \text{ V} - \underbrace{1.07 \text{ mA} \times 1 \text{ k}\Omega}_{1.07 \text{ V}} - \underbrace{\frac{101 \times 1.07 \text{ mA} \times 0.4 \text{ k}\Omega}{100}}_{0.4322 \text{ V}}$$

$$\Rightarrow \boxed{V_{CE} = 0.998 \text{ V}}$$

(b) AC Analysis:

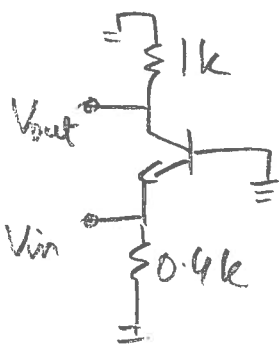


$$|A_v| = \frac{|V_{out}|}{|V_{in}|} = g_m \times 1 \text{ k}\Omega \Rightarrow \boxed{|A_v| = 42.8}$$

$$R_{in} = 0.4 \text{ k}\Omega \parallel \frac{1}{g_m} \Rightarrow \boxed{R_{in} = 0.39 \text{ k}\Omega}$$

$$\boxed{R_{out} = 1 \text{ k}\Omega}$$

5.73)

(a)

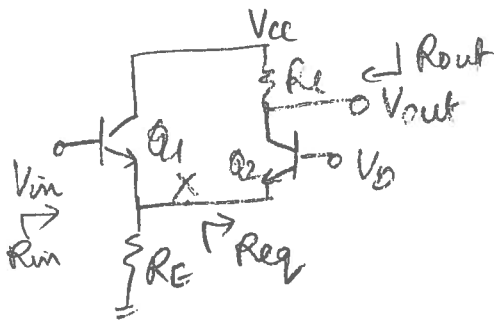

$$\boxed{R_{out} = R_C}$$

$$R_{eq} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$R_{in} = r_{\pi 1} + (\beta_1 + 1) R_{eq} \parallel R_E$$

$$\boxed{R_{in} = r_{\pi 1} + (\beta_1 + 1) \left[R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \right]}$$

$$= r_{\pi 1} + (\beta_1 + 1) (R_E \parallel r_{e2})$$

$$(b) \frac{|V_x|}{|V_{in}|} = \frac{R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$


$$\frac{|V_{out}|}{|V_x|} = g_{m2} R_C$$

$$|A_v| = \frac{|V_{out}|}{|V_{in}|} = \frac{|V_{out}|}{|V_x|} \cdot \frac{|V_x|}{|V_{in}|} \Rightarrow$$

$$\boxed{|A_v| = g_{m2} R_C \frac{R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}}$$

$$= g_{m2} R_C (R_E \parallel r_{e2})$$

5.83)

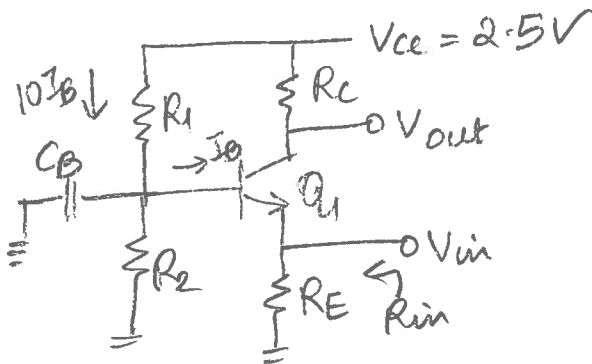

$$A_v = 20$$

$R_{in} = 50\Omega$ (R_{in} does not depend on R_E)

$$I_E R_E = 260\text{mV}$$

Since R_{in} does not depend on R_E , $R_{in} = \frac{1}{g_{m1}} = 50\Omega$

$$\Rightarrow \boxed{g_{m1} = 0.02\text{ S}^{-1}} \Rightarrow \frac{I_C}{V_T} = 0.02 \Rightarrow \boxed{I_C = 0.5\text{mA}}$$

$$\Rightarrow \boxed{I_B = 5\mu\text{A}} \Rightarrow I_E = 0.505\text{mA}$$

$$I_E R_E = 260\text{mV} \Rightarrow R_E = \frac{260\text{mV}}{0.505\text{mA}} \Rightarrow \boxed{R_E = 514.85\Omega}$$

$$A_v = g_{m1} R_C = 20 \Rightarrow R_C = \frac{20}{g_{m1}} \Rightarrow \boxed{R_C = 1\text{k}\Omega}$$

$$I_{R1} = 10I_B \Rightarrow \frac{V_{CC} - V_{BE1} - 260\text{mV}}{R_1} = 10I_B$$

$$\Rightarrow R_1 = \frac{2.5 - 0.7 - 0.26}{10 \times 5\mu} \Rightarrow \boxed{R_1 = 30.8\text{k}\Omega}$$

$$I_{R2} = I_{R1} - I_B = 9I_B \Rightarrow \frac{V_{BE1} + 0.26\text{V}}{R_2} = 9I_B$$

$$\Rightarrow R_2 = \frac{0.7 + 0.26}{9 \times 5\mu} \Rightarrow \boxed{R_2 = 21.33\text{k}\Omega}$$

Assuming the impedance of capacitance $|\frac{1}{sC_B}| \ll R_1, R_2$

We can write $A_v = \frac{R_C}{\frac{1}{g_{m1}} + \frac{sC_B}{\beta_1 + 1}}$ Now for this gain to

have no dependance on A_v , we can assume

$$\frac{1}{\beta_1(\beta_1 + 1)} \ll \frac{1}{g_{m1}}$$

Therefore at the lowest frequency of interest $f=200\text{Hz}$,
we can assume,

$$\frac{1}{sC_B(\beta+1)} = \frac{1}{10g_{m1}} \Rightarrow \frac{1}{2\pi(200)C_B(101)} = 5$$

$$\Rightarrow C_B = \frac{1}{2\pi \times 200 \times 101 \times 5} \Rightarrow \boxed{C_B = 1.58\mu\text{F}}$$