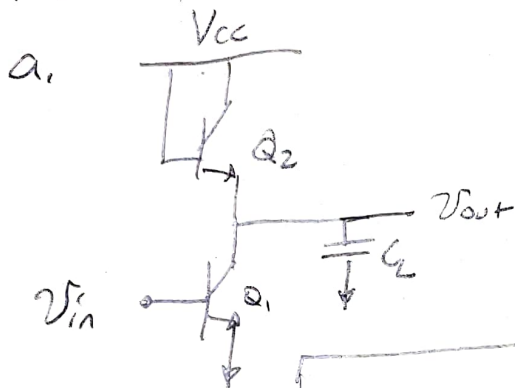



11.3



$$\omega_{3dB} = \frac{1}{R_{out} C_L}$$

$$R_{out} = r_{e2}$$

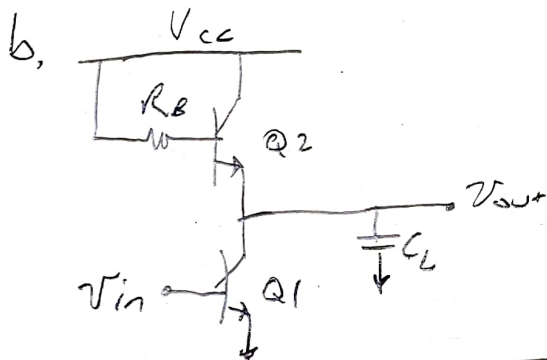
$$\omega_{3dB} = \frac{1}{r_{e2} C_L} \approx \frac{g_{m2}}{C_L}$$



$$\omega_{3dB} = \frac{1}{R_{out} C_L}$$

$$R_{out} = r_{e2} + \frac{R_B}{\beta + 1}$$

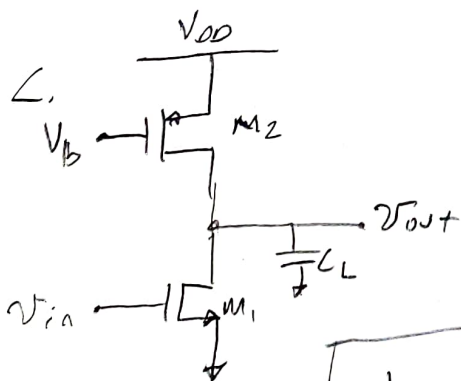
$$\omega_{3dB} = \frac{1}{\left(r_{e2} + \frac{R_B}{\beta + 1}\right) C_L} = \frac{g_{m2} (\beta + 1)}{\beta + g_{m2} R_B}$$



$$\omega_{3dB} = \frac{1}{R_{out} C_L}$$

$$R_{out} = r_{o1} \parallel r_{o2}$$

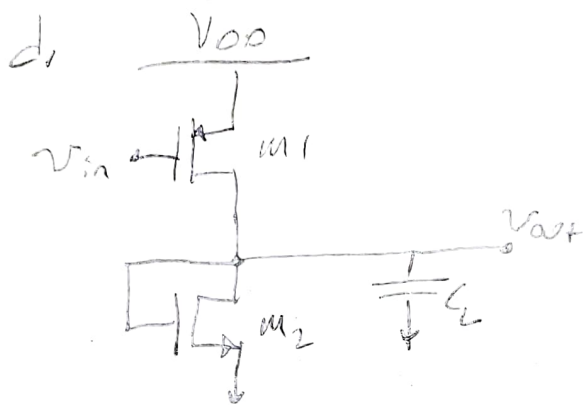
$$\omega_{3dB} = \frac{1}{(r_{o1} \parallel r_{o2}) C_L} = \frac{g_{o1} + g_{o2}}{C_L}$$




$$\omega_{3dB} = \frac{1}{R_{out} C_L}$$

$$R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}$$
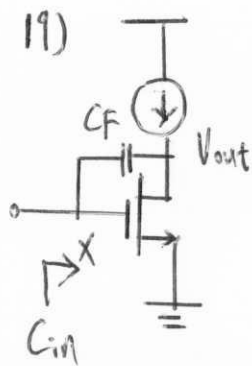
$$\omega_{3dB} = \frac{1}{(r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}) C_L} = \frac{g_{o1} + g_{o2} + g_{m2}}{C_L} \approx \frac{g_{m2}}{C_L}$$



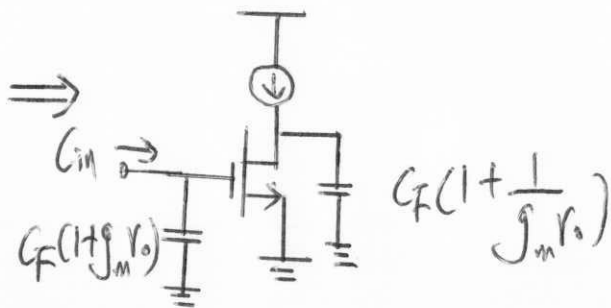
$$\lambda > 0, \text{ DC gain} = -g_m V_o$$



$$C_{in} = C_F (1 + g_m V_o), \text{ neglecting other caps.}$$

$$\text{As } \lambda \rightarrow 0, V_o \rightarrow \infty, \text{ DC gain} \rightarrow \infty,$$
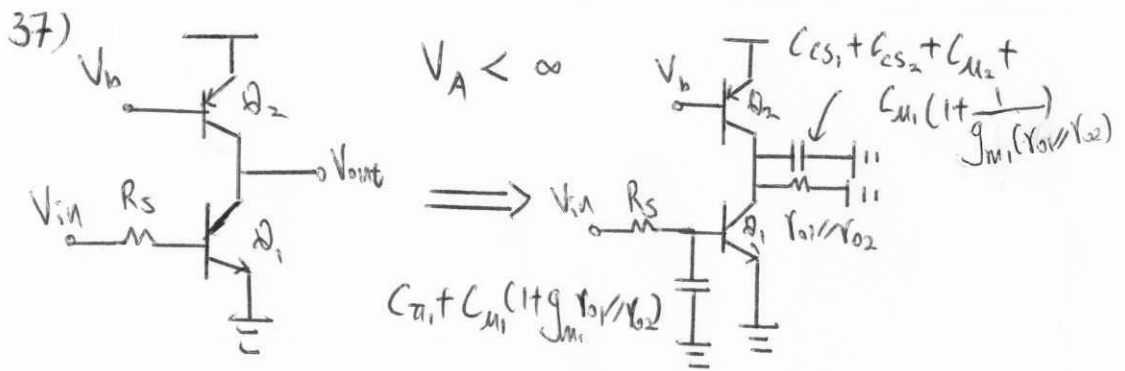
$$C_{in} \rightarrow \infty, \text{ this bandwidth will } \rightarrow 0.$$



$$A_{pin} = \frac{1}{(R_s // V_A) [C_{\pi 1} + C_M (1 + g_{m1}(V_{o1} // V_{o2}))]}$$


$$A_{pout} = \frac{1}{(V_{o1} // V_{o2}) [C_{cs1} + C_{cs2} + C_{m2} + C_{m1} (1 + 1 / (g_{m1}(V_{o1} // V_{o2})))]}$$

$$g_m V_o \gg 1$$

$$H(s) = \frac{g_m(V_{o1} // V_{o2}) (V_A // V_A + R_s)}{(1 + R_s [C_{\pi 1} + C_M (g_m(V_{o1} // V_{o2}))] s) (1 + (V_{o1} // V_{o2}) [C_{cs1} + C_{cs2} + C_{m2} + C_{m1}] s)}$$

46)

a)

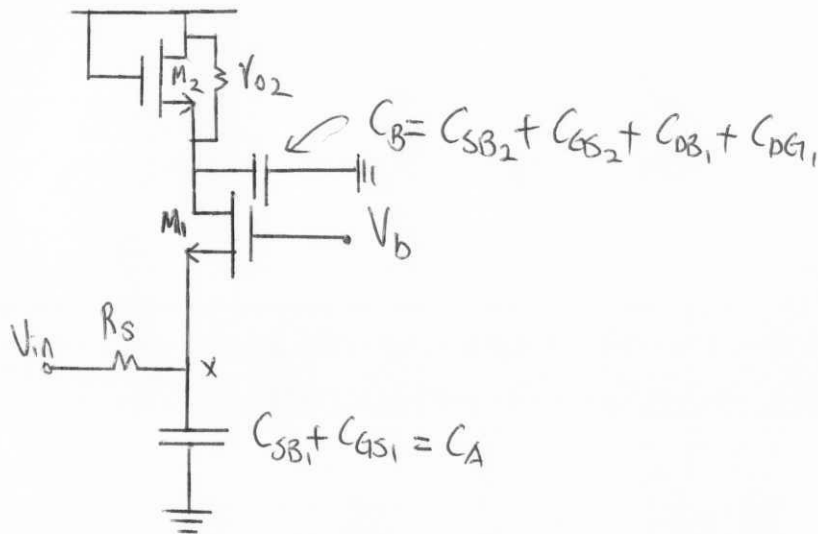

$$V_{out} = -(0 - V_x) g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right] = V_x g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right]$$

Node equation at X,  $\frac{V_x - V_{in}}{R_s} + V_x C_A s - g_m (0 - V_x) = 0$

$$V_x \left( \frac{1}{R_s} + C_A s + g_m \right) = \frac{V_{in}}{R_s} \Rightarrow V_x = \frac{V_{in}}{(1 + R_s C_A s + R_s g_m)}$$

substitute in  $V_x$  and solving for  $V_{out}/V_{in} \Rightarrow$


$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right]}{(1 + R_s C_A s + R_s g_m)}$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (1/g_{m2}) s + 1) (1 + R_s C_A s + R_s g_m)}$$


Where  $C_B = C_{SB2} + C_{GS2} + C_{DB1} + C_{DG1}$

$$C_A = C_{SB1} + C_{GS1}$$

11.48

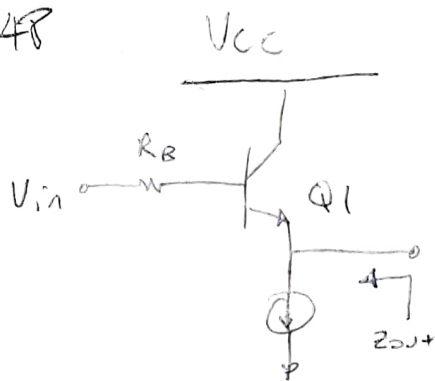

For AC Response

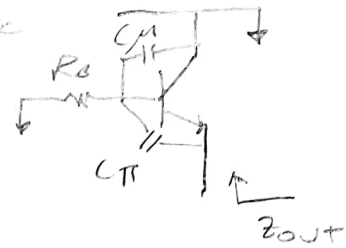

This is the same circuit in lecture 6, slide 62, but now we are including  $C_{\mu}$ .

We can start with the same transfer function and substitute

$$R_B \rightarrow R_B \parallel \frac{1}{sC_{\mu}} = \frac{R_B}{1 + sR_B C_{\mu}}$$

$$Z_{out} = \frac{\left( \frac{R_B}{1 + sR_B C_{\mu}} \right) r_{\pi} C_{\pi} s + r_{\pi} + \frac{R_B}{1 + sR_B C_{\mu}}}{r_{\pi} C_{\pi} s + \beta + 1}$$

$$= \frac{R_B r_{\pi} C_{\pi} s + r_{\pi} (1 + sR_B C_{\mu}) + R_B}{(r_{\pi} C_{\pi} s + \beta + 1) (1 + sR_B C_{\mu})}$$

$$Z_{out} = \frac{sR_B r_{\pi} (C_{\pi} + C_{\mu}) + r_{\pi} + R_B}{(r_{\pi} C_{\pi} s + \beta + 1) (1 + sR_B C_{\mu})}$$