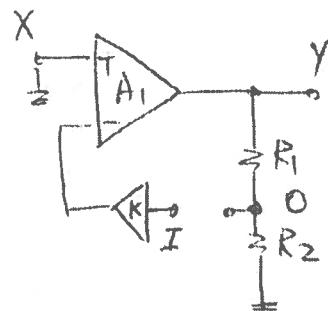


4.

(a)




$$O = Y \frac{R_2}{R_1 + R_2} = (-IK)A_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\Rightarrow -\frac{O}{I} = \text{Loop Gain} \\ = +KA_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

(X is grounded  
in loop-gain calculation)

(b)

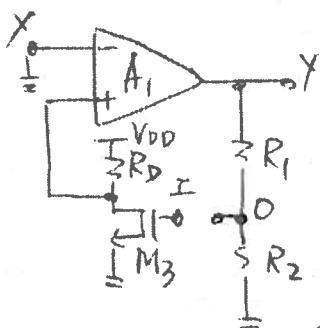

$$O = Y \left( \frac{R_2}{R_1 + R_2} \right)$$


$$= -IGm_3 R_D A_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\Rightarrow -\frac{O}{I} = \text{Loop Gain}$$

$$= +g_{m3} R_D A_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

(X is grounded)

(c)

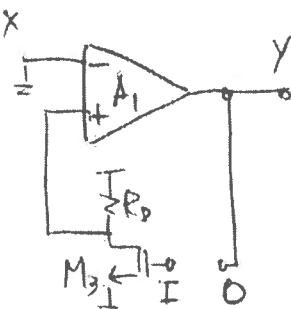


$$O = Y = -IGm_3 R_D A_1$$

$$\Rightarrow -\frac{O}{I} = \text{Loop Gain}$$

$$= +g_{m3} R_D A_1$$

(X is grounded)

(d)

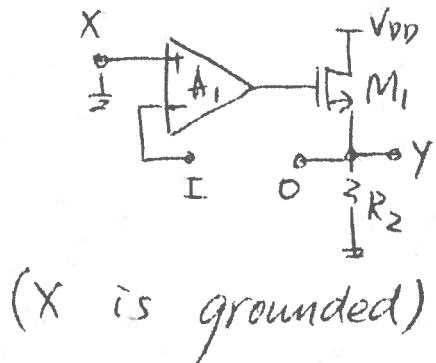


( $X$  is grounded)

$$0 = Y = -I \times \frac{g_m R_2}{1 + g_m R_2} \times A_1$$

$\Rightarrow \frac{O}{I} = \text{Loop Gain}$

$$= +A_1 \frac{g_m R_2}{1 + g_m R_2}$$

5. a.

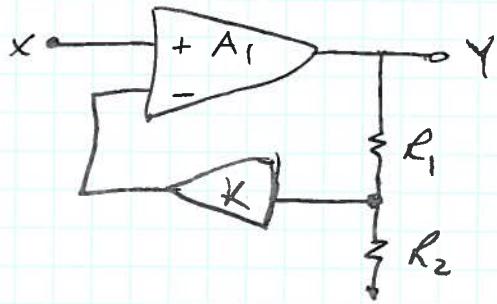


$$A_{OL} = A_1$$

$$\text{FB Factor} = \left( \frac{R_2}{R_1 + R_2} \right) K$$

$$\boxed{\frac{Y}{X} = \frac{A_1}{1 + \left( \frac{R_2}{R_1 + R_2} \right) K A_1}}$$

b.

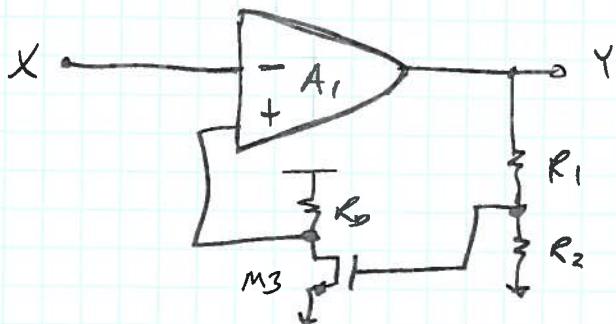


$$A_{OL} = -A_1$$

$$\text{FB Factor} = \left( \frac{R_2}{R_1 + R_2} \right) (-g_{m3} R_o)$$

$$\boxed{\frac{Y}{X} = \frac{-A_1}{1 + \left( \frac{R_2}{R_1 + R_2} \right) (g_{m3} R_o) (A_1)}}$$

c.

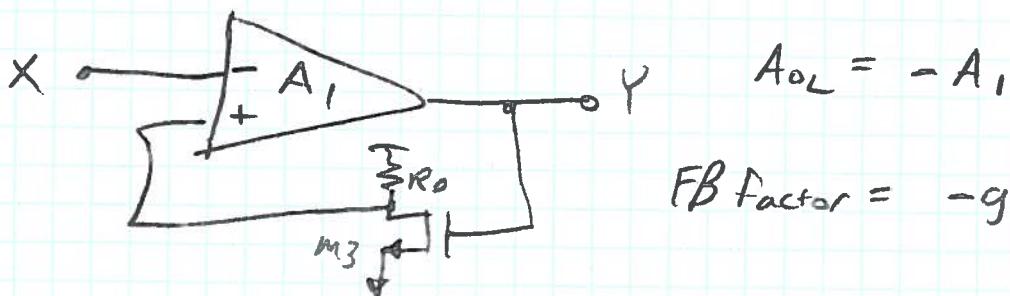


$$A_{OL} = -A_1$$

$$\text{FB Factor} = -g_{m3} R_o$$

$$\boxed{\frac{Y}{X} = \frac{-A_1}{1 + g_{m3} R_o A_1}}$$


d.

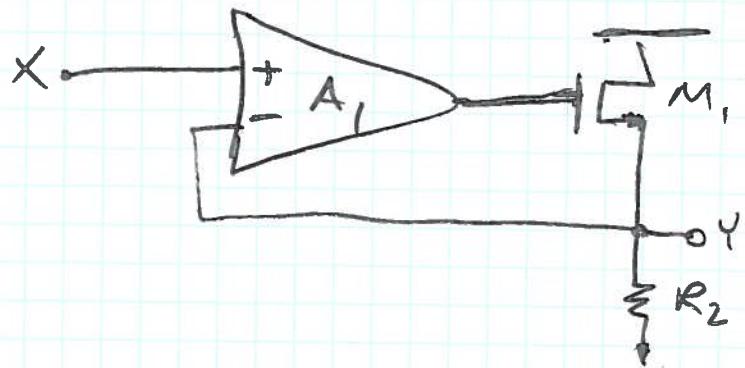

$$A_{OL} = \frac{A_1 R_2}{g_m + R_2} = \frac{A_1 g_m R_2}{1 + g_m R_2}$$

FB factor = 1
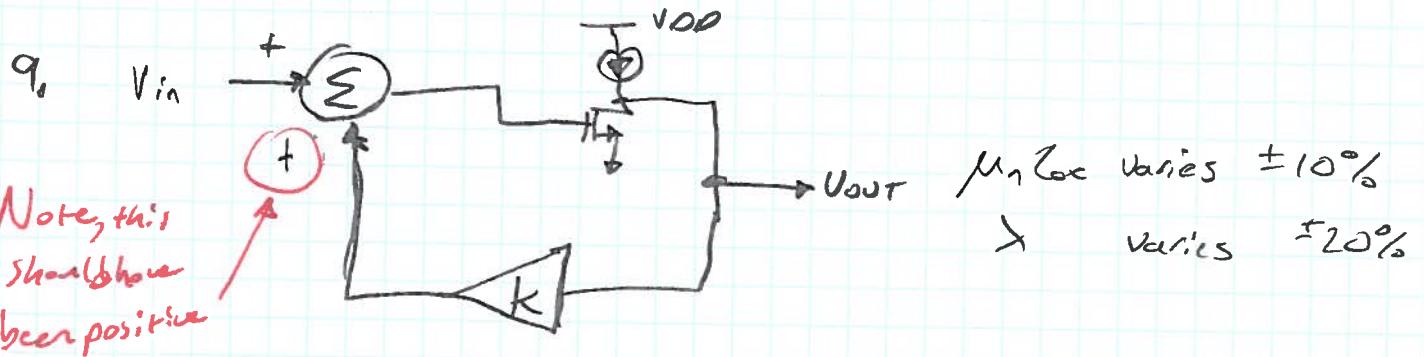
$$\frac{Y}{X} = \frac{\frac{A_1 g_m R_2}{1 + g_m R_2}}{1 + \frac{A_1 g_m R_2}{1 + g_m R_2}}$$



$$A_{OL} = -g_m I_{O1} \quad \text{FB Factor} = K$$

$$\frac{V_{out}}{V_{in}} = \frac{A_{OL}}{1+KA_{OL}} = \frac{-g_m I_{O1}}{1 + K g_m I_{O1}} = \frac{-(\sqrt{\mu_{n,\text{Zac}} \frac{W}{L}} 2 I_0) \left( \frac{1}{\lambda I_0} \right)}{1 + k(\sqrt{\mu_{n,\text{Zac}} \frac{W}{L}} 2 I_0) \left( \frac{1}{\lambda I_0} \right)}$$

First consider "High" Variation

$$\frac{|A_{OL}|}{1-KA_{OL}} = \frac{|A_{OL}|}{1+LG} = \frac{\frac{\sqrt{1.1}}{0.8} |A_{OL}|}{1 + \frac{\sqrt{1.1}}{0.8} LG} \leq \frac{1.05 / |A_{OL}|}{1+LG}$$

$$\frac{\sqrt{1.1}}{0.8} (1+LG) \leq 1.05 + \frac{1.05 \sqrt{1.1}}{0.8} LG$$

$$\frac{0.05 \sqrt{1.1}}{0.8} LG \geq \frac{\sqrt{1.1}}{0.8} - 1.05$$

$$LG \geq 3.98$$

Next consider "Low" Variation

$$\frac{|A_{OL}|}{1+LG} = \frac{\frac{\sqrt{0.9}}{1.2} |A_{OL}|}{1 + \frac{\sqrt{0.9}}{1.2} LG} \geq \frac{0.95 / |A_{OL}|}{1+LG}$$

$$\frac{\sqrt{0.9}}{1.2} (1+LG) \geq 0.95 + \frac{0.95 \sqrt{0.9}}{1.2} LG$$

$$\frac{0.05 \sqrt{0.9}}{1.2} LG \geq 0.95 - \frac{\sqrt{0.9}}{1.2}$$


$$LG \geq 4.03 \quad (\text{larger than above})$$

22.

~~22.~~ First, recognize that

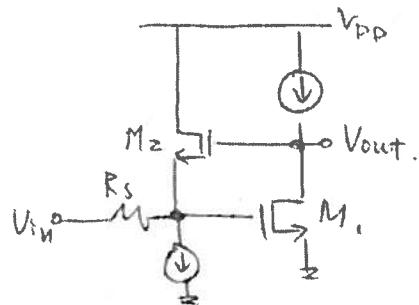- (a) both input & output  
are voltages.

\*  $V_{in}$  primarily drives the  
Gate of  $M_1$ .



Sequence: Suppose  $V_{in}$  increases by  $\Delta V_{in}$

$\Rightarrow V_{out}$  drops by  $+g_m \Delta V_{in} \times R_o$ , (Common-  
Source)

$\Rightarrow$  Source of  $M_2$  decreases by same  
amount (Source follower)

$\therefore V_{in} \uparrow \Rightarrow V_{M_1,D} \downarrow \Rightarrow V_{M_1,G} \downarrow$

$\Rightarrow$  effective  $V_{in}$  driving  $M_1,G \downarrow$

$\Rightarrow$  negative feedback

(b)  $V_{in} \uparrow \Rightarrow V_{out} \downarrow \Rightarrow V_{M_2,G} \uparrow$

$\Rightarrow$  effective  $V_{in}$  driving  $M_1,G \uparrow$

$\Rightarrow$  positive feedback

(c)  $V_{in} \uparrow \Rightarrow V_{out} \uparrow \Rightarrow U_{M_1,G} \uparrow$

$\Rightarrow$  effective  $V_{in}$  driving  $M_{1,G} \uparrow$

$\Rightarrow$  negative feedback.


(d)  $V_{in} \uparrow \Rightarrow V_{out} \uparrow$  (common-base,  $M_1$ )

$\Rightarrow U_{M_1,S} \downarrow$


$\Rightarrow$  effective  $V_{in}$  driving  $M_{1,S} \downarrow$

$\Rightarrow$  negative feedback.

27.

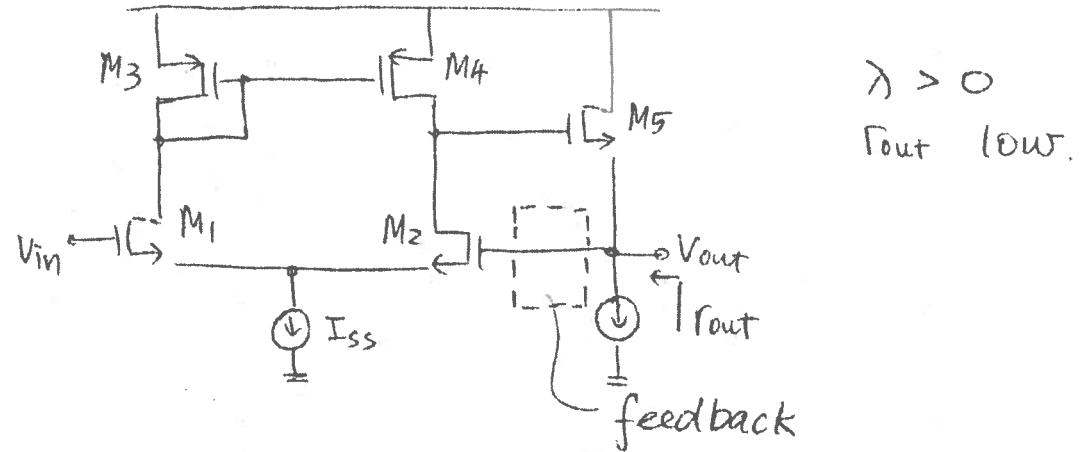

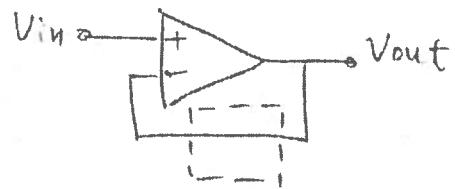Note that  $V_{out}$  is directly fed back to input:



$\therefore \text{gain} \approx 1$   
(a buffer)  
 $\Rightarrow k = 1$ .

A.O.L. (i.e. without feedback)


$$= g_m, (R_{O2} \parallel R_{O4}) \times \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \quad (\approx g_m, (R_{O2} \parallel R_{O4}))$$

$$\Rightarrow A_{C.L.} = \frac{A_{O.L.}}{1 + A_{O.L.} \cdot k} = \frac{g_m, (R_{O2} \parallel R_{O4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right)}{1 + g_m, (R_{O2} \parallel R_{O4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right)}$$

$$R_{out} = \frac{R_{out}(\text{no feedback})}{1 + A_{O.L.} \cdot k} = \frac{\left( \frac{1}{g_{m5}} \parallel r_{o5} \right)}{1 + g_m, (R_{O2} \parallel R_{O4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right)}$$

$$\text{Gain} = A = \frac{g_m r_o}{g_m r_o + 1}$$
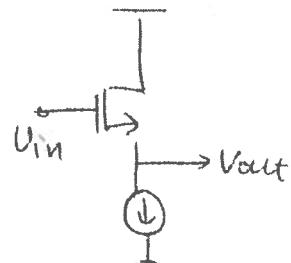
$$r_{\text{out}} = \frac{1}{g_m} \parallel r_o$$



$$\gamma > 0$$

In comparison, the amplifier's gain is reduced by  $\frac{g_{m1}(r_{o2} \parallel r_{o4})}{1 + g_{m1}(r_{o2} \parallel r_{o4})(\frac{g_{m5}r_{o5}}{g_{m5}r_{o5} + 1})}$  times.

(=  $\frac{\text{A.C.L.}}{A}$ ). Output resistance of the amplifier is reduced by  $[1 + g_{m1}(r_{o2} \parallel r_{o4})(\frac{g_{m5}r_{o5}}{g_{m5}r_{o5} + 1})]$  times.

33.

27.

$$R_{o.L.} = \frac{V_{out}}{i_{in}} \quad (\text{no feedback})$$

$$= R_D$$


K (feedback factor)

$$= g_{m_2} \times \frac{R_2}{R_1 + R_2}$$

$$\Rightarrow R_{c.L.} = \frac{V_{out}}{i_{in}} = \frac{R_D}{1 + R_D \times g_{m_2} \frac{R_2}{R_1 + R_2}}$$

$$r_{in}|_{c.L.} = \frac{g_{m_1}}{1 + R_D \times g_{m_2} \frac{R_2}{R_1 + R_2}}$$

$$r_{out}|_{c.L.} = \frac{R_D}{1 + R_D \times g_{m_2} \frac{R_2}{R_1 + R_2}}$$

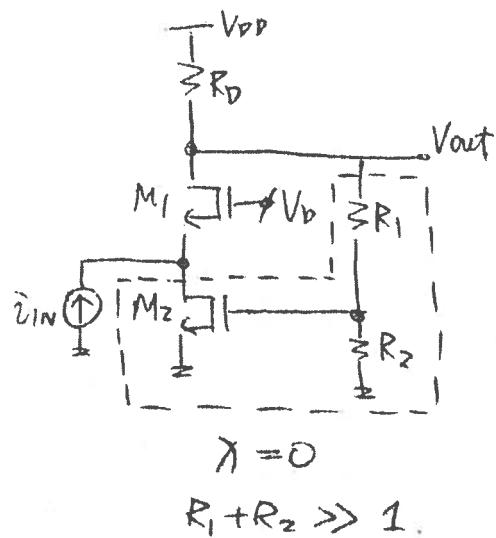

35.

36.

(a)  $G_{OL} = \frac{i_{out}}{v_{in}} = g_m, A_1$   
(common emitter)


(b)  $K$  (feedback factor)

$$\Rightarrow V_F = i_{out} \times R_M$$

$$\Rightarrow K = \frac{V_F}{i_{out}} = R_M$$


$$\therefore \text{Loop Gain} = G_{OL}K = g_m, A_1 R_M$$
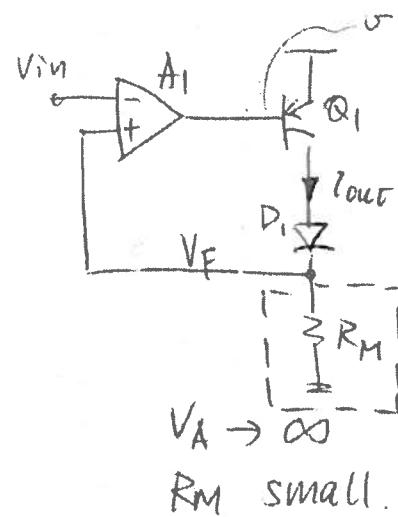
$$G_{CL} = \frac{G_{OL}}{1 + G_{OL}K} = \frac{g_m, A_1}{1 + g_m, A_1 R_M}$$




$R_M$  small.

40.

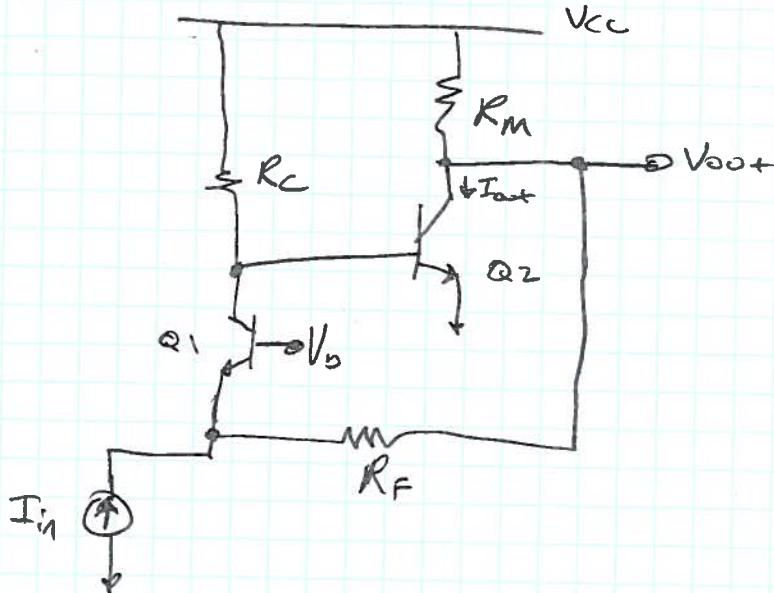 $R_M$  is small

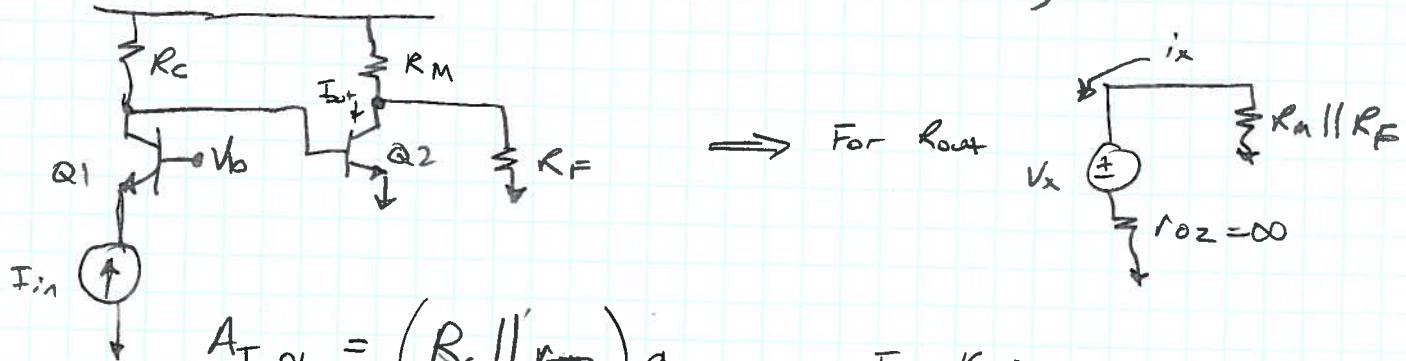
a. Breaking the loop (Current - Current FB)



$$A_{I,OL} = \left( R_C \parallel r_{\pi 2} \right) g_{m2}$$

$$R_{in,OL} = r_{c1} \approx \frac{1}{g_{m1}}$$

$$R_{out,OL} = \infty$$

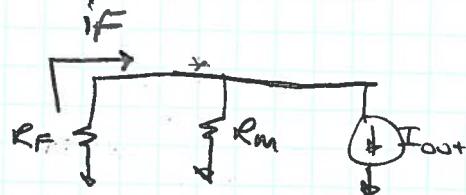For  $K$ :

$$A_{I,CL} = \frac{g_{m2} (R_C \parallel r_{\pi 2})}{1 + \left( \frac{R_M}{R_F + R_M} \right) g_{m2} (R_C \parallel r_{\pi 2})}$$

$$\approx \frac{g_{m2} R_C}{1 + \frac{g_{m2} R_C R_M}{R_F}}$$


$$R_{out,CL} = \infty$$

$$K = \frac{R_M}{R_F + R_M} \approx \frac{R_M}{R_F}$$

$$R_{in,CL} = \frac{1/g_{m1}}{1 + \left( \frac{R_M}{R_F + R_M} \right) g_{m2} (R_C \parallel r_{\pi 2})}$$

$$\approx \frac{1/g_{m1}}{1 + \frac{g_{m2} R_C R_M}{R_F}}$$

b. Breaking the loop (Voltage - Current)

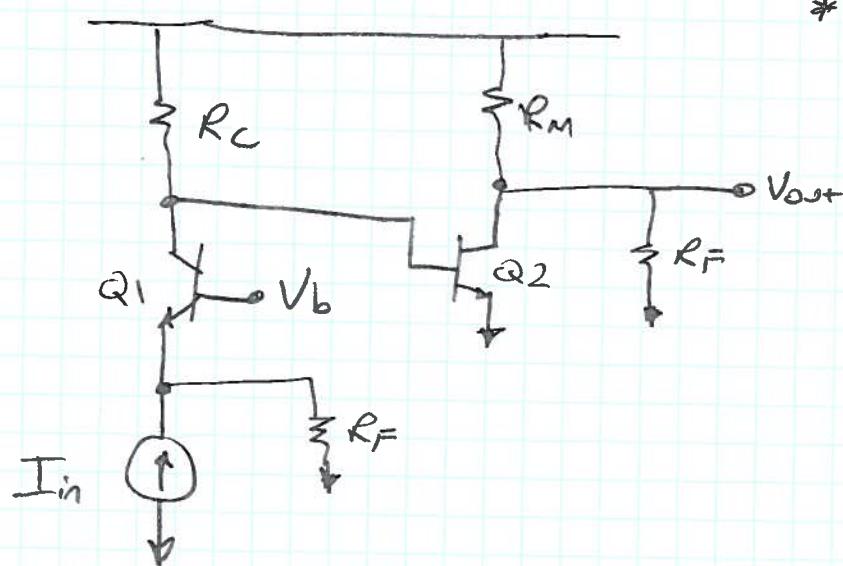


\* $R_F$  is very large

$$R_{OL} = \left( \frac{R_F}{R_F + r_{e1}} \right) (R_C || r_{\pi 2}) (-g_{m2}) (R_M || R_F)$$

$$\approx -g_{m2} R_M R_C$$

For K:

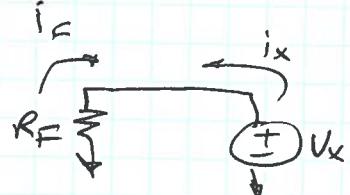

$$R_{in,OL} = R_F || r_{e1} \approx \frac{1}{g_{m1}}$$

$$R_{out,OL} = R_M || R_F \approx R_M$$

$$K = -\frac{1}{R_F}$$

$$R_{CL} \approx \frac{-g_{m2} R_M R_C}{1 + \frac{g_{m2} R_M R_C}{R_F}}$$

$$R_{in,CL} \approx \frac{\frac{1}{g_{m1}}}{1 + \frac{g_{m2} R_M R_C}{R_F}}$$

$$R_{out,CL} \approx \frac{R_M}{1 + \frac{g_{m2} R_M R_C}{R_F}}$$