
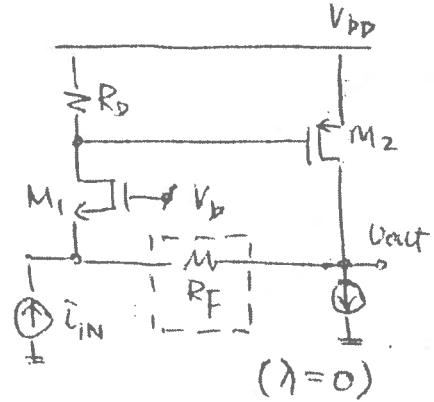


51.

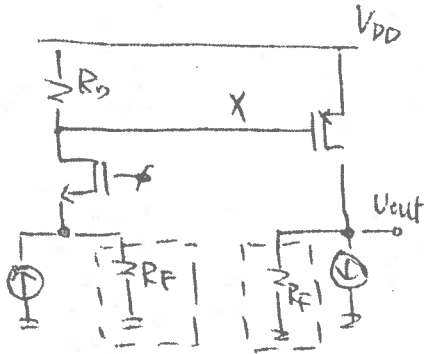(a) Breaking the feedback loop results in the following circuit:



$$R_{o.l.} = \frac{v_x}{i_{in}} \cdot \frac{v_{out}}{v_x}$$


$$= g_{m1} R_D \left(\frac{1}{g_{m1}} \parallel R_F \right) \times (g_{m2} R_F)$$

$$R_{in, OPEN} = \frac{1}{g_{m1}} \parallel R_F$$

$$R_{out, OPEN} = R_F$$

- Feedback factor k :

$$k = \frac{v_x}{i_x} = -\frac{1}{R_F}$$


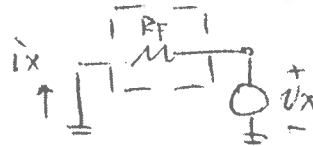


$$\Rightarrow R_{c.l.} = \frac{R_{o.l.}}{1 + R_{o.l.} \times k} = \frac{-g_{m1} g_{m2} R_D R_F \left(\frac{1}{g_{m1}} \parallel R_F \right)}{1 + g_{m1} g_{m2} R_D \left(\frac{1}{g_{m1}} \parallel R_F \right)}$$

$$R_{in, CLOSED} = \frac{\left(\frac{1}{g_{m1}} \parallel R_F \right)}{1 + g_{m1} g_{m2} R_D \left(\frac{1}{g_{m1}} \parallel R_F \right)}$$

$$R_{out, CLOSED} = \frac{R_F}{1 + g_{m1} g_{m2} R_D \left(\frac{1}{g_{m1}} \parallel R_F \right)}$$

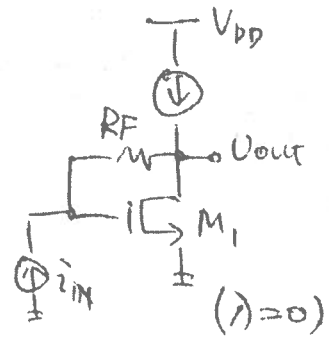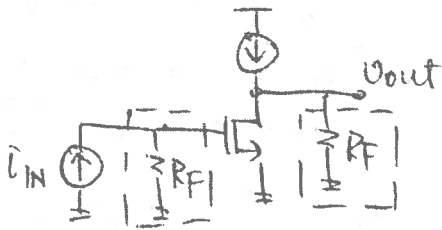(b) Breaking the feedback loop results in the following circuit:




$$R_{o.L.} = \frac{V_{out}}{i_{IN}} = -g_m R_F R_F = -g_m R_F^2$$

$$R_{in, OPEN} = R_F \quad R_{out, OPEN} = R_F$$

- Feedback factor K :

$$K = \frac{V_x}{i_x} = -\frac{1}{R_F}$$

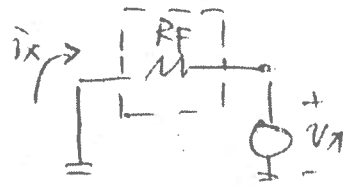
$$\Rightarrow R_{c.i.} = \frac{-g_m R_F^2}{1 + g_m R_F}$$




$$R_{in, CLOSED} = \frac{R_F}{1 + g_m R_F}$$

$$R_{out, CLOSED} = \frac{R_F}{1 + g_m R_F}$$

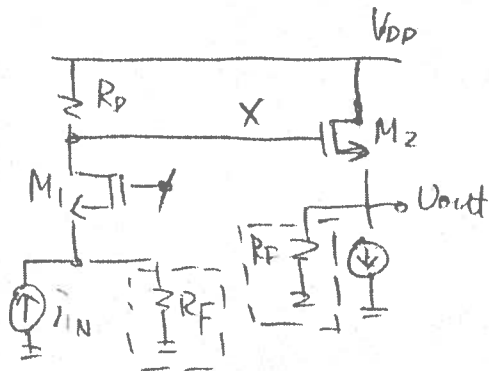(c) Breaking the feedback loop results in the following circuit:


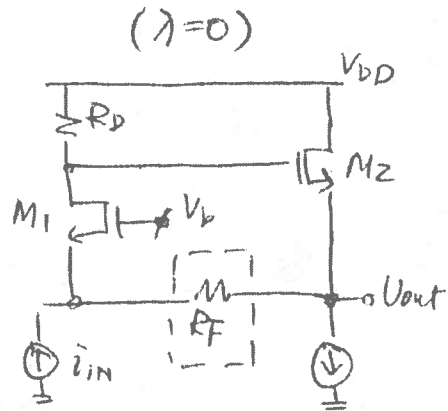
$$R_{in, OPEN} = \left(\frac{1}{g_{m1}} \parallel R_F \right)$$



$$\begin{aligned} R_{O.L.} &= \frac{U_{out}}{i_{IN}} = \frac{U_x}{i_{IN}} \cdot \frac{U_{out}}{U_x} \\ &= g_{m1} R_D \left(\frac{1}{g_{m1}} \parallel R_F \right) \times \\ &\quad g_{m2} \left(R_F \parallel \frac{1}{g_{m2}} \right) \end{aligned}$$

$$R_{out, OPEN} = \left(R_F \parallel \frac{1}{g_{m2}} \right)$$

- Feedback factor K :

$$K = \frac{U_x}{i_x} = -\frac{1}{R_F}$$







(Note: Feedback is positive.)

$$\begin{aligned} \Rightarrow R_{c.L.} &= \frac{R_{O.L.}}{1 + R_{O.L.} \times K} \\ &= \frac{g_{m1} g_{m2} R_D \left(\frac{1}{g_{m1}} \parallel R_F \right) \left(\frac{1}{g_{m2}} \parallel R_F \right)}{1 - g_{m1} g_{m2} \left(\frac{R_D}{R_F} \right) \left(\frac{1}{g_{m1}} \parallel R_F \right) \left(\frac{1}{g_{m2}} \parallel R_F \right)} \end{aligned}$$

$$R_{in, CLOSED} = \frac{\left(\frac{1}{g_{m1}} \parallel R_F \right)}{1 - \frac{R_{O.L.}}{R_F}}$$

$$R_{out, CLOSED} = \frac{\left(\frac{1}{g_{m2}} \parallel R_F \right)}{1 - \frac{R_{O.L.}}{R_F}}$$


57.

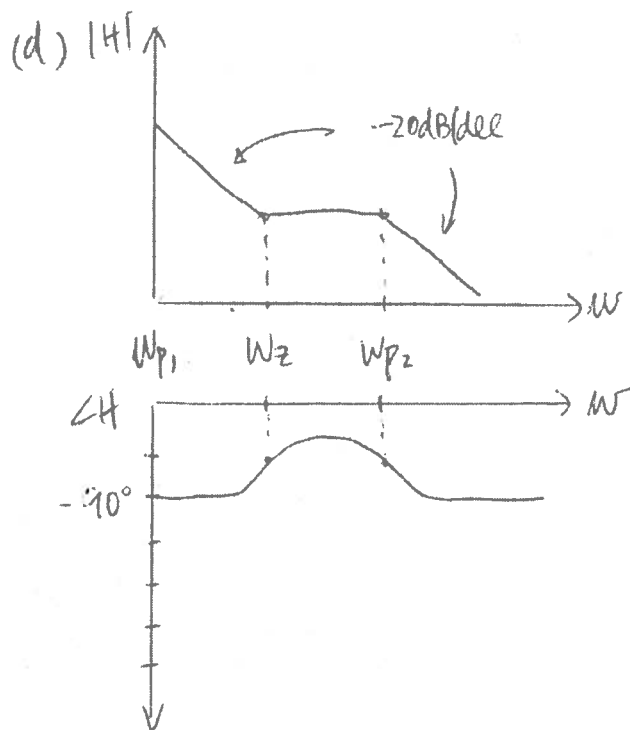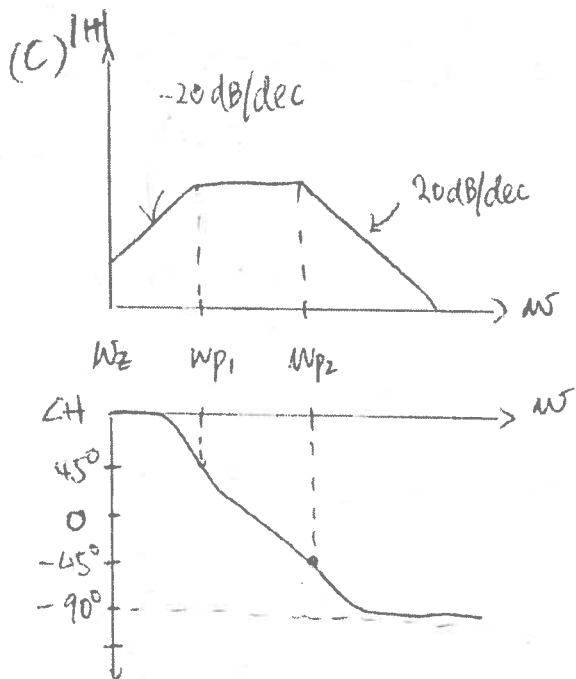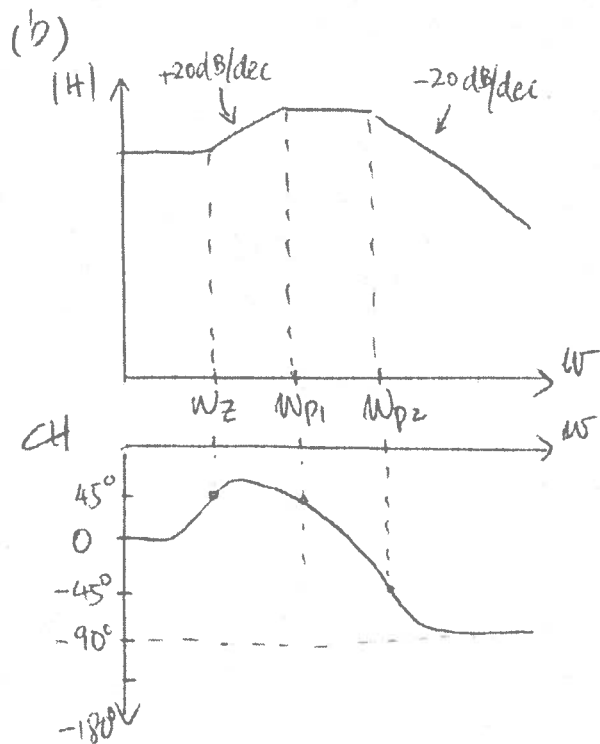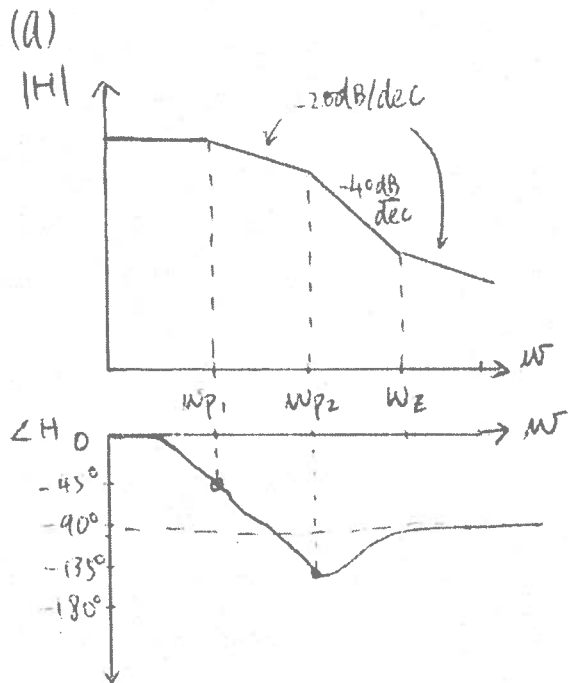

65.

$$H(s) = \frac{A_0}{1 + \frac{s}{\omega_p}}$$


$$k = 1.$$

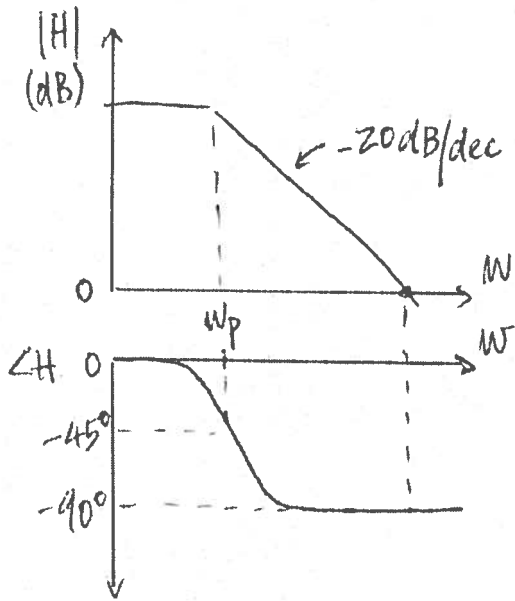

$$\therefore \text{Phase margin} = 180^\circ - 90^\circ = 90^\circ$$

(i.e. system is stable)

71.

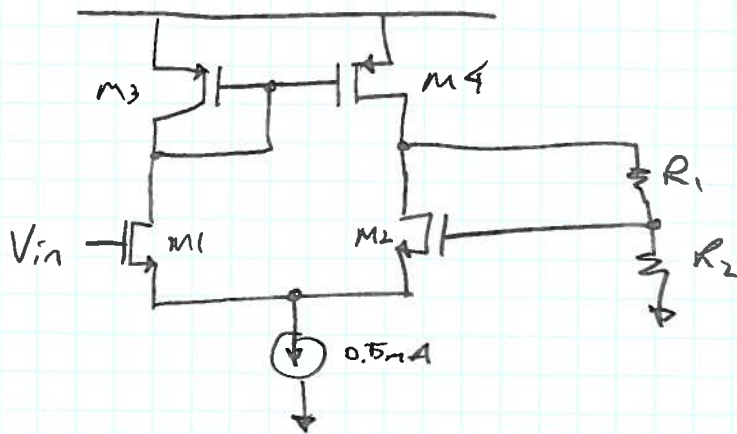

$$\text{Specs: } A_{OL} = 50$$

$$A_{CL} = 4$$

$$R_L + R_2 \approx 10(r_{o2} \parallel r_{o4})$$

As $R_L + R_2 \approx 10(r_{o2} \parallel r_{o4})$ we can neglect the output loading

$$A_{OL} = g_{m1} (r_{o2} \parallel r_{o4}) = 50$$

$$r_{o2} = \frac{1}{\lambda_N I_{D2}} = \frac{1}{(0.1V^{-1})(0.25mA)} = 40k\Omega$$

$$r_{o4} = \frac{1}{\lambda_P I_{D4}} = \frac{1}{(0.2V^{-1})(0.25mA)} = 20k\Omega$$

$$r_{o2} \parallel r_{o4} = 13.3k\Omega$$

$$g_{m1} = \frac{50}{13.3k\Omega} = 3.75 \text{ mA/V}$$

This can be achieved with

$$\frac{W}{L}_{1,2} = \frac{g_m^2}{\mu C_{ox} 2I_D} = \frac{(3.75 \text{ mA/V})^2}{(100 \text{ } \mu\text{A/V}^2)(2)(0.25 \text{ mA})} = 281$$

$$A_{CL} = \frac{A_{OL}}{1 + KA_{OL}}$$

$$K = \frac{A_{OL} - A_{CL}}{A_{OL} A_{CL}} = \frac{50 - 4}{(50)(4)} = 0.23$$


$$\text{Need: } k = \frac{R_2}{R_1 + R_2} = 0.23 \quad \text{and} \quad R_1 + R_2 = 10(13.3k\Omega)$$

$$R_2 = 0.23(133k\Omega) = 30.6k\Omega$$

$$R_1 = 133 \text{ kN} - 30.6 \text{ kN} = 102.4 \text{ kN}$$

$$R_1 = 102.4 \text{ kN}$$
$$R_2 = 30.6 \text{ kN}$$

75.

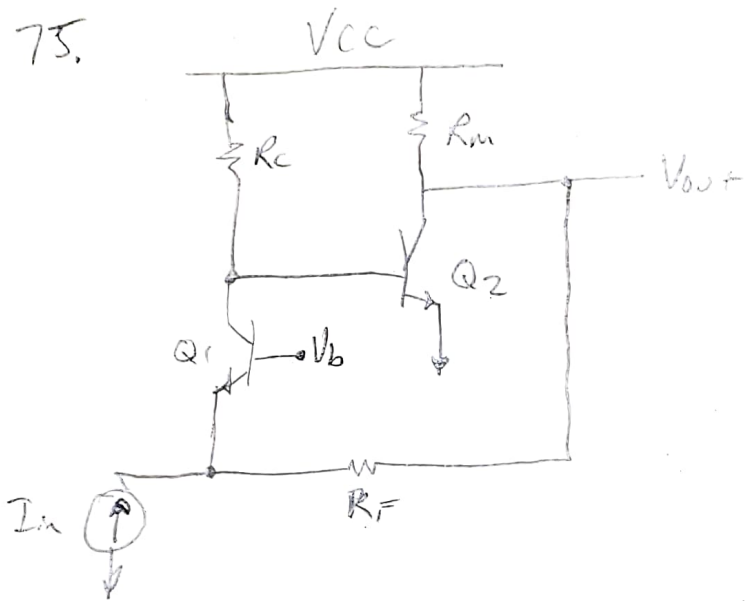

$$|R_{OL}| = 1k\Omega$$

$$I_{C1} = I_{C2} = 1mA$$


$$\beta = 100$$

$$V_A = \infty$$

R_F is large

Q. Need $|R_{OL}| = 20k\Omega$ $R_{out,OL} = 500\Omega$

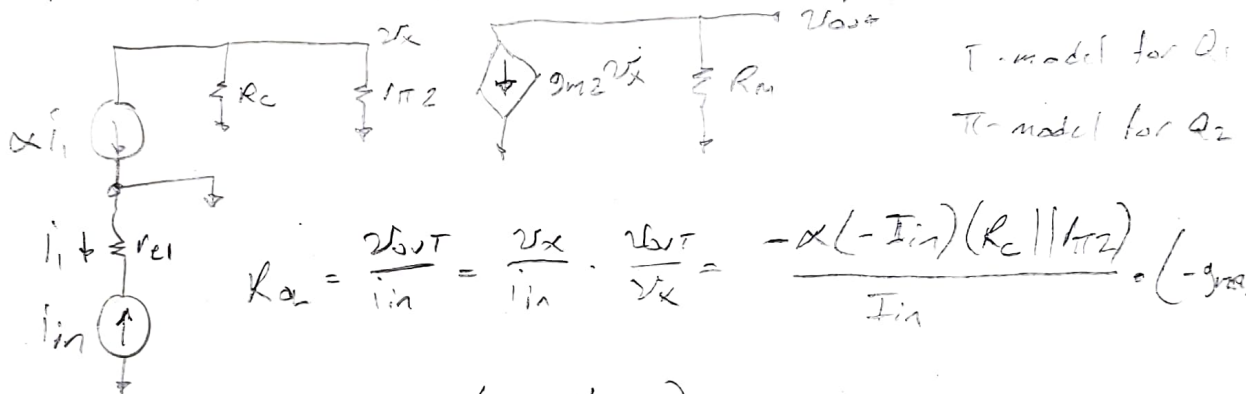Open-loop small-signal model w/ large R_F (ignored)



$$R_{OL} = \frac{v_{out}}{i_{in}} = \frac{v_x}{i_{in}} \cdot \frac{v_{out}}{v_x} = \frac{-\alpha(-I_{in})(R_C || r_{\pi 2})}{I_{in}} \cdot (-g_{m2} R_m)$$

$$R_{OL} = -\alpha(R_C || r_{\pi 2}) g_{m2} R_m$$

$$R_{out,OL} = \boxed{R_m = 500\Omega}$$

$$|R_{OL}| = \frac{\alpha g_{m2} R_m}{\frac{1}{R_C} + \frac{1}{r_{\pi 2}}} \Rightarrow \frac{1}{R_C} = \frac{\alpha g_{m2} R_m}{|R_{OL}|} - \frac{1}{r_{\pi 2}}$$

$$\frac{1}{R_C} = \frac{\left(\frac{100}{101}\right) \left(\frac{1mA}{25.9mV}\right) (500)}{20k\Omega} - \frac{1mA}{100(25.9mV)} = 570 \mu A/V$$


$$\boxed{R_C = 1.76k\Omega}$$

b. Find R_F for $R_{CL} = -1k\Omega$

$$R_{CL} = \frac{R_{OL}}{1 + KR_{OL}} \Rightarrow K = \frac{\frac{R_{OL}}{R_{CL}} - 1}{R_{OL}}$$

$$K = \frac{\frac{-20k\Omega}{-1k\Omega} - 1}{-20k\Omega} = -950 \text{ mA/V}$$

For K

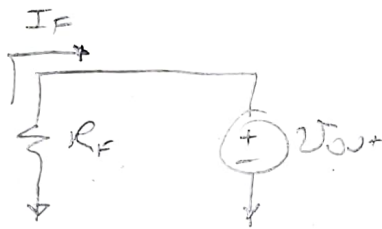

$$K = \frac{I_F}{V_{OUT}} = \frac{-V_{OUT}/R_F}{V_{OUT}}$$

$$K = -\frac{1}{R_F}$$

$$R_F = -\frac{1}{K} = -\frac{1}{(-950 \text{ mA/V})} = 1.05k\Omega$$

$$\boxed{R_F = 1.05k\Omega}$$

c. $R_{IN,CL}$, $R_{OUT,CL}$

$$R_{IN,CL} = \frac{R_{IN,OL}}{1 + KR_{OL}} = \frac{r_{e1}}{1 + KR_{OL}} = \frac{\frac{25.9mV}{1mA(\frac{101}{100})}}{1 + (-950 \text{ mA/V})(-20k\Omega)}$$

$$\boxed{R_{IN,CL} = 1.28\Omega}$$

$$R_{OUT,CL} = \frac{R_{OUT,OL}}{1 + KR_{OL}} = \frac{R_M}{1 + KR_{OL}} = \frac{500\Omega}{1 + (-950 \text{ mA/V})(-20k\Omega)}$$

$$\boxed{R_{OUT,CL} = 25\Omega}$$