

$$\text{Power} = 0.5 \text{W}$$

$$a. \quad A_V = \frac{R_L}{r_{e_1} + R_L} \approx \frac{R_L}{\frac{1}{g_m} + R_L} = 0.8$$

$$g_{m_1} = \frac{I_c}{V_T} = \frac{4}{8} = 0.5 \text{mA/V}$$

$$g_{m_1} = \frac{I_c}{V_T} \Rightarrow I_c = g_{m_1} V_T = (0.5 \text{mA})(25.9 \text{mV}) = 12.95 \text{mA}$$

$$I_c = 12.95 \text{mA}$$

$$b. \quad P_{avg} = \frac{V_p^2}{2R_L} \Rightarrow V_p = \sqrt{2R_L P_{avg}} = \sqrt{2(8\Omega)(0.5\text{W})}$$

$$V_p = 2.83 \text{V}$$

$$I_p = \frac{V_p}{R_L} = \frac{2.83 \text{V}}{8\Omega} = 354 \text{mA}$$

During the positive peak



$$I_{c1} = I_c + I_p = 12.95 \text{mA} + 354 \text{mA} = 367 \text{mA}$$

$$g_{m1} = \frac{I_{c1}}{V_T} = 14.2 \text{ A/V}$$

$$A_V = \frac{8\Omega}{14.2 \text{ A/V} + 8\Omega} = 0.991$$

$$A_V = 0.991$$

11.

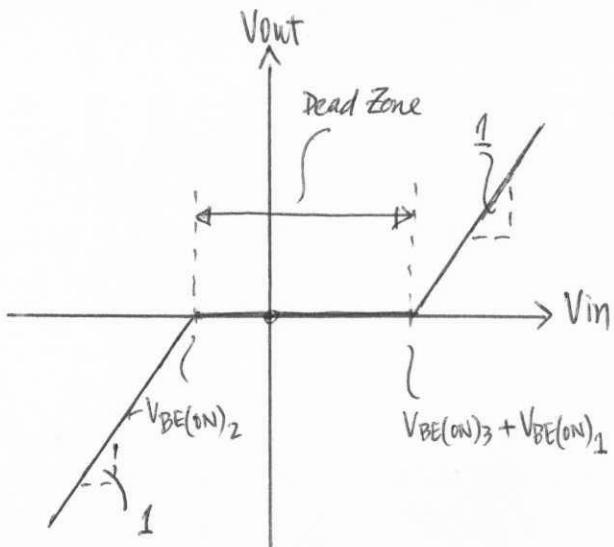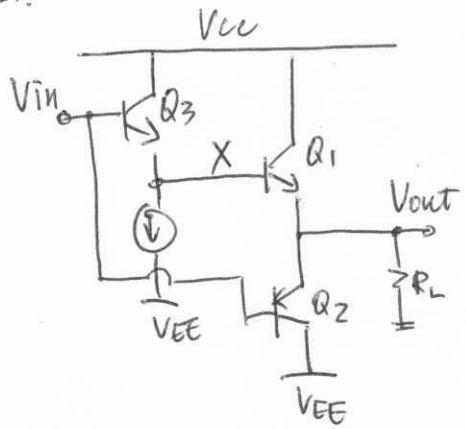

### Analysis

- $(0 < V_{in} < V_{BE(on)3} + V_{BE(on)1})$ :
  - $Q_1$  is OFF ( $V_{in} < V_{BE(on)1}$ ) }  $\Rightarrow V_{out} = 0$
  - $Q_2$  is OFF ( $V_{BE2}$  reverse-biased)
- $(-|V_{BE(on)2}| < V_{in} < 0)$ :
  - $Q_1, Q_2$  OFF }  $V_{out} = 0$
- $(V_{BE(on)3} + V_{BE(on)1} < V_{in} < V_{cc})$ 
  - $Q_1$  ON }  $V_{out} = V_{in} - V_{BE(on)3} - V_{BE(on)1}$
  - $Q_2$  OFF }
- $(-|V_{EE}| < V_{in} < -|V_{BE(on)2}|)$ 
  - $Q_2$  ON }  $V_{out} = V_{in} + |V_{BE(on)2}|$
  - $Q_1$  OFF }


17.

- $V_{out} = 0^\circ$

$$\Rightarrow I_{C_1} = I_{C_2} = I_{BIAS}$$

$$\Rightarrow I_{S_1} \exp\left(\frac{V_{in} + V_B - V_{out}}{V_T}\right) = I_{S_2} \exp\left(\frac{|V_{out} - V_{in}|}{V_T}\right)$$

$$\ln\left(\frac{I_{S_1}}{I_{S_2}}\right) + \frac{V_{in} + V_B - V_{out}}{V_T} = \frac{|V_{out} - V_{in}|}{V_T}$$

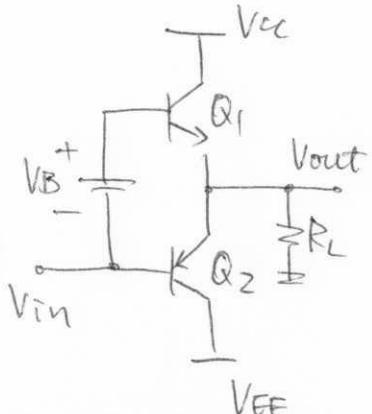

$$I_{S_1} = 5 \cdot 10^{-17} A$$

$$I_{S_2} = 8 \cdot 10^{-17} A$$

- For  $V_{out} = 0$ ,  $V_T = 0.026 V$ :

$$\Rightarrow \ln\left(\frac{5}{8}\right) + \frac{V_{in} + V_B}{0.026} = + \frac{V_{in}}{0.026}$$

$$I_{BIAS} = 5 \text{ mA}$$

$$(V_{out} = 0)$$

- Given  $I_{C_2} = 5 \text{ mA}$

$$\Rightarrow I_{S_2} \exp\left(-\frac{V_{in}}{0.026}\right) = 5 \text{ mA} \Rightarrow V_{in} = -0.83 V$$

$$I_{C_1} = I_{S_1} \exp\left(\frac{V_{in} + V_B - V_{out}}{V_T}\right) = (5 \cdot 10^{-17} A) \exp -\frac{0.83 + V_B}{V_T}$$

$$\Rightarrow V_B = 0.83 + 0.026 \ln\left(\frac{5 \text{ mA}}{5 \cdot 10^{-17} \text{ A}}\right).$$

$$\approx 1.67 V.$$

$$44. \quad V_p = 0.5V$$


$$R_L = 8\Omega$$

$$P_{RL} = \frac{V_p^2}{2R_L} = \frac{0.25}{16} = 0.0156 \text{ W}$$

$$P_I = -I \times V_{EE} = 0.14 \text{ W}$$

$$P_{Q_1} = I_1 \left( V_{CC} - \frac{V_p}{2} \right) = 0.1225 \text{ W}$$
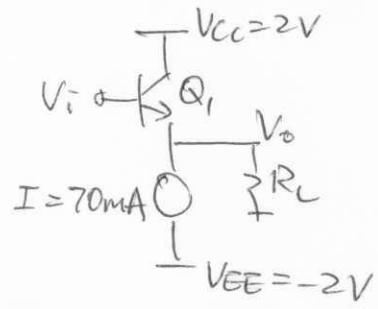
$$\therefore \eta = \frac{P_{RL}}{P_{RL} + P_I + P_{Q_1}} = \frac{0.0156}{0.2781} = 5.6\%$$



$$47. \quad V_{CC} = 3V \quad P_{RL} = 0.2W \quad R_L = 8\Omega.$$

$$P_{RL} = \frac{1}{2} \frac{V_P^2}{R_L} \Rightarrow V_P = \sqrt{2P_{RL} \times R_L} = 1.8V$$

$$\therefore \eta = \frac{P_{RL}}{P_{RL} + \frac{2V_P}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)} = \frac{0.2}{0.2 + \frac{36}{8} \left( \frac{3}{\pi} - \frac{1.8}{4} \right)}$$

**= 46.8%**