

ECEN326: Electronic Circuits


Spring 2022

Lab 10: Design of a BJT Shunt-Series Feedback Amp




Sam Palermo
Analog & Mixed-Signal Center
Texas A&M University

BJT Shunt-Series Feedback Amplifier

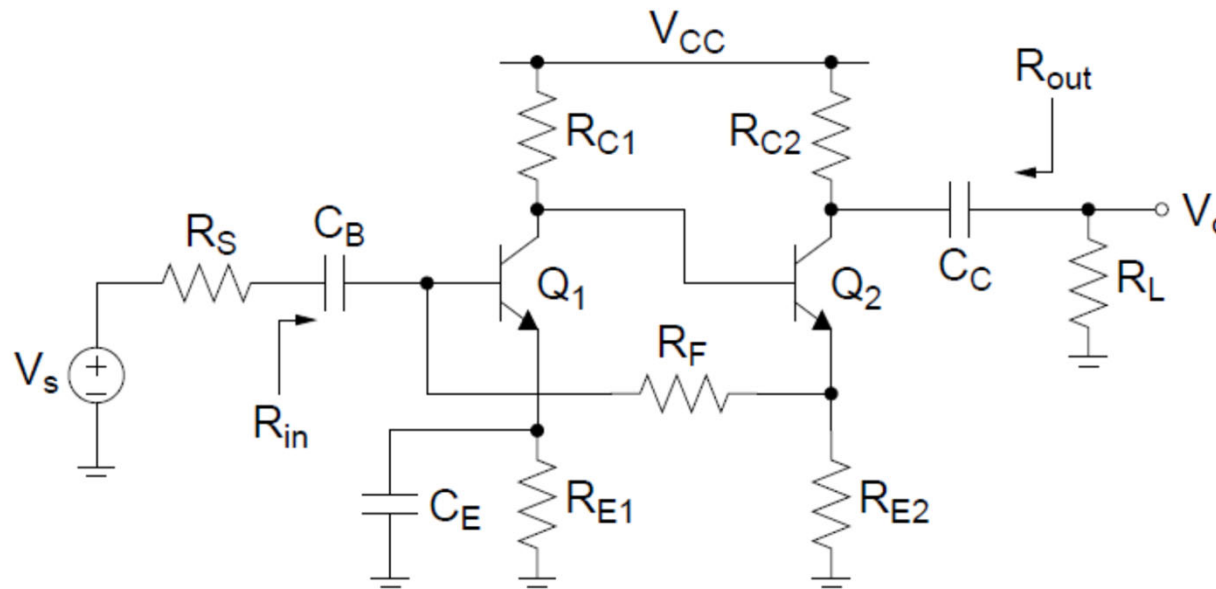

- From a feedback perspective, this circuit can be viewed as a current amplifier with the source current amplified to form the signal current through Q2
- Thus, we have **current-current feedback** with a parallel or “shunt” feedback resistor R_F and a “series” sensor resistor R_{E2}
- In the lab, it is easiest to measure this as a voltage amplifier with a standard voltage source input and taking the output as the Q_2 collector

Feedback Equivalent Circuit – Open Loop

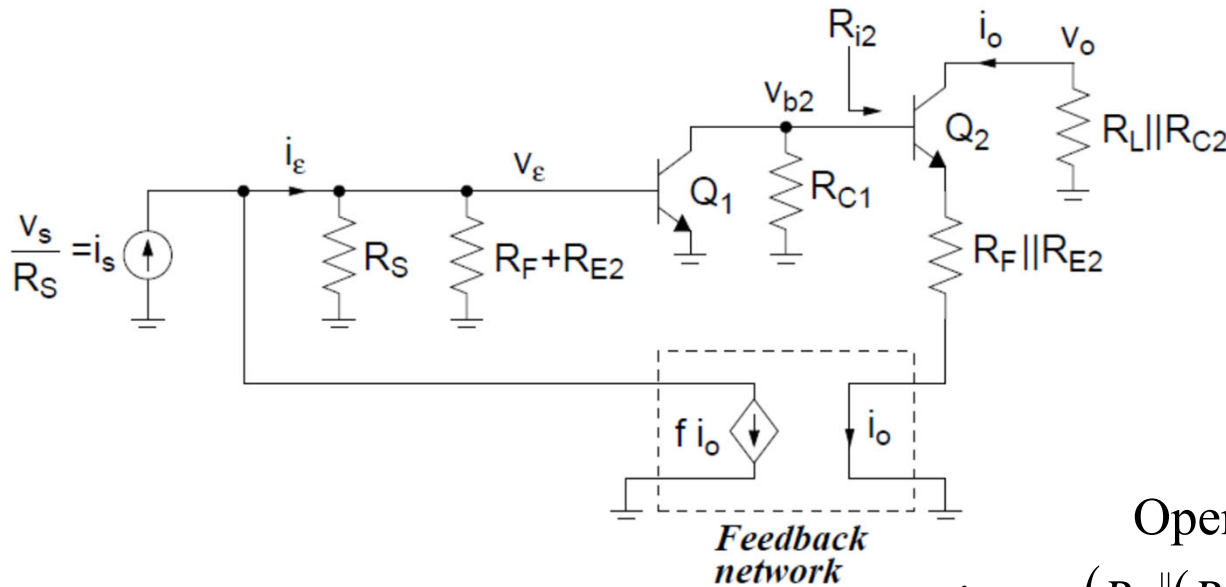

Assuming $\alpha = 1$

Open - Loop Current Gain :

$$a = \frac{i_o}{i_e} = - \frac{(R_S \parallel (R_F + R_{E2}) \parallel r_{\pi 1})(R_{C1} \parallel R_{i2})}{r_{e1}(r_{e2} + (R_F \parallel R_{E2}))} \approx - \frac{R_S g_{m1} R_{C1}}{R_{E2}}$$


$$\text{Feedback Factor: } f = - \frac{R_{E2}}{R_{E2} + R_F} \approx - \frac{R_{E2}}{R_F}$$

$$z_i = R_S \parallel (R_F + R_{E2}) \parallel r_{\pi 1} \approx R_S$$

$$z_o = R_T + r_{o2} + g_{m2} \frac{r_{\pi 2}}{r_{\pi 2} + (r_{o1} \parallel R_{C1})} r_{o2} R_T \approx g_{m2} r_{o2} R_{E2}$$

$$R_T = R_F \parallel R_{E2} \parallel (r_{\pi 2} + (r_{o1} \parallel R_{C1})) \approx R_{E2}$$

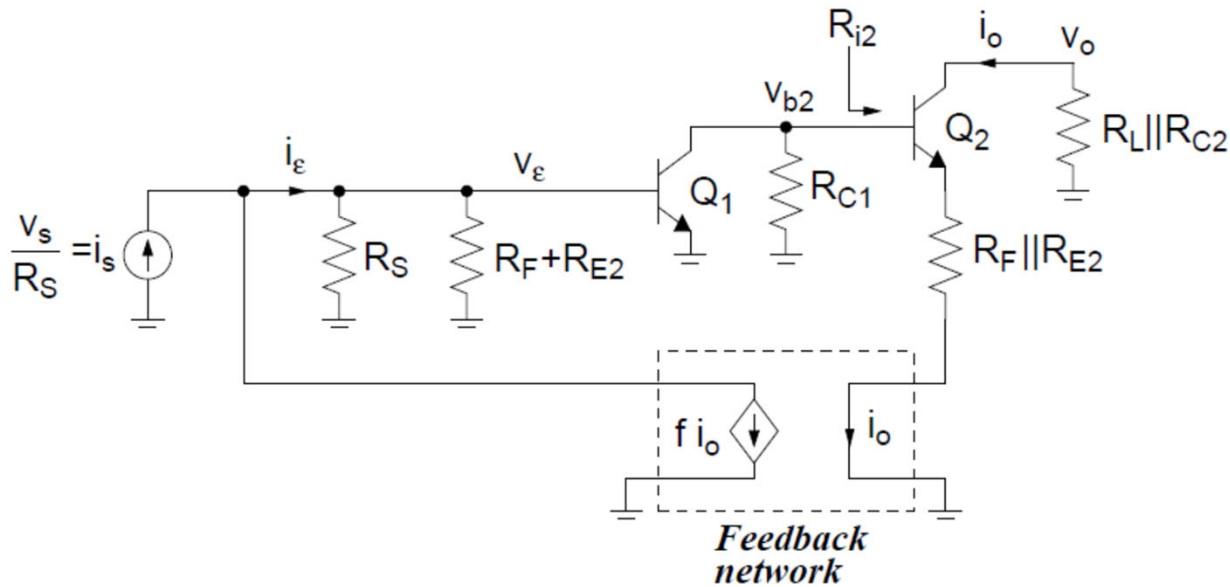
Feedback Equivalent Circuit – Closed Loop




$$A_i = \frac{i_o}{i_s} = \frac{a}{1 + af} \approx -\frac{R_F}{R_{E2}}$$

$$Z_i = \frac{z_i}{1 + af} \approx \frac{R_F}{g_{m1} R_{C1}}$$
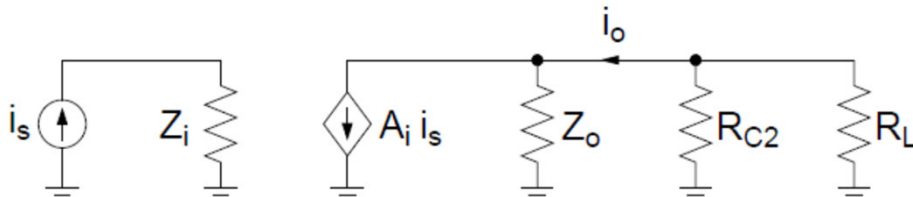
$$Z_o = z_o(1 + af) \approx g_{m2} r_{o2} R_{E2} \left(1 + \frac{R_S g_{m1} R_{C1}}{R_F} \right)$$



Converting to a Voltage-Mode Amplifier

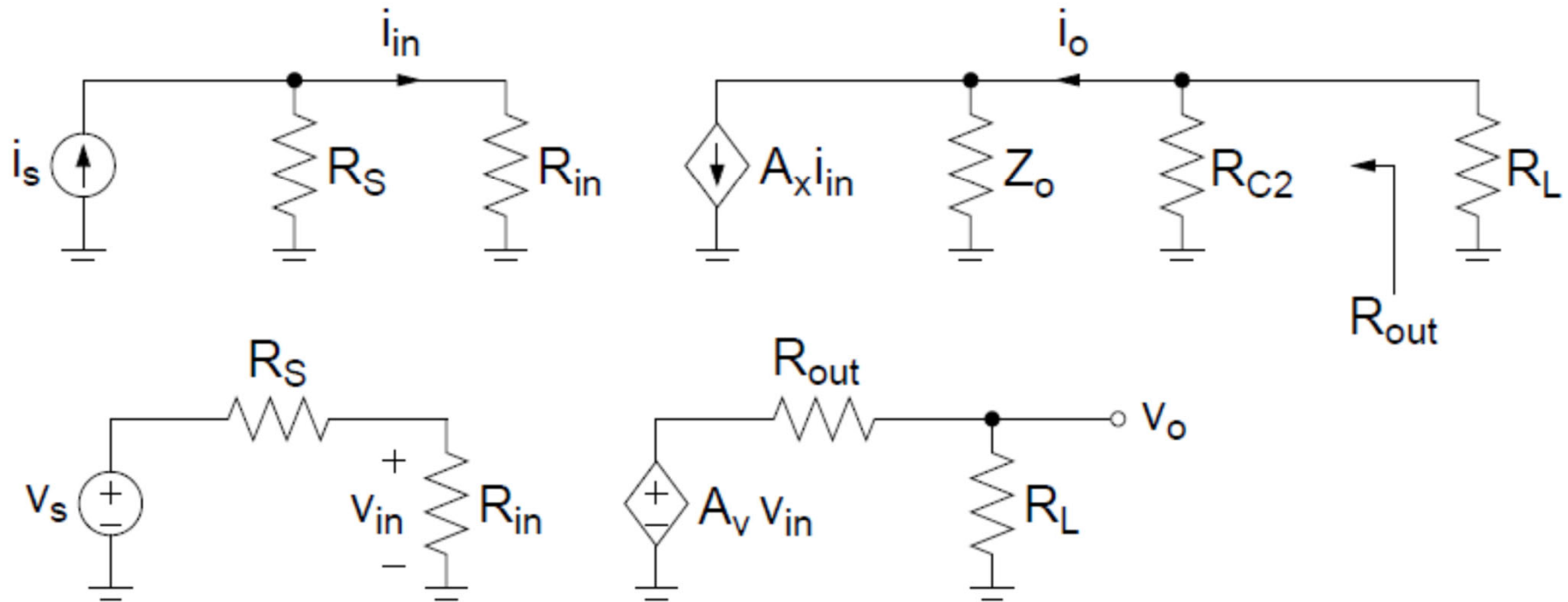


See details in lab manual

$$A_v \approx \frac{R_F R_{C2}}{R_{E2} R_S}$$

$$R_{in} \approx \frac{R_F}{g_{m1} R_{C1}}$$

$$R_{out} \approx R_{C2}$$

Design Procedure

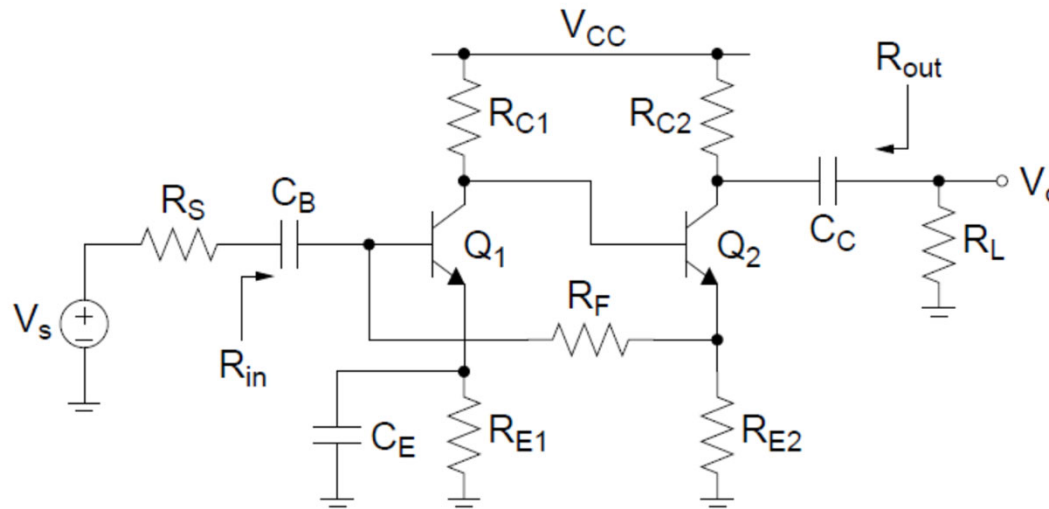

1. Using I_{supply} spec, apply most of the current to the output stage (7-8mA) for good distortion performance
2. The first stage should work well with 0.5-1mA
3. From DC conditions, set R_{E1} , R_{E2} , and R_{C1}
4. Using load line analysis (Eq 7), calculate R_{C2}
5. Set R_F to meet the voltage gain spec
6. Verify that you meet the af spec (Eq 19 & 20)