

ECEN326: Electronic Circuits

Spring 2022

Lecture 2: Transistor Models & Single-Stage Amplifiers




Sam Palermo
Analog & Mixed-Signal Center
Texas A&M University

Announcements


- Lab
 - Lab 1 report is due this week
 - Lab 2 report due next week
 - Use the Lab 2 updated specs
- HW
 - HW1 due today
 - HW2 due Feb 8
- Reading
 - Razavi Chapters 5 & 7

BJT Circuit Symbols

NPN

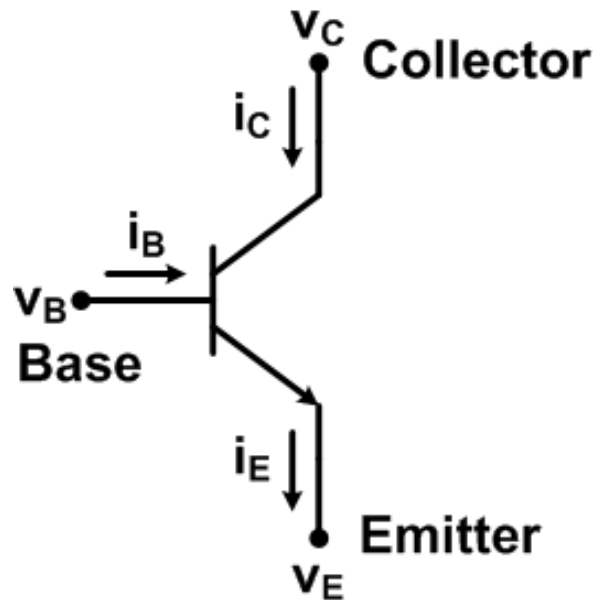


PNP

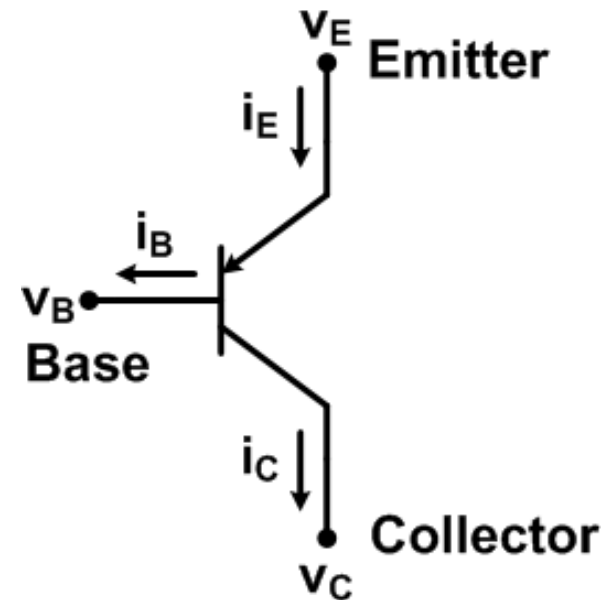


- BJTs are 3 terminal devices
 - Collector, Base, & Emitter
- 2 complementary BJT devices: NPN & PNP

MOSFET Circuit Symbols

NMOS

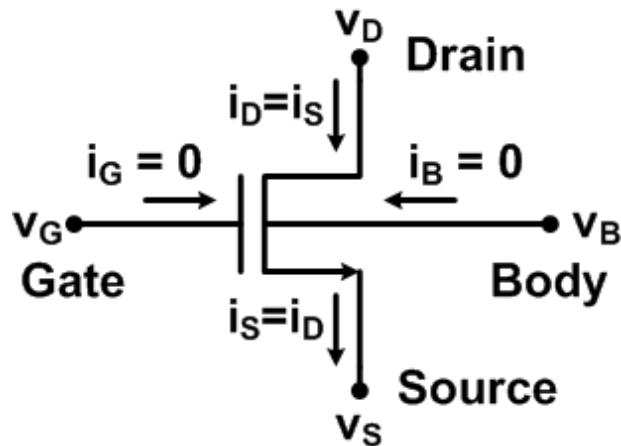


PMOS

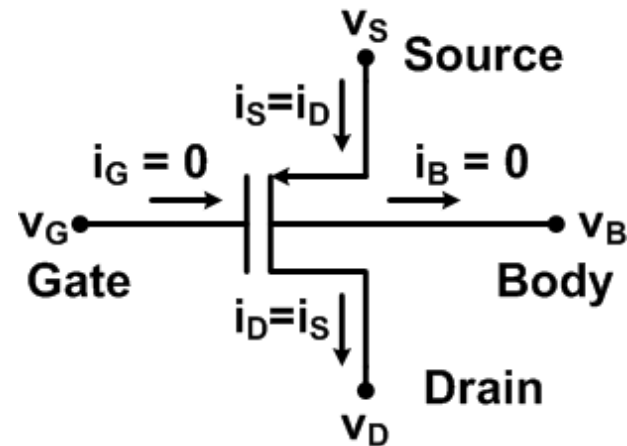

- MOSFETs are 4-terminal devices
 - Drain, Gate, Source, & Body
- Body terminal generally has small impact in normal operation modes, thus device is generally considered a 3-terminal device
 - Drain, Gate, and Source are respectively similar to the Collector, Base, and Emitter of the BJT
- 2 complementary MOSFETs: NMOS, PMOS

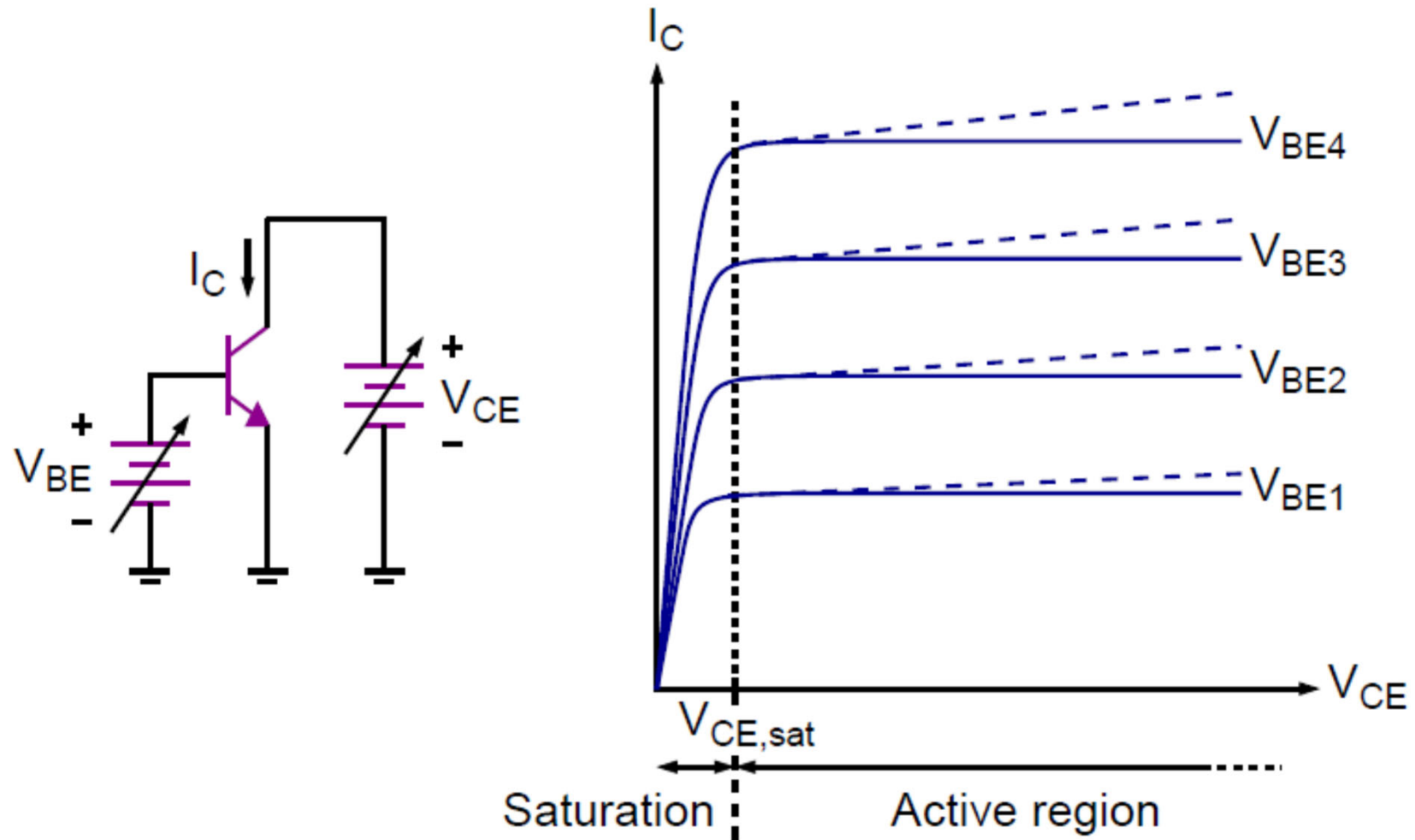
NPN "Large-Signal" (DC) Output Characteristic



- For analog applications, we generally desire the BJT to operate in the "Active" region

$$V_{CE} \geq V_{CE,sat} = 0.3V$$

NPN "Large-Signal" (DC) Model

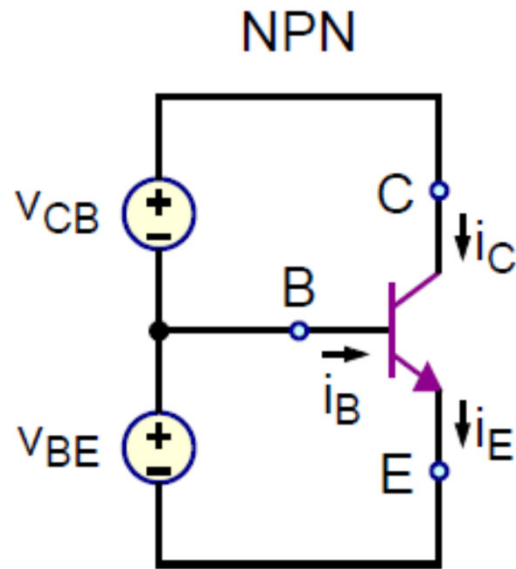

- Exact equation

$$V_{CE} \geq V_{CE,sat}$$

$$i_B = \frac{I_S}{\beta} e^{V_{BE}/V_T}$$

$$i_C = I_S e^{V_{BE}/V_T}$$


- However, V_{BE} doesn't change much over large values of I_C . So, for hand calculations we assume a fixed V_{BE} and use the following

$$V_{BE} = 0.7 \text{ V}$$

$$I_C = \beta I_B$$

$$I_E = I_C + I_B$$

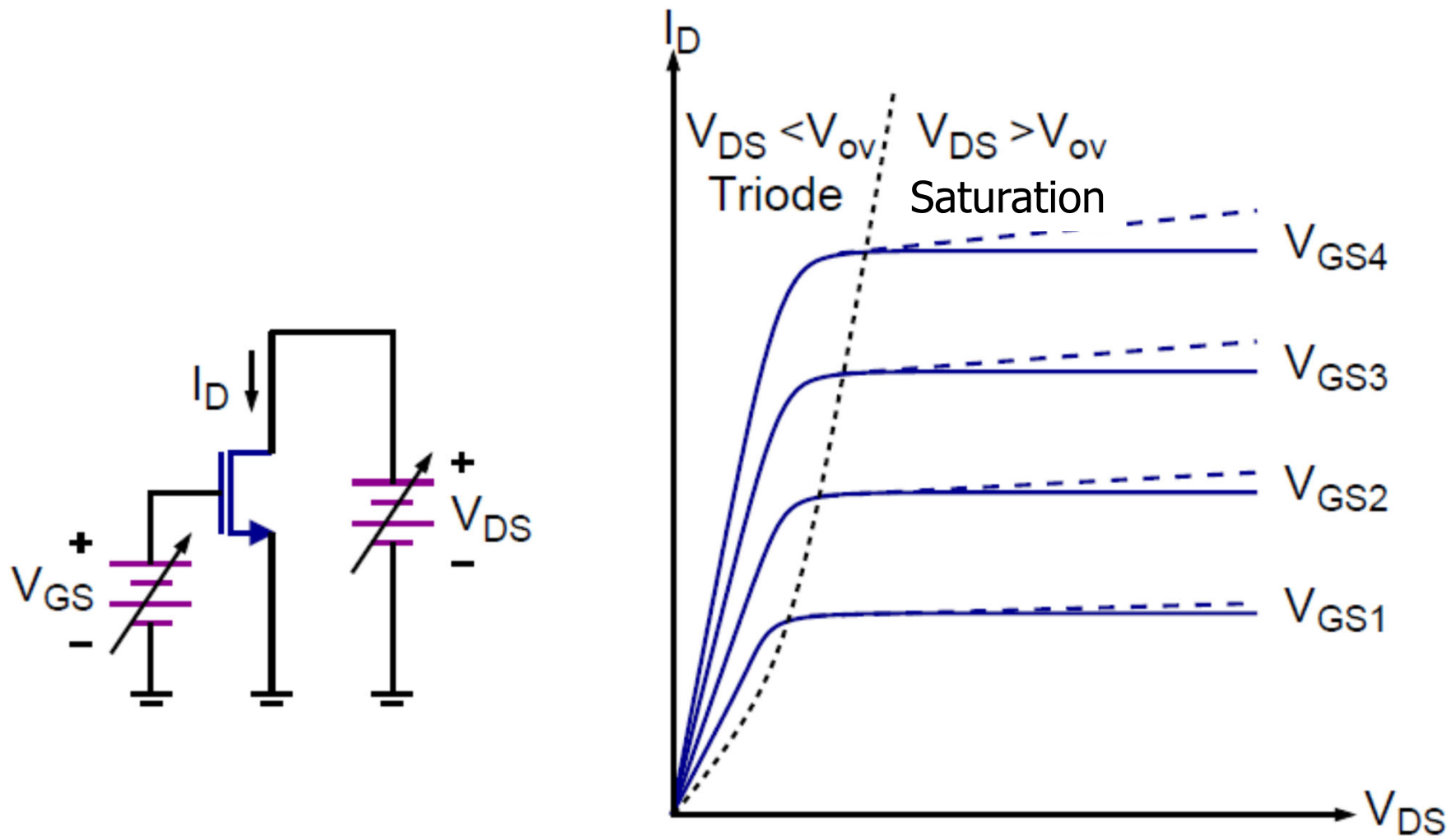
NMOS "Large-Signal" (DC) Output Characteristic



- For analog applications, we generally desire the MOSFET to operate in the "Saturation" region

$$V_{DS} \geq V_{OV} = V_{GS} - V_{tn}$$

NMOS "Large-Signal" (DC) Model

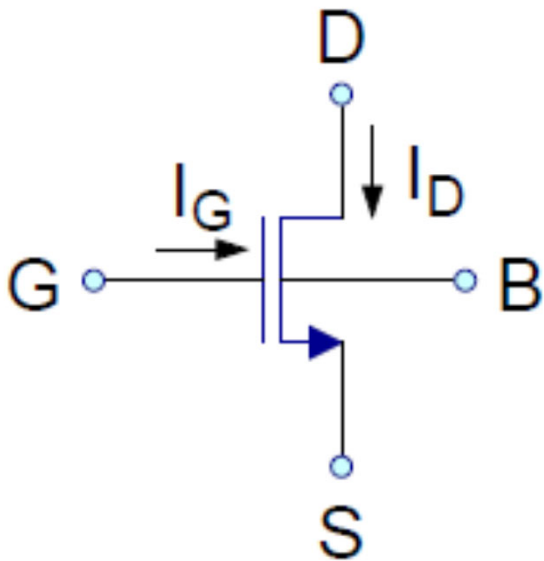

$$V_{DS} \geq V_{ov} \Rightarrow \text{Saturation}$$


$$V_{ov} = V_{GS} - V_{tn}$$

$$I_G = 0$$

$$I_D = \frac{k'_n}{2} \frac{W}{L} V_{ov}^2$$

$$\text{where } k'_n = \mu_n C_{ox}$$

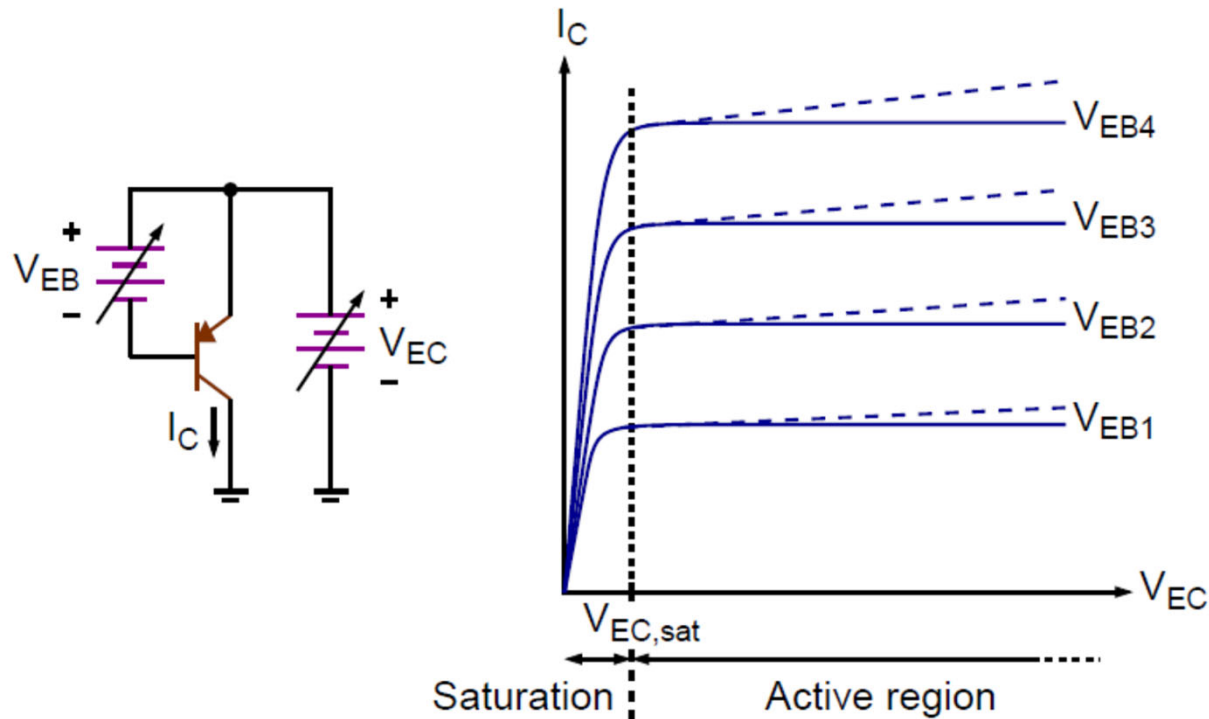
PNP "Large-Signal" (DC) Output Characteristic



- Similar operation to NPN transistor, except
 - I_C flows out of the device
 - Flip the terminal voltages in calculations
- For analog applications, we generally desire the BJT to operate in the "Active" region

$$V_{EC} \geq V_{EC,sat} = 0.3V$$

PNP "Large-Signal" (DC) Model

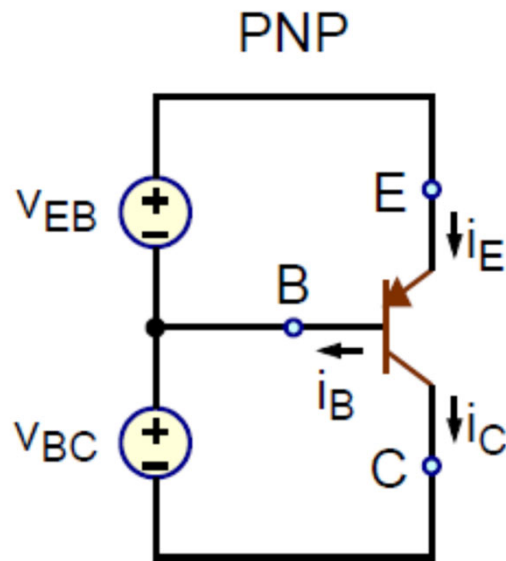

- Exact equation

$$V_{EC} \geq V_{EC,sat}$$

$$i_B = \frac{I_S}{\beta} e^{V_{EB}/V_T}$$

$$i_C = I_S e^{V_{EB}/V_T}$$


- However, V_{EB} doesn't change much over large values of I_C . So, for hand calculations we assume a fixed V_{EB} and use the following

$$V_{EB} = 0.7 \text{ V}$$

$$I_C = \beta I_B$$

$$I_E = I_C + I_B$$

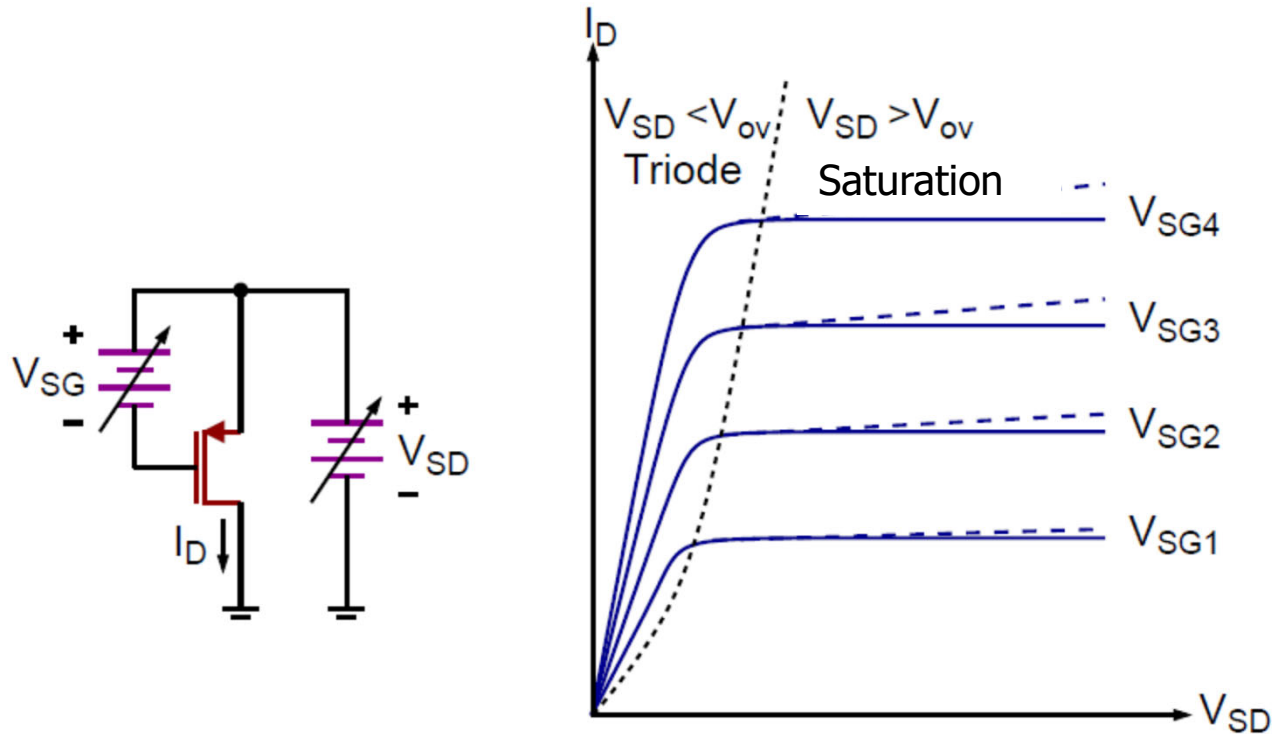
PMOS "Large-Signal" (DC) Output Characteristic



- Similar operation to NMOS transistor, except
 - I_D flows out of the device
 - Flip the terminal voltages in calculations
- For analog applications, we generally desire the BJT to operate in the "Saturation" region

$$V_{SD} \geq V_{OV} = V_{SG} - |V_{tp}|$$

PMOS "Large-Signal" (DC) Model

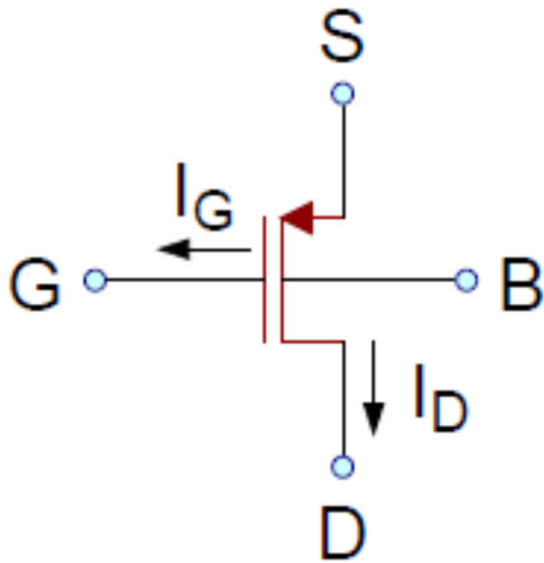

$$V_{SD} \geq V_{ov} \Rightarrow \text{Saturation}$$


$$V_{ov} = V_{SG} - |V_{tp}|$$

$$I_G = 0$$


$$I_D = \frac{k'_p}{2} \frac{W}{L} V_{ov}^2$$

$$\text{where } k'_p = \mu_p C_{ox}$$

Large-Signal "DC" Response

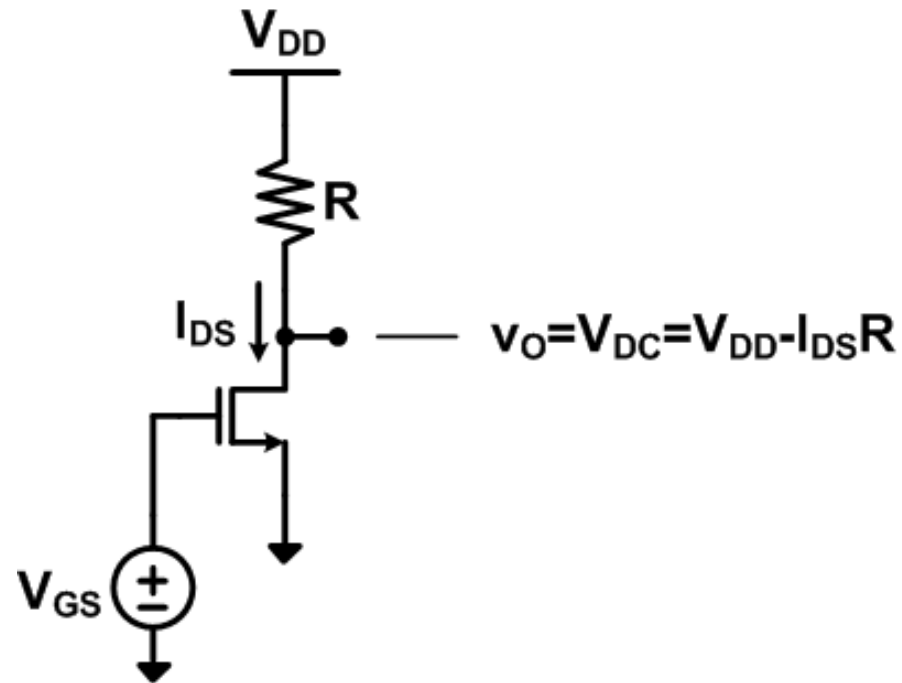


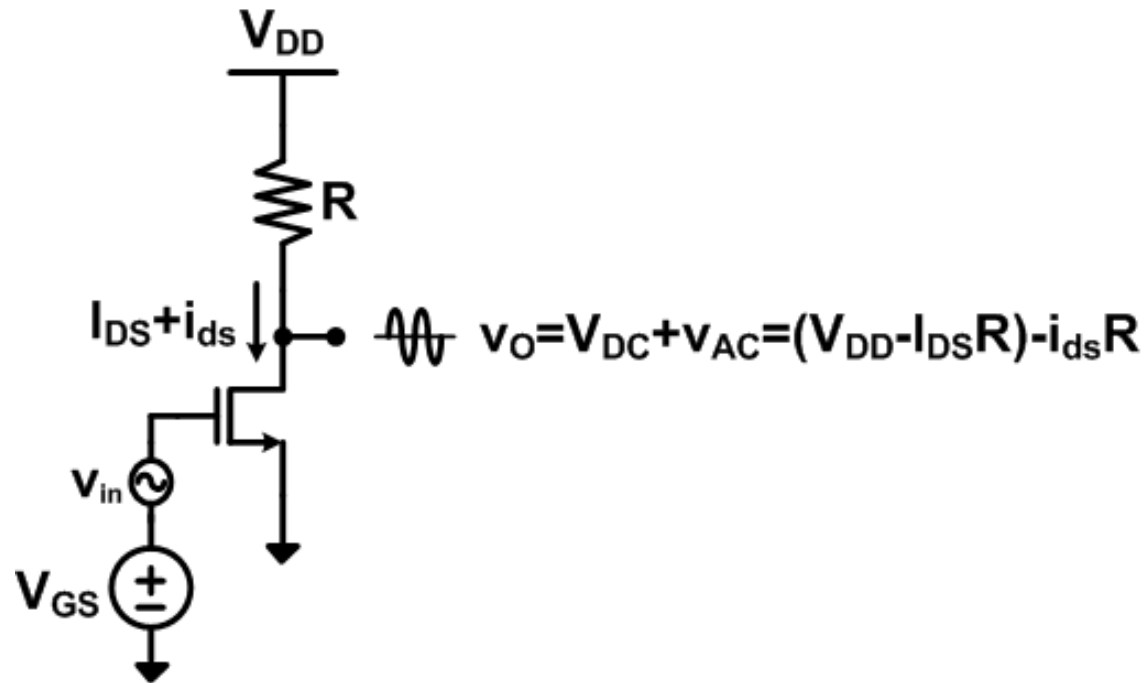
Large-Signal "DC" + Small-Signal "AC" Response




- For small-signal analysis, we "linearize" the response about the DC operating point
- If the signal is small enough, linearity holds and the complete response is the summation of the large-signal "DC" response and the small-signal "AC" response

DC Analysis vs. Small-Signal Analysis

DC Analysis

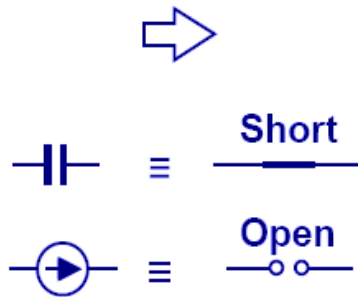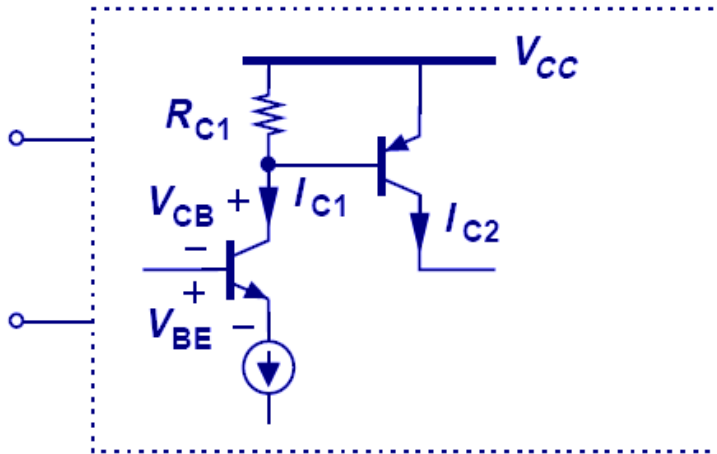


Small-Signal Analysis

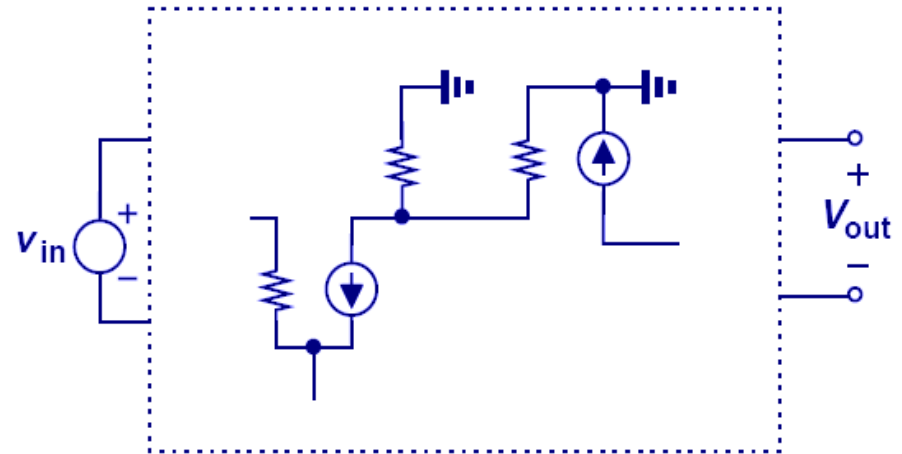


- First, DC analysis is performed to determine operating point and obtain small-signal parameters.
- Second, sources are set to zero and small-signal model is used.

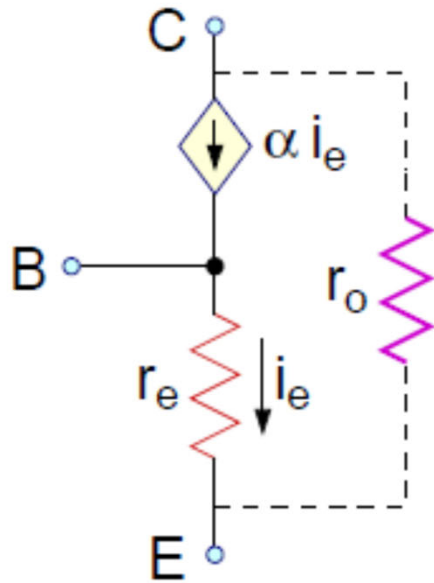NPN & NMOS Small-Signal T-Models ($r_o = \infty$)




$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m} \approx \frac{1}{g_m}$$

$$g_m = \frac{I_C}{V_T}$$

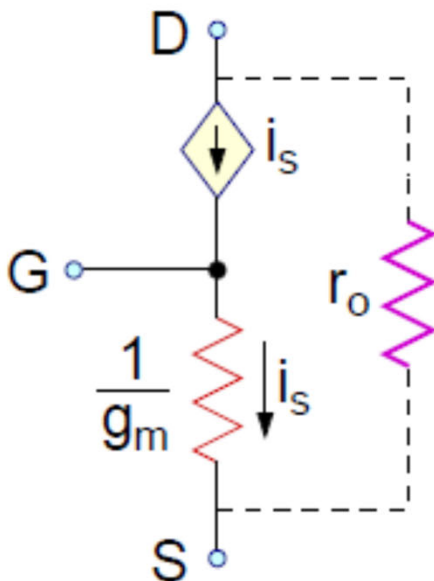

$$g_m = k'_n \frac{W}{L} V_{ov} = \sqrt{2k'_n \frac{W}{L} I_D}$$

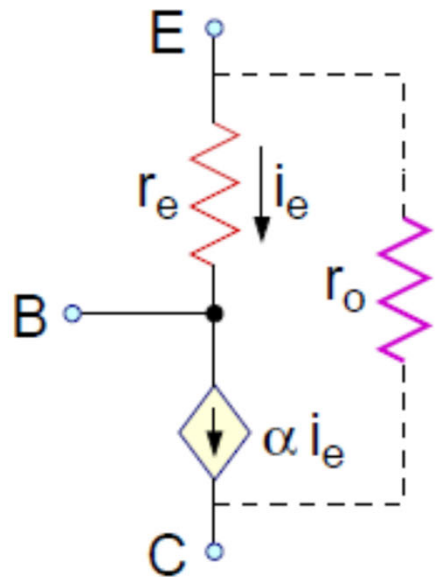Formal PNP & PMOS Small-Signal T-Models ($r_o = \infty$)




$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m} \approx \frac{1}{g_m}$$

$$g_m = \frac{I_C}{V_T}$$


- While these are the formal models, for both the PNP and PMOS device **you can use the exact same model as the NPN and NMOS device**

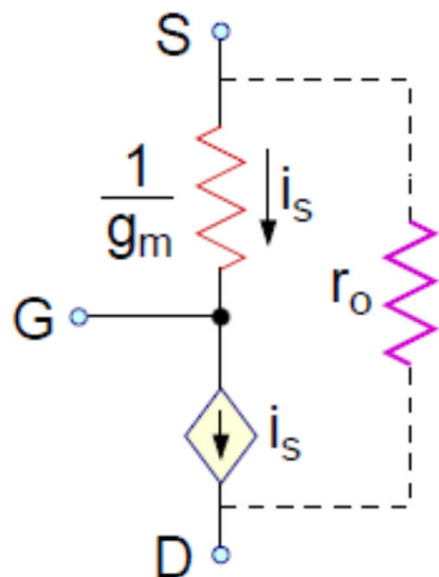- This is easier to remember
- Obtained by flipping the current sources in the formal model




$$g_m = k'_p \frac{W}{L} V_{ov} = \sqrt{2k'_p \frac{W}{L} I_D}$$

Input/Output Impedances

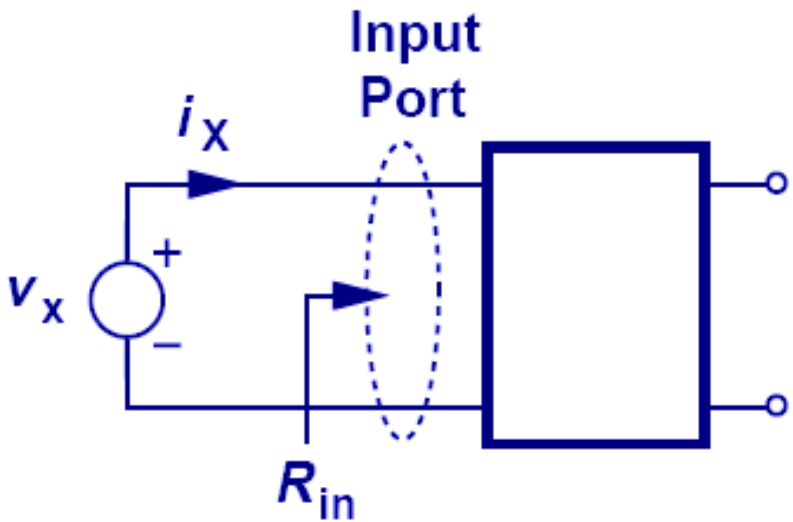

(a)

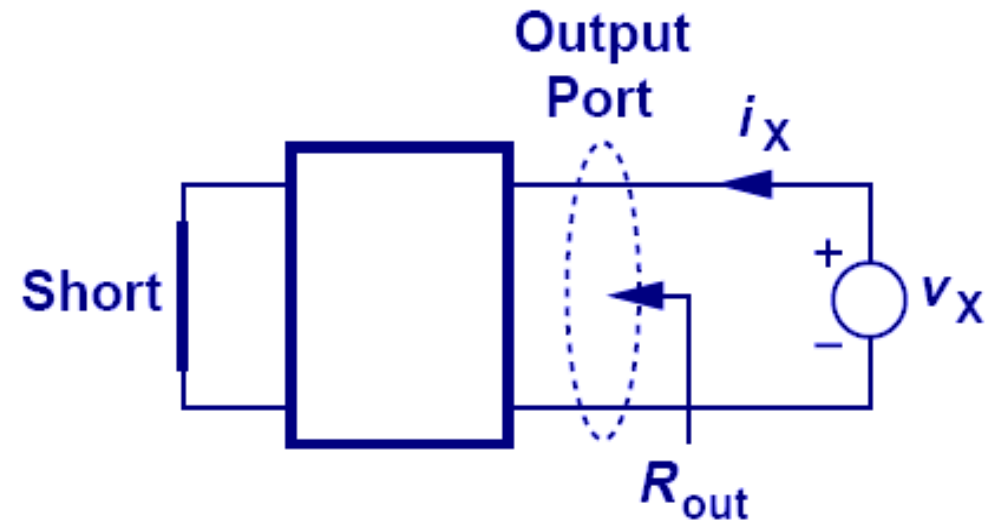


(b)

$$R_x = \frac{V_x}{i_x}$$


- The figure above shows the techniques of measuring input and output impedances.
- Small signal analysis is used

BJT Node AC Resistances ($r_o = \infty$)

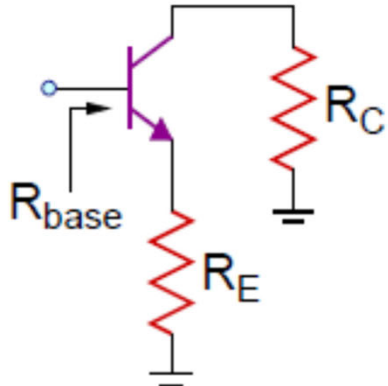


$$R_{\text{base}} = (\beta + 1)(r_e + R_E)$$

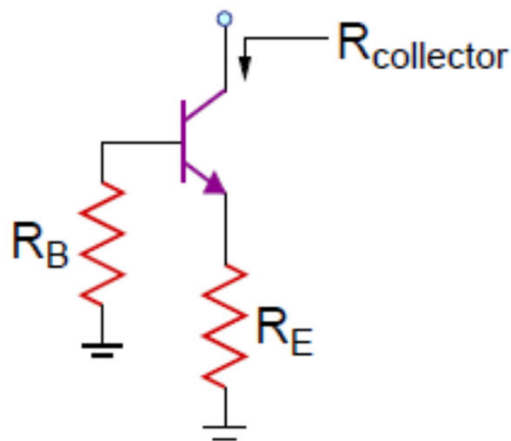- Using T-model, base AC resistance is the resistors connected from base through the emitter to ground **multiplied by $(\beta+1)$**



$$R_{\text{collector}} = \infty$$

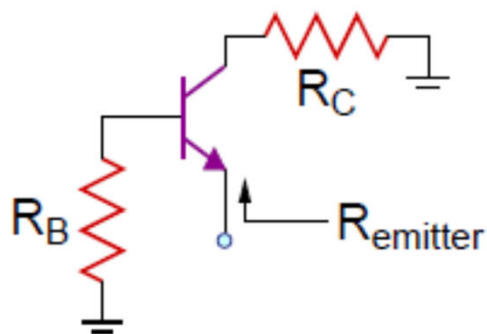- If r_o is ∞ , then collector AC resistance is ∞




$$R_{\text{emitter}} = r_e + \frac{R_B}{\beta + 1}$$

- Using T-model, emitter AC resistance is r_e plus the base resistor **divided by $(\beta+1)$**


BJT Amplifiers AC Gain ($r_o = \infty$)

CE Amp

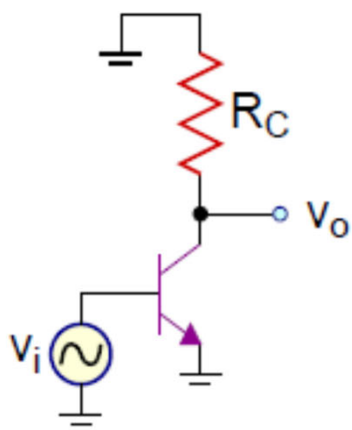


$$\frac{v_o}{v_i} = \frac{-\alpha R_C}{r_e}$$

CC Amp

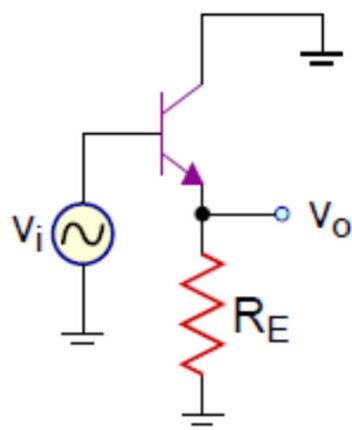


$$\frac{v_o}{v_i} = \frac{R_E}{r_e + R_E}$$

CB Amp

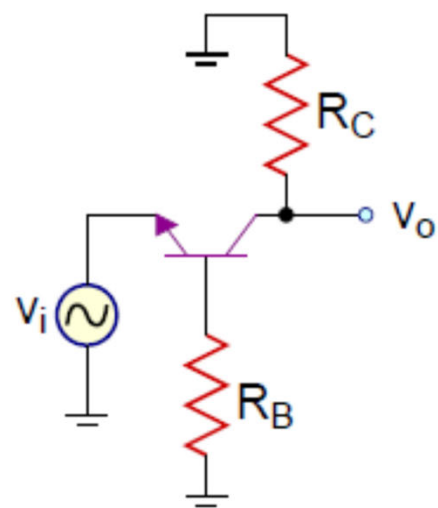


$$\frac{v_o}{v_i} = \frac{\alpha R_C}{R_{emitter}}$$

CE Amp w/ R_E

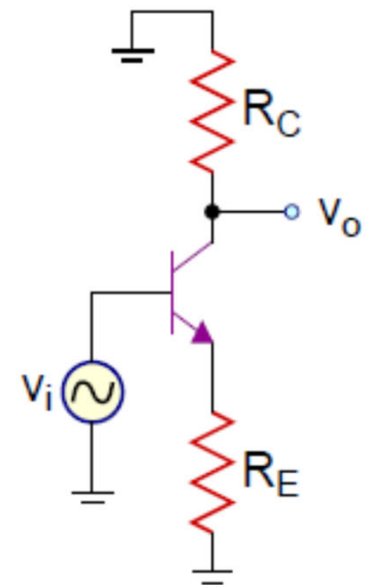


$$\frac{v_o}{v_i} = \frac{-\alpha R_C}{r_e + R_E}$$

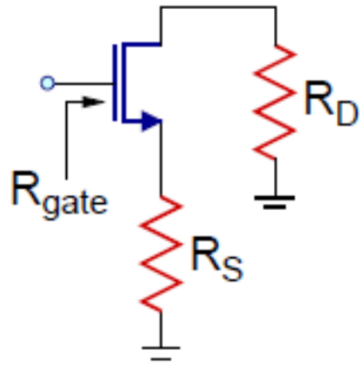MOSFET Node AC Resistances ($r_o = \infty$)




$$R_{\text{gate}} = \infty$$

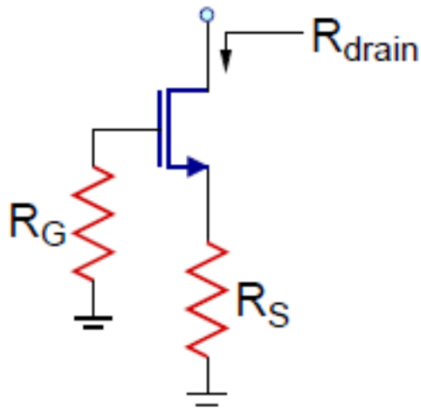- Gate input impedance is capacitive, which is assumed to be infinite resistance at low frequencies



$$R_{\text{drain}} = \infty$$

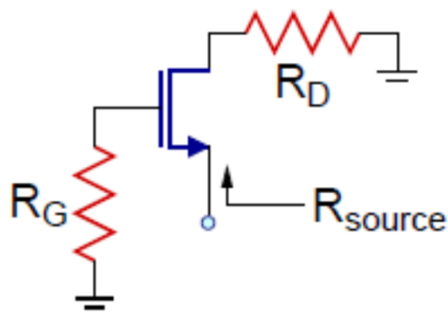- If r_o is ∞ , then drain AC resistance is ∞




$$R_{\text{source}} = \frac{1}{g_m}$$

- Using T-model, source AC resistance is the $1/g_m$ resistor


MOSFET Amplifiers AC Gain ($r_o = \infty$)

CS Amp

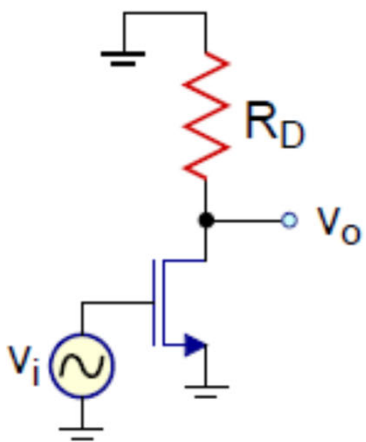


$$\frac{v_o}{v_i} = \frac{-R_D}{\frac{1}{g_m}}$$

CD Amp

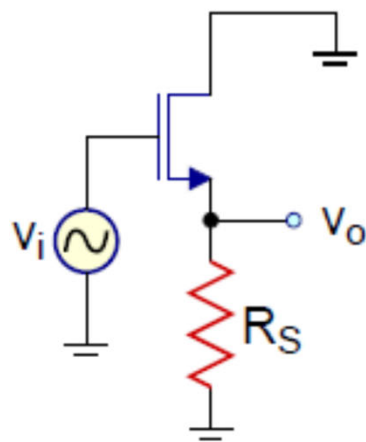


$$\frac{v_o}{v_i} = \frac{R_S}{\frac{1}{g_m} + R_S}$$

CG Amp

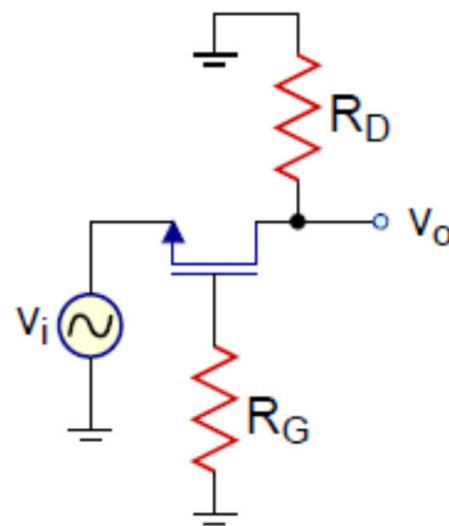


$$\frac{v_o}{v_i} = \frac{R_D}{R_{\text{source}}}$$

CS Amp w/ R_S

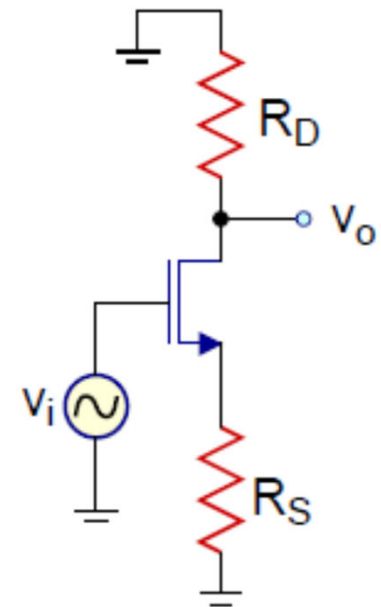

$$\frac{v_o}{v_i} = \frac{-R_D}{\frac{1}{g_m} + R_S}$$

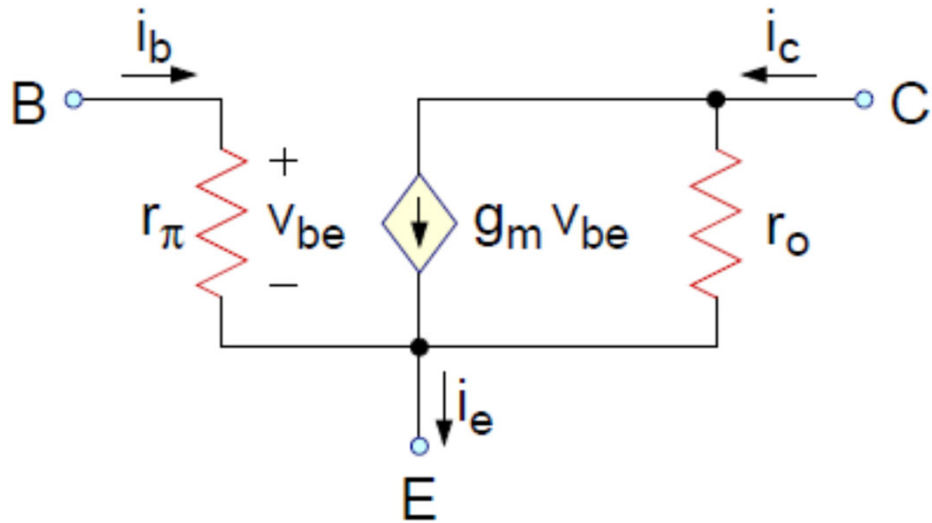NPN Small-Signal π Model & Introducing Finite r_o




Early Effect $\rightarrow r_o$

$$g_m = \frac{I_C}{V_T}$$


$$r_o = \frac{V_A}{I_C}$$

$$r_\pi = \frac{\beta}{g_m}$$

$$V_T = \frac{kT}{q}$$

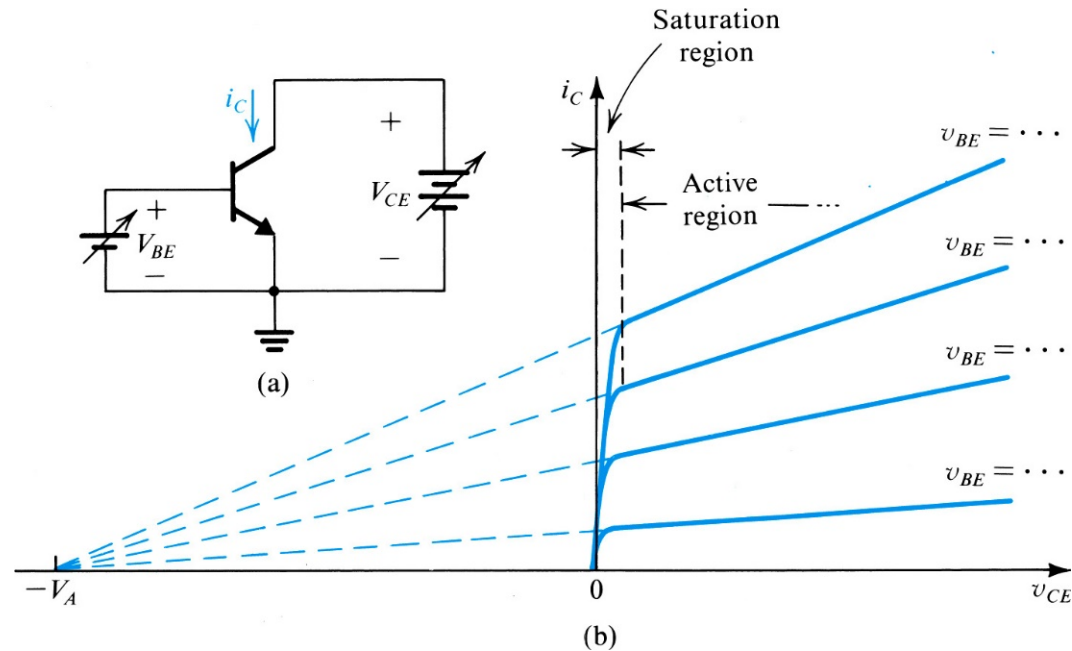

PNP Small-Signal π Model w/ Finite r_o

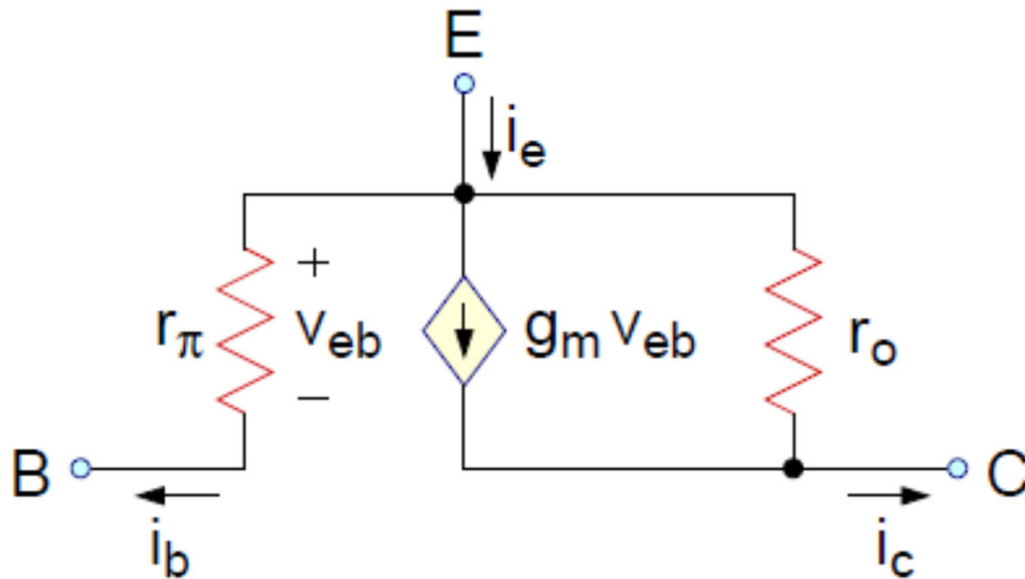

Early Effect $\rightarrow r_o$

$$g_m = \frac{I_C}{V_T}$$

$$r_o = \frac{V_A}{I_C}$$



$$r_\pi = \frac{\beta}{g_m}$$

$$V_T = \frac{kT}{q}$$

- While this is the formal model, **you can use the exact same model as the NPN device**
 - This is easier to remember
 - Obtained by flipping the small signal v_{eb} and the current source in the formal model

MOSFET – Impact of Body Voltage

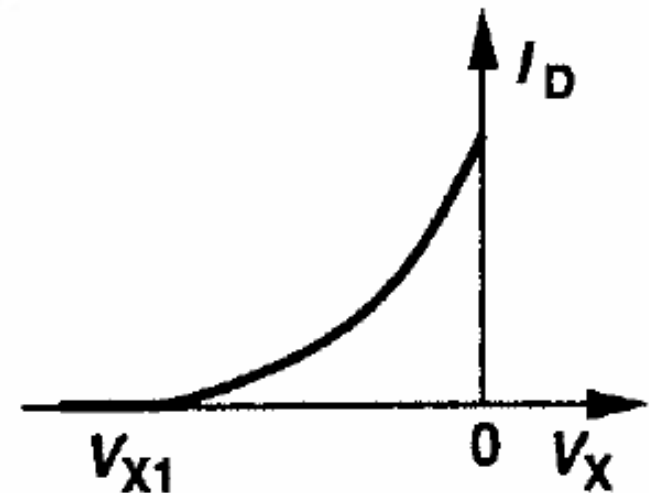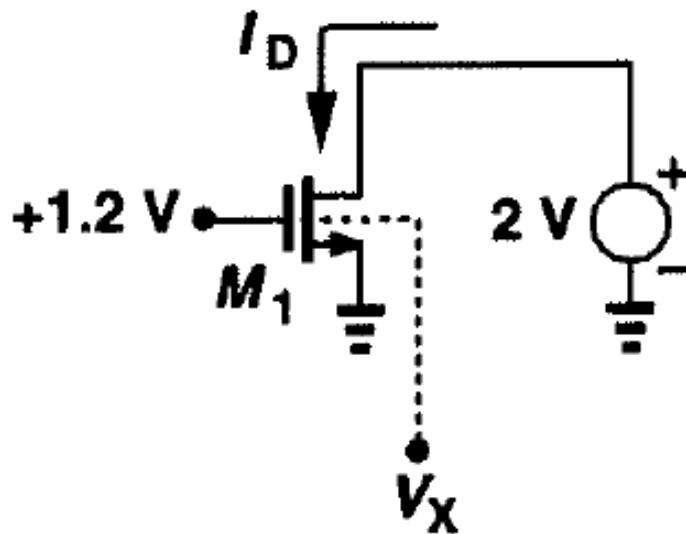- Before we go over the MOSFET π -model, let's consider the impact of the 4th terminal, the Body, on the drain current I_D
- The MOSFET V_{tn} is a function of the Body-Source voltage V_{BS}
 - If the threshold voltage changes, then so does I_D



$$I_D = \frac{\mu_n C_{ox} W}{2 L} (V_{GS} - V_{tn})^2 (1 + \lambda V_{DS})$$


[Razavi]

$$V_{tn} = V_{tn0} + \gamma \left[\sqrt{2\Phi_F + V_{SB}} - \sqrt{2\Phi_F} \right] \Rightarrow V_{tn0} |_{V_{SB}=0}$$

Body Transconductance, g_{mb}

- The small-signal drain current changes with V_{BS} modulation due to changes in V_{tn}


[Razavi]

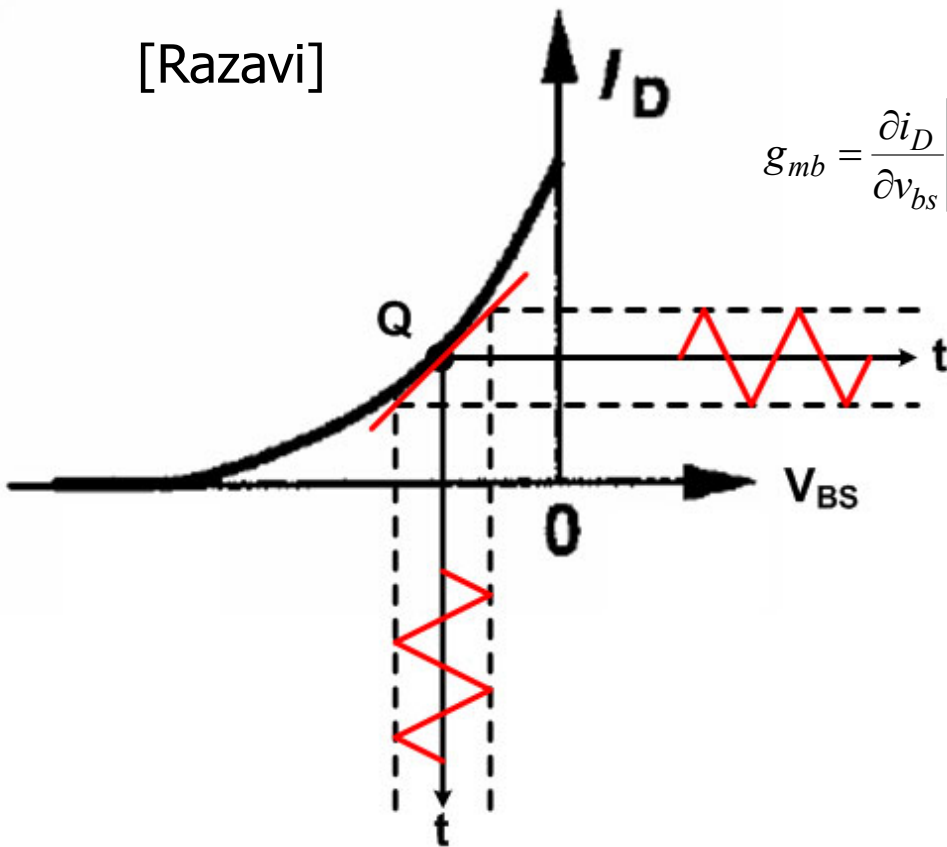

In Saturation (Neglecting λ Effects)

$$g_{mb} = \left. \frac{\partial i_D}{\partial v_{bs}} \right|_Q \approx \mu C_{OX} \frac{W}{L_{eff}} [V_{GS} - V_{tn}] \Big|_Q * \left(- \left. \frac{\partial V_{tn}}{\partial v_{bs}} \right|_Q \right) \cong \frac{\gamma g_m}{2\sqrt{2\phi_F + V_{SB}}}$$

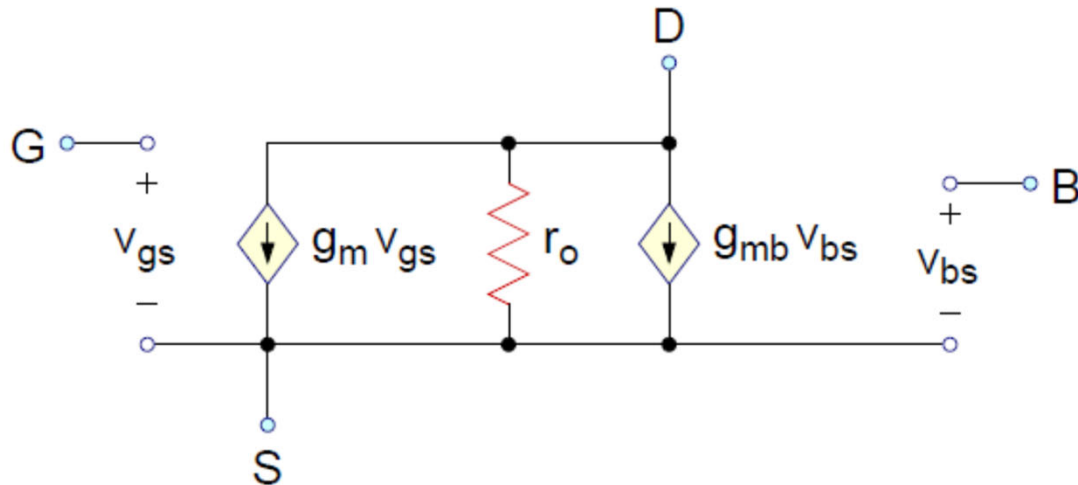NMOS Small-Signal π Model w/ Finite r_o & Body Transconductance g_{mb}



Channel Length Modulation $\rightarrow r_o$

Body Effect $V_{tn} = V_{tn0} + \gamma[\sqrt{2\Phi_F + V_{SB}} - \sqrt{2\Phi_F}] \Rightarrow V_{tn0}|_{V_{SB}=0} \rightarrow g_{mb}$

$$g_m = \sqrt{2k'_n \frac{W}{L} I_D}$$

$$r_o = \frac{1}{\lambda_n I_D}$$


$$g_{mb} = \chi g_m$$

$$k'_n = \mu_n C_{ox}$$

where $\chi = \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}}$

- Note, g_{mb} is generally a weak effect ($\sim 0.1g_m$). Thus, we often ignore it.
- In problems/assignments I'll make it clear when we need to consider it

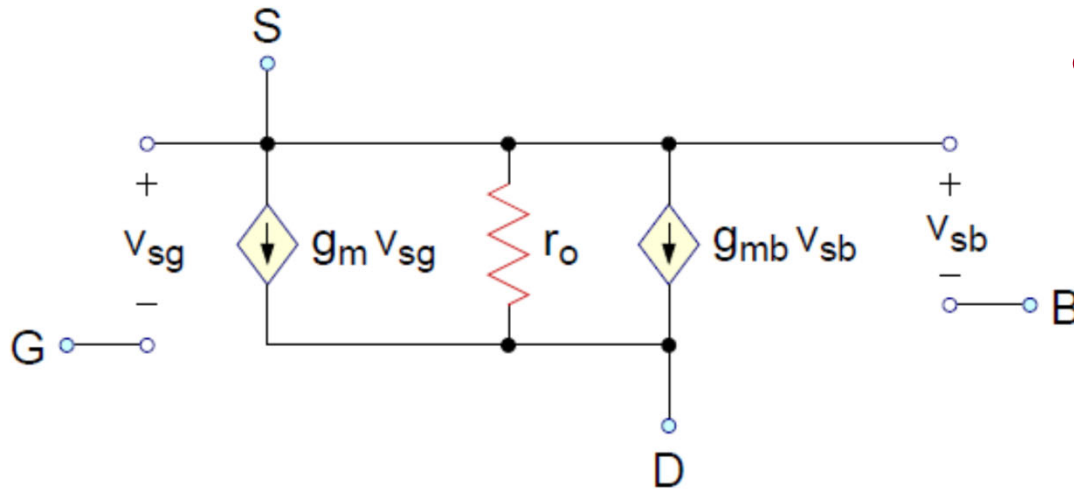PMOS Small-Signal π Model w/ Finite r_o & Body Transconductance g_{mb}



- While this is the formal model, **you can use the exact same model as the NMOS device**

- This is easier to remember
- Obtained by flipping the small signal v_{sg} and v_{sb} and the current sources in the formal model

Channel Length Modulation $\rightarrow r_o$
 Body Effect $V_{tp} = V_{tp0} + \gamma [\sqrt{2\Phi_F + V_{SB}} - \sqrt{2\Phi_F}] \Rightarrow V_{tp0}|_{V_{SB}=0} \rightarrow g_{mb}$

$$g_m = \sqrt{2k'_p \frac{W}{L} I_D}$$

$$r_o = \frac{1}{\lambda_p I_D}$$



$$g_{mb} = \chi g_m$$

$$k'_p = \mu_p C_{ox}$$

where $\chi = \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}}$

- Note, g_{mb} is generally a weak effect ($\sim 0.1g_m$). Thus, we often ignore it.
- In problems/assignments I'll make it clear when we need to consider it


Two-Port Modeling of Amplifiers

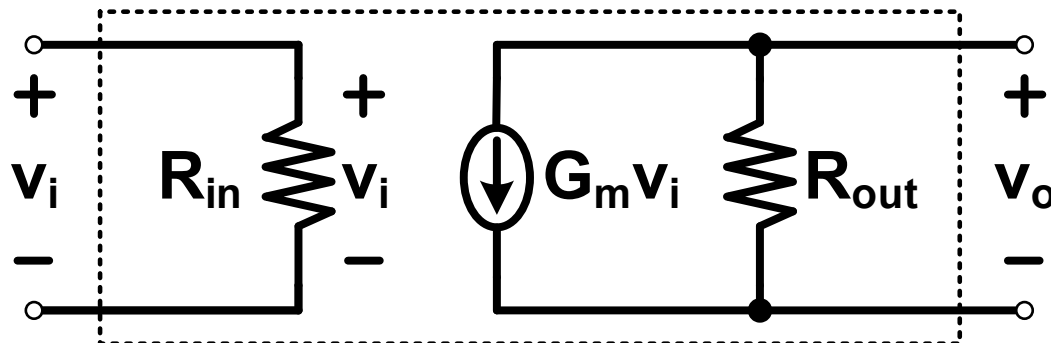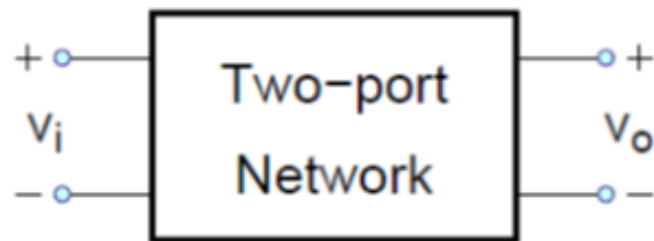

$$\frac{v_o}{v_i} = -G_m R_{out}$$


- It is often useful to model transistor amplifiers with a Norton-equivalent model consisting of a transconductance current source and parallel output resistance

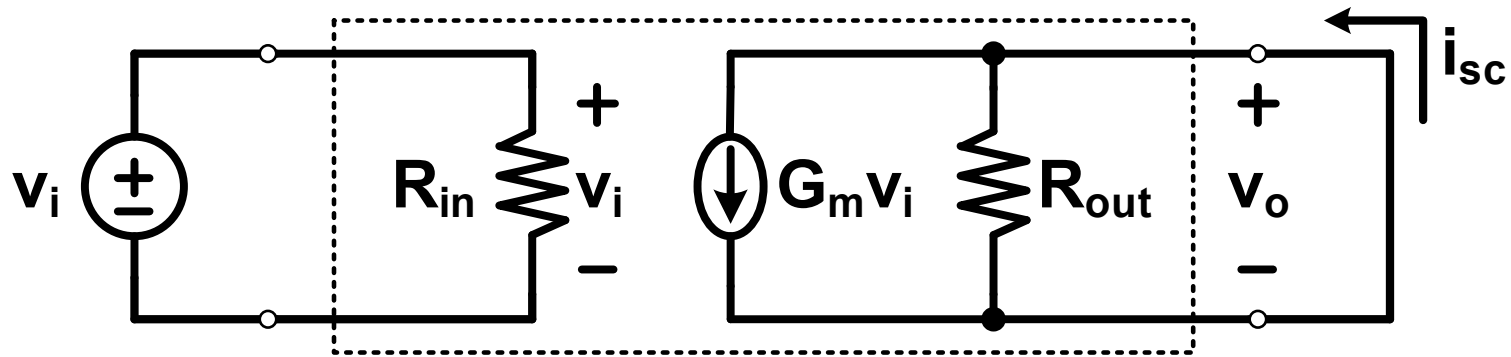Two-Port Modeling – Extracting G_m and R_n



$$G_m = \left. \frac{i_{sc}}{v_i} \right|_{v_o=0}$$

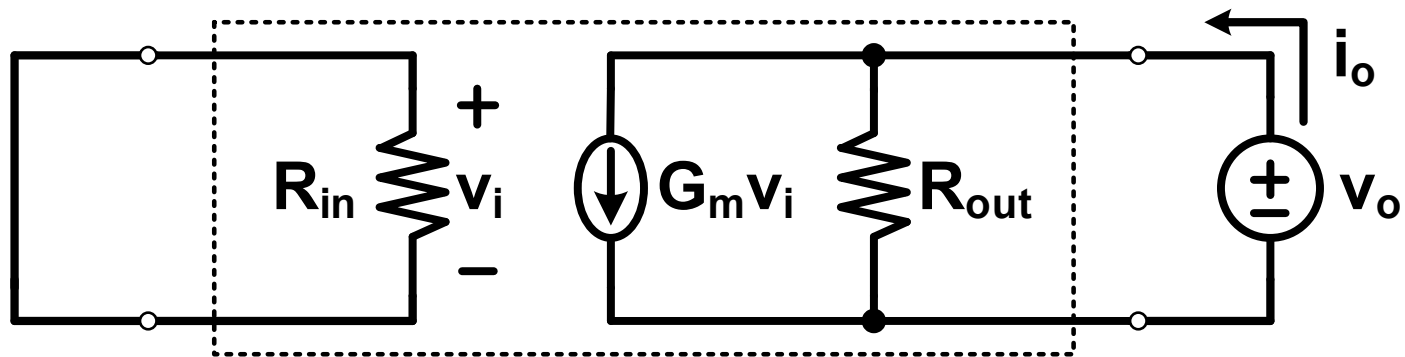
- Short the output, apply an input voltage stimulus, and measure output current



$$R_{out} = \left. \frac{v_o}{i_o} \right|_{v_i=0}$$

- Short the input, apply an output voltage stimulus, and measure current into output node

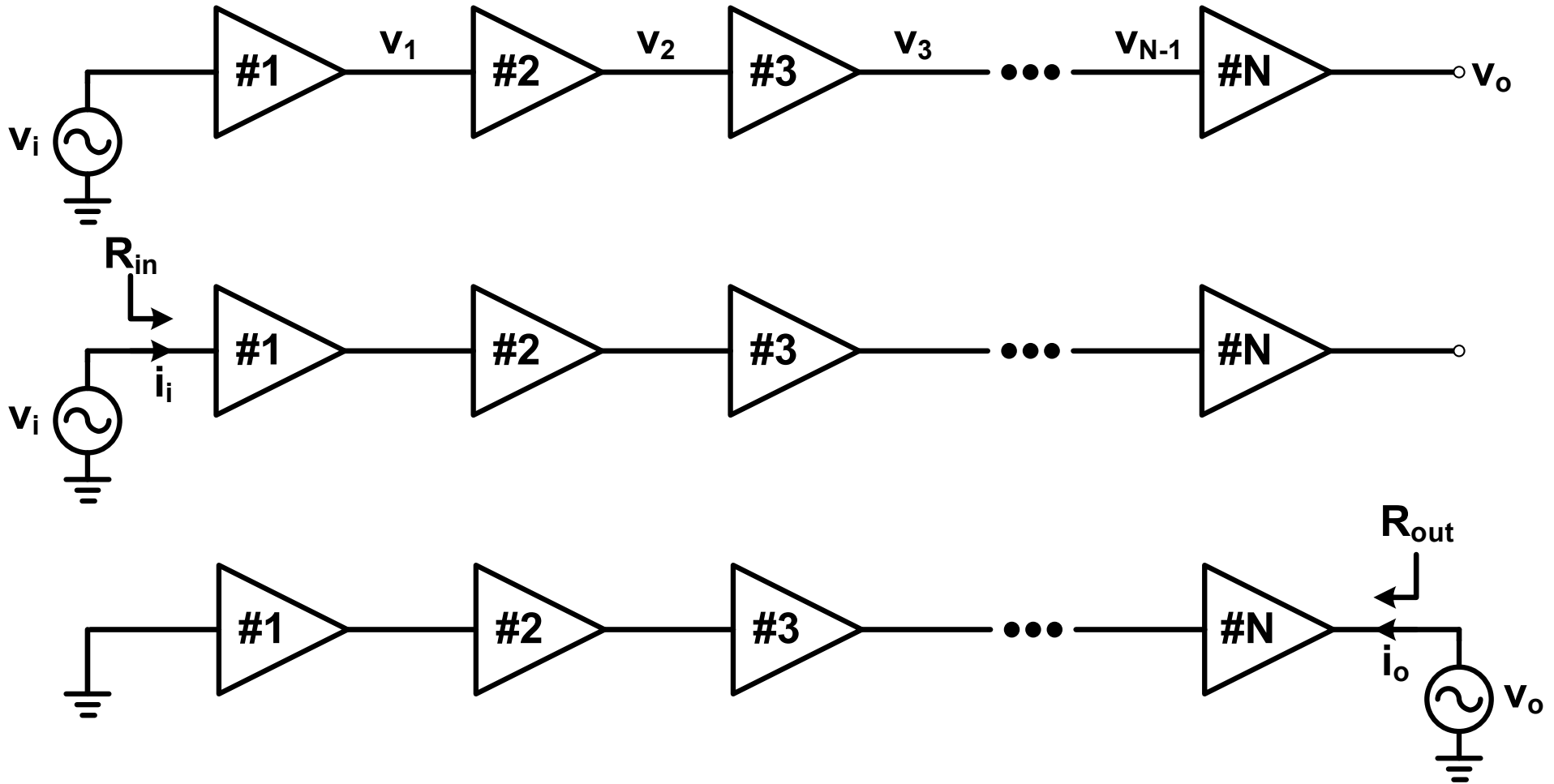Two-Port Modeling – Multi-Stage Amplifiers






$$\frac{v_o}{v_i} = \frac{v_1}{v_i} \frac{v_2}{v_1} \dots \frac{v_o}{v_{N-1}}$$

$$R_{in} = \frac{v_i}{i_i}$$

$$R_{out} = \frac{v_o}{i_o}$$

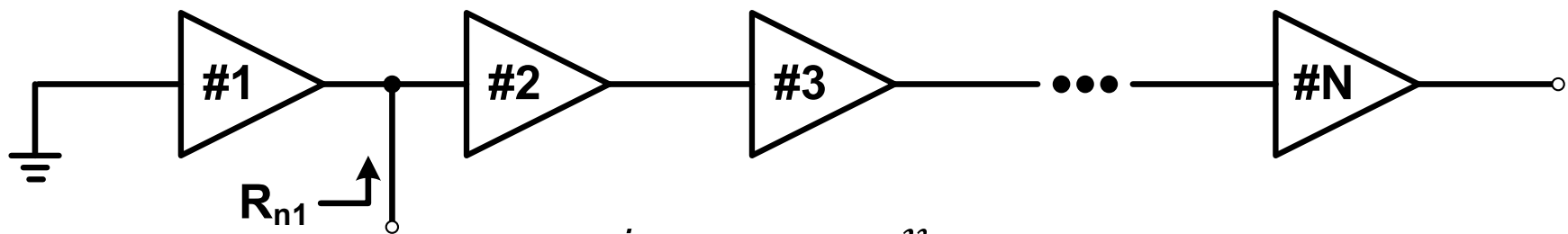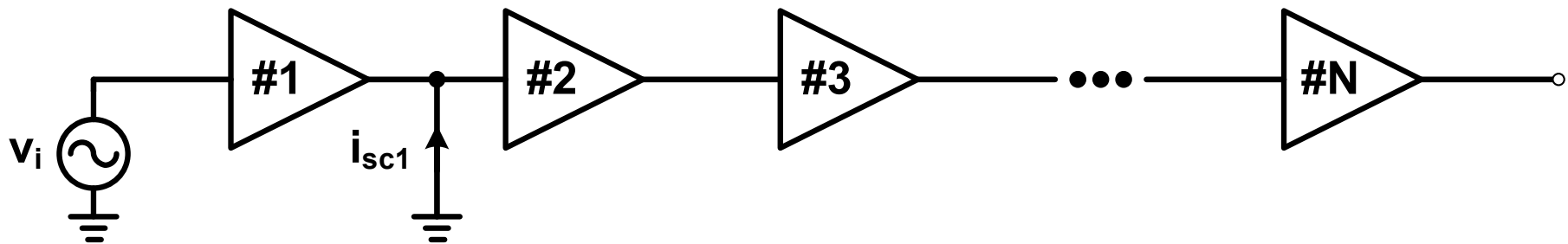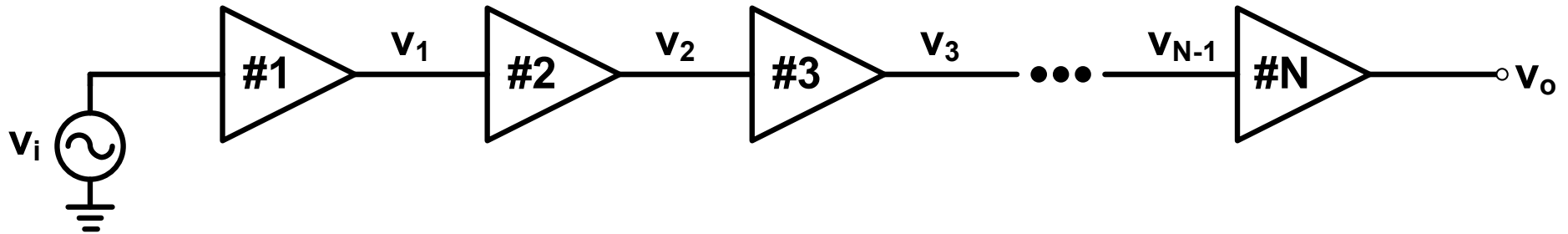Two-Port Modeling – Multi-Stage Amplifiers






$$G_{m1} = \frac{i_{sc1}}{v_i}$$

$$\frac{v_1}{v_i} = -G_{m1}R_{n1}$$

- Note, R_{n1} also includes the input resistance of Stage 2

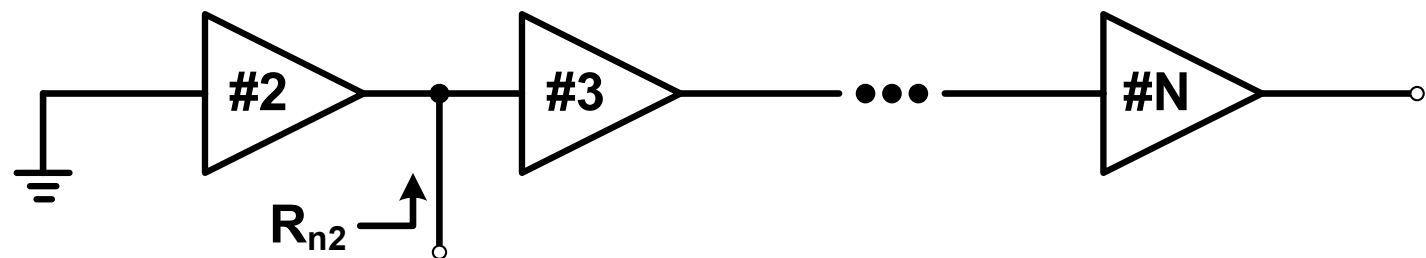
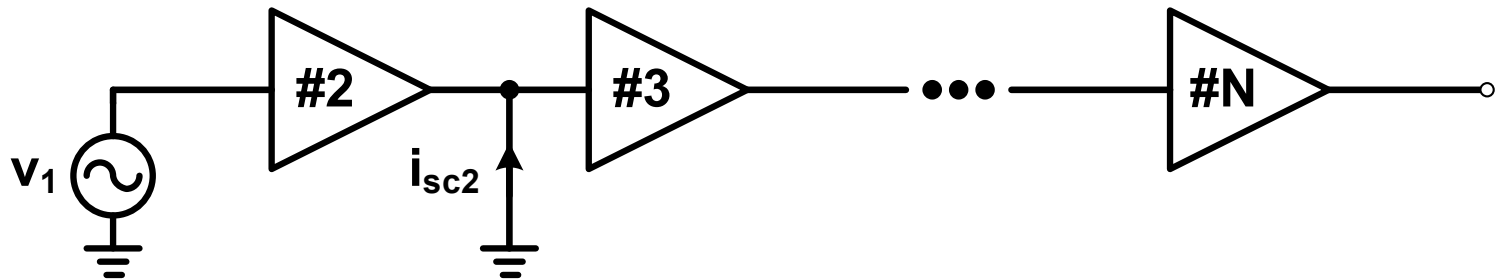
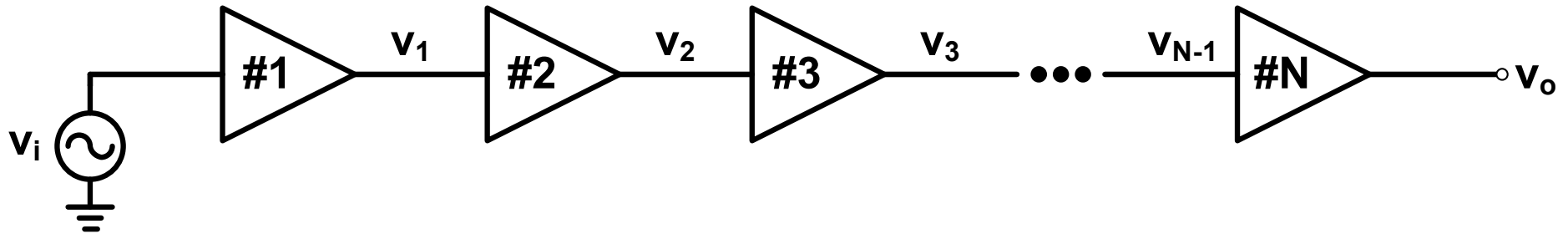
Two-Port Modeling – Multi-Stage Amplifiers



$$G_{m2} = \frac{i_{sc2}}{v_1} \qquad \frac{v_2}{v_1} = -G_{m2}R_{n2}$$

- Repeat procedure stage by stage

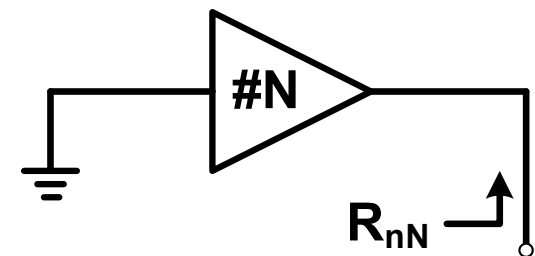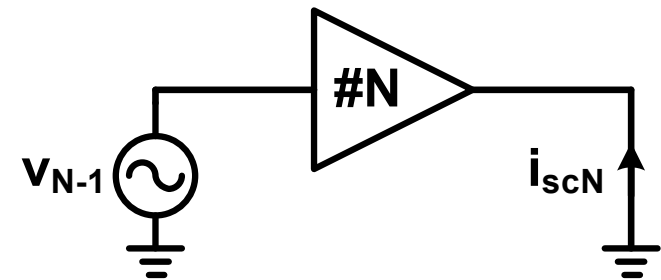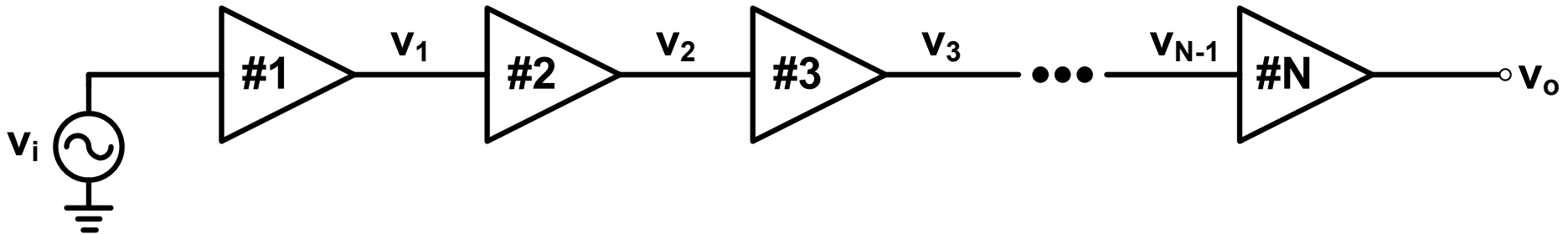Two-Port Modeling – Multi-Stage Amplifiers




$$G_{mN} = \frac{i_{scN}}{v_{N-1}} \quad \frac{v_o}{v_{N-1}} = -G_{mN}R_{nN}$$

- Repeat procedure stage by stage
- This procedure will be useful for analyzing multi-stage transistor amplifiers

BJT Amplifiers AC Gain ($r_o = \infty$)

CE Amp

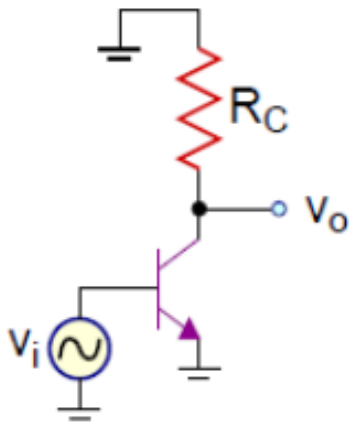


$$\frac{v_o}{v_i} = -g_m R_C = -\frac{\alpha R_C}{r_e}$$

$$G_m = g_m = \frac{\alpha}{r_e}$$

$$R_n = R_C$$

CE Amp w/ R_E

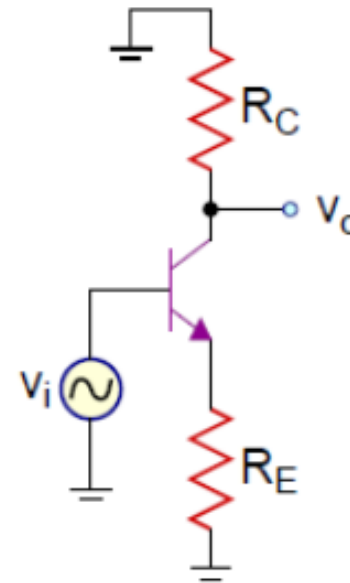


$$\frac{v_o}{v_i} = -\frac{g_m R_C}{1 + \frac{g_m R_E}{\alpha}} = -\frac{\alpha R_C}{r_e + R_E}$$

$$G_m = \frac{g_m}{1 + \frac{g_m R_E}{\alpha}} = \frac{\alpha}{r_e + R_E}$$

$$R_n = R_C$$

BJT Amplifiers AC Gain ($r_o = \infty$)

CC Amp

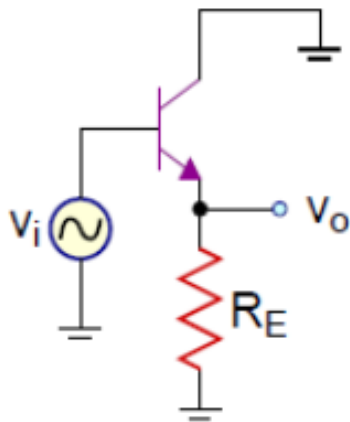


$$\frac{v_o}{v_i} = \frac{R_E}{r_e + R_E}$$

$$G_m = -\frac{1}{r_e}$$

$$R_n = r_e \parallel R_E$$

CB Amp

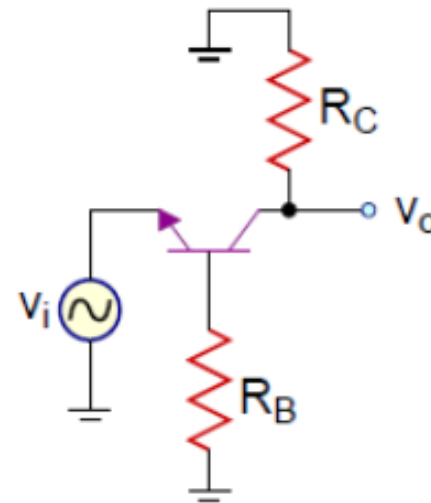


$$\frac{v_o}{v_i} = \frac{g_m R_C}{1 + \frac{g_m R_B}{\beta}} = \frac{\alpha R_C}{R_{emitter}}$$

$$G_m = -\frac{\beta}{r_e(\beta + 1) + R_B} = -\frac{\alpha}{R_{emitter}} = -\frac{g_m}{1 + \frac{g_m R_B}{\beta}}$$

$$R_n = R_C$$

MOSFET Amplifiers AC Gain ($r_o = \infty$)

CS Amp

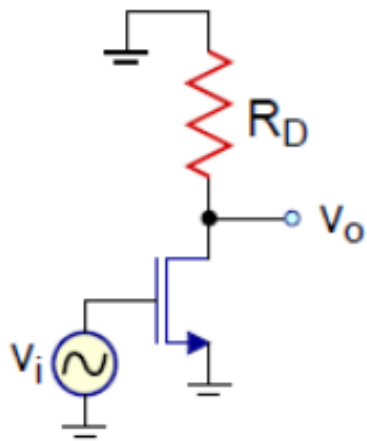


$$\frac{v_o}{v_i} = -g_m R_D$$

$$G_m = g_m$$

$$R_n = R_D$$

CS Amp w/ R_S

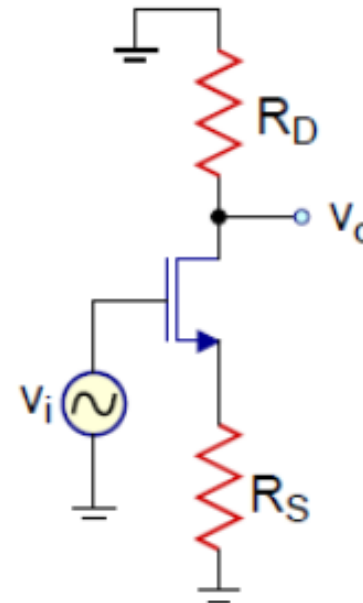


$$\frac{v_o}{v_i} = -\frac{g_m R_D}{1 + g_m R_S}$$

$$G_m = \frac{g_m}{1 + g_m R_S}$$

$$R_n = R_D$$

MOSFET Amplifiers AC Gain ($r_o = \infty$)

CD Amp

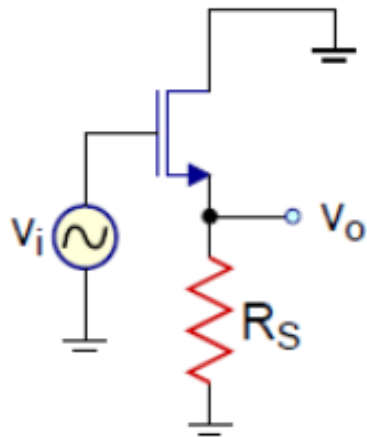


$$\frac{v_o}{v_i} = \frac{g_m R_S}{1 + g_m R_S}$$

$$G_m = -g_m$$

$$R_n = \frac{1}{g_m} \parallel R_S$$

CG Amp

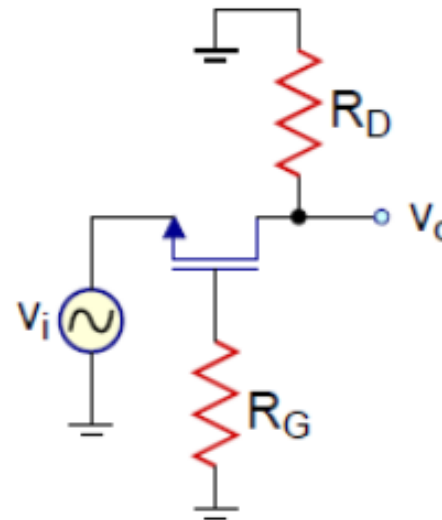


$$\frac{v_o}{v_i} = g_m R_D = \frac{R_D}{R_{source}}$$

$$G_m = -g_m = -\frac{1}{R_{source}}$$


$$R_n = R_D$$

3-Stage BJT Amplifier Example

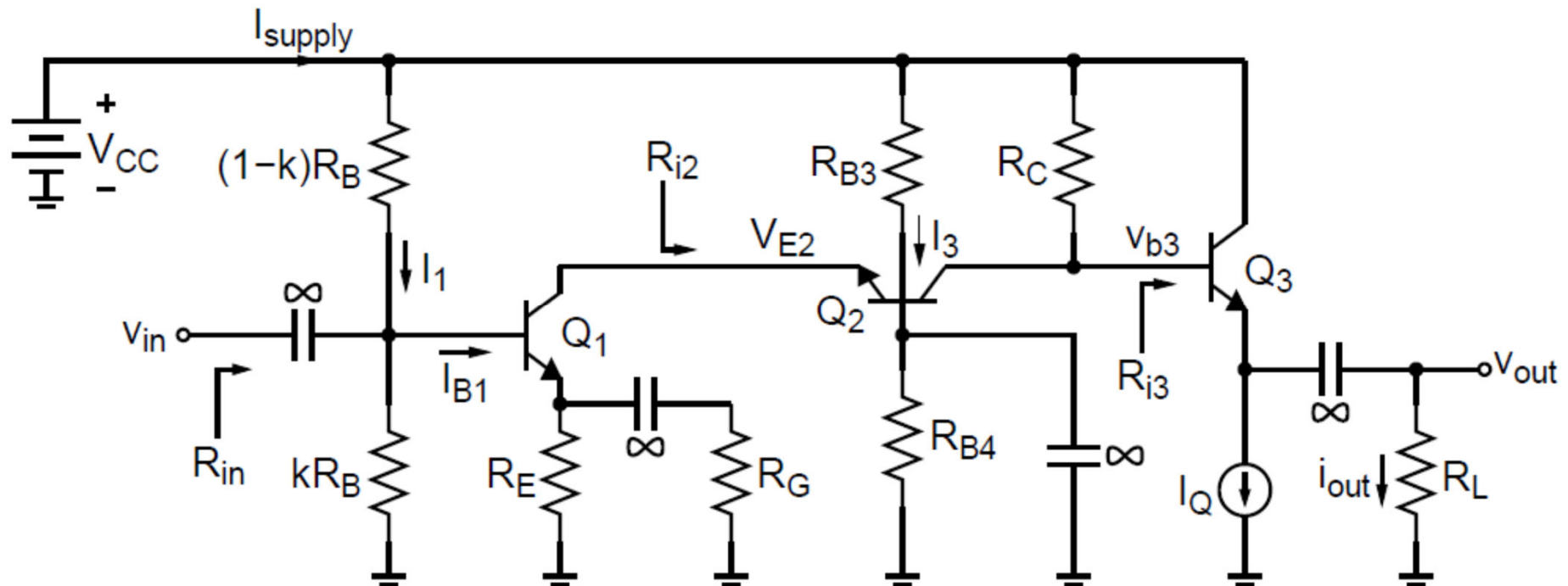

- This multi-stage amplifier consists of common-emitter, common-base, and common-collector amplifier
- The first two common-emitter and common-base stages are commonly used together, and are called a "cascode amplifier"
- The cascode stage provides all the voltage gain of the circuit, while the output common-collector circuit allows driving of a low-resistance load

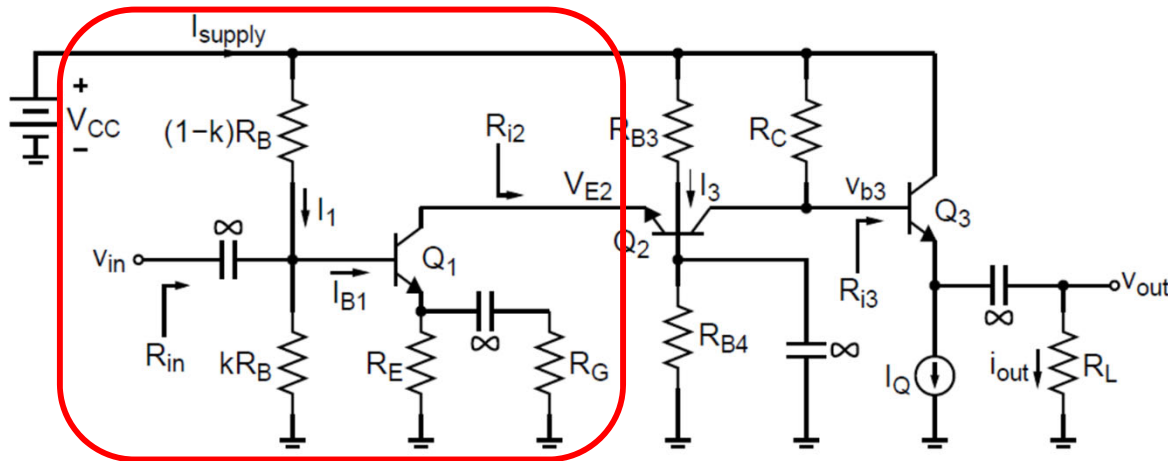3-Stage BJT Amplifier Example – 1st Stage Av



- Using the common-emitter amplifier equations, the gain from the input to V_{E2} is


$$A_{v1} = \frac{v_{e2}}{v_{in}} = -G_{m1}R_{n1}$$

$$G_{m1} = \frac{g_{m1}}{1 + \frac{g_{m1}(R_E \parallel R_G)}{\alpha}} = \frac{\alpha}{r_{e1} + R_E \parallel R_G}$$

$$R_{n1} = R_{i2} = r_{e2}$$

$$A_{v1} = -\frac{\alpha R_{i2}}{r_{e1} + R_E \parallel R_G}$$

CE Amp w/ R_E

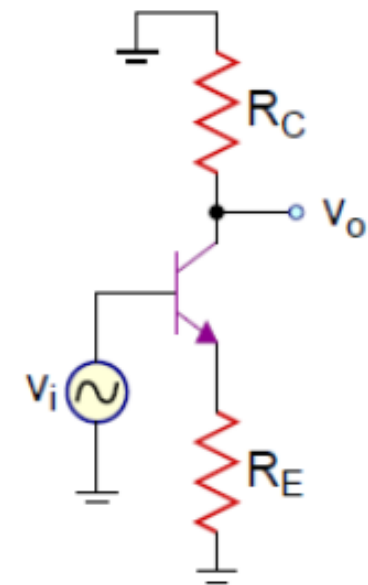


$$\frac{v_o}{v_i} = -\frac{g_m R_C}{1 + \frac{g_m R_E}{\alpha}} = -\frac{\alpha R_C}{r_e + R_E}$$

$$G_m = \frac{g_m}{1 + \frac{g_m R_E}{\alpha}} = \frac{\alpha}{r_e + R_E}$$

$$R_n = R_C$$

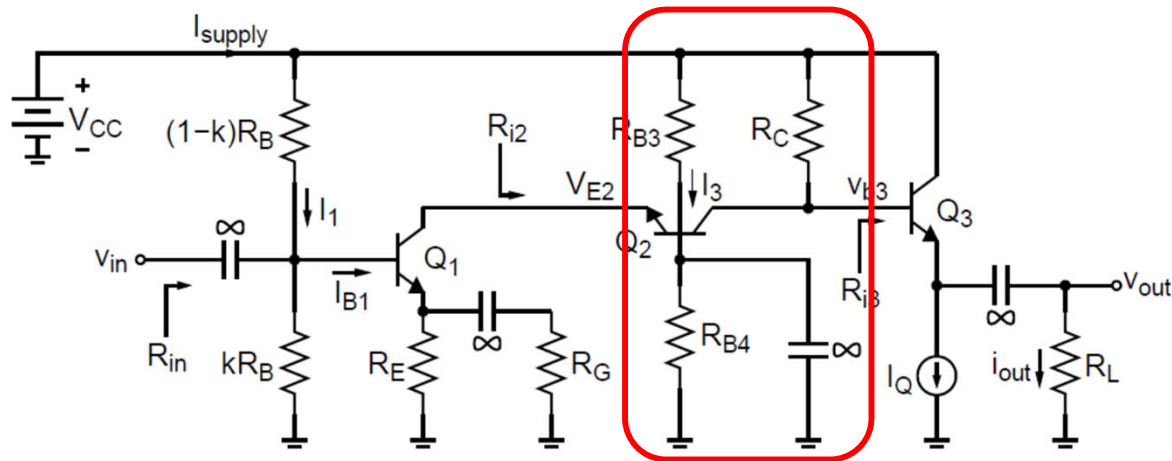3-Stage BJT Amplifier Example – 2nd Stage Av



- Using the common-base amplifier equations, the gain from V_{E2} to V_{B3} is


$$A_{v2} = \frac{v_{b3}}{v_{e2}} = -G_{m2}R_{n2}$$

$$G_{m2} = -\frac{\beta}{r_{e2}(\beta + 1)} = -\frac{\alpha}{R_{i2}} = -g_{m2}$$

$$R_{n2} = R_C \parallel R_{i3} = R_C \parallel [(\beta + 1)(r_{e3} + R_L)]$$

$$A_{v2} = \frac{\alpha(R_C \parallel [(\beta + 1)(r_{e3} + R_L)])}{R_{i2}}$$

CB Amp

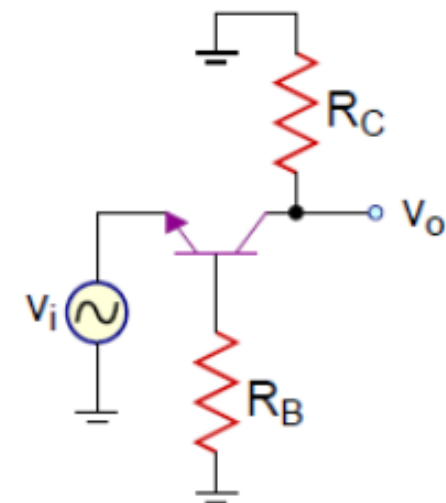


$$\frac{v_o}{v_i} = \frac{g_m R_C}{1 + \frac{g_m R_B}{\beta}} = \frac{\alpha R_C}{R_{emitter}}$$

$$G_m = -\frac{\beta}{r_e(\beta + 1) + R_B} = -\frac{\alpha}{R_{emitter}} = -\frac{g_m}{1 + \frac{g_m R_B}{\beta}}$$

$$R_n = R_C$$

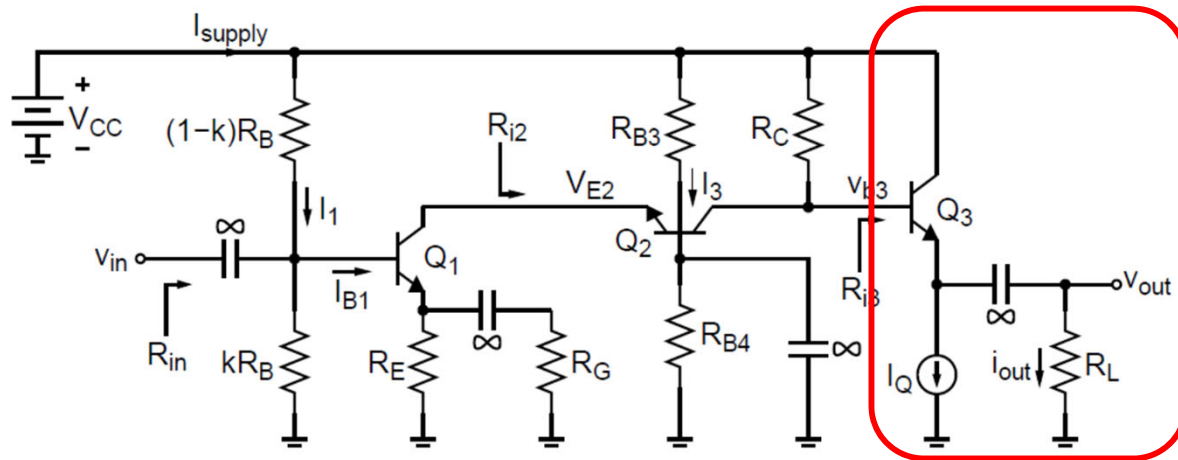3-Stage BJT Amplifier Example – 3rd Stage Av



- Using the common-collector amplifier equations, the gain from V_{B3} to V_{out} is


$$A_{v3} = \frac{v_{out}}{v_{b3}} = -G_{m3}R_{n3}$$

$$G_{m3} = -\frac{1}{r_{e3}}$$

$$R_{n3} = r_{e3} \parallel R_L$$

$$A_{v3} = \frac{R_L}{r_{e3} + R_L}$$

CC Amp

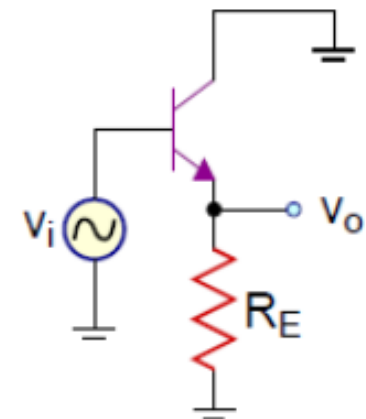


$$\frac{v_o}{v_i} = \frac{R_E}{r_e + R_E}$$

$$G_m = -\frac{1}{r_e}$$

$$R_n = r_e \parallel R_E$$

3-Stage BJT Amplifier Example – Total Av

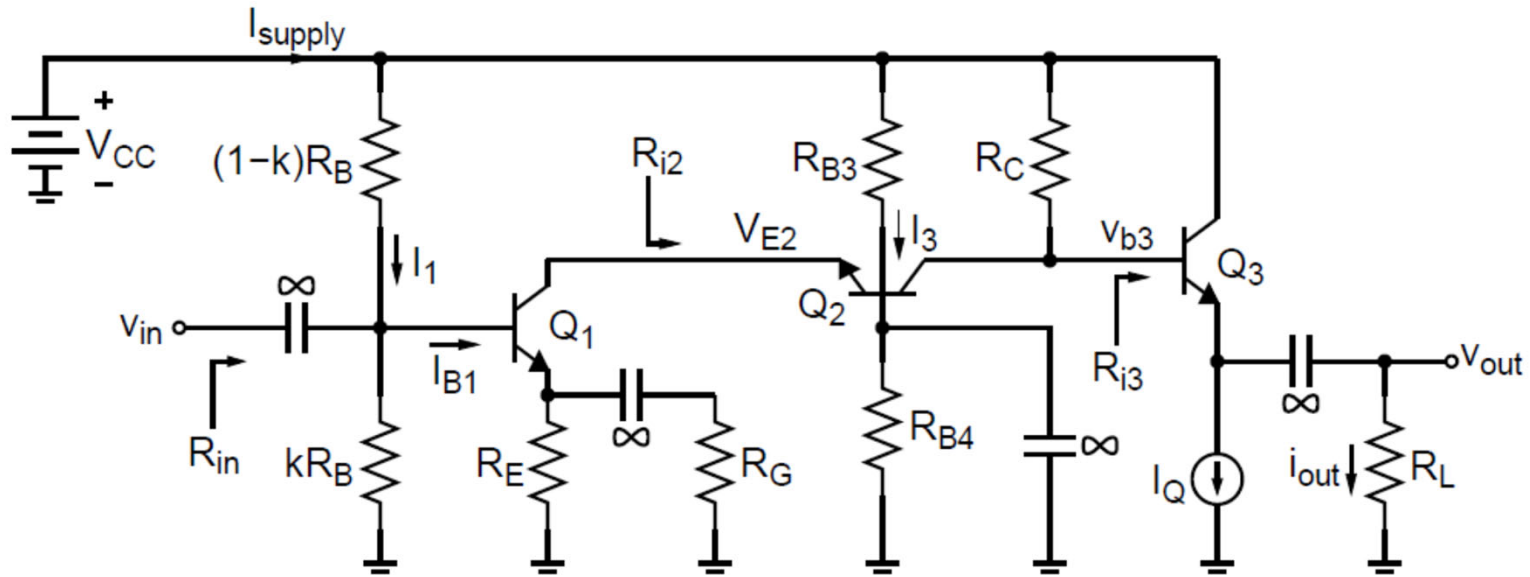


- The total gain is equal to the product of the individual stage gains

$$A_{v,tot} = \frac{v_{out}}{v_{in}} = A_{v1}A_{v2}A_{v3}$$

$$= \left(-\frac{\alpha R_{i2}}{r_{e1} + R_E \parallel R_G} \right) \left(\frac{\alpha (R_C \parallel R_{i3})}{R_{i2}} \right) \left(\frac{R_L}{r_{e3} + R_L} \right)$$

$$\approx \left(-\frac{R_C \parallel R_{i3}}{r_{e1} + R_E \parallel R_G} \right) \left(\frac{R_L}{r_{e3} + R_L} \right)$$


Amplifier Example I

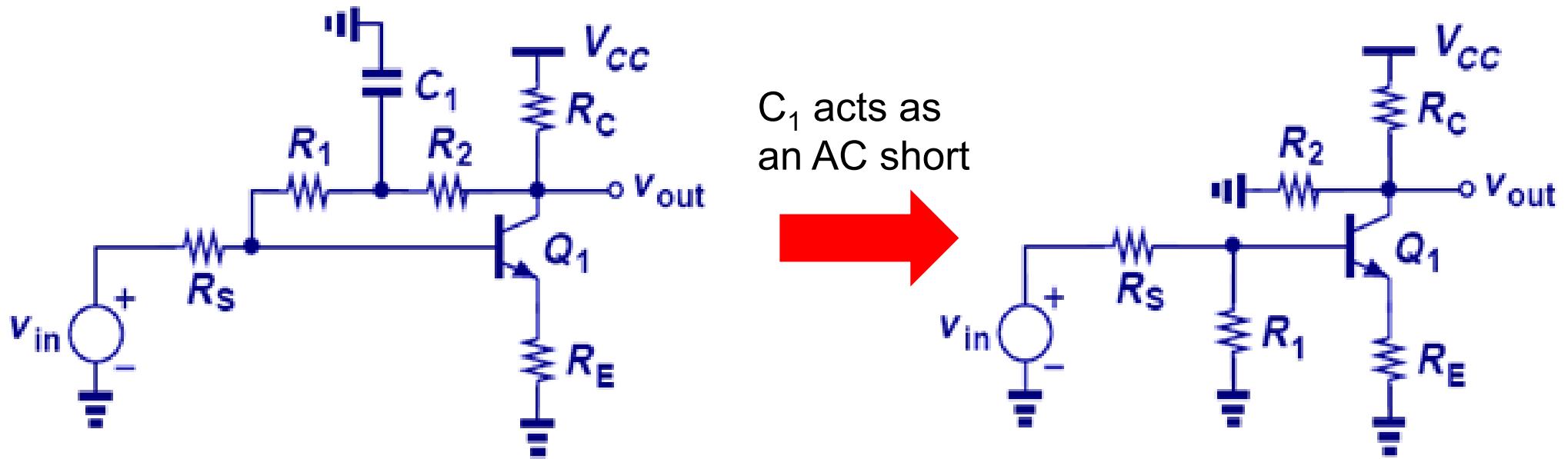

- The keys in solving this problem are recognizing the AC ground between R_1 and R_2 , and Thevenin transformation of the input network
- Then the common-emitter amplifier equations can be used

Amplifier Example I


- Find the input Thevenin equivalent

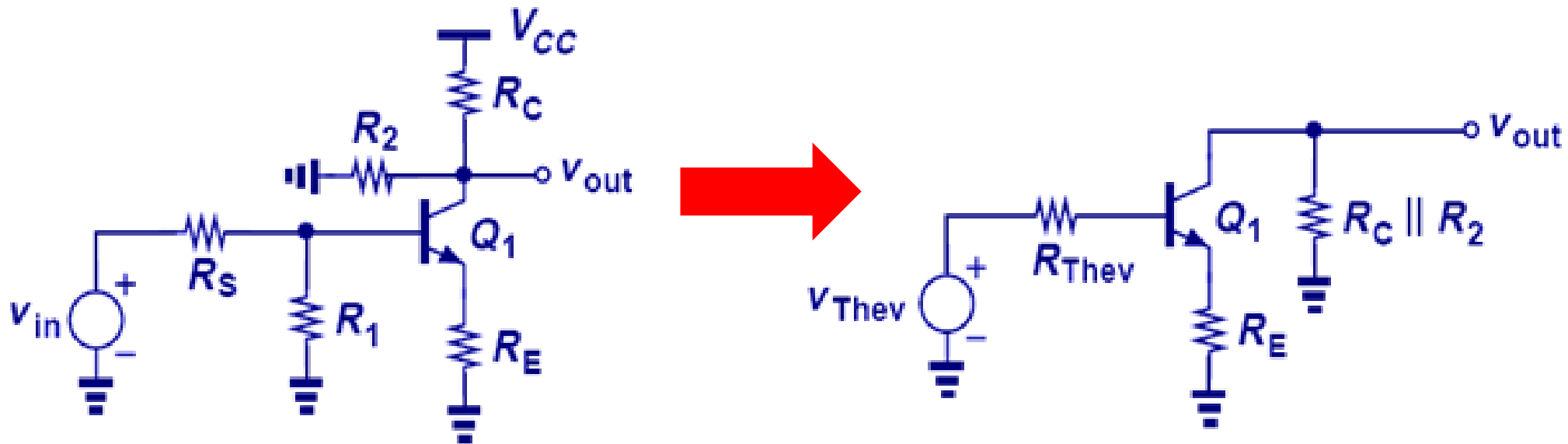

$$v_{Thev} = v_{in} \frac{R_1}{R_S + R_1} \quad R_{Thev} = R_S \parallel R_1$$

Amplifier Example I

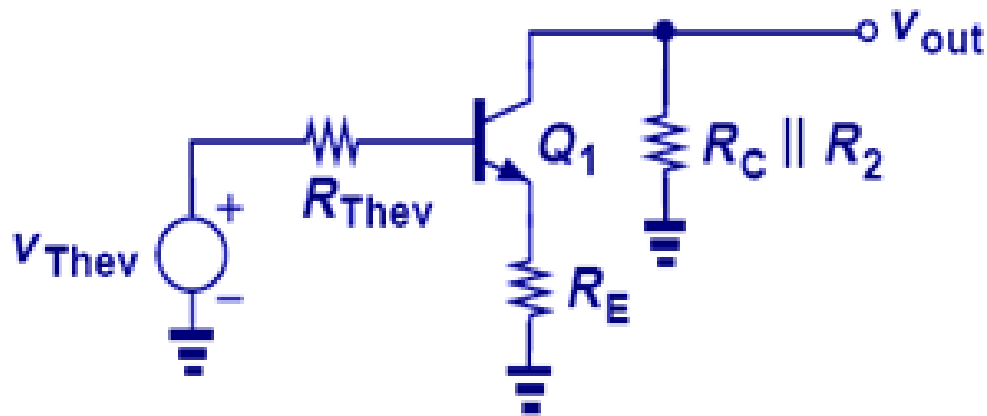
- Use the common-emitter amplifier equations



- As there is a base resistance (R_{Thev}), this must be reflected into the emitter by dividing by $(\beta+1)$ to use the derived equation


$$\frac{v_o}{v_i} = - \frac{\alpha(R_C \parallel R_2)}{\frac{R_1 \parallel R_S}{\beta+1} + r_e + R_E} \cdot \frac{R_1}{R_1 + R_S}$$

CE Amp w/ R_E

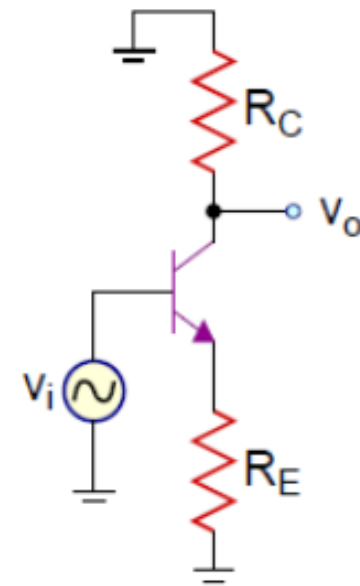

$$\frac{v_o}{v_i} = - \frac{g_m R_C}{1 + \frac{g_m R_E}{\alpha}} = - \frac{\alpha R_C}{r_e + R_E}$$


Amplifier Example II

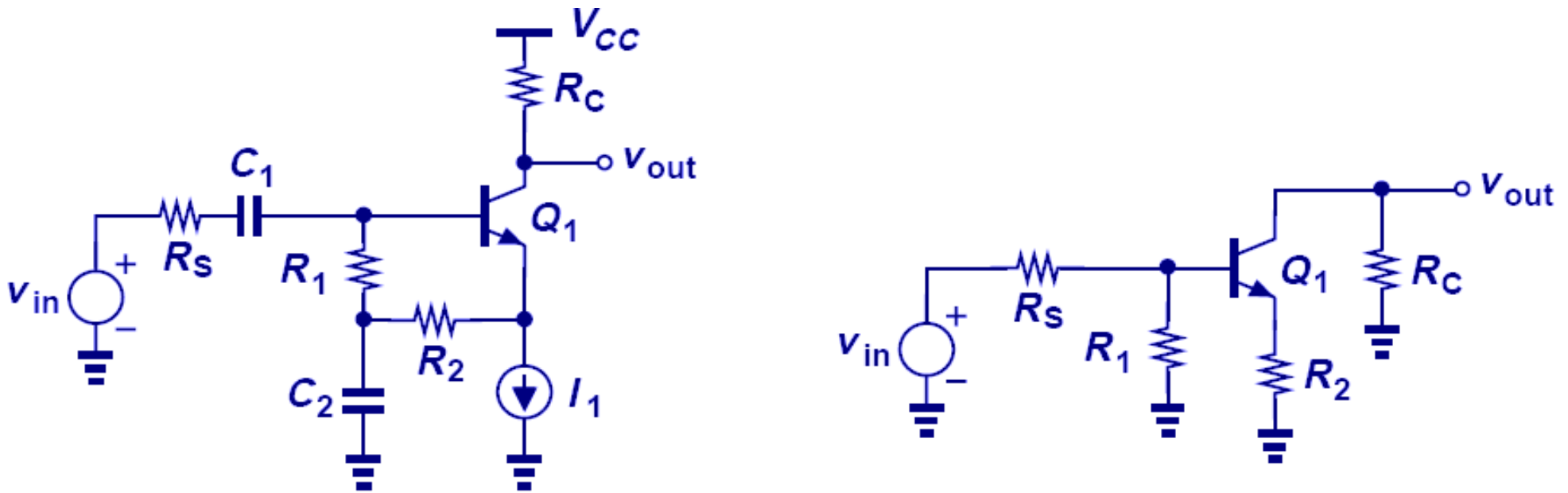

$$\frac{v_o}{v_i} = - \frac{\alpha R_C}{\frac{R_1 \parallel R_S}{\beta + 1} + r_e + R_2} \cdot \frac{R_1}{R_1 + R_S}$$

- Again, AC ground/short and Thevenin transformation are needed to transform the complex circuit into a simple stage with emitter degeneration.

Amplifier Example III

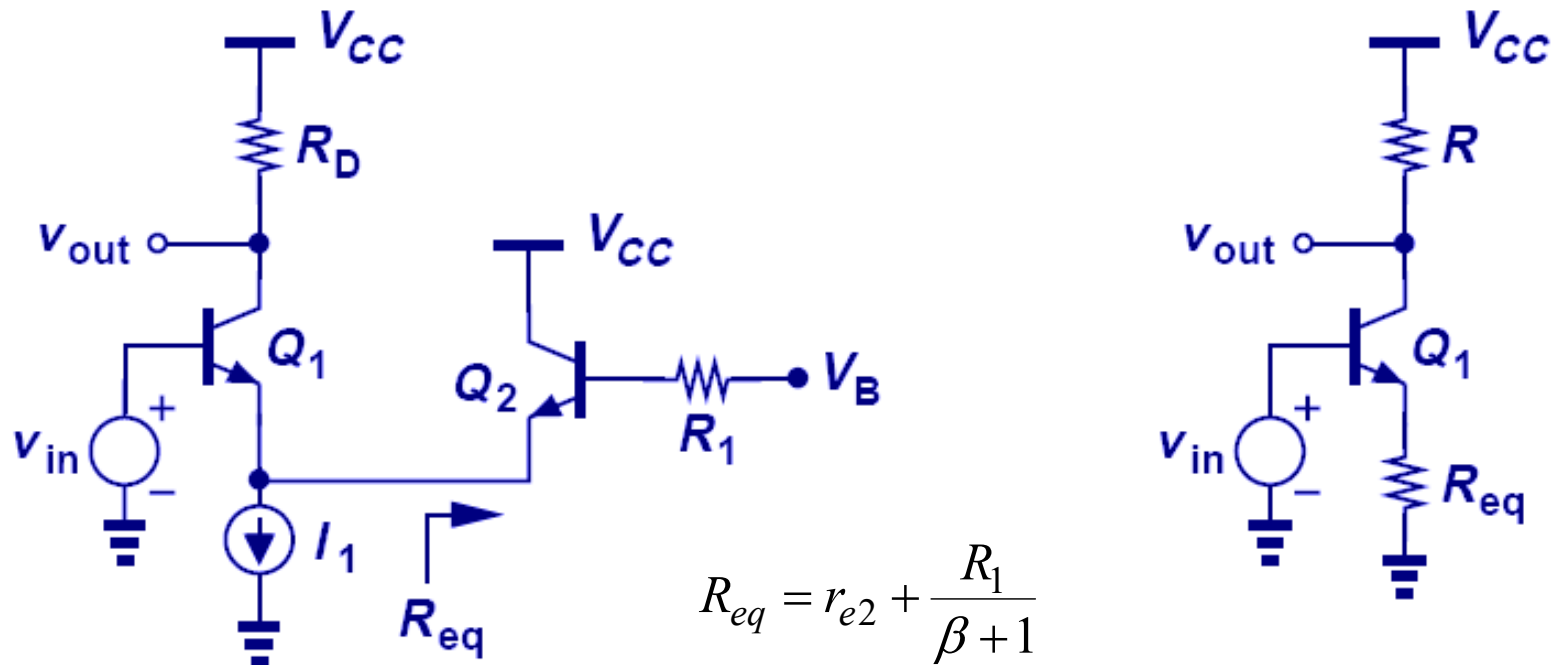

$$R_{eq} = r_{e2} + \frac{R_1}{\beta + 1}$$

$$R_{in} = (\beta + 1)(r_{e1} + R_{eq}) = (\beta + 1) \left(r_{e1} + r_{e2} + \frac{R_1}{\beta + 1} \right) = r_{\pi 1} + r_{\pi 2} + R_1$$

$$\frac{v_o}{v_i} = - \frac{\alpha R_D}{r_{e1} + r_{e2} + \frac{R_1}{\beta + 1}}$$

- The key for solving this problem is first identifying R_{eq} , which is the impedance seen at the emitter of Q_2 in parallel with the infinite output impedance of an ideal current source

Next Time

- Differential amplifiers
 - Razavi Chapter 10