

ECEN326: Electronic Circuits

Spring 2022

Lecture 8: Output Stages and Power Amplifiers



Sam Palermo
Analog & Mixed-Signal Center
Texas A&M University

Announcements

- Homework 8 due Apr 28
- Exam 3 May 5
 - 12:30 – 2:30
 - Closed book w/ one standard note sheet
 - 8.5"x11" front & back
 - Bring your calculator
 - Emphasis will be on Lectures 7-8
 - Sample Exam3s posted on website
- Reading
 - Razavi Chapter 14

Agenda

- General Output Stage Considerations
- Emitter Follower as a Power Amplifier
- Push-Pull Stage
- Improved Push-Pull Stage
- Large-Signal Considerations
- Heat Dissipation
- Efficiency and Power Amplifier Classes

Why Special Output Stages or Power Amplifiers?

- Power amplifiers are necessary to efficiently drive a load with high power
- Examples
 - A cellphone may need 1W of power at the antenna
 - Audio systems require tens to hundreds of Watts
- As ordinary voltage/current amplifiers are not suited for efficiently supporting these power levels, specialized output stages are necessary

Power Amplifier Characteristics

- Can drive a small “heavy” load resistance
 - Example: Speaker resistance can be 4-16Ω
- Delivers large current levels
 - Often in the hundreds of mA
- Requires large voltage swings
- Draws a large amount of power from the supplies
- Dissipates a large amount of power, and thus can get **hot**

Example : Delivering 1W to an 8Ω speaker

$$\text{Sinusoidal } P_{out} = \left(\frac{V_P}{\sqrt{2}} \right)^2 \cdot \frac{1}{R_L} = 1W$$

This results in a peak voltage

$$V_P = 4V$$

and a peak current

$$I_P = \frac{V_P}{R_L} = \frac{4V}{8\Omega} = 500mA$$

Power Amplifier Performance Metrics

- Linearity or Distortion
 - Audio amplifiers must have low distortion to reproduce music with high fidelity

- Power Efficiency


$$\eta = \frac{\text{Power Delivered to Load}}{\text{Power Drawn from Supply}}$$

- Maximum Voltage Rating
 - May require high power supplies
 - Transistors must have sufficiently high breakdown voltages


Agenda

- General Output Stage Considerations
- Emitter Follower as a Power Amplifier
- Push-Pull Stage
- Improved Push-Pull Stage
- Large-Signal Considerations
- Heat Dissipation
- Efficiency and Power Amplifier Classes

 Emitter Follower Large-Signal Behavior: Positive Half-Cycle




 Here V_{BE} is assumed to be 0.8 V due to the high current levels




- As V_{in} increases V_{out} also follows and Q_1 provides more current
- No major issue with the input signal positive half-cycle

 Emitter Follower Large-Signal Behavior: Negative Half-Cycle



(c)

 


(d)

- However as V_{in} decreases, V_{out} also decreases, shutting off Q_1 and resulting in a constant V_{out}
- The output signal clips at a minimum value of $-I_1 R_L$

 Example: Emitter Follower

- What are the input and output voltages when I_{C1} drops to 1% of I_1 ?



$$\text{Assume } I_S = 5 \times 10^{-15} \text{ A}$$

$$V_{in} - V_{BE} = V_{out}$$


$$V_{in} - V_T \ln \left[\frac{I_{C1}}{I_S} \right] = (I_{C1} - I_1) R_L$$

$$V_{in} = 25.9 \text{ mV} \ln \left[\frac{0.325 \text{ mA}}{5 \times 10^{-15} \text{ A}} \right] + (0.325 \text{ mA} - 32.5 \text{ mA}) 8 \Omega = 387 \text{ mV}$$


$$V_{out} = 387 \text{ mV} - 25.9 \text{ mV} \ln \left[\frac{0.325 \text{ mA}}{5 \times 10^{-15} \text{ A}} \right] = -258 \text{ mV}$$

- At this current level, the V_{BE} has dropped to 645mV
- For voltage levels much below 400mV, the output will saturate at $-I_1 R_L = -260 \text{ mV}$

Linearity of an Emitter Follower

 


(a)

 

(b)

 
- As V_{in} decreases the output waveform will be clipped, introducing nonlinearity in I/O characteristics
- Overall, the fixed I_1 limits the output swing



Agenda


- General Output Stage Considerations
- Emitter Follower as a Power Amplifier
- **Push-Pull Stage**
- Improved Push-Pull Stage
- Large-Signal Considerations
- Heat Dissipation
- Efficiency and Power Amplifier Classes

Push-Pull Stage

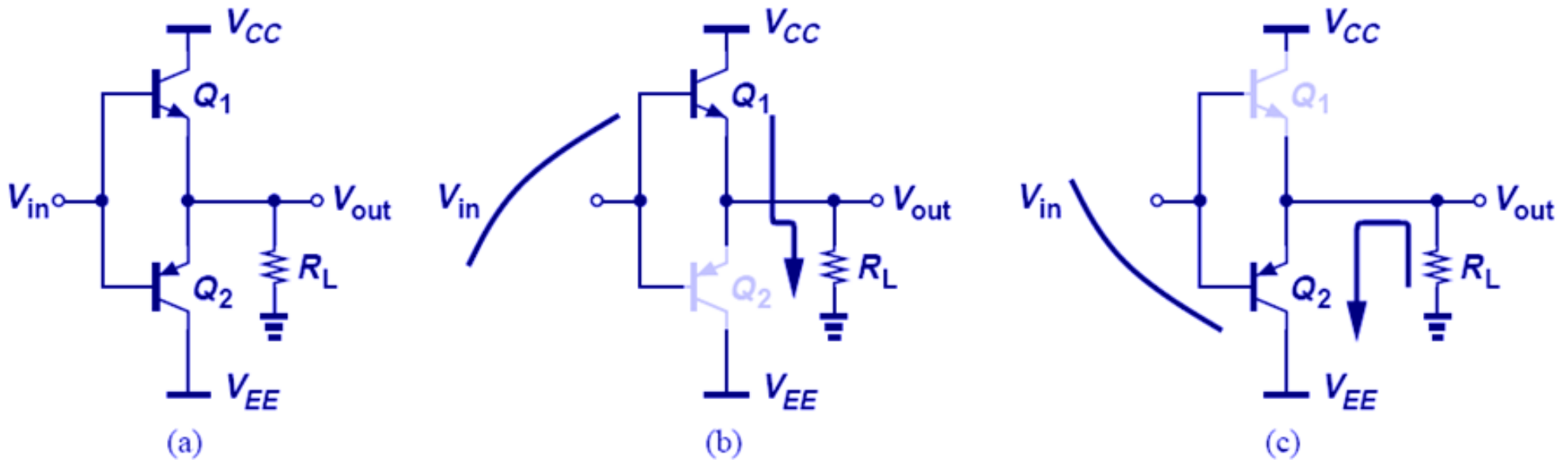


- As V_{in} increases, Q_1 is on and pushes a current into R_L .
- As V_{in} decreases, Q_2 is on and pulls a current out of R_L .
- For positive V_{in} , Q_1 shifts the output down and for negative V_{in} , Q_2 shifts the output up.

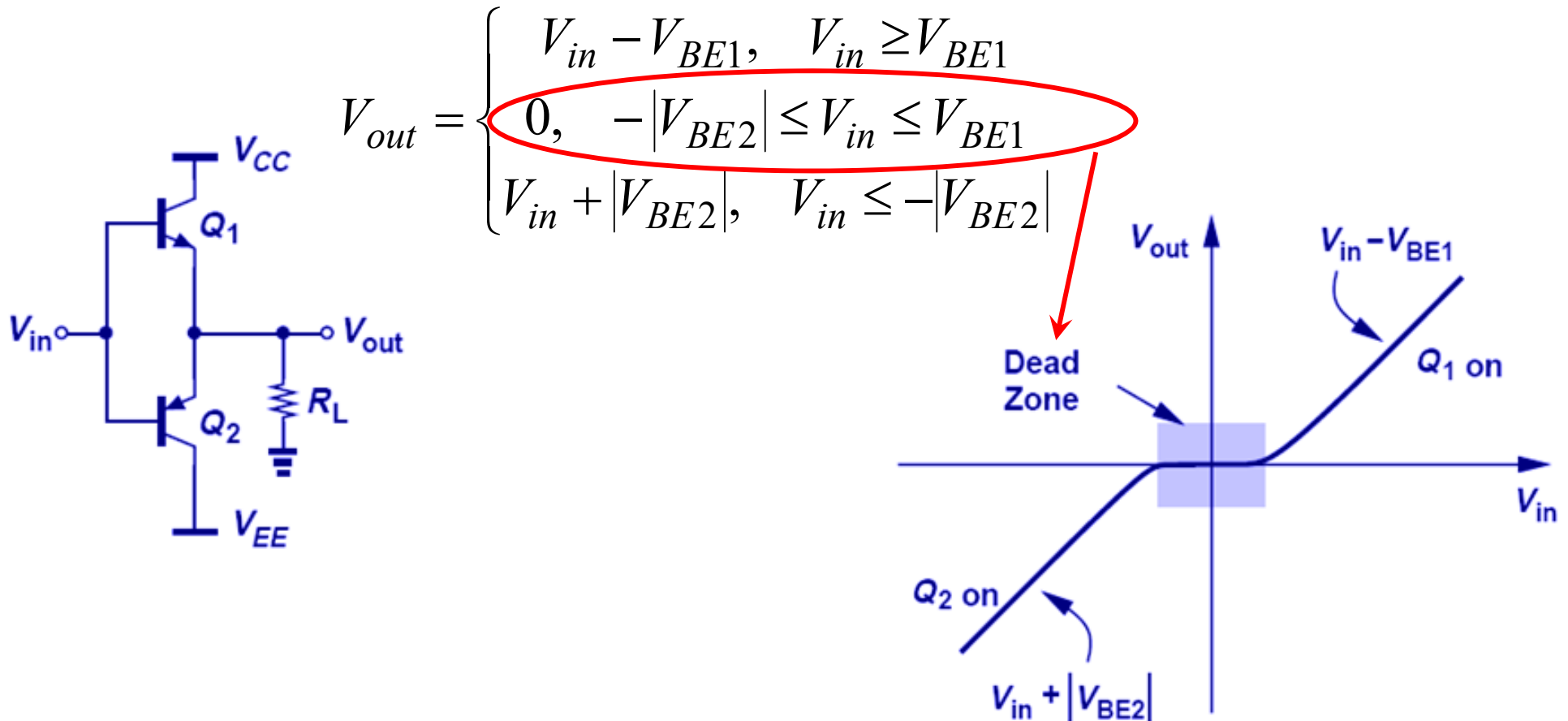Overall I/O Characteristics of Push-Pull Stage




- However, for small V_{in} , there is a dead zone (both Q_1 and Q_2 are off) in the I/O characteristic, resulting in gross nonlinearity
- The dead zone is from $-|V_{BE2}| \leq V_{in} \leq V_{BE1}$

Small-Signal Gain of Push-Pull Stage

 


$$A_v = \frac{R_L}{R_L + r_e}$$

 

- The push-pull stage exhibits a gain that tends to unity when either Q_1 or Q_2 is on.
- When V_{in} is very small, the gain drops to zero.

Sinusoidal Response of Push-Pull Stage

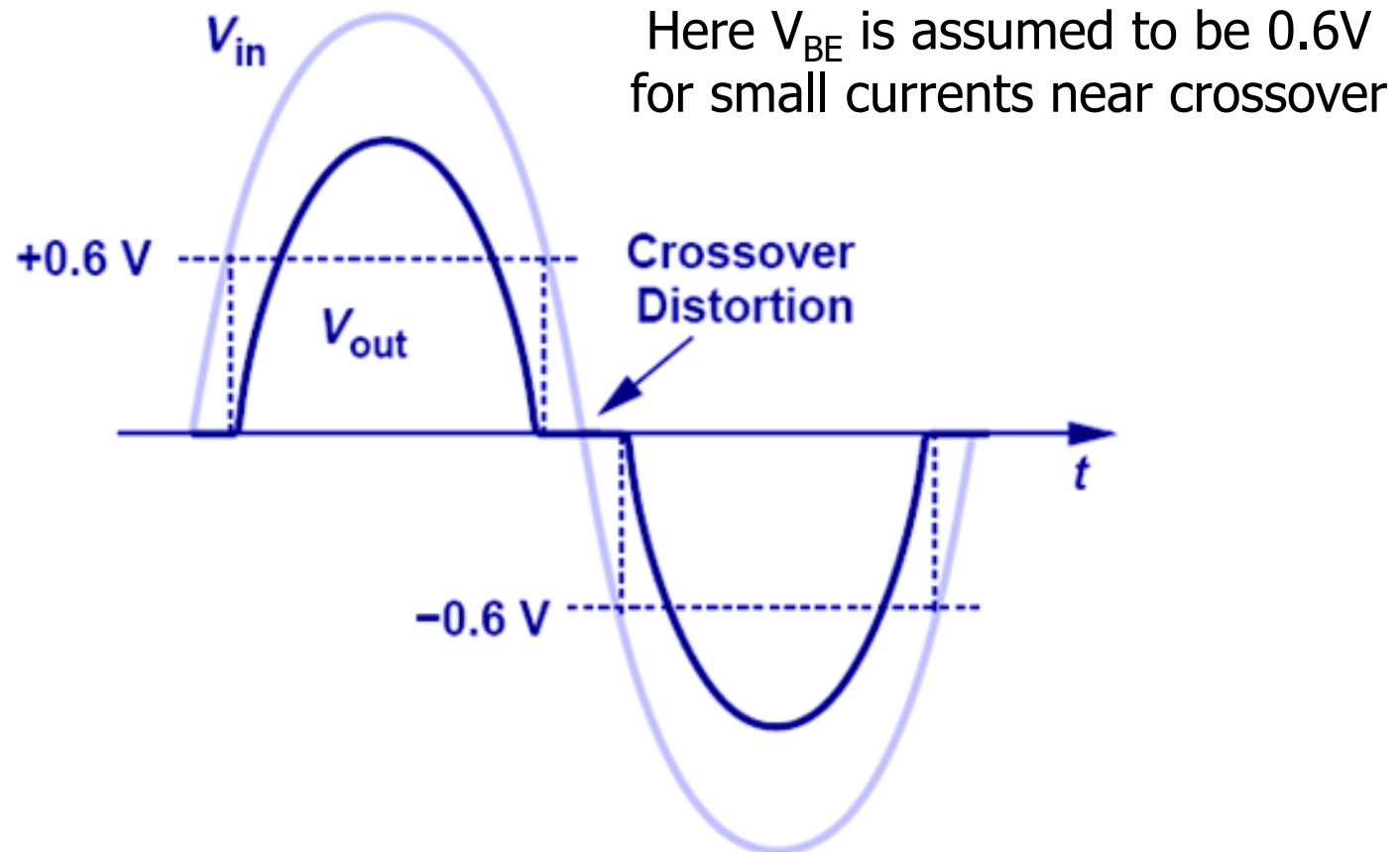


- For large V_{in} , the output follows the input with a fixed DC offset, however as V_{in} becomes small the output drops to zero and causes “Crossover Distortion.”

Agenda

- General Output Stage Considerations
- Emitter Follower as a Power Amplifier
- Push-Pull Stage
- Improved Push-Pull Stage
- Large-Signal Considerations
- Heat Dissipation
- Efficiency and Power Amplifier Classes

Improved Push-Pull Stage

 - With a battery of V_B inserted between the bases of Q_1 and Q_2 , the dead zone is eliminated.



What should V_B be so that at least one transistor is always on?


Q_2 turns off when $V_{in} = -|V_{BE2}|$

at this point we want Q_1 on, or $V_1 = V_{BE1}$


Thus, $V_B = V_1 - V_{in} = V_{BE1} - (-|V_{BE2}|)$

$$V_B = V_{BE1} + |V_{BE2}|$$

Implementation of V_B

 


(a)

 

(b)

- Since $V_B = V_{BE1} + |V_{BE2}|$, a natural choice would be two series diodes
- I_1 in figure (b) is used to bias the diodes and Q_1 .

Example: Current Flow I

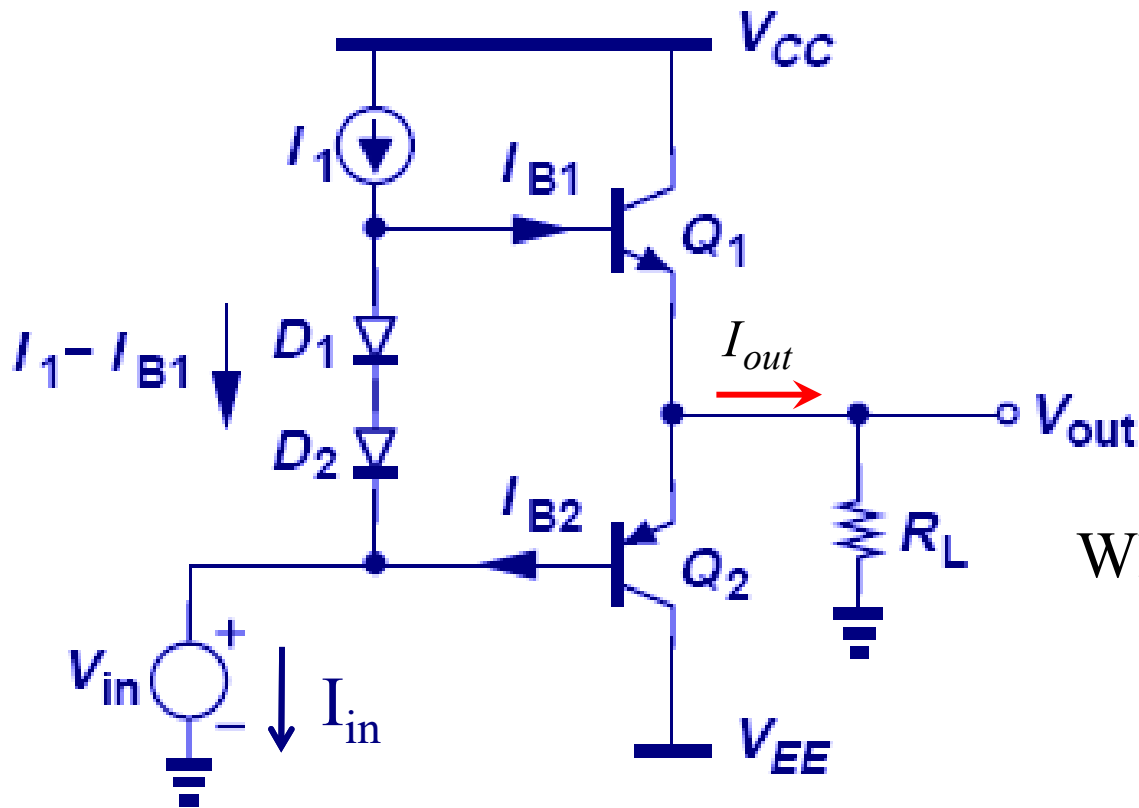

$$I_{in} = I_1 - I_{B1} + I_{B2}$$

When is $I_{in} = I_1$, assuming $\beta_1 = \beta_2$?

This occurs when $I_{B1} = I_{B2}$,
which implies that $I_{C1} = I_{C2}$

and that $I_{out} = 0$


Thus, this occurs when

$$V_{out} = 0$$

The V_{in} source must support I_1 and the Q_1 and Q_2 base current difference, which can excessively load the source

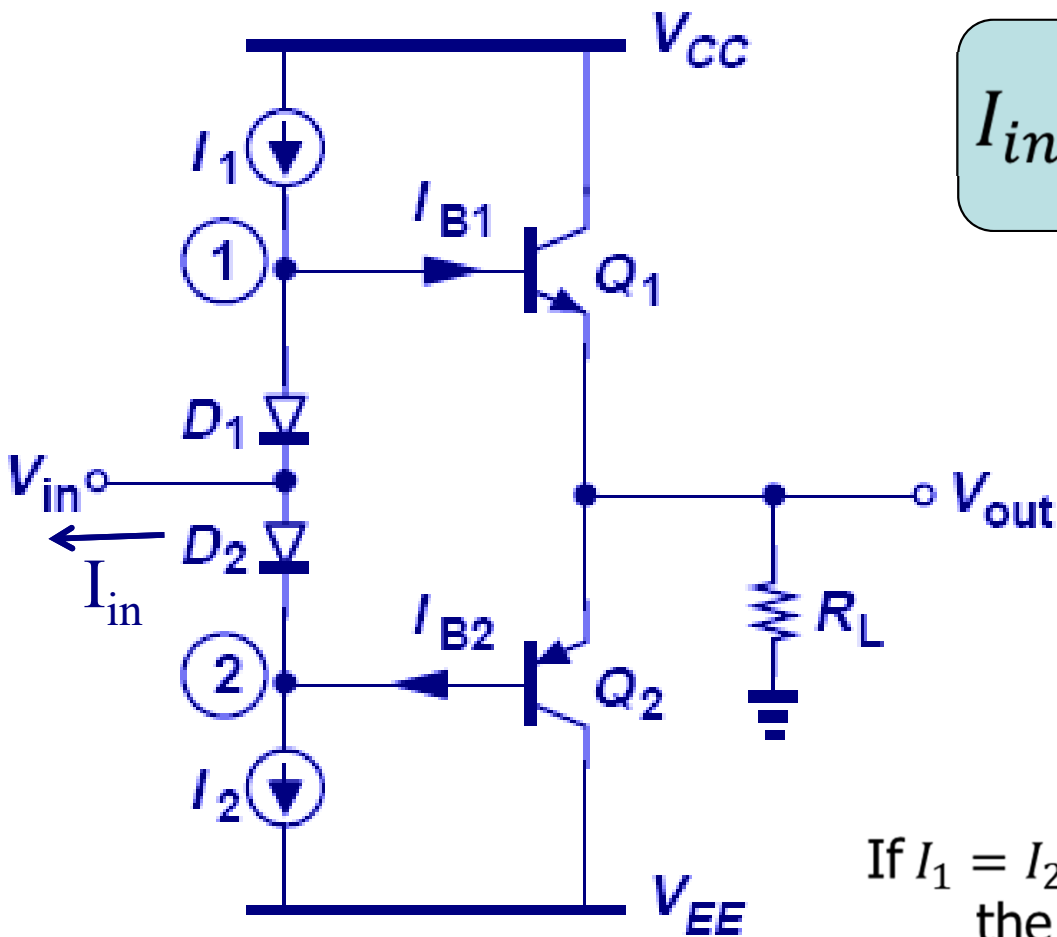Example: Current Flow II

- The offset between input and output is minimized when the input is in the middle of the diodes



$$I_{in} = (I_1 - I_2) + (I_{B2} - I_{B1})$$

If $V_{D1} \approx V_{BE1}$ and $V_{D2} \approx |V_{BE2}|$,
then $V_{out} \approx V_{in}$


Assuming a balanced design with

$$I_1 = I_2 \text{ and } I_{B1} \approx I_{B2},$$

then $I_{in} = 0$ when $V_{out} = 0$


If $I_1 = I_2$, then the V_{in} source must only support the Q_1 and Q_2 base current difference

Addition of CE Stage


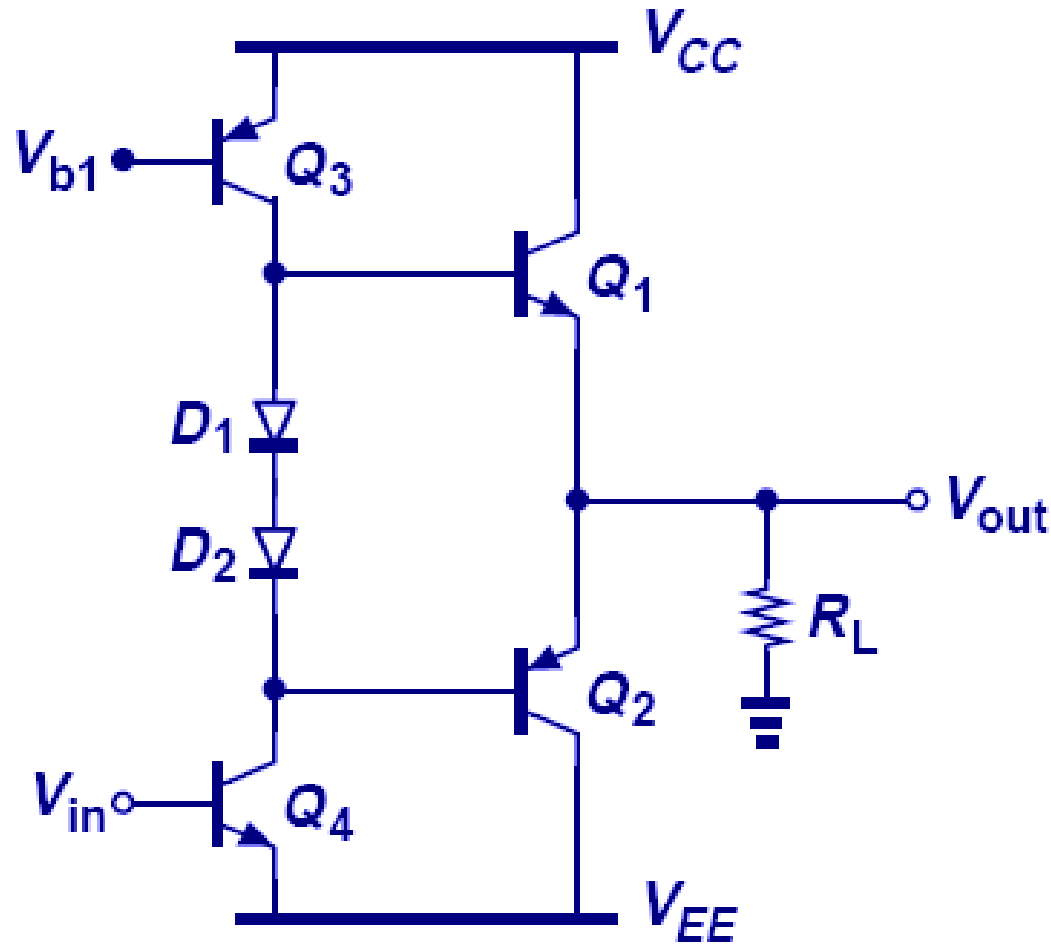


- A CE stage (Q_4) is added to provide voltage gain from the input to the bases of Q_1 and Q_2
- This push-pull circuit is often used in high-power output stages

Bias Point Analysis

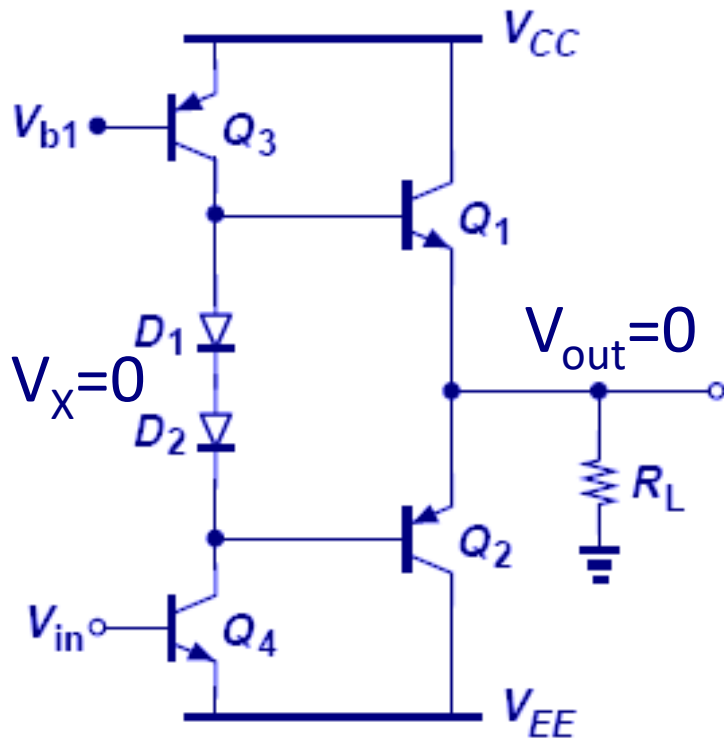

With $V_{out} = 0$ and assuming that $I_{C3} = I_{C4}$, $V_{D1} = V_{BE1}$, and $V_{D2} = |V_{BE2}|$ then the voltage in the middle of the diodes $V_X = 0$, and we can redraw the top half of the circuit

  

$$V_{D1} = V_T \ln \left(\frac{|I_{C3}|}{I_{S,D1}} \right) = V_{BE1} = V_T \ln \left(\frac{I_{C1}}{I_{S,Q1}} \right)$$

$$I_{C1} = \left(\frac{I_{S,Q1}}{I_{S,D1}} \right) |I_{C3}|$$


- For bias point analysis, the circuit can be simplified to the one on the right, which resembles a current mirror
- For a well-defined I_S ratio, D_1 can be realized as a diode-connected transistor

Small-Signal Analysis - I

In order to derive the gain of the circuit, we can treat it as a two - stage amplifier

$$\frac{v_{out}}{v_{in}} = \frac{v_N}{v_{in}} \cdot \frac{v_{out}}{v_N}$$

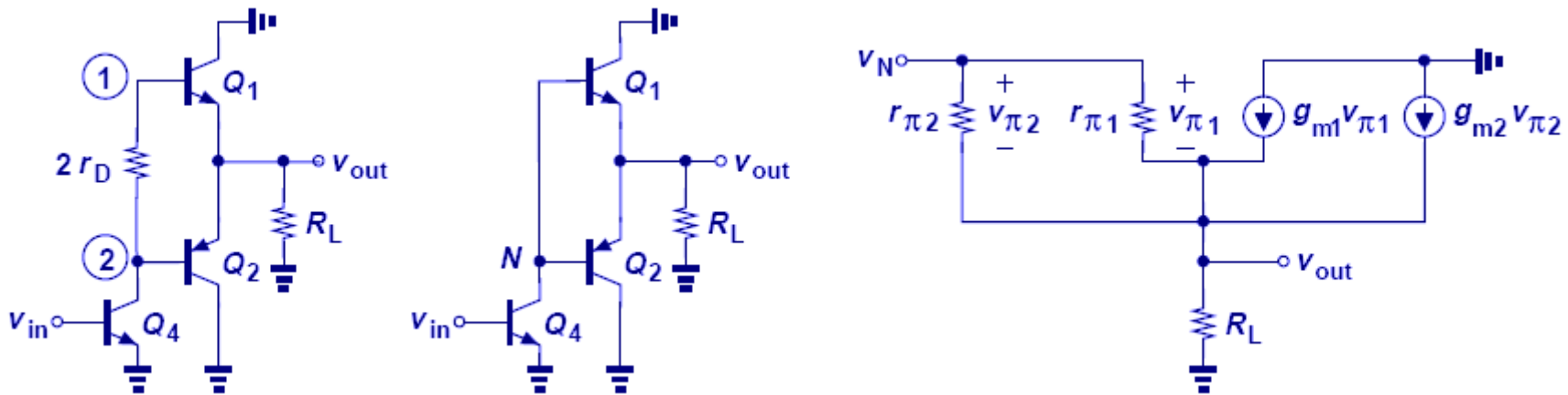Assuming $V_A = \infty$ and $r_D = 0$, the second stage can be viewed as 2 parallel emitter followers






$$\frac{v_{out}}{v_N} = \frac{R_L}{R_L + r_{e1} \parallel r_{e2}} \approx \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

Small-Signal Analysis - II

The gain of the first stage can be expressed as

$$\frac{v_N}{v_{in}} = -g_{m4}R_N \quad \text{where}$$
   
$$R_N = r_{\pi 1} \parallel r_{\pi 2} + (g_{m1} + g_{m2})(r_{\pi 1} \parallel r_{\pi 2})R_L$$




The overall gain is

$$\frac{v_{out}}{v_{in}} = \frac{v_N}{v_{in}} \cdot \frac{v_{out}}{v_N} = -g_{m4} \left[r_{\pi 1} \parallel r_{\pi 2} + (g_{m1} + g_{m2})(r_{\pi 1} \parallel r_{\pi 2})R_L \right] \left(\frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}} \right)$$

$$\frac{v_{out}}{v_{in}} = -g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L$$

Output Resistance Analysis

 - For the output resistance, we do need to consider the finite r_o of Q_3 & Q_4



$$R_{out} \approx \frac{1}{g_{m1} + g_{m2}} + \frac{r_{O3} \parallel r_{O4}}{(g_{m1} + g_{m2})(r_{\pi 1} \parallel r_{\pi 2})}$$

- If β is low, the second term of the output resistance will rise, which will be problematic when driving a small resistance.

Agenda

- General Output Stage Considerations
- Emitter Follower as a Power Amplifier
- Push-Pull Stage
- Improved Push-Pull Stage
- Large-Signal Considerations
- Heat Dissipation
- Efficiency and Power Amplifier Classes

Example: Biasing

Design Specs :

Common Emitter $A_v = 5$

Output Stage $A_v = 0.8$

with $R_L = 8\Omega$, $\beta_{npn} = 2\beta_{pnp} = 100$

and assume $I_{C1} \approx I_{C2}$


1. From the output stage gain and $I_{C1,2}$ conditions we can find $g_{m1,2}$ and $I_{C1,2}$

$$A_{v,OS} = \frac{v_{out}}{v_N} = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}} = 0.8$$


$$g_{m1} + g_{m2} = \frac{1}{2\Omega}$$

$$\text{with } I_{C1} = I_{C2} \Rightarrow g_{m1} = g_{m2} = \frac{1}{4}(\Omega^{-1}) = 250 \text{ mA/V}$$
 
$$\text{and } I_{C1} = I_{C2} = 6.5 \text{ mA}$$



Example: Biasing

 

2. From the Common Emitter gain condition we can find I_{C4}

$$A_{v,CE} = -g_{m4}R_N = -g_{m4} \left[r_{\pi 1} \parallel r_{\pi 2} + (g_{m1} + g_{m2})(r_{\pi 1} \parallel r_{\pi 2})R_L \right]$$


Using $r_{\pi 1} = 398\Omega$, $r_{\pi 2} = 199\Omega$, and $R_L = 8\Omega$

$$g_{m4} = 7.52 \text{ mA/V} \Rightarrow I_{C4} = 195 \mu\text{A}$$

However, this design procedure neglects any output swing specification!

 Problem of Base Current


Note, this assumes that I_{C3} is the same as I_{C4} , which may not exactly be the case due to the different $\beta_{1,2}$




- **195 μA of base current in Q_1 can only support 19.5 mA of collector current, insufficient for high current operation (hundreds of mA).**

Modification of the PNP Emitter Follower

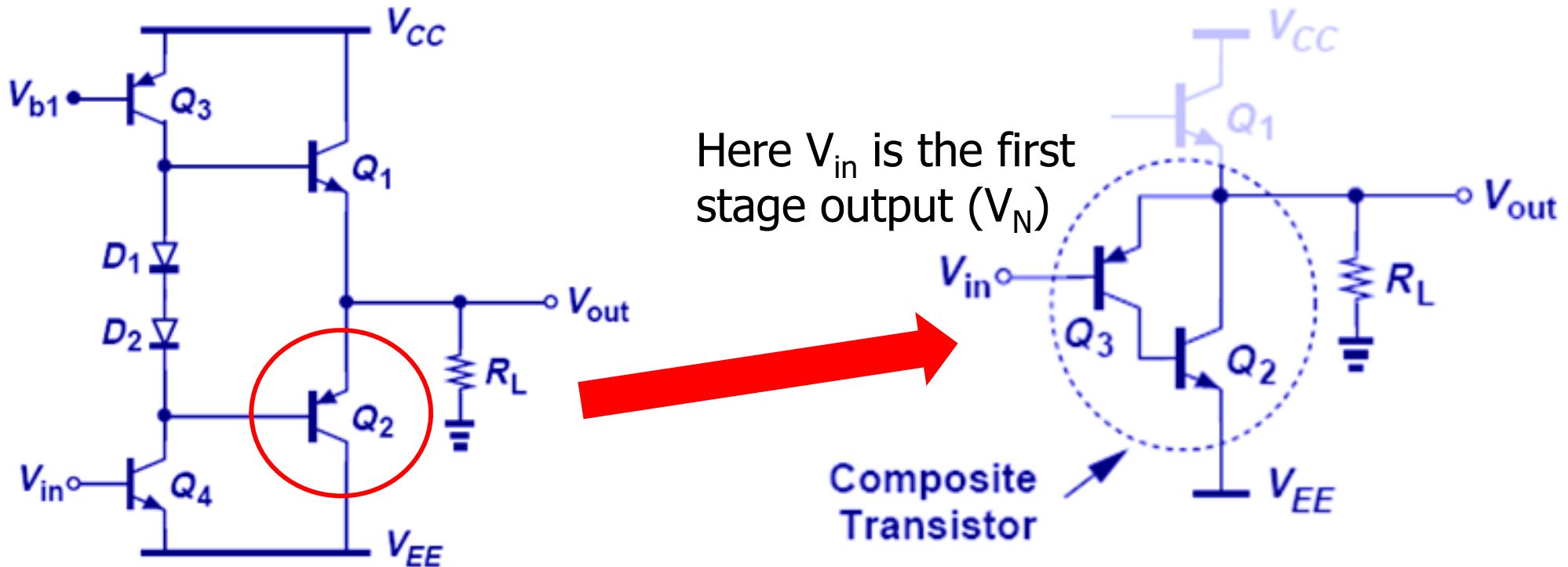
- Another output stage issue is that the Q_2 PNP transistor typically have low current gain (β) and low f_T
- Using a composite transistor consisting of an emitter follower PNP (Q_3) and a common emitter NPN (Q_2) allows for improved performance



 Modified PNP Emitter Follower Gain & Output Resistance



Small-Signal Model

 

Writing a KCL at the output node

$$\frac{v_{out} - v_{in}}{r_{\pi 3}} - g_{m3}(v_{in} - v_{out}) + g_{m2}(-g_{m3})(v_{in} - v_{out})r_{\pi 2} + \frac{v_{out}}{R_L} = 0$$

As the Q_3 collector current forms the Q_2 base current


$$g_{m2} = \beta_2 g_{m3}$$

$$\frac{v_{out}}{v_{in}} = \frac{R_L}{R_L + \frac{1}{(\beta_2 + 1)g_{m3} + \frac{1}{r_{\pi 3}}}}$$


$$R_{out} = \frac{1}{(\beta_2 + 1)g_{m3} + \frac{1}{r_{\pi 3}}} \approx \frac{1}{(\beta_2 + 1)g_{m3}}$$

Output resistance has been reduced by $\beta_2 + 1$ factor

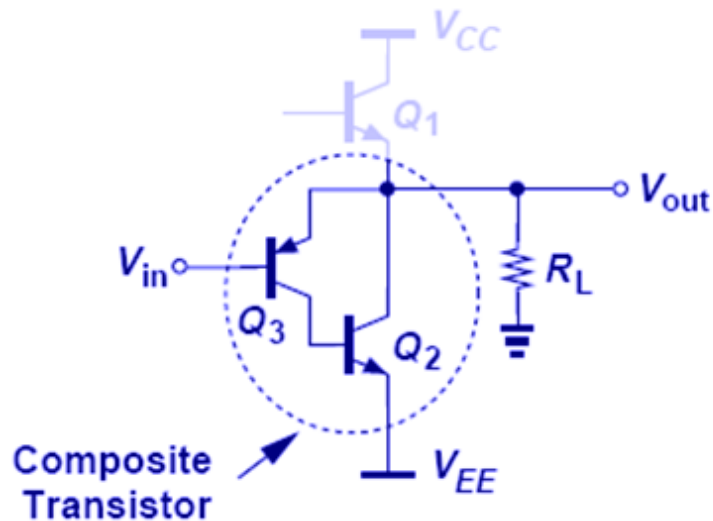Modified PNP Emitter Follower Input Resistance



Small-Signal Model

 


$$i_{in} = \frac{v_{in} - v_{out}}{r_{\pi 3}} = \frac{v_{in} - A_v v_{in}}{r_{\pi 3}}$$

$$R_{in} = \frac{v_{in}}{i_{in}} = \frac{r_{\pi 3}}{1 - A_v} = \frac{r_{\pi 3}}{1 - \frac{R_L}{R_L + \frac{1}{(\beta_2 + 1)g_{m3}}}}$$

$$R_{in} = r_{\pi 3} + \beta_3(\beta_2 + 1)R_L$$

Input resistance has been increased by $\sim(\beta_2 + 1)$ factor

Additional Bias Current

 


- Q_2 is often a large transistor to support the output current levels, resulting in large base capacitance
- I_1 is added to the base of Q_2 to provide an additional bias current to Q_3 so the capacitance at the base of Q_2 can be charged/discharged quickly

Example: Minimum V_{in}

- There is a minimum V_{in} for which the effective emitter follower transistors remain in active mode
- Here we conservatively assume for active mode we need a min. $V_{BC}=0V$


Simple PNP Emitter Follower

 

$$\text{Min } V_{in} \approx 0$$

$$V_{out} \approx |V_{EB2}|$$

Modified PNP Emitter Follower

 


$$\text{Min } V_{in} \approx V_{BE2}$$


$$V_{out} \approx |V_{EB3}| + V_{BE2}$$

- The modified PNP emitter follower has a reduced input range by V_{BE2}

HiFi Design

 
 
$$\frac{v_{out}}{v_{in}} = -g_{m4}(r_{\pi1} \parallel r_{\pi2})(g_{m1} + g_{m2})R_L$$




$$\frac{v_{out}}{v_{in}} \approx \frac{1}{K} = \frac{1}{\frac{R_2}{R_1 + R_2}} = 1 + \frac{R_1}{R_2}$$

- As g_{m1} and g_{m2} vary dramatically during large signal operation, the circuit displays nonlinear distortion

- Placing the output stage in a negative feedback loop allows for a more constant gain, and thus better linearity

Short-Circuit Protection

 - Excessive output stage current can result if the output is shorted to ground, damaging the circuit
- Q_s and r are used to “steal” some base current away from Q_1 when the output is accidentally shorted to ground, preventing short-circuit damage
- Drawbacks
 - r increases output resistance
 - Voltage drop across r reduces maximum output swing




Agenda

- General Output Stage Considerations
- Emitter Follower as a Power Amplifier
- Push-Pull Stage
- Improved Push-Pull Stage
- Large-Signal Considerations
- Heat Dissipation
- Efficiency and Power Amplifier Classes

Emitter Follower Power Rating

 The average power dissipated by Q_1 can be calculated by integrated the current - voltage product over a complete period and dividing by the period time.



$$P_{av} = \frac{1}{T} \int_0^T I_C V_{CE} dt$$

$$P_{av} = \frac{1}{T} \int_0^T \left(I_1 + \frac{V_P \sin \omega t}{R_L} \right) (V_{CC} - V_P \sin \omega t) dt$$

$$= \frac{1}{T} \int_0^T I_1 V_{CC} - I_1 V_P \sin \omega t + \frac{V_{CC} V_P \sin \omega t}{R_L} - \frac{V_P^2 \sin^2 \omega t}{R_L} dt$$

$$= \frac{1}{T} \int_0^T I_1 V_{CC} - \frac{V_P^2}{2R_L} (1 - \cos 2\omega t) dt$$

$$= I_1 V_{CC} - \frac{V_P^2}{2R_L} \xrightarrow{I_1 = \frac{V_P}{R_L}} I_1 \left(V_{CC} - \frac{V_P}{2} \right)$$


$$P_{av} = I_1 \left(V_{CC} - \frac{V_P}{2} \right)$$

$$P_{av, \max} = I_1 V_{CC}$$

➤ **Maximum power dissipated across Q_1 occurs in the *absence* of a signal.**

 Example: Current Source Power Dissipation

- The power dissipated by the I_1 current source is also important, as it will ultimately need to be realized at the transistor level also




$$P_{I_1} = \frac{1}{T} \int_0^T I_1 (V_{out} - V_{EE}) dt = \frac{1}{T} \int_0^T I_1 (V_P \sin \omega t - V_{EE}) dt$$

$$= \frac{1}{T} \int_0^T I_1 V_P \sin \omega t - I_1 V_{EE} dt$$

$$P_{I_1} = -I_1 V_{EE}$$


- Note that the I_1 power is positive, as V_{EE} is a negative supply

Push-Pull Stage Power Rating

 

- Assuming a symmetric design, the power ratings of Q_1 and Q_2 are the same and can be computed by integrating over a half-period.

Push-Pull Stage Power Rating

 

$$P_{av} = \frac{1}{T} \int_0^{T/2} V_{CE} I_C dt = \frac{1}{T} \int_0^{T/2} (V_{CC} - V_P \sin \omega t) \left(\frac{V_P}{R_L} \sin \omega t \right) dt$$

$$= \frac{1}{T} \int_0^{T/2} \frac{V_{CC} V_P}{R_L} \sin \omega t - \frac{V_P^2}{R_L} \sin^2 \omega t dt$$

$$= \frac{1}{T} \int_0^{T/2} \frac{V_{CC} V_P}{R_L} \sin \omega t dt - \frac{1}{T} \int_0^{T/2} \frac{V_P^2}{2R_L} (1 - \cancel{\cos 2\omega t}) dt$$



$$= \frac{V_{CC} V_P}{\pi R_L} - \frac{V_P^2}{4R_L}$$

$$P_{av} = \frac{V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)$$

Maximum power occurs with $V_P = \frac{2V_{CC}}{\pi}$

$$P_{av, \max} = \frac{V_{CC}^2}{\pi^2 R_L}$$

Example: Push-Pull P_{av}

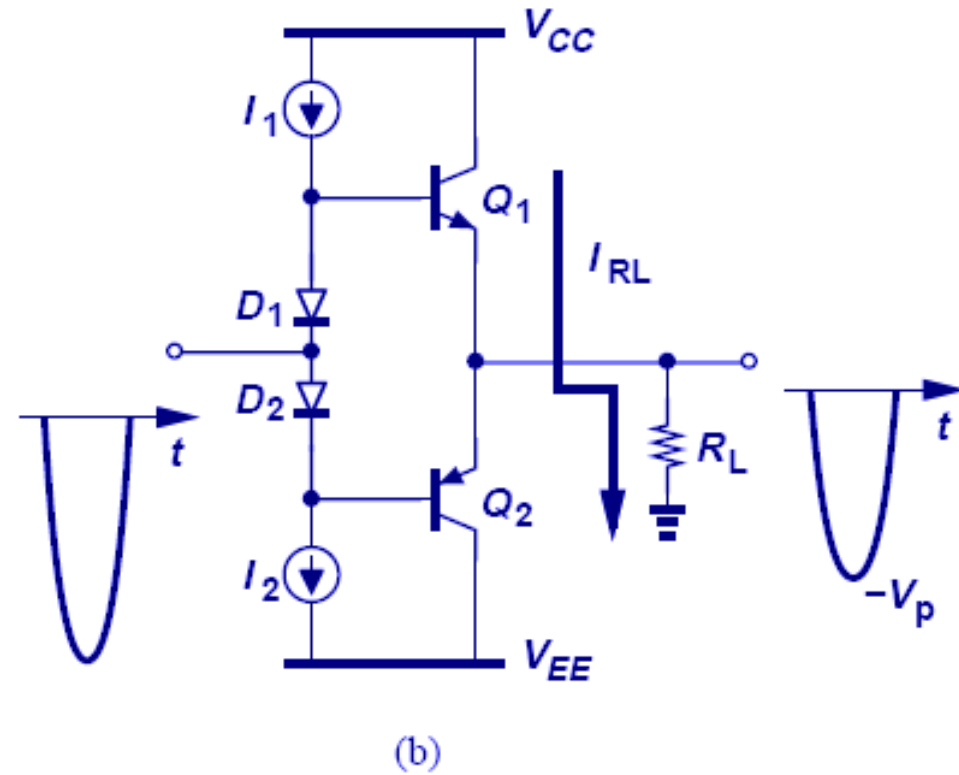 

$$P_{av} = \frac{V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)$$




$$\text{If } V_p = 4V_{CC}/\pi \rightarrow P_{av} = 0$$





Impossible since V_p cannot go above supply (V_{CC})

Heat Sink

 

- **Heat sink, provides large surface area to dissipate heat from the chip.**

Thermal Runaway

  

- For a constant I_C , V_{BE} has a **negative-to-absolute-temperature (NTAT)** coefficient of approximately $-2\text{mV}/^\circ\text{K}$
- Conversely, if the push-pull output stage is biased with a constant voltage, the current will increase with temperature
- This increased current results in more heat (higher temperature), and thus more current
- This positive feedback loop is called **thermal runaway** and can result in transistor damage

Thermal Runaway Mitigation

- Assuming that Q_3 and Q_4 have relatively constant bias currents with temperature (using good current mirror techniques), the diode voltages drop with temperature

Diode Voltages

$$V_{D1} + V_{D2} = V_T \ln \frac{I_{D1}}{I_{S,D1}} + V_T \ln \frac{I_{D2}}{I_{S,D2}} = V_T \ln \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}}$$


Transistor V_{BE} Voltages

$$V_{BE1} + V_{BE2} = V_T \ln \frac{I_{C1}}{I_{S,Q1}} + V_T \ln \frac{I_{C2}}{I_{S,Q2}} = V_T \ln \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}}$$

From a KVL, these voltage pairs are the same

$$V_T \ln \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} = V_T \ln \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}}$$
 
$$\frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} = \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}}$$



- Using diode biasing prevents thermal runaway since the currents in Q_1 and Q_2 will track those of D_1 and D_2 as long as their I_s 's track with temperature.

Agenda


- General Output Stage Considerations
- Emitter Follower as a Power Amplifier
- Push-Pull Stage
- Improved Push-Pull Stage
- Large-Signal Considerations
- Heat Dissipation
- Efficiency and Power Amplifier Classes

Power Amplifier Efficiency

- Power amplifier efficiency is critical because PAs draw a significant amount of power from the supply voltages
- Power amplifier efficiency is the ratio of the average power delivered to the load over the total power consumed from the supplies

$$\eta = \frac{\text{Power Delivered to Load}}{\text{Power Drawn from Supply}} = \frac{P_{out}}{P_{out} + P_{ckt}}$$

Emitter Follower Efficiency

 

The average power delivered to the load is

$$P_{out} = \frac{V_P^2}{2R_L}$$

The average power consumed by Q_1 is

$$P_{Q_1} = I_1 \left(V_{CC} - \frac{V_P}{2} \right)$$

The average power consumed by I_1 is

$$P_{I_1} = -I_1 V_{EE} = I_1 V_{CC} \quad \text{with } V_{EE} = -V_{CC}$$

Thus the total average circuit power is

$$P_{ckt} = I_1 \left(V_{CC} - \frac{V_P}{2} \right) + I_1 V_{CC} = I_1 \left(2V_{CC} - \frac{V_P}{2} \right)$$


The Emitter Follower Efficiency is $\eta_{EF} = \frac{\frac{V_P^2}{2R_L}}{\frac{V_P^2}{2R_L} + I_1 \left(2V_{CC} - \frac{V_P}{2} \right)}$

with $I_1 = \frac{V_P}{R_L} \Rightarrow \eta_{EF} = \frac{V_P}{4V_{CC}}$

- The emitter follower output stage only has a peak efficiency of 25% as V_P goes to V_{CC}
- Note, this can't actually be achieved, as we need some V_{CE} and voltage across I_1

Emitter Follower Efficiency Example

 - What if the emitter follower is designed to deliver V_p , but only operates with $V_p = V_{CC}/2$?



Now the average power delivered to the load is

$$P_{out} = \frac{\left(\frac{V_P}{2}\right)^2}{2R_L} = \frac{V_P^2}{8R_L}$$


The total average circuit power becomes

$$P_{ckt} = I_1 \left(2V_{CC} - \frac{V_P}{4} \right) = \frac{2V_P^2}{R_L} - \frac{V_P^2}{4R_L} \quad \text{with } I_1 = \frac{V_P}{R_L} \text{ and } V_{CC} = V_P$$

$$\eta_{EF} = \frac{\frac{V_P^2}{8R_L}}{\frac{V_P^2}{8R_L} + \frac{2V_P^2}{R_L} - \frac{V_P^2}{4R_L}} = \frac{1}{15}$$

- Now the efficiency drops to only 6.7%

Push-Pull Stage Efficiency

 

The average power delivered to the load is

$$P_{out} = \frac{V_P^2}{2R_L}$$

Both Q_1 and Q_2 consume an average power of

$$P_{Q_{1,2}} = \frac{V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)$$


The Push - Pull Stage Efficiency is $\eta_{PP} = \frac{\frac{V_P^2}{2R_L}}{\frac{V_P^2}{2R_L} + \frac{2V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)}$

$$\eta_{PP} = \frac{\pi V_P}{4V_{CC}}$$

- The push-pull output stage has a peak efficiency of 78.5% as V_P goes to V_{CC}
- Note, this can't actually be achieved, as we need some V_{CE} across both Q_1 and Q_2
- Also, we are excluding the input bias stage

Total Push-Pull Stage Efficiency

 - Assume that $I_1 = I_2$ and that they are chosen to allow a peak swing of V_P



In order to support a peak swing of V_P

$$I_1 = \frac{V_P}{\beta R_L}$$

The input bias stage power is

$$\frac{2V_{CC}V_P}{\beta R_L}$$


Thus the total push - pull stage efficiency is

$$\eta_{PP} = \frac{\frac{V_P^2}{2R_L}}{\frac{2V_P V_{CC}}{\pi R_L} + \frac{2V_{CC}V_P}{\beta R_L}}$$

$$\eta_{PP} = \frac{1}{4} \left(\frac{V_P}{\frac{V_{CC}}{\pi} + \frac{V_P}{\beta}} \right)$$

Class A Power Amplifiers


 
- Each transistor is on for the entire cycle
- Emitter follower is a Class A power amplifier



- Display high linearity, but low efficiency (25% maximum)

Class B Power Amplifiers

 
 
- Each transistor conducts for half the cycle
- Simple push-pull stage is a Class B power amp



- Display high efficiency, but low linearity
 - Bad crossover distortion

Class AB Power Amplifiers

  - Each transistor conducts for slightly more than a half-cycle
- Improved push-pull stage is a Class AB power amp



- Compromise between Class A and B
 - Good distortion at slightly degraded efficiency
- Many other PA classes exist (C, D, E, ...) and are often studied in grad-level RF circuit design classes

Thanks for the fun semester!!!