

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 474 – (Analog) VLSI Circuit Design

Fall 2012

Exam #1

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 4 pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		40
2		40
3		20
Total		100




Name: SAM PALERMO

UIN: _____


Problem 1 (40 points)

For the layout below, assume that all the commonly labeled diffusion areas are connected with the appropriate metal layers. Assume that $V_X=1.5V$, $V_Y=1V$, $V_Z=0.5V$, $V_{T0}=0.7V$, $\gamma=0$, and that all Spice parameters are given (i.e. C_j , C_{jsw} , C_{jc} , C_{ox} , C_{ov}). The dimensions are given in μm , with all the poly gates having a length of $2\mu m$ and $L_D=0.1\mu m$.

   - a) Draw the equivalent circuit. Combine all parallel transistors and given the total width and length of the equivalent transistors. (15 points)
- b) What region(s) are the transistors operating in? (5 points)
- c) For node X only, give an expression and calculate the total gate cap. (10 points)
- d) For node X only, give an expression and calculate the total junction cap. Note for the perimeter terms, include the sides underneath the gate. (10 points)



a. All unit transistors $\frac{10}{2}$

 

b. M1 $\Rightarrow V_{GS} = 1.5V - 1.0V = 0.5V$
 $V_{DS} = 1.5V - 1.0V = 0.5V$

$V_{GS} < V_T = 0.7V \Rightarrow$ Cutoff or Subthreshold

M2 $\Rightarrow V_{GS} = 1.5V - 0.5V = 1.0V$
 $V_{DS} = 1V - 0.5V = 0.5V$

$V_{GS} > V_T$ $\& \ V_{DS} > V_{GS} - V_T = 0.3V$
Saturation

c. For $C_{gx} \Rightarrow M1 = \text{Cutoff} \Rightarrow C_{gc} + C_{gsow}$ (Note C_{gd} is shorted out!!)
 $= (20\mu)(1.8\mu) \frac{C_{ox}C_{jc}}{C_{ox}+C_{jc}} + 20\mu(0.1\mu) = 36\mu^2 \frac{C_{ox}C_{jc}}{C_{ox}+C_{jc}} + 20\mu(0.1\mu)$

M2 = Sat. $\Rightarrow C_{gs} + C_{gd} = \frac{2}{3}(60\mu)(1.8\mu)C_{ox} + 60\mu(0.1\mu) + 60\mu(0.1\mu)$
 $= 72\mu^2(C_{ox} + 120\mu(0.1\mu))$


Total C_a
 $36\mu^2 \frac{C_{ox}C_{jc}}{C_{ox}+C_{jc}} + 72\mu^2(C_{ox} + 140\mu(0.1\mu))$

d. $C_{jx} \Rightarrow M1 = \text{Cutoff}$
 $C_{jx} = A_x C_j + P_x C_{jsw} = 6\mu(10\mu)C_j + (6\mu + 10\mu)2C_{jsw}$

$C_j = 1A \cdot 2 / \dots + 2 \dots$

 Problem 2 (40 points)

For the transistor below, assume $V_{T0}=0.7V$, $\gamma=0.45V^{1/2}$, and $2\Phi_F=0.9V$.



$$I_{DS} = I_0 \exp\left(\frac{(V_{GS} - V_{Tn})q}{\zeta kT}\right) \left(1 - \exp\left(-\frac{V_{DS}q}{kT}\right)\right) \quad (\text{Subthreshold})$$

$$I_{DS} = \mu_n C_{OX} \frac{W}{L - 2L_D} (V_{GS} - V_{Tn} - 0.5V_{DS}) V_{DS} \quad (\text{Triode})$$

$$I_{DS} = \frac{1}{2} \mu_n C_{OX} \frac{W}{L - 2L_D} (V_{GS} - V_{Tn})^2 (1 + \lambda V_{DS}) \quad (\text{Saturation})$$

$$V_{Tn} = V_{T0} + \gamma \left(\sqrt{|2\Phi_F| + V_{SB}} - \sqrt{|2\Phi_F|} \right)$$

$V_{SB} = 0.6V$

a. Calculate V_T and state the transistor's operation region. (10 points)

$$V_T = 0.7V + 0.45V^{1/2} \left(\sqrt{0.9V + 0.6V} - \sqrt{0.9V} \right) = 0.824V$$

$V_{GS} = 1.4V - 0.6V = 0.8V$

$V_T = 0.824V$

$V_{GS} < V_T \Rightarrow \text{Subthreshold}$

Operation Region = Subthreshold


b. Using the appropriate I_{DS} equation above, derive and sketch the small-signal model of the transistor. Include expressions for the g_m , g_o , and g_{mb} . (30 points)

$$g_m = \frac{\partial I_{DS}}{\partial V_{GS}} \bigg|_Q = \frac{I_0 q}{kT} \exp\left(\frac{(V_{GS} - V_T)q}{kT}\right) \left(1 - \exp\left(-\frac{V_{DS}q}{kT}\right)\right)$$

$$g_o = \frac{\partial I_{DS}}{\partial V_{DS}} \bigg|_Q = \frac{I_0 q}{kT} \exp\left(\frac{(V_{GS} - V_T)q}{kT}\right) \left(\exp\left(-\frac{V_{DS}q}{kT}\right)\right)$$

$$g_{mb} = \frac{\partial I_{DS}}{\partial V_{BS}} \bigg|_Q = \frac{I_0 q}{kT} (-1) \exp\left(\frac{(V_{GS} - V_T)q}{kT}\right) \left(1 - \exp\left(-\frac{V_{DS}q}{kT}\right)\right) (-1) \left(\frac{\gamma}{2\sqrt{|2\Phi_F| + V_{SB}}}\right)$$

$$= \frac{\gamma g_m}{2\sqrt{|2\Phi_F| + V_{SB}}}$$

 

Problem 3 (20 points)

Sketch a layout that matches two capacitors of unit size 7.5 and 3.3. Assume that the unit capacitors are sized $10\mu\text{m} \times 10\mu\text{m}$. **Make sure to give the non-unit capacitor(s) dimensions.** In the sketch clearly label the critical dimensions and use at least 2 layout matching techniques. **Also, write specifically the 2 layout matching techniques that you are using.** Note, if you use a common-centroid layout technique, it doesn't have to have perfect center-of-mass matching, but it should be close.

Need to match $\frac{\text{Perimeter}}{\text{Area}}$ for all caps

"C1" For 7.5 cap \Rightarrow 6 unit caps + 1 non-unit cap
 $w/A_{nu} = 1.5 A_u \quad (k_1 = 1.5)$


"C2" For 3.3 cap \Rightarrow 2 unit caps + 1 non-unit cap
 $w/A_{nu} = 1.3 A_u \quad (k_2 = 1.3)$

C1: $x_{nu1} = x_u (k_1 - \sqrt{k_1^2 - 1})$
 $= 10\mu(1.5 - \sqrt{1.5^2 - 1}) = 6.34\mu$

$x_{nu1} = \frac{k_1 x_u^2}{y_{nu1}} = \frac{1.5(10\mu)^2}{6.34\mu}$
 $= 23.7\mu$

C2: $y_{nu2} = 10\mu(1.3 - \sqrt{1.3^2 - 1}) = 6.76\mu$

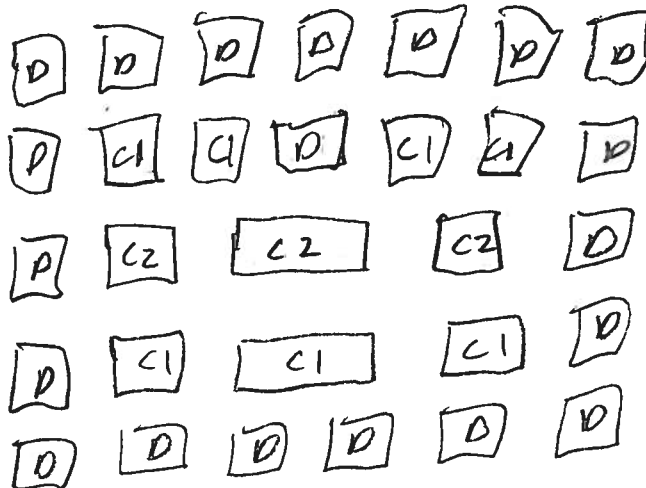$x_{nu2} = \frac{1.3(10\mu)^2}{6.76\mu}$
 $= 19.2\mu$



C1 Non-Unit

$6.34 \times 23.7\mu$

C2 Non-Unit

$6.76 \times 19.2\mu$

Layout Technique #1 = Dummies around entire perimeter

Layout Technique #2 = Common-Centroid (Approximately)