

**Texas A&M University
Department of Electrical and Computer Engineering**

ECEN 474/704 – (Analog) VLSI Circuit Design

Fall 2016

Exam #2

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 5 pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		30
2		30
3		40
Total		100


Name: SAM PALERMO

UIN: _____

Problem 1 (30 points)

For the following current source obtain the following:

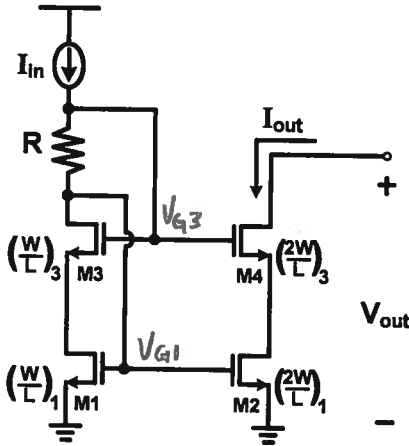- a) Give an expression for the output resistance. You can assume that all transistors are operating in saturation and that you can neglect body effect.
- b) Give an expression for the ^{minimum} compliance voltage at the output necessary to keep all transistors in saturation.
- c) Give an expression for the minimum resistor R value required to keep all the transistors in saturation for this minimum compliance voltage. Express this minimum R value as a function of I_{in} and the relevant transistor aspect ratio (W/L) values.



a. $r_o = r_{o2} + r_{o4} + g_{m4} r_{o4} r_{o2}$
 $\approx g_{m4} r_{o4} r_{o2}$

b. Minimum Compliance Voltage

$$V_{out} \geq V_{DSAT2} + V_{DSAT4}$$

c. ① $V_{G3} - V_{G1} = I_{in} R$

② Minimum $V_{G3} = V_{DSAT1} + V_{G33} = V_{DSAT1} + V_{DSAT3} + V_T$

Plugging ② into ①

Min $V_{G3} - V_{G1} = V_{DSAT1} + V_{DSAT3} + V_T - (V_{DSAT1} + V_T) = I_{in} R$

$V_{DSAT3} = I_{in} R$


$\sqrt{\frac{2I_{in}}{\mu_{ox}(\frac{W}{L})_3}} = I_{in} R$

$$R = \sqrt{\frac{2}{I_{in} \mu_{ox} (\frac{W}{L})_3}}$$

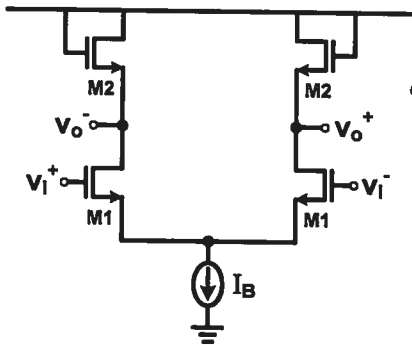Problem 2 (30 points)

For the fully differential amplifier below obtain the following:

- Give an expression for the differential gain, $A_{vd} = (v_{o^+} - v_{o^-}) / (v_{i^+} - v_{i^-})$. Do NOT neglect the transistors' r_o . Assume all transistors are operating in saturation and that you can neglect body effect.
- Give an expression for the dominant pole of the amplifier. This expression should include all the appropriate transistor capacitances and include the Miller effect when appropriate.



a.
$$A_{vd} = \frac{g_{m1}}{g_{o1} + g_{o2} + g_{m2}}$$

b.
$$\omega_p = \frac{g_{o1} + g_{o2} + g_{m2}}{C_{DB1} + C_{L01} + C_{SB2} + C_{GS2}}$$

Note neglecting Miller in C_{L01} because $1 - A_{vdc} = 1 - \left(-\frac{1}{A_{vd}} \right)$
 this is generally very small

- Now simplify the differential gain expression by letting the transistors' $r_o = \infty$. Assume that the transistors have the following transistor sizes:

M1 Size = W/L

M2 Size = $\alpha \cdot W/L$

What should α be to achieve a differential gain of 2?

$$A_{vd} = \frac{g_{m1}}{g_{m2}} = \frac{\sqrt{\mu_n \left(\alpha \frac{W}{L} \right) 2(I_B/2)}}{\sqrt{\mu_n \left(\alpha \frac{W}{L} \right) 2(I_B/2)}}$$


$$A_{vd} = \frac{1}{\sqrt{\alpha}} = 2$$

$$\alpha = \frac{1}{4}$$

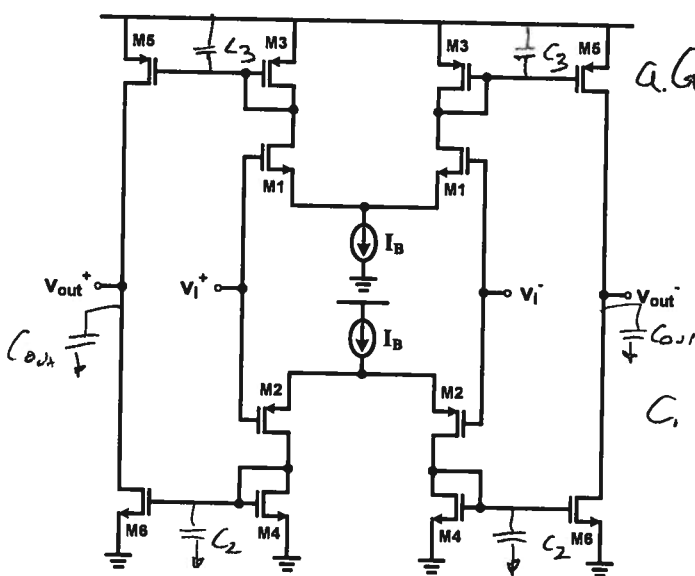Problem 3 (40 points)

For the amplifier below, assume all transistors are operating in saturation and that you can neglect body effect. Obtain expressions for the following:

- Small-signal transconductance.
- Output resistance.
- DC gain.
- The amplifier's three poles. Note, it's OK here to state this as a function of an effective capacitance at a certain node, but make sure to appropriately label the nodes.
- Output referred noise current power spectral density. Consider only thermal noise and include all important noise sources.
- Input referred noise voltage power spectral density. Consider only thermal noise and include all important noise sources.



$$a. G_m = \frac{g_{m1} g_{m5}}{g_{o1} + g_{o3} + g_{m3}} + \frac{g_{m2} g_{m6}}{g_{o2} + g_{o4} + g_{m4}}$$

$$b. R_{out} = \frac{1}{g_{o5} + g_{o6}}$$

$$c. A_v = G_m R_{out} = \frac{g_{m1} g_{m5}}{g_{o1} + g_{o3} + g_{m3}} + \frac{g_{m2} g_{m6}}{g_{o2} + g_{o4} + g_{m4}} \cdot \frac{1}{g_{o5} + g_{o6}}$$

$$d. \omega_{p1} = \frac{g_{o5} + g_{o6}}{C_{out}}, \omega_{p2} = \frac{g_{m4} + g_{o4} + g_{o2}}{C_2}, \omega_{p3} = \frac{g_{m3} + g_{o3} + g_{o1}}{C_3}$$

$$e. \frac{i_{o,n}^2}{\Delta f} = (i_{o1}^2 + i_{o3}^2 + i_{o5}^2 + i_{o2}^2 + i_{o4}^2 + i_{o6}^2) \cdot \left(\frac{1}{g_{o1} + g_{o3} + g_{m3}} \right)^2 \cdot g_{m5}^2 + g_{m5} + (g_{m2} + g_{m4}) \left(\frac{1}{g_{o2} + g_{o4} + g_{m4}} \right)^2 \cdot g_{m6}^2 + g_{m6}$$

$$f. \frac{v_{i,n}^2}{\Delta f} = \frac{i_{o,n}^2}{\Delta f} \left(\frac{1}{G_m} \right)^2$$

Scratch Paper