

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 474/704 – (Analog) VLSI Circuit Design

Spring 2018

Exam #3

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 6 pages (1 blank) in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		35
2		35
3		30
Total		100

Name: _____


SAM PALERMO

UIN: _____

Problem 1 (35 points)

For the fully-differential amplifier below, assume all transistors are operating in saturation and obtain expressions for the following:

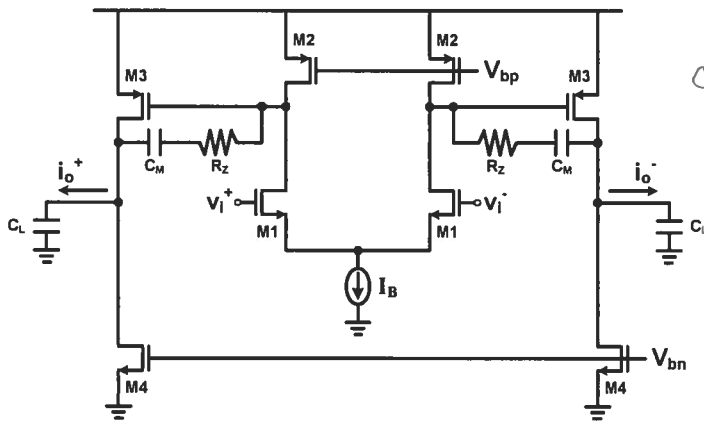- a) Small-signal differential transconductance, $(i_o^+ - i_o^-)/(v_i^+ - v_i^-)$.
- b) Fully differential amplifier DC gain, $A_{vd} = (v_o^+ - v_o^-)/(v_i^+ - v_i^-)$.
- c) The amplifier's two main poles. Note, it's OK to neglect the transistor capacitors here.
- d) Assuming that the dominant pole is at the first stage output, what is the value of R_z that cancels the second pole?



$$c. G_m = \frac{i_o^+}{v_i^+} = \left(\frac{-g_{m1}}{g_{o1} + g_{o2}} \right) (-g_{m3})$$

$$G_m = \frac{g_{m1} g_{m3}}{g_{o1} + g_{o2}}$$

$$b. R_{out} = \frac{1}{g_{o3} + g_{o4}} \Rightarrow A_v = G_m R_{out} = \frac{g_{m1} g_{m3}}{(g_{o1} + g_{o2})(g_{o3} + g_{o4})}$$

$$c. \omega_{p1} \approx - \frac{(g_{o1} + g_{o2})(g_{o3} + g_{o4})}{C_m g_{m3}} \quad \omega_{p2} \approx - \frac{g_{m3}}{C_L}$$

$$d. \omega_{p2} \approx - \frac{g_{m3}}{C_L} \quad \omega_z = \frac{1}{\left(\frac{1}{g_{m3}} - R_z\right) C_m}$$


$$\frac{1}{\left(\frac{1}{g_{m3}} - R_z\right) C_m} = - \frac{g_{m3}}{C_L}$$

$$\left(\frac{1}{g_{m3}} - R_z\right) C_m = - \frac{C_L}{g_{m3}}$$

$$R_z = \frac{1}{g_{m3}} \left(1 + \frac{C_L}{C_m}\right)$$

Problem 2 (35 points)

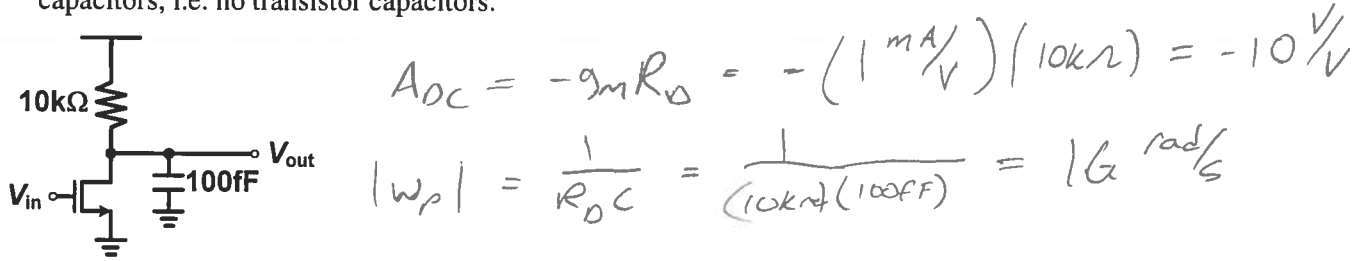- a. Give the transfer function (w/ numbers) of the single-stage amplifier shown below. Assume the transistor operates in saturation with $g_m=1\text{mA/V}$ and $\lambda=0$. Only consider the explicitly drawn capacitors, i.e. no transistor capacitors.




$$A_{DC} = -g_m R_D = -(1 \text{ mA/V})(10 \text{ k}\Omega) = -10 \text{ V/V}$$

$$|\omega_p| = \frac{1}{R_D C} = \frac{1}{(10 \text{ k}\Omega)(100 \text{ fF})} = 1 \text{ G rad/s}$$

$$H_1(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{-10}{1 + \frac{s}{10^9}}$$

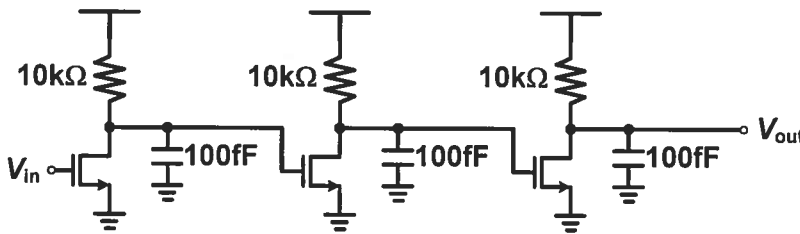- b. Now this single-stage amplifier is used in a 3-stage amplifier. Again, assume all transistors operate in saturation with $g_m=1\text{mA/V}$ and $\lambda=0$ and only consider the explicitly drawn capacitors, i.e. no transistor capacitors. Give the 3-stage amplifier transfer function and the frequency at which the amplifier's phase drops from the low-frequency phase value by -180° (ω_{px}).



$$\tan^{-1}\left(\frac{\omega_{px}}{10^9}\right) = 60^\circ$$

$$H(s) = (H_1(s))^3 = \frac{-10^3}{\left(1 + \frac{s}{10^9}\right)^3}$$


$$\omega_{px} = 1.73 \text{ G rad/s}$$

$$\angle H(j\omega) = -3 \tan^{-1}\left(\frac{\omega_{px}}{10^9}\right) = -180^\circ$$

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{-10^3}{\left(1 + \frac{s}{10^9}\right)^3}$$

$$\omega_{px} = 1.73 \text{ G rad/s}$$

c. Now this 3-stage amplifier is placed in feedback with $K=0.1$. Give the frequency at which the feedback system $|KH(s)|=1$ (ω_{GX}). Is the system stable?

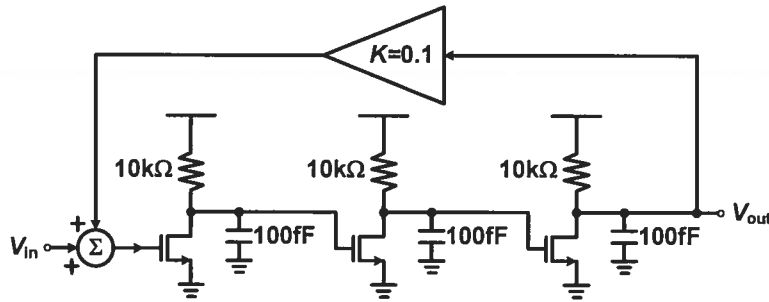

$$|KH(s)| = 1$$

$$\frac{(0.1)(10^3)}{\left(1 + \frac{\omega_{GX}^2}{10^{18}}\right)^3} = 1$$

$$\left(1 + \frac{\omega_{GX}^2}{10^{18}}\right)^{\frac{3}{2}} = 10^2$$


$$1 + \frac{\omega_{GX}^2}{10^{18}} = 21.5$$

$$\omega_{GX} = 4.53 \text{ Grad/s}$$

$\omega_{GX} = 4.53 \text{ Grad/s}$

System Stable? (Yes or No) *No* ($\omega_{GX} > \omega_{PX}$)

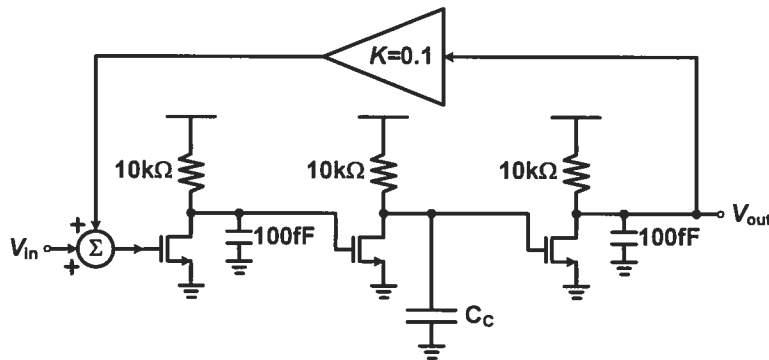d. Now only the second stage is modified with a large compensation capacitor C_c to establish a single dominant pole system. Assume that this dominant pole contributes -90° at the new ω_{GX} . Considering the other poles in the system, what is the capacitor value necessary for the feedback system (KH) to have a phase margin of 45° ?



For $PM = 45^\circ$

$$\angle KH(j\omega_{GXnew}) = -135^\circ$$

w/ one dominant pole $\angle KH(j\omega_{GXnew}) = -90^\circ - 2 \tan^{-1}\left(\frac{\omega_{GXnew}}{10^9}\right) = -135^\circ$

To place ω_{GXnew} at 414 Mrad/s

$$\omega_{p1}' = \frac{\omega_{GXnew}}{|KH|} = \frac{414 \text{ Mrad/s}}{10^2}$$

$C_c (PM=45^\circ) = 24.1 \text{ pF}$

$$\tan^{-1}\left(\frac{\omega_{GXnew}}{10^9}\right) = 22.5^\circ$$

$$\omega_{GXnew} = 414 \text{ Mrad/s}$$


$= 4.14 \text{ Mrad/s}$

4 $\omega_{p1}' = \frac{1}{R_D C_c} \Rightarrow C_c = \frac{1}{(10k\Omega)(4.14 \text{ Mrad/s})} = 24.1 \text{ pF}$

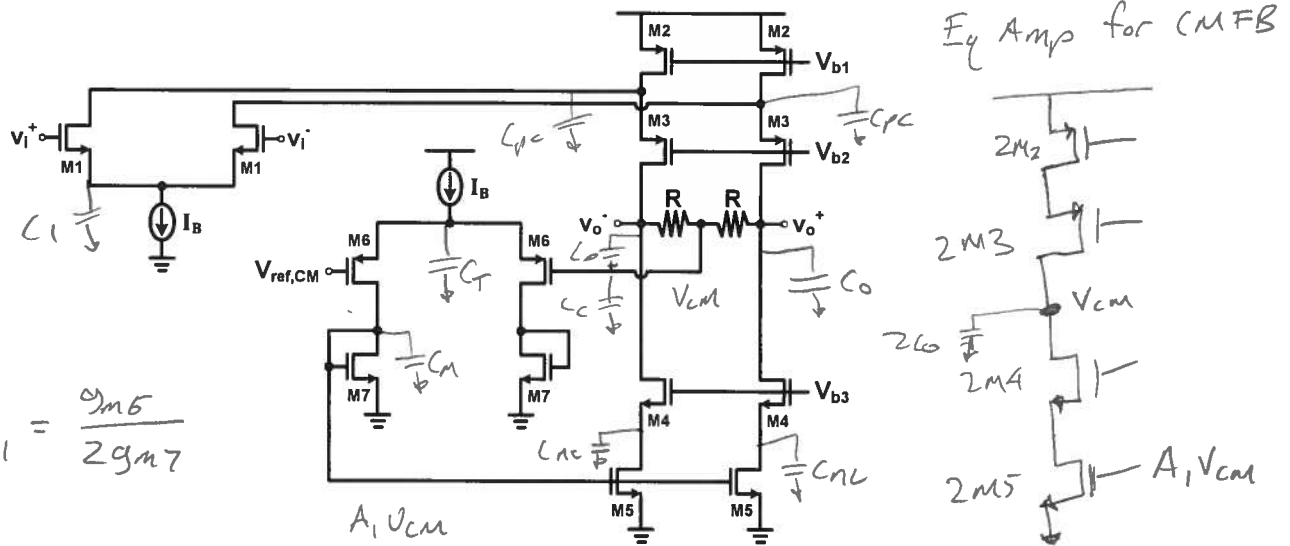Problem 3 (30 points)

For the fully differential amplifier with common-mode feedback (CMFB) below, assume all transistors are operating in saturation, and obtain the following:

- Neglecting the CMFB network, give an expression for the fully differential amplifier DC gain, $A_{vd} = (v_{o+} - v_{o-}) / (v_{i+} - v_{i-})$.
- Give an expression for the CMFB loop DC gain.
- Give expressions for the poles of the CMFB loop. Note, it's OK here to state this as a function of an effective capacitance at a certain node, but make sure to appropriately label the nodes.



$$A_1 = \frac{g_{m6}}{2g_{m7}}$$

$$a. A_{vd} \approx g_{m1} \left[g_{m3} r_{o3} (r_{o2} || r_{o1}) || g_{m4} r_{o4} r_{o5} \right]$$

$$b. \text{CMFB Loop Gain} = \left(\frac{g_{m6}}{2g_{m7}} \right) (-2g_{m5}) \left[2g_{m3} \frac{r_{o3}}{2} \frac{r_{o2}}{2} || 2g_{m4} \frac{r_{o4}}{2} \frac{r_{o5}}{2} \right]$$

$$= - \frac{g_{m6} g_{m5}}{2g_{m7}} \left[g_{m3} r_{o3} r_{o2} || g_{m4} r_{o4} r_{o5} \right]$$

$$c. \text{Poles at } \frac{1}{(g_{m3} r_{o3} r_{o2} || g_{m4} r_{o4} r_{o5}) C_c}$$

$$\frac{2}{RC_c}, \frac{2g_{m5}}{C_T}, \frac{g_{m7}}{C_M}, \frac{g_{m4}}{C_{nc}}, \frac{g_{m3}}{C_{pc}}, \frac{2g_{m1}}{C_1}$$

Scratch Paper
