

**Texas A&M University  
Department of Electrical and Computer Engineering**

**ECEN 474/704 – (Analog) VLSI Circuit Design**

**Spring 2016**

**Exam #3**

**Instructor: Sam Palermo**

- Please write your name in the space provided below
- Please verify that there are 5 pages (1 blank) in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		35
2		35
3		30
<b>Total</b>		<b>100</b>


Name: SAM PALERMO

UIN: \_\_\_\_\_
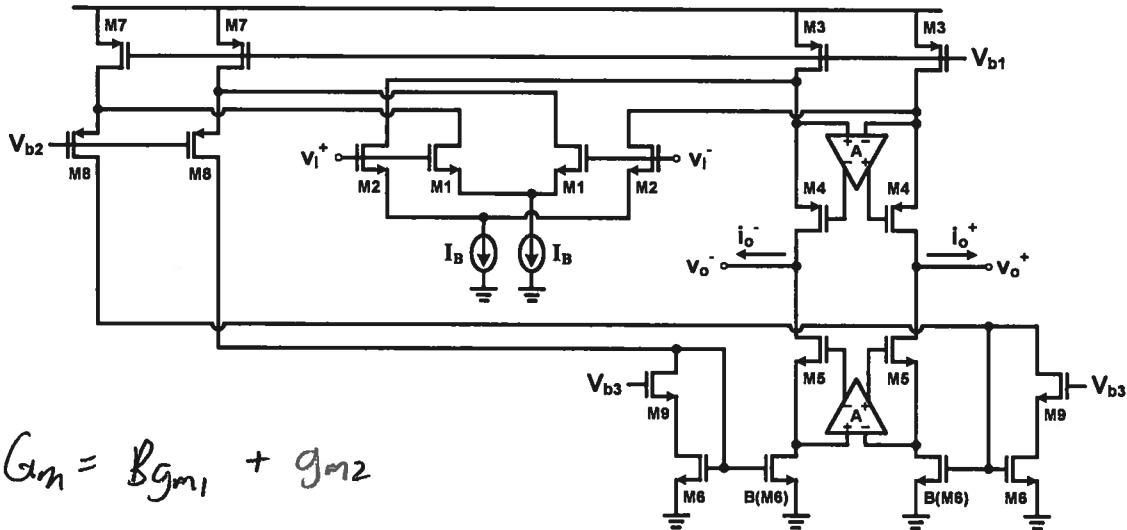
## Problem 1 (35 points)

For the fully-differential amplifier below, assume all transistors are operating in saturation, the internal amplifier blocks have finite gain  $A$  and infinite bandwidth. Note that the bottom-most nMOS transistors have a 1:B size ratio. Obtain expressions for the following:

- Small-signal differential transconductance,  $(i_o^+ - i_o^-)/(v_i^+ - v_i^-)$ .
- Output resistance.
- Fully differential amplifier DC gain,  $A_{vd} = (v_o^+ - v_o^-)/(v_i^+ - v_i^-)$ .
- Output referred noise current power spectral density. Consider only thermal noise and include all important noise sources.
- Input referred noise voltage power spectral density. Consider only thermal noise and include all important noise sources.



$$a. G_m = B g_{m1} + g_{m2}$$

$$b. R_{out} = \left[ r_{o5} g_{m5} (1+A) \frac{r_{o6}}{B} \parallel r_{o4} g_{m4} (1+A) (r_{o3} \parallel r_{o2}) \right]$$

$$c. A_v = G_m R_{out} = \left[ B g_{m1} + g_{m2} \right] \left[ r_{o5} g_{m5} (1+A) \frac{r_{o6}}{B} \parallel r_{o4} g_{m4} (1+A) (r_{o3} \parallel r_{o2}) \right]$$

$$d. \frac{i_{o,n}^2}{\Delta f} = (i_{o1}^2 + i_{o2}^2 + i_{o3}^2 + i_{o6}^2 + i_{o6MS}^2 + i_{o7}^2)^2$$

$$= \frac{16}{3} kT \left[ B^2 g_{m1} + g_{m2} + g_{m3} + B^2 g_{m6} + B g_{m6} + B^2 g_{m7} \right]$$

$$e. \frac{V_{i,n}^2}{\Delta f} = \frac{i_{o,n}^2}{\Delta f} \left( \frac{1}{G_m} \right)^2$$


## Problem 2 (35 points)

For the circuit shown below, assume that all transistors are operating in the saturation region except for M9. You can assume that the DC operating point for node B is the same as node A. Calculate the following using these transistor parameters.

$$K_P = \mu_n C_{ox} = 200 \mu A/V^2, V_{TH,N} = 0.4V, \lambda_N = 0.1V^{-1}$$

$$K_P = \mu_p C_{ox} = 100 \mu A/V^2, V_{TH,P} = -0.4V, \lambda_P = 0.1V^{-1}$$

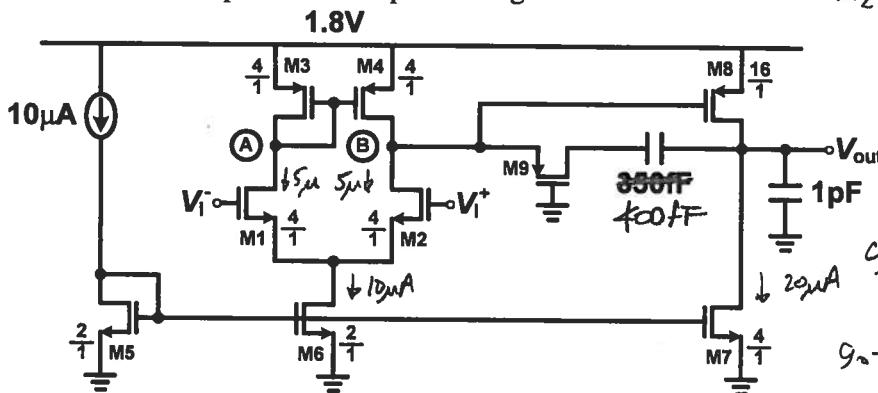- Low-frequency gain ( $A_{DC} = V_{out}/(V_i^+ - V_i^-)$ )
- Dominant pole ( $\omega_{p1}$ )
- Second pole ( $\omega_{p2}$ )
- Unity-gain frequency ( $\omega_{GX}$ )
- Give the M9 aspect ratio 60° phase margin



$$A_{DC} = \left( \frac{-g_{m2}}{g_{o2} + g_{o4}} \right) \left( \frac{-g_{m8}}{g_{o7} + g_{o8}} \right)$$

$$g_{m2} = \sqrt{(200\mu)(\frac{4}{1})(2)(5\mu)} = 89.4 \mu A/V$$

$$g_{o2} = g_{o4} = \lambda I_o = (0.1V^{-1})(5\mu A) = 0.5 \mu A/V$$

$$g_{m8} = \sqrt{(100\mu)(\frac{16}{1})(2)(20\mu)} = 253 \mu A$$

$$g_{o7} = g_{o8} = \lambda I_o = (0.1V^{-1})(20\mu A) = 2 \mu A$$

$$\text{Node } A = B = 1.8 - 0.4 - \sqrt{\frac{2(5\mu)}{100\mu(\frac{4}{1})}} = 1.24V$$

$$A_{DC} = \left( \frac{89.4 \mu}{0.5 \mu + 0.5 \mu} \right) \left( \frac{253 \mu}{2 \mu + 2 \mu} \right) = 5.65 \times 10^3 V/V$$

$$\omega_{p1} = - \frac{(g_{o2} + g_{o4})(g_{o7} + g_{o8})}{g_{m2} C_L} = - \frac{(0.5 \mu + 0.5 \mu)(2 \mu + 2 \mu)}{(253 \mu)(400f)} = - 39.5 \text{ rad/s} = - 6.29 \text{ kHz}$$

$$\omega_{p2} = - \frac{g_{m8}}{C_L} = - \frac{253 \mu}{1 \mu} = - 253 \text{ rad/s} = - 40.3 \text{ MHz}$$

$$\omega_{GX} = A_{DC} \cdot \omega_{p1} = (5.65 \times 10^3)(39.5 \text{ rad/s}) = 223 \text{ rad/s} = 35.5 \text{ MHz}$$

$$PM = 180^\circ - \tan^{-1}\left(\frac{\omega_{GX}}{\omega_{p1}}\right) - \tan^{-1}\left(\frac{\omega_{GX}}{\omega_{p2}}\right) - \tan^{-1}\left(\frac{\omega_{GX}}{\omega_Z}\right)$$

$$A_{DC} = 5.65 \times 10^3$$

$$\omega_{p1} = -39.5 \text{ rad/s}$$

$$\omega_{p2} = -253 \text{ rad/s}$$

$$\omega_{GX} = 223 \text{ rad/s}$$

$$60^\circ = 180^\circ - \tan^{-1}\left(\frac{223 \text{ rad/s}}{39.5 \text{ rad/s}}\right) - \tan^{-1}\left(\frac{223 \text{ rad/s}}{253 \text{ rad/s}}\right) - \tan^{-1}\left(\frac{223 \text{ rad/s}}{\omega_Z}\right)$$

$$60^\circ = 180^\circ - 90^\circ - 41.4^\circ - \tan^{-1}\left(\frac{223 \text{ rad/s}}{\omega_Z}\right)$$

$$(W/L)_9 \text{ for } PM=60^\circ = 1.92$$

$$11.4^\circ = -\tan^{-1}\left(\frac{223 \text{ rad/s}}{\omega_Z}\right)$$

$$\omega_Z = \frac{1}{(g_{m8} - R_2)C_L} \quad \frac{W}{L} = \frac{1}{(100\mu)(6.2k)(1.24 - 0A)}$$


$$\omega_Z = - \frac{223 \text{ rad/s}}{\tan(11.4^\circ)} = - 1.11 \text{ rad/s}$$

$$R_2 = \frac{1}{g_{m8}} - \frac{1}{\omega_Z C_L} = 6.2k$$
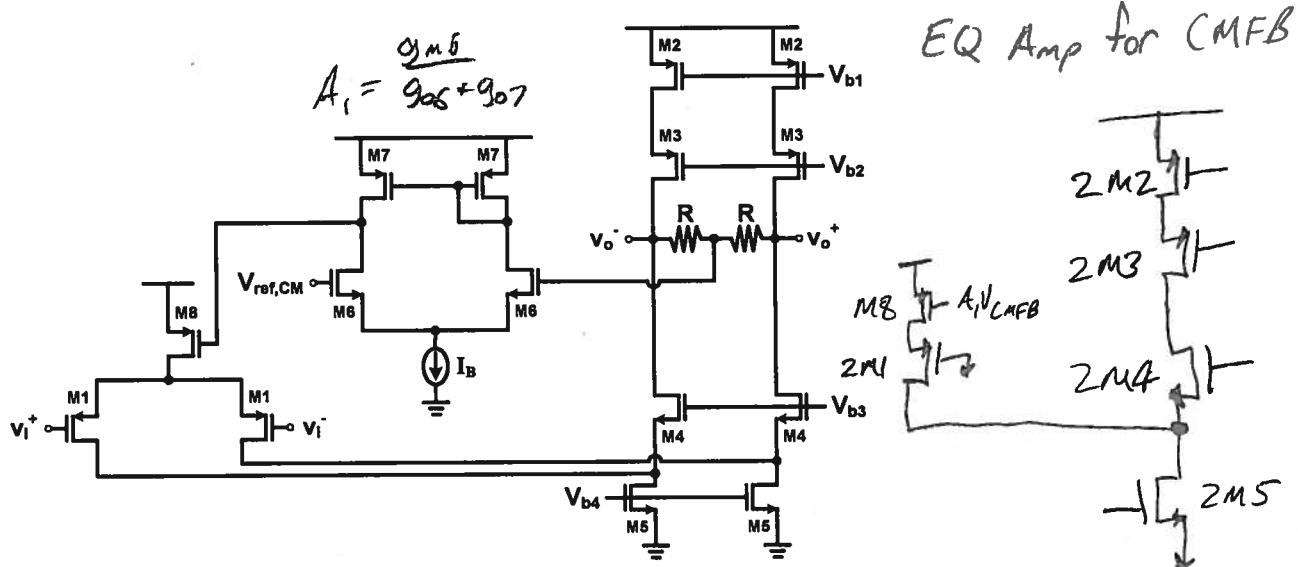
## Problem 3 (30 points)

For the fully differential amplifier with common-mode feedback (CMFB) below, assume all transistors are operating in saturation, and obtain the following:

- Neglecting the CMFB network, give an expression for the fully differential amplifier DC gain,  $A_{vd} = (v_o^+ - v_o^-)/(v_i^+ - v_i^-)$ .
- Give an expression for the CMFB loop DC gain.



$$a. A_{vd} = g_{m1} \left[ g_{m4} r_{o4} (r_{o5} || r_{o1}) || g_{m3} r_{o3} r_{o2} \right]$$

$$b. CMFB\ Loop\ Gain = \left( \frac{g_{m6}}{g_{o6} + g_{o7}} \right) \left( -g_{m8} \right) \left[ \left( 2g_{m4} \right) \left( \frac{r_{o4}}{2} \right) \left[ \frac{r_{o5}}{2} \parallel \left( 2g_{m1} \right) \left( \frac{r_{o1}}{2} \right) r_{o3} \right] \right] \parallel \\ \left[ \left( 2g_{m3} \right) \left( \frac{r_{o3}}{2} \right) \left( \frac{r_{o2}}{2} \right) \right]$$

$$\approx \left( -\frac{g_{m6} g_{m8}}{g_{o6} + g_{o7}} \right) \left( \frac{g_{m4} r_{o4} r_{o5}}{2} \parallel \frac{g_{m3} r_{o3} r_{o2}}{2} \right)$$

**Scratch Paper**