

ECEN474/704: (Analog) VLSI Circuit Design Spring 2018

Lecture 8: Frequency Response



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University



Announcements & Agenda

- HW2 Due Mar 6
- Reading
 - Razavi Chapters 3 & 6

Announcements & Agenda


- Common-Source Amp Frequency Response
- Open-Circuit Time Constants ($OC\tau$)
Bandwidth Estimation Technique
- Common-Drain Amp Frequency Response
- Common-Gate Amp Frequency Response
- Cascode Amp Frequency Response

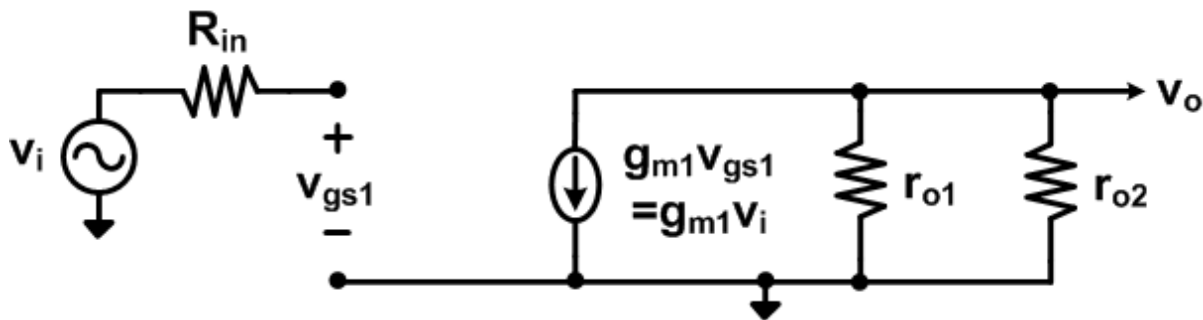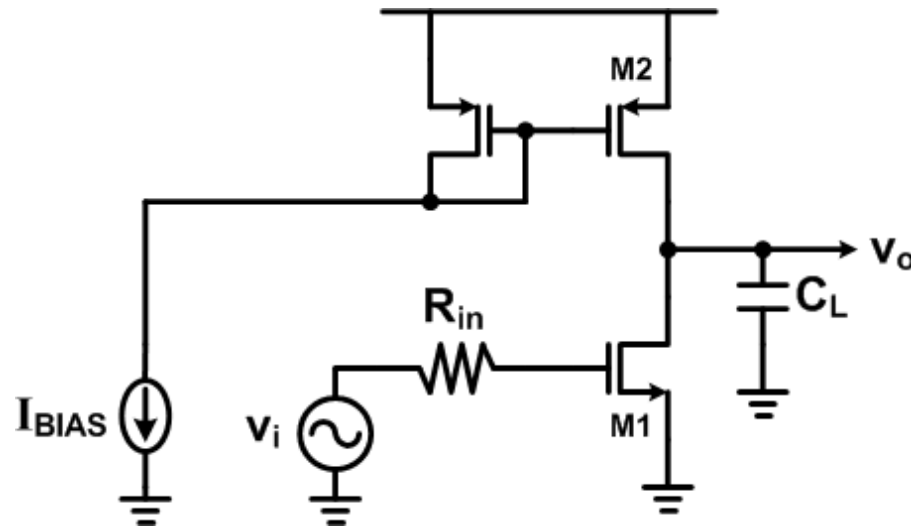Common-Source Amplifier: Low Frequency Response



$$\frac{v_o}{v_i} = - \frac{g_{m1}}{g_{o1} + g_{o2}}$$

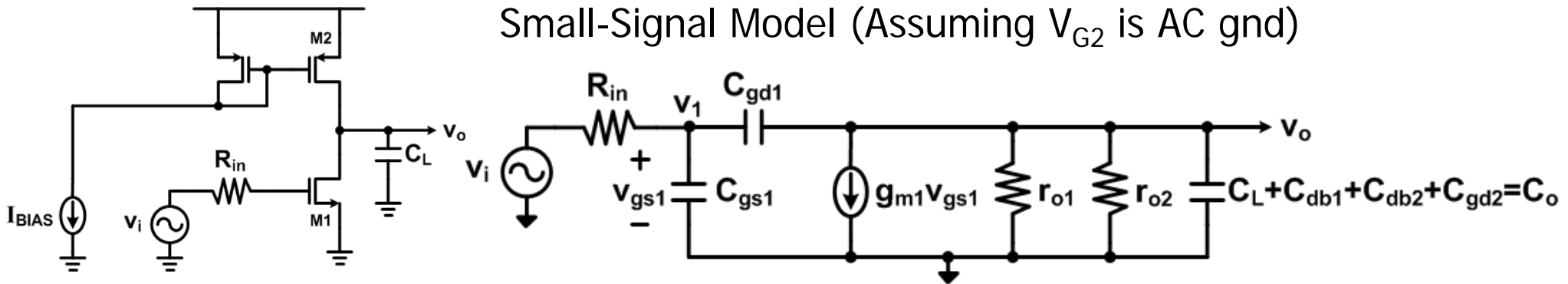Common-Source Amplifier: High Frequency Response



Small-Signal Model (Assuming V_{G2} is AC gnd)

$$\text{KCL @ Node } v_1 : (v_1 - v_i)G_{in} + v_1 s C_{gs1} + (v_1 - v_o) s C_{gd1} = 0$$

$$\text{KCL @ Node } v_o : (v_o - v_1) s C_{gd1} + g_{m1} v_1 + v_o (g_o + s C_o) = 0$$

$$\text{where } g_o = g_{o1} + g_{o2}$$

After some algebra, we get
the exact transfer function:

$$\frac{v_o}{v_i} = \frac{-g_m r_o \left(1 - s \frac{C_{gd1}}{g_{m1}} \right)}{1 + sa + s^2 b}$$


where

$$a = R_{in} [C_{gs1} + C_{gd1} (1 + g_m r_o)] + r_o (C_{gd1} + C_o)$$

and

$$b = R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)$$

Common-Source Amp Frequency Response

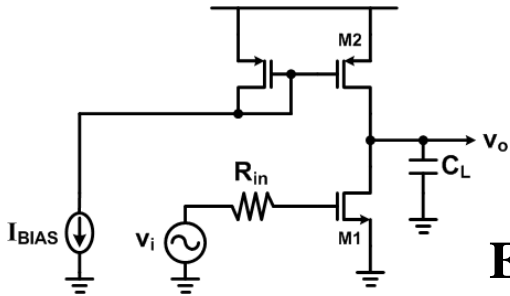

Exact Transfer Function :
$$\frac{v_o}{v_i} = \frac{-g_m r_o \left(1 - s \frac{C_{gd1}}{g_{m1}}\right)}{1 + sa + s^2 b}$$

For the common case when the two poles are real and far apart

Denominator
$$D(s) = \left(1 - \frac{s}{\omega_{p1}}\right) \left(1 - \frac{s}{\omega_{p2}}\right) = 1 - s \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right) + \frac{s^2}{\omega_{p1} \omega_{p2}} \cong 1 - \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1} \omega_{p2}}$$

Thus,
$$\omega_{p1} = -\frac{1}{a} = -\frac{1}{R_{in} [C_{gs1} + C_{gd1} (1 + g_{m1} r_o)] + r_o (C_{gd1} + C_o)}$$

and the transfer function can be approximated as a single pole system

$$A(s) = \frac{v_o}{v_i} \cong \frac{-g_{m1} r_o}{1 + s \left(R_{in} [C_{gs1} + C_{gd1} (1 + g_{m1} r_o)] + r_o (C_{gd1} + C_o) \right)}$$

Open-Circuit Time Constants (OC τ)

- Open-circuit time constants technique can be used to estimate bandwidth
 - Much easier than deriving transfer function
 - Accurate for systems with one dominant pole

$$\text{All - Pole Transfer Function : } \frac{v_o(s)}{v_i(s)} = \frac{a_0}{(\tau_1 s + 1)(\tau_2 s + 1) \dots (\tau_n s + 1)}$$

$$\text{Denominator : } b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + 1$$



$$\text{Here } b_n = \prod_{i=1}^n \tau_i \quad \text{and} \quad b_1 = \sum_{i=1}^n \tau_i$$

A Dominant - Pole System can be approximated as

$$\frac{v_o(s)}{v_i(s)} \cong \frac{a_0}{b_1 s + 1} = \frac{a_0}{\left(\sum_{i=1}^n \tau_i \right) s + 1}$$

$$\text{Bandwidth } \omega_h \cong \frac{1}{b_1} = \frac{1}{\sum_{i=1}^n \tau_i} = \omega_{h,est}$$


Open-Circuit Time Constants ($OC\tau$)

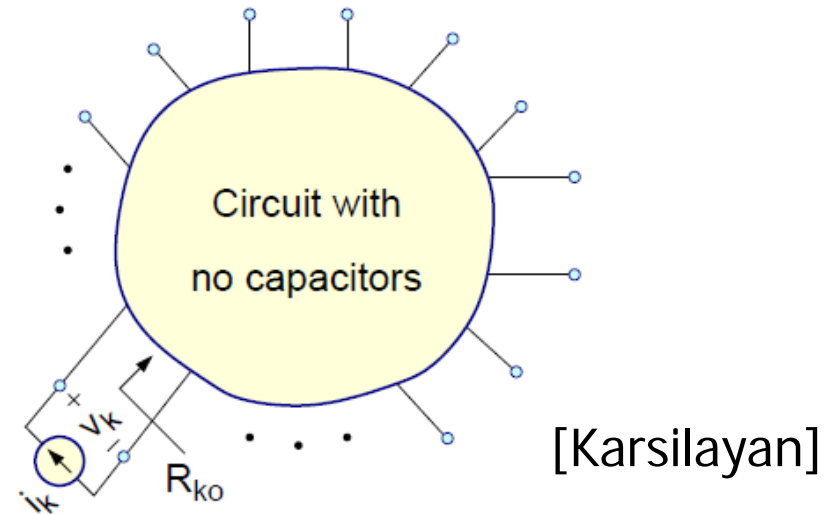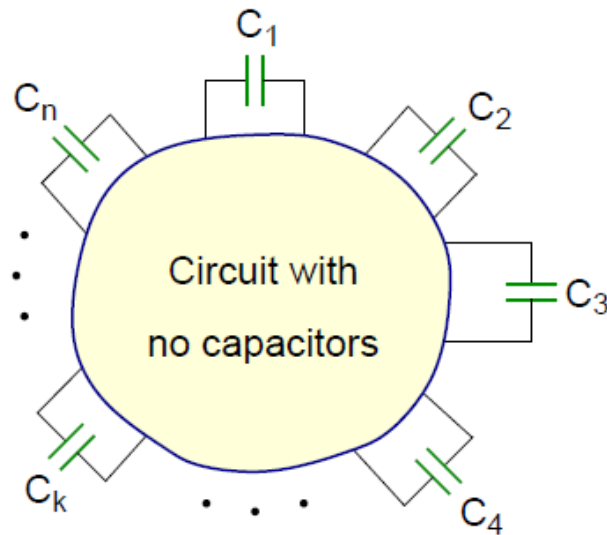


- To compute time-constants
 1. Compute effective resistance R_{ko} facing each k th capacitor with all other caps open-circuited
 2. Form the product $\tau_{ko} = R_{ko} C_k$
 3. Sum all n "open-circuit" time constants

$$\omega_{h,est} = \frac{1}{\sum_{k=1}^n R_{ko} C_k}$$

Common-Source Amp w/ $OC\tau$

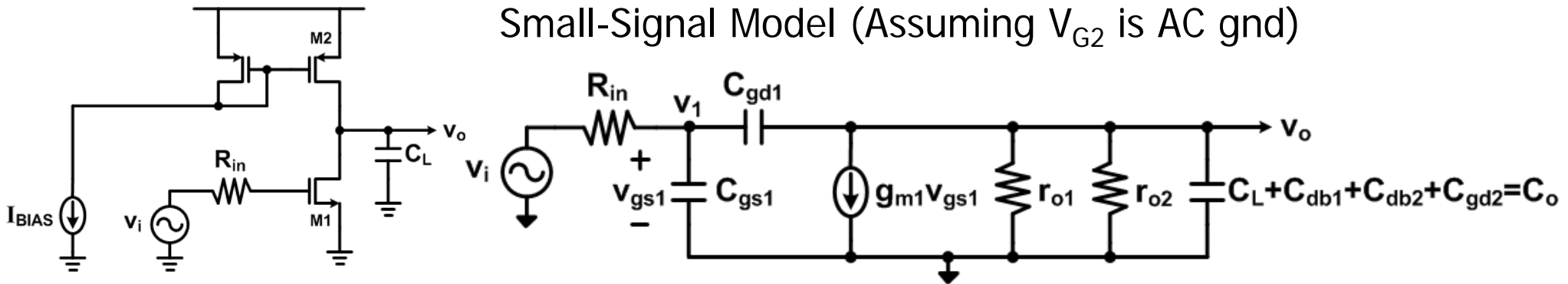


- For C_{gs1}

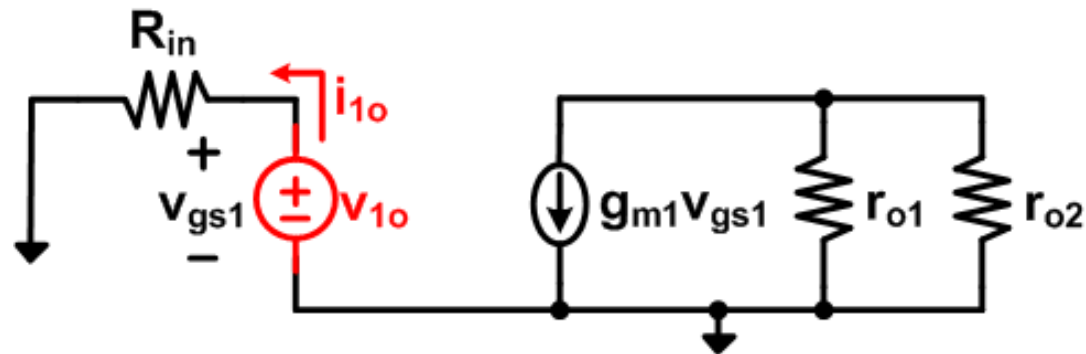


$$R_{1o} = \frac{v_{1o}}{i_{1o}} = \frac{v_{1o}}{\left(\frac{v_{1o}}{R_{in}} \right)} = R_{in}$$

$$\tau_{1o} = R_{in} C_{gs1}$$

Common-Source Amp w/ $OC\tau$

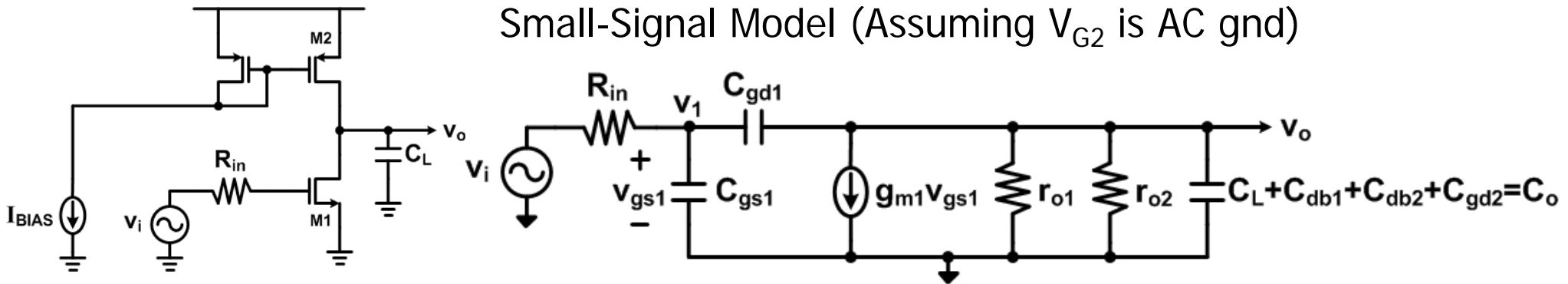

- For C_{gd1}

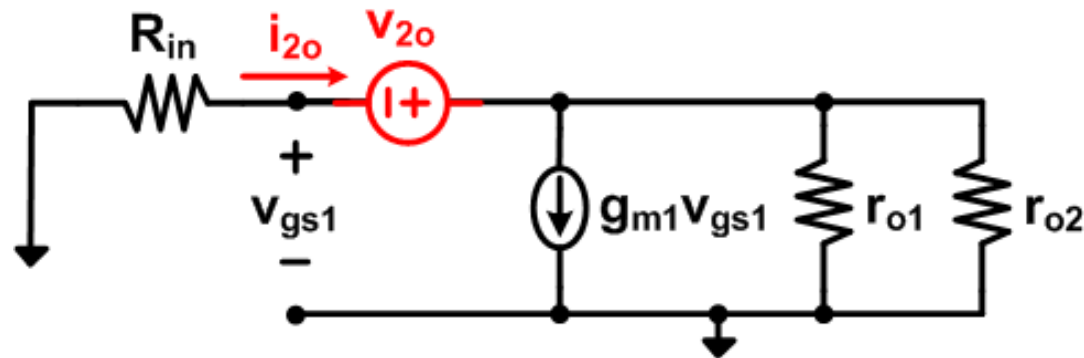

$$(1) \quad i_{2o} = g_m v_{gs1} + \frac{(v_{2o} + v_{gs1})}{r_o}$$


$$(2) \quad v_{gs1} = -i_{2o} R_{in}$$

Plugging (2) into (1) and solving for $\frac{v_{2o}}{i_{2o}}$


$$R_{2o} = \frac{v_{2o}}{i_{2o}} = R_{in} (1 + g_m r_o) + r_o$$

$$\tau_{2o} = (R_{in} (1 + g_m r_o) + r_o) C_{gd1}$$

Common-Source Amp w/ $OC\tau$

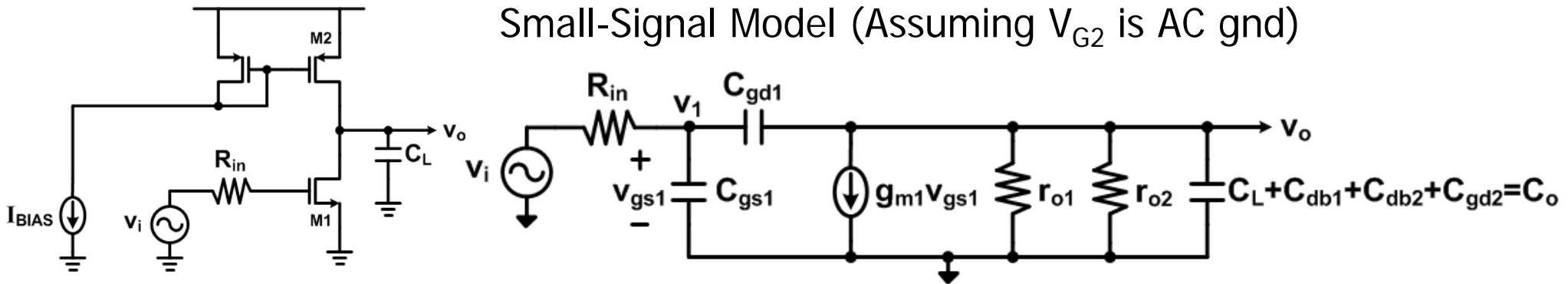


- For C_o

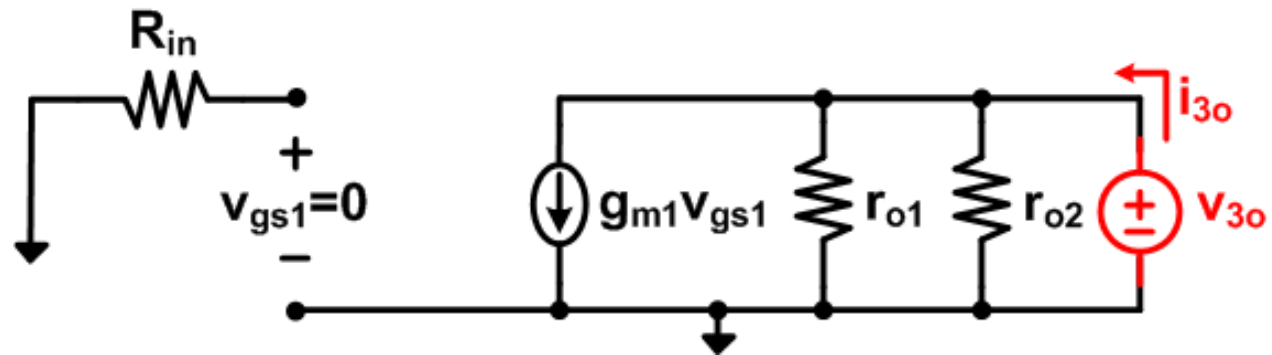

$$R_{3o} = \frac{v_{3o}}{i_{3o}} = \frac{v_{3o}}{\left(\frac{v_{3o}}{r_o} \right)} = r_o$$

$$\tau_{3o} = r_o C_o$$

Common-Source Amp w/ $OC\tau$

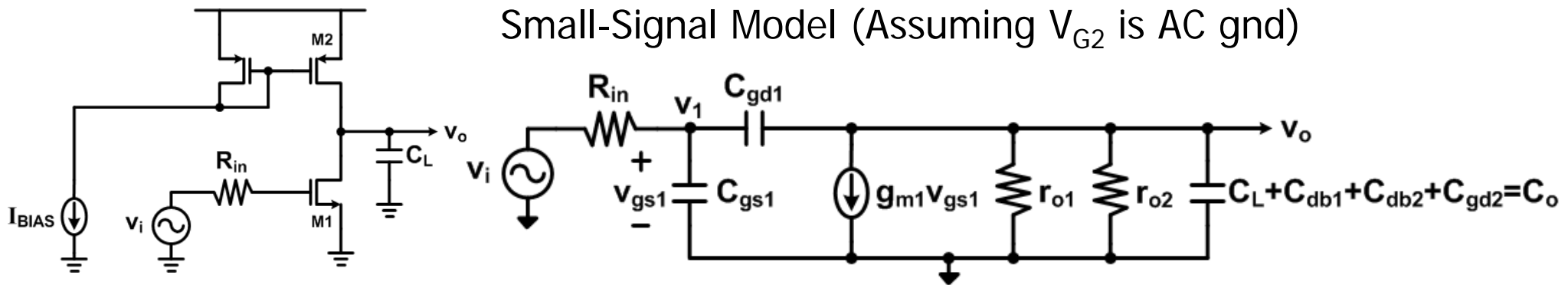

3 Time Constants: $\tau_{1o} = R_{in} C_{gs1}$, $\tau_{2o} = (R_{in}(1 + g_m r_o) + r_o) C_{gd1}$, $\tau_{3o} = r_o C_o$


$$b_1 = \sum_{i=1}^n \tau_i = R_{in} C_{gs1} + (R_{in}(1 + g_m r_o) + r_o) C_{gd1} + r_o C_o$$

$$\omega_{h,est} = \frac{1}{b_1} = \frac{1}{R_{in} C_{gs1} + (R_{in}(1 + g_m r_o) + r_o) C_{gd1} + r_o C_o}$$

Exactly the same as what we derived in Slide 6!

$$A(s) = \frac{v_o}{v_i} \cong \frac{-g_{m1} r_o}{1 + s(R_{in} [C_{gs1} + C_{gd1}(1 + g_{m1} r_o)] + r_o (C_{gd1} + C_o))}$$

Common-Source Amp w/ Large R_{in}

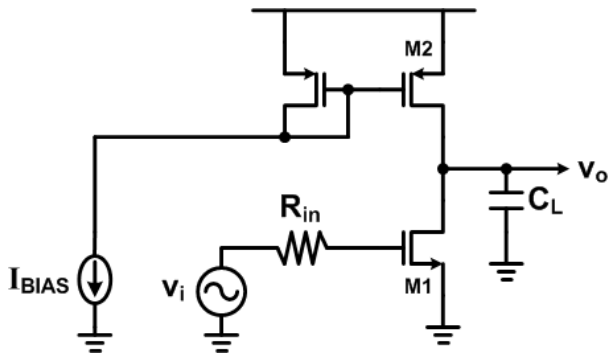

- Example: Using common-source output stage in a 2-stage OpAmp

$$A(s) = \frac{v_o}{v_i} \cong \frac{-g_{m1}r_o}{1 + s(R_{in}[C_{gs1} + C_{gd1}(1 + g_{m1}r_o)] + r_o(C_{gd1} + C_o))}$$

with $R_{in} \gg r_o$


$$A(s) = \frac{v_o}{v_i} \cong \frac{-g_{m1}r_o}{1 + sR_{in}[C_{gs1} + C_{gd1}(1 + g_{m1}r_o)]}$$

$$\omega_{p1} = -\frac{1}{R_{in}[C_{gs1} + C_{gd1}(1 + g_{m1}r_o)]}$$

- Dominant pole is formed by input resistance times transistor C_{gs} and C_{gd} which has been multiplied by $1 - A_{dc}$
 - $C_{gd}(1 - A_{dc})$ is called the Miller capacitance

Miller's Theorem

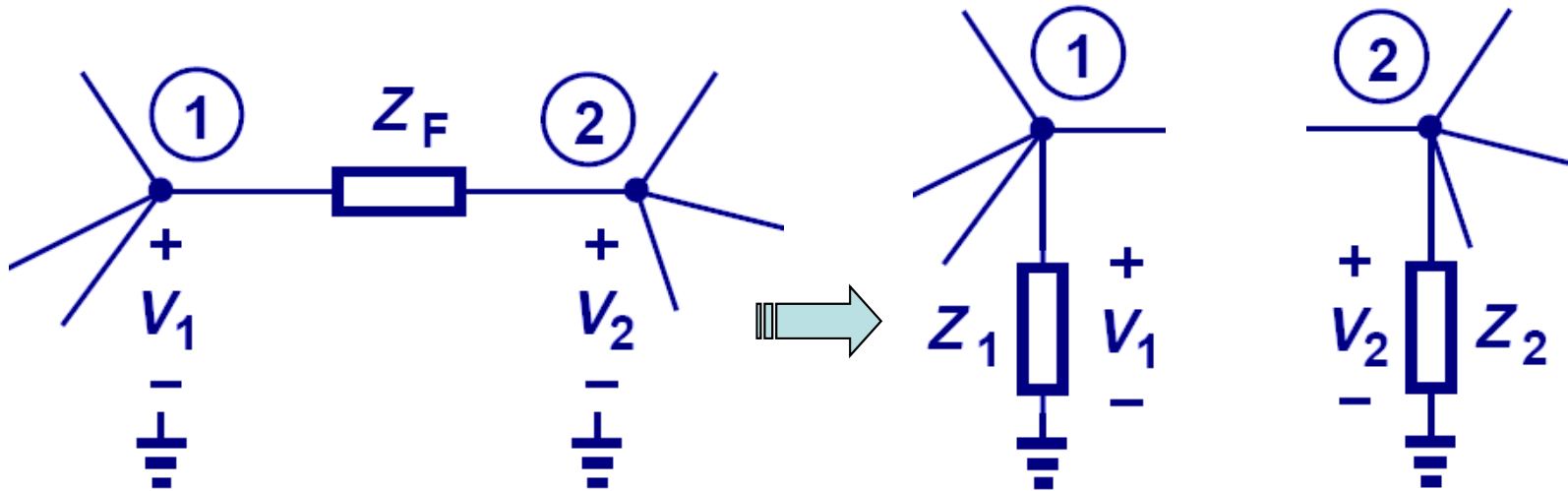➤ If A_v is the gain from node 1 to 2, then a floating impedance Z_F can be converted to two grounded impedances Z_1 and Z_2 .



I_1 should be the same in both circuits

$$I_1 = \frac{V_1 - V_2}{Z_F} = \frac{V_1}{Z_1}$$

$$Z_1 = \left(\frac{V_1}{V_1 - V_2} \right) Z_F = \left(\frac{1}{1 - \frac{V_2}{V_1}} \right) Z_F = \frac{Z_F}{1 - A_v}$$

where $A_v = \frac{V_2}{V_1}$

$$Z_1 = \frac{Z_F}{1 - A_v}$$


I_2 should be the same in both circuits

$$I_2 = \frac{V_2 - V_1}{Z_F} = \frac{V_2}{Z_2}$$

$$Z_2 = \left(\frac{V_2}{V_2 - V_1} \right) Z_F = \left(\frac{1}{1 - \frac{V_1}{V_2}} \right) Z_F = \frac{Z_F}{1 - \frac{1}{A_v}}$$

$$Z_2 = \frac{Z_F}{1 - 1/A_v}$$

Miller Multiplication

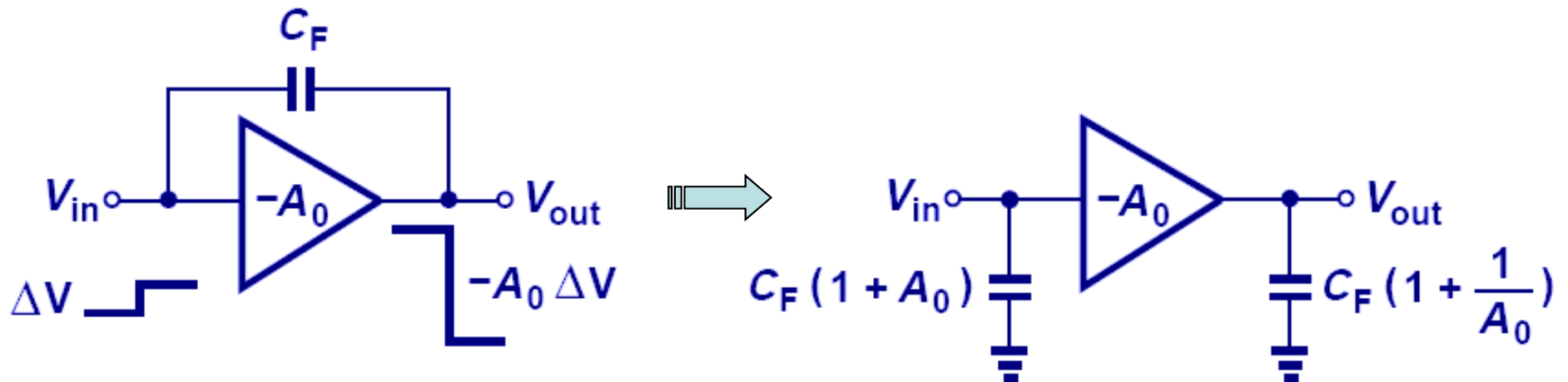


$$Z_{in} = \frac{1}{j\omega C_F (1 - A_v)} = \frac{1}{j\omega C_F (1 - (-A_o))} = \frac{1}{j\omega C_F (1 + A_o)}$$

Equivalent to an input cap that is the original C_F multiplied by $(1 + A_o)$

Following a similar procedure, the output cap is the original C_F multiplied by $\left(1 + \frac{1}{A_o}\right)$

➤ **With Miller's theorem, we can separate the floating capacitor. However, the input capacitor is larger than the original floating capacitor. We call this Miller multiplication.**

Common-Source Amp w/ Large R_{in}

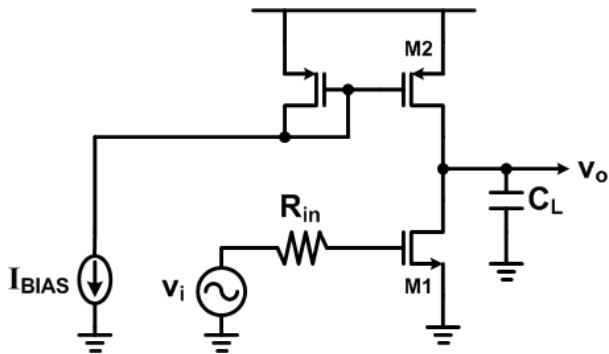

- What about the second pole?

Exact Transfer Function :
$$\frac{v_o}{v_i} = \frac{-g_m r_o \left(1 - s \frac{C_{gd1}}{g_{m1}}\right)}{1 + sa + s^2 b}$$

Denominator
$$D(s) = \left(1 - \frac{s}{\omega_{p1}}\right) \left(1 - \frac{s}{\omega_{p2}}\right) = 1 - s \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right) + \frac{s^2}{\omega_{p1} \omega_{p2}} \cong 1 - \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1} \omega_{p2}}$$


$$\frac{1}{\omega_{p1} \omega_{p2}} = b = R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)$$

$$\omega_{p2} = -\frac{1}{\omega_{p1} R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)} = -\frac{R_{in} [C_{gs1} + C_{gd1} (1 + g_{m1} r_o)]}{R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)}$$

Assuming that the Miller Cap, $C_{gd1} (1 + g_{m1} r_o)$, dominates

$$\omega_{p2} \cong -\frac{g_m C_{gd1}}{C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o}$$

Common-Source Amp w/ Small R_{in}

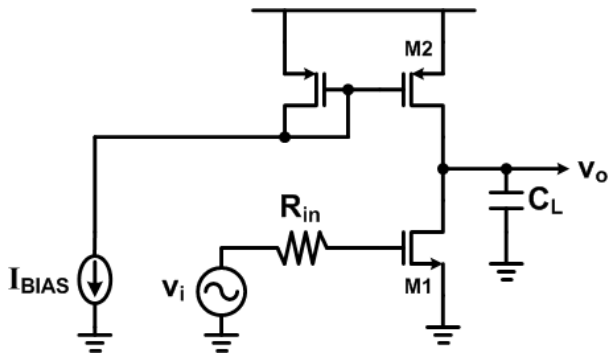

- Example: Source-follower driving the common-source amp

$$A(s) = \frac{v_o}{v_i} \cong \frac{-g_{m1}r_o}{1 + s(R_{in}[C_{gs1} + C_{gd1}(1 + g_{m1}r_o)] + r_o(C_{gd1} + C_o))}$$


with $r_o \gg R_{in}$

$$A(s) = \frac{v_o}{v_i} \cong \frac{-g_{m1}r_o}{1 + sr_o(C_{gd1} + C_o)}$$

$$\omega_{p1} = -\frac{1}{r_o(C_{gd1} + C_o)}$$

- Dominant pole is formed by output resistance times output capacitance plus transistor C_{gd}

Common-Source Amp w/ Small R_{in}

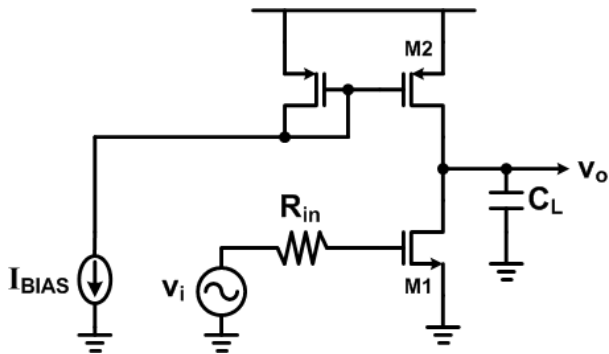

- What about the second pole?

Exact Transfer Function:
$$\frac{v_o}{v_i} = \frac{-g_m r_o \left(1 - s \frac{C_{gd1}}{g_{m1}}\right)}{1 + sa + s^2 b}$$


Denominator
$$D(s) = \left(1 - \frac{s}{\omega_{p1}}\right) \left(1 - \frac{s}{\omega_{p2}}\right) = 1 - s \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right) + \frac{s^2}{\omega_{p1} \omega_{p2}} \cong 1 - \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1} \omega_{p2}}$$

$$\frac{1}{\omega_{p1} \omega_{p2}} = b = R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)$$

$$\omega_{p2} = -\frac{1}{\omega_{p1} R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)} = -\frac{r_o (C_{gd1} + C_o)}{R_{in} r_o (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)}$$

$$\omega_{p2} = -\frac{C_{gd1} + C_o}{R_{in} (C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o)} \cong -\frac{1}{R_{in} (C_{gs1} + C_{gd1})} \quad \text{(with large } C_o)$$

Common-Source Amp Frequency Response

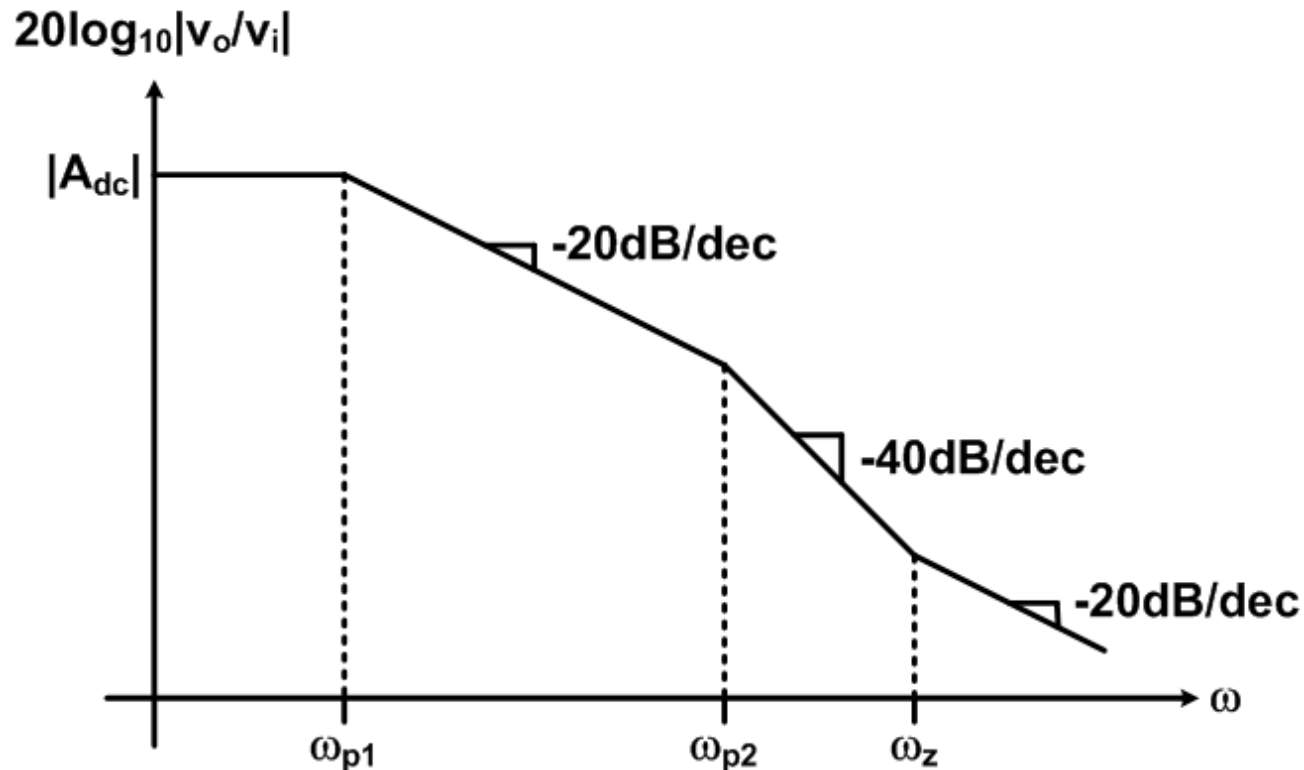

Large R_{in}


Small R_{in}

$$A_{dc} = -g_m r_o \quad \omega_z = \frac{g_{m1}}{C_{gd1}}$$

$$\omega_{p1} = -\frac{1}{R_{in} [C_{gs1} + C_{gd1} (1 + g_{m1} r_o)]} \quad \omega_{p1} = -\frac{1}{r_o (C_{gd1} + C_o)}$$

$$\omega_{p2} \cong -\frac{g_{m1} C_{gd1}}{C_{gd1} C_{gs1} + C_{gs1} C_o + C_{gd1} C_o} \quad \omega_{p2} \cong -\frac{1}{R_{in} (C_{gs1} + C_{gd1})}$$

Common-Source Amp Input Impedance

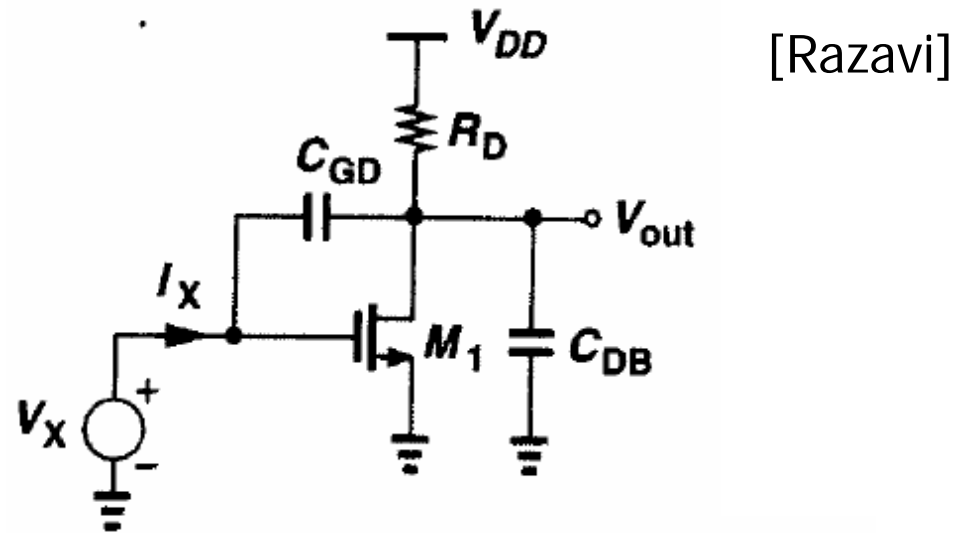


Neglecting Output Cap:
$$Z_{in} = \frac{1}{[C_{GS} + (1 + g_m R_D)C_{GD}]s}$$

Input impedance is purely capacitive ($C_{gs} + \text{Miller } C_{gd}$)



Considering Output Cap:
$$\frac{V_X}{I_X} = \frac{1 + R_D(C_{GD} + C_{DB})s}{C_{GD}s(1 + g_m R_D + R_D C_{DB}s)}$$

Low frequency is capacitive, but then impedance experiences a zero followed by a second pole

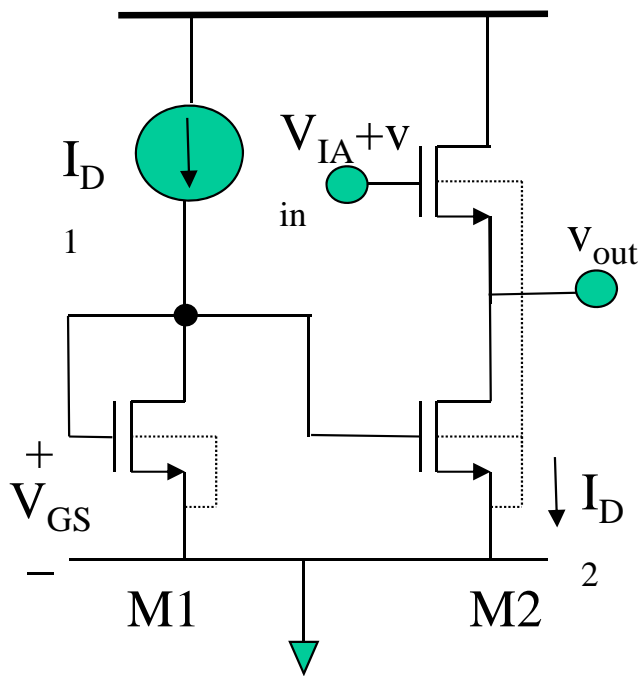Small signal analysis: Common-drain (source follower) amplifier





Small signal equivalent circuit

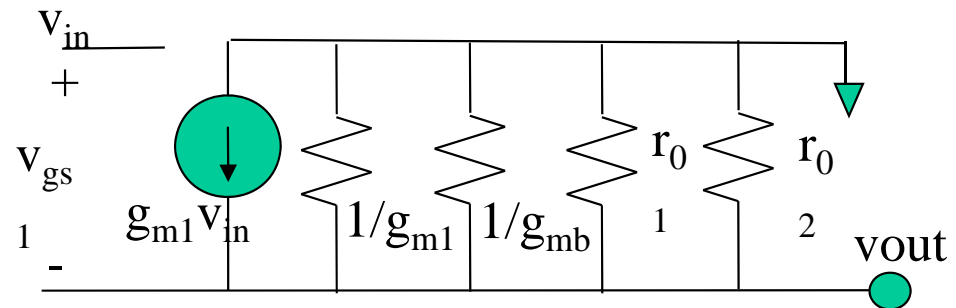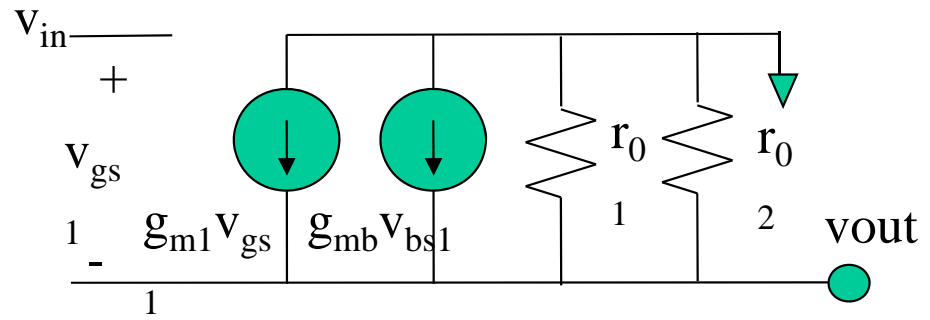

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1}}{g_{m1} + g_{mb} + g_{o1} + g_{o2}}$$



Common-Drain Amplifier: High Frequency Response

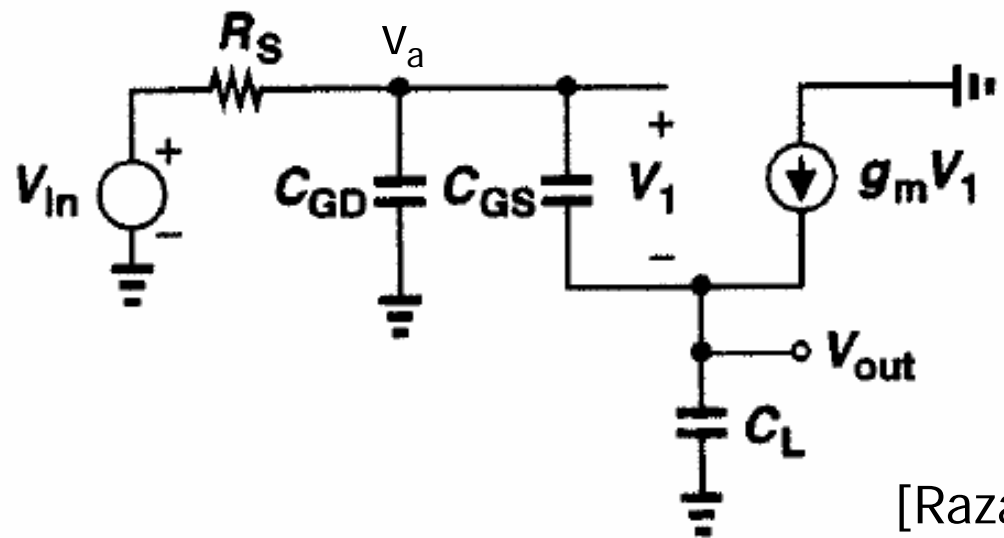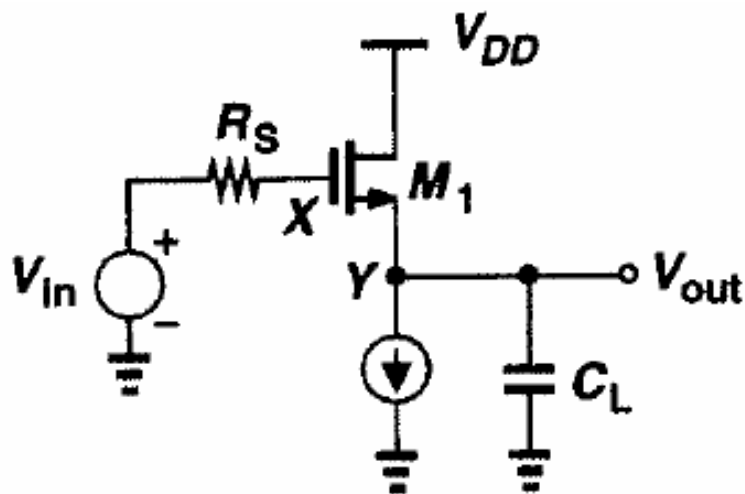- Simplifying the schematic a bit for SSA
 - Ideal current source load and neglecting transistor r_o and g_{mb} (i.e. $\lambda = \gamma = 0$)
 - Will result in an optimistic DC gain estimate



[Razavi]

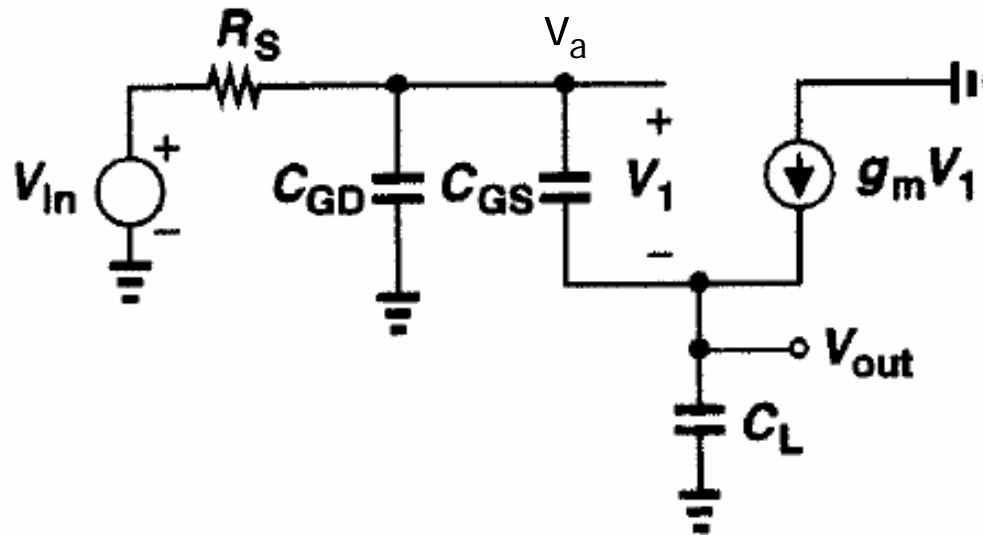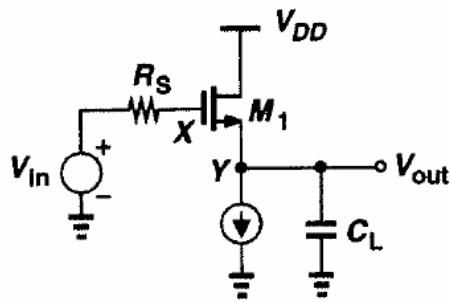Common-Drain Amplifier: High Frequency Response



[Razavi]


$$\text{KCL @ Node } v_a : (v_a - v_i)G_S + v_a s C_{gd} + (v_a - v_o) s C_{gs} = 0$$

$$\text{KCL @ Node } v_o : (v_o - v_a) s C_{gs} - g_m (v_a - v_o) + v_o s C_L = 0$$

After some algebra:

$$\frac{V_{out}}{V_{in}}(s) = \frac{g_m + C_{GS}s}{R_S(C_{GS}C_L + C_{GS}C_{GD} + C_{GD}C_L)s^2 + (g_m R_S C_{GD} + C_L + C_{GS})s + g_m}$$

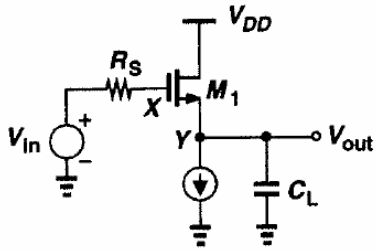Common-Drain Amplifier: High Frequency Response



$$\frac{V_{out}}{V_{in}}(s) = \frac{g_m + C_{GS}s}{R_S(C_{GS}C_L + C_{GS}C_{GD} + C_{GD}C_L)s^2 + (g_m R_S C_{GD} + C_L + C_{GS})s + g_m}$$

- From this simplified transfer function:

$$A_{dc} = \frac{g_m}{g_m} = 1 \quad (\text{Optimistic})$$

$$\text{Exact } A_{dc} = \frac{g_m}{g_m + g_o + g_{mb}}$$


$$\omega_z = -\frac{g_m}{C_{gs}}$$

2 poles, If we assume that they are spaced far apart :

$$\omega_{p1} \approx \frac{g_m}{g_m R_S C_{GD} + C_L + C_{GS}} = \frac{1}{R_S C_{GD} + \frac{C_L + C_{GS}}{g_m}}$$

Common-Drain Amp Input Impedance

[Razavi]

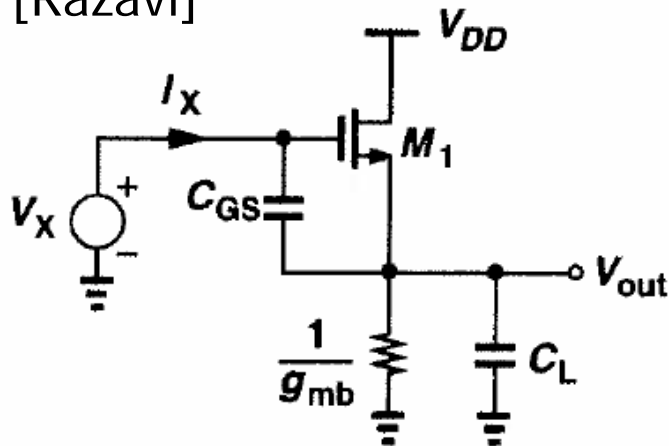

$$Z_{in} = \frac{1}{C_{GS}} + \left(1 + \frac{g_m}{C_{GS}}\right) \frac{1}{g_{mb} + C_{LS}}$$

Low Frequency: $Z_{in} \approx \frac{1}{C_{GS}} \left(1 + \frac{g_m}{g_{mb}}\right) + \frac{1}{g_{mb}}$


Equivalent to a series capacitive term $C_{gs} \left(\frac{g_{mb}}{g_m + g_{mb}} \right)$ and resistive term $\frac{1}{g_{mb}}$

High Frequency: $Z_{in} \approx \frac{1}{C_{GS}} + \frac{1}{C_{LS}} + \frac{g_m}{C_{GS}C_{LS}^2}$

Series combination of C_{gs} and C_L and a negative resistance term $\left(-\frac{g_m}{C_{gs}C_L\omega^2} \right)$

The negative resistance term can be utilized in oscillator design


Common-Drain Amp Output Impedance

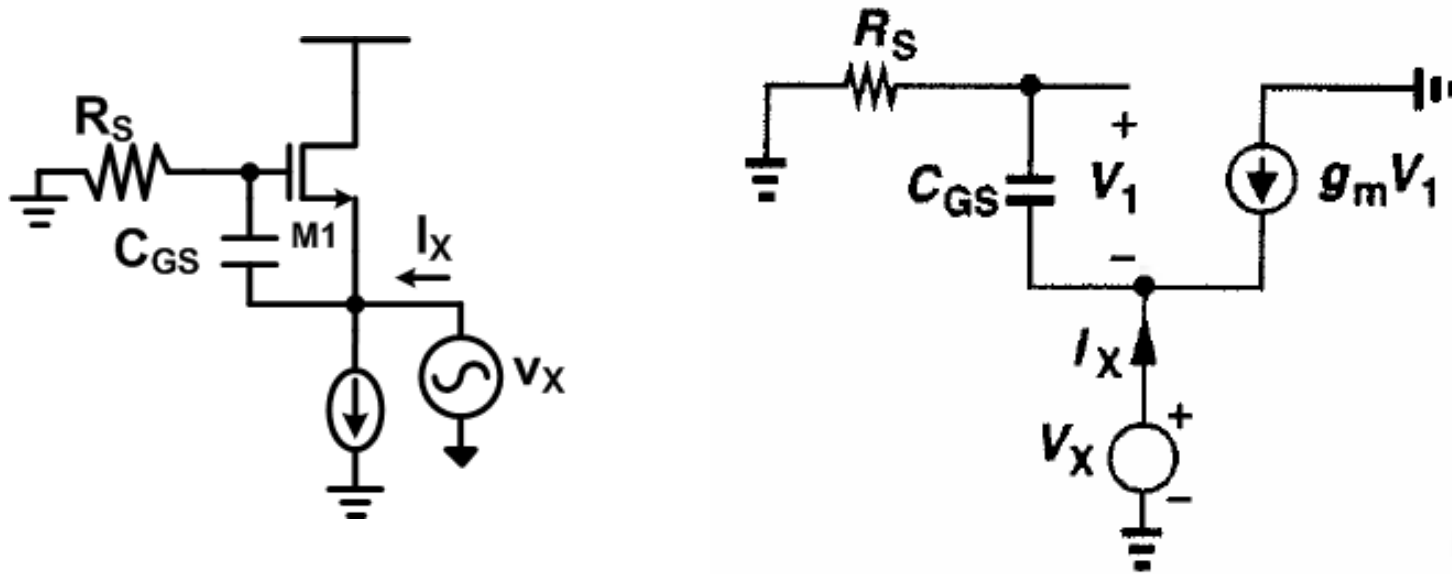


$$Z_{out} = \frac{V_X}{I_X} = \frac{R_S C_{GS} s + 1}{g_m + C_{GS} s}$$

- Pole at very high frequency
- Zero at potentially low frequency if R_S is large
 - Impedance can increase with frequency, i.e. display inductive behavior

Common-Drain Amp Output Impedance

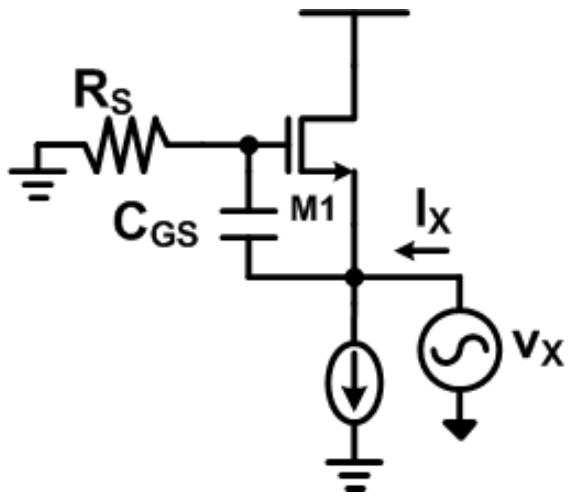
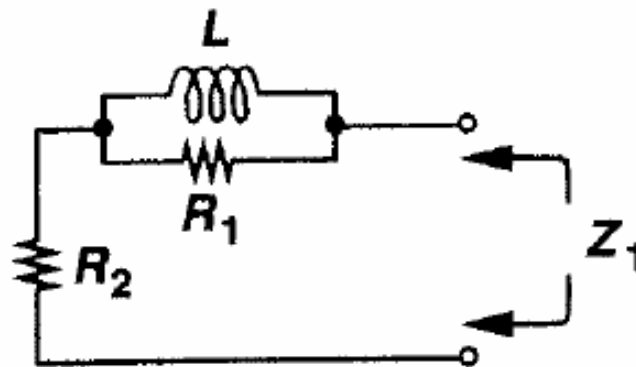
$$Z_{out} = \frac{V_X}{I_X} = \frac{R_S C_{GS} s + 1}{g_m + C_{GS} s}$$




$$R_2 = \frac{1}{g_m}$$

$$R_1 = R_S - \frac{1}{g_m}$$

$$L = \frac{C_{GS}}{g_m} \left(R_S - \frac{1}{g_m} \right) \approx \frac{R_S C_{GS}}{g_m} \text{ if } R_S \gg \frac{1}{g_m}$$

Transient Behavior w/ Large C_L

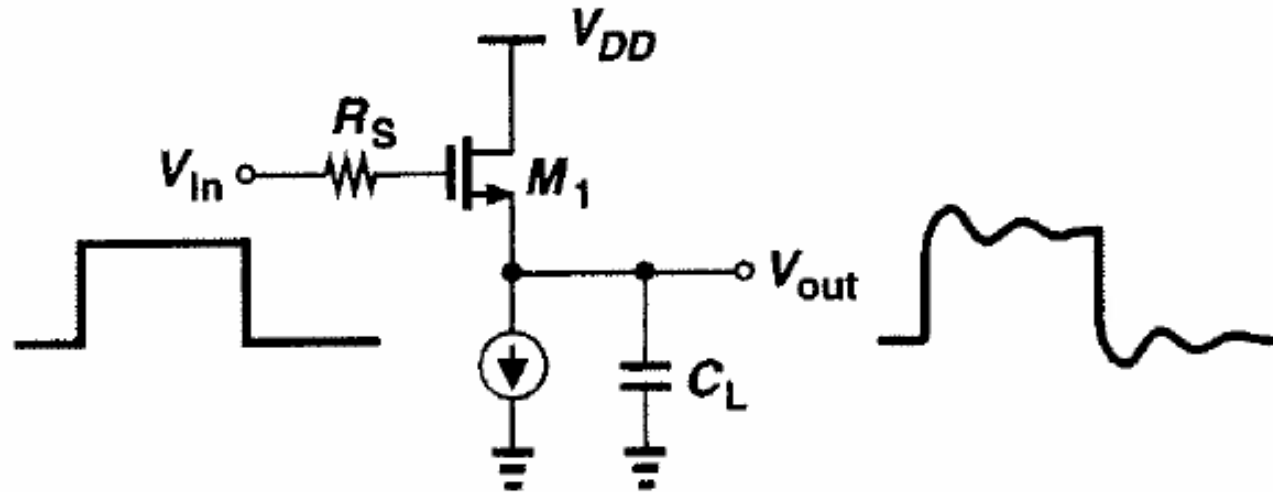


- Inductive output impedance in combination with a large load capacitance can create undesired “ringing” in the transient response
- If we have a large R_S and C_L , then the assumption that we have one dominant pole is no longer valid
- Both poles (potentially complex) should be considered in the analysis


$$\frac{V_{out}}{V_{in}}(s) = \frac{g_m + C_{GS}s}{R_S(C_{GS}C_L + C_{GS}C_{GD} + C_{GD}C_L)s^2 + (g_m R_S C_{GD} + C_L + C_{GS})s + g_m}$$

Common-Gate Amp Low Frequency Response

- No R_S

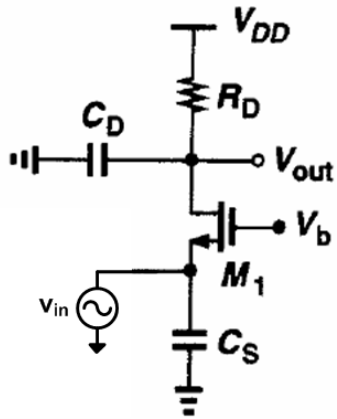

- With R_S

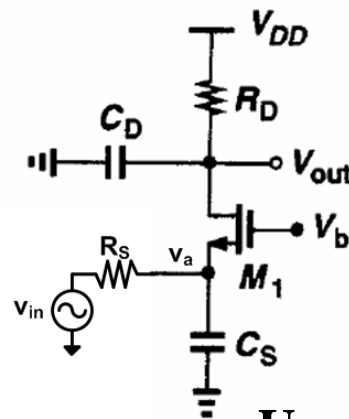

$$\frac{v_{out}}{v_a} \text{ is given from left}$$

How to get from v_{in} to v_a ?

Use amplifier input impedance and voltage divider

Neglecting transistor r_o


$$\frac{v_{out}}{v_{in}} = (g_m + g_{mb})R_D$$

$$R_{in} = \frac{1}{g_m + g_{mb}}$$

$$v_a = \frac{\frac{1}{g_m + g_{mb}}}{R_S + \frac{1}{g_m + g_{mb}}} v_{in} = \frac{1}{1 + (g_m + g_{mb})R_S} v_{in}$$

$$\frac{v_{out}}{v_{in}} = \frac{v_a}{v_{in}} \frac{v_{out}}{v_a} = \frac{(g_m + g_{mb})R_D}{1 + (g_m + g_{mb})R_S} \approx \frac{R_D}{R_S} \text{ if } R_S \text{ is large}$$

Common-Gate Amp Frequency Response

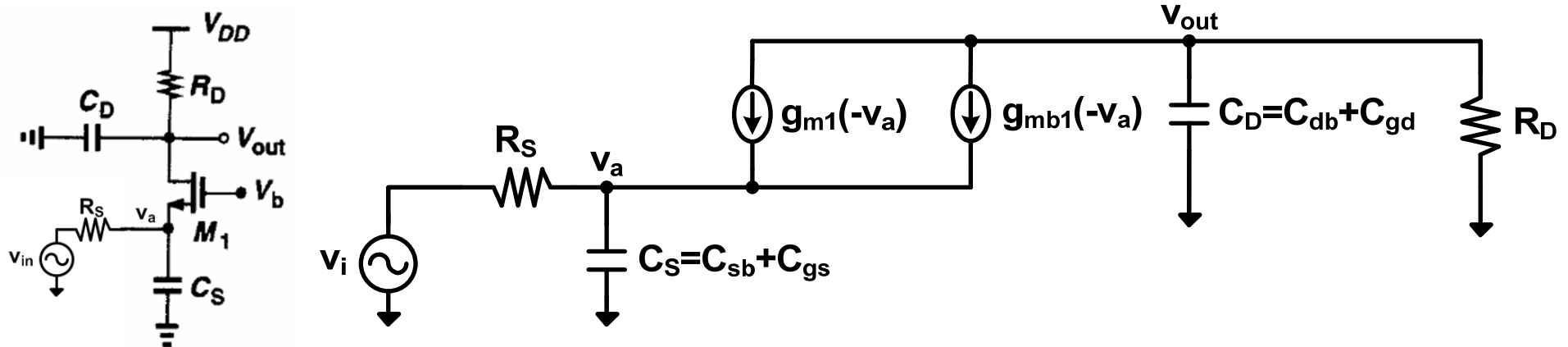


$$\frac{V_{out}}{V_{in}}(s) = \frac{(g_m + g_{mb})R_D}{1 + (g_m + g_{mb})R_S} \frac{1}{\left(1 + \frac{C_S}{g_m + g_{mb} + R_S^{-1}s}\right) (1 + R_D C_D s)}$$

- No zero
- No Miller capacitor multiplication
- Low input impedance limits effectiveness as a voltage amplifier
- Useful as a current-to-voltage (transimpedance) amplifier

Cascode Amp Frequency Response

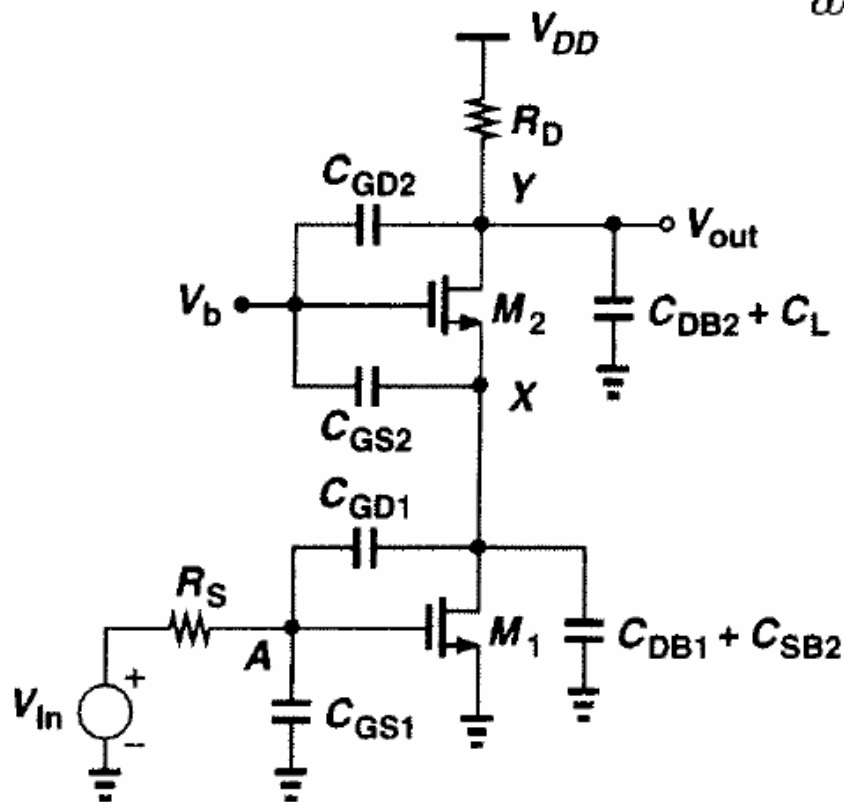- If we associate the poles with the nodes A, X, and Y
 - Note, this is only an approximation, as it ignores interactions caused by “feedforward” caps (C_{gd}) and resistors
- 3 pole system



Input Pole

$$\omega_{p,A} = \frac{1}{R_S \left[C_{GS1} + \left(1 + \frac{g_{m1}}{g_{m2} + g_{mb2}} \right) C_{GD1} \right]}$$

Internal Pole – High Frequency


$$\omega_{p,X} = \frac{g_{m2} + g_{mb2}}{2C_{GD1} + C_{DB1} + C_{SB2} + C_{GS2}}$$

Output Pole

$$\omega_{p,Y} = \frac{1}{R_D(C_{DB2} + C_L + C_{GD2})}$$

Cascode Amp Output Impedance

- Simplified Model

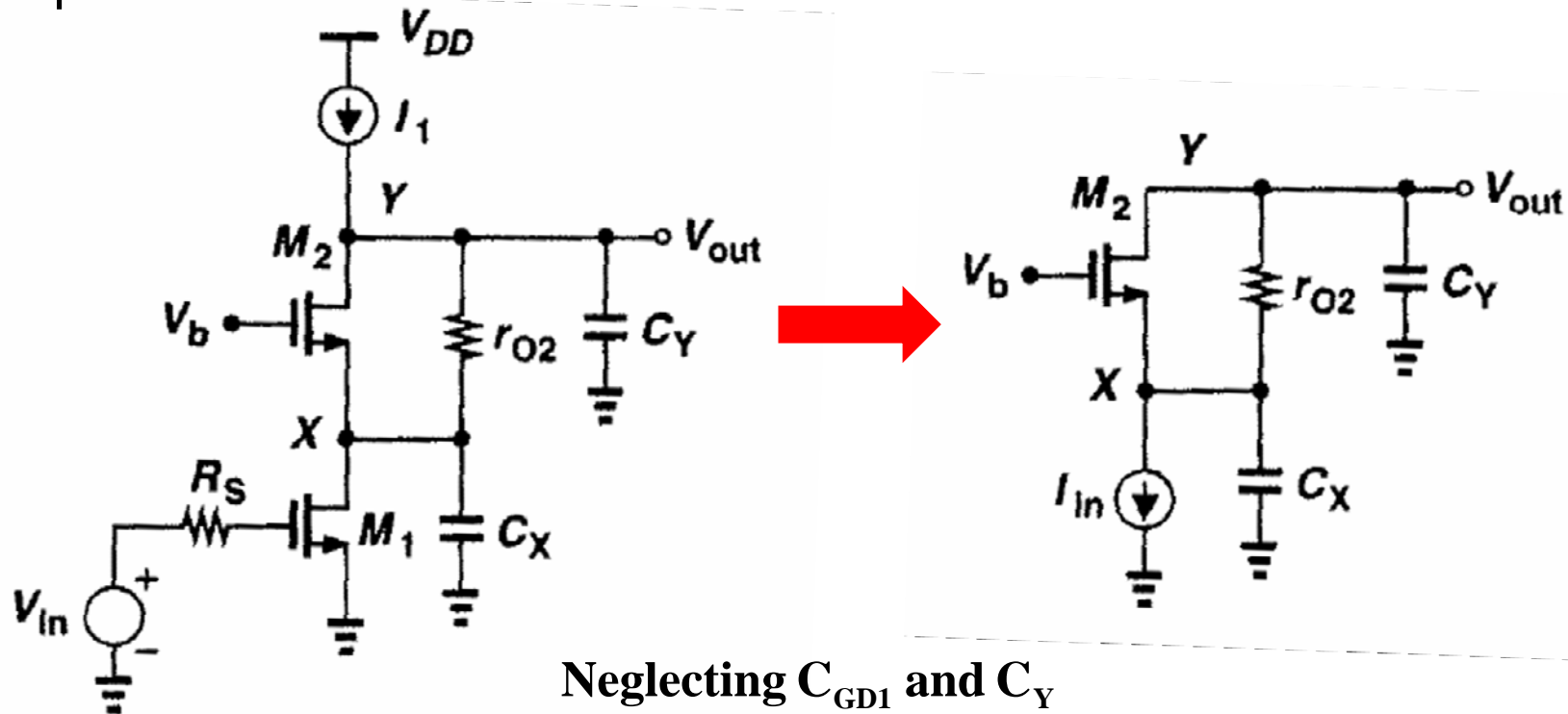

Neglecting C_{GD1} and C_Y

$$Z_{out} = r_{o2} + Z_X + g_{m2}r_{o2}Z_X$$

$$\text{where } Z_X = r_{o1} \parallel \frac{1}{sC_X}$$

$$\text{Output Impedance Pole } \omega_{Zout} = \frac{1}{r_{o1}C_X}$$

Next Time

- Differential Amplifiers