

# ECEN474/704: (Analog) VLSI Circuit Design Spring 2018

---

## Lecture 15: Fully Differential Amplifiers & CMFB



Sam Palermo  
Analog & Mixed-Signal Center  
Texas A&M University

# Announcements

---


- Project Report Due May 1
  - Email it to me by 5PM
- Exam 3 is on May 3
  - 3PM-5PM

# Agenda


---

- Fully differential circuits
- Common-mode feedback circuits
- Multi-OTA stages CMFB
- OTA-C filter w/ CMFB example
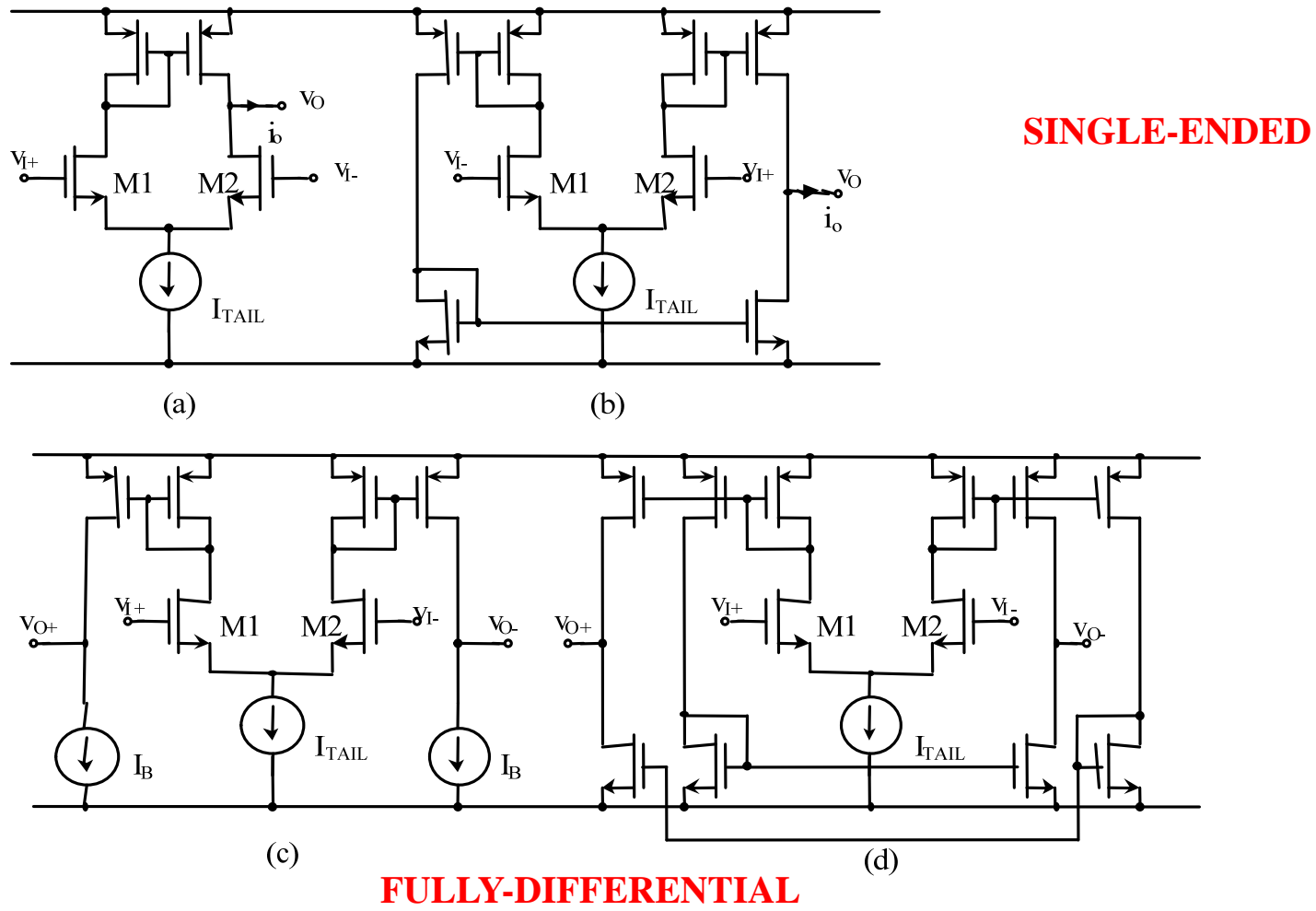
## Basic Operational Transconductance Amplifier Topologies



# Fully-Differential Circuits

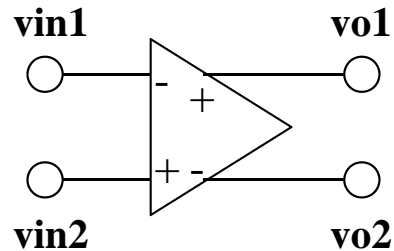

In general:

$$v_{o1} = \frac{v_{o1} - v_{o2}}{2} + \frac{v_{o1} + v_{o2}}{2} = \frac{v_{od}}{2} + v_{oc}$$

$$v_{o2} = \frac{v_{o2} - v_{o1}}{2} + \frac{v_{o1} + v_{o2}}{2} = -\frac{v_{od}}{2} + v_{oc}$$

➤ Hence

$$\begin{bmatrix} v_{od} \\ v_{oc} \end{bmatrix} = \begin{bmatrix} A_{dd} & A_{dc} \\ A_{cd} & A_{cc} \end{bmatrix} \begin{bmatrix} v_{id} \\ v_{ic} \end{bmatrix}$$

**Differential-mode output**

$$A_{dd} = \left. \frac{v_{od}}{v_{id}} \right|_{v_{ic}=0}$$


$$A_{dc} = \left. \frac{v_{od}}{v_{ic}} \right|_{v_{id}=0}$$

$$A_{cd} = \left. \frac{v_{oc}}{v_{id}} \right|_{v_{ic}=0}$$

$$A_{cc} = \left. \frac{v_{oc}}{v_{ic}} \right|_{v_{id}=0}$$

**Common-mode output**
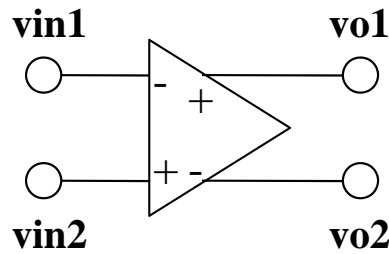
# Fully-Differential Filters: Effects of current source impedance and mismatches




A very important parameter:

$$CMRR = \frac{A_{dd}}{A_{dc}}$$

w/  $v_{id} = v_{i2} - v_{i1}$  and  $v_{ic} = \frac{v_{i2} + v_{i1}}{2}$

Solving the circuit:

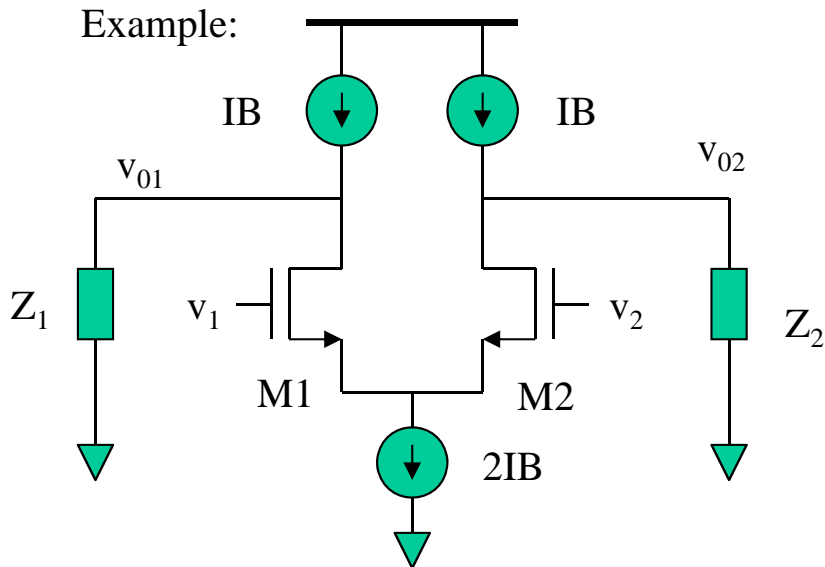


$$v_{01} = \frac{g_{m1}g_{m2}Z_1}{g_{m1} + g_{m2} + Y_s} \left[ \left(1 + \frac{Y_s}{2g_{m2}}\right)v_{id} - \left(\frac{Y_s}{g_{m2}}\right)v_{ic} \right]$$

$$v_{02} = \frac{g_{m1}g_{m2}Z_2}{g_{m1} + g_{m2} + Y_s} \left[ -\left(1 + \frac{Y_s}{2g_{m1}}\right)v_{id} - \left(\frac{Y_s}{g_{m1}}\right)v_{ic} \right]$$

$Y_s$  is the admittance associated with the current source  $2IB$

# Fully-Differential Filters: Non-idealities

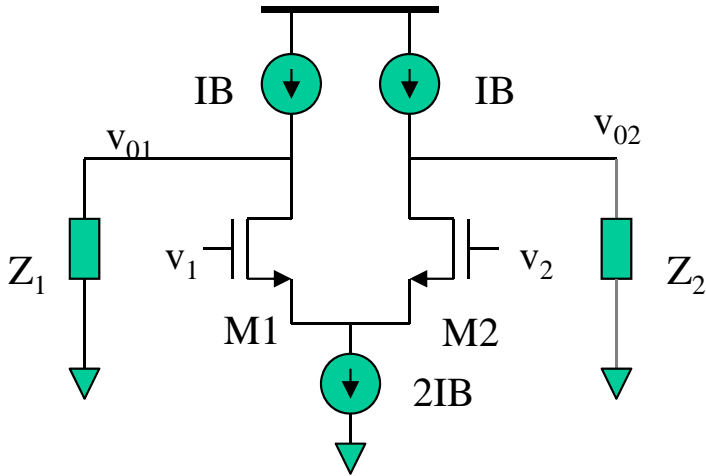**Voltage gain: Note the effects of the mismatches, especially in  $A_{dc}$  and  $A_{cd}$**



$$CMRR = \frac{A_{dd}}{A_{dc}} \cong \frac{g_{m1} \left( 1 + \frac{Z_1}{Z_2} \right)}{Y_s \left( 1 - \frac{g_{m1} Z_1}{g_{m2} Z_2} \right)}$$


$$A_{dd} = \frac{v_{o1} - v_{o2}}{v_{i2} - v_{i1}} \Big|_{v_{ic}=0} = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2} + Y_s} \left[ Z_1 + Z_2 + \frac{Y_s}{2} \left( \frac{Z_1}{g_{m2}} + \frac{Z_2}{g_{m1}} \right) \right]$$

$$A_{dc} = \frac{v_{o1} - v_{o2}}{(v_{i2} + v_{i1})/2} \Big|_{v_{id}=0} = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2} + Y_s} \left[ Y_s \left( \frac{Z_2}{g_{m1}} - \frac{Z_1}{g_{m2}} \right) \right]$$

$$A_{cd} = \frac{(v_{o2} + v_{o1})/2}{v_{i2} - v_{i1}} \Big|_{v_{ic}=0} = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2} + Y_s} \left( \frac{1}{2} \right) \left[ Z_1 - Z_2 + \frac{Y_s}{2} \left( \frac{Z_1}{g_{m2}} - \frac{Z_2}{g_{m1}} \right) \right]$$

$$A_{cc} = \frac{(v_{o2} + v_{o1})/2}{(v_{i2} + v_{i1})/2} \Big|_{v_{id}=0} = - \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2} + Y_s} \left( \frac{1}{2} \right) \left[ Y_s \left( \frac{Z_2}{g_{m1}} + \frac{Z_1}{g_{m2}} \right) \right]$$

# Fully-Differential Circuits

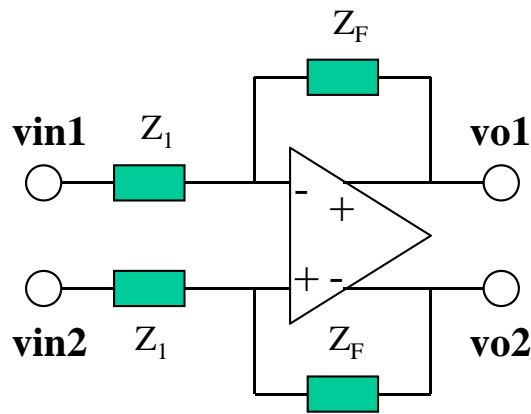

➤ Ideal voltage gain


$$A_{dd} = \frac{v_{o1} - v_{o2}}{v_{in2} - v_{in1}} = \frac{Z_f}{Z_1}$$

➤ Ideally even-order distortions are cancelled

➤ Ideally common-mode signals are rejected

➤ What sets the output common-mode of these circuits?

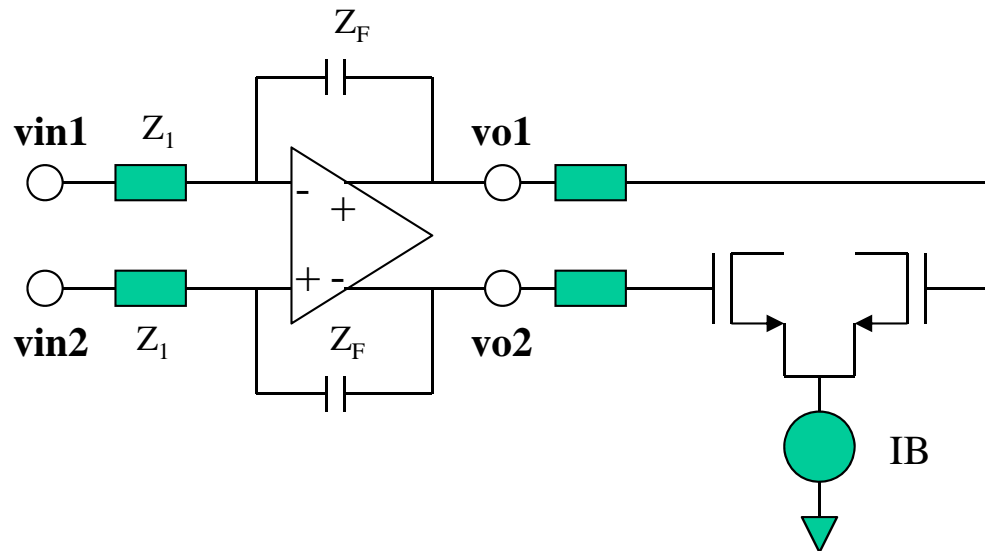➤ Function of the amplifier output resistance




**Common-mode offsets can impact the performance of the following stages**

- Can exceed the common-mode input range of preceding stages
- With finite  $A_{cc}$  can accumulate in a multi-stage amplifier circuit


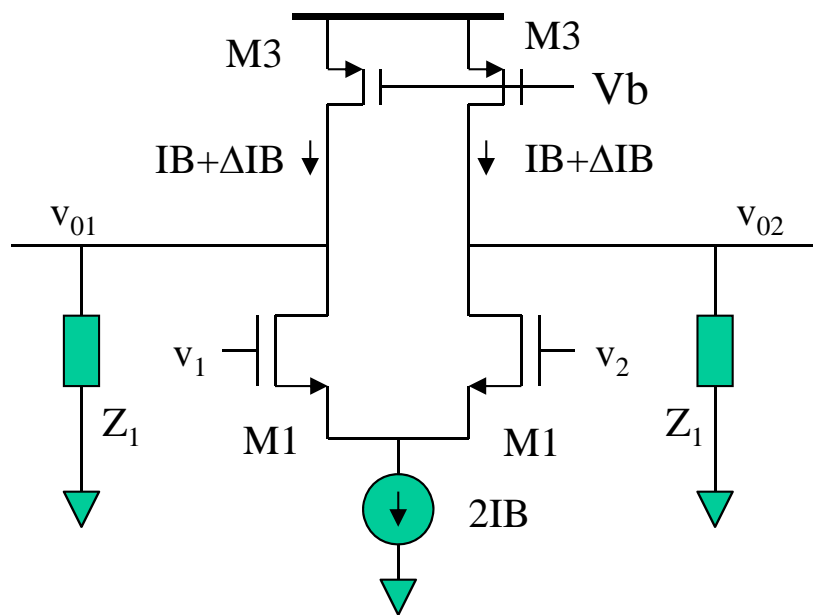
## Fully-Differential Amplifiers: COMMON-MODE DC offset



✓ If  $\Delta IB$  is positive transistors M3 eventually will be biased in triode region (small resistance)

✓ dc gain reduces drastically

✓ Linear range is further minimized

✓ THD increases


✓ The common-mode output impedance is the parallel of the equivalent output resistance (M1 and M3) and the parasitic capacitors.

✓ For large dc gain, the output impedance at nodes  $v_{01}$  and  $v_{02}$  are further increased and  $\Delta IB$  produces a dc offset =  $R_{out}\Delta IB$ .

**Large common-mode offsets!**

✓ How can this issue be fixed?
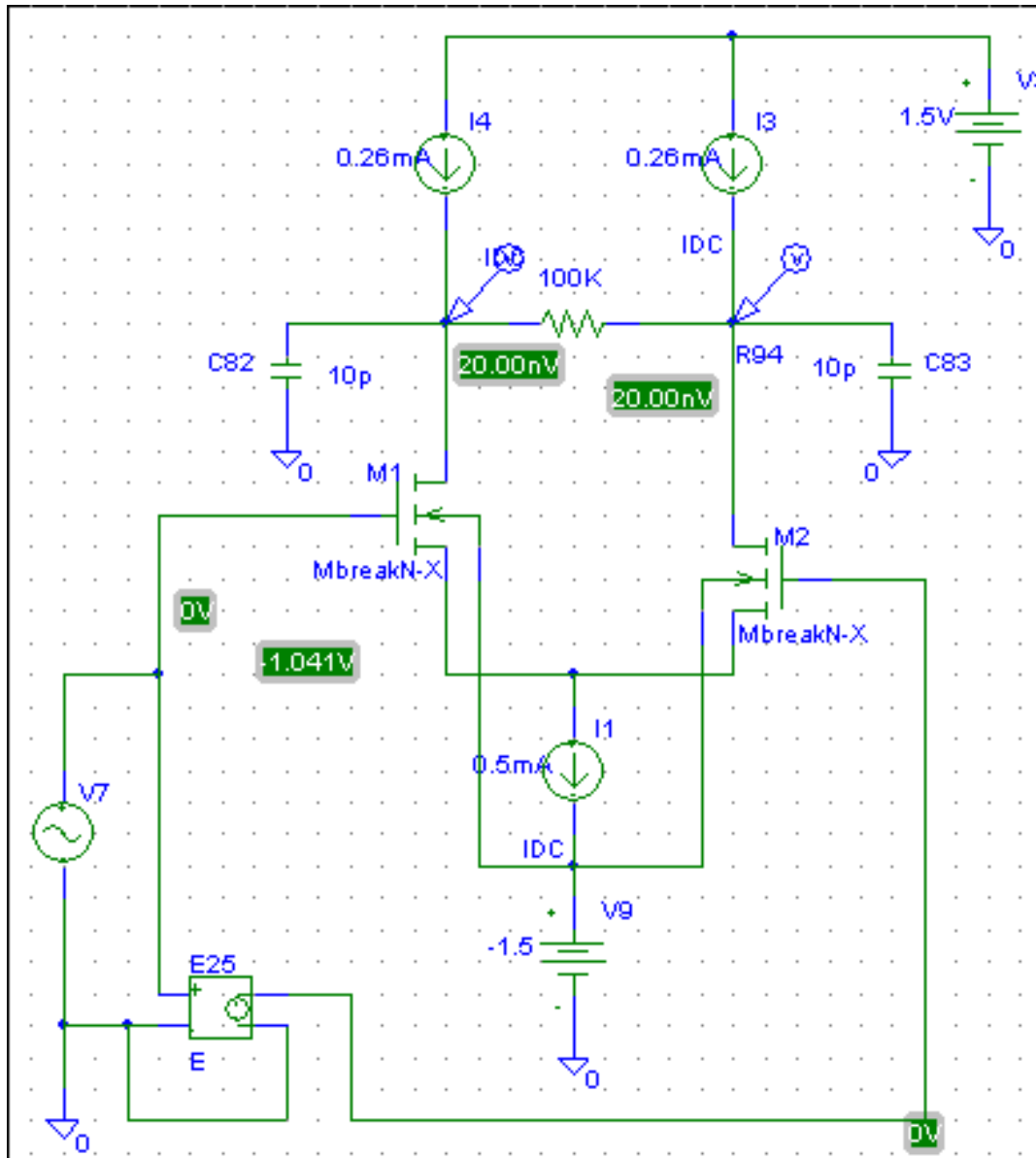
## Fully-Differential Amplifiers: Characterization





✓ Common-mode current offset of 0.01 mA per side is added on purpose

Tail current is 0.5 mA while the current sources on top are 0.26 mA!

✓ Differential input voltage is set at 0

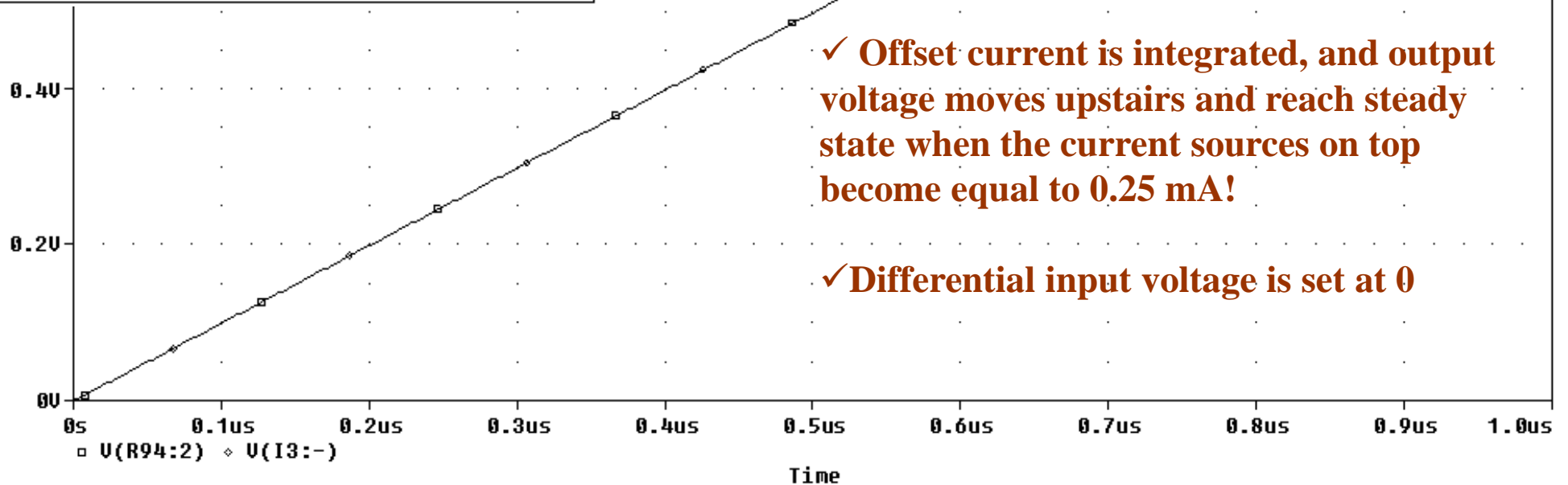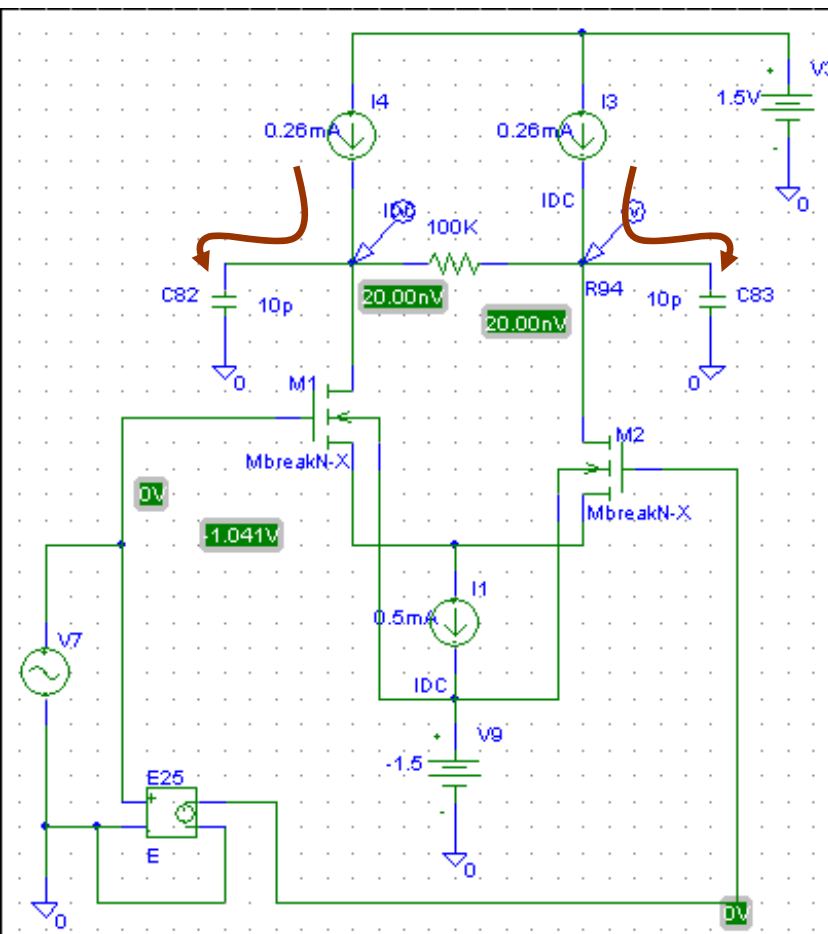
# Operational Amplifiers: Characterization



✓ Offset current is integrated, and output voltage moves upstairs and reach steady state when the current sources on top become equal to 0.25 mA!

✓ Differential input voltage is set at 0
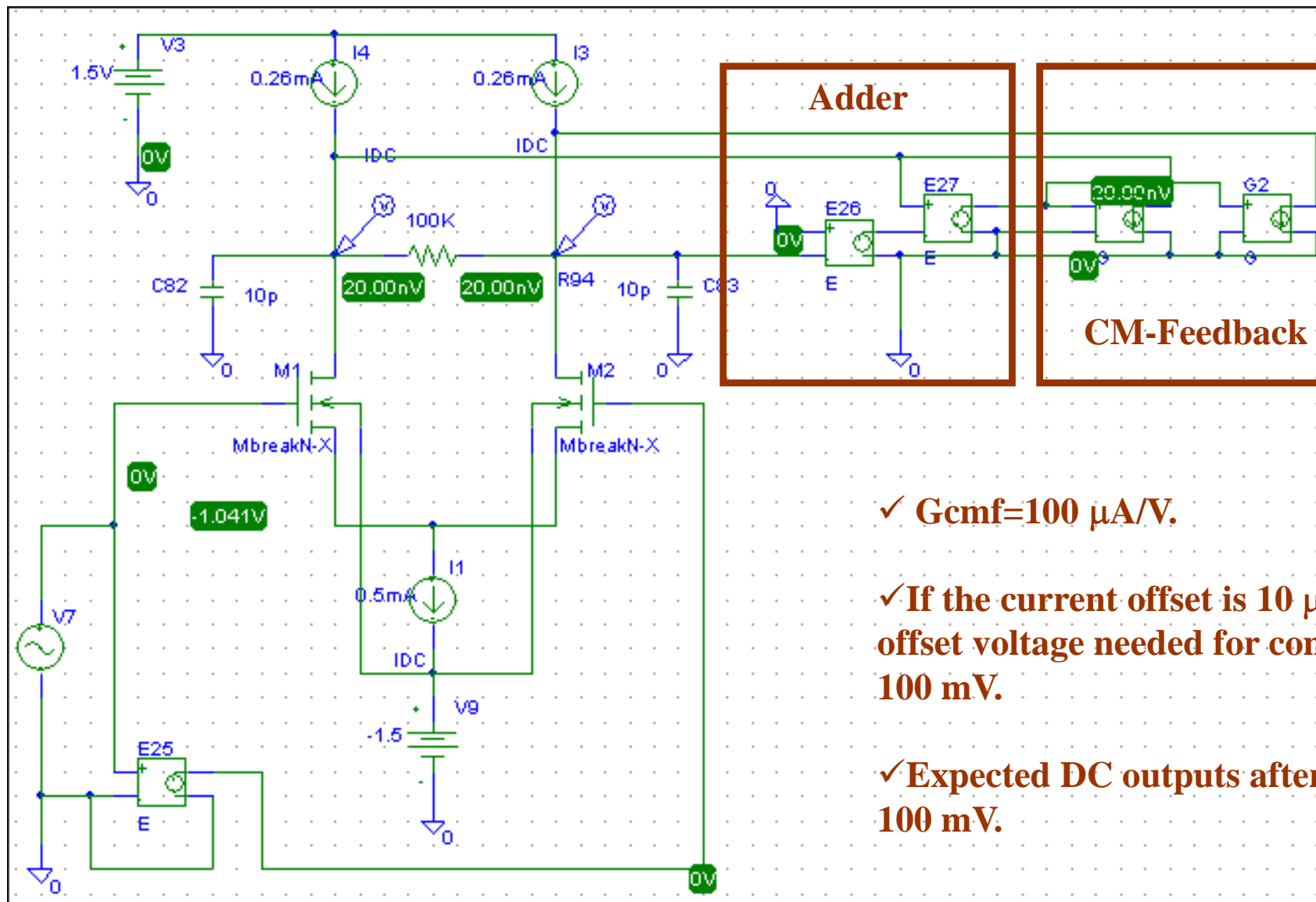
# Fully-Differential Amplifiers: Common-mode Feedback




✓  $G_{cmf} = 100 \mu\text{A/V}$ .

✓ If the current offset is  $10 \mu\text{A}$ , then the offset voltage needed for compensation is 100 mV.

✓ Expected DC outputs after settling are 100 mV.
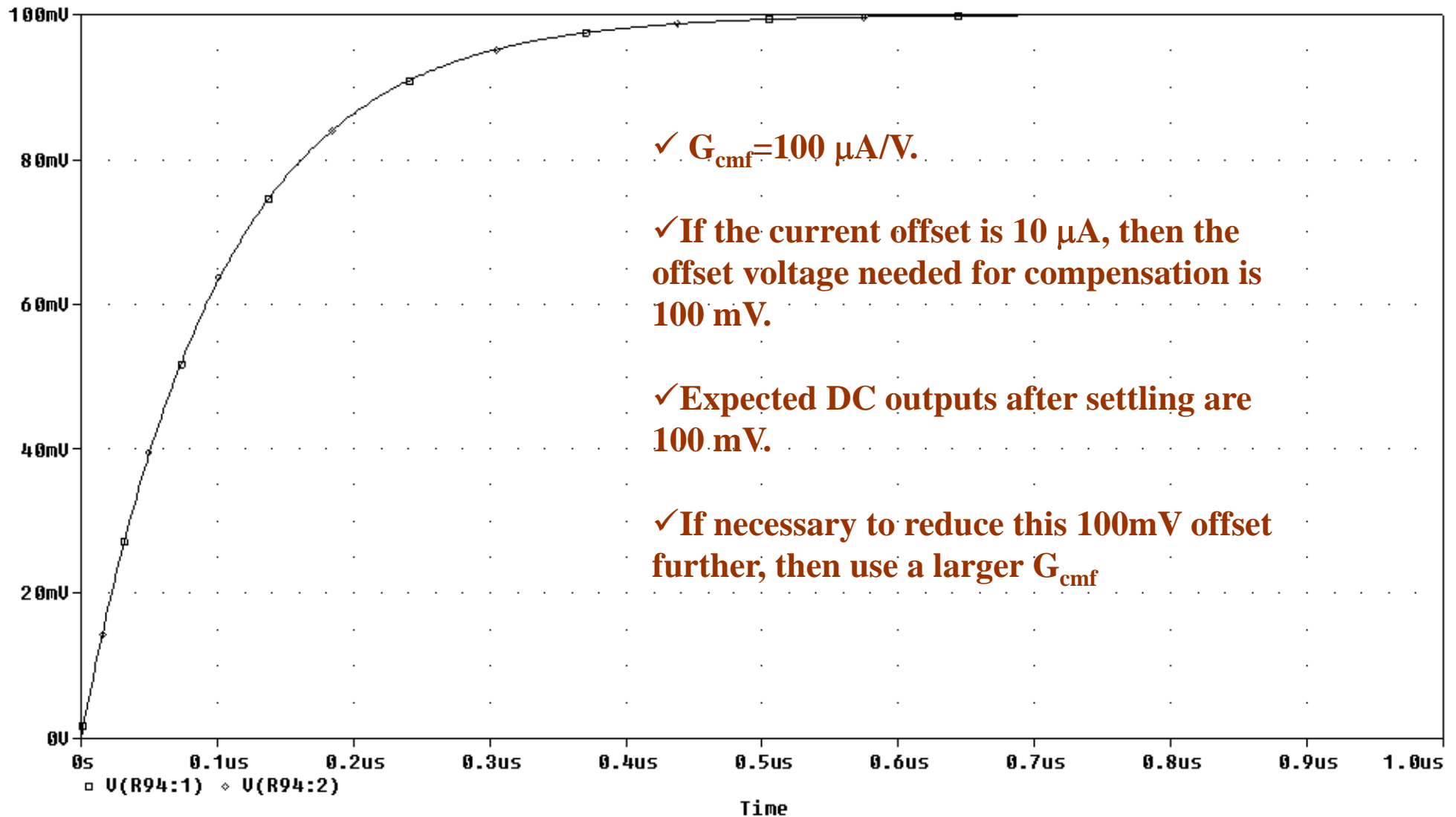
## Fully-Differential Amplifiers: Common-mode Feedback



# Agenda

---


- Fully differential circuits
- Common-mode feedback circuits
- Multi-OTA stages CMFB
- OTA-C filter w/ CMFB example

## What is a common-mode feed-back correction circuit ?


A common mode **feed-back** circuit is a circuit sensing the common-mode voltage, comparing it with a proper reference, and feeding back the correcting common-mode signal (both nodes of the fully-differential circuit) with the purpose to cancel the output common-mode current component, and to fix the dc outputs to the desired level.


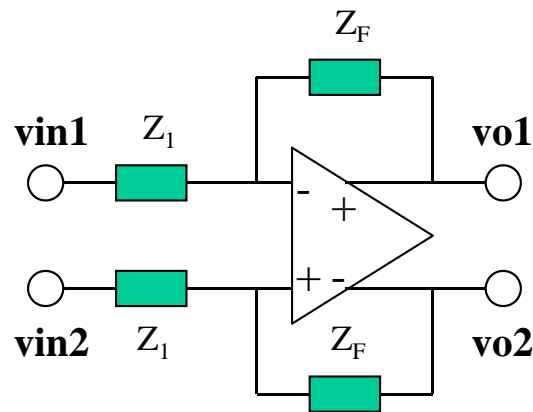
## Fully-Differential Amplifiers: CMFB Principle



Simplest common-mode detector

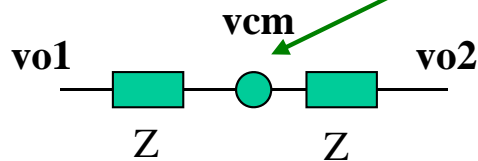


$$v_{cm} = \frac{v_{o1} + v_{o2}}{2}$$

- A common-mode feedback loop must be used: Circuit must operate on the common-mode signals only!
- BASIC IDEA: CMFB is a circuit with very small impedance for the common-mode signals but transparent for the differential signals.
- Use a common-mode detector (eliminates the effect of differential signals and detect common-mode signals)
- Analyze the common-mode feedback loop: Large transconductance gain and enough phase margin
- Minimum power consumption


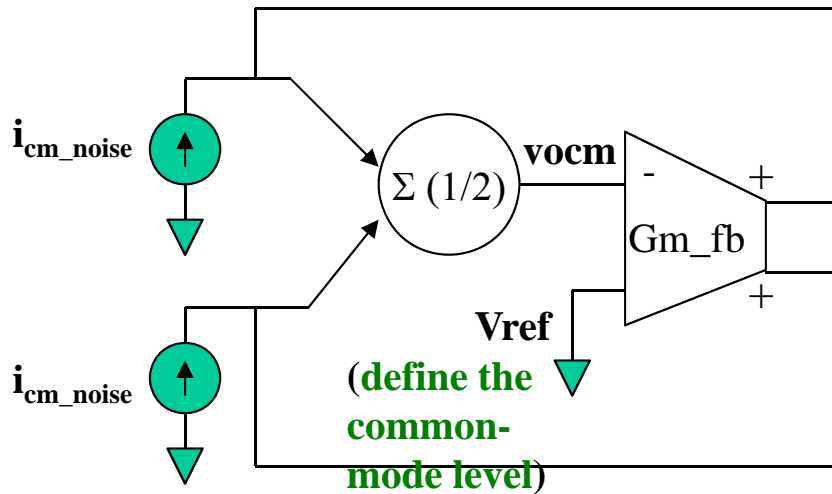
## CMFB Principles: Analysis of the loop for common-mode signals only




- Analysis for common-mode noise; for instance noise due to power supplies:
- $i_{o1} = i_{o2} = i_{cm\_noise}$

➤ **The two outputs can be connected together for the analysis of the CMFB loop!**

### ➤ BASIC CONCEPTS:

- The common-mode input noise is converted into a common-mode voltage (common-mode voltage noise) by the common-mode transconductance of the CMFB  $= 1/G_{m\_fb}$ .

### ↓ Effect of common-mode noise:

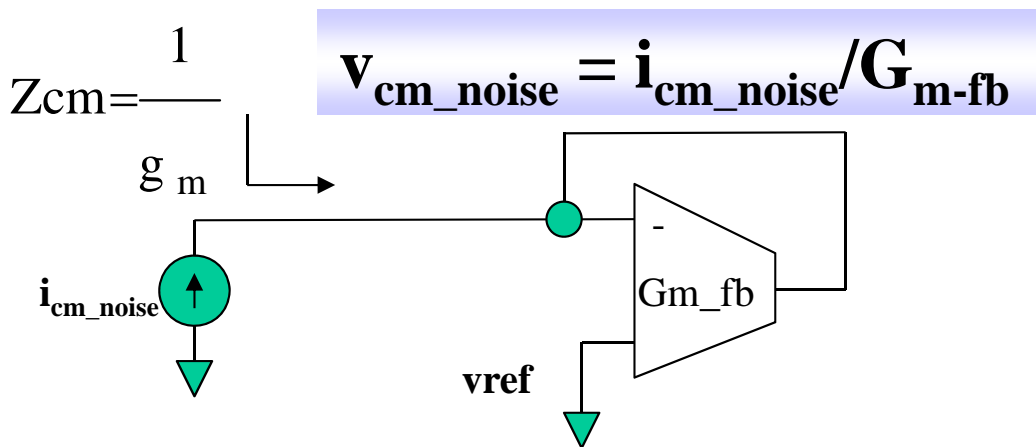


### ➤ common-mode voltage variations

$$v_{cm\_noise} = i_{cm\_noise} / G_{m\_fb} !!$$

- **The larger  $G_{m\_fb}$  the smaller the effects of the common-mode noise!**



# Fully-Differential Amplifiers: CMFB

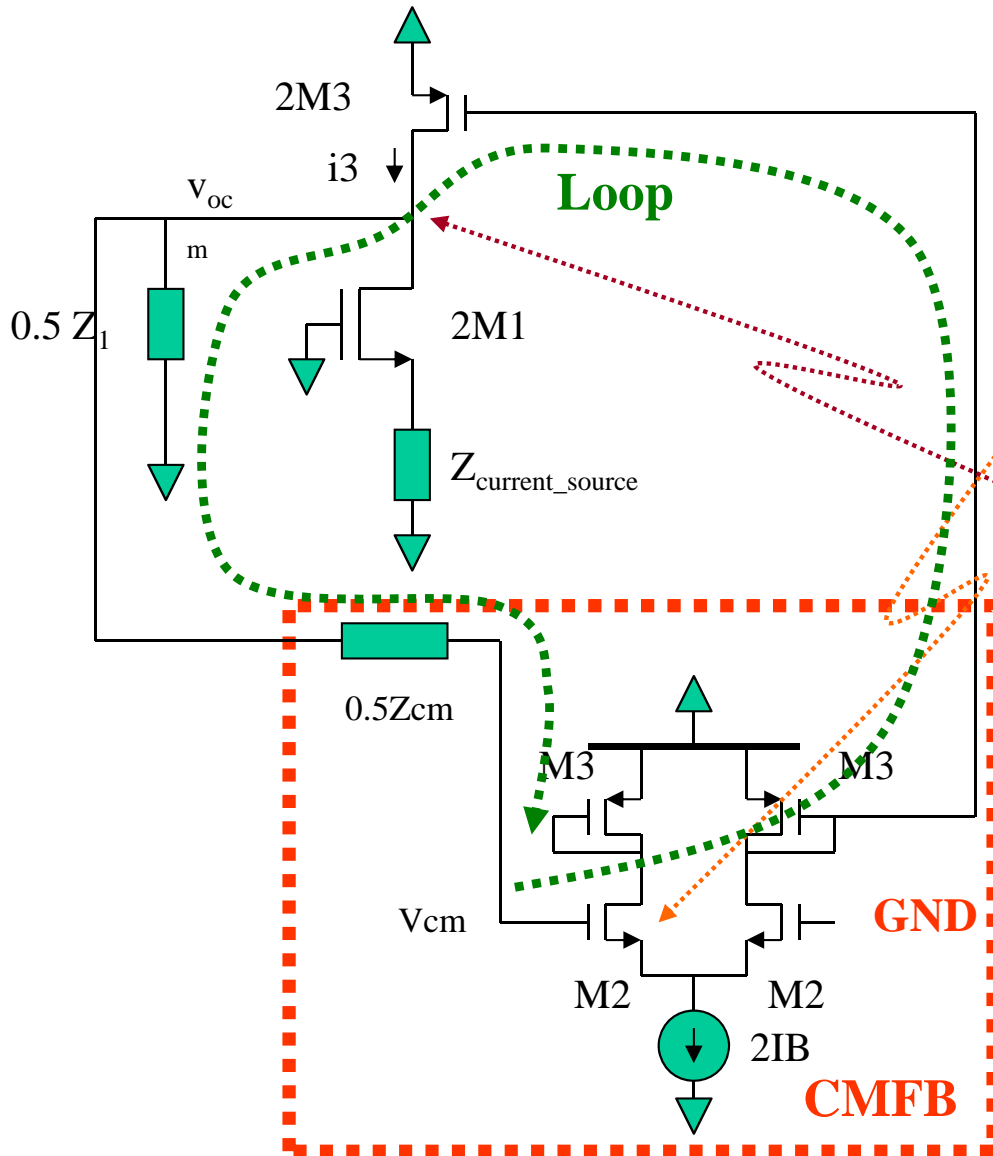

➤ **CMFB Characteristics:**

➤ DC Transconductance gain =  $g_{m2}/2$

➤ Loop gain (ignoring poles)

$$\approx \left(\frac{g_{m2}}{2}\right) \left(\frac{1}{g_{m3}}\right) (-2g_{m3}) \left(\frac{Z_1}{2}\right) = -\frac{g_{m2}Z_1}{2}$$


➤ dominant pole at the output

➤ 3 additional poles in the loop

➤ **DC OFFSET IS AROUND  $2I_{off}/g_{m2}$**

# Fully-Differential Amplifiers: CMFB Principles


Can be removed for CMFB analysis

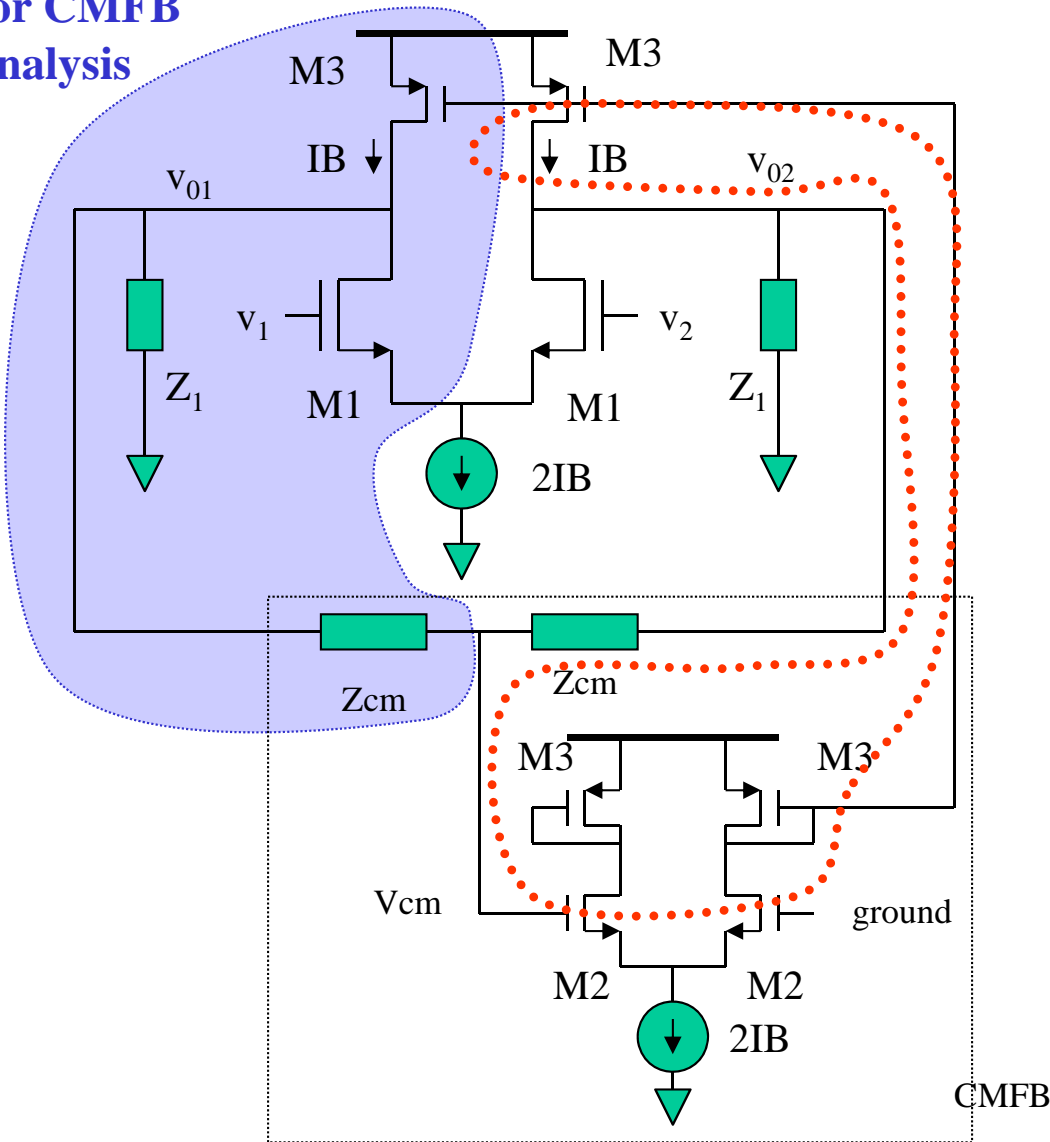


➤ Common-mode stability: DC gain and most relevant poles

- 1 pole at vcm ( $1/RC$ )
- 1 pole at M2 source ( $2g_{m2}/C_2$ )
- 1 pole at gate of M3 ( $g_{m3}/C_{P3}$ )
- 1 pole at the output ( $g_{o1}/C_1$ )

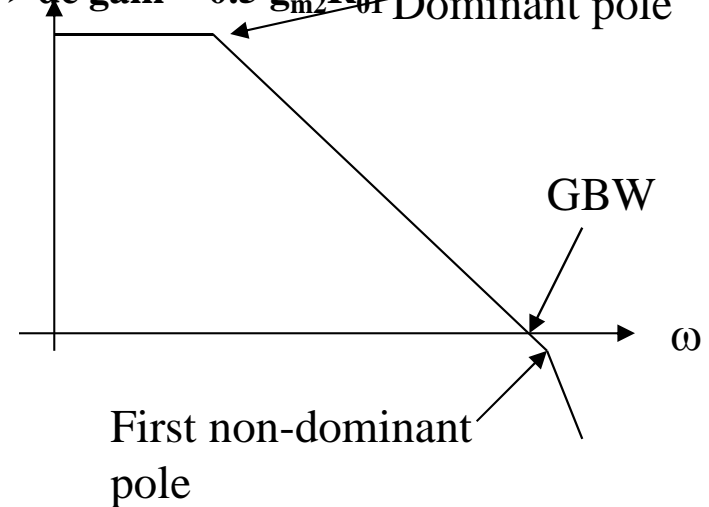➤ dc gain =  $0.5 g_{m2} R_{o1}$  Dominant pole




**Be sure phase margin > 45°**

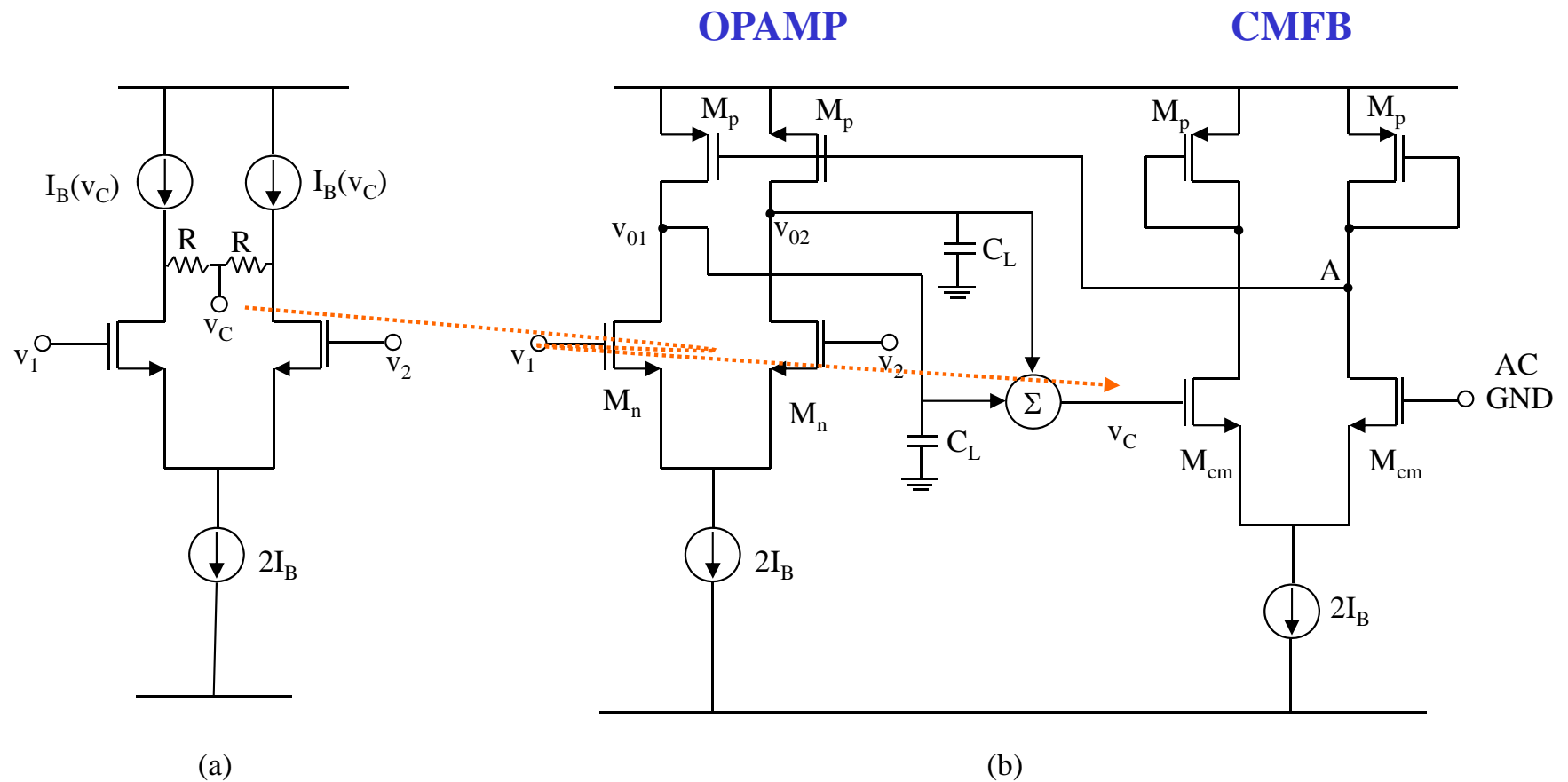

**Fig. 3 Common-mode feedback basic circuit concept. (a) Basic common-mode detector, (b) A CMOS CMFB Implementation.**

**Notice that the resistors R reduce the differential gain!**

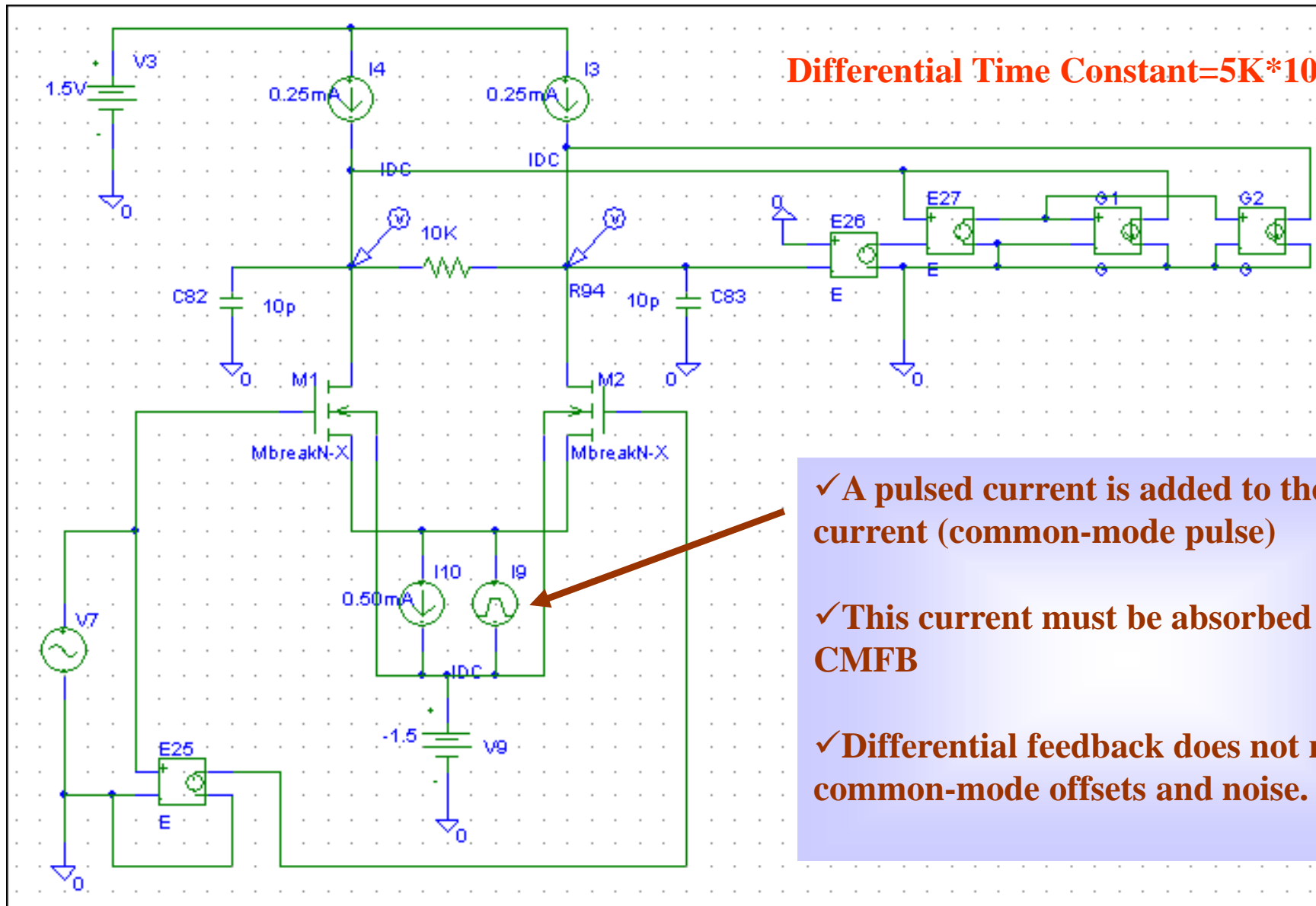
## Fully-Differential Amplifiers: Common-mode pulse



**Differential Time Constant =  $5K * 10P = 50nsecs$**

- ✓ A pulsed current is added to the tail current (common-mode pulse)
- ✓ This current must be absorbed by the CMFB
- ✓ Differential feedback does not reduce common-mode offsets and noise.

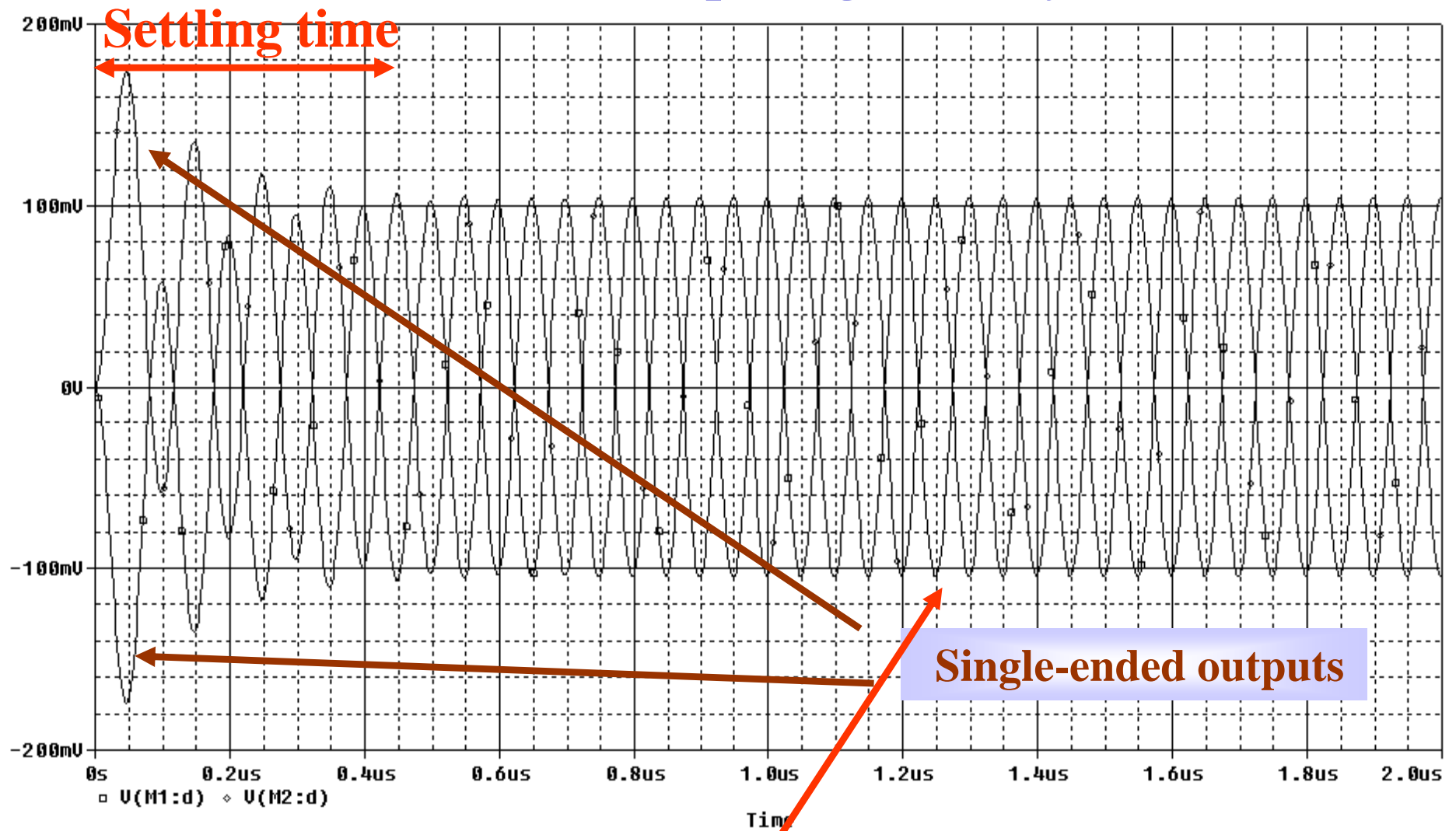
## Fully-Differential Amplifiers with CMFB Differential input signals only



Seems to be that the system is working fine, isn't it?

# Fully-Differential Amplifiers with CMFB
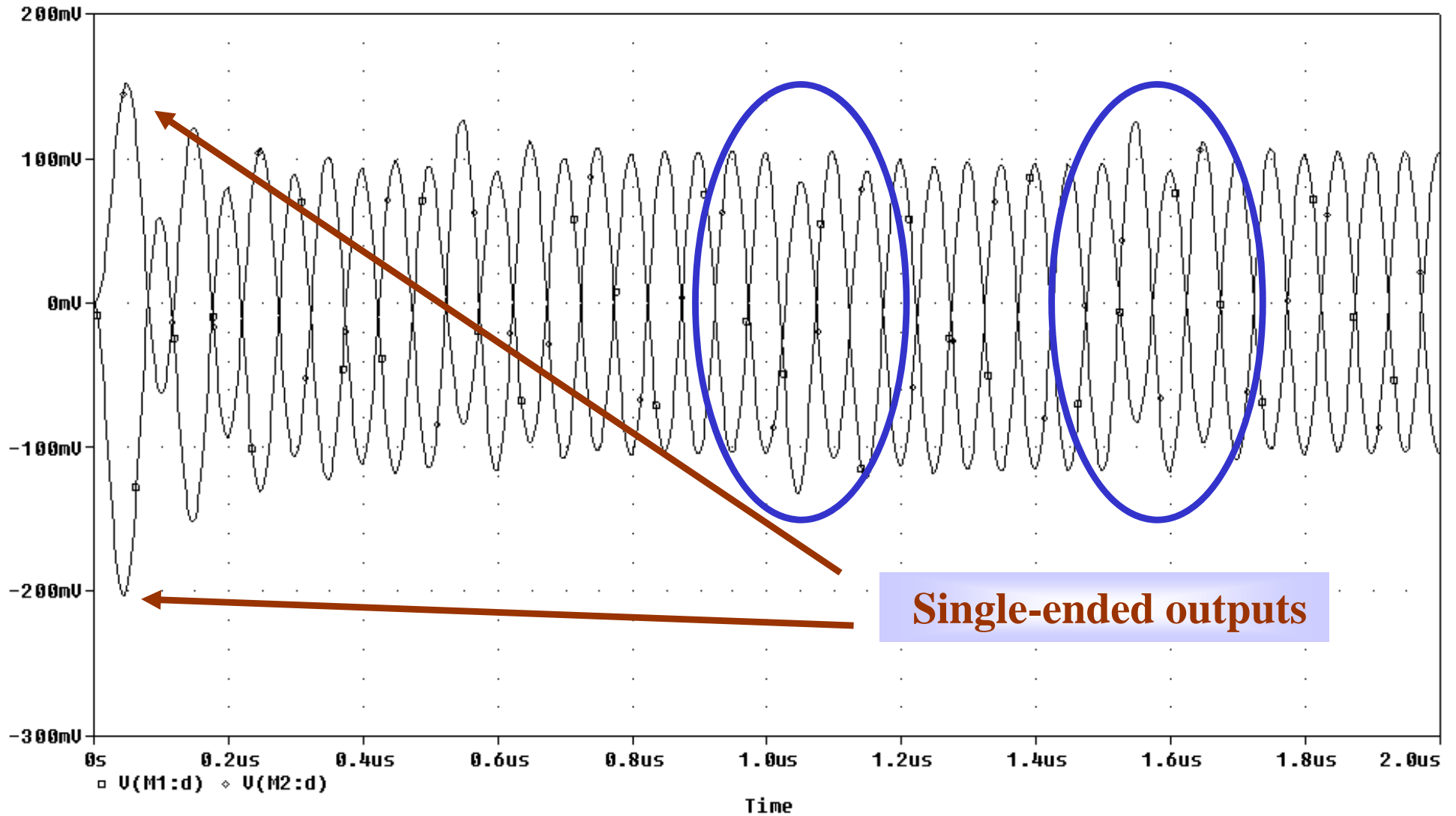
## Differential input signals + common-mode pulses






# Fully-Differential Amplifiers with CMFB


## Differential input signals + common-mode pulses
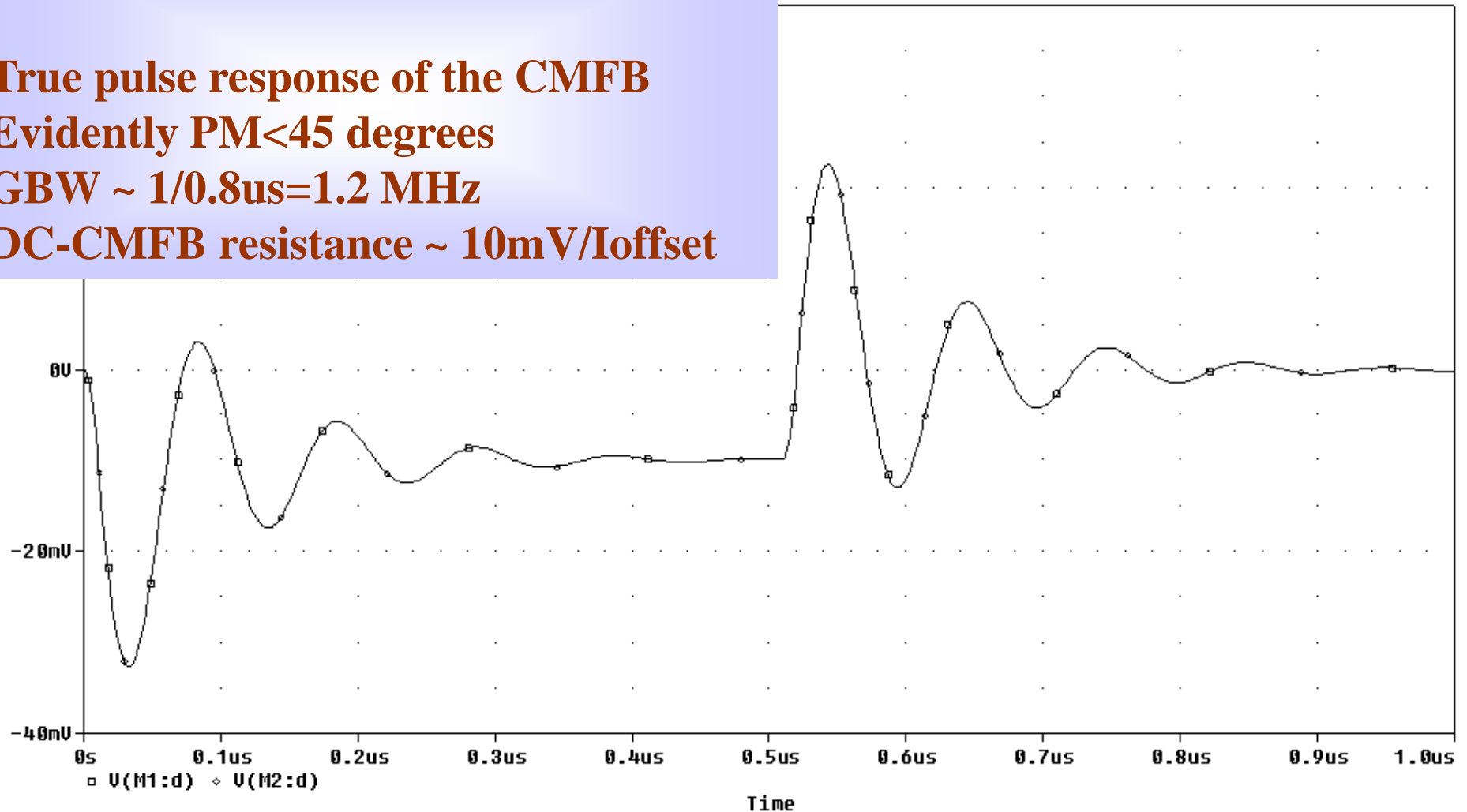
### Common-mode output


True pulse response of the CMFB  
Evidently  $PM < 45$  degrees  
 $GBW \sim 1/0.8\mu s = 1.2$  MHz  
DC-CMFB resistance  $\sim 10$  mV/Ioffset



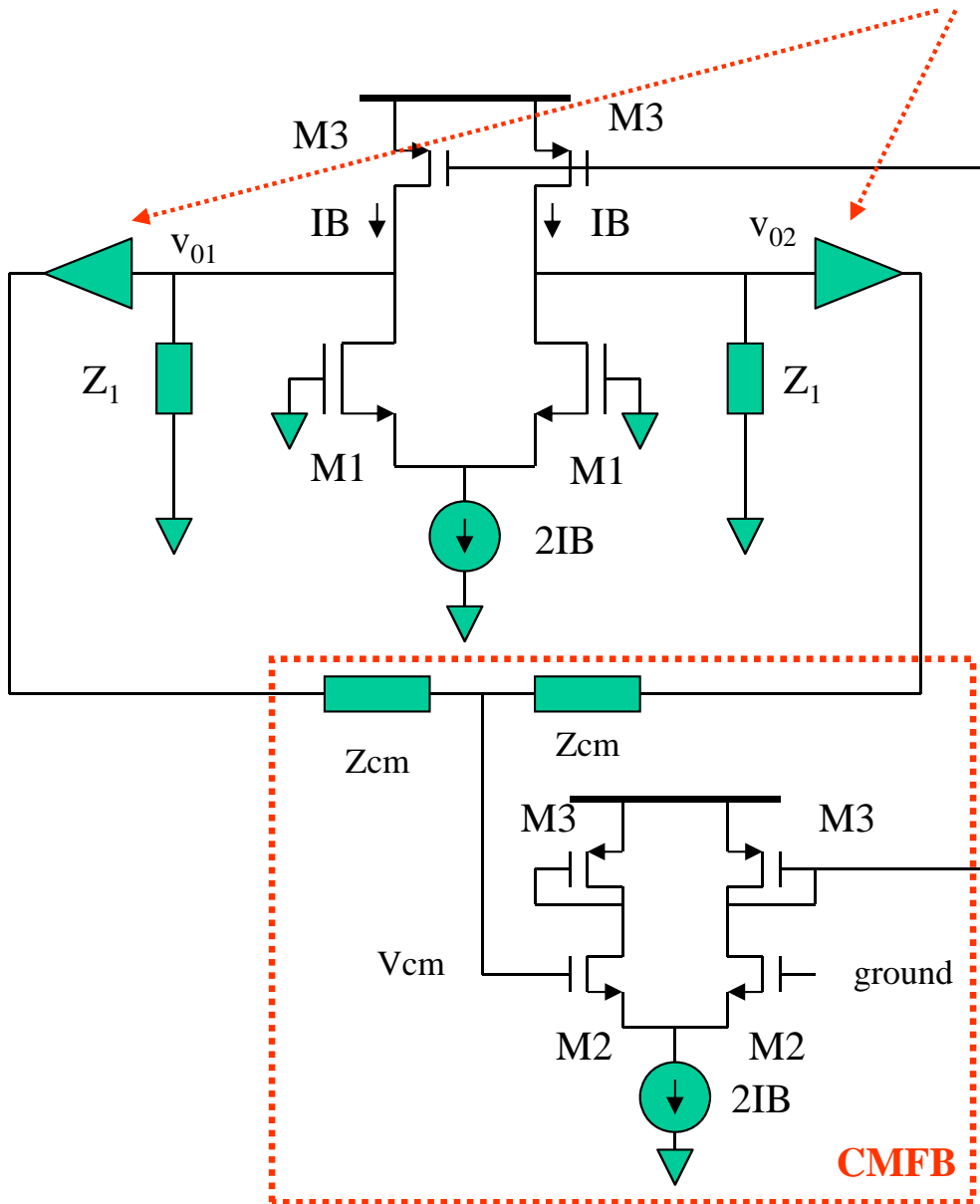
# Fully-Differential Filters: Adding buffers to handle the resistive CM-detector



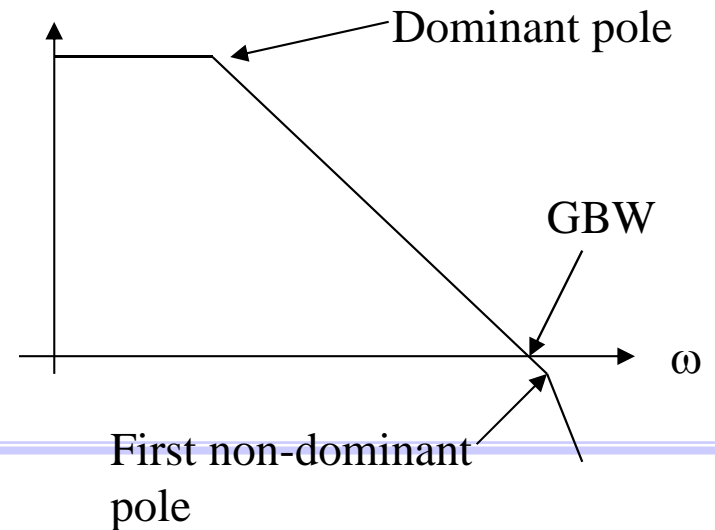- **The stability conditions are exactly the same for OTA's and OPAMP's:**
- 1 pole at vcm ( $1/RC$ )
- 1 pole at M2 source ( $2g_{m2}/C_2$ )
- 1 pole at gate of M3 ( $g_{m3}/C_{P3}$ )
- 1 pole at the output ( $g_{o1}/C_1$ )
- 1 pole at buffer output
- **In OPAMP's you can use resistors as common-mode detector due to the presence of the output buffers**
- dc gain =  $0.5g_{m2}R_{o1}$




# Isolated Common-Mode Sensing

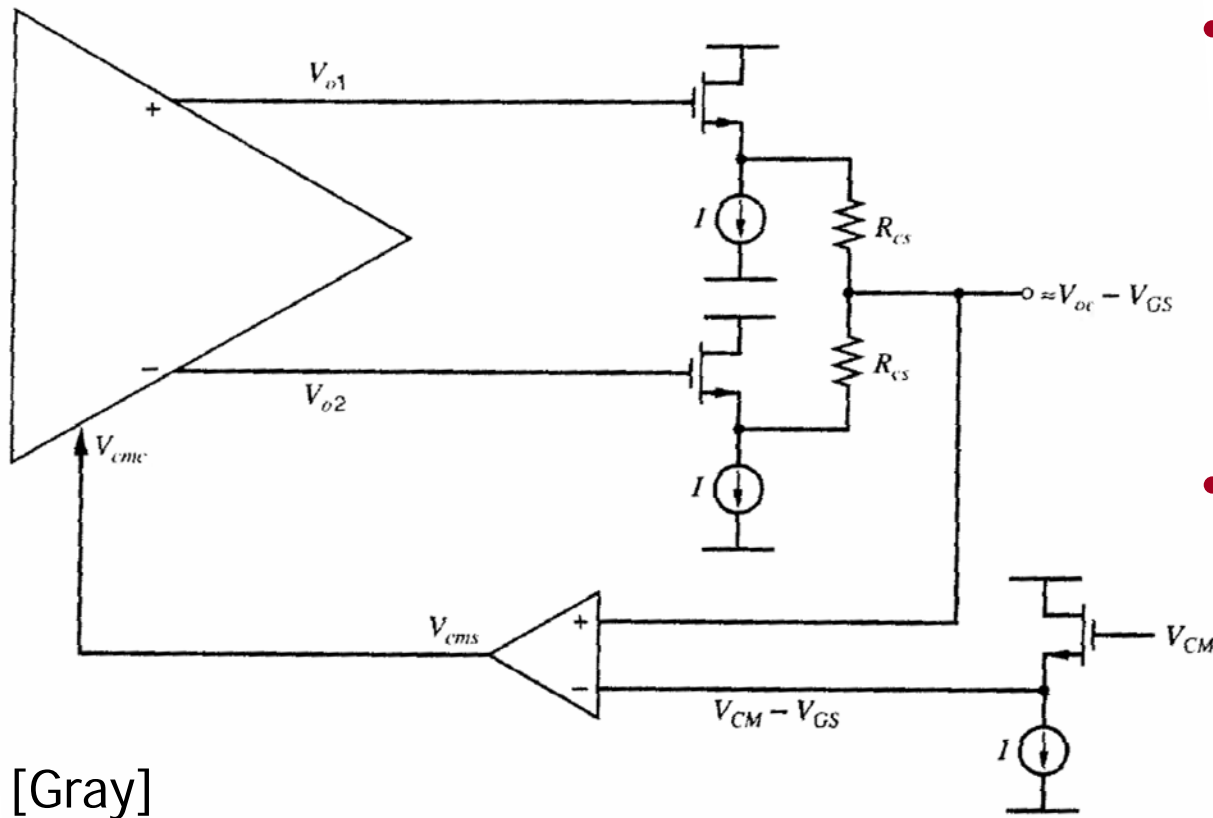

- Source-Followers isolate the loading of the common-mode sensor resistors
- Need to have a replica source follower to set the appropriate reference level for the CMFB amplifier

# Two Differential Pair CM Sensor

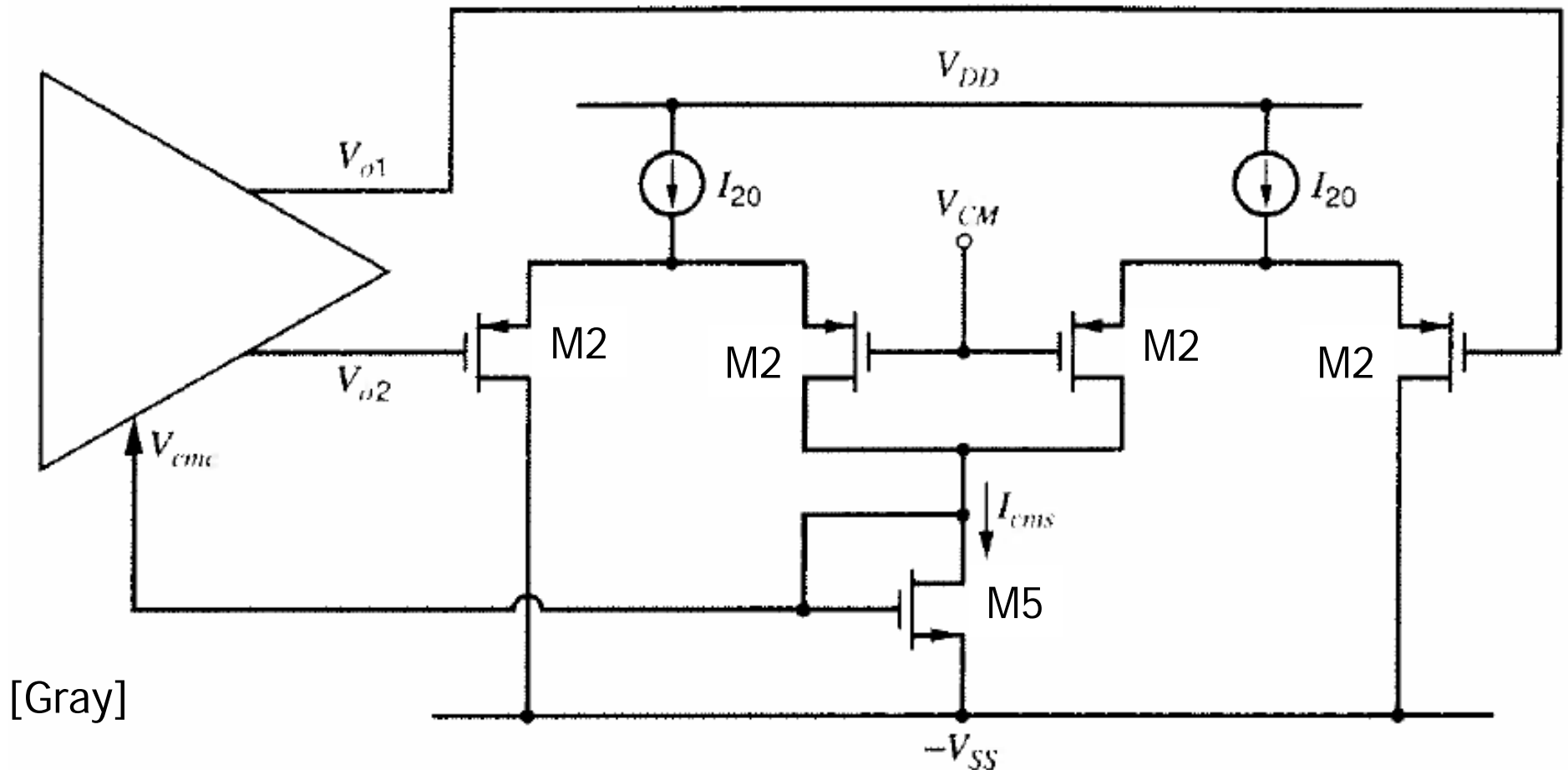

$$I_{cms} = I_{CM,DC} + I_{CM,AC} = I_{20} + g_{m2}(V_{oc} - V_{CM})$$

$$G_{cmf} = g_{m2}$$

$$V_{cmc} = V_{CM,DC} + \frac{g_{m2}}{g_{m5}}(V_{oc} - V_{CM})$$



# Agenda

---


- Fully differential circuits
- Common-mode feedback circuits
- Multi-OTA stages CMFB
- OTA-C filter w/ CMFB example
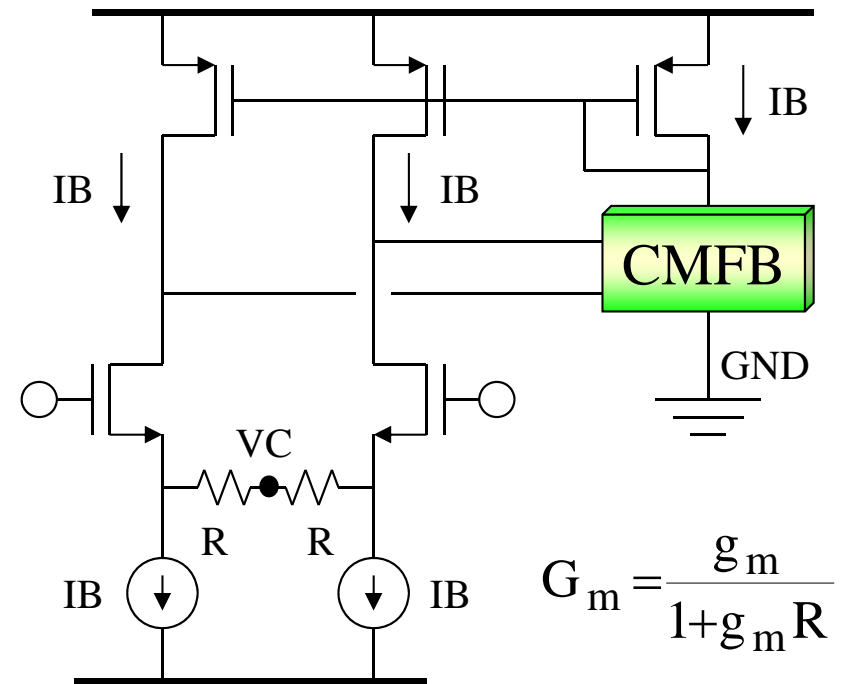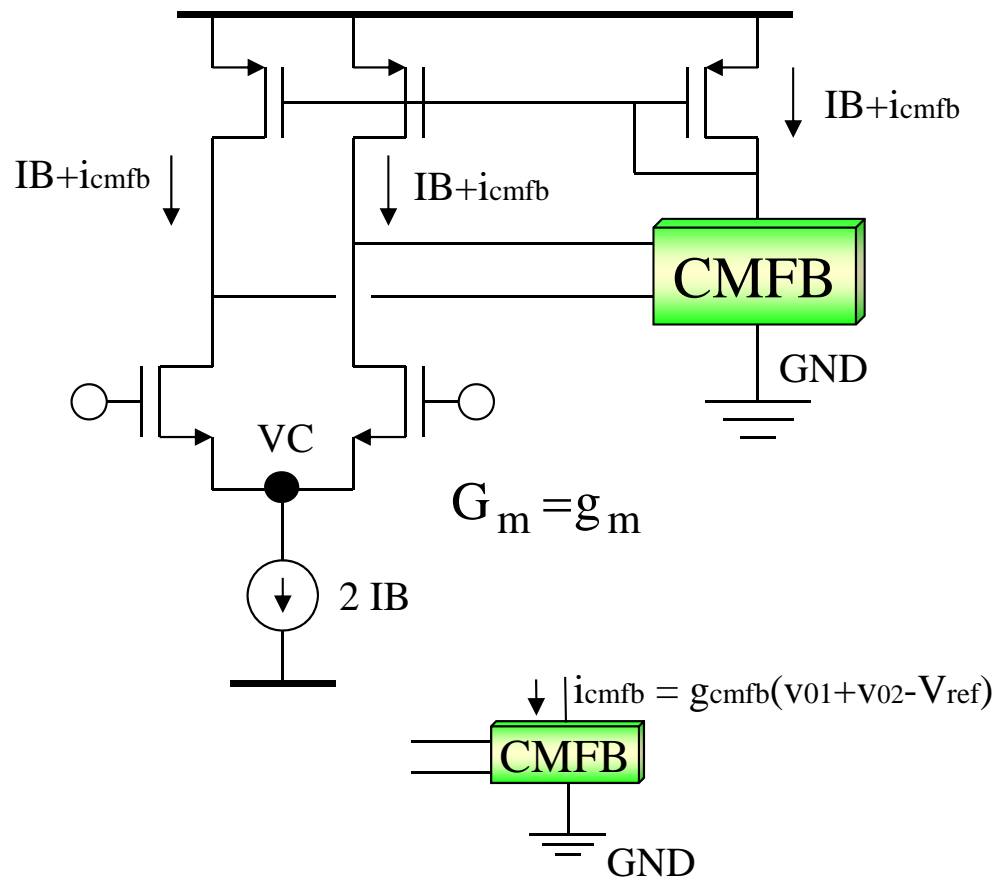
## CMFB is required for Differential Structures

CMFB Requirements: Fixes the OTA output (low offset) ==> High dc loop gain  
Reduction of common-mode noise ==> Large Bandwidth



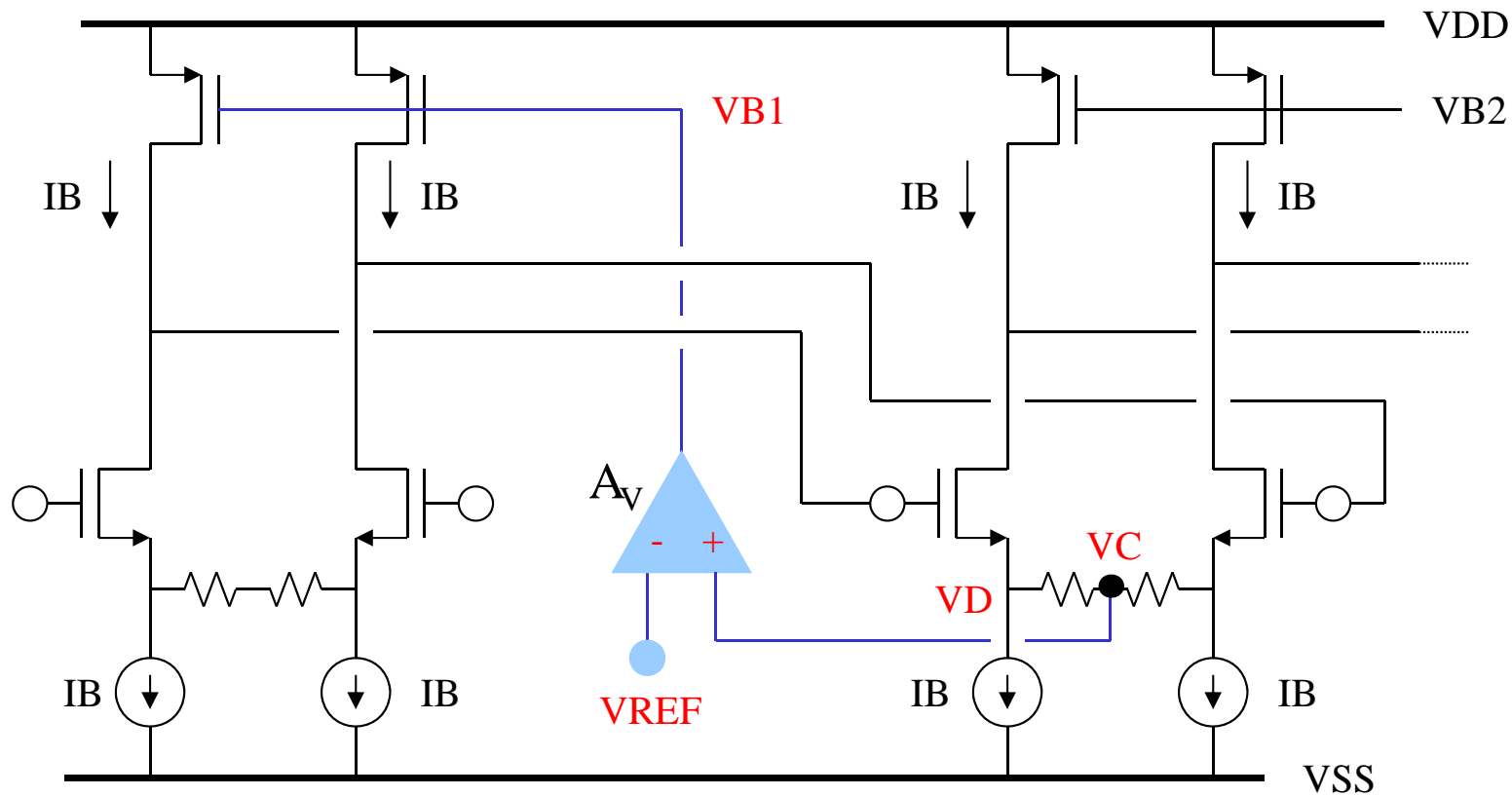
## Efficient CMFB for Differential Pair Based OTAs



**Common-mode loop gain =  $A_v G_{m_p} R_L$**

**4 poles in the CMFB loop. Loop stability requires  $A_v G_{m_p} / C_L < \omega_{p2} @ VC, \omega_{p3} @ VB1, \omega_{p4} @ VB2$**
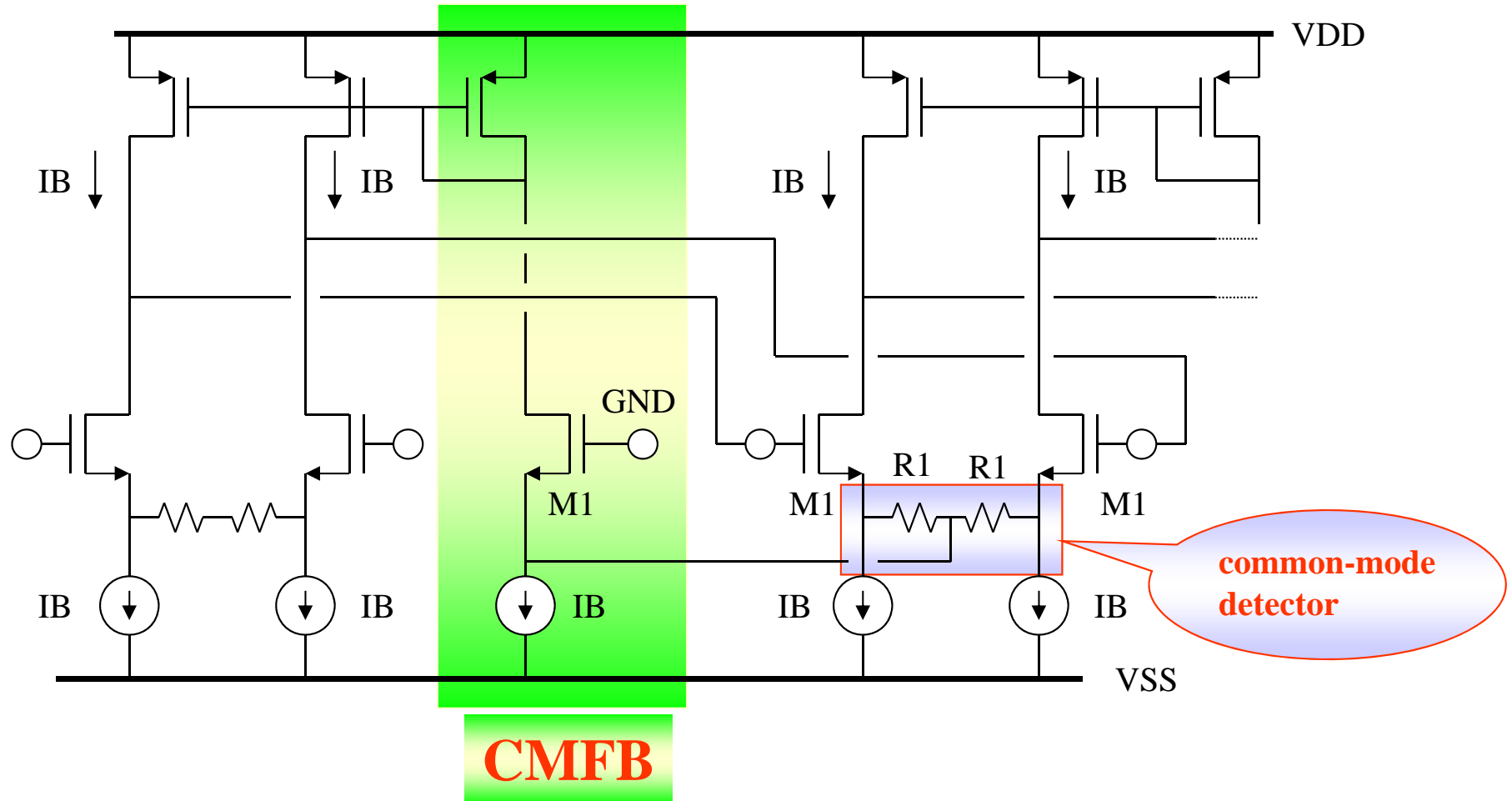
## Efficient CMFB for Pseudo-Differential OTAs






# Agenda

---


- Fully differential circuits
- Common-mode feedback circuits
- Multi-OTA stages CMFB
- OTA-C filter w/ CMFB example
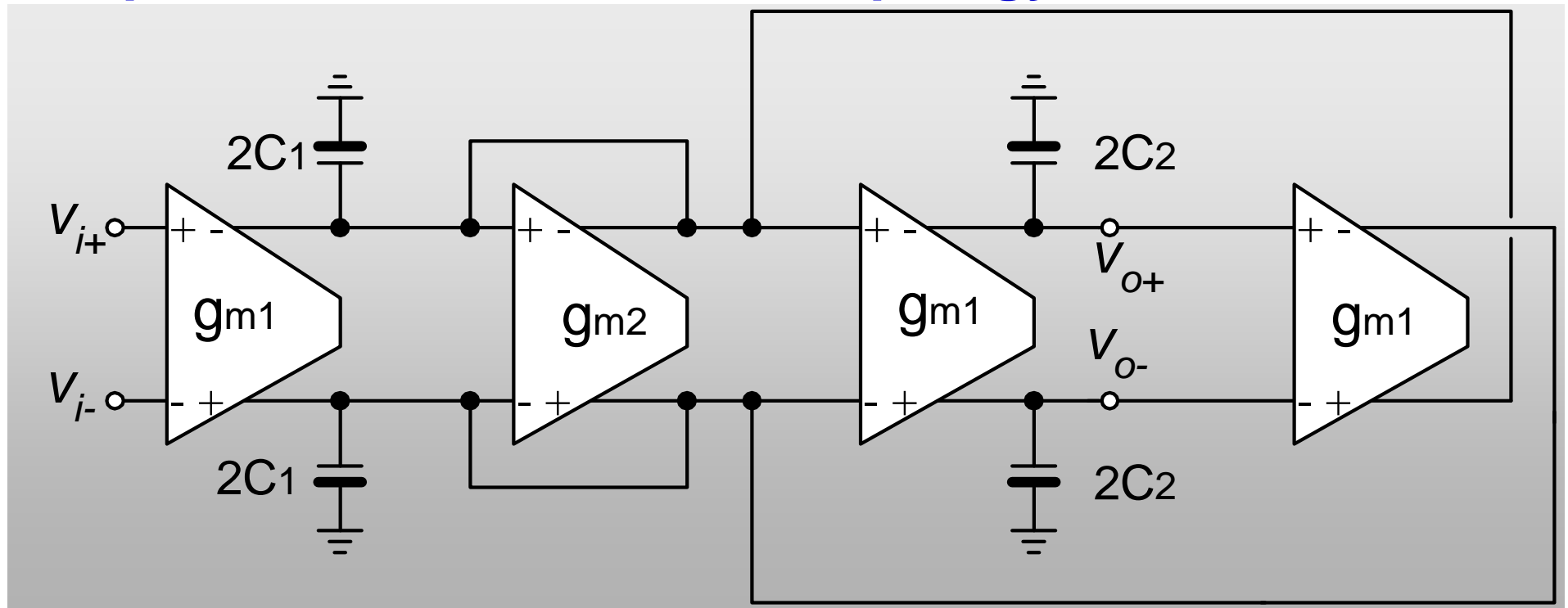
# Filter is based on Biquadratic Cells: Biquad Realization in Gm-C topology




	$f_0$ (MHz)	$G_{m1}$ (mA/V)	$G_{m2}$ (mA/V)
<b>Biquad 1</b>	<b>537.6</b>	<b>5.4</b>	<b>9.6</b>
<b>Biquad 2</b>	<b>793.2</b>	<b>5.4</b>	<b>5.07</b>
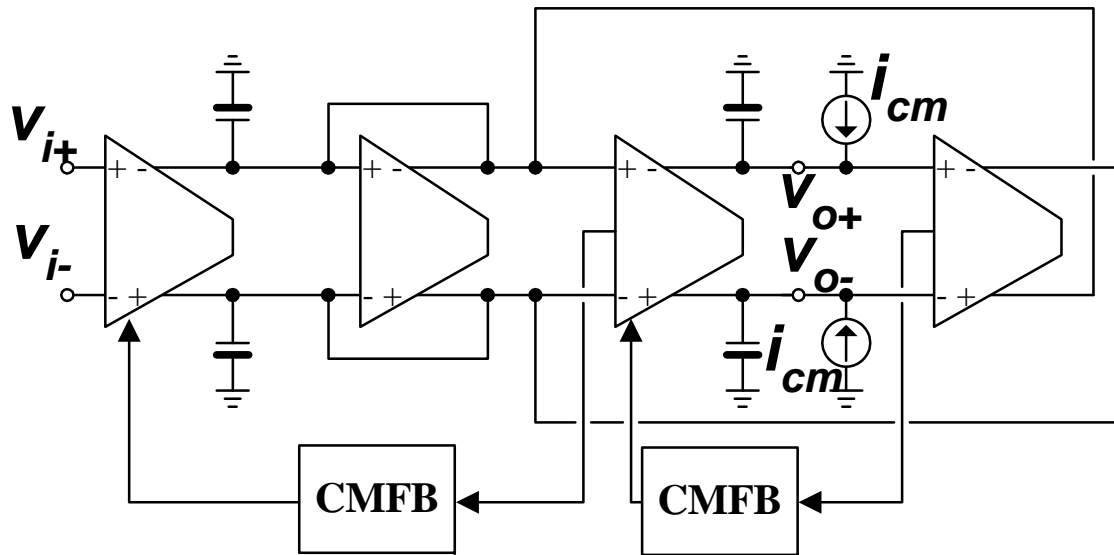
# Time Domain characterization of the CMFB




- Common-mode characterization using common-mode current pulses
- One CMFB circuit per pole

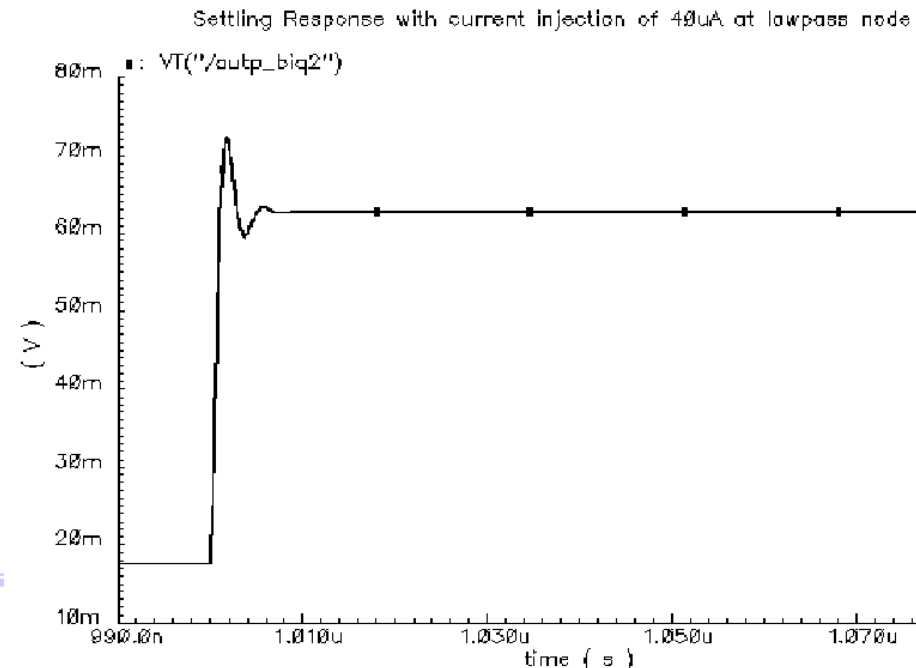- Pulse response of the CMFB
- Phase margin is better than 45 degrees


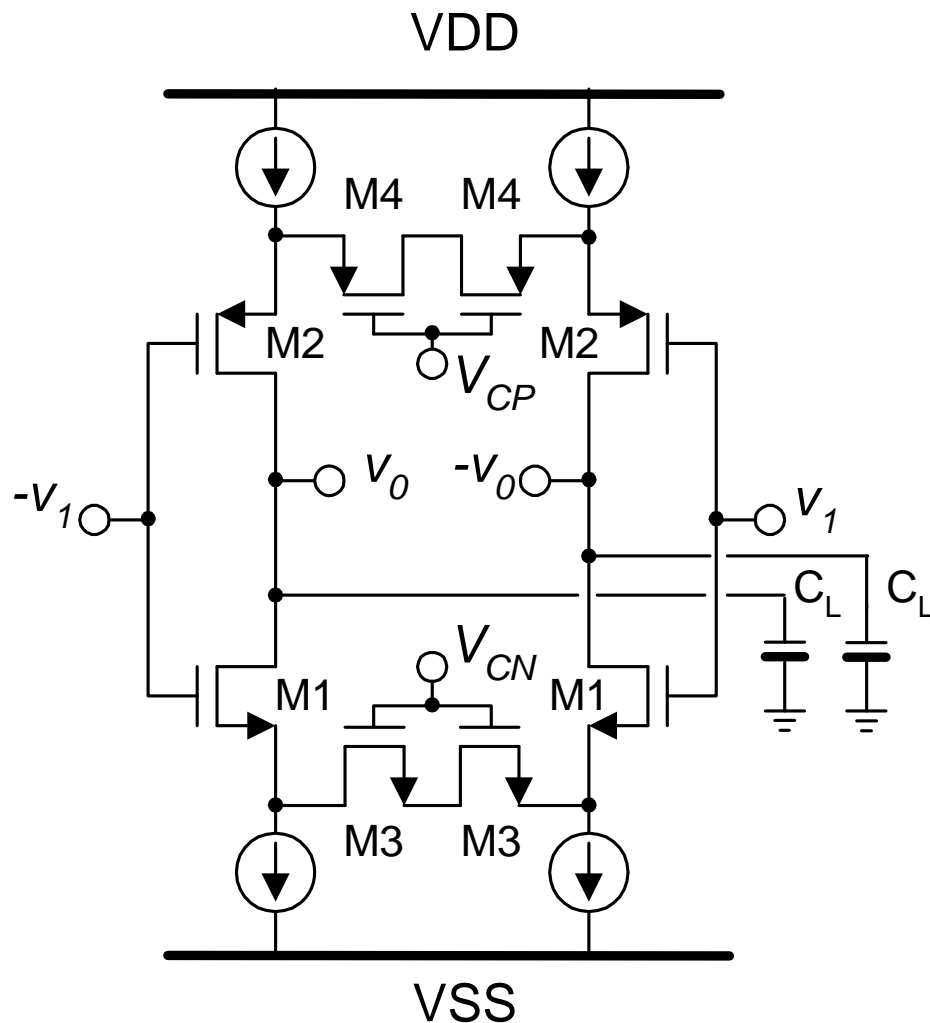
# OTA based on complementary differential pairs



- Efficient OTA based on linear complementary differential pairs

$$G_m = \frac{g_{m1}}{g_{m1}R_{M3} + 1} + \frac{g_{m2}}{g_{m2}R_{M2} + 1}$$

- Linear circuit due to source degeneration M3 and M4
- Suitable for fast applications


IEEE TRANSACTIONS ON CIRCUITS AND SYSTEMS—I: REGULAR PAPERS, VOL. 53, NO. 4, APRIL 2006

811

A CMOS 140-mW Fourth-Order Continuous-Time Low-Pass Filter Stabilized With a Class AB Common-Mode Feedback Operating at 550 MHz



Pankaj Pandey, Jose Silva-Martinez, and Xuemei Liu
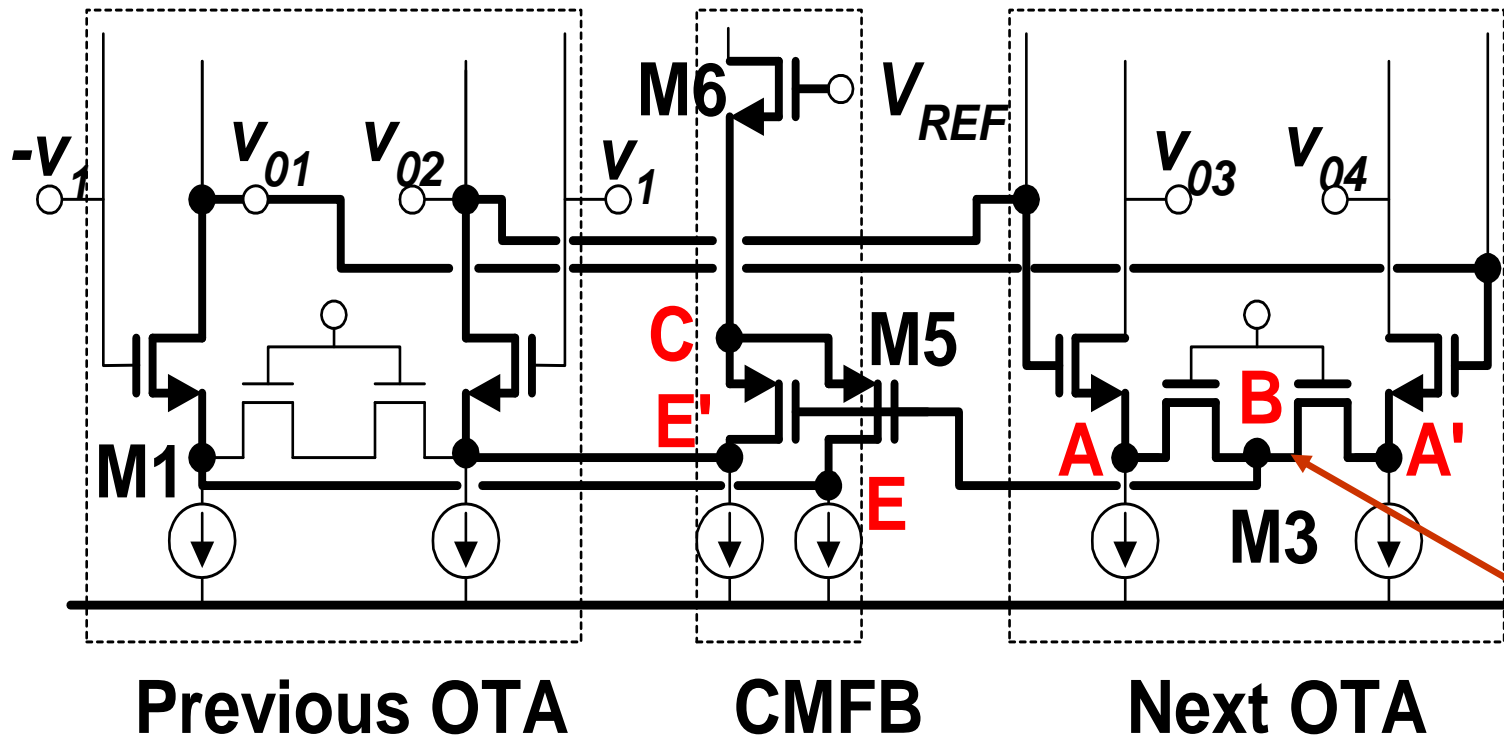
# Optimized Class AB Common-mode Feedback




- Class AB error amplifier is used
- 4 non-dominant poles at A~E
- 2 LHP zeros at A and C (Helpful in BW extension)
- Most important non-dominant pole at B
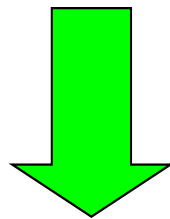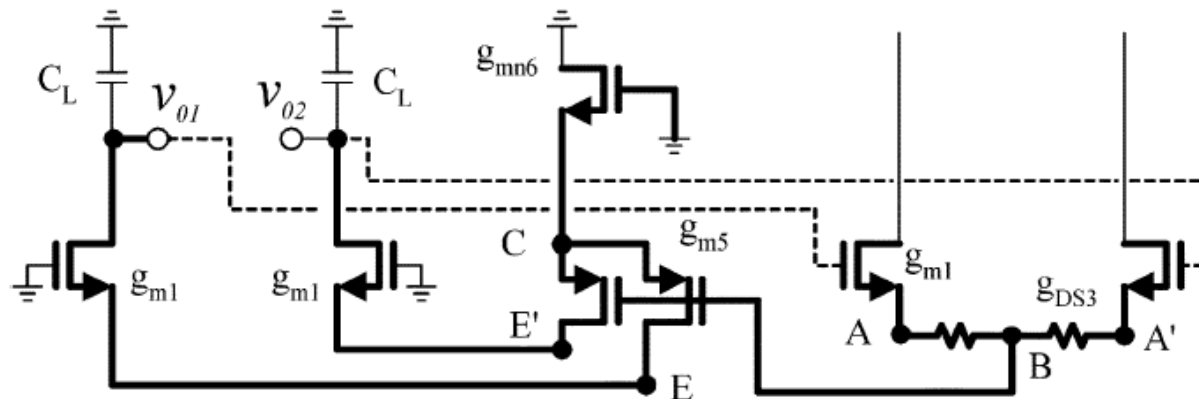
# Analysis of Class AB Common-mode Feedback



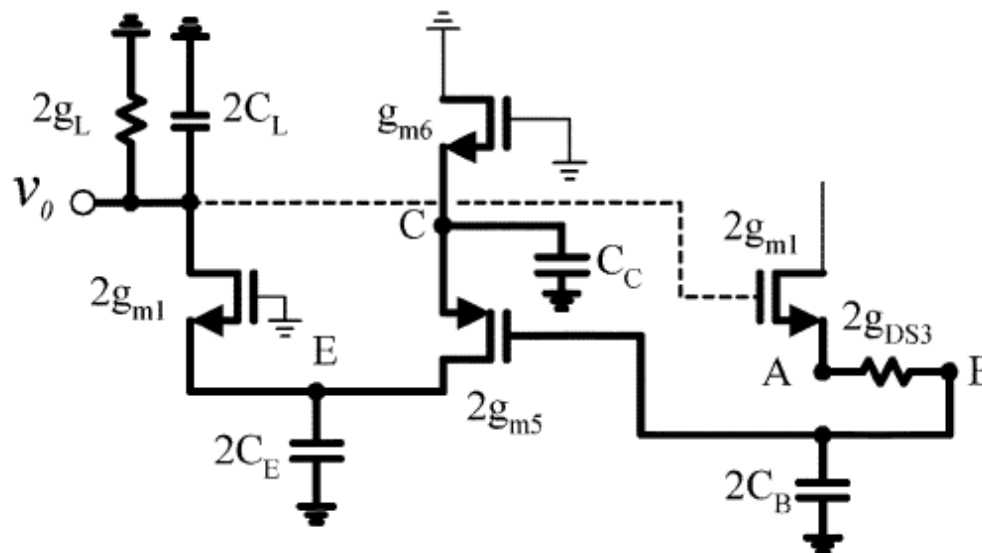CMFB can be simplified  
taking advantage of  
circuit's symmetry



# Class AB CMFB Analysis

$$A_{VCMFB} \cong \left( \frac{\frac{g_{m5}}{\left(1 + \frac{2g_{m5}}{g_{m6}}\right)g_L}}{\left(1 + \frac{sC_L}{g_L}\right)\left(1 + \frac{sC_B}{g_{03}}\right)\left(1 + \frac{sC_E}{g_{m1}}\right)} \right) \times \left( \frac{1 + \frac{sC_{gs1}}{g_{m1}}}{1 + \frac{sC_A}{g_{m1}}} \right) \left( \frac{1 + \frac{sC_C}{g_{m6}}}{1 + \frac{sC_C}{g_{m6} + 2g_{m5}}} \right)$$

$$\cong \left( \frac{\frac{g_{m5}}{\left(1 + \frac{2g_{m5}}{g_{m6}}\right)g_L}}{\left(1 + \frac{sC_L}{g_L}\right)\left(1 + \frac{sC_B}{g_{03}}\right)\left(1 + \frac{sC_E}{g_{m1}}\right)} \right)$$

- 2 pole-zero pairs (A and C) are very close to each other
- Allows for stable CMFB

---

## Remarks

- **DC operating points for high impedances are difficult to fix**
- **Fully differential amplifiers with high output impedance nodes must use common-mode feedback circuits .**
- **Common mode circuits can fix the DC operating points as well as minimize the common mode output components.**
- **Low voltage constraints impose optimal bias conditions at both the input and output ports of an amplifier.**
- **Common mode circuits for LV should be used both at the input and output**



# Next Time

---

- Output Stages