

ECEN474: (Analog) VLSI Circuit Design

Fall 2010

Lecture 24: OTA-C Filters



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

Announcements


- Project
 - Preliminary report due Nov 19
 - No layout
 - Focus is on good circuit design
- No Class on Monday 11/15

Agenda

- OTA-C Filters
- Material is related primarily to Project #3
- Full class on filters offered (458, 622)

OTA-C Filter Applications

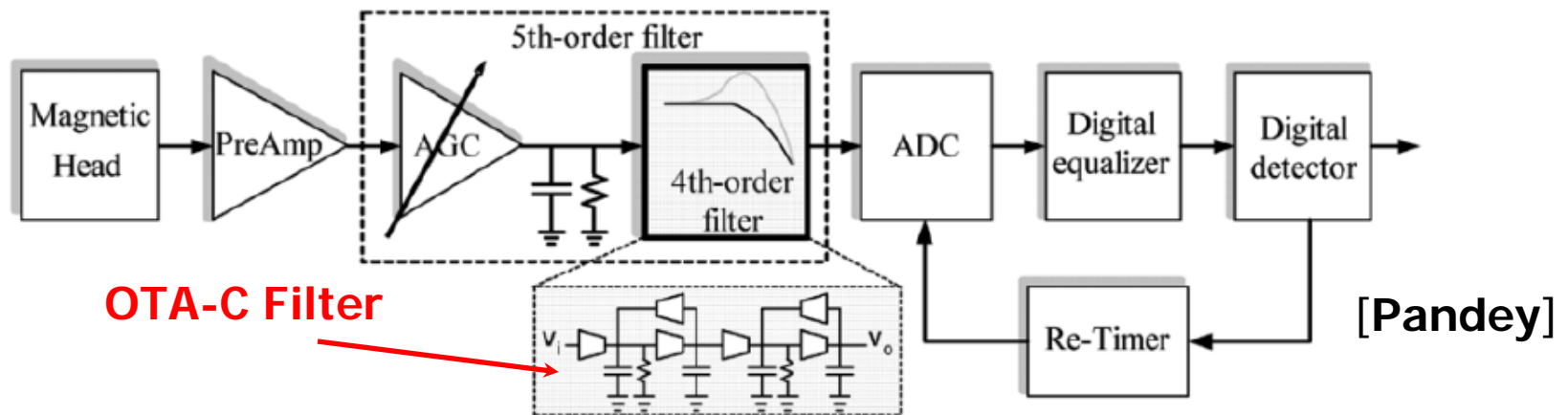
- Hard-disk drives require linear phase filters (>100MHz)
- RF systems require filters in the GHz range
- Wireless xcvrs intermediate frequency (IF) filters (>100MHz)
- Often used with variable gain amplifiers (VGAs) for automatic-gain control (AGC) to maximize dynamic range
- Low noise, low power, and high linearity are required



Hard-Disk Drive Receiver Front-End

OTA-Based Active Resistor

[Schaumann]






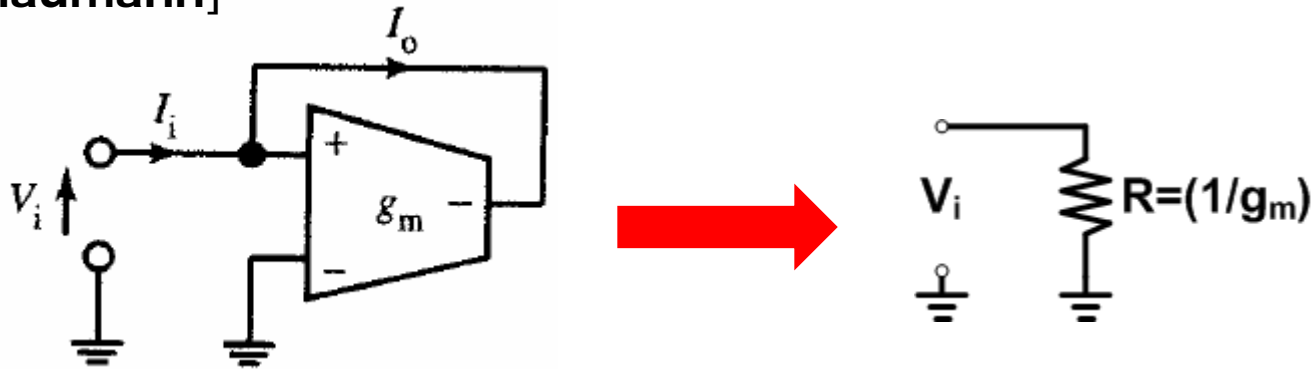


$$I_i = I_o = g_m V_i$$


$$R = \frac{V_i}{I_i} = \frac{1}{g_m}$$

OTA-Based Active Resistors

[Schaumann]

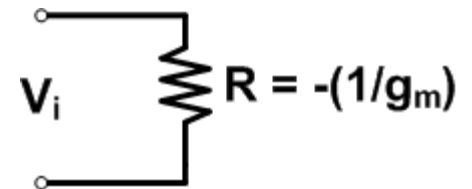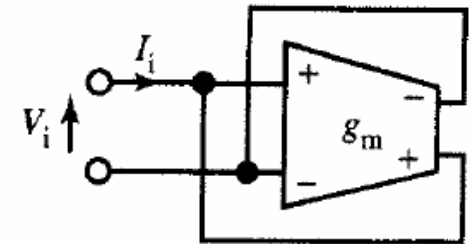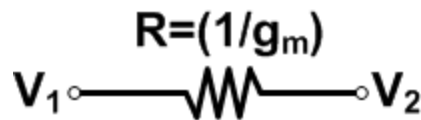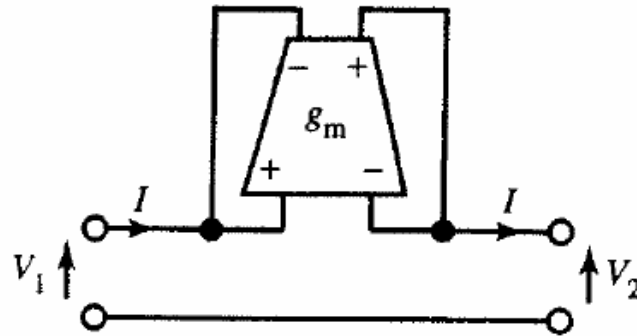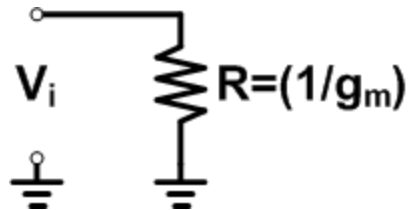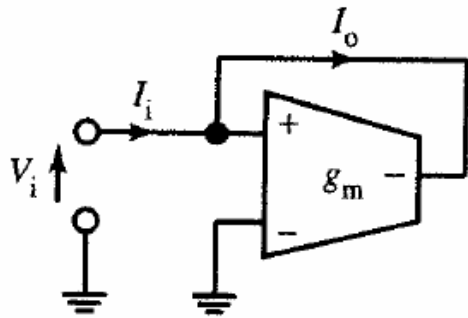


OTA-Based Integrator

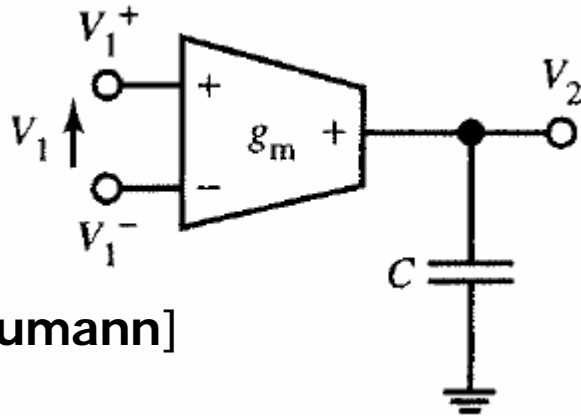

Ideally $\frac{V_2}{V_1} = \frac{g_m}{sC}$

[Schaumann]

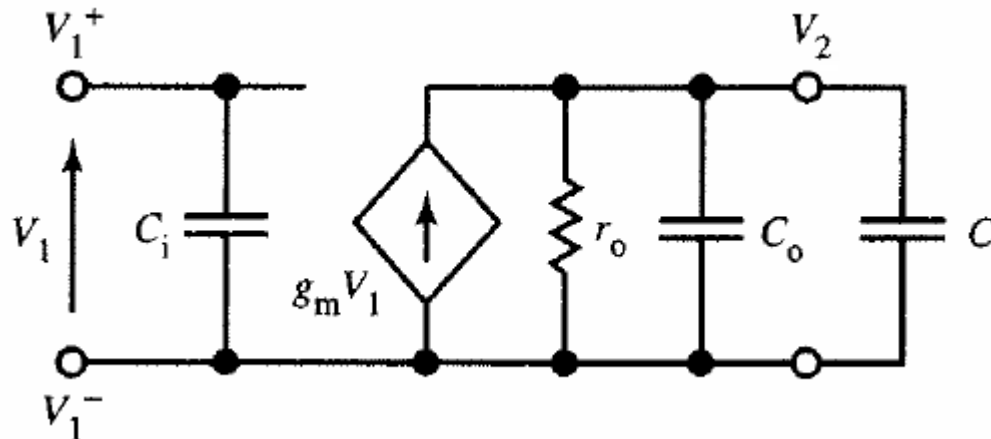
- Finite OTA r_o causes a non-zero pole
- OTA C_o reduces integration constant



$$\frac{V_2}{V_1} = \frac{g_m}{s(C + C_o) + g_o}$$

Lossy g_m -C Integrator (1st-Order LPF)

[Schaumann]

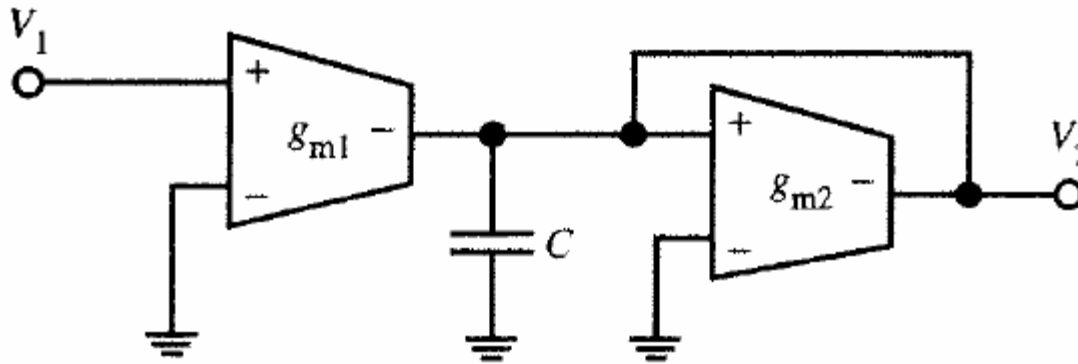


$$\text{Ideally } \frac{V_2}{V_1} = -\frac{g_{m1}}{sC + g_{m2}}$$


Considering finite OTA output resistance and non - zero input and output capacitance

$$\frac{V_2}{V_1} = -\frac{g_{m1}}{s(C + 2C_o + C_i) + g_{m2} + 2g_o}$$

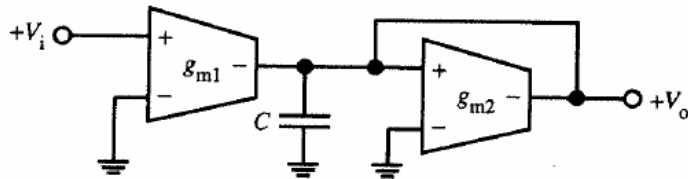Fully Differential Lossy g_m -C Integrator




- Pseudo-Differential

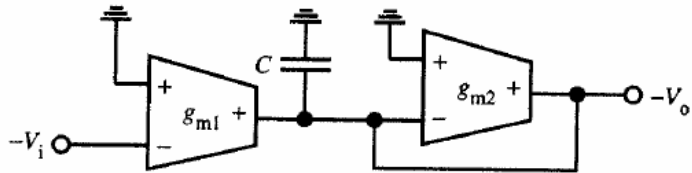


(a)

[Schaumann]

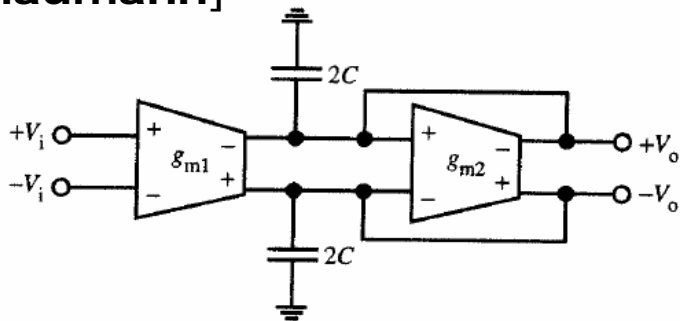

(b)

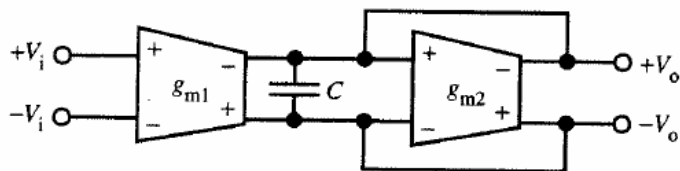- Fully Differential
 - $2C$ because full g_m current goes to each side




(c)

- Why just C here?

OTA-Based Inductor

[Schaumann]

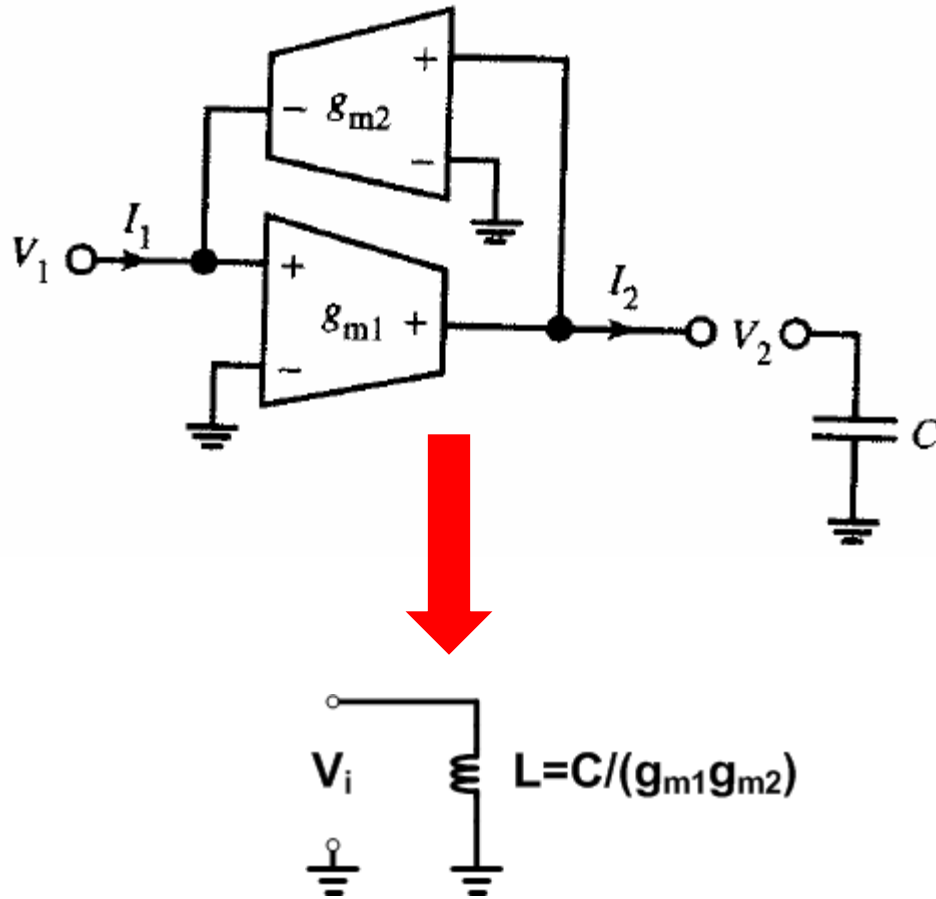

$$I_1 = g_{m2} V_2$$

$$I_2 = g_{m1} V_1$$

From these two equations

$$\frac{V_1}{I_1} = \frac{1}{g_{m1} g_{m2}} \frac{I_2}{V_2}$$

$$Z_1 = \frac{1}{g_{m1} g_{m2}} Y_2$$



If $Y_2 = sC$

$$Z_1 = \frac{sC}{g_{m1} g_{m2}} = sL_{eff}$$

$$L_{eff} = \frac{C}{g_{m1} g_{m2}}$$


Differential Grounded Inductor

[Schaumann]

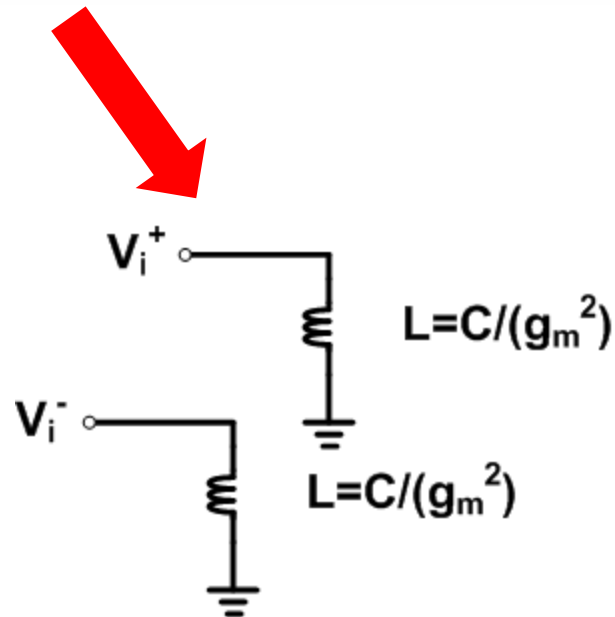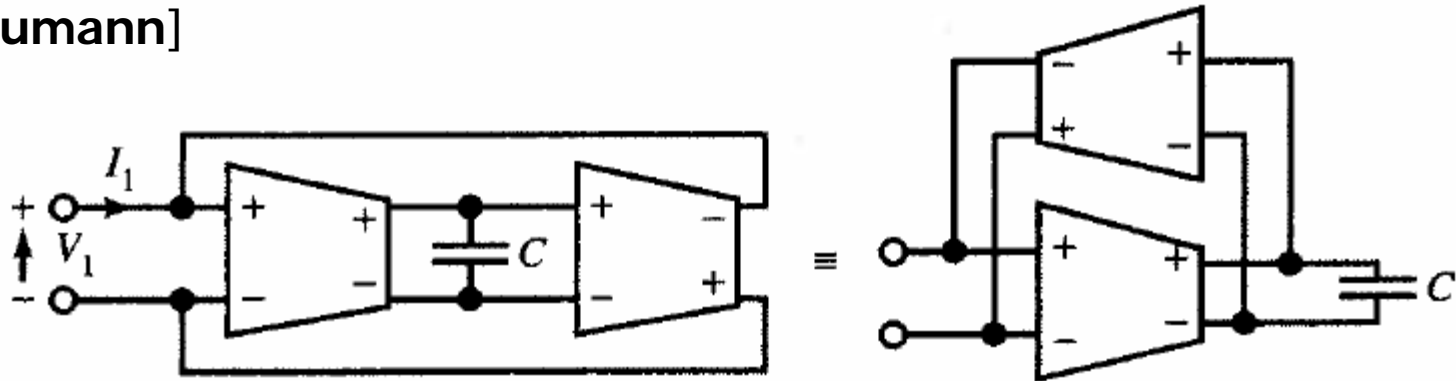


Second-Order Filter

[Silva]

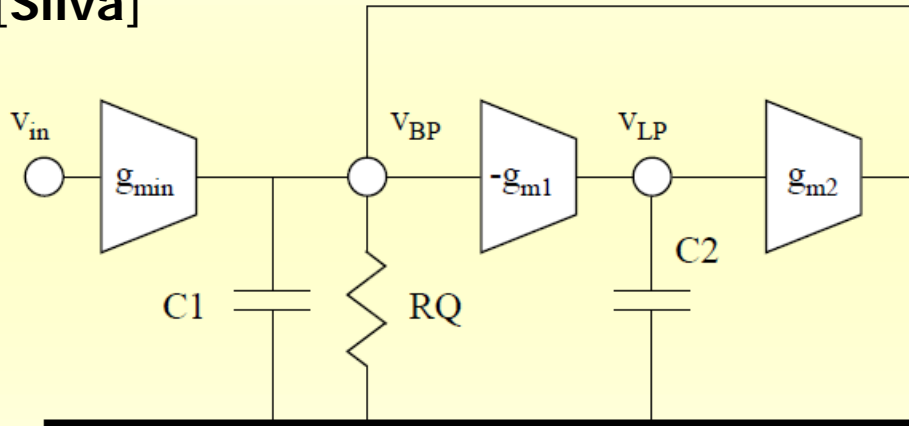

Continuous-time biquad

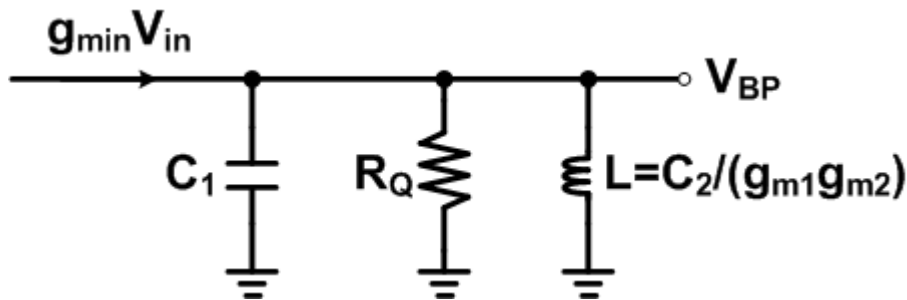

$$\frac{V_{BP}}{V_{in}} = \frac{s \left(\frac{g_{min}}{C_1} \right)}{s^2 + s \left(\frac{1}{R_Q C_1} \right) + \frac{g_{m1} g_{m2}}{C_1 C_2}} = \frac{s \left(\frac{g_{min}}{C_1} \right)}{s^2 + s \left(\frac{\omega_o}{Q} \right) + \omega_o^2}$$

$$\frac{V_{LP}}{V_{in}} = - \frac{\left(\frac{g_{min} g_{m1}}{C_1 C_2} \right)}{s^2 + s \left(\frac{1}{R_Q C_1} \right) + \frac{g_{m1} g_{m2}}{C_1 C_2}} = - \frac{\left(\frac{g_{min} g_{m1}}{C_1 C_2} \right)}{s^2 + s \left(\frac{\omega_o}{Q} \right) + \omega_o^2}$$


$$\omega_o = \sqrt{\frac{g_{m1} g_{m2}}{C_1 C_2}}$$

$$Q = \sqrt{\frac{C_1}{C_2} (g_{m1} g_{m2} R_Q^2)}$$


$$A_{V_{peak}} = g_{min} R_Q$$

Differential Second-Order Filter

[Mohieldin]

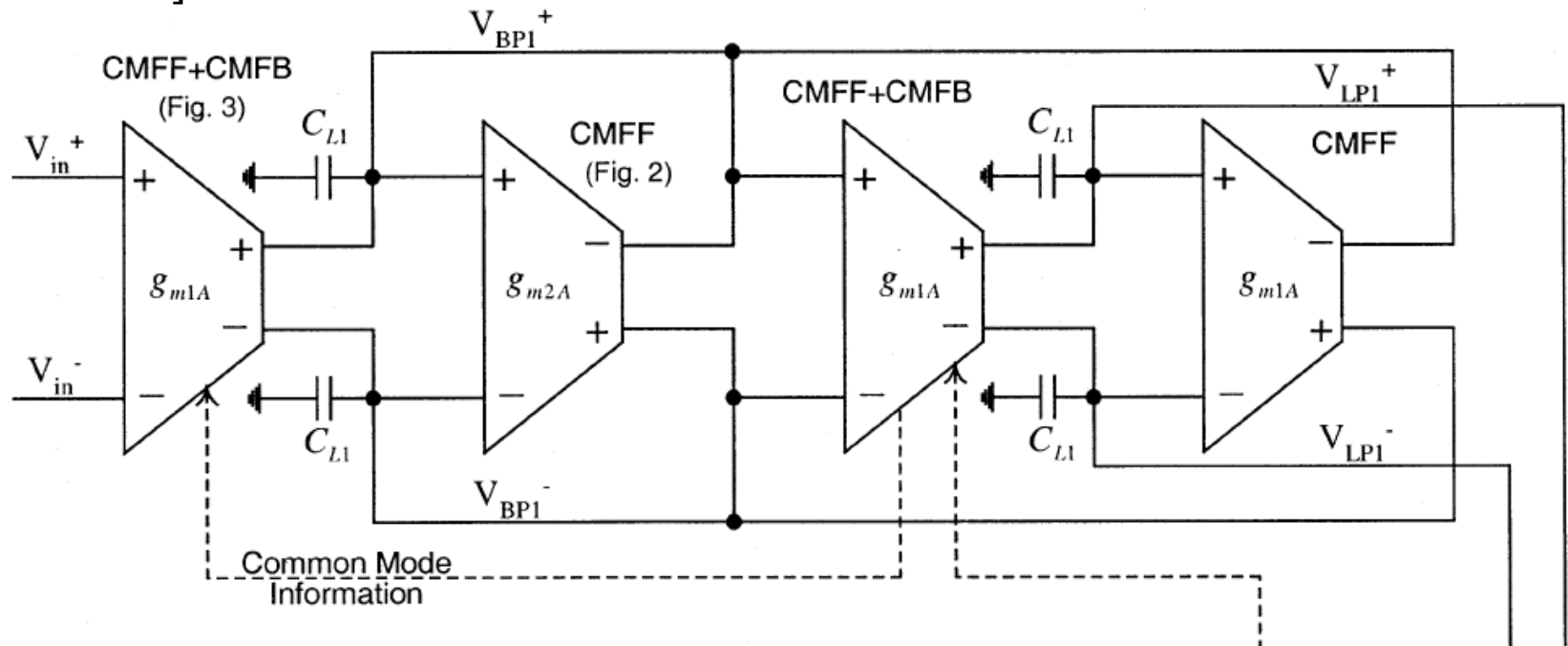

OTA Output Resistance Effects

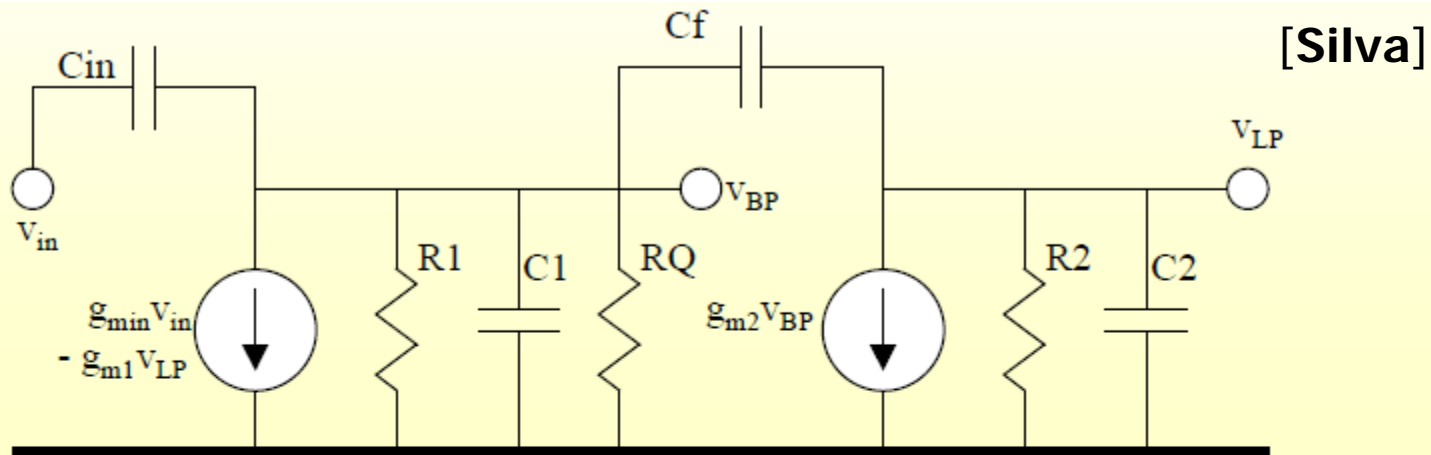

$$\omega_0 \cong \omega_{0ideal} \sqrt{1 + \frac{1}{Q_{ideal} A_V}}$$


CENTER FREQUENCY IS LITTLE SENSITIVE TO A_V

$$BW \cong BW_{ideal} \left(1 + 2 \frac{Q_{ideal}}{A_V} \right)$$

BW IS QUITE SENSITIVE TO A_V

$$A_V = g_{m1} R_1 \quad (R_1 = R_2 \text{ OTA output resistance})$$

OTA Non-Dominant Pole Effects

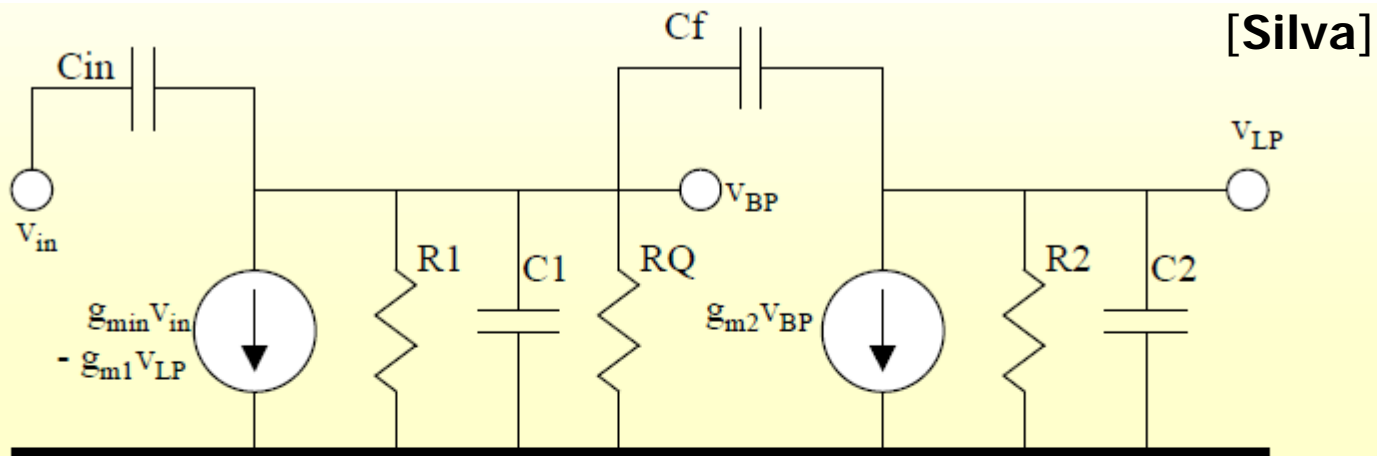

Single pole model:

$$g_m \approx \frac{g_{m0}}{1 + \frac{s}{\omega_{p1}}}$$

$$\omega_0 = \omega_{0ideal} \sqrt{\frac{1}{1 + \frac{2BW_{ideal}}{\omega_{p1}}}}$$

$$\text{error} \approx -\frac{BW_{ideal}}{\omega_{p1}}$$


Sensitive

$$BW \approx BW_{ideal} \left(1 - 2Q_{ideal} \frac{\omega_{0ideal}}{\omega_{p1}} \right)$$

$$\text{error} \approx -2Q_{ideal} \frac{\omega_{0ideal}}{\omega_{p1}}$$

Quite sensitive !!!

OTA Parasitic Capacitor Effects

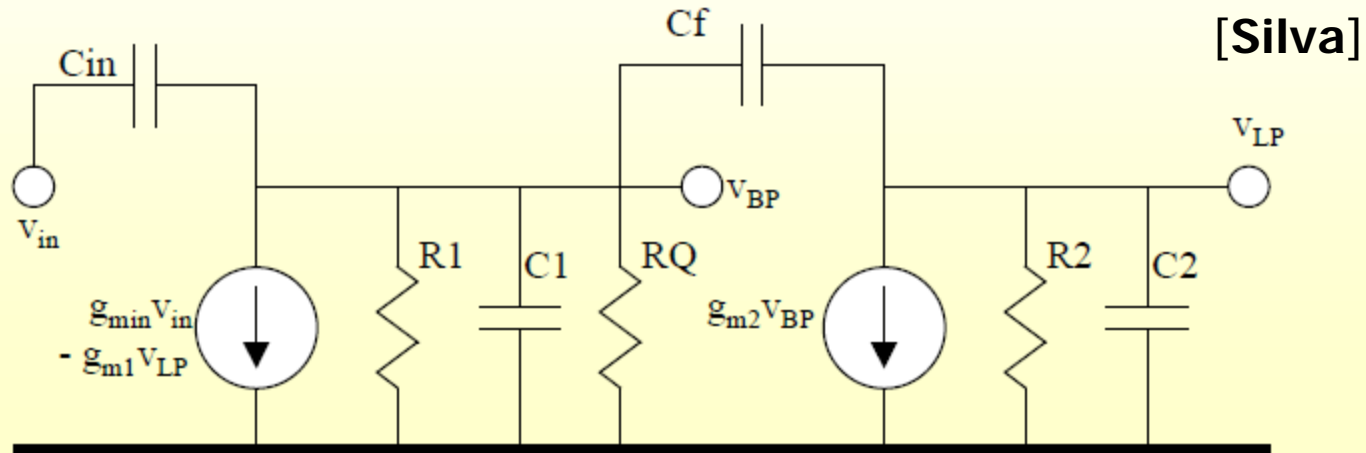

$$\omega_0 = \omega_{0ideal} \sqrt{\frac{1}{1 + \frac{C_f}{C_1} + \frac{C_f}{C_2} + \frac{C_{in}(C_2 + C_f)}{C_1 C_2}}}$$

Little sensitive

C_1 and C_2 are affected by the grounded parasitic capacitors (partially corrected by the automatic tuning system).


$$BW = BW_{ideal} \frac{1 + \left(1 + \frac{g_{m2} - g_{m1}}{g_1}\right) \frac{C_f}{C_2}}{1 + \frac{C_{in}}{C_1} + \frac{C_f}{C_1} + \frac{C_f}{C_2} \left(1 + \frac{C_{in}}{C_1}\right)}$$

Little sensitive

C_{in} introduces a high frequency zero.

Filters are little sensitive to miller effects !!!

OTA-C BPF Modeling Simulations

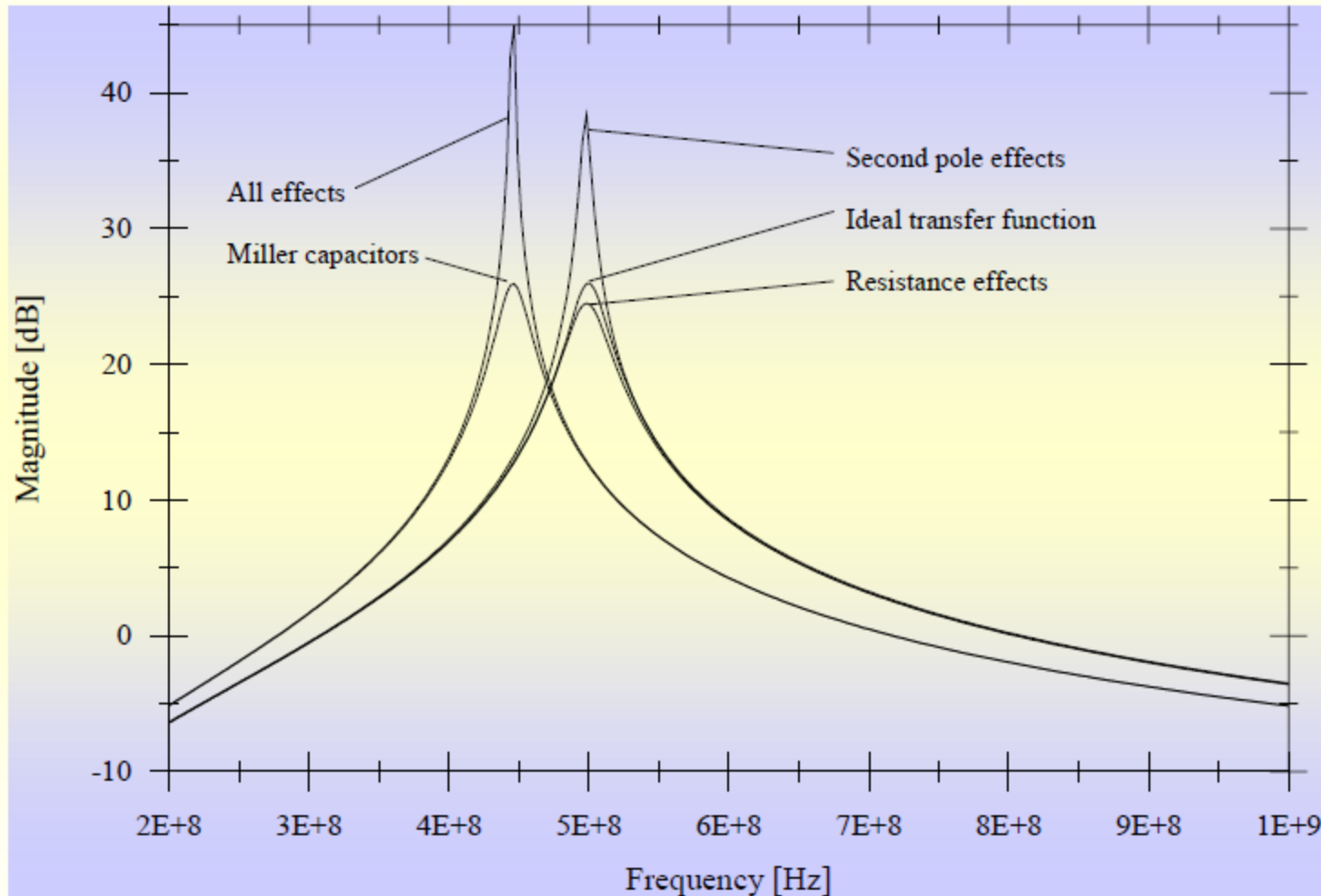


[Silva]

- Little sensitive to OTA output resistances
- Very sensitive to second poles
- Parasitic capacitors should be accounted in the ATS (matching)


4th-Order BPF

4th-Order Filter Example

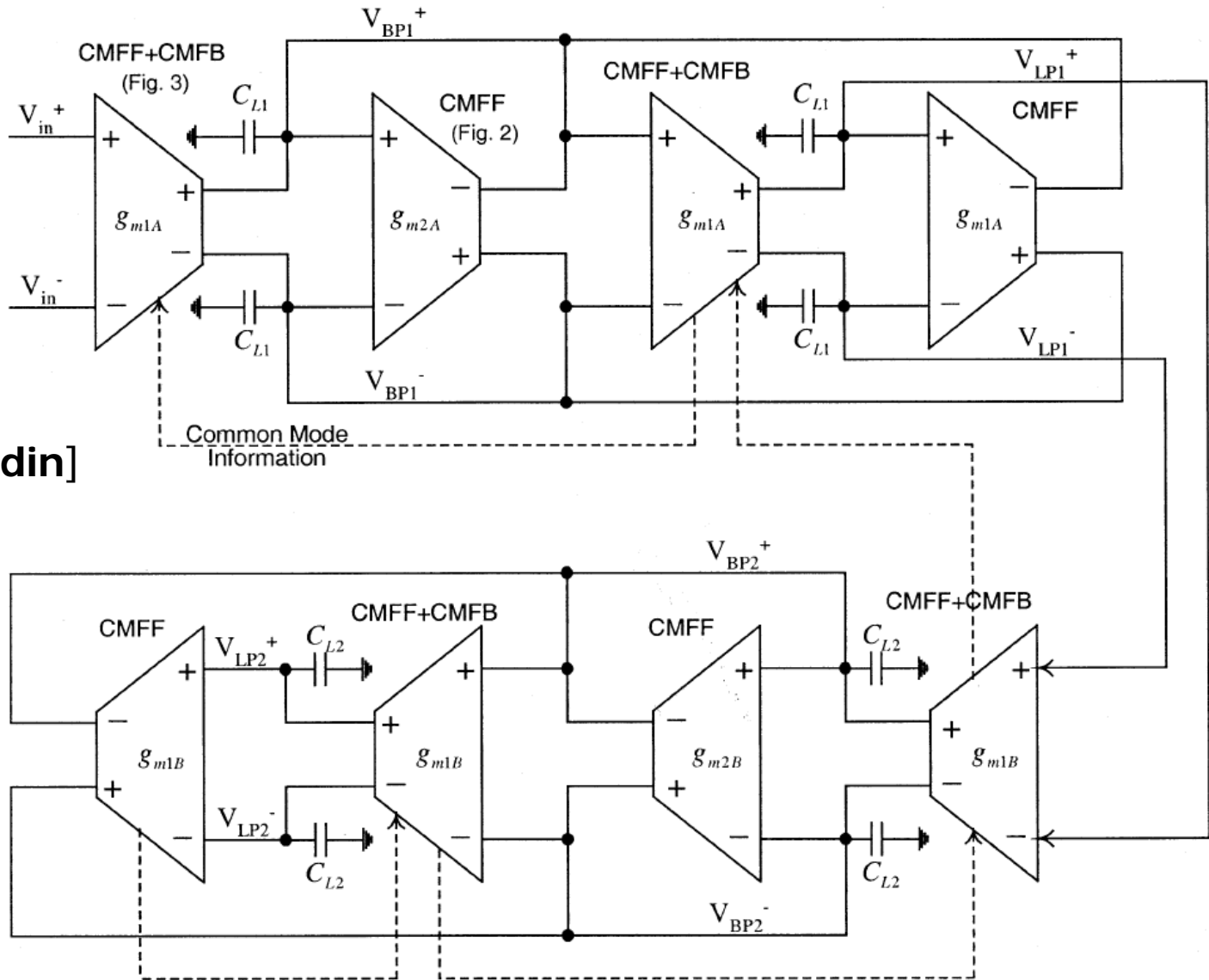

[Mohieldin]


Magnitude, Phase, and Group Delay

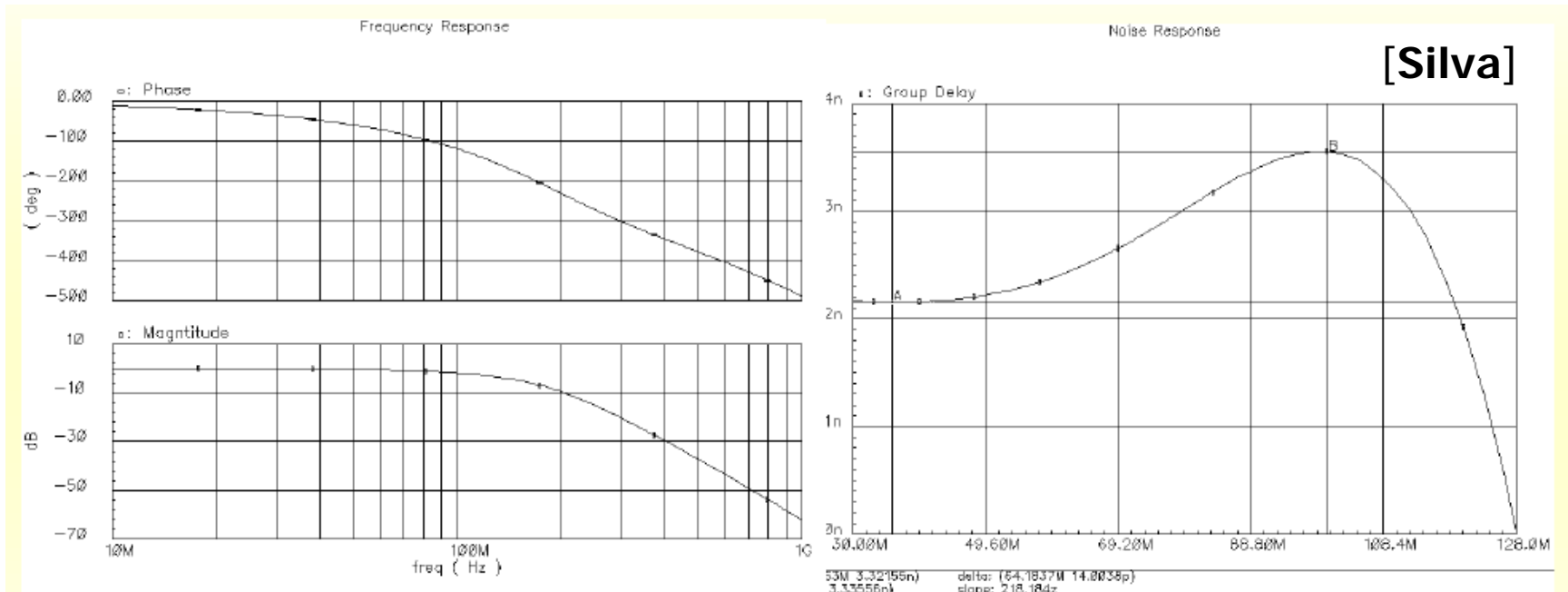

Magnitude and phase response for the 4th order filter

Group delay: Effects of the parasitic poles

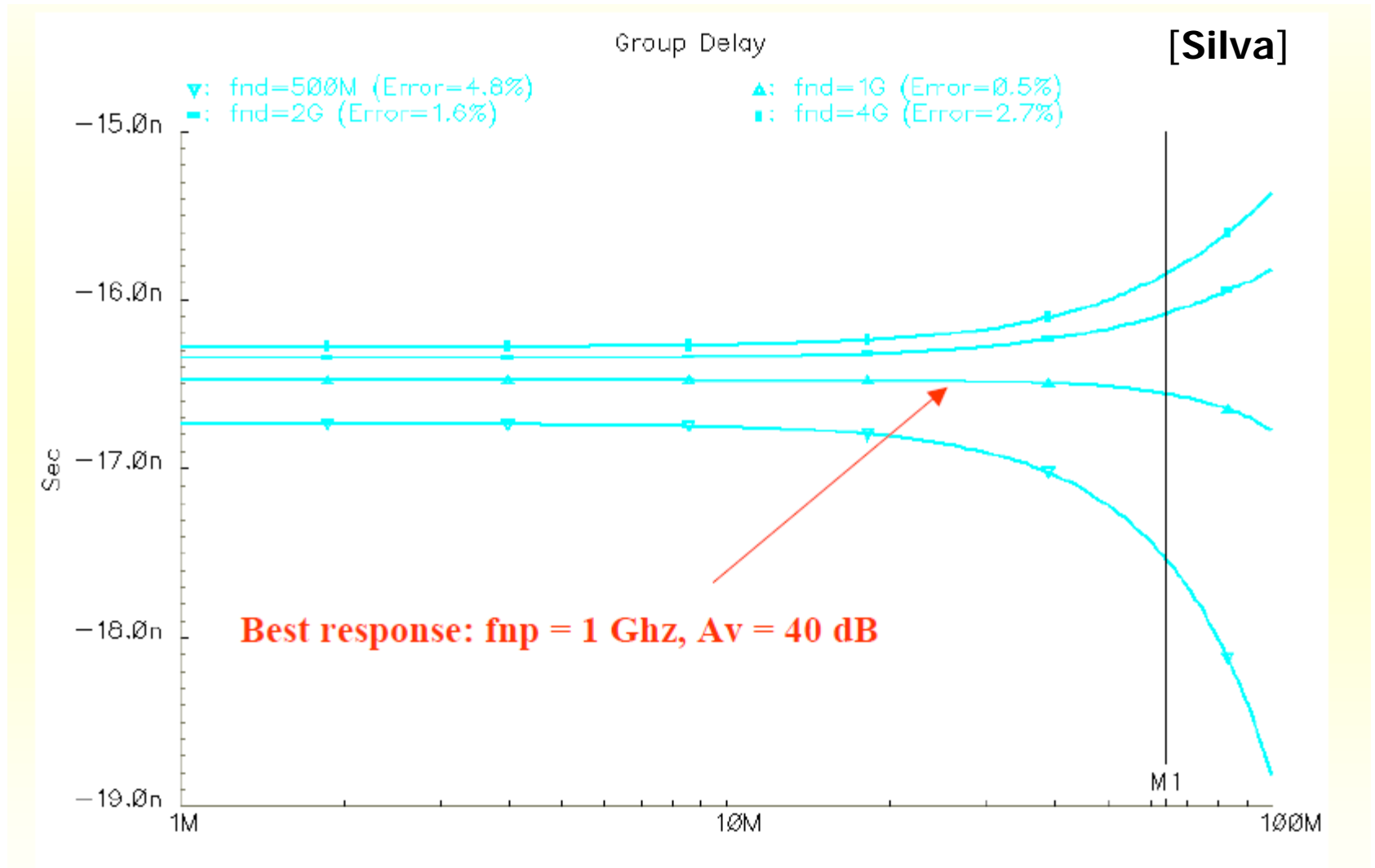Optimization: Non-Dominant Pole & DC Gain



Useful References

IEEE TRANSACTIONS ON CIRCUITS AND SYSTEMS—I: REGULAR PAPERS, VOL. 53, NO. 4, APRIL 2006

811

A CMOS 140-mW Fourth-Order Continuous-Time Low-Pass Filter Stabilized With a Class AB Common-Mode Feedback Operating at 550 MHz

Pankaj Pandey, Jose Silva-Martinez, and Xuemei Liu

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 38, NO. 4, APRIL 2003

663

Brief Papers

A Fully Balanced Pseudo-Differential OTA With Common-Mode Feedforward and Inherent Common-Mode Feedback Detector

Ahmed Nader Mohiaddin, *Student Member, IEEE*, Edgar Sánchez-Sinencio, *Fellow, IEEE*, and José Silva-Martínez, *Senior Member, IEEE*

- “Design of Analog Filters” by R. Schauman (Filters Textbook)

Next Time

- Analog Applications
 - Variable-Gain Amplifiers
 - Switch-Cap Filters, Broadband Amplifiers
- Bandgap Reference Circuits
- Distortion