

**Texas A&M University**  
**Department of Electrical and Computer Engineering**

**ECEN 689 – Optical Interconnects**

**Spring 2020**

**Exam #2**

**Instructor: Sam Palermo**

- Please write your name in the space provided below
- Please verify that there are 5 pages in your exam
- Good Luck!

Problem	Score	Max Score
1		50
2		50
<b>Total</b>		<b>100</b>

Name: SAM PALERMO

UIN: \_\_\_\_\_


**Table 4.1** Numerical relationship between  $Q$  and bit-error rate.

$Q$	$BER$	$Q$	$BER$
0.0	1/2	5.998	$10^{-9}$
3.090	$10^{-3}$	6.361	$10^{-10}$
3.719	$10^{-4}$	6.706	$10^{-11}$
4.265	$10^{-5}$	7.035	$10^{-12}$
4.753	$10^{-6}$	7.349	$10^{-13}$
5.199	$10^{-7}$	7.651	$10^{-14}$
5.612	$10^{-8}$	7.942	$10^{-15}$

**Table 4.6** Numerical values for  $BW_n$  and  $BW_{n2}$ .

$H(f)$	$BW_n$	$BW_{n2}$
1st-order low pass	$1.57 \cdot BW_{3dB}$	$\infty$
2nd-order low pass, crit. damped ( $Q = 0.500$ )	$1.22 \cdot BW_{3dB}$	$2.07 \cdot BW_{3dB}$
2nd-order low pass, Bessel ( $Q = 0.577$ )	$1.15 \cdot BW_{3dB}$	$1.78 \cdot BW_{3dB}$
2nd-order low pass, Butterworth ( $Q = 0.707$ )	$1.11 \cdot BW_{3dB}$	$1.49 \cdot BW_{3dB}$
Brick wall low pass	$1.00 \cdot BW_{3dB}$	$1.00 \cdot BW_{3dB}$
Rectangular (impulse response) filter	$0.500 \cdot B$	$\infty$
NRZ to full raised-cosine filter	$0.564 \cdot B$	$0.639 \cdot B$

**Key MOS Equations**

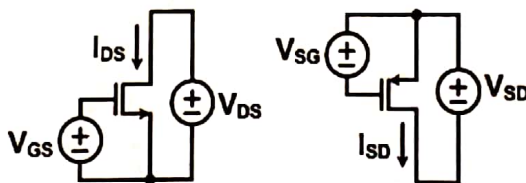

$$\text{Saturation: NMOS } I_{DS} = \frac{1}{2} K P_N \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$\text{Saturation: PMOS } I_{SD} = \frac{1}{2} K P_P \frac{W}{L} (V_{SG} - |V_{TP}|)^2$$

$$\text{Triode: NMOS } I_{DS} = K P_N \frac{W}{L} \left( V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$\text{Triode: PMOS } I_{SD} = K P_P \frac{W}{L} \left( V_{SG} - |V_{TP}| - \frac{V_{SD}}{2} \right) V_{SD}$$

$$\text{NMOS } g_m = \frac{\partial I_{DS}}{\partial V_{GS}}, \text{ PMOS } g_m = \frac{\partial I_{SD}}{\partial V_{SG}}$$

$$\text{NMOS } g_o = \frac{\partial I_{DS}}{\partial V_{DS}}, \text{ PMOS } g_o = \frac{\partial I_{SD}}{\partial V_{SD}}$$

Problem 1 (50 points)

A 25Gb/s optical receiver consists of a TIA followed by a comparator acting as the decision circuit.

- a) The TIA is designed to yield a 2<sup>nd</sup>-order low-pass Bessel response with BW<sub>3dB</sub>=18GHz. It has an input-noise spectrum described by

$$i_n^2(f) = \alpha_0 + \alpha_2 f^2 = 10^{-22} \frac{A^2}{Hz} + (5 \times 10^{-43} \frac{A^2}{Hz^3}) f^2.$$

What is the input rms noise current? Refer to the Page 2 table for relevant noise bandwidths.

$$\overline{i_n^2} = \alpha_0 B_{W1} + \frac{\alpha_2}{3} B_{W2}^3 = 10^{-22} \left( \frac{A^2}{Hz} \right) (1.15) (18GHz) + \frac{5 \times 10^{-43} \frac{A^2}{Hz^3}}{3} \left[ (1.78) (18GHz) \right]^3$$

$$\overline{i_n^2} = 7.55 \times 10^{-12} A^2 \Rightarrow i_{n,rms} = 2.75 \mu A$$

$$i_{n,amp}^{rms} = 2.75 \mu A$$

- b) Assuming an avalanche photodetector (APD) with R=0.8A/W, M=10, and F=3, what is the receiver sensitivity at a BER=10<sup>-12</sup>, including both amplifier and detector noise? You can assume an ideal extinction ratio and zero dark current. Also calculate the total low-level and high-level rms noise currents.

$$\overline{P}_{sens,APD} = \frac{1}{M} \frac{Q i_{n,amp}^{rms}}{R} + F \frac{Q^2 B_{W1}}{R} = \frac{7.035 (2.75 \mu A)}{10(0.8)} + \frac{3 (7.035)^2 (1.6 \times 10^{-19}) (1.15)}{0.8 (18GHz)}$$

$$= 3.03 \mu W = -25.2 dBm$$

$$\overline{P}_{sens} = -25.2 dBm$$

$$i_{n,0}^{rms} = i_{n,amp}^{rms} = 2.75 \mu A$$

$$i_{n,0}^{rms} = 2.75 \mu A$$

$$i_{n,1}^{rms} = \sqrt{FM^2 2q R \overline{P}_{sens} B_{W1} + (i_{n,amp}^{rms})^2} = \sqrt{3(10)^2 4(1.6 \times 10^{-19})(0.8)(3.03 \mu W)(1.15)(18GHz) + (2.75 \mu A)^2}$$

$$i_{n,1}^{rms} = 4.15 \mu A$$

- c) The APD also has a dark current of 100nA. What is the power penalty associated with this dark current. Here we can assume that the receiver noise is dominated by amplifier noise for this calculation.

$$PP = \sqrt{1 + \frac{FM^2 2q I_{DK} B_{W1}}{i_{n,amp}^2}} = \sqrt{1 + \frac{3(10)^2 (2)(1.6 \times 10^{-19})(100nA)(1.15)(18GHz)}{(2.75 \mu A)^2}}$$


$$PP = 1.013 = 0.056 dB$$

$$PP_{IDK} = 0.056 dB$$



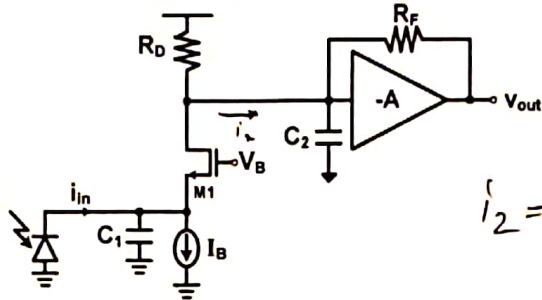Problem 2 (50 points)

For the TIA shown below, assume that all transistors are operating in saturation with  $r_o = \infty$ . Also assume that the voltage amplifier has infinite bandwidth, but finite open-loop gain  $A$ .



$$v_{out} = -i_2 R_F \left( \frac{A}{A+1} \right)$$

$$i_2 = i_{in} \left( \frac{R_D}{R_{in2} + R_D} \right) = \frac{i_{in} R_D}{\frac{R_F}{A+1} + R_D}$$

Obtain expressions for the following:

- a) Low-Frequency Transimpedance ( $v_{out}/i_{in}$ ). Note, don't neglect the impact of  $R_D$ .
- b) The TIA's two poles. Note, it's OK to neglect the transistor capacitors here.

$$v_{out} = -i_{in} \left( \frac{R_D R_F}{\frac{R_F}{A+1} + R_D} \right) \left( \frac{A}{A+1} \right)$$

$$R_T = \frac{v_{out}}{i_{in}} = \frac{-R_D R_F}{\frac{R_F}{A+1} + R_D} \left( \frac{A}{A+1} \right)$$

Input Pole:  $\omega_1 = \frac{g_{m1}}{C_1}$

Middle-Node Pole:  $\omega_2 = \frac{1}{C_2 (R_D || R_{in2})}$  where  $R_{in2} = \frac{R_F}{A+1}$

- c) Now assume that  $R_D$  is relatively large. What does the low-frequency transimpedance expression simplify to? What benefit does this topology offer over just using an input feedback TIA?

$$R_T \approx -R_F \left( \frac{A}{A+1} \right)$$

This is the same as an input feedback TIA, but we have the ability to set the input pole  $\omega/g_{m1}$  without impacting the TIA stability.